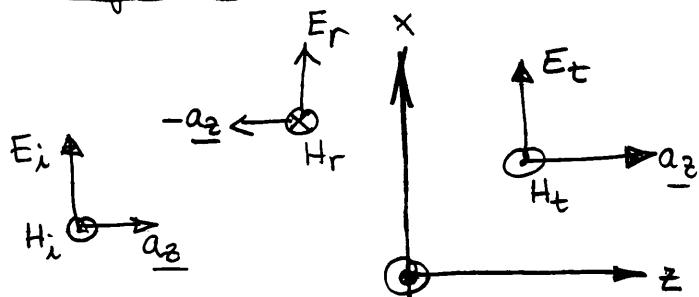


reflection of waves



$$\epsilon_1, \mu_1 \Rightarrow \alpha_1, \beta_1 \quad \epsilon_2, \mu_2 \Rightarrow \alpha_2, \beta_2, \gamma_2$$

we talk about polarization \rightarrow direction of E field.
This is E field parallel to interface.

If σ not given assume $\sigma = 0$

\Rightarrow lossless media $\hat{\eta} = \sqrt{\mu/\epsilon}$ in each media

incident

$$\hat{E}_i = E_i e^{-j\beta_1 z}$$

$$\hat{H}_i = \frac{E_i}{\eta_1} e^{-j\beta_1 z}$$

transmitted

$$\hat{E}_t = E_t e^{-j\beta_2 z}$$

$$\hat{H}_t = \frac{E_t}{\eta_2} e^{-j\beta_2 z}$$

reflected-

$$\hat{E}_r = E_r e^{+j\beta_1 z}$$

$$\hat{H}_r = -\frac{E_r}{\eta_1} e^{+j\beta_1 z}$$

what do we know about fields at interface

Tangential E is continuous

Tangential H

$$H_{1t} - H_{2t} = JS$$

\therefore tan E is continuous.

total field $z < 0$

$$E_i e^{-j\beta_1 z} + E_r e^{+j\beta_1 z}$$

$$\frac{E_i}{\eta_1} e^{-j\beta_1 z} - \frac{E_r}{\eta_1} e^{+j\beta_1 z}$$

total field $z > 0$

$$E_t e^{-j\beta_2 z}$$

$$\frac{E_t}{\eta_2} e^{-j\beta_2 z}$$

all continuous at $z=0$

$$E_i + E_r = E_t$$

$$\frac{E_i}{\eta_1} - \frac{E_r}{\eta_1} = \frac{E_t}{\eta_2}$$

E_i is usually known \Rightarrow find E_r and E_t



$$E_r = \frac{\gamma_2 - \gamma_1}{\gamma_2 + \gamma_1} E_i \quad \hat{r}$$

$$E_t = \frac{2\gamma_2}{\gamma_2 + \gamma_1} E_i \quad \hat{t}$$

$$1 + \hat{r} = \hat{t}$$


These
are
general
results
with
complex
impedances

Polarization

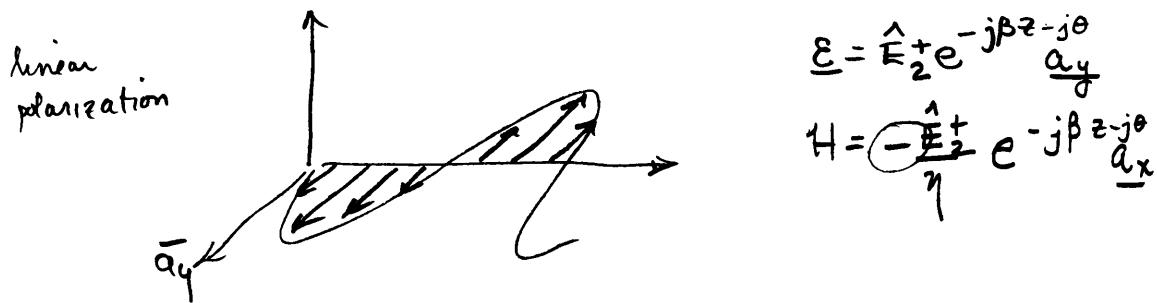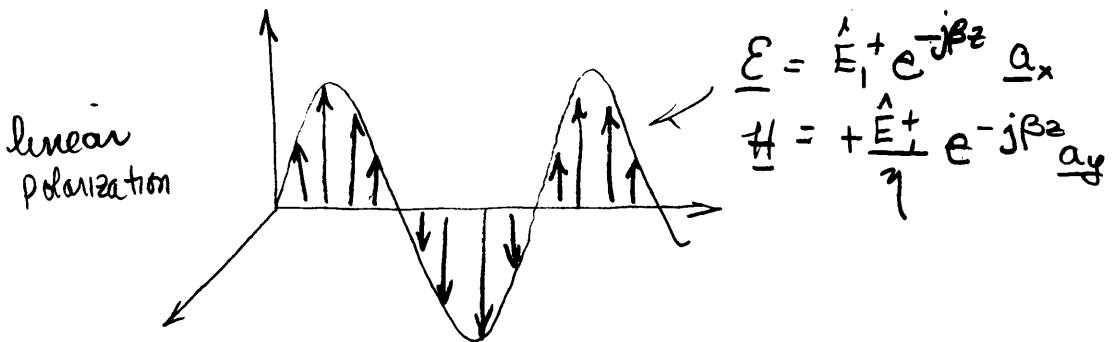

if both of these are added together
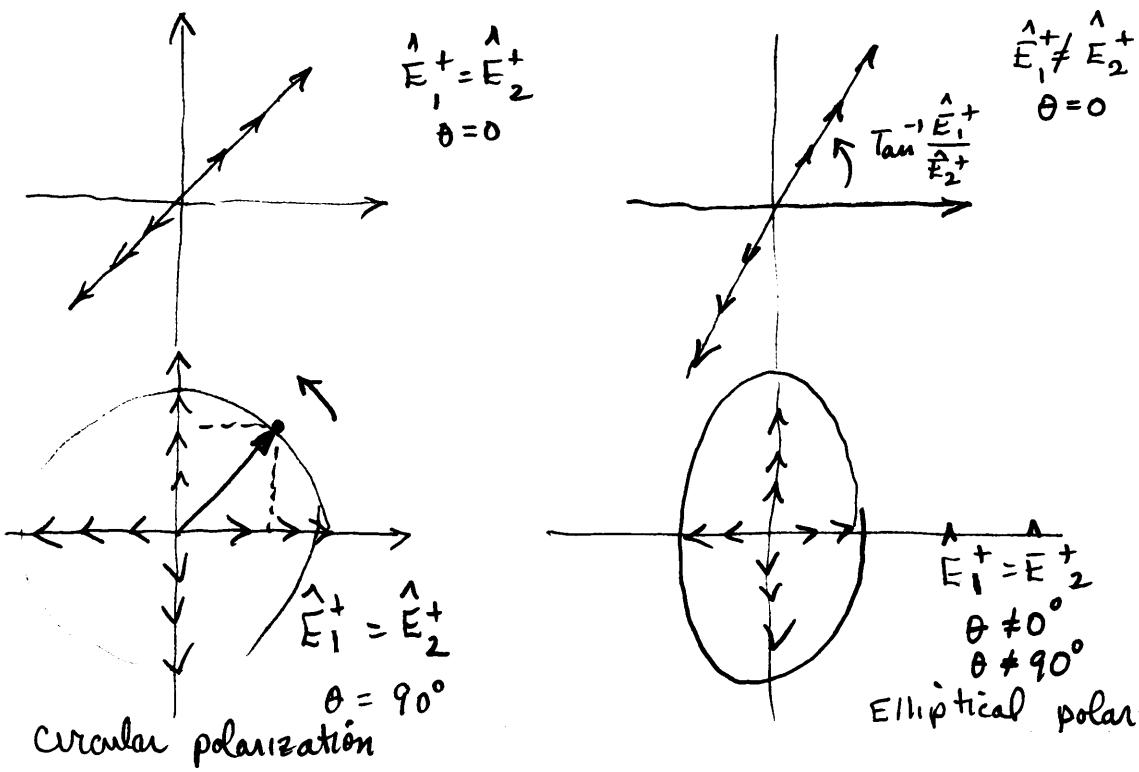
$$\underline{E}_{\text{tot}} = \hat{E}_1^+ e^{-j\beta z} \underline{a}_x + \hat{E}_2^+ e^{-j\beta z - j\theta} \underline{a}_y$$



reflection from a perfect conductor

what is $\hat{\eta}$ for a perfect conductor?

$$\hat{\eta} = \frac{j\omega \mu}{\sigma} = \frac{j\omega \mu}{\sigma + j\omega \epsilon}$$

as $\sigma \rightarrow \infty \quad \hat{\eta} \rightarrow 0$

here is error

This confirms that there are no fields in perfect conductors for

$$\begin{array}{l} \text{$\hat{\eta}_2$ in conductor} \\ \text{$\hat{\eta}_1$ in dielectric} \end{array} \quad \hat{R} = \frac{\hat{\eta}_2 - \hat{\eta}_1}{\hat{\eta}_2 + \hat{\eta}_1} \rightarrow -\frac{\hat{\eta}_1}{\hat{\eta}_1} = -1$$

$$\hat{T} = \frac{2\hat{\eta}_2}{\hat{\eta}_2 + \hat{\eta}_1} \rightarrow 0$$


All the wave is reflected producing a standing wave, i.e. a wave which does not move in space.

$$\hat{E}(z,t) = \underbrace{\hat{E}_i (e^{-j\beta_1 z} + \frac{E_r}{\hat{E}_i} e^{j\beta_1 z})}_{\text{total field}} \rightarrow \hat{E}_i (e^{-j\beta_1 z} - e^{-j\beta_1 z})$$

$$\hat{H}(z,t) = \frac{\hat{E}_i}{\hat{\eta}_1} \left(e^{-j\beta_1 z} - \frac{E_r}{\hat{E}_i} e^{j\beta_1 z} \right) \rightarrow \hat{H}_i (e^{-j\beta_1 z} + e^{j\beta_1 z})$$

$$\hat{E}_r(z,t) \rightarrow -2j \hat{E}_i \sin \beta_1 z$$
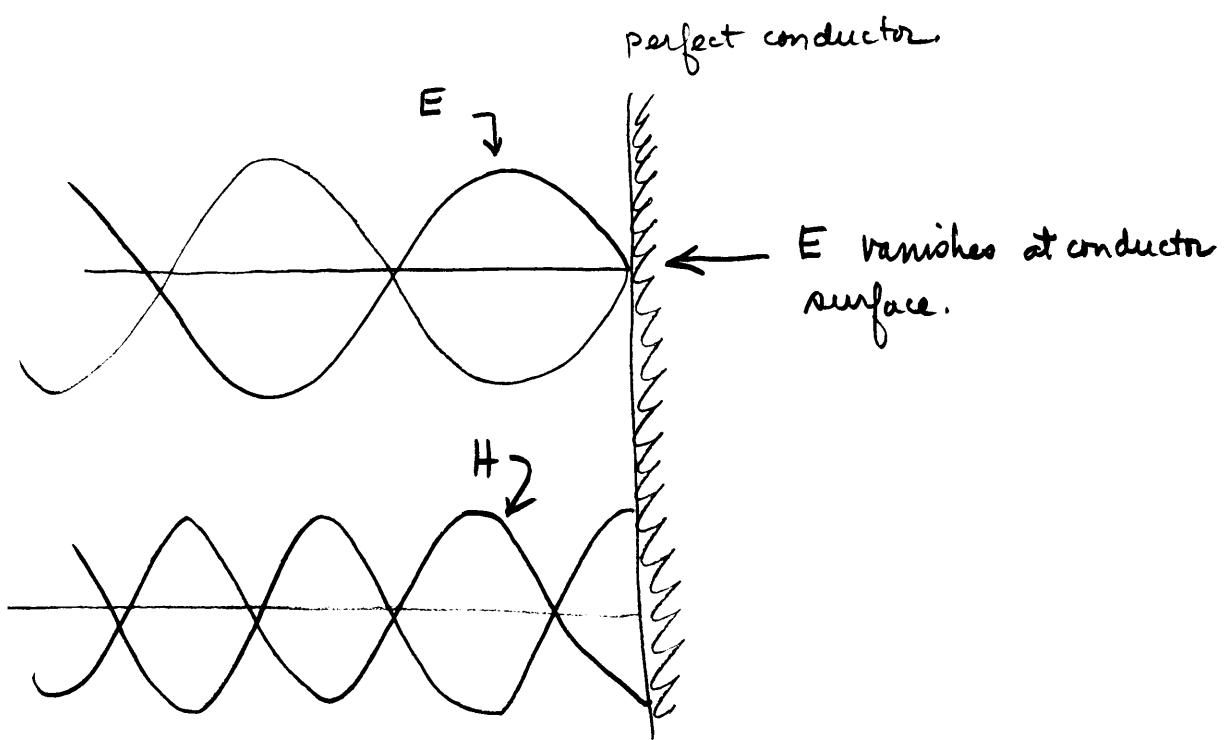
$$\hat{F}(z,t) \rightarrow 2 \frac{\hat{E}_i}{\hat{\eta}} \cos \beta_1 z$$



propagation in arbitrary direction

up to now we've assumed waves propagate along coordinate axes so description was simple.

complex Helmholtz wave equations:

$$\nabla^2 \hat{\underline{E}} = \gamma^2 \hat{\underline{E}}, \quad \nabla^2 \hat{\underline{H}} = \gamma^2 \hat{\underline{H}}$$

with solutions of form for a plane wave propagating in +z direction

$$\hat{\underline{E}} = \hat{\underline{E}}^+ e^{-\gamma z} + \hat{\underline{E}}^- e^{+\gamma z}$$

$$\hat{\underline{H}} = \hat{\underline{H}}^+ e^{-\gamma z} + \hat{\underline{H}}^- e^{+\gamma z}$$

In most general case (restrict attention to E field)

$$\underline{E} = \underline{E}^+ e^{-\gamma \underline{n} \cdot \underline{r}} + \underline{E}^- e^{+\gamma \underline{n} \cdot \underline{r}}$$


where $\underline{r} = x \underline{a_x} + y \underline{a_y} + z \underline{a_z}$ general position vector


$\underline{n} = n_x \underline{a_x} + n_y \underline{a_y} + n_z \underline{a_z}$ unit vector in direction of propagation

recall $\gamma = \alpha + j\beta$

For moment, pick $\alpha = 0$

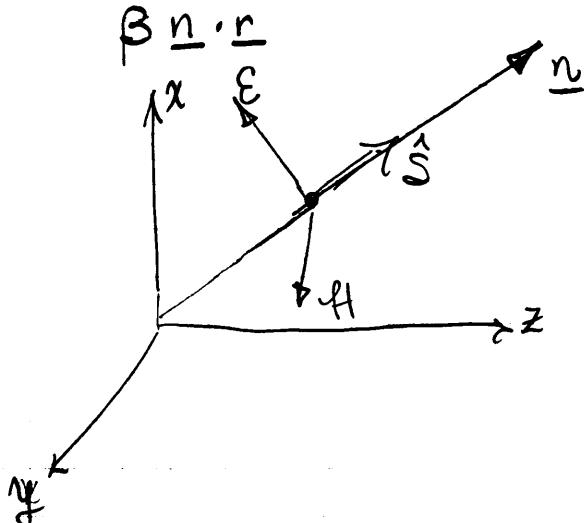surface of constant phase is described by



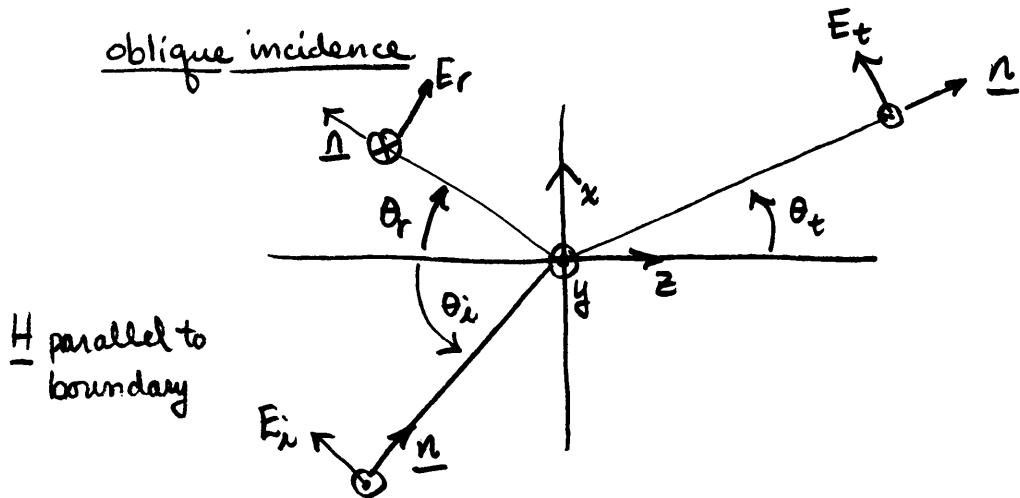

what is incident wave?

$$\hat{\underline{E}_i} = E_i (\underline{a_x} \cos \theta_i - \underline{a_z} \sin \theta_i) e^{-j\beta_1 (x \sin \theta_i + z \cos \theta_i)}$$

$$\begin{aligned} \underline{\beta} \underline{n} \cdot \underline{r} &= \beta_1 (\underline{a_x} \sin \theta_i + \underline{a_z} \cos \theta_i) \cdot (x \underline{a_x} + z \underline{a_z}) \\ &= \beta_1 x \sin \theta_i + \beta_1 z \cos \theta_i \end{aligned}$$

$$\hat{\underline{H}_i} = \underline{a_y} \frac{\underline{E}_i}{\eta_1} e^{-j\beta_1 (x \sin \theta_i + z \cos \theta_i)}$$

note that $\hat{\underline{E}_i}$ had to be decomposed, \underline{H} does not since it lies along a principal axis

what is reflected wave?

$$\hat{\underline{E}_r} = \hat{\underline{E}_r} (\underline{a_x} \cos \theta_r + \underline{a_z} \sin \theta_r) e^{-j\beta_1 (x \sin \theta_r - z \cos \theta_r)}$$

$$\hat{\underline{H}_r} = -\frac{\hat{\underline{E}_r}}{\eta_1} \underline{a_y} e^{-j\beta_1 (x \sin \theta_r - z \cos \theta_r)}$$

what is transmuted wave? looks essentially like incident wave

$$\hat{E}_t = \hat{E}_t (\underline{a_x} \cos \theta_t - \underline{a_z} \sin \theta_t) e^{-j\beta_2 (x \sin \theta_t + z \cos \theta_t)}$$

$$\hat{H}_t = \frac{\hat{E}_t}{\eta_2} \underline{a_y} e^{-j\beta_2 (x \sin \theta_t + z \cos \theta_t)}$$

what happens at $z=0$.

$$E_i, H_i$$

$$E_r, H_r$$

$$E_t, H_t$$

(E)

$$E_i (\underline{a_x} \cos \theta_i - \underline{a_z} \sin \theta_i) e^{-j\beta_1 x \sin \theta_i} E_r (\underline{a_x} \cos \theta_r + \underline{a_z} \sin \theta_r) e^{-j\beta_1 x \sin \theta_r}$$

$$E_t (\underline{a_x} \cos \theta_t - \underline{a_z} \sin \theta_t) \\ \curvearrowright e^{-j\beta_2 x \sin \theta_t}$$

(H)

$$\frac{E_i}{\eta_1} \underline{a_y} e^{-j\beta_1 x \sin \theta_i}$$

$$-\frac{E_r}{\eta_1} \underline{a_y} e^{-j\beta_1 x \sin \theta_r}$$

$$\frac{E_t}{\eta_2} e^{-j\beta_2 x \sin \theta_t}$$

what do we equate?

at $z=0$ tangential components must be continuous

$$E_{\text{tan}}: E_i \cos \theta_i e^{-j\beta_1 x \sin \theta_i} + E_r \cos \theta_r e^{-j\beta_1 x \sin \theta_r} = E_t \cos \theta_t e^{-j\beta_2 x \sin \theta_t}$$

$$H_{\text{tan}}: \frac{E_i}{\eta_1} e^{-j\beta_1 x \sin \theta_i} - \frac{E_r}{\eta_1} e^{-j\beta_1 x \sin \theta_r} = \frac{E_t}{\eta_2} e^{-j\beta_2 x \sin \theta_t}$$

Since this must be true for all x .

$$\beta_1 x \sin \theta_i = \beta_2 x \sin \theta_t = \beta_2 x \sin \theta_t$$

$$\text{or } \sin \theta_i = \sin \theta_r \Rightarrow \theta_i = \theta_r$$

$$\frac{\sin \theta_t}{\sin \theta_i} = \frac{\beta_2}{\beta_1}$$

Snell's Law

If exponents are equal :

$$E_i \cos \theta_i + E_r \cos \theta_r = E_t \cos \theta_t$$

$$\frac{E_i}{\eta_1} - \frac{E_r}{\eta_1} = \frac{E_t}{\eta_2}$$

Solutions are


Fresnel Equations $\Gamma_{II} = \frac{E_r}{E_i} = \frac{\hat{\eta}_2 \cos \theta_t - \hat{\eta}_1 \cos \theta_i}{\hat{\eta}_2 \cos \theta_t + \hat{\eta}_1 \cos \theta_i}$

$$T_{II} = \frac{E_t}{E_i} = \frac{2 \hat{\eta}_2 \cos \theta_i}{\hat{\eta}_2 \cos \theta_t + \hat{\eta}_1 \cos \theta_i}$$

for E_{II} to interface (i.e. H perpendicular)


$$\Gamma_T = \frac{\hat{\eta}_2 \cos \theta_i - \hat{\eta}_1 \cos \theta_t}{\hat{\eta}_2 \cos \theta_i + \hat{\eta}_1 \cos \theta_t}$$
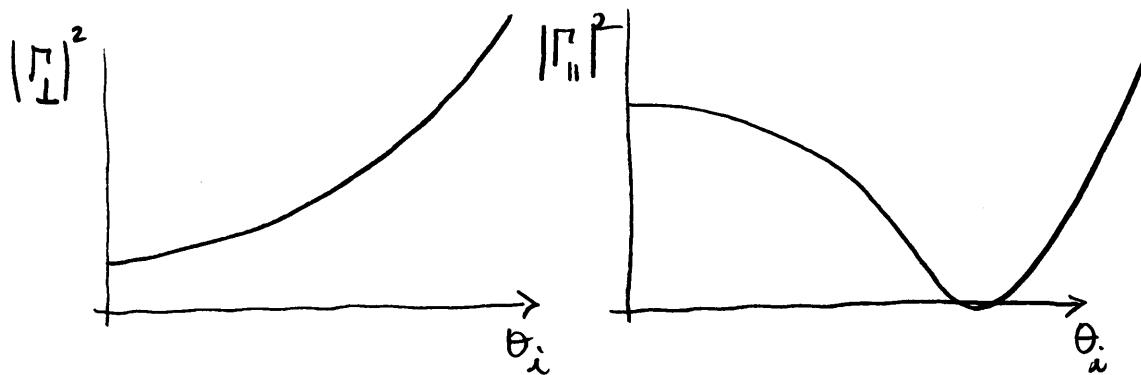
$$T_T = \frac{2 \hat{\eta}_2 \cos \theta_i}{\hat{\eta}_2 \cos \theta_i + \hat{\eta}_1 \cos \theta_t}$$



transmission lines

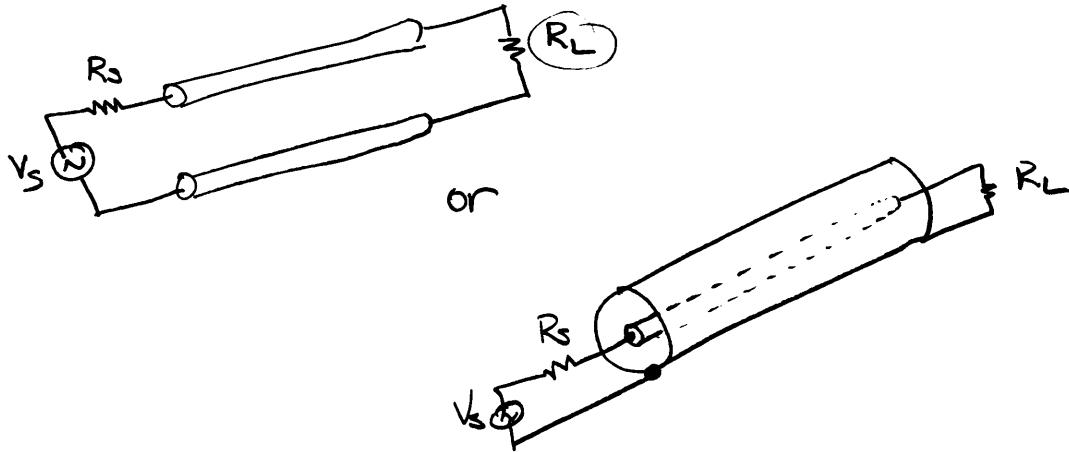guide propagation of energy from one point to another
typically two conductors (infinitely long at first)





These are uniform, i.e. cross-section is uniform
so static E & H field problems we have already solved!

Maxwell's Equations:

$$\oint \underline{E} \cdot d\underline{l} = -\mu \frac{\partial}{\partial t} \int \underline{H} \cdot d\underline{s}$$

$$\oint \underline{H} \cdot d\underline{l} = \int \underline{g} \cdot d\underline{s} + \frac{\partial}{\partial t} \int \underline{E} \cdot d\underline{s}$$

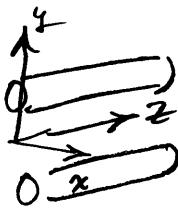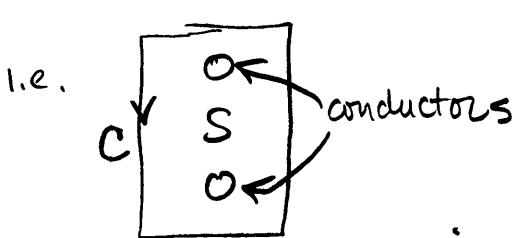for a transmission line pick contour C in transverse direction



call these x, y coordinates

Then: $\oint (\underline{E}_x dx + \underline{E}_y dy) = -\mu \frac{\partial}{\partial t} \int H_z dx dy$

$$\oint (H_x dx + H_y dy) = \int g_z dx dy + \epsilon \frac{\partial}{\partial t} \int E_z dx dy$$

but $H_z = E_z = 0$ transverse components only
for plane waves.

since $d\underline{s} = \underline{a}_z dx dy$

this means

$$\oint \underline{E} \cdot d\underline{l} = 0$$


$$\oint \underline{H} \cdot d\underline{l} = \int \underline{J}_z \cdot d\underline{s}$$

These are the static solutions!

This means that

- ① electric field is conservative even though field is time varying
- ② per unit length inductance is constant
- ③ per unit length capacitance is constant

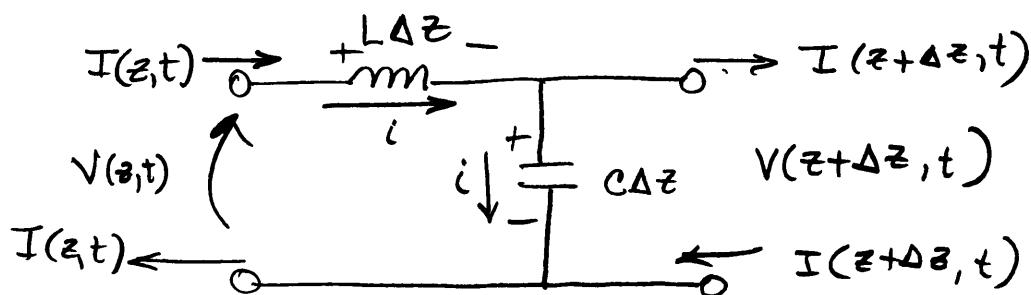What we will do now is see if these ^{lumped} constant per unit length parameters can lead to plane waves.



I can always stick these together to make a long line.

circuits:

voltage drop across inductor

$$V(z, t) - V(z + \Delta z, t) = L \Delta z \frac{\partial I(z, t)}{\partial t}$$

$$\therefore \frac{V(z + \Delta z, t) - V(z, t)}{\Delta z} = -L \frac{\partial I(z, t)}{\partial t}$$

voltage across capacitor $i = C \frac{dV}{dt} \propto V = \int i dt$

$$I(z, t) - I(z + \Delta z, t) = C \frac{\partial V(z + \Delta z, t)}{\partial t}$$

from ①

$$\frac{I(z + \Delta z, t) - I(z, t)}{\Delta z} = -C \frac{\partial}{\partial t} \left\{ V(z, t) - L \Delta z \frac{\partial I(z, t)}{\partial t} \right\}$$

$$\frac{I(z + \Delta z, t) - I(z, t)}{\Delta z} = -C \frac{\partial V(z, t)}{\partial t} + LC \Delta z \frac{\partial^2 I(z, t)}{\partial t^2}$$

$$\frac{\partial I(z, t)}{\partial z} = -C \frac{\partial V(z, t)}{\partial t}$$

going the other way we get,

$$\frac{\partial V(z, t)}{\partial z} = -L \frac{\partial I(z, t)}{\partial t}$$

differential each again to get

$$\frac{\partial^2 I}{\partial z^2} = -C \frac{\partial}{\partial t} \frac{\partial}{\partial z} V(z, t)$$

$$\frac{\partial^2 V}{\partial z^2} = -L \frac{\partial}{\partial t} \frac{\partial}{\partial z} I(z, t)$$

} interchange order

$$\frac{\partial}{\partial z} \frac{\partial}{\partial t}$$

what do we get

$$\left. \begin{aligned} \frac{\partial^2 I}{\partial z^2} &= LC \frac{\partial^2 I}{\partial t^2} \\ \frac{\partial^2 V}{\partial z^2} &= LC \frac{\partial^2 V}{\partial t^2} \end{aligned} \right\} \begin{aligned} \text{define } v &= \frac{1}{\sqrt{LC}} \\ \text{look just like} \\ \text{Helmholtz equations} \end{aligned}$$

Solutions:

$$V(z,t) = V^+(z-ut) + V^-(z+ut)$$


$$I(z,t) = I^+(z-ut) + I^-(z+ut)$$

just as for traveling ^(plane)waves. V and I are related by impedance.

$$I^+(z-ut) = \frac{V^+(z-ut)}{R_c}$$

$$I^-(z+ut) = -\frac{V^-(z+ut)}{R_c}$$

$$R_c = \sqrt{\frac{L}{C}}$$

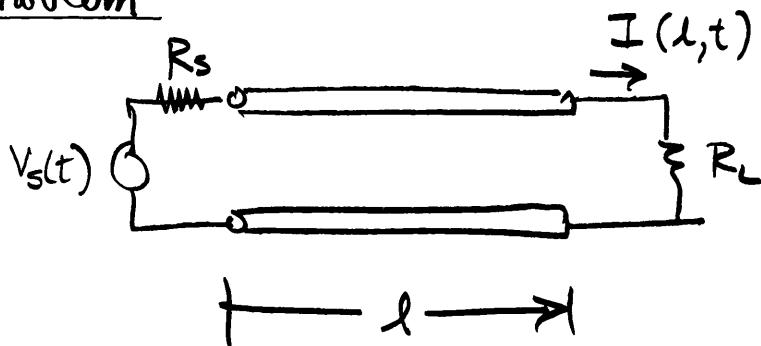problemwhat is $V(l,t)$?

$$V(l,t) = I(l,t) R_L \quad \left. \right\} \text{at the load}$$

use time
instead of
 t
as
variable of
interest

$$\begin{aligned} V^+(t - \frac{l}{u}) &= R_c I^+(t - \frac{l}{u}) \\ V^-(t + \frac{l}{u}) &= -R_c I^-(t + \frac{l}{u}) \end{aligned} \quad \left. \right\} \text{on the line}$$

transmission line

we must sum these up and see what meets B.C.'s.

$$\begin{aligned} V(l,t) &= V^+(t - \frac{l}{u}) + V^-(t + \frac{l}{u}) \\ &= V^+(t - \frac{l}{u}) \left[1 + R_L \right] \end{aligned}$$


where $R_L = \frac{V^-(t + \frac{l}{u})}{V^+(t - \frac{l}{u})}$ reflected
incident

$$\begin{aligned} I(l,t) &= I^+(t - \frac{l}{u}) + I^-(t + \frac{l}{u}) \\ &= \frac{V^+(t - \frac{l}{u})}{R_c} - \frac{V^-(t + \frac{l}{u})}{R_c} \\ &= \frac{1}{R_c} V^+(t - \frac{l}{u}) \left[1 - R_L \right] \end{aligned}$$

12B

A transmission line is charged to $V_0 = +100V$ and left with both ends open. The line has a distributed capacitance of 88.6 pF/m and a distributed inductance of $2.22 \times 10^{-7} \text{ H/m}$. The line is 3 meters long.

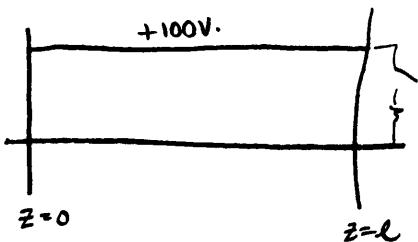- if at time $t=0$ a 33Ω resistor is connected across one end of the line, how long is the pulse that is applied to the load and what is $V_L(t)$?
- If the resistor is 25Ω , sketch $V_L(t)$



$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{2.22 \times 10^{-7}}{88.6 \times 10^{-12}}} = \sqrt{25050} \approx 50 \Omega$$

$$u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2.22 \times 10^{-7})(88.6 \times 10^{-12})}} = 2.25 \times 10^8 \text{ m/sec.}$$

$$V(z,t) = V^+(z+ut) + V^-(z-ut)$$

$$I(z,t) = \frac{V^+(z-ut)}{Z_0} - \frac{V^-(z+ut)}{Z_0}$$

$$T = \frac{l}{u} = \frac{3}{2.25 \times 10^8} = 1.33 \times 10^{-8} \text{ sec}$$

for a steady line with no loading

$$V(0,t) = V^+ + V^- = 100$$


$$I(0,t) = \frac{V^+}{50} - \frac{V^-}{50} = 0$$

$$V^+ + V^- = 100$$

$$V^+ - V^- = 0$$

$$\therefore V^+ = V^- = 50$$

Example : short pulse on a line tough

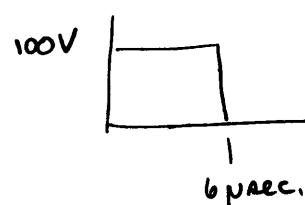



$$C = 100 \text{ pF/m}$$

$$L = 0.25 \text{ } \mu\text{H/m}$$


$$u = \frac{1}{\sqrt{LC}} = 200 \times 10^6 \text{ m/sec}$$

$$Z = \sqrt{\frac{L}{C}} = 50 \Omega$$

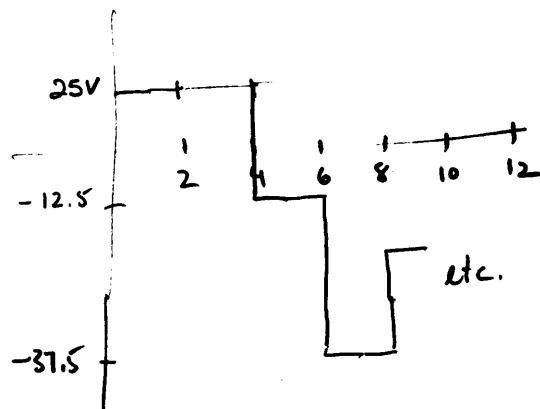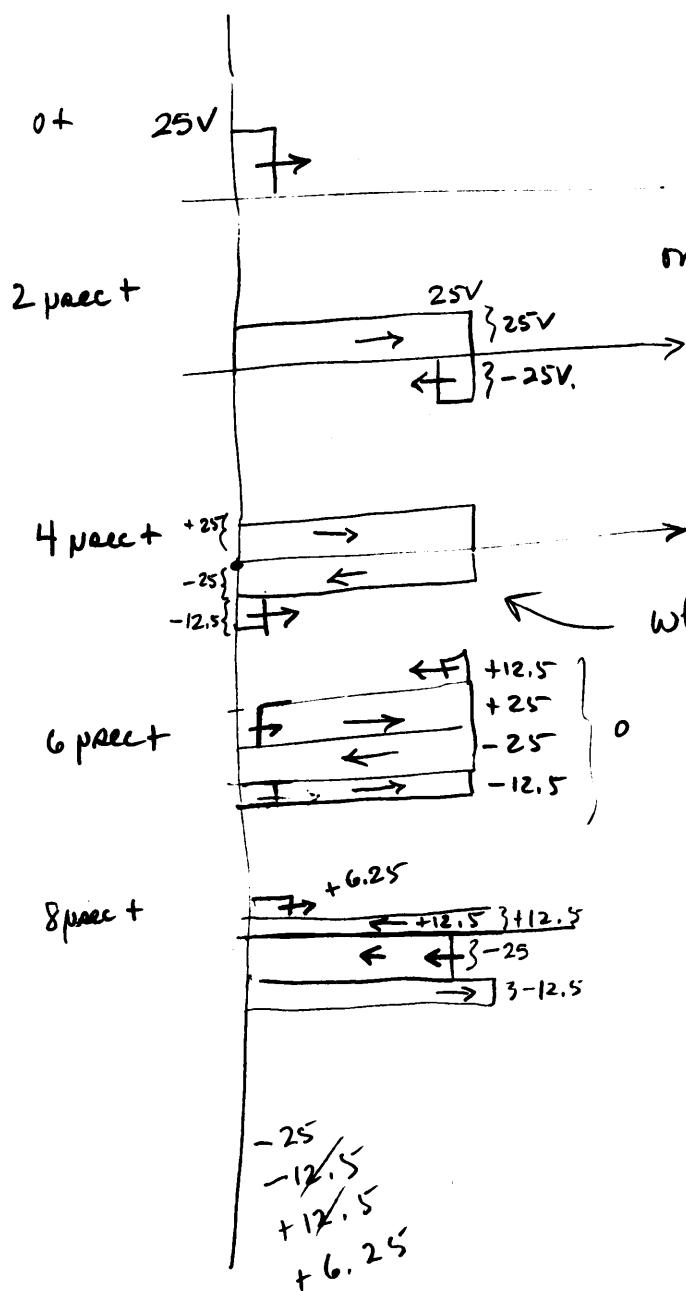
$$T = \frac{400 \text{ m}}{200 \times 10^6 \text{ m/sec}} = 2 \mu\text{sec}$$



summary of transmission line results

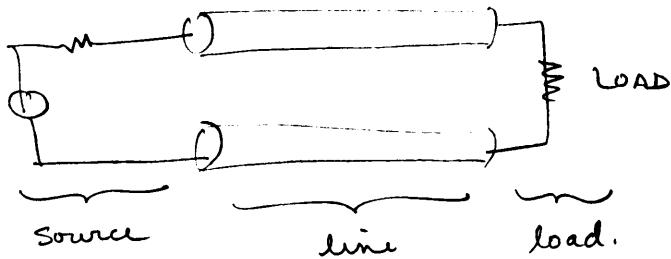

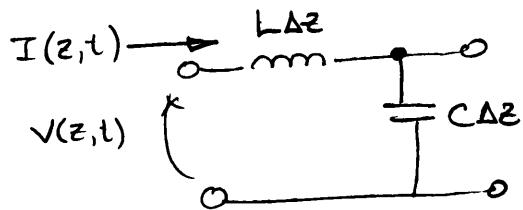has inductance & capacitance per unit length,



transmission line equations:

$$\frac{\partial^2 V}{\partial z^2} = \frac{1}{u^2} \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial z^2} = \frac{1}{u^2} \frac{\partial^2 I}{\partial t^2}$$

$$u = \frac{1}{\sqrt{LC}}$$

from before solutions look like

$$V(z,t) = V^+(z - ut) + V^-(z + ut)$$

$$I(z,t) = \underbrace{I^+(z - ut)}_{\substack{\text{total} \\ \text{wave}}} + \underbrace{I^-(z + ut)}_{\substack{\text{wave in} \\ +z \text{ direction}}} + \underbrace{I^-}_{\substack{\text{wave in} \\ -z \text{ direction}}}$$

reflection coefficient

$$V(z,t) = V^+ \left(1 + \frac{V^-}{V^+} \right) = V^+ \left(1 + R_V \right)$$

$$I(z,t) = I^+ \left(1 + \frac{I^-}{I^+} \right) = I^+ \left(1 + R_I \right)$$

relationship between voltage & current is resistance, or ^{opposite directions} impedance

$$I(z,t) = \frac{V^+(z - ut) - V^-(z + ut)}{Z_0} = \frac{V^+}{Z_0} \left(1 - \frac{V^-}{V^+} \right)$$

$$= \frac{V^+}{Z_0} (1 - R_V)$$

$$\xrightarrow{\text{at load}} V(l,t) = Z_L I(l,t)$$

$$V(l,t) = V^+ (1 + \Gamma_L^{(v)}) \quad \xrightarrow{\frac{V^+}{Z_0} (1 - \Gamma_L^{(v)})}$$

$$\cancel{V^+ (1 + \Gamma_L^{(v)})} = \frac{Z_L}{Z_0} \cancel{V^+ (1 - \Gamma_L^{(v)})}$$


Solving for $\Gamma_L^{(v)}$

$$\Gamma_L^{(v)} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \left\{ \text{just like } \Gamma_L = \frac{\hat{\eta}_2 - \hat{\eta}_1}{\hat{\eta}_2 + \hat{\eta}_1} \right.$$





$$\Gamma_L(I) = -\Gamma_L^{(v)} \quad \left. \right\}$$

Example: long pulse on shorted line





$$\leftarrow l = uT \rightarrow$$

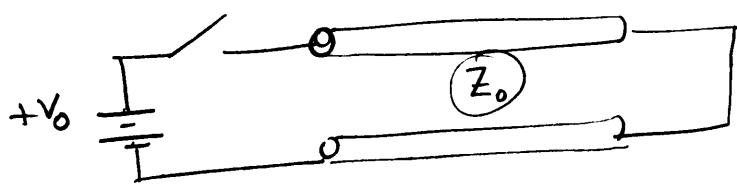


how about I

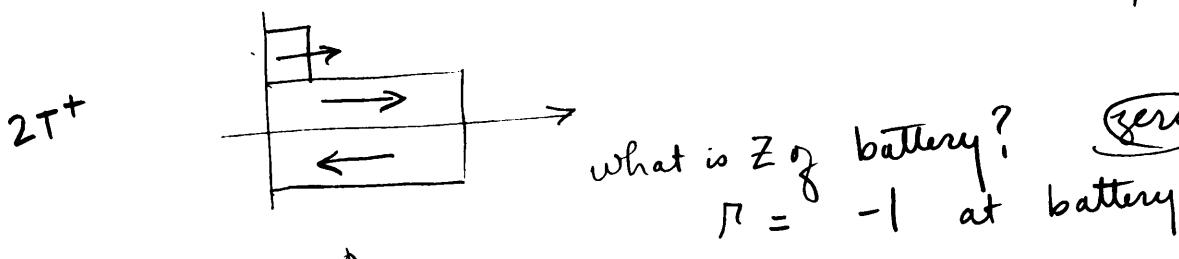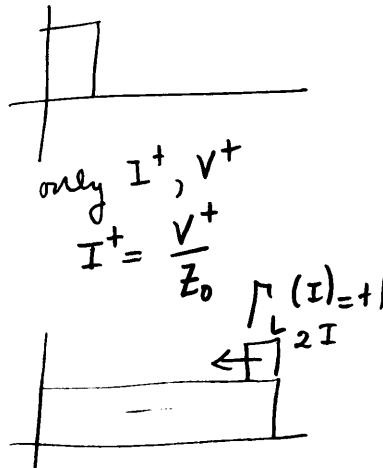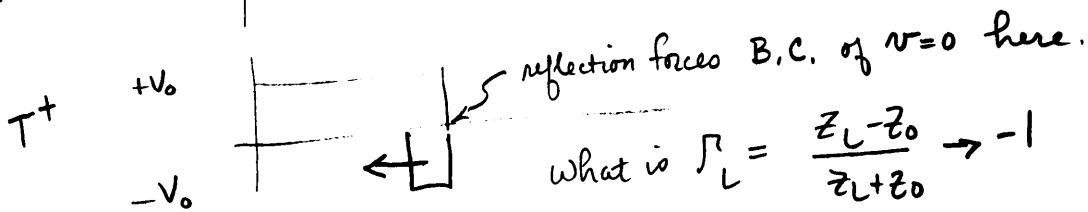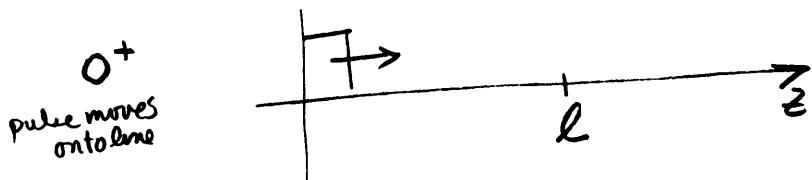

this just goes back and forth

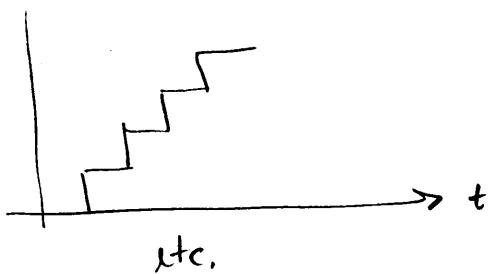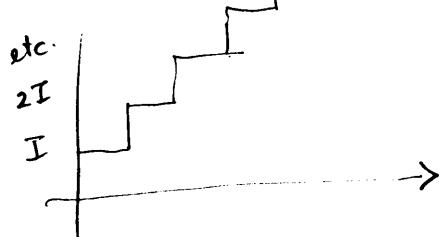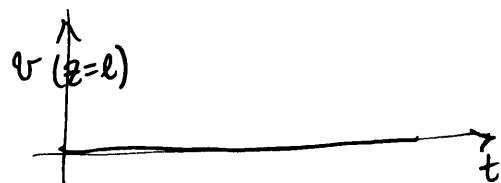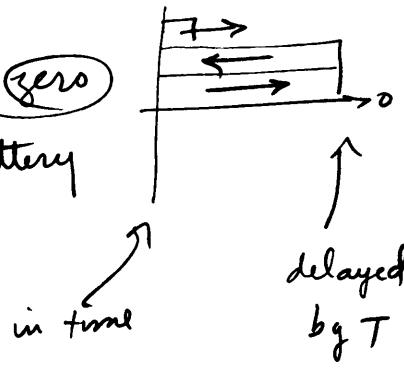

long pulse w/ numbers.

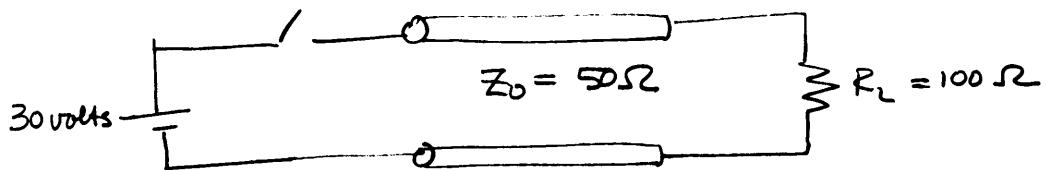

$$v = 200 \text{ m/sec.}$$








$$L = 400 \text{ meters}$$



$$T = \frac{400 \text{ m}}{200 \text{ m/sec}} = 2 \text{ sec long}$$

what do we expect $\rightarrow 30$ volts at load

$$i = \frac{E}{R} = \frac{30}{100} = 0.3 \text{ Amps.}$$

trace pulse...

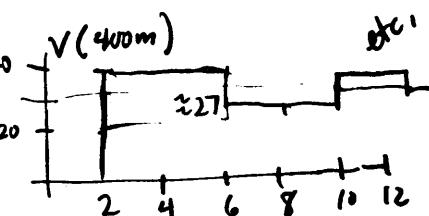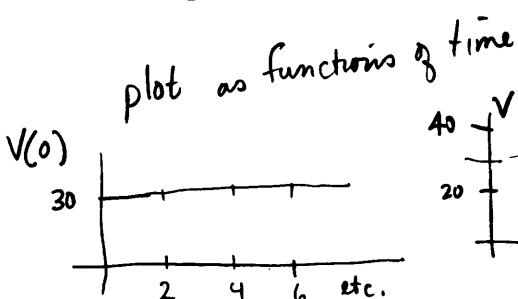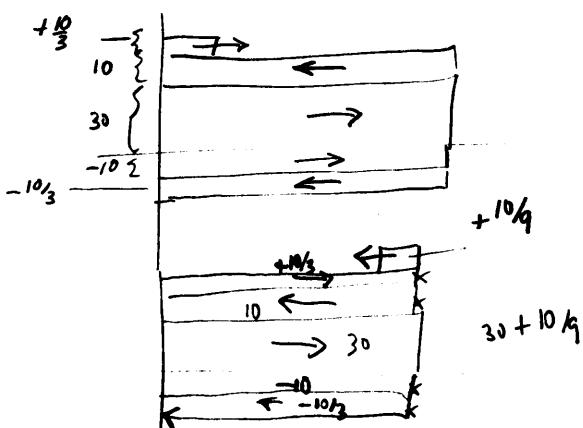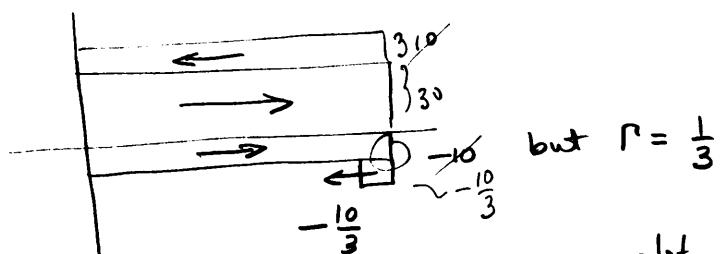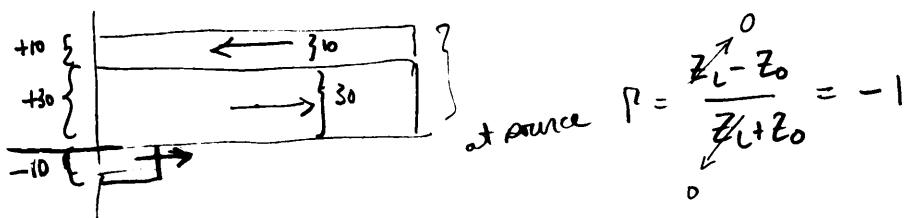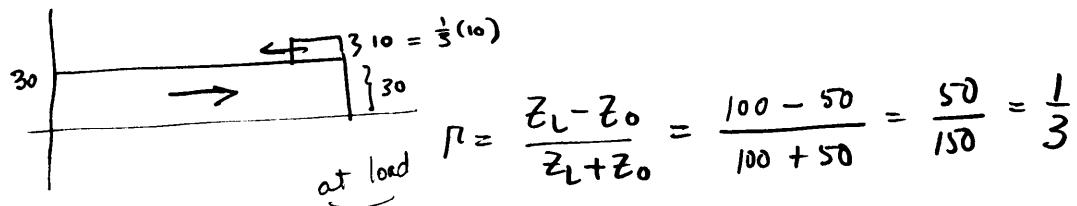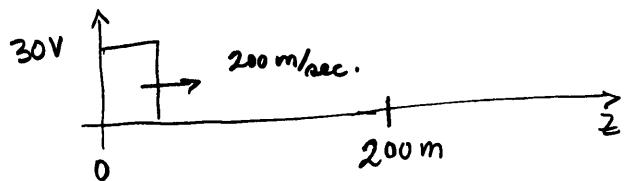

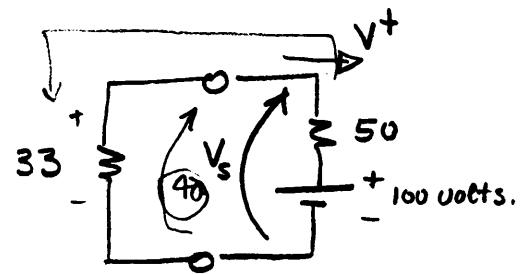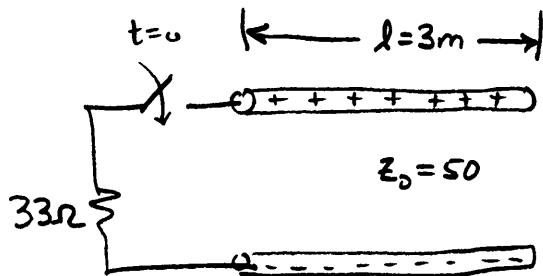

Since $V_s \neq V_b$ except when $R = \infty$,
a wave is launched...



$$V_s = V_b + \frac{R_s}{R_s + z_0} V^+$$


$$\text{Therefore } V_s = + \frac{100}{50 + 33} \cdot 33 = +40 \text{ volts.}$$

Voltage across $R = 33\Omega$ resistor is sum of initial voltage V_b and that of launched wave.

$$V_s = V_b + V^+$$
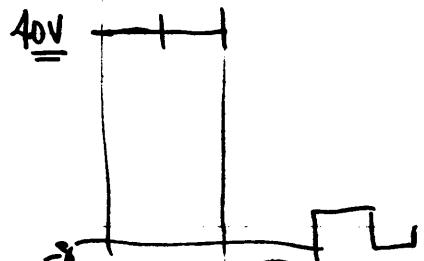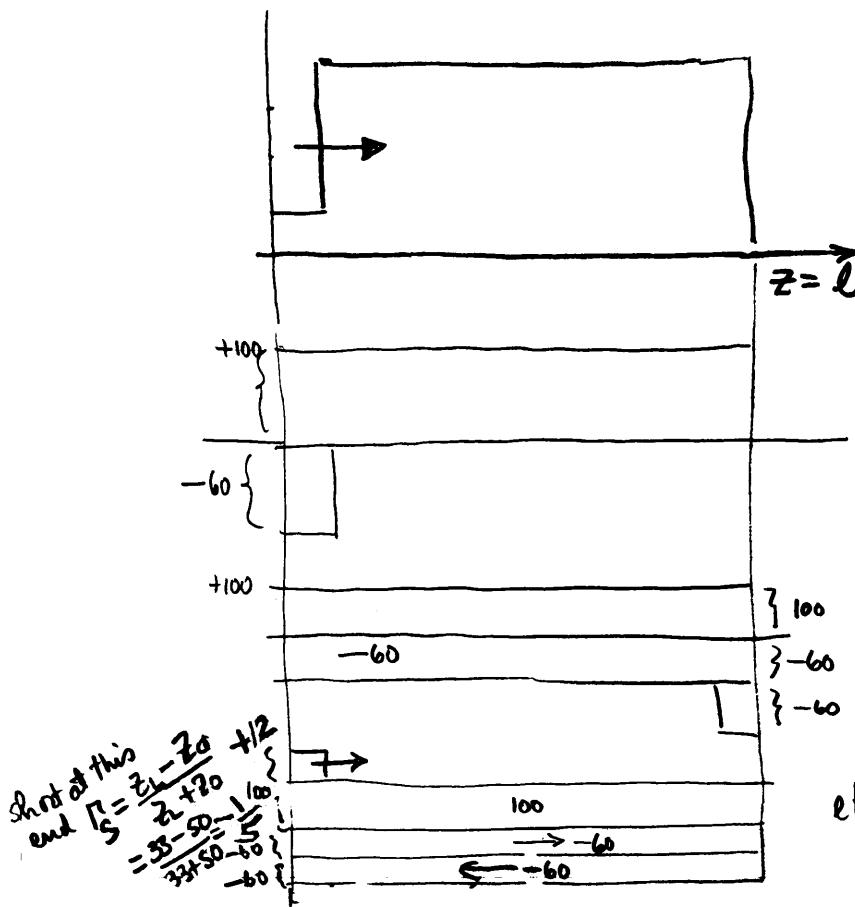
$$40 = 100 + V^+ \quad \therefore V^+ = -60 \text{ volts.}$$



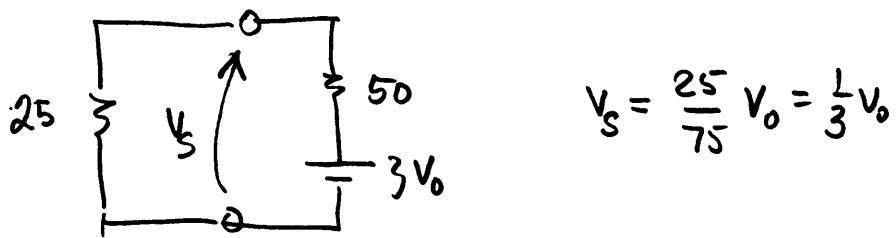


$$\Gamma_L^{(v)} = \frac{Z_L - Z_0}{Z_L + Z_0} = +1$$

$$\Gamma_s^{(v)} = \frac{Z_s - Z_0}{Z_s + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{25}{75} = -\frac{1}{3}$$

$$V_s = V^+ + V_0 \quad \text{but } V_s = \frac{1}{3} V_0$$


$$\frac{1}{3} V_0 = V^+ + V_0$$


$$\therefore V^+ = -\frac{2}{3} V_0$$

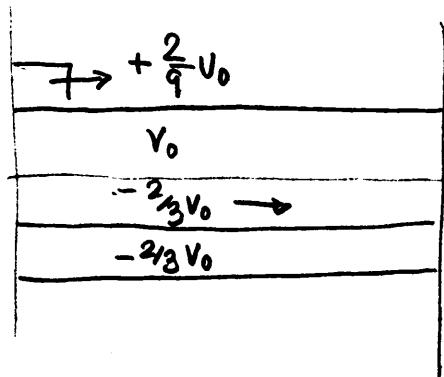



$$V_0 - \frac{4}{3} V_0 + \frac{2}{3} V_0$$

$$\frac{9 - 12 + 2}{9}$$

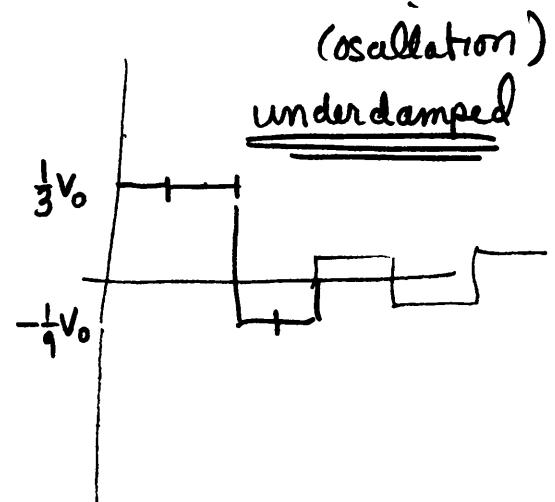

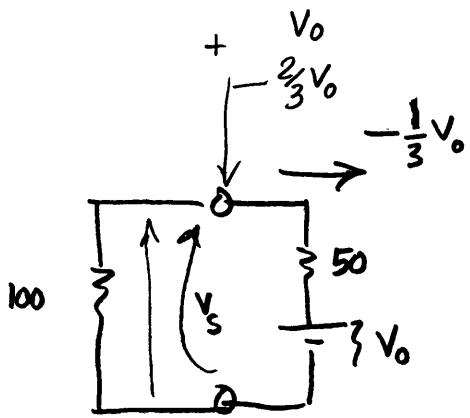

$$\frac{2}{3}V_o \quad \{ V_o$$

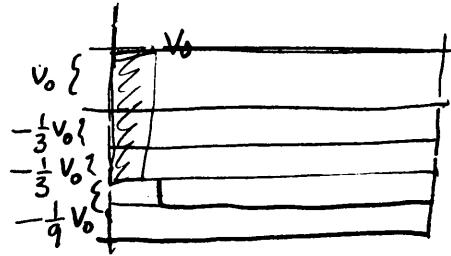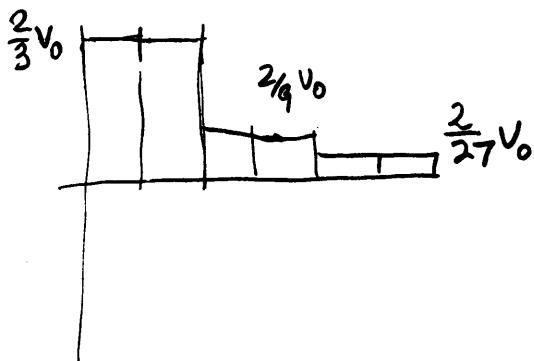

$$V_s = \frac{100}{150} V_o = \frac{2}{3}V_o$$

NOT (-1)

$$P_S(v) = \frac{Z_S - Z_0}{Z_S + Z_0} = \frac{100 - 50}{100 + 50} = \left(\frac{1}{3}\right)$$


$$+ \frac{1}{3}V_o - \frac{1}{9}V_o$$

$$\frac{3-1}{9}V_o = \frac{8}{9}V_o$$



$$V_o - \frac{2}{3}V_o - \frac{2}{9}V_o - \frac{1}{27}V_o$$

$$\frac{27 - 18 - 6 - 1}{27} = \frac{2}{27} V_o$$

overdamped (decay)

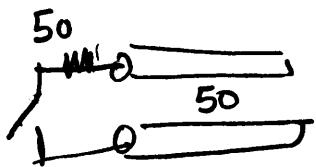


critically damped

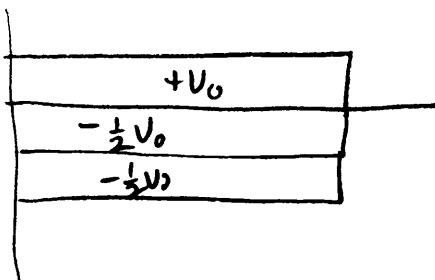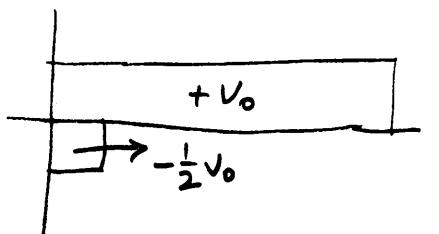



nothing

$$\begin{aligned} V_S &= V^+ + V_B \\ \frac{1}{2}V_0 &\approx V^+ + V_B \\ \therefore V^+ &\approx \frac{1}{2}V_0 \end{aligned}$$

short pulses

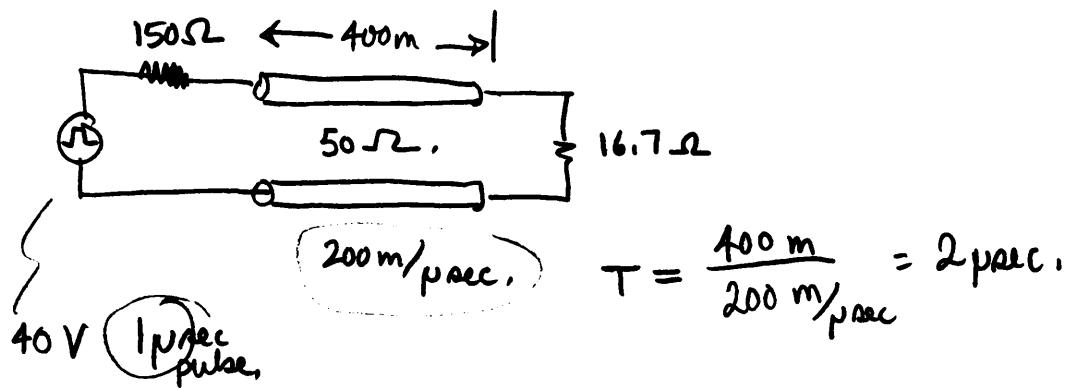
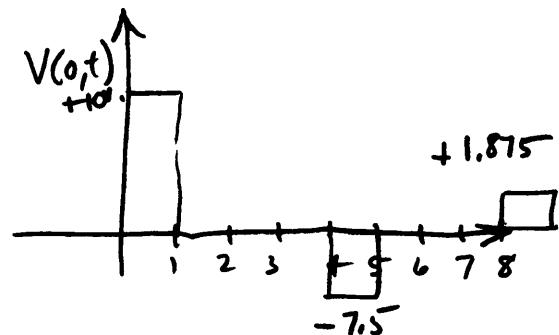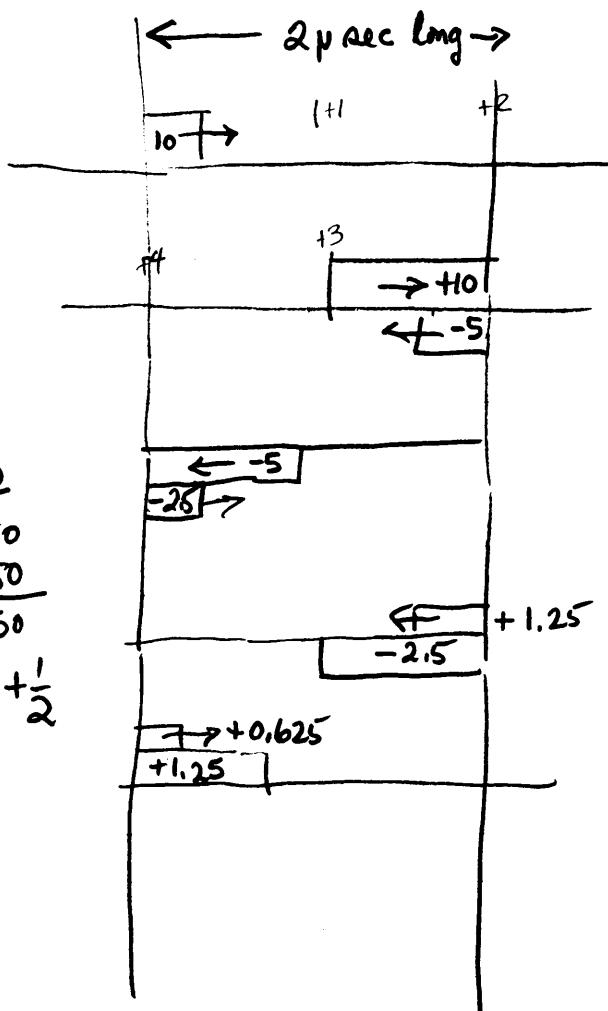
$$\text{into line: } V^+ = \frac{50}{200} (40) = 10 \text{ V.}$$





etc.

oscillating


Tough

problem for you to do:

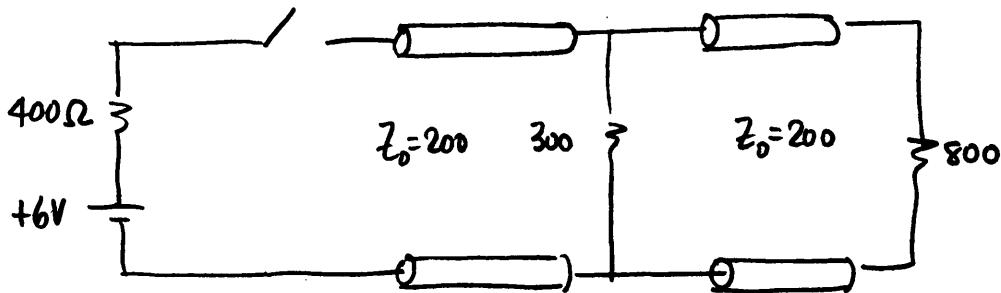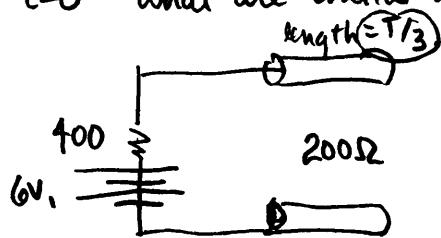length = $T/3$ at $t=0$ what are initial voltage & current waves...


$$V^+ = \left(\frac{200}{600}\right) 6 = 2 \text{ Volts.}$$

$$I^+ = \frac{V^+}{Z_0} = \frac{2 \text{ Volts}}{200\Omega} = 0.01 \text{ Amps.}$$

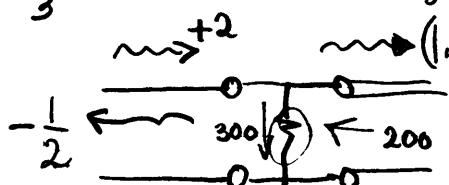at $t = T/3$ what is total voltage & current in the shunt

$$R = \frac{(200)(300)}{200 + 300} = 120\Omega$$
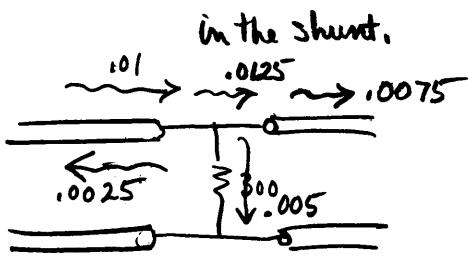
$$\begin{aligned} R_{\text{shunt}} &= \frac{Z_{\text{shunt}} - Z_0}{Z_{\text{shunt}} + Z_0} = \frac{120 - 200}{120 + 200} = -\frac{80}{320} \\ &= -\frac{1}{4} \end{aligned}$$



$$R_I = -R_V = +\frac{1}{4}$$

$$i_{\text{cable}} = \frac{1.5 \text{ Volts}}{200\Omega} = .0075 \text{ A}$$

$$i_{\text{generator}} = \frac{1.5 \text{ Volts}}{300\Omega} = .005 \text{ A.}$$

How about sinusoidal (phasor) solutions of transmission line equations?

motivations:

- ① most of the world is analog
 - ② represent digital pulses by Fourier series
- $$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{j\omega n t}$$
- ③ simple solutions

transmission line equations

$$\frac{\partial^2 V}{\partial z^2} = + LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial z^2} = + LC \frac{\partial^2 I}{\partial t^2}$$

$$V(z,t) = \Re \left[\hat{V}(z) e^{j\omega t} \right]$$

$$I(z,t) = \Re \left[\hat{I}(z) e^{j\omega t} \right]$$

$$\frac{d^2 \hat{V}}{dz^2} e^{j\omega t} = + LC (j\omega)^2 \hat{V}(z) e^{j\omega t}$$

$$\frac{d^2 \hat{V}(z)}{dz^2} = - \omega^2 LC \hat{V}(z) \quad \text{canceling } e^{j\omega t}$$

$$u = \sqrt{LC} \quad \therefore \frac{d^2 \hat{V}(z)}{dz^2} = - \left(\frac{\omega^2}{u^2} \right) \hat{V}(z)$$


solutions: $e^{\pm j \frac{\omega}{u} z}$

$$\therefore \hat{V}(z) = \hat{V}^+ e^{-j \frac{\omega}{u} z} + \hat{V}^- e^{+j \frac{\omega}{u} z}$$

$$\hat{I}(z) = \hat{I}^+ e^{-j \frac{\omega}{u} z} + \hat{I}^- e^{+j \frac{\omega}{u} z}$$

$$= \frac{\hat{V}^+}{Z_0} e^{-j \frac{\omega}{u} z} - \frac{\hat{V}^-}{Z_0} e^{+j \frac{\omega}{u} z}$$

let's look at a circuit

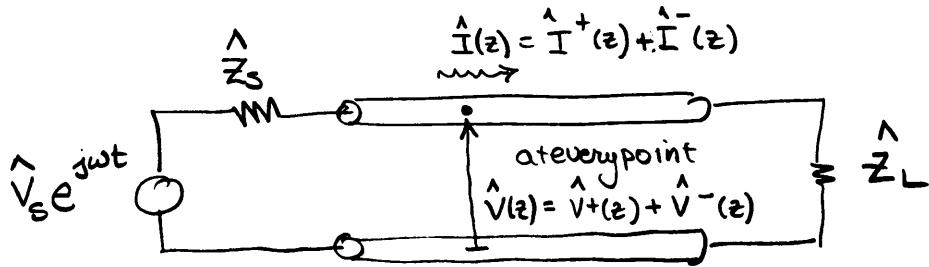

we can define $\hat{Z}(z)$ at every point

$$\hat{Z}(z) = \frac{\hat{V}(z)}{\hat{I}(z)} = \frac{\hat{V}^+(z) + \hat{V}^-(z)}{\hat{I}^+(z) + \hat{I}^-(z)} \neq Z_0$$

furthermore, since $\hat{Z}(z)$ is distributed we can also write p , the reflection coefficient, everywhere.

$$\hat{p}(z) = \frac{\hat{V}^-(z)}{\hat{V}^+(z)} = \frac{\hat{V}^- e^{+j\beta z}}{\hat{V}^+ e^{-j\beta z}} = \frac{\hat{V}^-}{\hat{V}^+} e^{j2\beta z}$$

$$\begin{aligned} \hat{V}(z,t) &= \hat{V}^+ e^{-j\beta z} + \hat{V}^- e^{+j\beta z} \\ &= \hat{V}^+ e^{-j\beta z} \left[1 + \frac{\hat{V}^- e^{j\beta z}}{\hat{V}^+ e^{-j\beta z}} \right] = \underbrace{\hat{V}^+ e^{-j\beta z}}_{\text{everywhere.}} \left[1 + \hat{p}(z) \right] \end{aligned}$$

$$\begin{aligned} \hat{I}(z,t) &= \frac{\hat{V}^+ e^{-j\beta z}}{Z_0} - \frac{\hat{V}^- e^{+j\beta z}}{Z_0} \\ &= \frac{\hat{V}^+}{Z_0} e^{-j\beta z} \left[1 - \frac{\hat{V}^- e^{j\beta z}}{\hat{V}^+ e^{-j\beta z}} \right] = \frac{\hat{V}^+ e^{-j\beta z}}{Z_0} \left[1 - \hat{p}(z) \right] \end{aligned}$$

$$\hat{Z}(z) = \frac{\hat{V}(z)}{\hat{I}(z)} = \frac{\hat{V}^+ e^{-j\beta z} [1 + \hat{p}(z)]}{\hat{V}^+ e^{-j\beta z} [1 - \hat{p}(z)]} = Z_0 \frac{1 - \hat{p}(z)}{1 + \hat{p}(z)}$$

Equations needed to solve most problems


are

$\hat{P}(z) = \frac{\hat{V}_-}{\hat{V}_+} e^{j2\beta z}$
$\hat{Z}(z) = Z_0 \frac{1 + \hat{P}(z)}{1 - \hat{P}(z)}$

Simple proof: $\hat{P}(z) = \frac{\hat{V}_-}{\hat{V}_+} e^{j2\beta z}$

$$\hat{P}(z=\lambda) = \hat{P}_L = \frac{\hat{V}_-}{\hat{V}_+} e^{j2\beta\lambda}$$

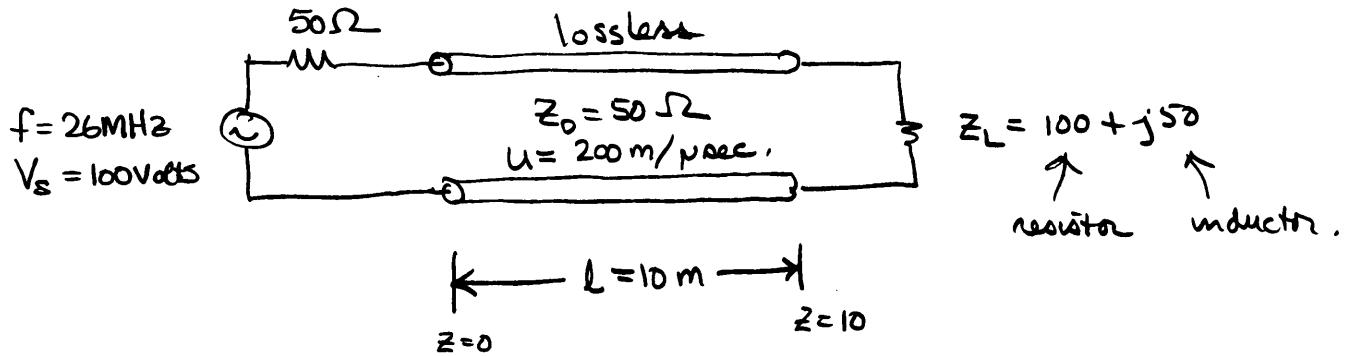dividing $\frac{\hat{P}(z)}{\hat{P}_L} = e^{j2\beta(z-\lambda)}$



What is Z at $z=0$

V at $z=0$ and $z=L$

$$\beta = \frac{\omega}{u} = \frac{2\pi(26 \times 10^6)}{200 \times 10^6} = 0.82 \text{ rad/meter}$$

electrical length

$$2\beta L = (2)(0.82 \text{ rad/m}) (10\text{m}) = 16.34 \text{ radians}$$


$\boxed{2\beta L} = 936^\circ = 936 - 2 \cdot 360 = \boxed{216^\circ}$

No matter how long our line really is this is its phase shift, or electrical length....

what is $\hat{P}(z=L)$?

$$\hat{P}_L = \frac{\hat{Z}_L - \hat{Z}_0}{\hat{Z}_L + \hat{Z}_0} = \frac{100 + j50 - 50}{100 + j50 + 50} = \frac{50 + j50}{150 + j50}$$

$$= (0.4 + j0.2)$$

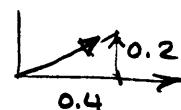

transform P_L to $P(0)$

$$\begin{aligned} P(0) &= P_L e^{-j2\beta L} \\ &= (0.4 + j0.2)(e^{-j216^\circ}) \\ &= (0.4 + j0.2)(-0.809 + j0.58) \\ &= -0.44 + j0.0702. \end{aligned}$$


knowing P_L we relate it to Z_{in}

$$\hat{Z}_{in} = Z(0) = Z(0) \frac{1 + P(0)}{1 - P(0)}$$

$$= (50) \left(\frac{1 + 0.44 + j0.07}{1 + 0.44 - j0.07} \right) = 50 \frac{0.58 + j0.07}{1.44 - j0.07}$$

$$= 50 (0.38 + j0.06) = \boxed{19 + j3.36 \Omega}$$

generator see's

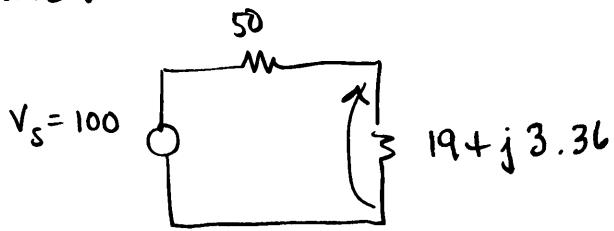

$$\hat{V}(0) = \frac{\hat{Z}_{in}}{\hat{Z}_s + \hat{Z}_{in}} V_s = \frac{19 + j3.36}{50 + 19 + j3.36} \cdot 100 = \frac{19 + j3.36}{69 + j3.36} (100)$$

$$= (0.277 - j0.035) 100$$

$$= 27.7 - j3.5 \text{ volts}$$

how do we get $\hat{V}(z=0)$. Ans:

$$\begin{aligned}\hat{V}(z) &= V^+ e^{-j\beta z} + V^- e^{-j\beta z} \\ &= V^+ e^{-j\beta z} \left[1 + \left| \frac{V^-}{V^+} e^{-j2\beta z} \right| \right] \\ &\quad \uparrow \qquad \qquad \qquad \text{this is } P(z) \\ &\quad \text{unknown}\end{aligned}$$

$$\text{at } z=0 \quad 27.7 - j3.5 = V^+ (1) [1 + P(0)]$$

$$\begin{aligned}\text{what is } P(0)? \quad P(0) &= P_L e^{-j2\beta z} \\ &= P_L e^{-j216^\circ} \\ &= (0.4 + j0.2)(\cos 216^\circ - j \sin 216^\circ) \\ &= (0.4 + j0.2)(-0.809 + j0.5878) \\ &= -0.44 + j0.074\end{aligned}$$

$$(27.7 - j3.5) = V^+ (1) [1 - 0.44 + j 0.074]$$

$$V^+ = \frac{27.7 - j 3.5}{.56 + j 0.074} = (147.8 - j 12.57) \text{ volts}$$

$$\hat{v}(z=\ell) = V^+ e^{-j\beta z} [1 + \rho(z=\ell)] \\ = (47.8 - j 12.57)(e^{-j 108^\circ})(1 + 0.4 + j 0.2)$$


$$2\beta z = 936^\circ$$

$$\rho z = 468^\circ$$

$$\beta z = 108^\circ$$

$$= (47.8 - j 12.57)(-.3090 + j 0.9511)(1.4 + j 0.2)$$

$$= -13.8 + j 68.52$$

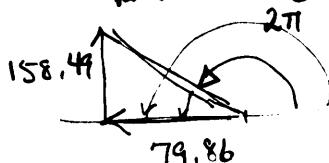

This example was a simple example but note how complex the algebra was

usually we are only interested in impedances, not voltages. There is a quick way of finding impedance transformations.

$$\text{Recall } \hat{Z}(z=l) = \hat{Z}_L = \hat{Z}_0 \frac{1 + \hat{\rho}(z=l)}{1 - \hat{\rho}(z=l)}$$

$$\hat{\rho}(z=l) = \frac{\hat{Z}_L - \hat{Z}_0}{\hat{Z}_L + \hat{Z}_0}$$

$$\hat{\rho}(z) = \rho_L e^{+j2\beta(z-l)}$$

Combine these equations to get


$$\hat{Z}_{IN}(z) = \hat{Z}_0 \frac{\hat{Z}_L + j\hat{Z}_0 \tan \beta(l-z)}{\hat{Z}_0 + j\hat{Z}_L \tan \beta(l-z)}$$

$$\hat{Z}_{IN}(z=0) = \hat{Z}_0 \frac{\hat{Z}_L + j\hat{Z}_0 \tan \beta l}{\hat{Z}_0 + j\hat{Z}_L \tan \beta l}$$

This is very easy to use if l is in wavelengths.

$$\text{say } l = \frac{\lambda}{4}$$
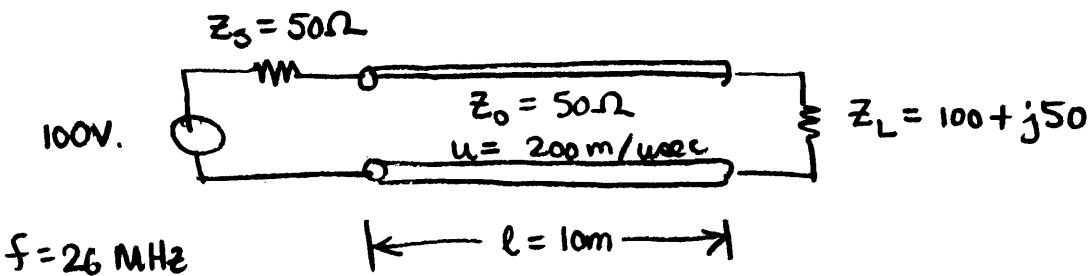
$$\text{but } \beta = \frac{2\pi}{\lambda}$$



$$\beta = \frac{\omega}{u} = \frac{2\pi f}{u} = \frac{(26 \times 10^6) 2\pi}{200 \frac{\text{m}}{10^{-6}}} = 0.8168 \text{ rad/m.}$$

$$2\beta l = 2(0.8168 \text{ rad/m})(10\text{m}) = 16.34 \text{ rad} = 936.2^\circ$$

$$= 936 - 720 \approx 216.2^\circ$$

* we can compute ρ_L since Z_L and Z_0 are known.

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 + j50 - 50}{100 + j50 + 50} = \frac{50 + j50}{150 + j50}$$

$$= 0.4 + j0.2 = 0.4472 e^{j26.57^\circ}$$

* since $\rho(z) = \rho_L e^{-j2\beta(l-z)}$

$$\rho(0) = (0.4472 e^{j26.57^\circ})(e^{-j216.2^\circ})$$

$$= 0.4472 e^{-j189.63}$$

$$= -0.441 + j0.07$$


* we can now calculate the input impedance

$$Z_{in}^{(0)} = Z_0 \frac{1 + \rho(0)}{1 - \rho(0)} = 50 \frac{1 + (-0.441 + j0.07)}{1 - (-0.441 + j0.07)}$$

$$= 50 \left(\frac{0.559 + j0.07}{1.441 - j0.07} \right) = 50 (0.385 + j0.067)$$

$$= 19.23 + j3.36 = 19.52 e^{j9.9^\circ}$$

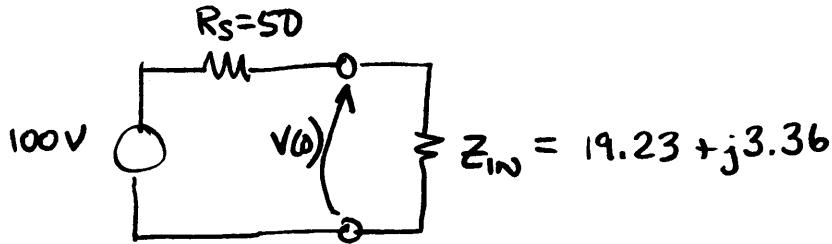* the input voltage comes from a complex voltage divider



$$\hat{v}(0) = \frac{Z_{in}}{Z_{in} + 50} 100 = \frac{19.23 + j3.36}{19.23 + j3.36 + 50} (100) = \\ = (27.95 + j3.49) \text{ volts} = 28.16 e^{+j7.13^\circ}$$

* What is the voltage anywhere on the line

$$\hat{V}(z) = v^+ e^{j2\beta z} [1 + \rho(z)]$$

idea we know $\hat{v}(0)$, $\hat{\rho}(0)$

$$\hat{\rho}(z)$$

want $\hat{v}(l)$. So if we can determine the $v^+ e^{j2\beta z}$
we can determine $\hat{V}(z)$ anywhere.

$$\hat{v}(0) = v^+ (1) [1 + \rho(0)]$$

$$v^+ = \frac{\hat{v}(0)}{1 + \hat{\rho}(0)} = \frac{27.95 + j3.49}{1 + (-.441 + j0.07)}$$

$$= \frac{27.95 + j3.49}{0.559 + j0.07} = 50.0 - j0.0176 = 50.0 e^{-j.02}$$

now calculate $\hat{v}(l=10m)$

$$\hat{V}(z) = v^+ \bar{e}^{-j\beta z} [1 + \rho(z)]$$


$$\hat{V}(10) = (50 e^{-j.02})(\bar{e}^{-j128^\circ})(1 + \rho_L)$$

$$= 50 e^{-j0.02} \bar{e}^{-j128^\circ} \frac{1.443 e^{j2.18^\circ}}{1.443 e^{j2.18^\circ} + .441 + j0.07} = 1.444 + j0.07$$

$$= 72.15 \bar{e}^{-j125.2^\circ} = (-41.6 - j58.9) \text{ volts}$$

$$Z_{in} = 19.2 + j3.5 \Omega = 19.52 e^{j13.33}$$

* Voltage into line

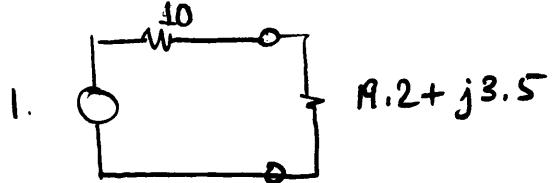

$$\hat{V}_o(0) = 1 \frac{19.2 + j3.5}{10 + 19.2 + j3.5} = \frac{19.2 + j3.5}{29.2 + j3.5}$$

$$\hat{V}(0) = 0.66 + j0.040 \text{ (volts)} = 0.66 e^{j3.46^\circ}$$

* current into line

$$\begin{aligned} \hat{I}(0) &= \frac{\hat{V}(0)}{Z_{in}(0)} = \frac{0.66 + j0.04}{19.2 + j3.5} = (0.036 - j0.0041) \text{ Amps} \\ &= 0.034 e^{-j6.86^\circ} \end{aligned}$$

* input power

$$\begin{aligned} P_{in} &= \frac{1}{2} \operatorname{Re} [\hat{V}(0) \hat{I}^*(0)] \\ &= \frac{1}{2} \operatorname{Re} [(0.66 + j0.04)(0.036 + j0.0041)] \\ &= \frac{1}{2} \operatorname{Re} [0.022 + j0.0041] \\ &= 0.011 \text{ watts into line} \end{aligned}$$

* loss less line so $P_{LOAD} = P_{in} = 0.011 \text{ watts.}$

* compute load voltage as before...

$$\hat{V}(z) = V^+ e^{-j\beta z} [1 + \hat{\rho}(z)]$$

known: $\hat{V}(0)$, $\hat{\rho}(0)$, $\hat{\rho}_L$

$$\text{at } z=0. \quad \hat{\rho}(z=0) = \hat{\rho}_L e^{-j2\beta l} = 0.447 e^{j26.57} e^{-j216^\circ} \\ = 0.447 e^{-189.4} \\ \hat{\rho}(0) = -0.441 + j0.07$$

$$V^+ = \frac{\hat{V}(0)}{1 + \hat{\rho}(0)} = \frac{0.66 + j0.04}{1 - 0.441 + j0.07} = \frac{0.66 + j0.04}{0.559 + j0.07}$$

$$V^+ = 1.17 - j0.075 = 1.17 e^{-j3.67^\circ}$$

$$\hat{V}(l) = (1.17 e^{-j3.67^\circ}) e^{-j\beta l} [1 + \hat{\rho}_L] \\ = (1.17 e^{-j3.67^\circ})(e^{-j108^\circ})(\underbrace{1 + 0.4 + j0.2}_{1.4 + j0.2} = 1.414 e^{j8.13})$$


$$V(l) = (1.17 e^{-j3.67^\circ})(e^{-j108^\circ})(1.414 e^{j8.13}) \\ = 1.65 e^{-j103.5}$$

$$\hat{I}(l) = \frac{\hat{V}(l)}{Z_L} = \frac{1.65 e^{-j103.5}}{100 + j50} = 111.8 e^{j26.6} = 0.0148 e^{-j130.1}$$

$$\text{Power} = \frac{1}{2} \operatorname{Re} [\hat{V}(l) \hat{I}^*(l)] = \frac{1}{2} \operatorname{Re} [1.65 e^{-j103.5} 0.0148 e^{+j130.1}] \\ = \frac{1}{2} \operatorname{Re} [0.02442 e^{j26.6}] = \frac{1}{2} \operatorname{Re} [0.022 + j0.011]$$

≈ 0.011 watts.

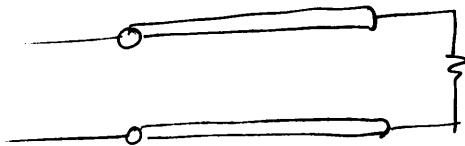let's look at getting line voltages simply.



$$\text{Recall } \hat{V}(z) = \hat{V}^+ e^{-j\beta z} [1 + \hat{\rho}(z)]$$

$$|\hat{V}(z)| = |\hat{V}^+| |1 + \hat{\rho}(z)|$$


↑
independent of z look at z -dependence of this

$$\hat{\rho}(z) = |\hat{\rho}(z)| e^{j\theta_p}$$

$$\text{but } \hat{\rho}(z) = \frac{V^-}{V^+} e^{j2\beta z}$$

$$\text{so } |\rho(z)| = \frac{V^+}{V^-} \quad \left. \begin{array}{l} \text{assume } V^+ \\ V^- \text{ real} \end{array} \right)$$

$$|1 + \rho(z)| = \left| 1 + \frac{V^-}{V^+} e^{j2\beta z} \right| =$$

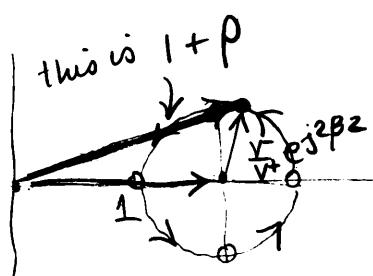

this looks like
the crank of a
locomotive!

how can we interpret this

$$\hat{V}(z) = V^+ e^{-j\beta z} [1 + \hat{\rho}(z)]$$

$$|\hat{V}(z)| = |V^+| |e^{-j\beta z}| |1 + \hat{\rho}(z)|$$



$$= |V^+| |1 + \hat{\rho}(z)|$$

magnitude of 1

obviously $|\hat{V}(z)|$ is periodic

$|V|_{\max}$

$|V|_{\min}$

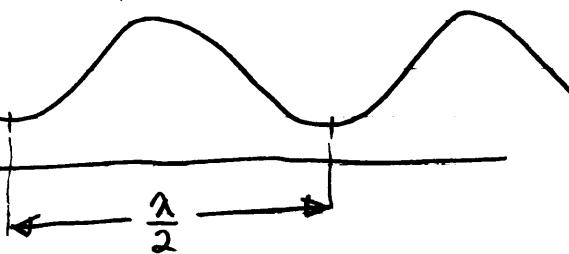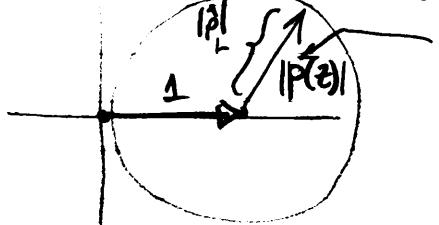

$$\hat{\rho}(z) = \hat{\rho}_L e^{j2\beta(z-\ell)}$$

$$2\beta(\lambda) = 2 \frac{2\pi}{\lambda}, x = 2\pi$$

$$|\hat{V}|_{\max} = |V^+| (1 + |\rho_L|)$$

$$\frac{2x}{\lambda} = 1$$

$$x = \frac{\lambda}{2}$$


$$|\hat{V}|_{\min} = |V^+| (1 - |\rho_L|)$$

$$VSWR = \frac{1 + |\rho_L|}{1 - |\rho_L|} \quad 0 \leq |\rho_L| \leq 1$$

$$1 \leq VSWR < \infty$$



plot $|\hat{V}_{max}|$ $Z_L = 0$ $\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$

$$|\rho_L| = 1$$

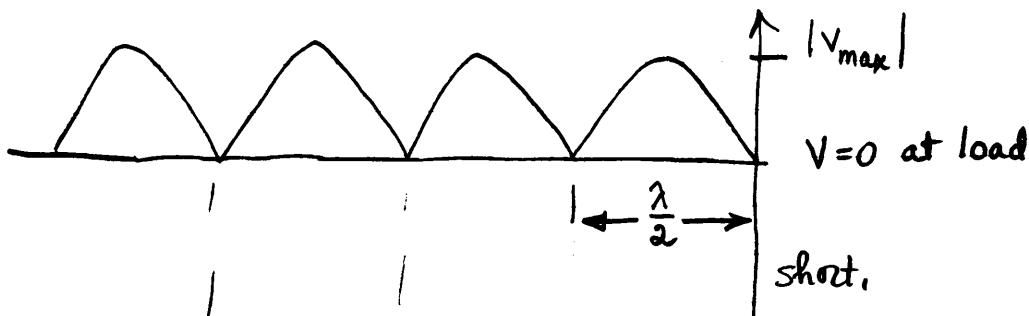

How about $\hat{I}(z) = \frac{V^+}{Z_0} e^{-j\beta z} [1 - \hat{\rho}(z)]$


$$|\hat{I}(z)| = \left| \frac{V^+}{Z_0} \right| [1 - |\rho(z)|]$$

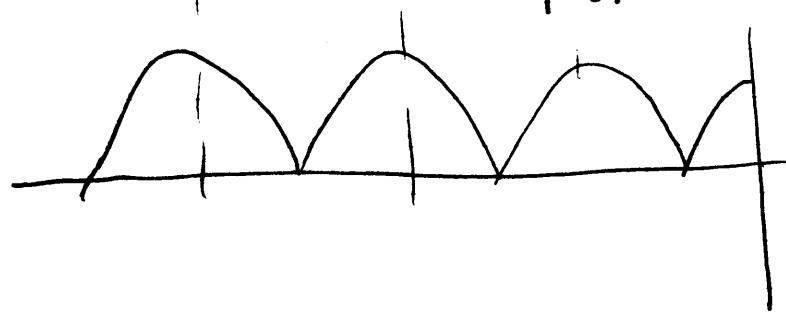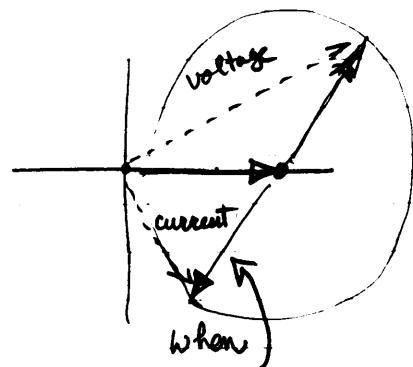

when voltage = max
current = min


at load when $Z_L = \infty$ $\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} = +1$

$$|\rho_L| = 1$$

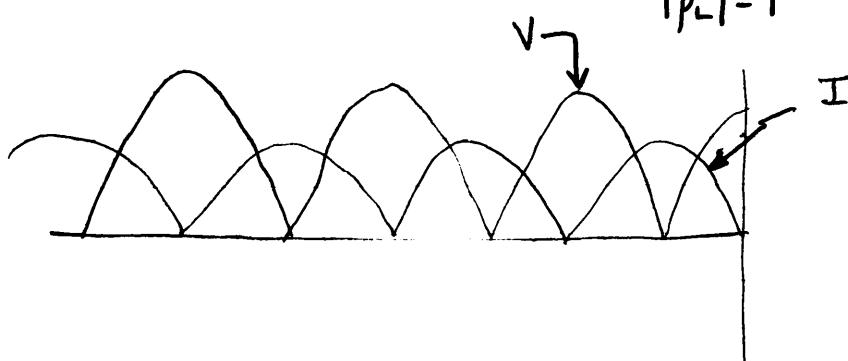


if $Z_L = Z_0$ $\rho \rightarrow 0$ and $|V| = \text{constant}$
 $|I| = \text{constant}$.

i.e.

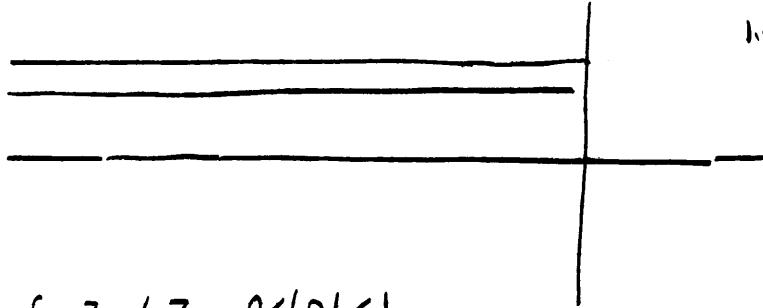

if $Z_L \neq Z_0$ $0 < |\rho| < 1$

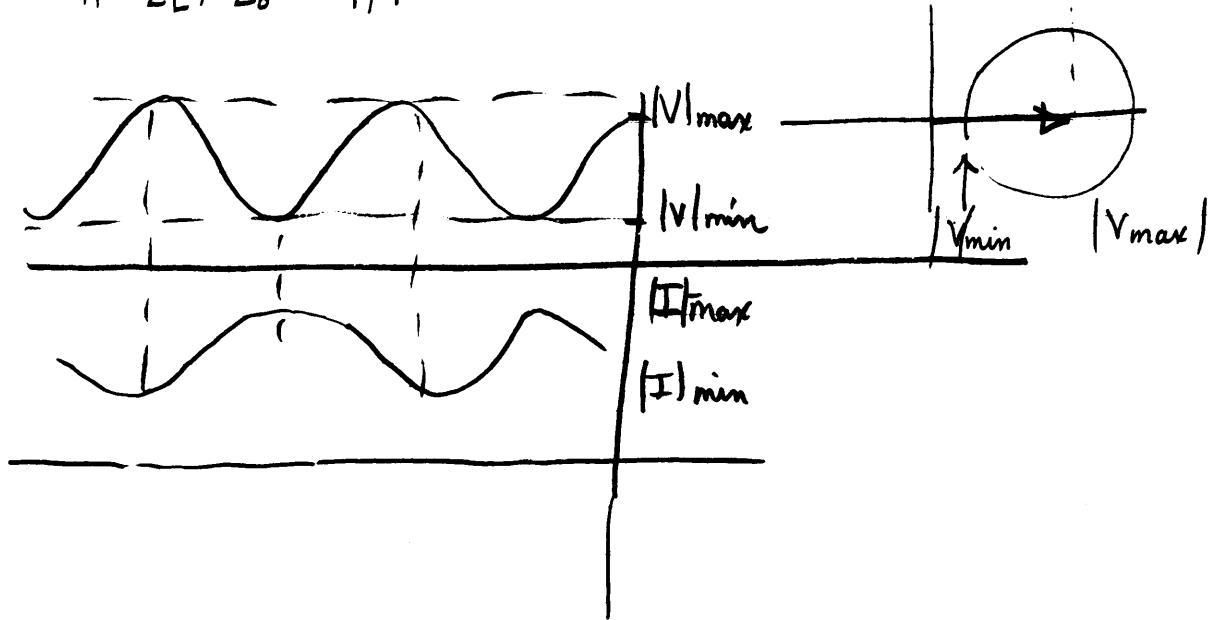

Notes about things on the line


$$\hat{P}(z) = P_L e^{-j2\beta(z-l)}$$

this is periodic in 2π

$$\hat{V}(z) = V^+ e^{-j\beta z} [1 + \hat{f}(z)]$$

$$\hat{V}(l) = V^+ e^{-j\beta l} + V^- e^{+j\beta l}$$
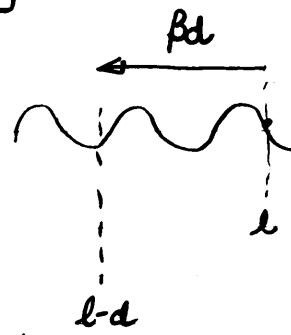
$$\hat{I}(l) = \frac{V^+}{Z_0} e^{-j\beta l} - \frac{V^-}{Z_0} e^{+j\beta l}$$



with respect to the load....

$$\hat{V}(l-d) = (V^+ e^{-j\beta l}) e^{j\beta d} + (V^- e^{+j\beta l}) e^{-j\beta d}$$

$$\hat{I}(l-d) = \left(\frac{V^+}{Z_0} e^{-j\beta l} \right) e^{j\beta d} - \left(\frac{V^-}{Z_0} e^{+j\beta l} \right) e^{-j\beta d}$$

expand $\stackrel{\pm}{e}^{j\beta d}$

$$\hat{V}(l-d) = V^+ e^{-j\beta l} \cos \beta d + j V^+ e^{-j\beta l} \sin \beta d + V^- e^{+j\beta l} \cos \beta d - j V^- e^{+j\beta l} \sin \beta d$$


$$\hat{I}(l-d) = \left(\frac{V^+}{Z_0} e^{-j\beta l} \right) \cos \beta d + j \left(\frac{V^+}{Z_0} e^{-j\beta l} \right) \sin \beta d - \left(\frac{V^-}{Z_0} e^{+j\beta l} \right) \cos \beta d + j \left(\frac{V^-}{Z_0} e^{+j\beta l} \right) \sin \beta d$$

$$\hat{V}(l-d) = (V^+ e^{-j\beta l} + V^- e^{+j\beta l}) \cos \beta d + j (V^+ e^{-j\beta l} - V^- e^{+j\beta l}) \sin \beta d$$

$$\hat{I}(l-d) = \left(\frac{V^+ e^{-j\beta l}}{Z_0} - \frac{V^- e^{+j\beta l}}{Z_0} \right) \cos \beta d + j \left(\frac{V^+ e^{-j\beta l}}{Z_0} + \frac{V^- e^{+j\beta l}}{Z_0} \right) \sin \beta d.$$

$$\hat{V}(l-d) = \hat{V}(l) \cos \beta d + j Z_0 \hat{I}(l) \sin \beta d$$
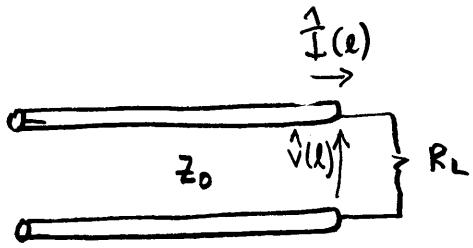
$$\hat{I}(l-d) = \hat{I}(l) \cos \beta d + j \frac{\hat{V}(l)}{Z_0} \sin \beta d.$$




$$\text{at load } Z_L = R_L \text{ and } I(l) = \frac{\hat{V}(l)}{R_L}$$

$$\text{then } \hat{V}(l-d) = \hat{V}(l) \cos \beta d + j \frac{Z_0}{R_L} \hat{V}(l) \sin \beta d = \hat{V}(l) \left[\cos \beta d + j \frac{Z_0}{R_L} \sin \beta d \right]$$



$$\hat{I}(l-d) = \frac{\hat{V}(l) \cos \beta d + j \frac{Z_0}{R_L} \hat{V}(l) \sin \beta d}{\frac{Z_0}{R_L}} = \frac{\hat{V}(l)}{\frac{Z_0}{R_L}} \left[\cos \beta d + j \frac{R_L}{Z_0} \sin \beta d \right]$$


\uparrow
 $I(l)$

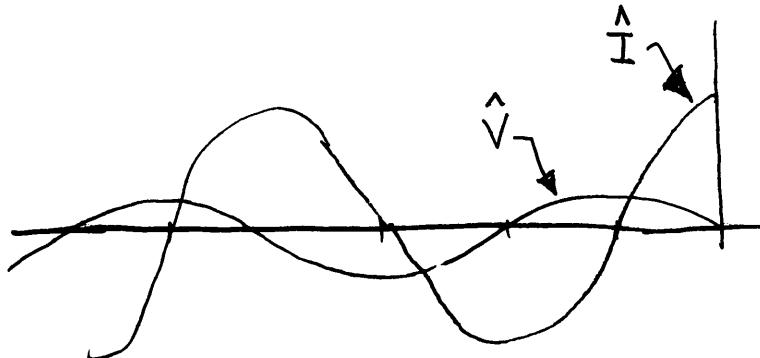suppose $R_L = 0$ a short then $V(l) = 0$



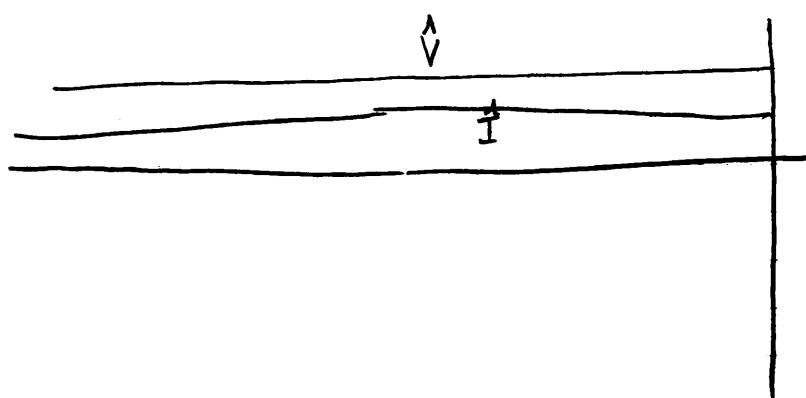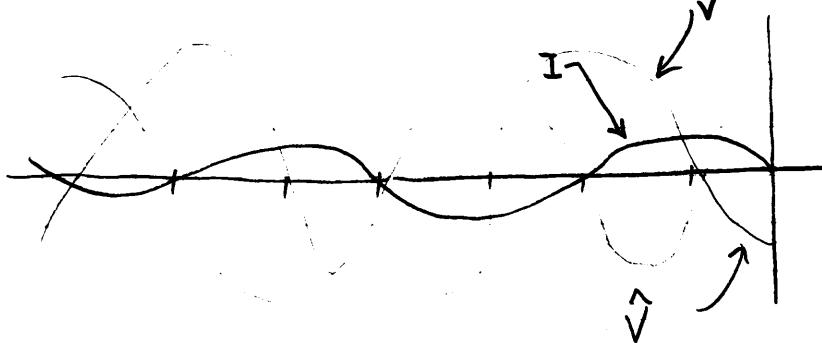
suppose $R_L = \infty$ an open then $I(l) = 0$



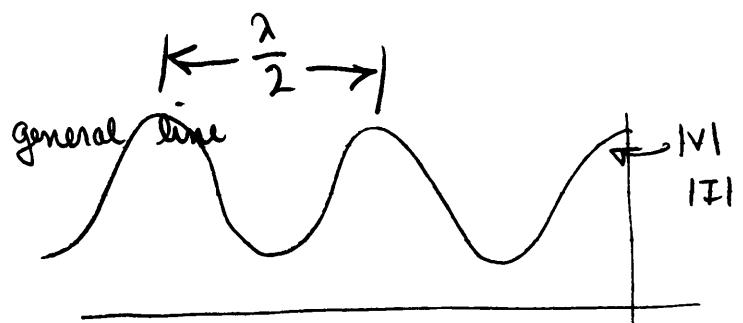

simpler way $\hat{V}(z) = V^+ e^{-j\beta z}$

load voltage, average power to load

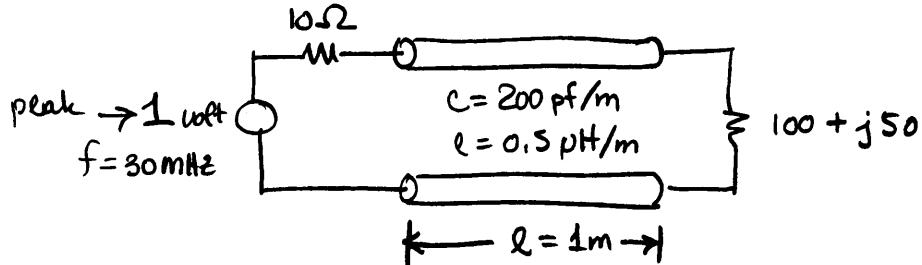

* basic parameters

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.5 \times 10^{-6}}{200 \times 10^{-12}}} = 50 \Omega$$

$$u = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.5 \times 10^{-6})(200 \times 10^{-12})}} = 10^8 \text{ m/sec.}$$

$$\beta = \frac{\omega}{u} = \frac{2\pi \cdot 30 \times 10^6}{10^8} = 1.8849 = \frac{2\pi}{\lambda}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{1.8849} = 3.333 \text{ meters}$$

line is $\frac{1}{3.333} \lambda = 0.3\lambda$ long

* reflection coefficient at load.

$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 + j50 - 50}{100 + j50 + 50} = \frac{50 + j50}{150 + j50} = 0.4 + j0.2$$

$$= 0.447 e^{j26.57^\circ}$$


* what is the input impedance

$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

$$\tan \beta l = \tan \frac{2\pi}{\lambda} \cdot 0.3\lambda = \tan (1.885 \text{ radians}) = \tan (108^\circ)$$

$$= -3.078$$
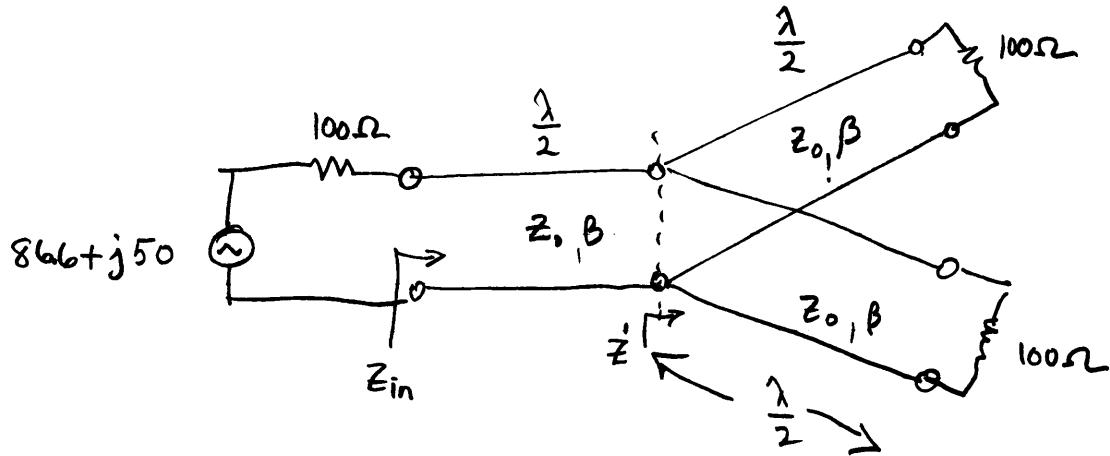
$$Z_{in} = \frac{(100 + j50) + j(50)(-3.078)}{(50) + j(100 + j50)(-3.078)} = \frac{100 - j103.88}{203.9 - j307.8} = .384 + j.07$$



a $\frac{\lambda}{2}$ line

$$Z' = z_0 \frac{z_L + j z_0 \tan \beta l}{z_0 + j z_L \tan \beta l}$$

$$\tan \frac{2\pi}{\lambda} \cdot \frac{\lambda}{2} = \tan \pi \rightarrow 0$$

$$\therefore Z' = z_0 \frac{z_L}{z_0} = z_L$$

two 100 ohm resistors in parallel $\Rightarrow 50 \Omega$

$$Z_{in} = z_0 \frac{50 + j z_0 \tan^0 \pi}{z_0 + j 50 \tan^0 \pi} \rightarrow 50 \Omega$$

$$V_{in} = \left(\frac{50}{50+100} \right) (86.6 + j50) = 28.87 + j16.6 = 33.3 e^{j30^\circ}$$

$$V(z) = \hat{V}^+ e^{-j\beta l} (1 + \hat{p}(z))$$

$$V_{in} = V(0) = V^+ (1 + p(0)) \quad p(0) = \frac{z_s - z_0}{z_s + z_0}$$

$$\beta l = \pi$$


$$V\left(\frac{\lambda}{2}\right) = V^+ e^{-j\beta l} \left(1 + \hat{p}\left(\frac{\lambda}{2}\right)\right)$$

$$\therefore \frac{V_{in}}{V\left(\frac{\lambda}{2}\right)} = \frac{V^+ (1 + p(0))}{V^+ e^{-j\beta l} \left(1 + \hat{p}\left(\frac{\lambda}{2}\right)\right)} = e^{j\beta l}$$

$$V\left(\frac{\lambda}{2}\right) = V_{in} e^{-j\beta l} = V_{in} e^{-j\pi}$$

same relationship for rest of line

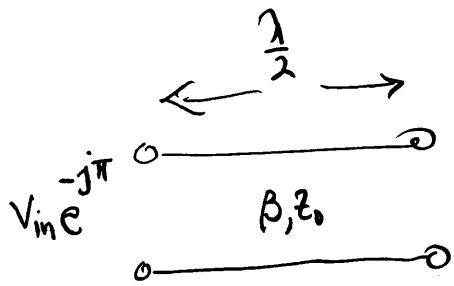but $p(z) = p_0 e^{j2\beta l}$
goes to 2π
so $p(z)$ is periodic in π
and $p\left(\frac{\lambda}{2}\right) = p(0)$



$$V(z) = V^+ e^{-j\beta z} [1 + \hat{\rho}(z)]$$

$$V(0) = V^+ [1 + \hat{\rho}(0)]$$

$$\therefore V^+ [1 + \hat{\rho}(0)] = V_{in} e^{-j\pi}$$


$$V\left(z = \frac{\lambda}{2}\right) = V^+ e^{-j\pi} \left[1 + \hat{\rho}\left(\frac{\lambda}{2}\right)\right] = V^+ e^{-j\pi} [1 + \hat{\rho}(0)]$$

\uparrow
[periodic]

$$= V^+ [1 + \hat{\rho}(0)] e^{-j\pi} = V_{in} e^{-j\pi} e^{-j\pi}$$

$$= V_{in} \boxed{e^{-j2\pi}} \rightarrow 1$$

$$\boxed{\therefore V_{ANT} = V_{in}}$$

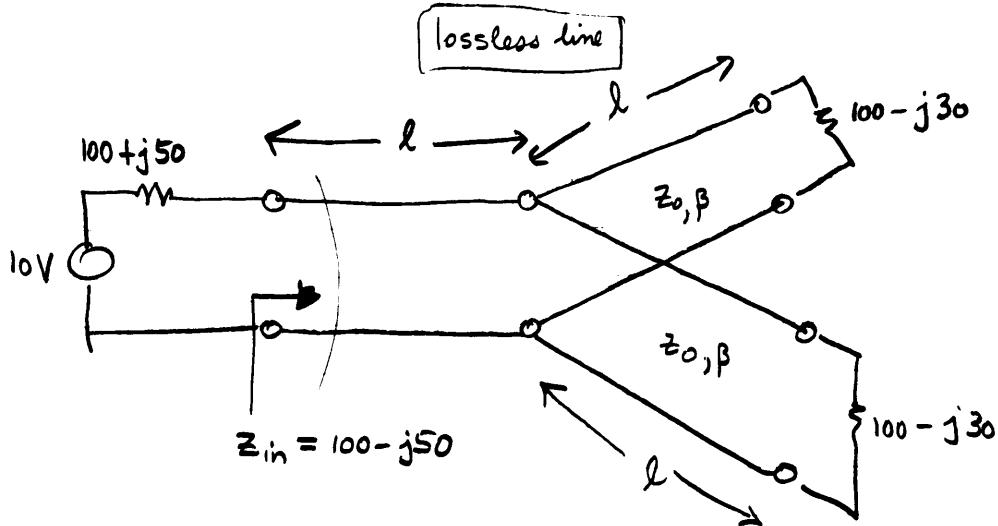

$$\begin{aligned}
 V_{in} &= \frac{z_{in}}{100+j50+z_{in}} 10V \\
 &= \left(\frac{100-j50}{100+j50+100-j50} \right) 10 = \left(\frac{100-j50}{200} \right) 10 = (0.5-j0.25) 10 \\
 &= 5-j2.5 \text{ volts. } = 5.59 e^{-j26.6^\circ}
 \end{aligned}$$

lossless

use power, NOT voltage

$$Z_{in} = 100-j50 = 111.8 e^{-j26.6}$$

what is P_{in} ?

$$I_{in} = \frac{\hat{v}(0)}{Z_{in}} = \frac{V_{in}}{Z_{in}} = \frac{5.59 e^{-j26.6}}{111.8 e^{-j26.6}} = 0.05$$

$$\begin{aligned}
 P_{in} &= \frac{1}{2} \operatorname{Re} [\hat{v}(0) \hat{I}(0)^*] = \frac{1}{2} \operatorname{Re} [(5-j2.5)(.05)] = \frac{1}{2} (.125) \\
 &= 0.125 \text{ watts.}
 \end{aligned}$$

$$\text{Power to one antenna} \quad .125/2 = 62.5 \text{ mW.}$$

$$P_A = \frac{1}{2} \operatorname{Re} \left[\hat{v}(0) \frac{\hat{v}^*}{Z_A^*} \right] = \frac{1}{2} |\hat{v}^*|^2 \operatorname{Re} \left(\frac{1}{Z_A^*} \right)$$

$$\begin{aligned}
 |\hat{v}|^2 &= \frac{2P_A}{\operatorname{Re} \left(\frac{1}{Z_A^*} \right)} = \frac{2(.0625)}{\operatorname{Re} (0.009 - j0.0027)} = \frac{2(.0625)}{.009} \\
 &= 13.88 \text{ volts}^2
 \end{aligned}$$

average voltage

$$|\hat{v}| = 3.72 \text{ volts.}$$

Simple line transformations.

If $Z_L = 0$ a short

$$Z_{IN}(z=0) = Z_0 \frac{j Z_0 \tan \beta l}{Z_0} = \boxed{j Z_0 \tan \beta l}$$

this looks like an inductor
 $j\omega L$

$$\beta = \frac{2\pi}{\lambda}$$

$$\text{for } l = \frac{\lambda}{4} \quad \beta l \rightarrow \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}.$$

$$\text{Then } Z_{IN}(z=0) = j Z_0 \tan \frac{\pi}{2} \rightarrow \infty \quad \underline{\text{this is an open}}$$

Suppose $Z_L = \infty$ an open

this looks like a capacitor $\frac{1}{j\omega C}$

$$Z_{IN}(z=0) = Z_0 \frac{\frac{Z_L}{j}}{j \frac{Z_L}{Z_0} \tan \beta l} = \boxed{-j \frac{Z_0}{\tan \beta l}} \rightarrow 0 \quad \underline{\text{a short}}$$

Note that these are only for a.c. impedances
NOT for d.c.

A quarter wavelength line transforms everything

$$\text{consider } \beta l \rightarrow \frac{\pi}{2} \quad Z_L = j\omega L$$

$$Z_{IN}(z=0) = Z_0 \frac{j\omega L + j Z_0 \tan \frac{\pi}{2}}{Z_0 + j(j\omega L) \tan \frac{\pi}{2}} \rightarrow Z_0 \frac{j Z_0}{j(j\omega L)} = -j \frac{Z_0^2}{\omega L}$$

looks like a capacitor.

This also holds true for any multiple of $\frac{\lambda}{2}$ plus $\frac{\lambda}{4}$.

$$Z_{IN}(z=0) = Z_0 \frac{j\omega L + j Z_0 \tan \beta l}{Z_0 + j(j\omega L) \tan \beta l}$$

