 


station lay-out

simplified power supply wiring



Dmm is electrically separate from common


three modes of measurement.

- single ended
- differential
- current

Frequency limited performance.

uses low frequency, very accurate dual slope integration

see p.418 Horowitz
capacitor voltage.

 


use digital counter to time this period

Signal generator

2 - outputs.

600 Ω output.

Pulse output
SYNC

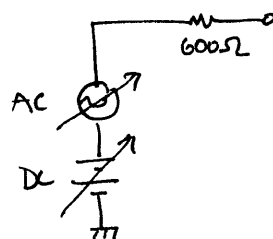

EEAP 243 Lecture #2.

Lab #1 done this week

Lab partners posted tonite if not assigned

Labs due tuesday next week. (where?)

announce in next class

→ Office hours Thursday 10-3

Lab questions assigned: 1, 4, 7 MUST BE TYPED


INCLUDE DATA LOG SHEET
(will be returned)

T.A. must initial data sheet (and date it)


make up labs MONDAY } evening 7-9 pm.
 TUESDAY }

Dmm



we don't have Keithley's
we have Flukes.

 

How to measure voltage & current

 

Power supplies :


 
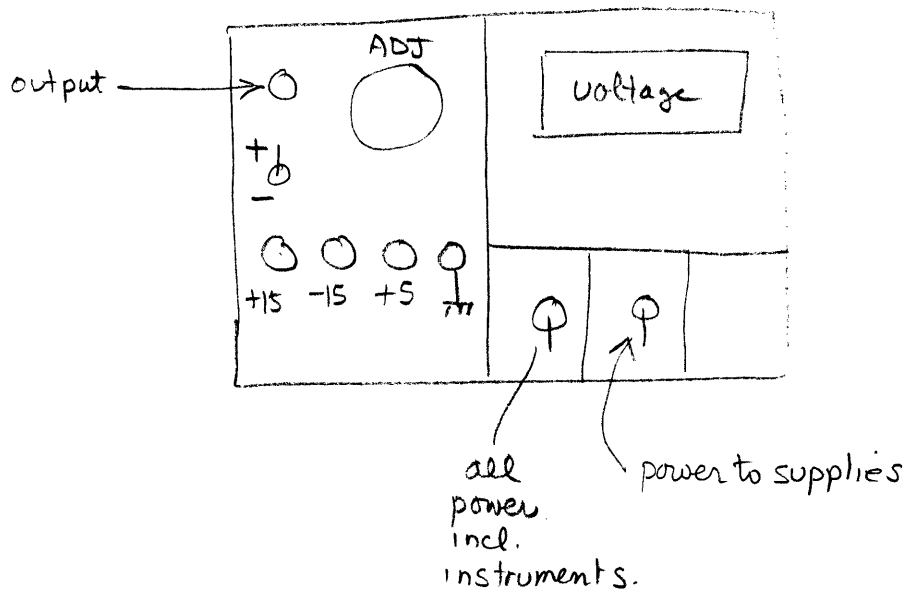


You will measure these voltages. Use DC power switch

No reading if com not connected!

Scope


basic background

 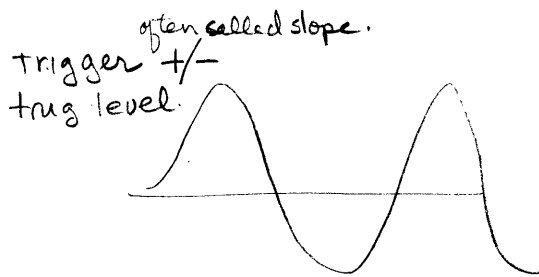 

CH1 } single channel.
CH2 }
DUAL } most used.
ADD }
X-Y }

POINT OUT VARIABLE SENSITIVITY, multiples sensitivity
TURN CLOCKWISE i.e. reduces it

MAGNIFY - don't push IN.

 

adjust to coupling you want.

adjust gnd to some
screen marking.

trigger slope $+/-$ } synchronizes oscillator with
level level input voltage level.

Bright Line should always be out.

Is a special automatic sweep.

if NO signal keeps screen display!

lab write-ups due by start of next lab - typically Tuesday.


resistors
(transparency)

capacitors
electrolytics
tantalum






can explode if you reverse polarity

disk ceramics

 

symbols used

 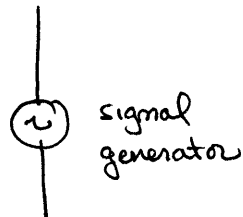 

EEAP 243

CIRCUITS LABORATORY

LABORATORY HANDBOOK

SPRING 1988

Copyright 1988
PROFESSOR F. MERAT
GLENNAN 515
368-4572

EEAP 243 COURSE GRADING POLICY


1. Each lab will be worth a maximum of four points.
A $\geq$ 3.5
B $\geq$ 2.5
C $\geq$ 1.5
D $\geq$ 1
F<1
2. Late labs will be deducted 1 point per day late to a maximum of three points to be deducted—any lab not handed in will count -3 points toward your final grade.
3. There will be no final.
4. All grades will be based upon points accumulated in the course through graded labs.
5. The final course grade will be based upon the following point distribution:
A $\geq$ 52.5
B $\geq$ 37.5
C $\geq$ 22.5
D $\geq$ 15
F<15
assuming that 15 labs will be assigned. If 15 labs are not assigned (very likely) the grade cutoff points will be reduced proportionately.
7. Lab writeups will consist of the data collected by the lab group PLUS the answers to assigned questions. The proper collection of the lab data will be worth one point; the answers to the lab questions will be worth three points.




Your grade will be based upon a strict interpretation of this point distribution and the above rules. There will be no exceptions without notes from the Dean's Office.

No student who has not passed EEAP 241 (or its equivalent) and is not concurrently enrolled in EEAP 242 will be allowed to take EEAP 243. The only exception will be students who have already taken EEAP 242 or its equivalent.


Lab requires two meters — work across

 

 
models of most instruments include internal resistances



resistors

 

 connect circuit on your proto board or just use clips.





ordinary diode




zener diode



  Boylestad and Nashelsky have a good explanation



AC measurements:

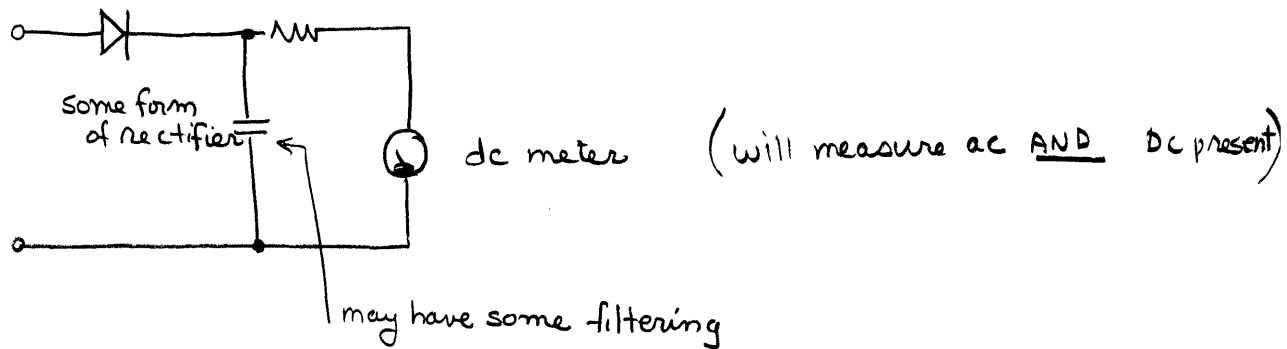

could be confusing

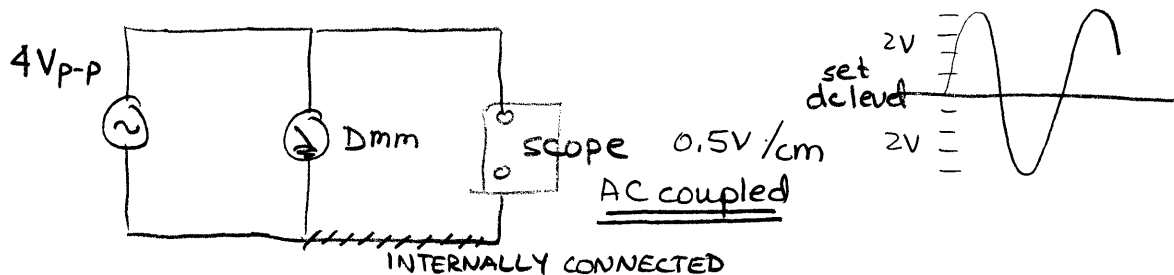


table 2-5

	<u>Vernier</u> signal generat	<u>range</u>	<u>time</u> [this is NOT critical]	<u>scope</u> (Volts Not cm)	<u>meter</u> (set to AC volts)
frequency ↓					

RMS Measurements

general

$$V_{RMS} = \sqrt{(AC)^2 + (DC)^2}$$

more technically:

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

For sinusoidal signals the above formula reduces to

$$\text{if } V(t) = V_m \cos \omega t$$

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

For signals of different frequencies


$$V_{L,RMS} = \sqrt{V_{f1,RMS}^2 + V_{f2,RMS}^2 + \dots + V_{fn,RMS}^2}$$

↑
one of these can be dc

Note that the rms value of a dc voltage is the dc voltage.

$$\text{For triangle } V_{RMS} = \frac{V_m}{\sqrt{3}}$$

for this lab

 


DC coupled

do for
sine
square
triangle
pulse

measure AC & DC components.

pulse is a little misleading

Part 4 KCL

 

LAY THIS OUT
BEFORE YOU
COME TO CLASS

Record tolerances
of your resistors

use superposition
loop equations, etc.

$$-10 + 12k(i_1 - i_4) + 5 = 0$$

$$-5 + 1.2M(i_2 - i_5) - 15 = 0$$

$$+15 + 15k(i_3 - i_6) = 0$$


$$15k(i_4) + 12k(i_4 - i_1) + 1.2k(i_4 - i_5) = 0$$

$$1.2k(i_5 - i_4) + 1.2M(i_5 - i_2) + 5.6k(i_5 - i_6) = 0$$


$$5.6k(i_6 - i_5) + 15k(i_6 - i_3) + 560i_6 = 0$$

6 equations in 6 unknowns.

Part 5 - Z of test equipment

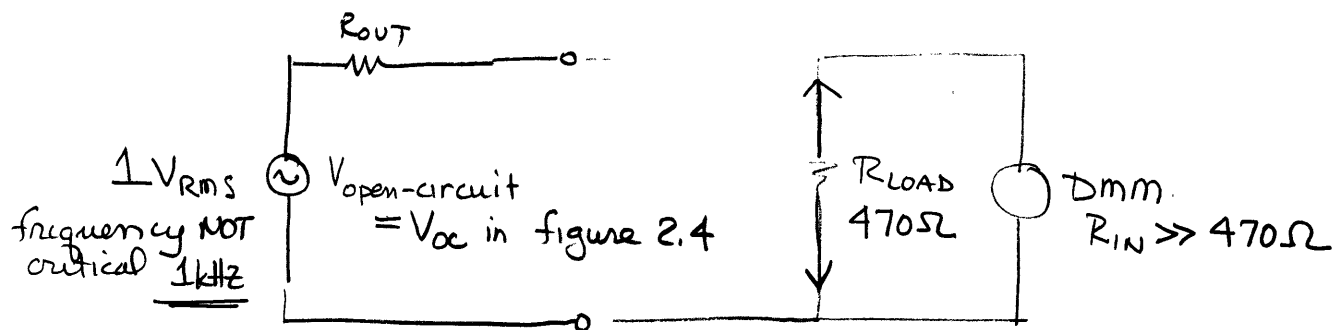

VOLTAGE DIVIDER

 

$R_{initially} = 10k\Omega$.

probably won't detect any differences until $R = 1m$ or $10m$


capacitors

marked with value in microfarads
or scientific notation in picofarads

$## \times 10^{\#}$


$$\therefore 333 = 33,000 \text{ pf} = .033 \text{ pf.}$$

 very important which way electrolytics go in a circuit




capacitors can explode if polarity is reversed

 rms voltages $V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$



$$V_{rms} = 2V.$$


$$\text{since } \sqrt{\frac{1}{T} \int_0^T 2^2 dt} = \sqrt{\frac{1}{T} 4t \Big|_0^T} = 2$$

 

$$V_{rms} = \sqrt{\frac{1}{2} \left[\int_0^1 (2)^2 dt + \int_1^2 (-2)^2 dt \right]}$$

$$= \sqrt{\frac{1}{2} 4 + \frac{1}{2} 4} = \sqrt{4} = 2$$

Add two together

 


$$V_{rms} = \sqrt{\frac{1}{2} \int_0^1 (4)^2 dt} = \sqrt{\frac{1}{2} \cdot 16} = 2\sqrt{2} \text{ volts.}$$

this is the basis for the formula

$$V_{rms} = \sqrt{V_{AC,rms}^2 + V_{dc}^2}$$

$$= \sqrt{4 + 4} = 2\sqrt{2}$$

Input impedance and time response.

 

for dc. $V_{0, \text{ideal}} = V_s \frac{R_2}{R_1 + R_2}$

$V_{0, \text{real}} = V_s \frac{R_2 \parallel R_{IN}}{R_1 + R_2 \parallel R_{IN}}$

if $R_1 = R_2 = R$ for $R_{IN} \gg R$ $V_0 \cong \frac{1}{2} V_s$


for $R_{IN} \ll R$ $V_0 \rightarrow 0$

to calculate R_{IN} , you want $R_{IN} \cong R$

$R_{IN, \text{meter}} \cong 10\text{M}$


$R_{IN, \text{scope}} \cong 1\text{M}$ $C_{IN, \text{scope}} = 28\text{pF}$

Is C negligible?

 

thevenized supply


$\Rightarrow$
Thevenize again

 

$$f_{\text{cutoff}} = \frac{1}{2\pi RC} = \frac{1}{2\pi (48 \times 10^3) (28 \times 10^{-12})} \cong$$

bare wires pick up a lot of noise because they act as antennas

coax is used to reduce noise

 


shield adds a lot of capacitance, possibly 50pf/foot.

a 6 foot length of cable is now 300 pf
+ 28 pf of scope.

$$f_{\text{cutoff}} = \frac{1}{2\pi(48 \times 10^3)(328 \text{ pf})} \approx 10 \text{ kHz, not very useful.}$$

improve by compensating probe.

 


$$\frac{V_{\text{measured}}}{V_T} = \frac{Z_{\text{scope}}}{R_T + Z_{\text{scope}}}$$

for the above conditions

$$\frac{V_{\text{measured}}}{V_T} \approx 0.95 \text{ at low frequencies}$$


$$\begin{aligned}
 f_{\text{cutoff}} &= \frac{1}{2\pi RC} \\
 &= \frac{1}{2\pi(1\text{M} \parallel 50\text{K})(300 + 28 \text{ pf})} \\
 &\approx 10.1 \text{ kHz}
 \end{aligned}$$

 time domain analysis - Consider a simple attenuator



independent of f


in reality we have

 

If $R_1 = R_2 = 1\text{ M}$ and $C_2 = 15\text{ pF}$.


$$f_{\text{cutoff}} = \frac{1}{2\pi(500 \times 10^3)(15 \times 10^{-12})}$$

 The way to extend the frequency response is to compensate the probe by bypassing it with a capacitance C_1 ,



if $R_1 = R_2$ the bridge will be balanced independent of frequency.

Now, what happens with probe

 

$$\frac{V_m}{V_T} = \frac{Z_s}{R_T + Z_s + Z_p} \quad \text{where} \quad Z_s = \frac{R_s}{1 + s R_s C_s} \quad Z_p = \frac{R_p}{1 + s R_p C_p}$$

$$= \frac{\frac{R_s}{1 + s R_s C_s}}{R_T + \frac{R_p}{1 + s R_p C_p} + \frac{R_s}{1 + s R_s C_s}} \quad \text{multiply through by} \quad \frac{1 + s R_s C_s}{1 + s R_s C_s}$$

$$= \frac{R_s}{R_T (1 + s R_s C_s) + R_p \left(\frac{1 + s R_s C_s}{1 + s R_p C_p} \right) + R_s}$$

Now, consider what happens if $R_p C_p = R_s C_s$

$$\Rightarrow \frac{R_s}{R_T (1 + s R_p C_p) + R_p + R_s}$$

$$= \frac{R_s}{R_s + R_p} \frac{R_s + R_p}{R_T (1 + s R_p C_p) + R_p + R_s}$$

voltage divider with no frequency dependence.

define $R_{eq} = R_s + R_p$

$$\frac{R_{eq}}{R_T (1 + s R_p C_p) + R_{eq}}$$

$$\text{but } R_p C_p = R_p C_p \frac{C_s + C_p}{C_s + C_p} = \frac{R_p C_s C_p + \overbrace{R_p C_p C_p}^{R_s C_s}}{C_s + C_p} = \frac{R_p C_s C_p + R_s C_s C_p}{C_s + C_p}$$

$$= (R_s + R_p) \left(\frac{C_p C_s}{C_p + C_s} \right)$$

↑
 C_{eq}

$$\therefore \frac{V_{\text{measured}}}{V_T} = \underbrace{\frac{R_s}{R_s + R_p}}_{\text{division factor}} \underbrace{\frac{R_{eq}}{R_T (1 + s R_{eq} C_{eq}) + R_{eq}}}_{H(s) \text{ frequency response factor}}$$

Suppose we set $R_p = 99 \text{ M}\Omega$

$$\text{then } C_p = \frac{R_s C_s}{R_p} = \frac{1 \text{ m} (328 \text{ pf})}{99 \text{ m}} = 3.31 \text{ pf}$$

$$\therefore \frac{V_{\text{measured}}}{V_{\text{in}}} = \frac{1}{1 + 99} = \frac{1}{100}$$

$$R_{eq} = R_s + R_p = 1 \text{ m} + 99 \text{ m}$$

$$C_{eq} = \frac{C_s C_p}{C_s + C_p} = \frac{(328)(3.31)}{328 + 3.31} = 3.28 \text{ pf.}$$

$$H(s) = \frac{R_{eq}}{R_T + s R_T R_{eq} C_{eq} + R_{eq}} = \frac{R_{eq}}{R_T + R_{eq} + s R_T R_{eq} C_{eq}}$$


$$= \frac{R_{eq} / (R_T + R_{eq})}{1 + s \left(\frac{R_T R_{eq}}{R_T + R_{eq}} \right) C_{eq}}$$

$$H(0) \rightarrow \frac{R_{eq}}{R_T + R_{eq}} = \frac{100 \text{ m}}{48 \text{ K} + 100 \text{ m}} \approx .9995$$

$$f_{\text{cutoff}} = \frac{1}{2\pi \left(\frac{R_T R_{eq}}{R_T + R_{eq}} \right) C_{eq}} \approx \frac{1}{2\pi (48 \text{ K})(3.28 \text{ pf})} \approx 970 \text{ kHz.}$$

which is actually better than scope with no coax.

 Consider the response to a unit step in voltage , 



by Kirchhoff's Law $V = \frac{q}{C_1} + \frac{q}{C_2} = \frac{C_1 + C_2}{C_1 C_2} q$.

at $t = 0^+$

$$v_o(0^+) = \frac{q}{C_2} = \frac{\frac{C_1 C_2}{C_1 + C_2} V}{C_2} = \frac{C_1}{C_1 + C_2} V$$

$\therefore$ the initial output voltage is determined by the capacitors.



the final output voltage will be determined by the resistors

$$v_o(\infty) = \frac{R_2}{R_1 + R_2} V$$


For the circuit to be compensated $v_o(0^+) = v_o(\infty)$ or any other time in between. Then

$$\frac{C_1}{C_1 + C_2} V = \frac{R_2}{R_1 + R_2} V \quad \text{or} \quad C_1 R_1 + C_1 R_2 = C_1 R_2 + C_2 R_2$$


$$\text{or} \quad R_1 C_1 = R_2 C_2.$$

  

 If we include the source impedance R_s we get.



 break this connection for the moment
since the capacitors alone determine $v_o(0^+)$ and the
resistors alone determine $v_o(\infty)$



If $R_s \ll (R_1 + R_2)$ usually true then the input waveform will have
a time constant $\tau \cong R_s C'$ where $C' = \frac{C_1 C_2}{C_1 + C_2}$.

If the input were directly connected to the output, i.e. the input of the
scope the time constant would be

$$\tau' \cong R_s C_2 \quad \text{connected straight through.}$$

so, the improvement in rise-time is $\frac{\tau'}{\tau} = \frac{R_s C_2}{R_s C'} = \frac{C_2 (C_1 + C_2)}{C_1 C_2}$

problem $\rightarrow$

$$= \frac{C_1 + C_2}{C_1} > 1$$

$\therefore$ probe decreases timeconstant


However, this is at the expense of signal level since

$$\frac{V'(\infty)}{V(\infty)} = \frac{\frac{R_2}{R_s + R_2}}{\frac{R_2}{R_1 + R_2 + R_s}} = \frac{R_1 + R_2 + R_s}{R_2 + R_s} \approx \frac{R_1 + R_2}{R_2}$$

$\therefore$ probe decreases signal by $\frac{R_2}{R_1 + R_2}$.

diodes	74
power diodes	92
zener diodes	74-82

Figure 4.1

 


can set your scope to get 8 divisions across using variable adjust on time base

$$\frac{360}{8} = 45^\circ \text{ / div.}$$

use DMM to measure series L of inductor !

don't do part 2,

 

$$Z_{11} = j\omega L \parallel \left(R + \frac{1}{j\omega C}\right)$$

$$= \frac{(j\omega L) \left(R + \frac{1}{j\omega C}\right)}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\frac{V_B}{V_S} = \frac{Z_{11}}{Z_{11} + R_S} = \frac{(j\omega L) \left(R + \frac{1}{j\omega C}\right) \frac{1}{R + j\omega L + \frac{1}{j\omega C}}}{(j\omega L) \left(R + \frac{1}{j\omega C}\right) \frac{1}{R + j\omega L + \frac{1}{j\omega C}} + R_S}$$


$$= \frac{(j\omega L) \left(R + \frac{1}{j\omega C}\right)}{(j\omega L) \left(R + \frac{1}{j\omega C}\right) + R_S \left(R + j\omega L + \frac{1}{j\omega C}\right)}$$

$$\frac{V_{OUT}}{V_S} = \frac{(j\omega L) \left(R + \cancel{\frac{1}{j\omega C}}\right)}{(j\omega L) \left(R + \frac{1}{j\omega C}\right) + R_S \left(R + j\omega L + \frac{1}{j\omega C}\right)} \left(\frac{\cancel{\frac{1}{j\omega C}}}{\frac{1}{j\omega C} + R}\right)$$

$$= \frac{\frac{\omega L}{\omega C}}{R_S R + \frac{j\omega L}{j\omega C} + R j\omega L + R_S j\omega L + \frac{R_S}{j\omega C}}$$


$$= \frac{\frac{L}{C}}{R_S R + \frac{L}{C} + j \left(R\omega L + R_S \omega L - \frac{R_S}{\omega C}\right)}$$


$$\left| \frac{V_{OUT}}{V_S} \right|$$

 

$$\angle \frac{V_{OUT}}{V_S}$$

$$\angle 0 - \angle +90$$


 


 

$$\frac{V_B}{V_s} = \frac{\frac{1}{j\omega C}}{R_s + j\omega L + \frac{1}{j\omega C}}$$

$$\left| \frac{V_B}{V_s} \right| = \frac{\left| \frac{1}{j\omega C} \right|}{\left| R_s + j\left(\omega L - \frac{1}{\omega C}\right) \right|}$$
  
$$\angle \frac{V_B}{V_s} = \angle \frac{1}{j\omega C} - \angle R_s + j\left(\omega L - \frac{1}{\omega C}\right)$$




Given that

$$H(s) = \frac{10s}{(1+s)(1+\frac{s}{10})}$$


plot $|H(j\omega)|$ and $\angle H(j\omega)$

Solution:

$$20 \log_{10}|H(j\omega)| = 20 \log_{10}(10) + 20 \log_{10}|\omega| - 20 \log_{10}|1+j\omega| - 20 \log_{10}|1+\frac{j\omega}{10}|$$

 


which sum up to

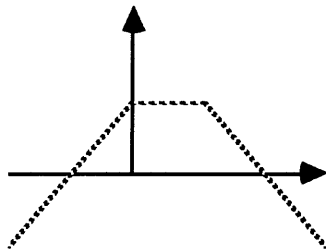


Similarly, the phases are

$$\angle H(j\omega) = \angle 10 + \angle j\omega - \angle(1+j\omega) - \angle(1+\frac{j\omega}{10})$$

which can be graphically represented as






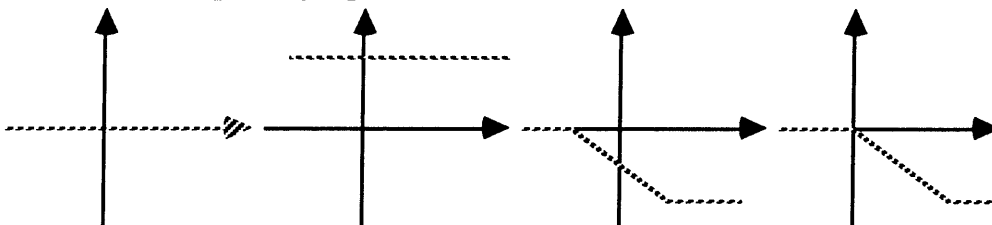


and summed to give

 

Fourier Analysis


periodic signals

  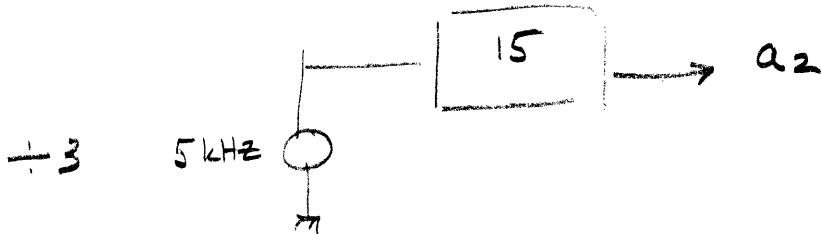 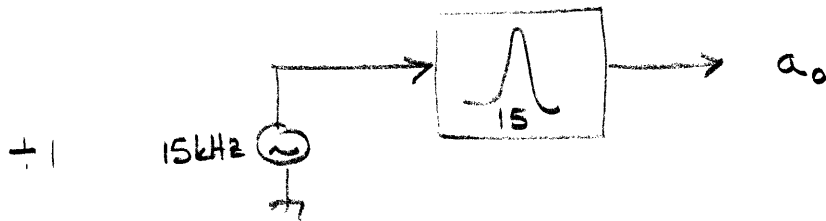 

...

doesn't give phase
just magnitude

Part 3 resonance.


 


$$Z_{||} = \frac{1}{j\omega C} \parallel j\omega L = \frac{j\omega C \cdot \frac{1}{j\omega L}}{\frac{1}{j\omega C} + j\omega L}$$

$$= \frac{C/L}{j(\omega L - \frac{1}{\omega C})}$$


$$\frac{V_{OUT}}{V_{IN}} = \frac{Z_{||}}{Z_{||} + R} = \frac{\frac{C/L}{j(\omega L - \frac{1}{\omega C})}}{\frac{C/L}{j(\omega L - \frac{1}{\omega C})} + R}$$
  
$$\frac{V_{OUT}}{V_{IN}} = \frac{C/L}{C/L + Rj(\omega L - \frac{1}{\omega C})} = \frac{C/LR}{\frac{C}{LR} + j(\omega L - \frac{1}{\omega C})}$$



measure L, R C using digital LRC meter

 A system has the pole-zero diagram shown below.




- (a) Sketch the magnitude of the system frequency response for K very small, i.e. near the $j\omega$ axis.
- (b) Indicate what happens to your answer for (a) as K becomes larger, i.e. the poles move away from the $j\omega$ axis.

Solution:


(a)
 
$$H(j\omega) \approx K \frac{j\omega - 0}{(j\omega - s_1)(j\omega - s_2)} \rightarrow K \frac{\omega}{(\omega_0 + \omega)(\omega_0 - \omega)} = K \frac{\omega}{\omega_0^2 - \omega^2}$$



- (b) as K increases the peak diminishes and broadens

real transformers

 


typically only specified as rms ac voltage for a given secondary current.

→ what is color code?

- RED
- YELLOW (CT)
- GREEN
-
-

half-wave rectifier

 

diode characteristics

max. current diode can handle

$$I_{dc} = \text{average load current} = \frac{V_{dc}}{R_L} \quad (\text{usually listed as } I_0 \text{ on datasheet})$$

1N4001 has an I_0 of 1A.


$$\text{If } R_L = 10\Omega \text{ in above bridge rectifier, } I_{dc} = \frac{5.66}{10\Omega} \approx 0.56 \text{ A which is OK}$$

Sections 1.25 - 1.28 in Horowitz


on negative half cycle diode is off and must withstand the peak voltage without conducting current.

maximum reverse voltage is called PIV or PRV.

Full-wave rectifier

 

When D1 is on, D2 is off and vice versa.

 

$= \frac{1}{2} V_{peak}$ (due to center tap)

$$\frac{\sqrt{2}}{2} (12.6) \approx 8.91 \text{ volts.}$$


dc is now $\frac{2}{\pi} V_{peak}$ since twice as much dc to average.

$$\frac{2}{\pi} (\sqrt{2} \cdot 12.6) = 5.67 \text{ volts.}$$

if $R_L = 10\Omega$ as before $I_{dc} = \frac{5.67}{10\Omega} = 0.567 \text{ A}$


peak across each diode is only $\frac{1}{2}$ as much

 but each diode need only be $\frac{1}{2}$ this since each diode's current looks like



how about PIV of each diode



$$PIV = \sqrt{2} (12.6)$$

 


apply KVL around this loop!

most popular rectifier circuit — bridge rectifier

  
full peak voltage of half-wave rectifier
higher average value of full wave.



positive half-cycle
KVL for diode

 

V_{OUT}
(across R_L)

 

$$\text{If } R_L = 10\Omega \quad I_{dc} = \frac{11.3 \text{ volts}}{10\Omega} = 1.13 \text{ A.}$$

but each diode only conducts $\frac{1}{2}$ cycle so its ratings drop to $\frac{1.13}{2} \text{ A.}$





use KVL around loop shown above

$$V_{peak} - PIV - 0 = 0$$

$$\therefore PIV = V_{peak}.$$

capacitor input filter

4

   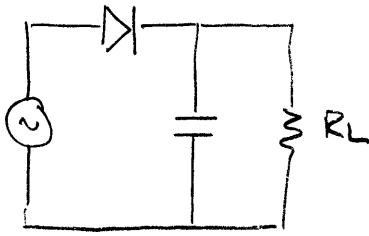

for a capacitor $C = \frac{Q}{V}$ or $V = \frac{Q}{C}$.

from the graph $V_{ripple} = V_1 - V_2 = \frac{Q_1}{C} - \frac{Q_2}{C} = \frac{Q_1 - Q_2}{C}$

C does not change


Now: $\frac{V_1 - V_2}{T_1 - T_2} = \frac{1}{C} \frac{Q_1 - Q_2}{T_1 - T_2}$

If $R_L C$ is very large $T_1 - T_2 \approx T$, the period of the ripple.

$$\frac{V_1 - V_2}{T} = \frac{1}{C} \frac{Q_1 - Q_2}{T} = \frac{1}{C} I$$


$$\therefore V_{ripple} = V_1 - V_2 \approx \frac{I}{C} T = \frac{I}{fC}$$

capacitors

 

capacitors can explode if polarity is reversed!


Zener diode regulation

 



(equals I_Z)
$$I_S = \frac{V_S - V_Z}{R_S}$$

if $V_Z = 0$
$$I = \frac{V_S}{R_S}$$

if $I_Z = 0$
$$V_Z = V_S$$

 


Zener regulator

  

$$V_T = \frac{R_L}{R_S + R_L} V_S$$

$$R_T = R_S \parallel R_L$$

 

assume diode is working.
(broken down)

R_s is for current limiting


$$I_s = \frac{V_s - V_z}{R_s}$$

$$I_L \approx \frac{V_z}{R_L}$$

$$\therefore I_z = I_s - I_L$$

Zener dropout point


(see section 2.04)
of Horowitz

 

whenever $I_z \rightarrow 0$ regulation is lost,


1.30 diode clamps

rectifying differentiator

 


has a 0.6 volt loss !

bias diode

 


diode switching.


 



diode clamps.

standard for
all CMOS
circuits

 

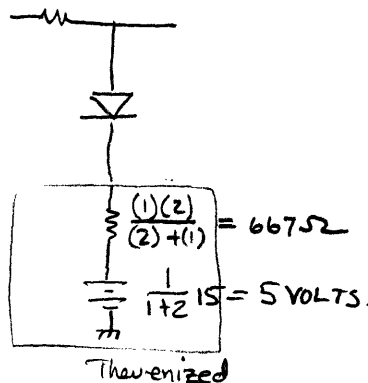 if $V_{IN} > 5.0 + 0.7$ volts output saturates at 5.7 volts.



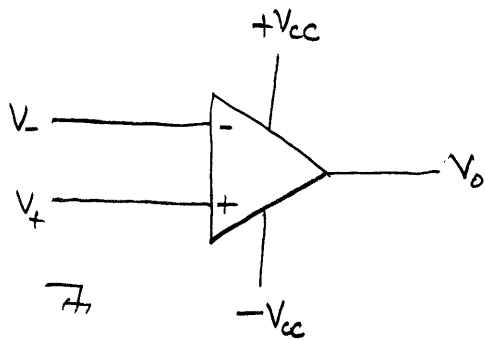


most op-amps require + and - power supplies

$$V_{out} = A(V_+ - V_-)$$


$$\text{or } \frac{V_o}{A} = V_+ - V_-$$

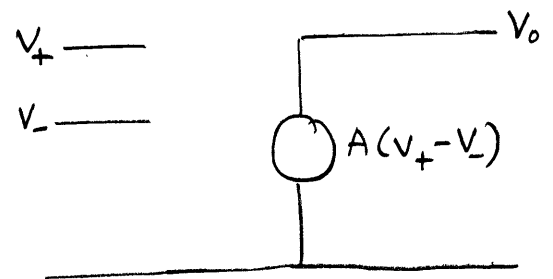normal assumptions $A \rightarrow \infty$
 $I_{os} \rightarrow 0$
 $V_{os} \rightarrow 0$
 these are related to Horowitz's golden rules.



Analyzed in 3.04 Horowitz
with unity feedback

unity gain voltage follower

 

if $I_L = \frac{V_o}{R_L}$ is not large
 the output voltage = V_+


$$V_{out} = A(V_+ - V_-) \quad \text{but } V_- = V_{out}$$

$$V_{out} = A(V_+ - V_{out})$$

$$V_{out} + A V_{out} = A V_+$$

$$\frac{V_{out}}{V_+} = \frac{1+A}{A} \approx 1 \quad \text{if } A \text{ is large.}$$

without feedback

 


ΔV_{in} linear region may be only a few millivolts.

If $A = 10^5$ and $V_{OUT} = 30$ volts

then $\Delta V_{in} = \frac{30}{100 \times 10^3} = 0.3 \text{ mV}$ (and usually less)

with feedback

 

in this circuit

$$V_{OUT} = A(V_+ - V_-)$$

using superposition

$$V_- = \frac{R_{IN}}{R_{IN} + R_F} V_{OUT} + \frac{R_F}{R_{IN} + R_F} V_{IN}$$

$$\therefore V_- = \frac{R_{IN} V_{OUT} + R_F V_{IN}}{R_{IN} + R_F}$$


but $V_{OUT} = A(V_+ - V_-) = -AV_-$ since $V_+ = 0$

$$\frac{V_{OUT}}{-A} = \frac{R_{IN}}{R_{IN} + R_F} V_{OUT} + \frac{R_F}{R_{IN} + R_F} V_{IN}$$

$$\therefore V_{OUT} \left(-\frac{1}{A} - \frac{R_{IN}}{R_{IN} + R_F} \right) = \frac{R_F}{R_{IN} + R_F} V_{IN}$$


$$\frac{V_{OUT}}{V_{IN}} = \frac{-A R_F}{(R_{IN} + R_F) + R_{IN} A} \rightarrow -\frac{R_F}{R_{IN}}$$

Figure 2:

 

AC: $20 V_{p-p}$
DC: 0 (supposedly).

Figure 3:

 


power lines radiate

unstable w/o
decoupling capacitors.
for LF357 due to large
input impedance

simply want an ac short to
ground.

3.08 precautions with op-amps


clipping

 

if $V_{in} = +10$ $V_{out} = -15$, etc.

suppose $V_{in} = 2V_{DC} + 1V \cos \omega t$. OK

 but if either ac or dc component increases
clipping occurs.




- ① Vary V_{DC} to see V_{out}
- ② set $V_{DC} = 0$
increase V_{AC} to see
what happens.
- ③ record for $V_{in} = 5V_{p-p}$.

problems with real op-amps

- p.113 1. $I_{os} \neq 0$ already saw this
- p.107 2. finite slew rate $\left| \frac{dV}{dt} \right| < \text{constant}$
- p.107 3. finite GBW
- p.112. 4. $V_{os} \neq 0$

slew rate p.107.

 


slew rate = $\frac{\Delta V}{\Delta t}$.
record both.

Interesting problems with real op-amps

1. $V_{os} \neq 0$
2. $I_{os} \neq 0$ ← already saw this.
3. finite GBW
4. finite slew rate

finite GBW p. 107
mc1741 data sheet.

 

$$\text{gain}_{\text{db}} = 20 \log_{10} \left(\frac{V_{\text{OUT}}}{V_{\text{IN}}} \right)$$

for example. $\times 1000$ gain

$$G = 20 \log_{10}(10^3) = 60 \text{ dB.}$$

→ about 1 kHz BW.


if $G = 40 \text{ dB}$ ($\times 100$ gain)

→ about 10 kHz BW


$G = 20 \text{ dB}$ ($\times 10$)

→ about 100 kHz BW.


circuit

 

Thevenize input:

 

 find this for
10, 100, 1k, open
for LM741 and
LF357



$$\text{gain} = \frac{100k}{0.1k} = 1000$$

input is zero
output $\neq 0$.
measure for both. LM741 and LF357


$$V_{os} \approx \frac{V_B(\text{dc})}{1000}$$

trim to zero using special circuit

read history of op-amp on p.115.

non-inverting amplifier

0.1

 


$$V_o = A(V_+ - V_-) = A\left(V_{in} - \frac{R_1}{R_1 + R_2} V_o\right).$$

$$V_o \left(1 + \frac{AR_1}{R_1 + R_2}\right) = A V_{in}$$


$$\frac{V_o}{V_{in}} = \frac{A}{1 + \frac{AR_1}{R_1 + R_2}} \rightarrow \frac{R_1 + R_2}{R_1} \quad \text{as } A \rightarrow \infty$$

$$\approx 1 + \frac{R_2}{R_1}$$

see p. 95 Horowitz

 

 if source is ac coupled you must provide a resistance to ground for I_{os} , otherwise the amp will not work.



We can use superposition to analyze this circuit

If $V_1 = 0$ then we have an ordinary inverting op-amp given by

$$V_o = -\frac{R_2}{R_1} V_2$$

The analysis for $V_2 = 0$ is a little more complex.

$$\text{If } V_2 = 0, \text{ then } V_- = \frac{R_1}{R_1 + R_2} V_o$$

$$V_+ = \frac{R_4}{R_4 + R_3} V_1$$

$$V_o = A (V_+ - V_-)$$

$$V_o = A \left(\frac{R_4}{R_4 + R_3} V_1 - \frac{R_1}{R_1 + R_2} V_o \right)$$

$$V_o + \frac{A R_1}{R_1 + R_2} V_o = \frac{A R_4}{R_3 + R_4} V_1$$

$$\left(\frac{R_1 + R_2 + A R_1}{R_1 + R_2} \right) V_o = \left(\frac{A R_4}{R_3 + R_4} \right) V_1$$

$$V_o = \frac{A R_1 + A R_2}{A R_1 + R_1 + R_2} \frac{R_4}{R_3 + R_4} V_1$$

and as $A \rightarrow \infty$

$$V_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_1$$

by superposition

$$V_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_1 - \frac{R_2}{R_1} V_2$$

$$V_o = \frac{R_2}{R_1} \left[\frac{R_1}{R_2} \left(\frac{R_1 + R_2}{R_3 + R_4} \right) V_1 - V_2 \right]$$

$$V_o = \frac{R_2}{R_1} \left[\left(\frac{R_1 + R_2}{R_2} \right) \left(\frac{R_4}{R_3 + R_4} \right) V_1 - V_2 \right]$$

Now, if the coefficient of V_1 is 1

$$V_o = \frac{R_2}{R_1} [V_1 - V_2]$$


this is a differential amplifier whose output depends upon the difference between the inputs. For $\frac{R_1 + R_2}{R_2} \frac{R_4}{R_3 + R_4} = 1$

$$\text{we get } \frac{R_1 + R_2}{R_2} = \frac{R_3 + R_4}{R_4}$$

$$\text{or } \frac{R_1}{R_2} + 1 = \frac{R_3}{R_4} + 1$$

The requirement is that $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

 The input current at the non-inverting input depends upon R_3 and R_4 . (Assuming I_{os} is very small). On the other hand the input current at the inverting input is dependent upon R_1 and V_1 . This is undesirable in high-performance systems where we want R_{in} to be always very large. Consequently we will usually precede each input by a non-inverting amplifier.



Experimental Procedures

3

ideal amplifier only responds to $(V_2 - V_1)$

real amplifiers also have a small dependence on the individual input voltages

A_{cm} common-mode

A_{dm} difference-mode

$$V_{icm} \triangleq \text{average of the two inputs} = \frac{V_1 + V_2}{2}$$

$$V_{idm} = \text{difference of the inputs} = V_1 - V_2$$

An amplifier's output is thus given by

$$V_o = A_{cm} V_{icm} + A_{dm} V_{idm}$$

$$= A_{cm} \frac{V_1 + V_2}{2} + A_{dm} (V_1 - V_2)$$

$$= \left(\frac{A_{cm}}{2} + A_{dm} \right) V_1 + \left(\frac{A_{cm}}{2} - A_{dm} \right) V_2$$

 

with two constants we can represent any two coefficients

In a real-application we want A_{cm} to be as small as possible

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

A very good amp will have CMRRs greater than 100db.


how to generate differential and common mode signals.



T1 generates a differential mode signal between A and B.


T2 generates a common mode (common to A and B) voltage at A and B; The 150 ohm resistor provides a ground path for T2.

technically

 


comparator — determine which of two signals is larger
 — know when a signal exceeds a given threshold.

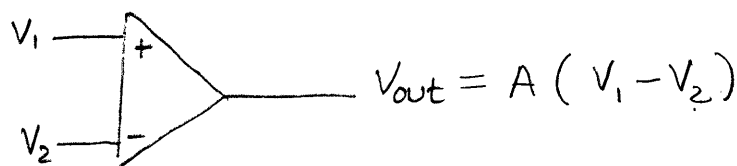
simplest comparator — high gain differential amplifier




if $V_2 = 0$

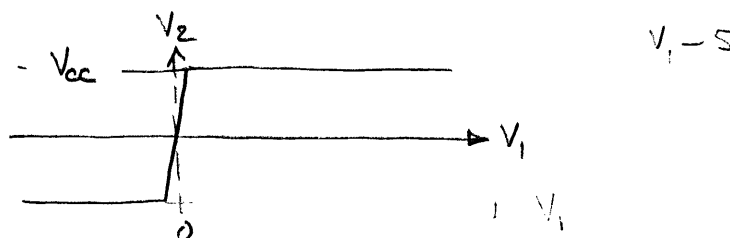


$V_2 \neq 0, V_2 > 0$

 

$V_2 < 0$

 

lab circuit

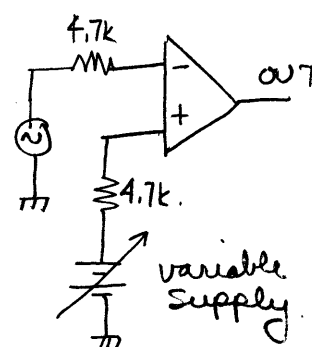



excellent for alarms!

op-amps are usually not good — use specialized IC chips instead
 i.e., LM311
 with better output circuits


Never use negative feedback — unstable with negative feedback.

 need high gain for comparator
 lower gain reduces comparator action,



 


problems with noise :

 

say you have a 5V input with 0.1 volt noise

 
How to eliminate noise — feedback to
get hysteresis



POSITIVE FEEDBACK!

Figures 3.54, 3.55, 3.56 are very good.

not for above diagram

 


Examples:
for Schmitt
triggers

$$V_{in} = 0 \Rightarrow$$

$$V_{out} = +15$$

suppose $R_2 = R_3$ then $V_+ = 7.5$ volts,
forcing $V_{out} = +15$

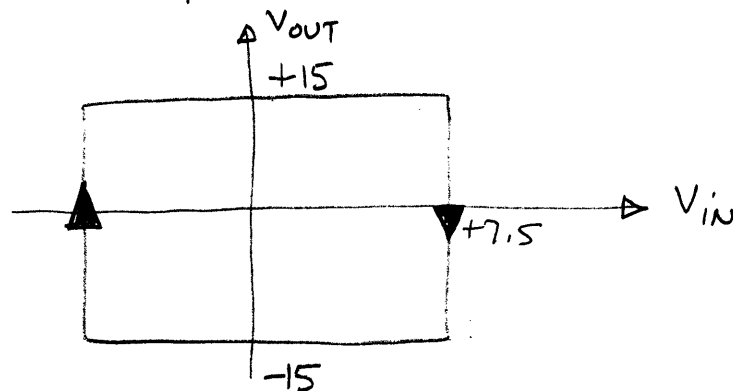If the input voltage rises to $+7.5$ no change in V_{out}
When input rises to $+7.50015$ output switches to $-15V$
and V_+ changes to -7.5 volts, voltage must drop
to below -7.5 volts, i.e. -7.50015 before the
output switches.




what are the
upper and lower
trigger points
set by?


$$\left(\frac{2.2}{10+2.2} \right) 15 = \frac{2.2}{12.2} 15$$

$$\approx 2.7 \text{ volts.}$$



Sample calculation

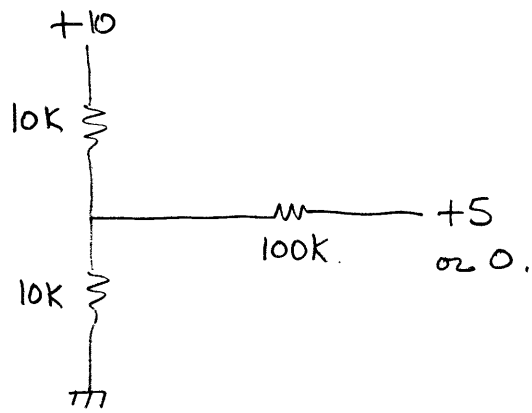



use superposition

 

$\Rightarrow$


 
 


$\Rightarrow$

  

$$V_+ = \frac{9.09}{10 + 9.09} (10) = 4.76$$
  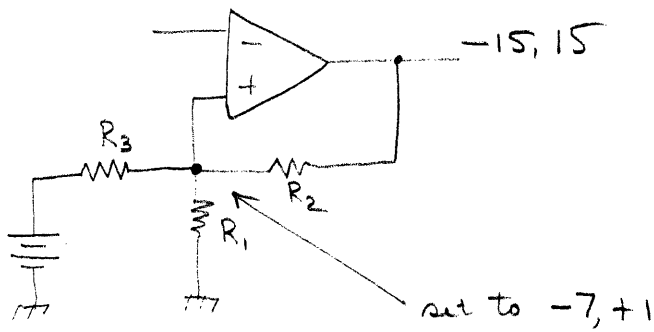
$$V_+ = \frac{5}{100 + 5} (5) = \frac{5}{105} (5) = 0.24V$$




pick $R_1 = 6.8k$

$$\text{Then } \left(\frac{6.8}{6.8 + R_2} \right) 15 = 7$$

$$R_2 = \frac{(6.8)(15)}{7} - 6.8 = 14.57 - 6.8 = 7.7k$$

$\Rightarrow$ pick $R_1 = 6.8k$

$$R_2 = 7.5k$$


 


$$\text{This gives } \frac{6.8}{6.8 + 7.5} 15 = 7.13 \text{ volts}$$

Set $V = -7.13 \text{ volts}$

$$R_3 = \frac{+1 - (-7.13)}{1.720 \text{ mA}}$$
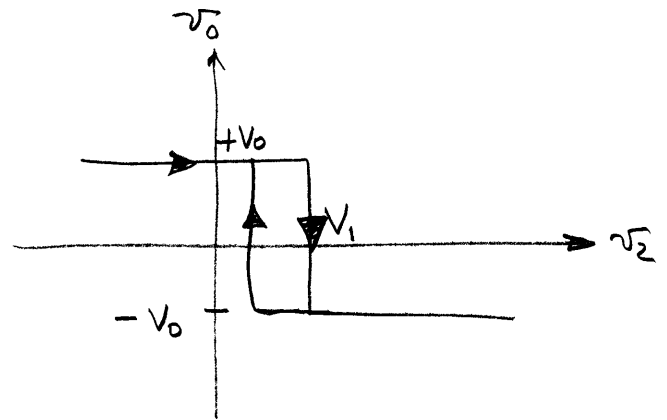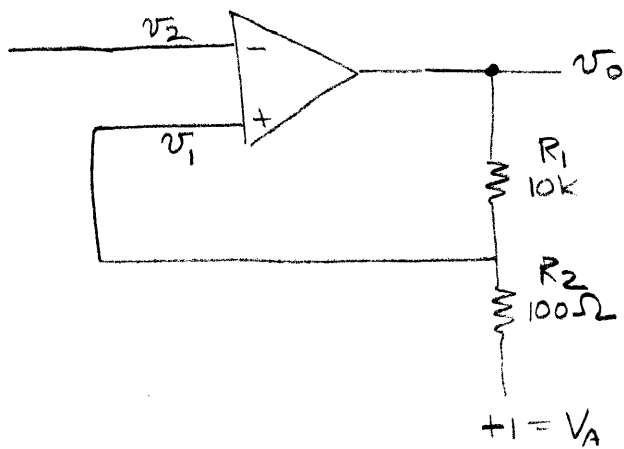
$$= \frac{8.13}{1.720 \text{ mA}} = 4.73k$$



$$v_0 = A v_2$$

feedback gain

$$T = - \frac{R_2 A v}{R_1 + R_2}$$

Let $v_0 = +V_0$


$$v_1 = V_A + \frac{R_2}{R_1 + R_2} (V_0 - V_A) \equiv V_1$$

notice that if v_2 is increased v_0 remains constant at V_0 and $v_1 = V_1$ until $v_2 = V_1$.


At this threshold, the output switches to $v_0 = -V_0$

$$v_1 = V_A - \frac{R_2}{R_1 + R_2} (V_0 + V_A) \equiv V_2 < V_1$$

 difference between V_2 and V_1 is the hysteresis:



Hybrid- π transistor model.

 


β_{dc} dc beta

β_o ac beta

r_{π} input resistance

$$g_m = \frac{|I_c|}{25 \text{ mV}}$$

$\beta \approx$ independent of I_c .

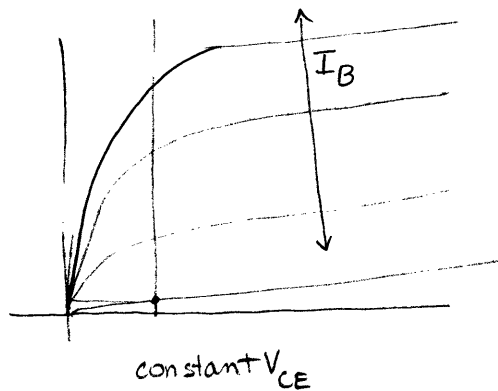


$$\beta_{dc} = \frac{I_c}{I_B}$$

depends upon
where Q-point
is located.

$$\left\{ \beta_o = \beta_{Ac} = \frac{\Delta I_c}{\Delta I_B} \right.$$

DC analysis

 


$$I_C = 1mA \text{ or } I_C = 100mA.$$

$$I_B = \frac{V_B - 0.7}{R_B}$$

$$\therefore \beta_{DC} = \frac{I_C}{I_B} = \frac{I_C R_B}{V_B - 0.7}$$

AC analysis:

 

dc bias does not change so r_{π} does not change.

dc bias circuit not shown.

$$V_B \approx \frac{10}{101} V_A \quad \text{irregardless of } R_S \text{ or } R_B \text{ or } r_{\pi} \quad \text{since } 10\Omega \text{ is so small.}$$

$$V_B = \frac{V_A}{101}$$

If $R_S = 0$

$$V = V_B$$

$$V_F = - (g_m V) (r_o \parallel R_L) \approx R_L \text{ since } r_o \gg R_L$$

$$V_F \approx - g_m \frac{V_A}{101} R_L = - g_m r_{\pi} \left(\frac{V_A}{101} \right) \frac{R_L}{r_{\pi}} = - \beta_{AC} \left(\frac{V_A}{101} \right) \frac{R_L}{r_{\pi}}$$

If $R_S = 4.7K$.

$$V = V_B \frac{r_{\pi}}{r_{\pi} + 4.7K}$$

$$V_F \approx - (g_m) \frac{V_A}{101} \left(\frac{r_{\pi}}{r_{\pi} + 4.7K} \right) R_L = - \beta_{AC} \left(\frac{V_A}{101} \right) \frac{R_L}{r_{\pi} + 4.7K}$$

$$\therefore \left[\frac{V_F}{V_A} = - \frac{\beta_{AC}}{101} \frac{R_L}{r_{\pi} + R_S} \right]$$

unknowns are β and r_{π} .

$$- \underbrace{\frac{101}{R_L} \frac{V_F}{V_A}}_{\text{call this } K} = \frac{\beta_{AC}}{r_{\pi} + R_S}$$

$$K_1 = \frac{\beta_{AC}}{r_{\pi}}$$

$$K_2 = \frac{\beta_{AC}}{r_{\pi} + 4.7k}$$

solve for β_{AC} $r_{\pi} K_1 = \beta_{AC} = K_2 (r_{\pi} + 4.7k)$

$$r_{\pi} K_1 = r_{\pi} K_2 + (4.7k) K_2 ,$$

$$r_{\pi} (K_1 - K_2) = (4.7k) K_2$$


$$r_{\pi} = \frac{(4.7k) K_2}{K_1 - K_2} .$$

Part 2

151



distortion

, adjust V_{gen} to get V_F shown below

 

adjust the scale factor and variable sensitivity so that both waveforms ~~are~~ ^{have} identical amplitudes subtract the waveforms and record.

Part 3

  


simple ac analysis

$$V = V_{IN} \frac{r_{\pi}}{(\beta+1)R_E + r_{\pi}}$$

$$V_{OUT} = (g_m V) R_C = \frac{g_m V_{IN} r_{\pi}}{(\beta+1)R_E + r_{\pi}} \cdot R_C = \frac{\beta R_C}{(\beta+1)R_E + r_{\pi}} V_{IN}$$
 
$$\boxed{\frac{V_{OUT}}{V_{IN}} = \frac{\beta R_C}{(\beta+1)R_E + r_{\pi}} \approx \frac{R_C}{R_E}}$$




- ① do dc measurements, no ac
- ② do ac measurements
- ③ now $R_L \rightarrow 4.7k$ measure ac out.
- ④ $R_L \rightarrow \infty$, $R_S \rightarrow 27k$ measure at point H
- ⑤ measure $\frac{V_{OUT}}{V_{IN}}$ for $V_{IN} = 1, 2, 3, 4 V_{p-p}$.

cutoff & saturation


curve tracer.


readouts

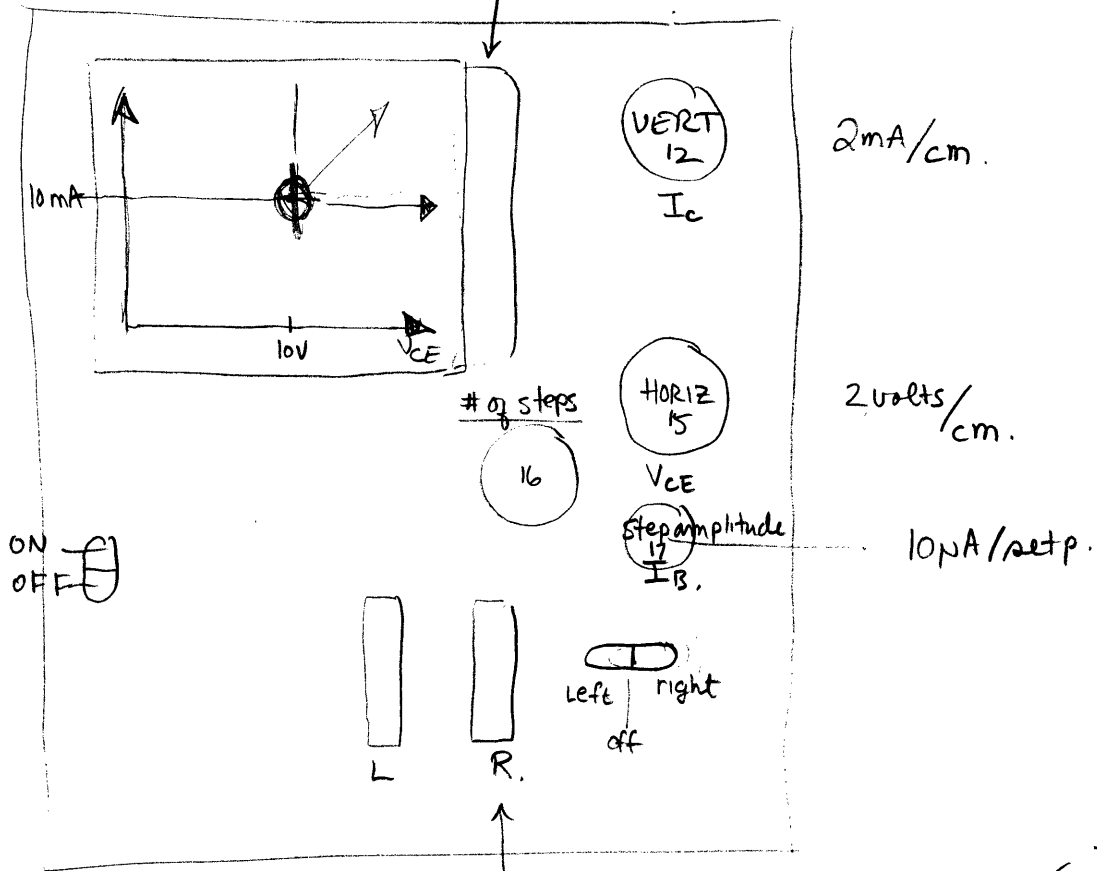

your transistor.

mention this.

 

 

FIRST bad method


measure C, D, I, J resistance to ground — BAD, pick up power supply voltages.

disconnect power supplies and ground H and E — re-measure.


characteristics

SECOND bad method

(a) TOO SMALL To measure ac current

 


(b)

 


active

THIRD bad method (passive)

 

correct method.


3

 

measure dc values once

measure ac values
for $R_L = \infty$
4.7k
470
47

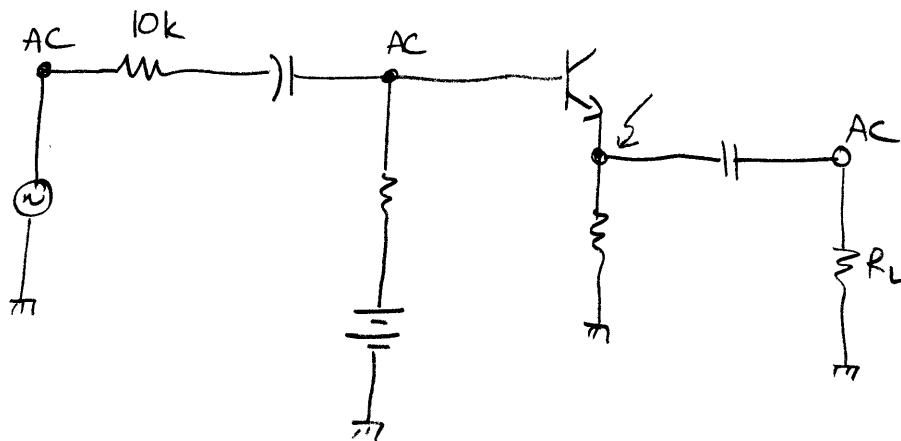
now add a 10k input resistance and repeat all ac procedures.



$R_L = \infty$
4.7k
470
47.

analysis

3a

 

works best when $Z_L > Z_o$

for output.
measure

V_{oc}
 $V_{4.7k}$
 V_{470}
 V_{47}

$$V_{out} = \frac{Z_L}{Z_L + Z_o} A V_{in}$$

if $Z_L = \infty$ $V_{out} = A V_{in} = V_{oc}$


$Z_L = 4.7k$ $V_{out} = \frac{4.7k}{4.7k + Z_o} V_{oc}$

$Z_L = 470$ $V_{out} = \frac{470}{470 + Z_o} V_{oc}$

$Z_L = 47$ $V_{out} = \frac{47}{47 + Z_o} V_{oc}$

test to see how
consistent these
are.

for input.

 


by inspection if $Z_s = 0$ $V_{oc} = A V_s$

if $Z_s \neq 0$ $V_{in} = \frac{Z_i}{Z_i + Z_s} V_s$


$$V_{out} = A V_{in} = \frac{A Z_i}{Z_i + Z_s} V_s$$

$$\therefore \frac{V_{out, Z_s=0}}{V_{out, Z_s}} = \frac{Z_i}{Z_i + Z_s}$$

and solve for Z_i

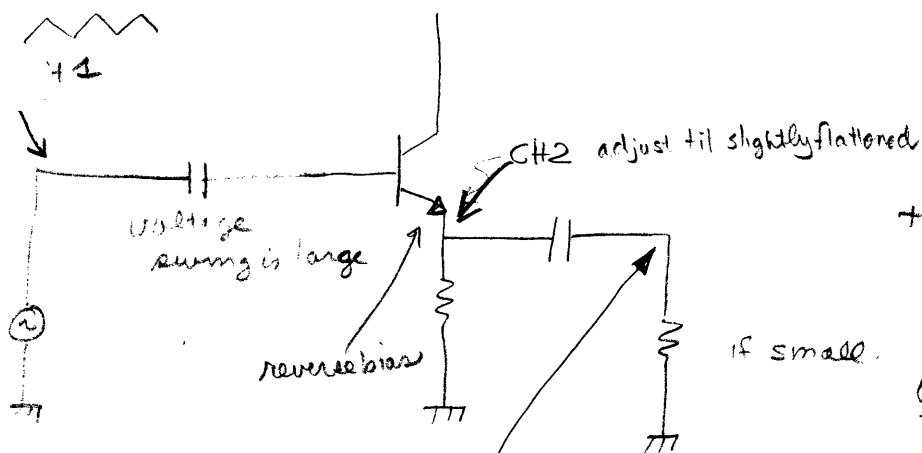


adjust so that it just flattens

 


measure dc voltage differential between ground and flattened part of waveform here.

DC CHARACTERISTICS OF BJTs AND FETs

Before we can understand how to design circuits using BJTs and FETs we must review their basic properties. These basic properties are functions of the operational mechanisms of these devices, i.e. the solid state physics which is covered in other courses. The bipolar transistor, or BJT, comes in two types: npn and pnp referring to the physical construction of the device. The npn transistor is a thin slice of p-type material sandwiched between two slabs of n-type material as shown below.

 


The middle layer is called the base; the substrate (or base upon which the entire structure is fabricated) is called the collector; and the top layer is called the emitter. The net result of this construction is that two diode junctions are formed: one between the collector and base and the other between the base and emitter. In practice, both transistor junctions (the diodes referred to above) are forward biased. Proper bias for npn and pnp transistors are shown below.

 

The net result of this bias is that current continuously flows through the junctions of the transistor; however, it is the relative magnitudes of these currents and the relationships between these currents that make the transistor an amplifier. For an npn transistor we can regard current as entering the

transistor at both the base and collector and exiting at the emitter. This makes the emitter current the sum of the collector and base currents. The base current is quite small, however, and controls the collector current. The ratio of collector current to base current is the dc beta of the transistor and is denoted by β_{DC} . This ability to amplify current is what makes the bipolar transistor so useful, and even though the primary mode of operation of the BJT is current based, it can usefully function as a voltage and power amplifier when placed in a proper circuit.

 
The operation of the BJT can be summarized in the relationship between the base current I_B , the collector current I_C and the collector-emitter voltage V_{CE} . The exact relationship can be derived only after a fair digression into physical electronics. Suffice it to say that all bipolar junction transistors have characteristics similar to those shown in the graph below.



For amplifier operation the BJT is used in the "linear" region where the slope of the I_C - V_{CE} curve is almost constant. This linear region makes possible an amplifier with very little distortion as will be discussed later. One wants to avoid operation, for amplifiers, in the saturated region characterized by small V_{CE} (typically 0.2 volts or less). Similarly, one

wants to avoid operation in the region to the far right of the graph. This is the region in which large electric field strengths from the large V_{CE} can destroy the transistor junction.

Field effect transistors, or FETs, are voltage-biased rather than current biased like BJTs. The basic structure of the FET is a thin connection between two terminals of similar semiconducting material. For example, the p-type material is used to connect two pieces of n-type material through a narrow n-type gate region as shown below. The two pieces of n-type material are known as the drain and source with current flow from the drain to the source for the FET shown below. The p-type/n-type connecting region is known as the channel region and the p-type material is called the gate.

 


The drain current is at its maximum value I_{DSS} when the gate-source voltage is zero. The precise definition of I_{DSS} is that it is the short circuit drain current, i.e. the drain current that flows when the gate is shorted to the source. For operation of the FET as a control device the gate-source voltage must be negative. This creates a reverse biased diode and produces a depletion region in the neighborhood of the gate. This depletion region reduces the amount of free carriers and consequently reduces the current flow between the source and drain. As the gate-source potential becomes more negative it eventually reaches a point called the pinchoff voltage V_p where the gate depletion regions close together and the source-drain

current becomes essentially zero. The exact relationship between the drain current and V_{GS} is an exact square-law relationship:

$$I_D = I_{DSS} \left(1 - \frac{|V_{GS}|}{V_P}\right)^2$$

The pinchoff voltage (actually $-V_P$) is also the drain-source voltage which marks the boundary between the ohmic and pinch-off regions of operation of the FET. Essentially, the FET behaves like a variable (but non-linear) resistance in the ohmic region and then remains essentially constant for $V_{DS} > V_P$. For amplifiers it is this linear or pinch-off region that is of interest. In the pinch-off region the drain current is almost linearly proportional to the V_{GS} and independent of V_{DS} (see graph below).

 

The ratio of change in I_D to the corresponding change in V_{GS} is known as the device transconductance g_m and is of fundamental concern when using the FET as an amplifier. The transconductance when the gate-source voltage is zero is denoted by g_{m0} and is often specified by the transistor manufacturer. The transconductance g_{m0} , the drain


saturation current I_{DSS} and the pinch-off voltage V_p are all related by the relationship

$$g_{mo} = \frac{2I_{DSS}}{|V_p|}$$

where $|V_p|$ is the absolute value of the pinch-off voltage.


The above discussion was for a n-channel junction FET, or JFET for short. The same device with the semiconductor materials reversed is known as a p-channel JFET.

 There is a special version of the JFET known as the MOSFET which is of particular interest in this course. The MOSFET or Insulated Gate FET, is a FET in which a silicon dioxide layer electrically insulates the gate electrode from the rest of the transistor. The internal structure of a MOSFET is shown below.



Since the FET operates by the electrode field created between the gate and the drain and source regions the insulated gate FET also functions in the same manner as an ordinary FET. However, the insulated gate now shifts the gate-source voltages and effectively reduces any already small gate currents to effectively zero.



MOSFETs are characterized as enhancement or enhance/depletion mode devices depending upon the properties of the channel. In enhancement mode MOSFETs the drain current increases as V_{GS} increases; however, the channel only exists when V_{GS} is greater than a certain threshold voltage V_T . In enhancement/depletion mode MOSFETs the drain current increases as V_{GS} increases and the FET will continue to operate for $V_{GS} > 0$. Note that enhancement mode MOSFETs are the only type of FET which can operate with a forward biased gate. It must be pointed out that the polarity of V_{GS} is determined by the type of the bulk semiconducting material. Characteristic curves for n-type (not n-channel) enhancement and enhancement/depletion MOSFETs are shown below.

 

V_{GS}	
enhancement	enhancement /depletion
+5	+2
+4	+1
+3	0
+2	-1
+1	-2
0	





The structure of the MOSFET is such that multiple gates can be fabricated for a common drain-source geometry. This allows the MOSFET to be used for logic circuits and active devices such as mixers where it is important to keep the device inputs electrically isolated from each other.

  
Field effect transistors — voltage amplifiers




the drain current is at a maximum when $V_{GS} = 0$
 we call this maximum current I_{DSS}
 specifically I_{DSS} is the drain current when the gate is short circuited to the source.

without going into a lot of detail a FET operates like a voltage controlled resistor. Suppose $V_{GS} = 0$. For small values of V_{DS} we have a typical resistor's linear $i-v$ relationship. As V_{DS} increases the gate-drain junction becomes more reverse biased and a larger depletion region, i.e. an area with few mobile charges appears. As V_{DS} increases the depletion region increases increasing the resistance of the junction and lowering the slope (conductance) of the $i-v$ curve.

  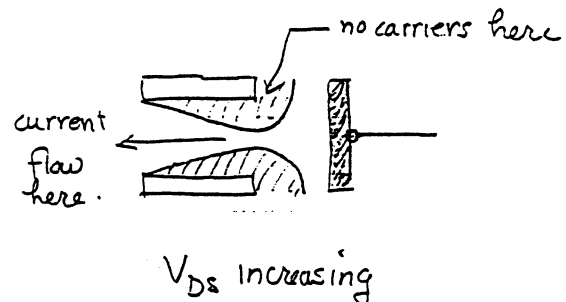 

 

 As we vary V_{DS} we can generate a family of device curves



at cutoff (or pinchoff) for a constant V_{DS} (V_P decreases as V_{GS} decreases)

$$V_{DS}(\text{pinchoff}) \approx V_{P0} + V_{GS} = V_P$$

$\uparrow$ pinchoff for zero V_{GS}
 $\uparrow$ pinchoff voltage

The operation of the junction FET can be mathematically summarized as

1. ohmic region

$$I_D = I_{DSS} \left[2 \left(1 + \frac{V_{GS}}{V_{P0}} \right) \frac{V_{DS}}{V_{P0}} - \left(\frac{V_{DS}}{V_{P0}} \right)^2 \right]$$

for V_{DS} small

$$I_D \approx \frac{2 I_{DSS}}{V_{P0}} \left(1 + \frac{V_{GS}}{V_{P0}} \right) V_{DS}$$

looks like a resistor with

$$\frac{1}{r_{DS}} \approx \frac{2 I_{DSS}}{V_{P0}} \left(1 + \frac{V_{GS}}{V_{P0}} \right)$$

2. saturation region

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_{PO}} \right)^2$$

note: $V_{GS} < 0$
 $V_{PO} > 0$


3. cutoff region $I_D = 0$

A transistor manufacturer will often specify the transconductance g_{mo} defined by


$$g_{mo} = \frac{2 I_{DSS}}{|V_{PO}|}$$

MOSFET


The MOSFET is a special version of the JFET in which a silicon dioxide layer electrically insulates the gate electrode from the rest of the transistor. Basically the MOSFET behaves identically to a JFET. As V_{GS} becomes more negative the minority carriers become depleted and the MOSFET behaves exactly like a JFET. However, because the gate is insulated from the rest of the transistor no p-n junction is formed at the gate and even if V_{GS} becomes positive no gate current can flow. If V_{GS} becomes positive negative charges are induced in the channel creating an "effective" larger majority carrier concentration. This increases the conductivity of the channel and increases I_D . When $V_{GS} > 0$ the MOSFET is operating in the enhancement mode.

 

 Certain MOSFET's can only operate in the enhancement mode. This is because a channel is formed by the applied field (adding majority carriers) and does not exist when $V_{GS} \leq 0$.



 A very common way of displaying FET characteristics is the transfer characteristic curve which plots I_D as a function of V_{GS} , i.e. the output versus the input for a FET.



all are n-channel.


Why use FET's? their transfer characteristics

A square-law relationship is good for mixers, amplifiers and gain-controlled stages.

$$g_m \triangleq \frac{\Delta I_D}{\Delta V_{GS}} \quad \text{so this is the parameter that will be important.}$$

g_{m0} is also the slope of the transfer characteristic.


Specialized MOSFET - dual gate

 


Very useful for mixers:

FET small signal model


circuits II (midband) model:

 


high frequency models;

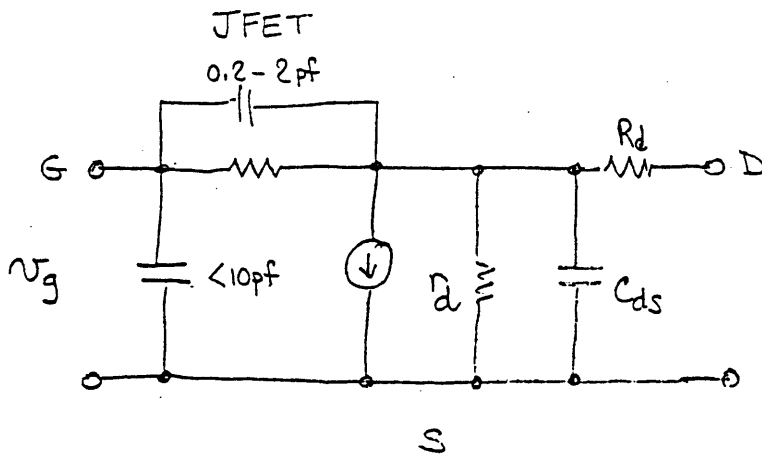

MOSFET

 

simplified high frequency π model

 

C_{gd} feedback capacitance
0.05 - 5 pf

C_{gs} input capacitance
0.1 - 10 pf

r_d effective channel resist
500 - 5000 Ω

C_{ds} is usually small enough
to be neglected.

In general, a FET is NOT better than a BJT at high frequencies



- ① The input impedance drops rapidly with frequency and quickly becomes reactive for a FET. (Even though the FET still has a somewhat higher impedance this can be made up for by a matching circuit for a BJT)
- ② A BJT usually has a better power gain.
- ③ The BJT has a larger gain bandwidth product.

FET data sheets

transconductance $g_{mo} = \frac{2I_{DSS}}{|V_p|}$

C_{iss} common source short-circuit input capacitance
 C_{rss} reverse transfer capacitance
 C_{ds} output capacitance

use π -model

  

$$C_{gd} \approx C_{rss}$$


$$C_{gs} \approx C_{iss} - C_{rss}$$

$$C_{ds} \approx C_{oss} - C_{rss}$$

corresponds to C_p .

input $\parallel$ feedback

output $\parallel$ feedback.


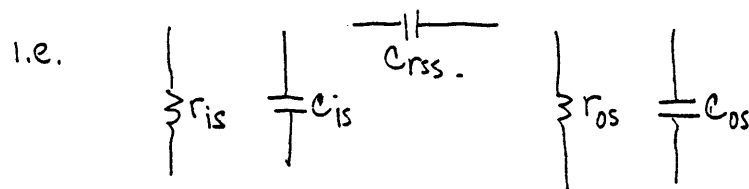


Biasing FET's (p. 93)

simple self-bias circuit

Why does this work?

leakage current I_{gss} thru gate.

  

use KVL on gate bias circuit.

$$0 = I_{gss} R_G + V_{GS} + (I_{gss} + I_D) R_S$$

usually $I_{gss} \ll I_D$

$$V_{GS} = -(I_{gss} R_G + R_S I_D)$$

differentiate with respect to I_{gss}

$$\frac{\partial V_{GS}}{\partial I_{gss}} = -R_G - R_S \frac{\partial I_D}{\partial I_{gss}}$$


equivalent to stability criteria except for FET's.

$$\text{pick } R_G \leq -R_S \left. \frac{\partial I_D}{\partial I_{gss}} \right|_{\max} + \left. \frac{\partial V_{GS}}{\partial I_{DSS}} \right|_{\min}$$


usually $R_G \sim 1 - 1.5 M\Omega$

FET amplifier topologies


common gate

 

common source

 

common drain (source follower)

 


properties of a FET amplifier

	common gate	common source	common drain
R_{IN}	500Ω	∞	∞
R_{OUT}	∞	$20k\Omega$	500Ω
A_v	-4	-4	0.80

$$(g_m = 2 \times 10^{-3} S, r_d = 20k\Omega, r_L = 2k\Omega)$$

Example.
JFET bias

 

For the JFET shown

$$I_{DSS} = 8 \text{ mA}$$

$$V_P = -6 \text{ V}$$

Bias at $I_D = 2.0 \text{ mA}$, $V_{DS} = 10 \text{ V}$

① Find V_{GS} from transfer characteristic

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P} \right)^2$$

$$2 = 8 \left(1 + \frac{V_{GS}}{-6} \right)^2$$

$$\frac{1}{4} = \left(1 + \frac{V_{GS}}{-6} \right)^2$$

$$\pm \frac{1}{2} = 1 + \frac{V_{GS}}{-6}$$

$$\frac{1}{6} V_{GS} = -1 + \frac{1}{2}, -1 - \frac{1}{2} = -\frac{1}{2}, -\frac{3}{2}$$

$$V_{GS} = -3, -9$$

← beyond Pinchoff

$$\Rightarrow V_{GS} = -3 \text{ volts}$$

② Pick $R_G \approx 0.5 \text{ M}\Omega$

③ Use KVL at input

$$V_{GS} = -I_G R_G - I_D R_S \approx -I_D R_S$$


$$R_S \approx \frac{-V_{GS}}{I_D} = \frac{+3}{2 \text{ mA}} = 1.5 \text{ K}$$

④ Use KVL at output

$$V_{DD} = I_D R_D + V_{DS} + I_S R_S$$


$$R_D = \frac{V_{DD} - V_{DS} - I_S R_S}{I_D} = \frac{20 - 10 - 1.5(2 \text{ mA})}{2 \text{ mA}} = 3.5 \text{ K}$$

Example: depletion type MOSFET

 

$$4 < V_p < 6 \text{ volts}$$

$$8 < I_{DSS} < 10 \text{ mA}$$

 

bias at $I_D = 5 \text{ mA}$, $V_{DS} = 8 \text{ V}$ with $\pm 10\%$ variation in I_D

① use transfer characteristic to get V_{GS}

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_p}\right)^2$$

$$\pm \left(1 + \frac{V_{GS}}{V_p}\right) = \sqrt{\frac{I_D}{I_{DSS}}}$$

$$V_{GS} = V_p \left(\pm \sqrt{\frac{I_D}{I_{DSS}}} - 1 \right)$$

V_{GS} will be a maximum when V_p is a maximum, I_D is a maximum

$$V_{GS} = 6 \left(\pm \sqrt{\frac{5.5}{10}} - 1 \right) = 6(\pm .74 - 1) = \begin{cases} -1.56 \\ -10.44 \end{cases} \leftarrow \text{below pinch}$$

use 10% variation in I_D

V_{GS} will be a minimum when V_p is a minimum, I_D is a minimum


$$V_{GS} = 4 \left(\pm \sqrt{\frac{4.5}{8}} - 1 \right) = 4(\pm .75 - 1) = \begin{cases} -1.0 \\ -7.0 \end{cases} \leftarrow \text{below pinch}$$

?? ~~$V_{GS} = 4 \text{ to } 10.44$~~ volts due to parameter variation

② small signal analysis

$$V_{GS} = V_G - R_S I_D$$
 
$$I_D = \frac{V_G}{R_S} - \frac{1}{R_S} V_{GS}$$



$$\therefore R_S = \frac{\Delta V_{GS}}{\Delta I_D} = \frac{-1.55 + 1.0}{5.5 \text{ mA} - 4.5 \text{ mA}} = \frac{-0.55}{1 \text{ mA}} = 550 \Omega$$

③ find V_G

$$V_G = V_{GS} + I_D R_S$$


$$\text{use average } V_{GS} = \frac{-1.55 - 1.0}{2} = -1.275$$

$$V_G = -1.275 + (5 \times 10^{-3})(550) = +1.475$$

nominal value

④ pick simple voltage divider

 pick $R_3 = 500 \text{ K}$ for leakage current



pick $R_1 = 100 \text{ K}$

$$\frac{R_2}{R_1 + R_2} 20 = 1.475$$

$$20R_2 = 1.475R_1 + 1.475R_2$$

$$R_2 = \frac{1.475R_1}{18.525} = 0.0796 (100 \text{ K})$$

$$= 7.9 \text{ K}$$





⑤ use KVL at output

$$V_{DD} = I_D R_D + V_{DS} + I_S R_S$$

$$20 = (5) R_D + 8 \text{ V} + (5)(550)$$

$$R_D = \frac{20 - 8}{5 \text{ mA}} - 550 \Omega = 1850 \Omega$$

part 1.

  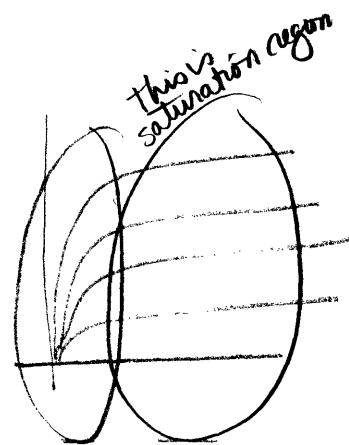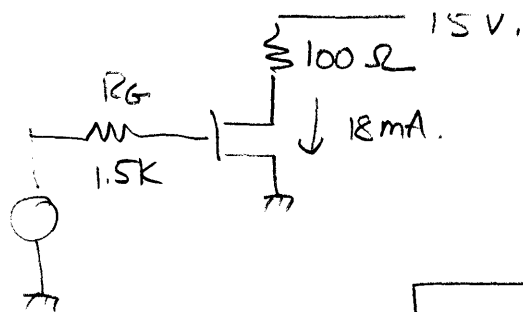


$$I_d = I_{dss} \left(1 - \frac{V_{gs}}{V_p}\right)^2$$

$$\text{If } V_{gs} \rightarrow 0$$

$$I_d = I_{dss}$$

if the transistors are identical

 


$$\text{if } I_d = I_{dss} \text{ then } V_{gs} \Rightarrow 0$$

as I_d increases above I_{dss} .

$$I_{dss} \left(1 - \frac{V_{gs}}{V_p}\right)^2 I_d > I_{dss}$$

$$\text{Then } \left(1 - \frac{V_{gs}}{V_p}\right)^2 > 1$$

$$1 - \frac{V_{gs}}{V_p} > 1 \quad \therefore V_{gs} > |V_p|$$

 

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_{DSS} = 12 - 18mA$$

$$g_{fs} = \frac{CS \text{ forward transfer conductance}}{1 - 6.5mV}$$

$$P_d = (1k)(15) = 1.5 \text{ watts}$$

$$I_D = I_{DSS} \left(1 - \frac{I_D R_S}{V_p} \right)^2$$

$$\frac{I_D}{I_{DSS}} = \left(1 - \frac{I_D R_S}{V_p} \right)^2$$


$$\frac{I_D}{I_{DSS}} = 1 - 2 \frac{I_D R_S}{V_p} + \frac{I_D^2 R_S^2}{V_p^2}$$

$$I_D^2 \left(\frac{R_S}{V_p} \right)^2 - 2 \frac{I_D R_S}{V_p} - \frac{I_D}{I_{DSS}} + 1 = 0$$

$$\frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$I_D = \frac{\left(\frac{2 R_S}{V_p} + \frac{1}{I_{DSS}} \right) \pm \sqrt{\left(\frac{2 R_S}{V_p} + \frac{1}{I_{DSS}} \right)^2 - 4 \left(\frac{R_S}{V_p} \right)^2}}{2 \left(\frac{R_S}{V_p} \right)^2}$$

 
know R_S , V_p and I_{DSS} from transistor characteristics
otherwise measure I_D and solve for I_{DSS} or V_p .



$$Z_{OUT} \approx R_S$$


$$Z_{IN} \approx \infty$$

$$V_{OUT} \approx + g_m R_S$$

 



dead
give away
 $V_{GS} = 0.$
 $\therefore I_D = I_{DSS}$
 
$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P} \right)^2$$




As I add a load resistor
 $I_D > I_{DSS}$ for Q2
 V_{GS} changes

basic JET characteristic

  

V_{DS} increasing

 

saturation region
~
amplifier region

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P} \right)^2$$

$$g_m = \frac{2 I_{DSS}}{V_P}$$

V_P & g_{m0} measured at $V_{GS} = 0$.

small signal model.


 
 



Figure 2B.

 

$$V_{out} = -(g_m V_{GS}) (100k)$$

$$\frac{V_{out}}{V_{in}} = -g_m R_L$$

Figure 2c

 

$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} = -I_D R_S$$

add a 1k and see what happens.