

P 2.2 [a] 8 [b] 6 [c] 4 [d] $v_a - R_1$, $v_b - R_3$ [e] 6

- [f] (1) $v_a - R_1 - R_4 - R_2$
 (2) $v_b - R_2 - R_5 - R_3$
 (3) $R_4 - R_6 - R_5$
 (4) $v_a - R_1 - R_6 - R_3 - v_b$
 (5) $v_a - R_1 - R_4 - R_5 - R_3 - v_b$
 (6) $v_a - R_1 - R_6 - R_5 - R_2$
 (7) $v_b - R_2 - R_4 - R_6 - R_3$

P 2.3 [a] $i_o = \frac{v_o}{20} = \frac{100}{20} = 5 \text{ A}$

$$v_a = 5(24) = 120 \text{ V}$$

$$i_a = \frac{120}{40} = 3 \text{ A}$$


[b] $i_g = i_a + i_o = 3 + 5 = 8 \text{ A}$

[c] $p_g(\text{delivered}) = 8v_a = 960 \text{ W}$

P 2.7 The interconnection is not valid because it violates Kirchhoff's current law. Summing the currents at the lower node yields

$$5 - 20 + 10 \neq 0$$

P 2.8 [a]

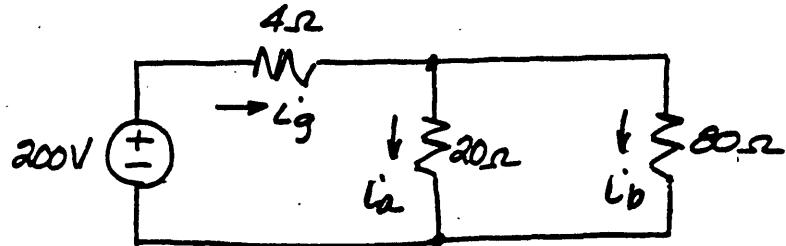

$$20i_a = 80i_b \quad i_g = i_a + i_b = 5i_b$$

$$i_a = 4i_b$$

$$200 = 4i_g + 80i_b = 20i_b + 80i_b = 100i_b$$

$$i_b = 2\text{A}, \quad \therefore i_a = 8\text{A}$$

[b] $i_b = 2\text{A}$

[c] $v_o = 80i_b = 160\text{ V}$

[d] $p_{4\Omega} = i_g^2 4 = 100(4) = 400\text{ W}$

$$p_{20\Omega} = i_a^2 20 = (64)(20) = 1280\text{ W}$$

$$p_{80\Omega} = i_b^2 80 = 4(80) = 320\text{ W}$$


[e] $p_{200\text{V}}(\text{delivered}) = 200i_g = 2000\text{ W}$

Check:

$$\sum P_{\text{diss}} = 400 + 1280 + 320 = 2000\text{ W}$$

$$\sum P_{\text{del}} = 2000\text{ W}$$

P 2.10 [a]

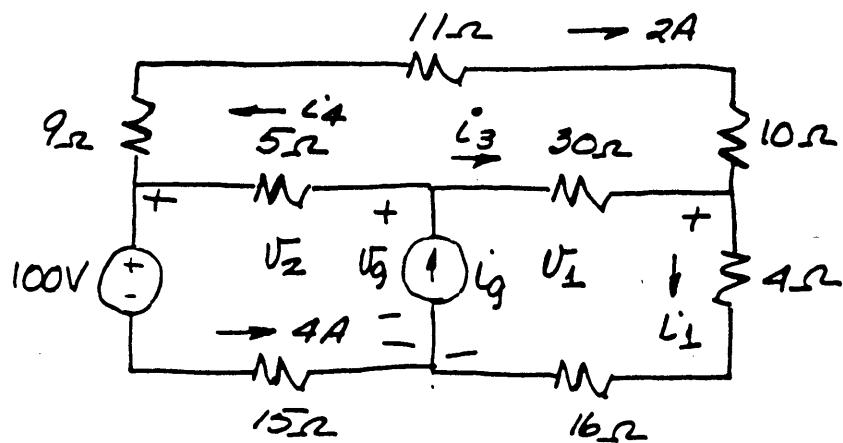

$$v_2 = 100 + 4(15) = 160 \text{ V}$$

$$v_1 = 160 - 30(2) = 100 \text{ V}$$

$$i_1 = \frac{v_1}{20} = \frac{100}{20} = 5 \text{ A}$$

$$i_3 = i_1 - 2 = 5 - 2 = 3 \text{ A}$$

$$v_g = v_1 + 30i_3 = 100 + 90 = 190 \text{ V}$$

$$v_g - 5i_4 = v_2$$

$$5i_4 = v_g - v_2 = 190 - 160 = 30 \text{ V}$$

$$i_4 = \frac{30}{5} = 6 \text{ A}$$

$$i_g = i_3 + i_4 = 3 + 6 = 9 \text{ A}$$

[b] $p_{9\Omega} = (2)^2(9) = 36 \text{ W}$

$$p_{11\Omega} = (2)^2(11) = 44 \text{ W}$$


$$p_{10\Omega} = (2)^2(10) = 40 \text{ W}$$

$$p_{30\Omega} = (3)^2(30) = 270 \text{ W}$$

$$p_{5\Omega} = (6)^2(5) = 180 \text{ W}$$

$$p_{4\Omega} = (5)^2(4) = 100 \text{ W}$$

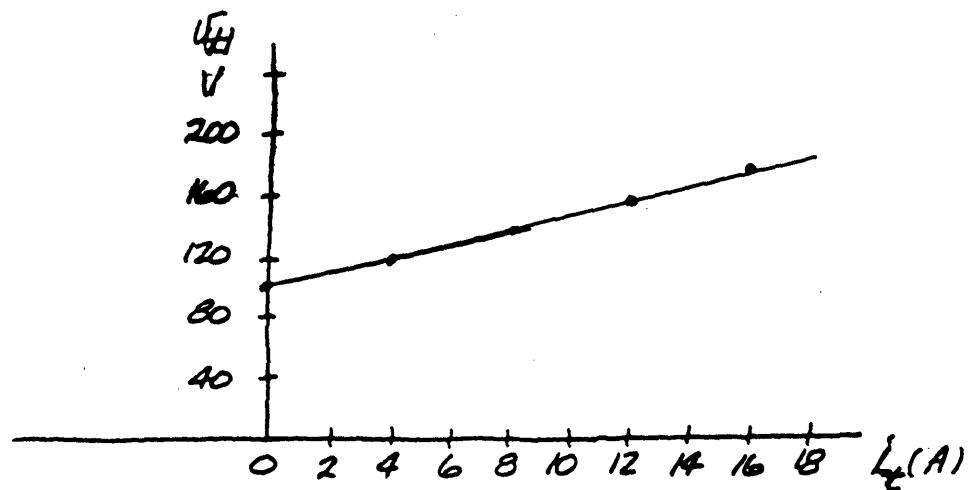
P 2.14 [a] Plot the $v - i$ characteristic




$$\text{From the plot: } R = \frac{\Delta v}{\Delta i} = \frac{180 - 100}{16 - 0} = \frac{80}{16} = 5\Omega$$

When $i_t = 0$, $v_t = 100 \text{ V}$
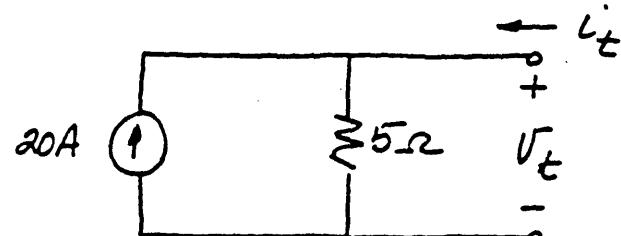
$$\therefore i_s = 100; \quad i_s = 20 \text{ A}$$



[b]

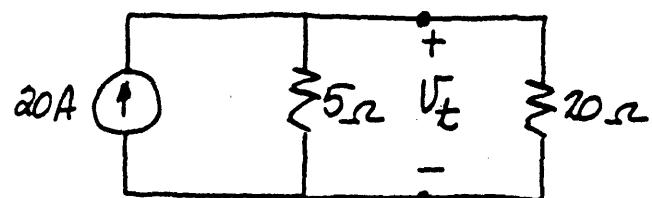

$$-20 + \frac{v_t}{5} + \frac{v_t}{20} = 0$$

$$\therefore 5v_t = 400; \quad v_t = 80 \text{ V}$$

$$p_{20\Omega} = \frac{(80)^2}{20} = 320 \text{ W}$$

$$\text{P 2.22} \quad 40i_2 + \frac{v_o}{40} + \frac{v_o}{10} = 0$$

$$1600i_2 + 5v_o = 0$$

$$i_2 = \frac{-5v_o}{1600} = \frac{-25}{1600} = -15.625 \text{ mA}$$

$$v_1 = 80i_2 = -1.25 \text{ V}$$

$$25i_1 + \frac{v_1}{20} + \frac{v_1}{80} = 0$$


$$2000i_1 + 5v_1 = 0$$

$$i_1 = \frac{-5v_1}{2000} = \frac{6.25}{2000} = 3.125 \text{ mA}$$

$$v_g = 320i_1 = 1000 \text{ mV} = 1 \text{ V}$$

P 3.1 [a] From Ex. 3-1: $i_1 = 4 \text{ A}$, $i_2 = 8 \text{ A}$, $i_s = 12 \text{ A}$
 at node x: $-12 + 4 + 8 = 0$, at node y: $12 - 4 - 8 = 0$

[b]

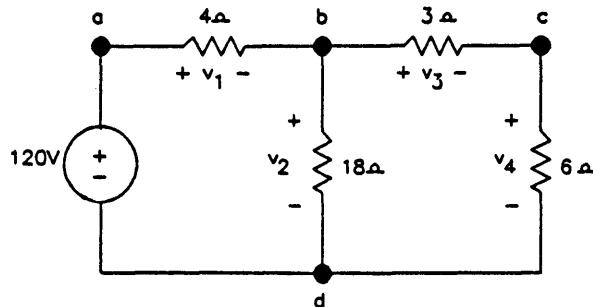

$$v_1 = 4i_s = 48 \text{ V} \quad v_3 = 3i_2 = 24 \text{ V}$$

$$v_2 = 18i_1 = 72 \text{ V} \quad v_4 = 6i_2 = 48 \text{ V}$$

$$\text{loop abda: } -120 + 48 + 72 = 0,$$

$$\text{loop bcdb: } -72 + 24 + 48 = 0,$$

$$\text{loop abcda: } -120 + 48 + 24 + 48 = 0$$

P 3.2 [a] $p_{4\Omega} = i_s^2 4 = (12)^2 4 = 576 \text{ W}$ $p_{18\Omega} = (4)^2 18 = 288 \text{ W},$
 $p_{3\Omega} = (8)^2 3 = 192 \text{ W}$ $p_{6\Omega} = (8)^2 6 = 384 \text{ W}$

[b] $p_{120\text{V}(\text{delivered})} = 120i_s = 120(12) = 1440 \text{ W}$

[c] $p_{\text{diss}} = 576 + 288 + 192 + 384 = 1440 \text{ W}$

P 3.3 [a] $5\Omega // 20\Omega = 4\Omega \quad \therefore R_{ab} = 10 + 4 + 6 = 20\Omega$

[b] $200\Omega // 50\Omega = 40\Omega$

$$20\Omega + 40\Omega = 60\Omega$$

$$\frac{1}{R_{ab}} = \frac{1}{30} + \frac{1}{60} + \frac{1}{60} = \frac{4}{60} = \frac{1}{15} \text{ V}$$

$$\therefore R_{ab} = 15\Omega$$

$$P3.4 [a] R_{ab_a} = 4\Omega // 12\Omega = 3\Omega$$

$$R_{ab_b} = [2.5 // 7.5 // 5 // 15 // 5 + 7] // 8 + 8 = 4 + 8 = 12\Omega$$


$$R_{ab_c} = [6 // 3 + 3] // 20 + 7 = 11\Omega$$

$$[b] P_{15V} = \frac{15^2}{3} = 75 \text{ W}$$

$$P_{48V} = \frac{48^2}{12} = 192 \text{ W}$$

$$P_{22V} = \frac{22^2}{11} = 44 \text{ W}$$

P3.8 [a]

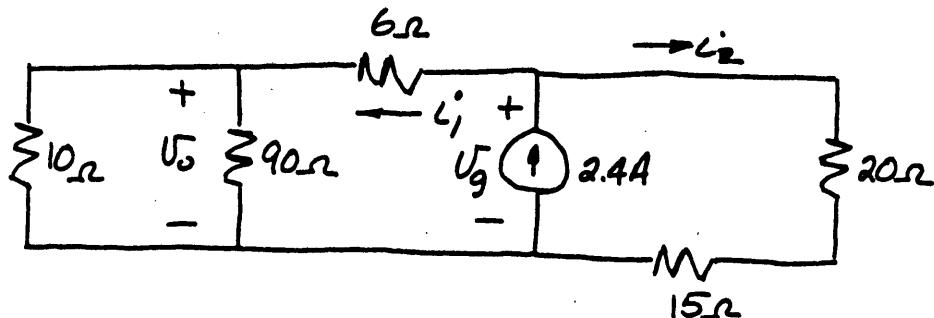

$$10 // 90 = 9\Omega, \quad 9 + 6 = 15\Omega, \quad 15 + 20 = 35\Omega$$

$$i_1 = \frac{(2.4)(35)}{(35 + 15)} = \frac{35}{50}(2.4) = 1.68 \text{ A}$$

$$v_o = (9)(1.68) = 15.12 \text{ V}$$

$$[b] i_2 = 2.4 - 1.68 = 0.72 \text{ A}$$

$$p_{20\Omega} = i_2^2(20) = (0.72)^2(20) = 10.368 \text{ W}$$

$$[c] v_g = 35i_2 = 35(0.72) = 25.20 \text{ V}$$

$$p_g(\text{dev}) = (25.2)(2.4) = 60.48 \text{ W}$$

P3.12 [a]

$$v_a = \frac{18}{8} \times 6 = 13.5 \text{ V}$$

$$v_b = \frac{18}{12} (3) = 4.5 \text{ V}$$


$$v_a + v_x = v_b$$

$$v_x = 4.5 - 13.5 = -9 \text{ V}$$

[b] $v_a = \frac{v_s}{8} \times 6 = 0.75v_s$

$$v_b = \frac{v_s}{12} (3) = 0.25v_s$$
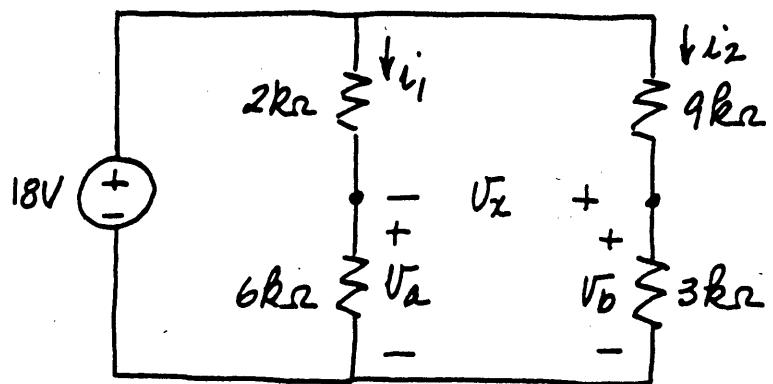
$$v_x = v_b - v_a = 0.25v_s - 0.75v_s = -0.5v_s$$



$$\text{P 3.17 [a]} \quad v_o = \frac{80R_2}{(R_1 + R_2)} = 20$$

$$\therefore \frac{R_2}{R_1 + R_2} = \frac{20}{80} = \frac{1}{4}; \quad \therefore 3R_2 = R_1$$

$$\text{Let } R_e = R_2 // R_L = \frac{R_2 R_L}{R_2 + R_L}$$

$$v_o = \frac{80R_e}{R_1 + R_e} = 18; \quad \frac{R_e}{R_1 + R_e} = \frac{18}{80} = \frac{9}{40}$$

$$40R_e = 9R_1 + 9R_e; \quad 31R_e = 9R_1 = 27R_2; \quad R_e = \frac{(37.8)R_2}{R_2 + 37.8}$$

$$\frac{31(37.8)R_2}{R_2 + 37.8} = 27R_2$$

$$\therefore \frac{31(37.8)}{27} = R_2 + 37.8; \quad R_2 = 5.6 \text{ k}\Omega; \quad R_1 = 3(5.6) = 16.8 \text{ k}\Omega$$

[b] Power dissipated in R_1 will be maximum when the voltage across R_1 is maximum. This will occur under load conditions.

$$v_{R_1} = 80 - 18 = 62 \text{ V}$$

$$P_{R_1} = \frac{(62)^2}{16.8} \times 10^{-3} = 228.81 \text{ mW}$$

P 3.18 Refer to the solution of Problem 3.17. The divider will reach its dissipation limit when the power dissipated in R_1 equals 0.25 W.

Notes:

The dissipation in R_2 will be equal to or less than $P_{R_2} \leq \frac{400}{5.6} = 71.43 \text{ mW}$

The dissipation in R_1 can reach a maximum of $P_{R_1} = \frac{6400}{16.8} = 380.95 \text{ mW}$

When the dissipation in R_1 is 250 mW, the voltage across R_1 is

$$v_{R_1}^2 = 0.25(16.8 \times 10^3) = 4200, \quad v_{R_1} = 64.81 \text{ V}$$

$$\therefore v_o = 80 - 64.81 = 15.19 \text{ V}$$

$$\therefore \frac{80R_e}{R_1 + R_e} = 15.19, \quad \therefore R_e = 3.94 \text{ k}\Omega$$

$$\therefore \frac{5.6R_L}{5.6 + R_L} = 3.94, \quad R_L = 13.27 \text{ k}\Omega \quad (\text{minimum value})$$

P 3.22

$$i_4 = \frac{G_4}{\sum G} 10^{-3}$$

$$i_2 = 2i_3 = \frac{4G_4}{\sum G} \times 10^{-3}$$

$$i_3 = 2i_4 = \frac{2G_4}{\sum G} \times 10^{-3}$$

$$i_1 = 2i_2 = \frac{8G_4}{\sum G} \times 10^{-3}$$

$$i_1 + i_2 + i_3 + i_4 = 10^{-3} = \frac{G_4}{\sum G} \times 10^{-3}(8 + 4 + 2 + 1)$$

$$\therefore \frac{15G_4}{\sum G} = 1 \quad \text{or} \quad 15G_4 = \sum G$$

$$i_4 R_4 = 1$$

$$\therefore \left(\frac{G_4}{\sum G} \times 10^{-3} \right) \left(\frac{1}{G_4} \right) = 1$$

$$\therefore \sum G = 10^{-3}$$

$$\therefore G_4 = \frac{10^{-3}}{15}, \quad R_4 = \frac{1}{G_4} = 15,000 \Omega$$

$$i_3 = \frac{G_3 \times 10^{-3}}{\sum G} = \frac{2G_4}{\sum G} \times 10^{-3}$$

$$\therefore G_3 = 2G_4 = \frac{2 \times 10^{-3}}{15}, \quad R_3 = \frac{1}{G_3} = 7500 \Omega$$

$$i_2 = \frac{G_2 10^{-3}}{\sum G} = \frac{4G_4 \times 10^{-3}}{\sum G}$$

$$\therefore G_2 = 4G_4, \quad R_2 = \frac{15}{4} \times 10^3 = 3750 \Omega$$

$$i_1 = \frac{G_1 \times 10^{-3}}{\sum G} = \frac{8G_4 \times 10^{-3}}{\sum G}$$


$$\therefore G_1 = 8G_4, \quad R_1 = \frac{15 \times 10^3}{8} = 1875 \Omega$$

$$\begin{aligned}
 \text{P7.3 [a]} \quad i &= \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{200} \int_0^t 5 \times 10^{-3} dx + 0, \quad 0 \leq t \leq 2 \text{ ms} \\
 &= \frac{5000}{200} t, \quad 0 \leq t \leq 2 \text{ ms} \\
 &= 25t, \quad 0 \leq t \leq 2 \text{ ms}
 \end{aligned}$$

$$2 \text{ ms} \leq t \leq \infty$$

$$\begin{aligned}
 i &= \frac{1}{L} \int_{2 \times 10^{-3}}^t 0 dx + i(2 \times 10^{-3}) = 0 + 50 \text{ mA} \\
 \therefore i &= 25t \text{ mA}, \quad 0 \leq t \leq 2 \text{ ms} \\
 i &= 50 \text{ mA}, \quad 2 \text{ ms} \leq t \leq \infty
 \end{aligned}$$


[b]

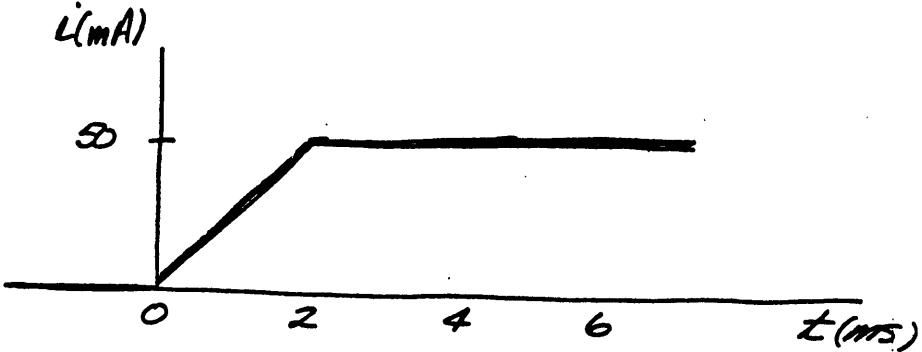

P7.5 [a] $i = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0) = \frac{10^3}{20} \int_{4\pi \times 10^{-3}}^t -50 \sin 250x dx - 10$

 $= -2500 \left[\frac{-\cos 250x}{250} \right]_{4\pi \times 10^{-3}}^t - 10 = 10[\cos 250t - \cos \pi] - 10$
 $i = 10 \cos 250t \text{ A}$

[b]

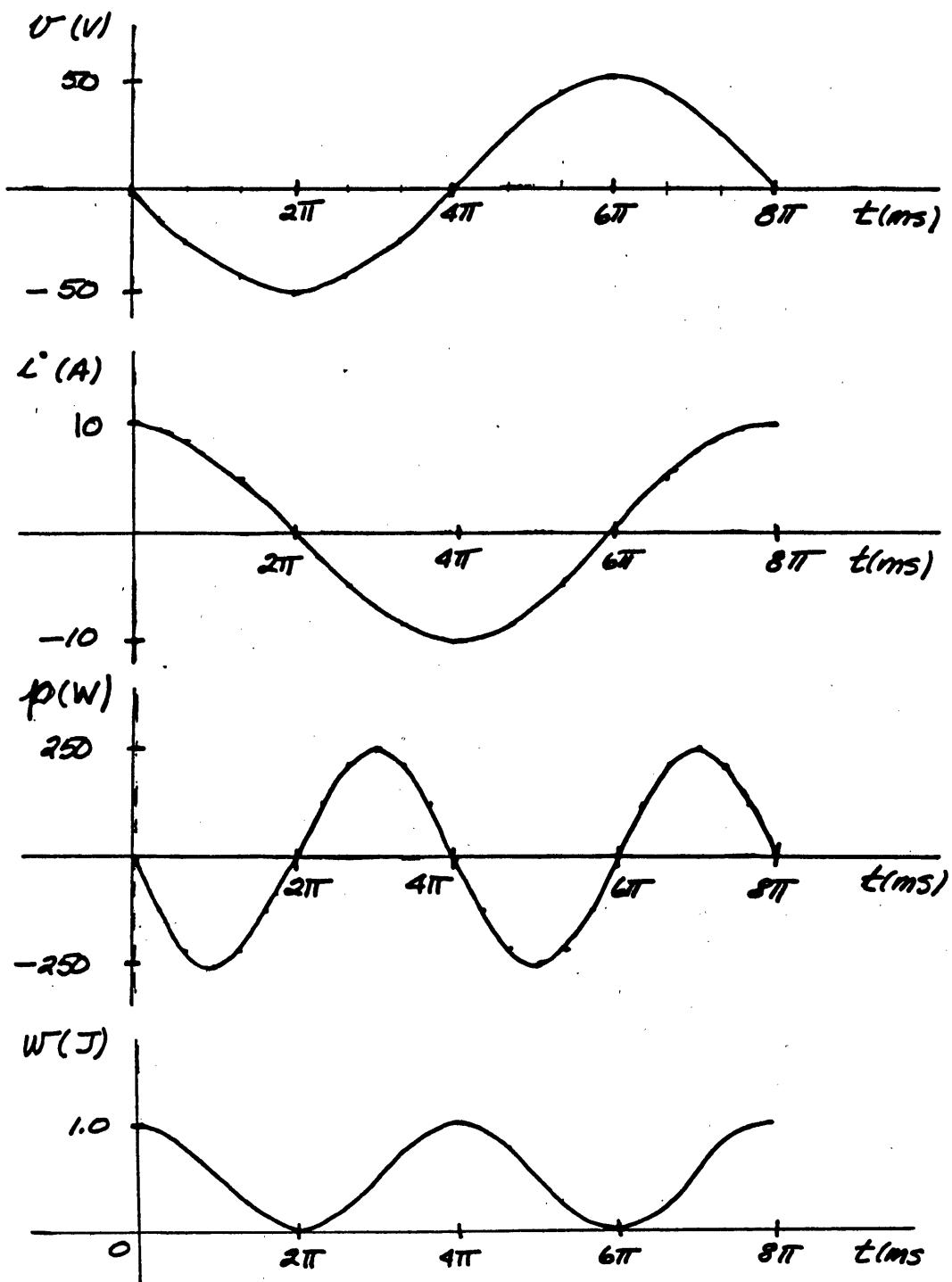

[c] Absorbing power: $2\pi - 4\pi \text{ ms}$
 $6\pi - 8\pi \text{ ms}$

Delivering power: $0 - 2\pi \text{ ms}$
 $4\pi - 6\pi \text{ ms}$

$$\mathbf{P7.13} \quad [\text{a}] \quad w(0) = \frac{1}{2}C[v(0)]^2 = \frac{1}{2}(0.2) \times 10^{-6}(150)^2 = 2250 \times 10^{-6} = 2.25 \text{ mJ}$$

$$[\text{b}] \quad v = (A_1 t + A_2)e^{-5000t}$$

$$v(0) = A_2 = 150 \text{ V}$$

$$\frac{dv}{dt} = -5000e^{-5000t}(A_1 t + A_2) + e^{-5000t}(A_1)$$

$$= (-5000A_1 t - 5000A_2 + A_1)e^{-5000t}$$

$$\frac{dv}{dt}(0) = A_1 - 5000A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{250 \times 10^{-3}}{0.2 \times 10^{-6}} = 1250 \times 10^3$$

$$\therefore 1.25 \times 10^6 = A_1 - 5000(150)$$

$$A_1 = 1.25 \times 10^6 + 75 \times 10^4 = 2.0 \times 10^6 \frac{\text{V}}{\text{s}}$$

$$[\text{c}] \quad v = (2 \times 10^6 t + 150)e^{-5000t}$$

$$i = C \frac{dv}{dt} = 0.2 \times 10^{-6} \frac{d}{dt} (2 \times 10^6 t + 150)e^{-5000t}$$

$$i = \frac{d}{dt} [(0.4t + 30 \times 10^{-6})e^{-5000t}]$$

$$= (0.4t + 30 \times 10^{-6})(-5000)e^{-5000t} + e^{-5000t}(0.4)$$

$$= (-2000t - 150 \times 10^{-3} + 0.4)e^{-5000t}$$

$$= (0.25 - 2000t)e^{-5000t} \text{ A}, \quad t \geq 0$$

- P 7.15**
- [a] $v = \frac{1}{C} \int_0^t -50 \times 10^{-3} dx + 15 = (10^7)(-50 \times 10^{-3})x \Big|_0^t + 15$
 $v = -50 \times 10^4 t + 15, \quad 0 \leq t \leq 10 \mu s$
 $v(10 \mu s) = -50 \times 10^4 (10 \times 10^{-6}) + 15 = -5 + 15 = 10 V$
- [b] $v = 10^7 \int_{10 \times 10^{-6}}^t 0.1 dx + 10 = 10^6 x \Big|_{10 \times 10^{-6}}^t + 10 = 10^6 t - 10 + 10$
 $v = 10^6 t, \quad 10 \mu s \leq t \leq 20 \mu s$
 $v(20 \mu s) = 10^6 (20 \times 10^{-6}) = 20 V$
- [c] $v = 10^7 \int_{20 \times 10^{-6}}^t 0.16 dx + 20 = 10^7 (0.16)[t - 20 \times 10^{-6}] + 20$
 $= 1.6 \times 10^6 t - 32 + 20$
 $v = 1.6 \times 10^6 t - 12, \quad 20 \mu s \leq t \leq 40 \mu s$
- [d] $v(40 \mu s) = 64 - 12 = 52 V$
 $v(t) = 52, \quad 40 \mu s \leq t \leq \infty$