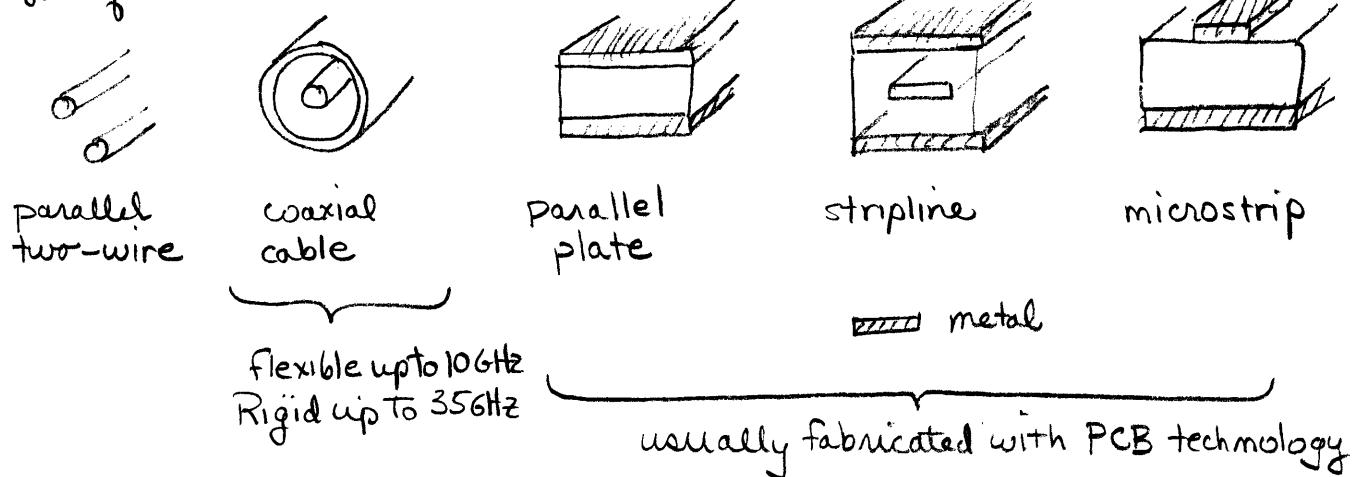



Types of uniform transmission lines



Transmission lines have two conductors.

Distributed circuit model of two-conductor transmission line.

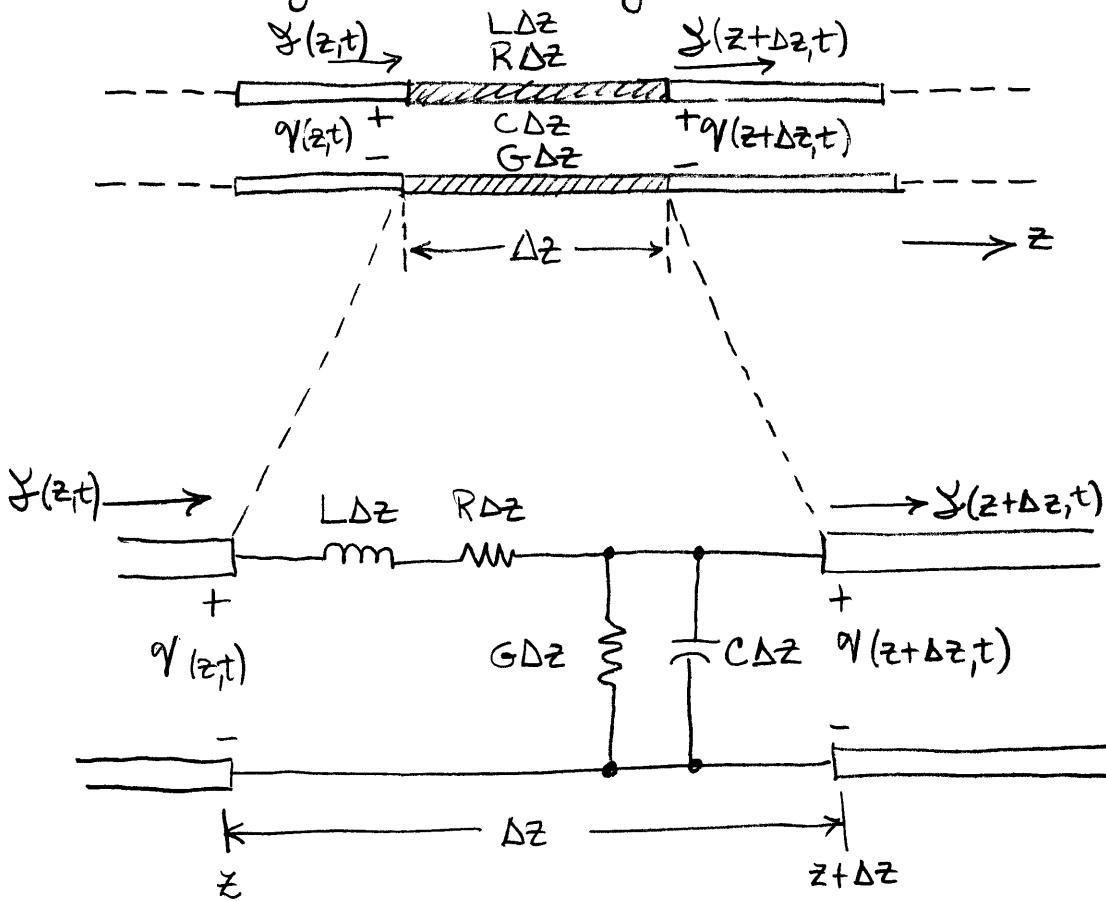(Many models are possible. Calculate L & C from definitions and electromagnetic field configurations)



This is basically the simplest model.

Relate input and output voltages (KVL)

$$-\mathcal{V}(z, t) + L \Delta z \frac{\partial \mathcal{Y}(z, t)}{\partial t} + R \Delta z \mathcal{Y}(z, t) + \mathcal{V}(z + \Delta z, t) = 0$$

Rearranging

$$\mathcal{V}(z + \Delta z, t) - \mathcal{V}(z, t) = -R \Delta z \mathcal{Y}(z, t) - L \Delta z \frac{\partial \mathcal{Y}(z, t)}{\partial t}$$

$$\lim_{\Delta z \rightarrow 0} \frac{\mathcal{V}(z + \Delta z, t) - \mathcal{V}(z, t)}{\Delta z} = -R \mathcal{Y}(z, t) - L \frac{\partial \mathcal{Y}(z, t)}{\partial t}$$

$$\frac{\partial \mathcal{V}(z, t)}{\partial z} = -R \mathcal{Y}(z, t) - L \frac{\partial \mathcal{Y}(z, t)}{\partial t} \quad (1)$$

Do KCL at output node ($\sum_{+in} i = 0$)

$$+ \mathcal{Y}(z, t) - G \Delta z \mathcal{V}(z + \Delta z, t) - C \Delta z \frac{\partial \mathcal{V}(z + \Delta z, t)}{\partial t} - \mathcal{Y}(z + \Delta z, t) = 0$$

Rearranging

$$\mathcal{Y}(z + \Delta z, t) - \mathcal{Y}(z, t) = -G \Delta z \mathcal{V}(z + \Delta z, t) - C \Delta z \frac{\partial \mathcal{V}(z + \Delta z, t)}{\partial t}$$

Slightly more complex

$$\text{expand } \mathcal{V}(z + \Delta z, t) = \mathcal{V}(z, t) + \frac{\partial \mathcal{V}(z, t)}{\partial t} \Delta z + \frac{\partial^2 \mathcal{V}(z, t)}{\partial t^2} \frac{z}{2} \Delta z + \dots$$

$$\lim_{\Delta z \rightarrow 0} \frac{\mathcal{Y}(z + \Delta z, t) - \mathcal{Y}(z, t)}{\Delta z} = -G \mathcal{V}(z, t) - C \frac{\partial \mathcal{V}(z, t)}{\partial t} - \lim_{\Delta z \rightarrow 0} \left\{ \begin{array}{l} \text{higher order} \\ \text{terms} \end{array} \right\}$$

and in the limit

$$\frac{\partial \mathcal{Y}(z, t)}{\partial z} = -G \mathcal{V}(z, t) - C \frac{\partial \mathcal{V}(z, t)}{\partial t} \quad (2)$$

2.2.2. Lossless lines

$$R = G = 0$$

$$(1) \text{ becomes } \frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t}$$

$$(2) \text{ becomes } \frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t}$$

$$\frac{\partial^2 V}{\partial z^2} = \frac{\partial}{\partial z} \left(\frac{\partial V}{\partial z} \right) = \frac{\partial}{\partial z} \left(-L \frac{\partial I}{\partial t} \right) = -L \frac{\partial}{\partial z} \left(\frac{\partial I}{\partial z} \right) = -L \frac{\partial}{\partial t} \left(-C \frac{\partial V}{\partial t} \right)$$

$$\frac{\partial^2 V}{\partial z^2} = +LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial z^2} = \frac{\partial}{\partial z} \left(\frac{\partial I}{\partial z} \right) = \frac{\partial}{\partial z} \left(-C \frac{\partial V}{\partial t} \right) = -C \frac{\partial}{\partial t} \left(\frac{\partial V}{\partial z} \right) = -C \frac{\partial}{\partial t} \left(-L \frac{\partial I}{\partial t} \right)$$

$$\frac{\partial^2 I}{\partial z^2} = +LC \frac{\partial^2 I}{\partial t^2}$$

reverse order of differentiation

These are the wave equations for voltage & current.

Consider voltage equation

$$\frac{\partial^2 V}{\partial z^2} = \frac{1}{v_p^2} \frac{\partial^2 V}{\partial t^2} \quad \text{where } v_p = \frac{1}{\sqrt{LC}}$$

v_p is a function of the electrical & magnetic properties of the media and NOT the geometry.

General solution is

$$V(z, t) = f(t - \frac{z}{v_p}) = f(\xi) \quad \text{where } \xi = t - \frac{z}{v_p}$$

This can be easily confirmed.

$$\frac{\partial V}{\partial t} = \frac{\partial V}{\partial \xi} \frac{\partial \xi}{\partial t} = \frac{\partial V}{\partial \xi}$$

Differentiating again

$$\frac{\partial^2 V}{\partial t^2} = \underbrace{\frac{\partial}{\partial t} \frac{\partial V}{\partial \xi}}_{\text{reversing order}} = \frac{\partial}{\partial \xi} \left(\frac{\partial V}{\partial t} \right) = \frac{\partial^2 V}{\partial \xi^2} \quad \text{since } \frac{\partial \xi}{\partial t} = 1$$

and

$$\frac{\partial \eta}{\partial z} = \frac{\partial \eta}{\partial \xi} \frac{\partial \xi}{\partial z}$$

$$\frac{\partial \eta}{\partial z} = -\frac{1}{v_p} \frac{\partial \eta}{\partial \xi}$$

where

$$\frac{\partial \xi}{\partial z} = -\frac{1}{v_p} \frac{\partial z}{\partial z}$$

$$\frac{\partial \xi}{\partial z} = -\frac{1}{v_p}$$

differentiating again

$$\frac{\partial^2 \eta}{\partial z^2} = -\frac{1}{v_p} \frac{\partial}{\partial z} \left(\frac{\partial \eta}{\partial \xi} \right) = -\frac{1}{v_p} \frac{\partial}{\partial \xi} \left(\frac{\partial \eta}{\partial z} \right) = -\frac{1}{v_p} \frac{\partial}{\partial \xi} \left(-\frac{1}{v_p} \frac{\partial \eta}{\partial \xi} \right)$$

$$\frac{\partial^2 \eta}{\partial z^2} = +\frac{1}{v_p^2} \frac{\partial^2 \eta}{\partial \xi^2}$$

$$\Rightarrow \frac{\partial^2 \eta}{\partial t^2} = v_p^2 \frac{\partial^2 \eta}{\partial z^2} \quad \blacksquare$$

Actually two solutions

$$\eta(z, t) = f^+ \left(t - \frac{z}{v_p} \right) + f^- \left(t + \frac{z}{v_p} \right)$$

$$\uparrow f \left(t - \frac{z}{v_p} \right)$$

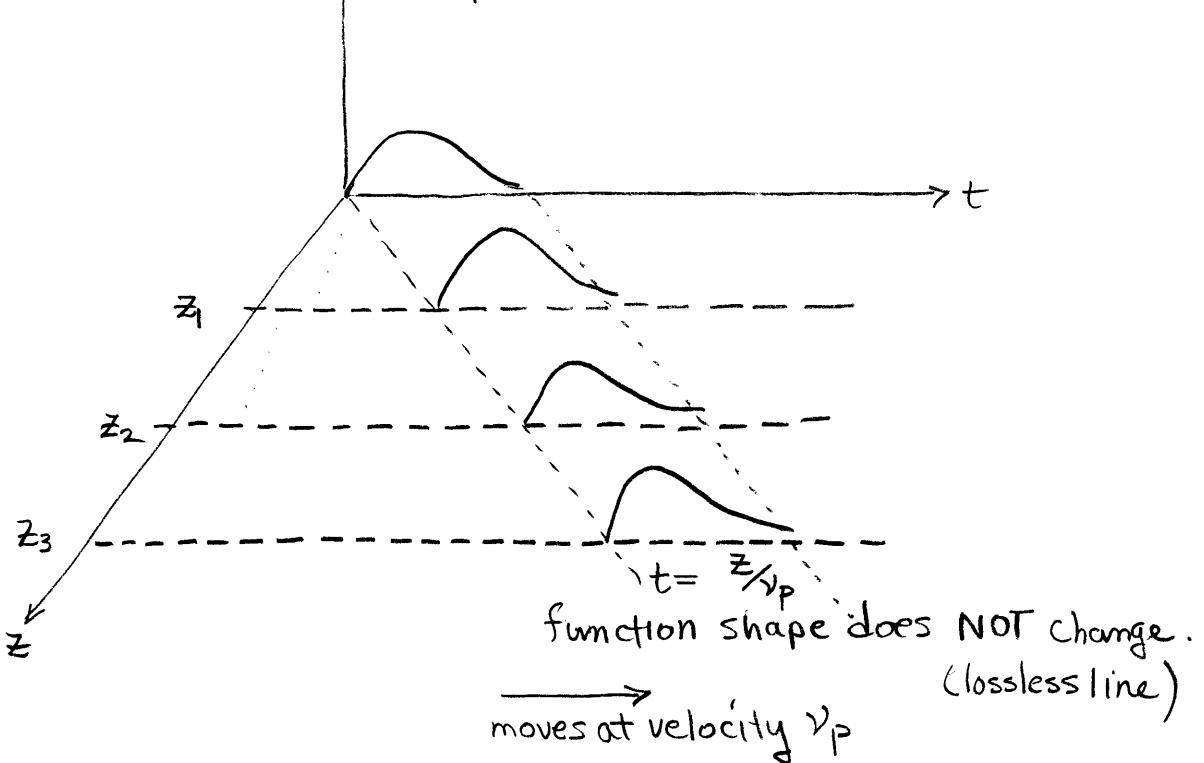


Table 2.1 Propagation speeds in some materials

Air	30 cm/ns
Glass	3-15 cm/ns
Polyethylene	20.0 cm/ns
Teflon	20.7 cm/ns

Consider current equation

$$\frac{\partial^2 \psi}{\partial z^2} = LC \frac{\partial^2 \psi}{\partial t^2}$$

Since this is the same as the previous equation the solution is of the form

$$\psi(z,t) = g\left(t - \frac{z}{v_p}\right) = g(\xi) \text{ where } v_p = \frac{1}{\sqrt{LC}}$$

To relate $\psi(z,t)$ and $\psi(z,t)$

$$\text{use } \frac{\partial \psi}{\partial z} = -L \frac{\partial \psi}{\partial t}$$

$$\frac{\partial \psi}{\partial z} = -\frac{1}{v_p} \frac{\partial \psi}{\partial \xi} = -\frac{1}{v_p} \frac{\partial f}{\partial \xi} = -\sqrt{LC} \frac{\partial f}{\partial \xi}$$

$$\frac{\partial \psi}{\partial t} = \frac{\partial g}{\partial \xi} \frac{\partial \xi}{\partial t} = \frac{\partial g}{\partial \xi}$$

$$\therefore -\sqrt{LC} \frac{\partial f}{\partial \xi} = -L \frac{\partial g}{\partial \xi}$$


$$\frac{\partial f}{\partial \xi} = \sqrt{\frac{L}{C}} \frac{\partial g}{\partial \xi}$$

$$\therefore g = \frac{1}{\sqrt{\frac{L}{C}}} f = \frac{1}{Z_0} f \quad \text{where } Z_0 \equiv \sqrt{\frac{L}{C}}$$

the characteristic impedance of the transmission line.

Z_0 = the ratio of voltage to current for a single wave propagating in $+z$ direction

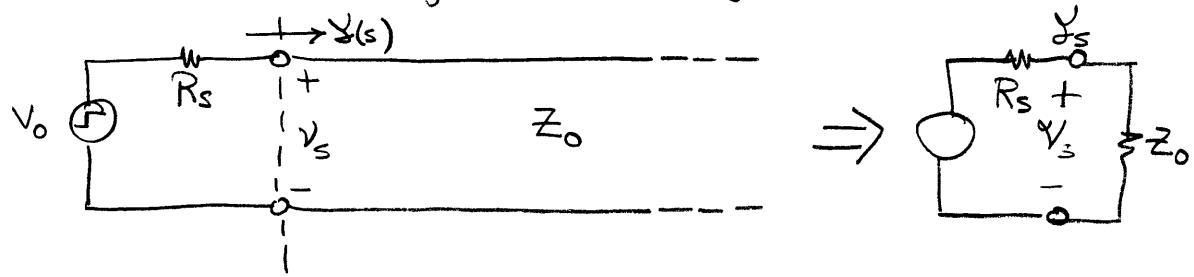Example 2-1 Step response of an infinitely long lossless line.





The initial voltage at the source end (no reflection) so just \mathcal{V}^+


$$\alpha \mathcal{V}_s(t) = \mathcal{V}^+(z=0, t) = \frac{V_o}{Z_0 + R_s} \quad \text{The line looks like } Z_0 \text{ to the } +z \text{ traveling wave. i.e., } \mathcal{V}_s \text{ and } Y_s \text{ at input}$$

since Z_0 is the resistance that the line appears to the source initially
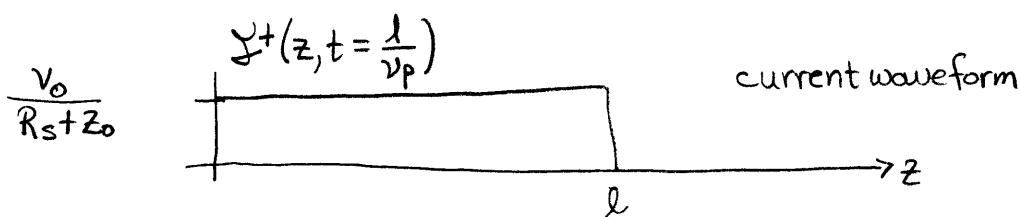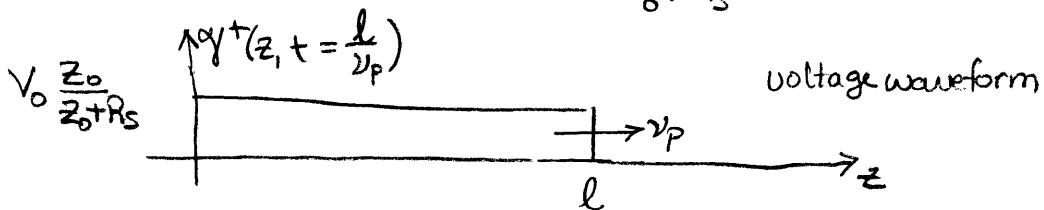
$$\mathcal{V}_s(t) = \mathcal{V}^+(z=0, t) = \frac{V_o}{Z_0 + R_s}$$



2. Reflection from an open end

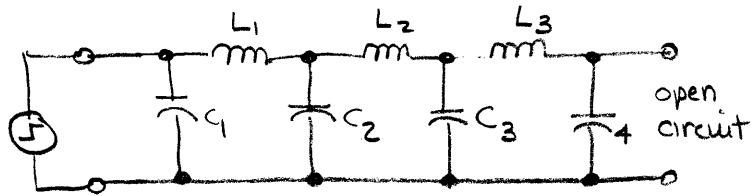

There is an orderly progression of voltages down the line.




Remember the I.C.'s for $L \& C$ { Capacitors look like shorts
Inductors look like opens

Initially, there is no voltage across C_1 (a short) and L_1 blocks a voltage to C_2 .

However, C_1 charges up and a voltage appears across it. L_1 starts to allow current through to charge C_2 .

C_2 is initially a short and L_2 is open. But C_2 starts to charge up and current passes through L_2 .

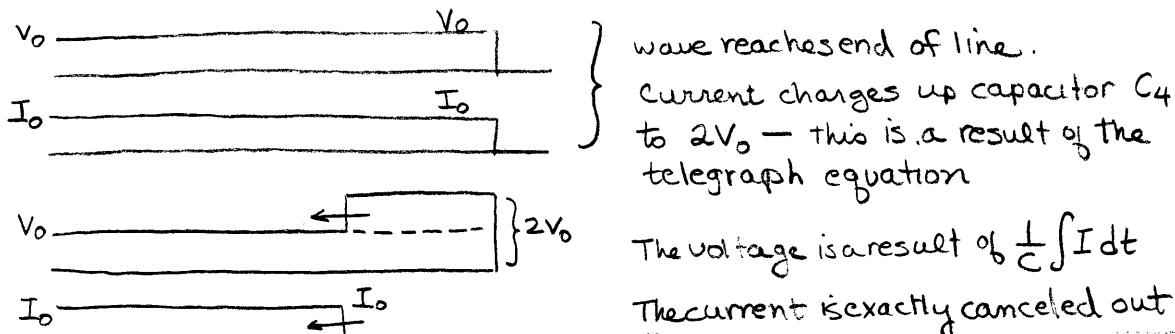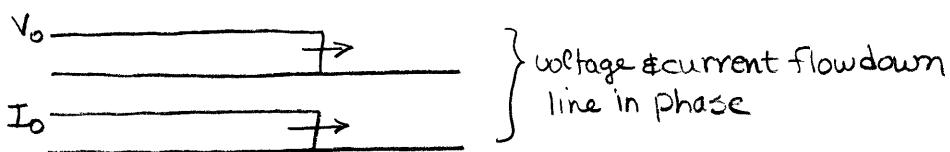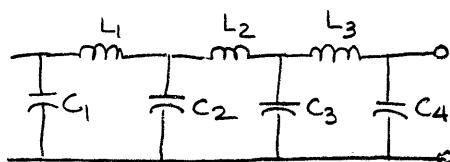
If the inductance of the line is small, the line looks like a single capacitor



The voltage is a result of $\frac{1}{C} \int I dt$

The current is exactly canceled out.
There MUST be zero current at the end of an open line.

2.3 Reflection at discontinuities

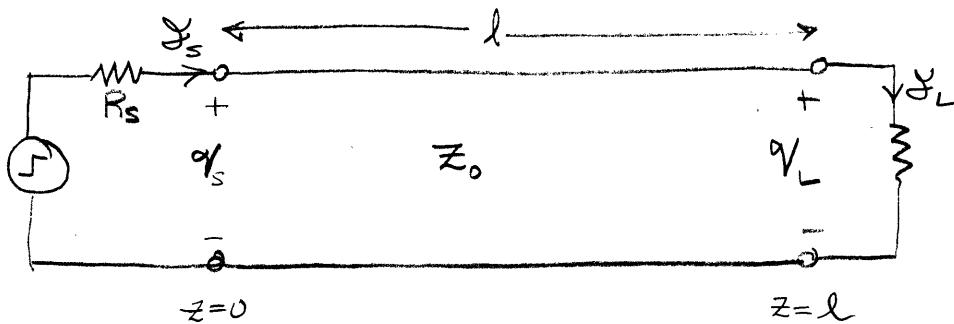

$$\xrightarrow{t>0} \gamma_1^+(z,t)$$

$$t_d = \frac{l}{v_p}$$

$$\xleftarrow[t > t_d]{-} \gamma_1^-(z,t)$$

the amplitude of
The reflected wave
is determined by
the boundary conditions

write
total γ & \mathcal{Y}
at load

$$\begin{cases} V_L(t) = \gamma_1^+(l,t) + \gamma_1^-(l,t) \\ \mathcal{Y}_L(t) = \frac{\gamma_1^+(l,t)}{Z_0} - \frac{\gamma_1^-(l,t)}{Z_0} \end{cases}$$

current is flowing
towards source

boundary condition comes from R_L at load side

$$V_L(t) = \mathcal{Y}_L(t) R_L$$

$$\therefore \mathcal{Y}_L(t) = \frac{V_L(t)}{R_L}$$

$$\frac{\gamma_1^+(l,t)}{Z_0} - \frac{\gamma_1^-(l,t)}{Z_0} = \frac{\gamma_1^+(l,t)}{R_L} + \frac{\gamma_1^-(l,t)}{R_L}$$

$$\left(\frac{1}{Z_0} - \frac{1}{R_L} \right) \gamma_1^+(l,t) = \left(\frac{1}{R_L} + \frac{1}{Z_0} \right) \gamma_1^-(l,t)$$

$$\Gamma_L = \frac{\gamma_1^-(l,t)}{\gamma_1^+(l,t)} = \frac{\frac{1}{Z_0} - \frac{1}{R_L}}{\frac{1}{Z_0} + \frac{1}{R_L}} = \frac{R_L - Z_0}{R_L + Z_0}$$

$$\xrightarrow{t > 2t_d} \gamma_2^+(z,t)$$

this wave will get back to source where similar process occurs.

$t > 2t_d$

$$\underline{V}_s(t) = \underbrace{\underline{V}_i(0,t)}_{\text{initial source is still on}} + \underbrace{\underline{V}_i^-(0,t)}_{\text{reflected wave from load}} + \underbrace{\underline{V}_2^+(0,t)}_{\text{newly generated wave at load/line interface}}$$


$$\underline{V}_s(t) = \underline{V}_i^+(0,t) + \underline{V}_i^-(0,t) + \underline{V}_2^+(0,t)$$

Note that
 $\underline{V}_i^-(0,t) = -\frac{1}{Z_0} \underline{V}_i^-(0,t)$

Just as $\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$ occurred at load

$\Gamma_s = \frac{R_s - Z_0}{R_s + Z_0}$ occurs at source
reflects reflection back to load.

bounce diagram

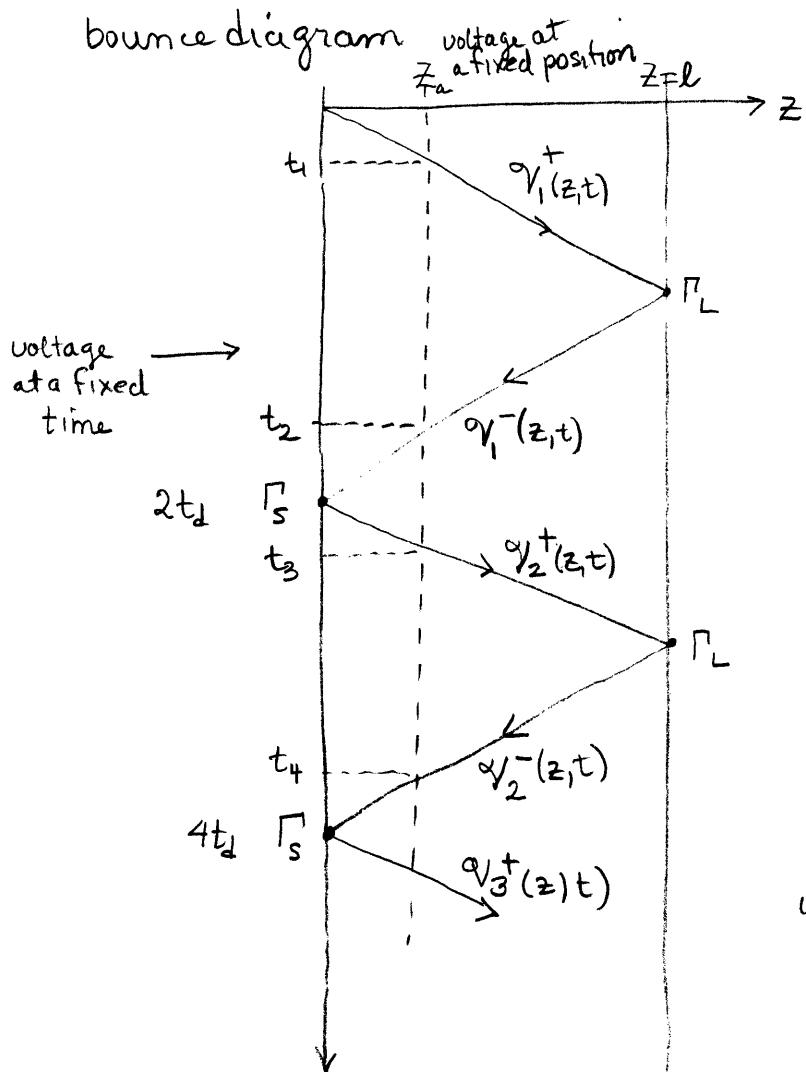



to find $\underline{V}(z_a, t)$

$$\underline{V}(z_a, t) = \begin{cases} 0 & 0 < t < t_1 \\ \underline{V}_i^+(z_a, t) & t_1 < t < t_2 \\ \underline{V}_i^+(z_a, t)(1 + \Gamma_L) & t_2 < t < t_3 \\ \underline{V}_i^+(z_a, t)(1 + \Gamma_L + \Gamma_L \Gamma_s) & t_3 < t < t_4 \\ \dots & \dots \end{cases}$$


wave evolution

2.2.3 Open & Short Circuited Lines

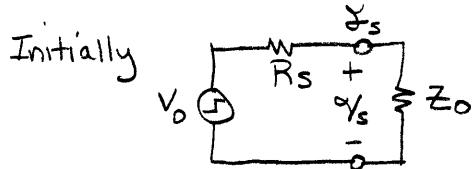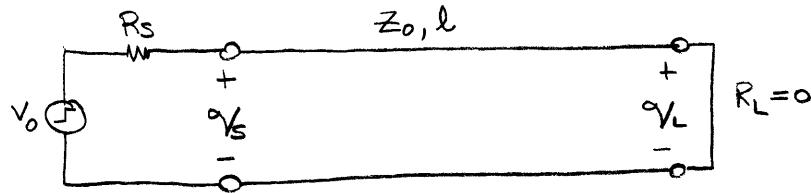Example 2-2 Short Circuited Lossless Line





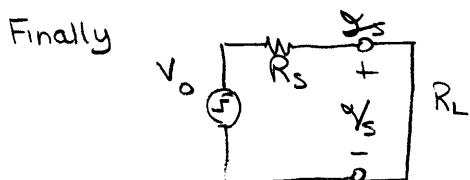Initially the line looks like the characteristic impedance.



Finally the line looks like the short that it is.

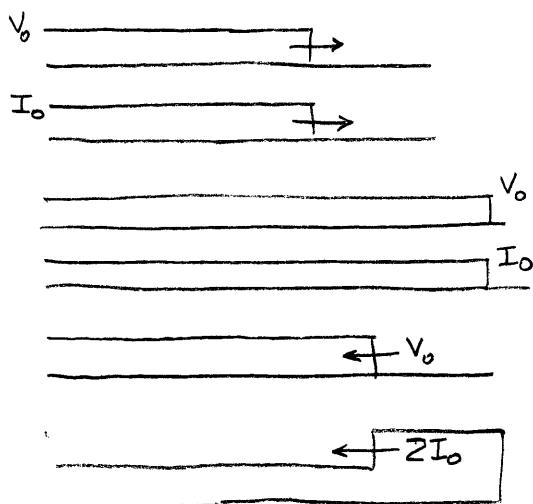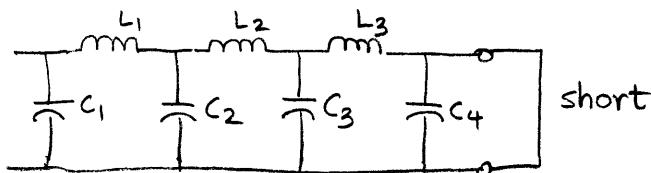The short circuit behaves differently than the open.




C_3 is charged to V_o , but C_4 is shorted and cannot charge.

The short discharges C_3 through L_3 doubling the current through L_3 and propagating down the line.


Analyze using a bounce diagram and Γ_L .

R_s also has an effect.


$$(a) R_s = Z_0/3$$

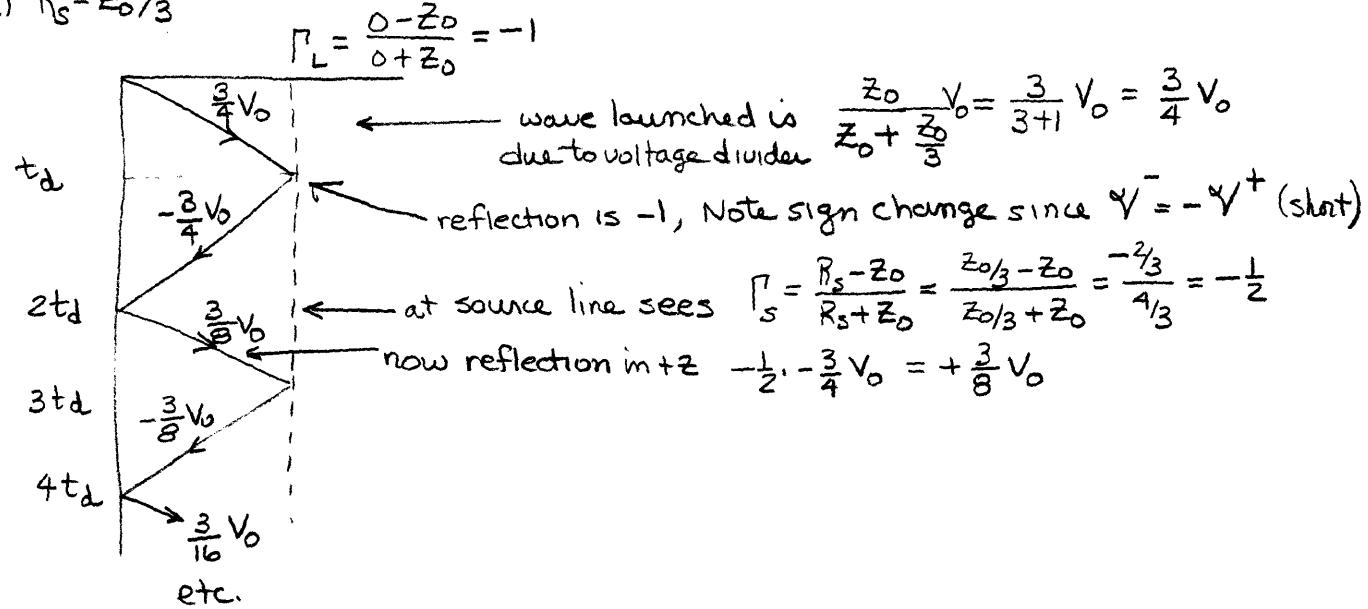


$$(b) R_s = Z_0$$

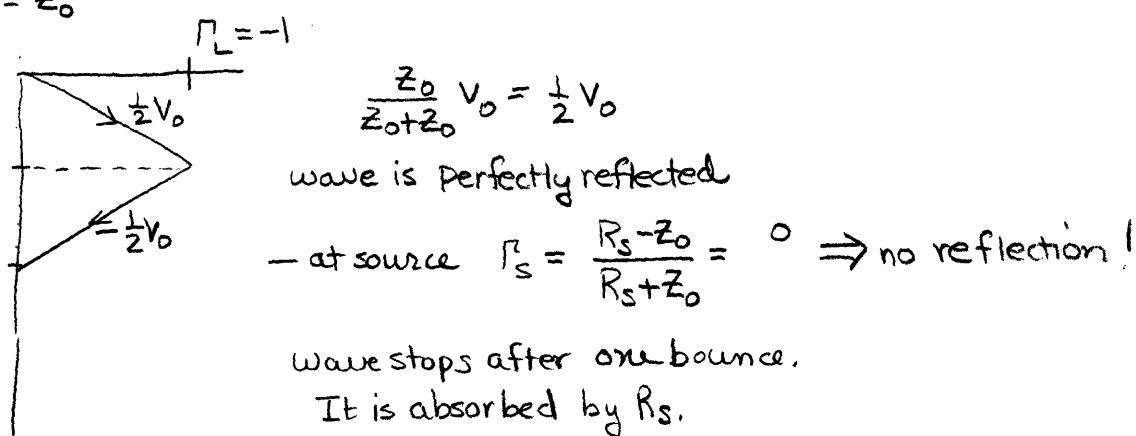


$$(c) R_s = 3Z_0$$

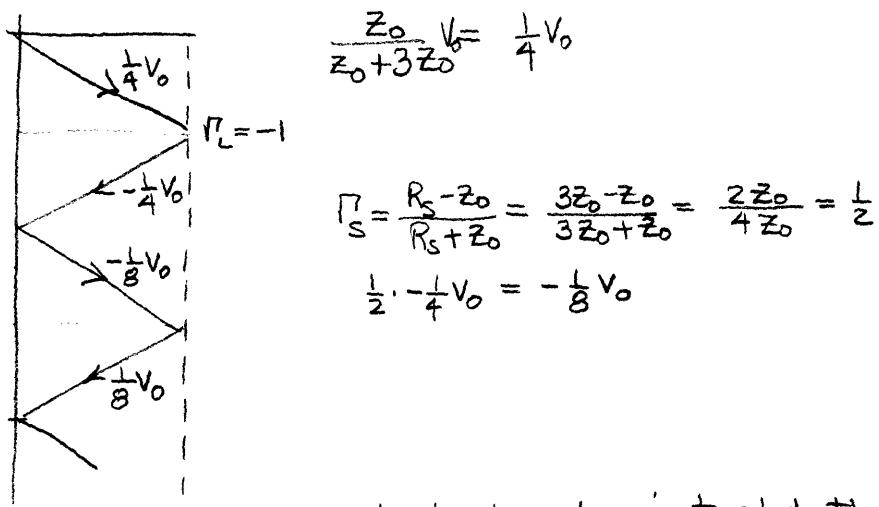

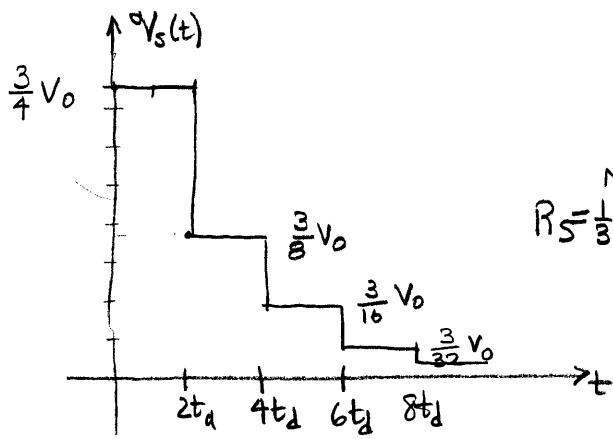
What's interesting is to plot these voltages as a function of time.



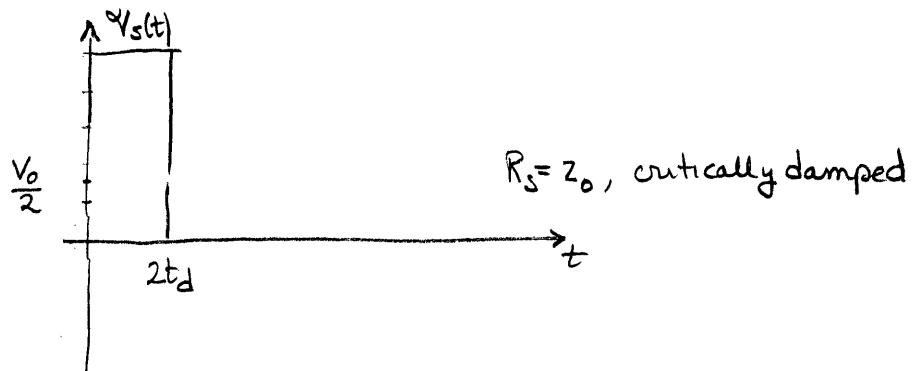Note how wave decays to zero.
 $R_S = \frac{1}{3}Z_0$ overdamped.





$R_S = Z_0$, critically damped

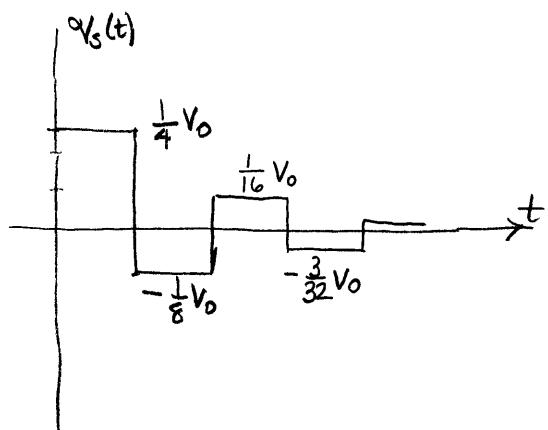


$R_S = 3Z_0$, underdamped

This is ringing.

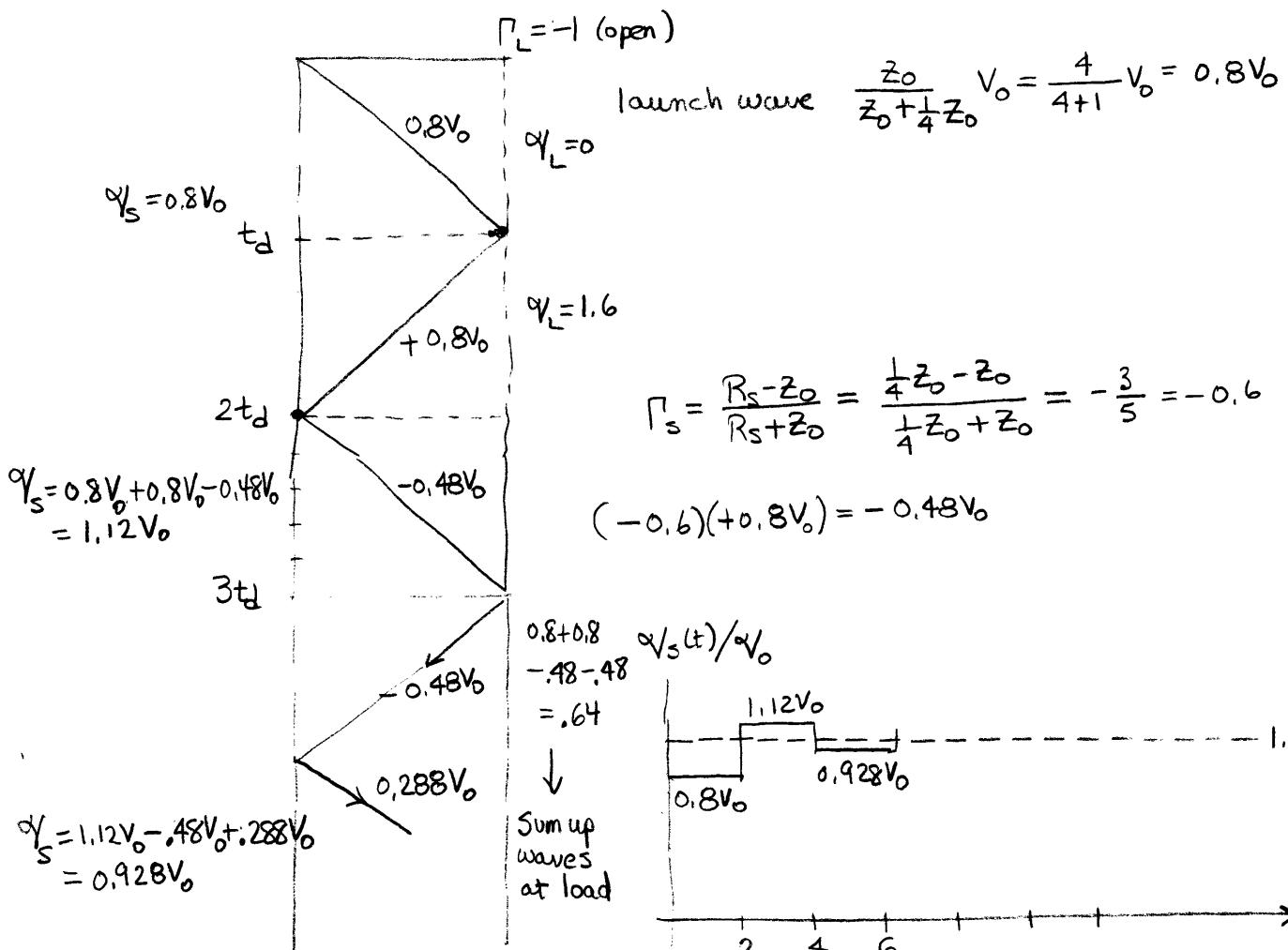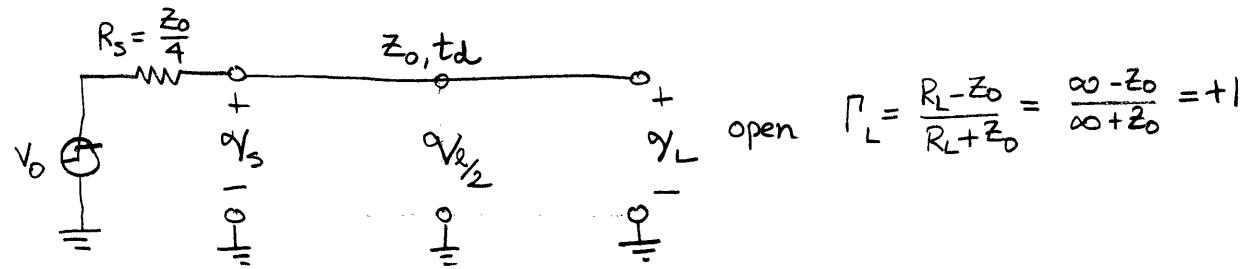


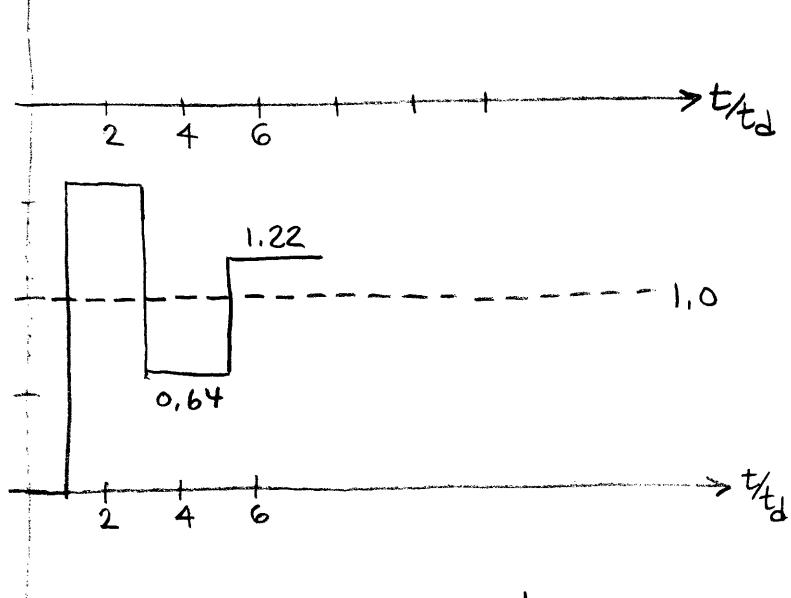You have to sum
all the waves.
at source.
this way.



Again you see ringing because
 $R_s \neq Z_0$

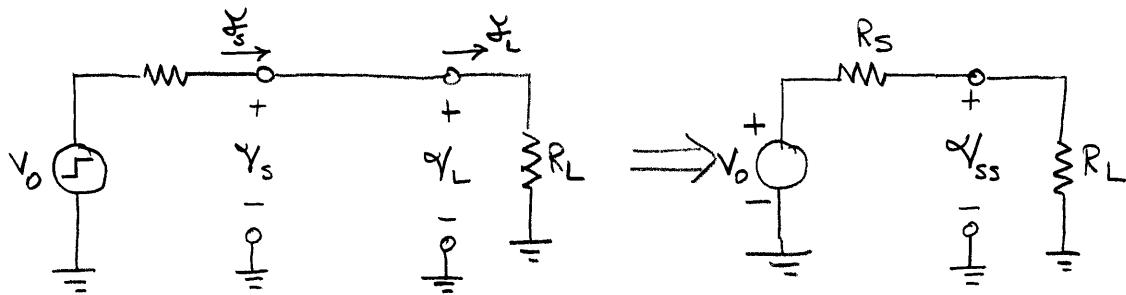2.4 Transient response / resistive terminations



steady-state equivalent circuit

The voltage at any position z on the line is given by. (steady state)

$$\psi(z, t=\infty) = \psi_1^+(z, \infty) + \psi_1^-(z, \infty) + \psi_2^+(z, \infty) + \psi_2^-(z, \infty) + \psi_3^+(z, \infty) + \dots$$

ψ_1^+ launched pulse at source
 ψ_1^- reflected pulse at load
 ψ_2^+ reflected pulse at source

using source and load reflectances we can re-write this as

$$\begin{aligned} \psi(z, \infty) &= \psi_1^+(z, \infty) + \Gamma_L \psi_1^+(z, \infty) + \Gamma_s \Gamma_L \psi_1^+(z, \infty) + \Gamma_L \Gamma_s \Gamma_L \psi_1^+(z, \infty) + \Gamma_s \Gamma_L \Gamma_s \Gamma_L \psi_1^+(z, \infty) + \dots \\ &= \underbrace{\psi_1^+ [1 + (\Gamma_s \Gamma_L) + (\Gamma_s \Gamma_L)^2 + (\Gamma_s \Gamma_L)^3 + \dots]}_{\text{these are reflections at source end}} + \underbrace{\psi_1^+ [\Gamma_L + \Gamma_s \Gamma_L^2 + \Gamma_s^2 \Gamma_L^3 + \dots]}_{\text{these are reflections at load end}} \\ &\quad - \psi_1^+ \left[\frac{1}{1 - \Gamma_s \Gamma_L} \right] + \psi_1^+ \Gamma_L \left[\frac{1}{1 - \Gamma_s \Gamma_L} \right] \end{aligned}$$

$$\psi(z, \infty) = \psi_1^+(z, \infty) \frac{1 + \Gamma_L}{1 - \Gamma_s \Gamma_L}$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}, \quad \Gamma_s = \frac{R_s - Z_0}{R_s + Z_0}, \quad \psi_1^+(z, \infty) = \frac{Z_0}{R_s + Z_0} V_o$$




Substituting,

$$\psi(z, \infty) = \frac{Z_0}{R_s + Z_0} V_o \frac{1 + \frac{R_L - Z_0}{R_L + Z_0}}{1 - \left(\frac{R_s - Z_0}{R_s + Z_0} \right) \left(\frac{R_L - Z_0}{R_L + Z_0} \right)} = \frac{Z_0 V_o}{R_s + Z_0} \frac{(R_s + Z_0)(R_L + Z_0) + (R_L - Z_0)(R_s - Z_0)}{(R_s + Z_0)(R_L + Z_0) - (R_s - Z_0)(R_L - Z_0)}$$


$$\psi(z, \infty) = \frac{Z_0 V_o}{R_s + Z_0} \frac{2 R_L}{R_s R_L + Z_0 R_L + Z_0 R_s + Z_0^2 - R_s R_L + Z_0 R_L + Z_0 R_s - Z_0^2} = \frac{2 R_L Z_0 V_o}{Z_0 (2(R_L + R_s))}$$

$$\psi(z, \infty) = \frac{R_L}{R_L + R_s} V_o \quad \text{as if transmission line is not there.}$$

Step response of resistively terminated lossless line.

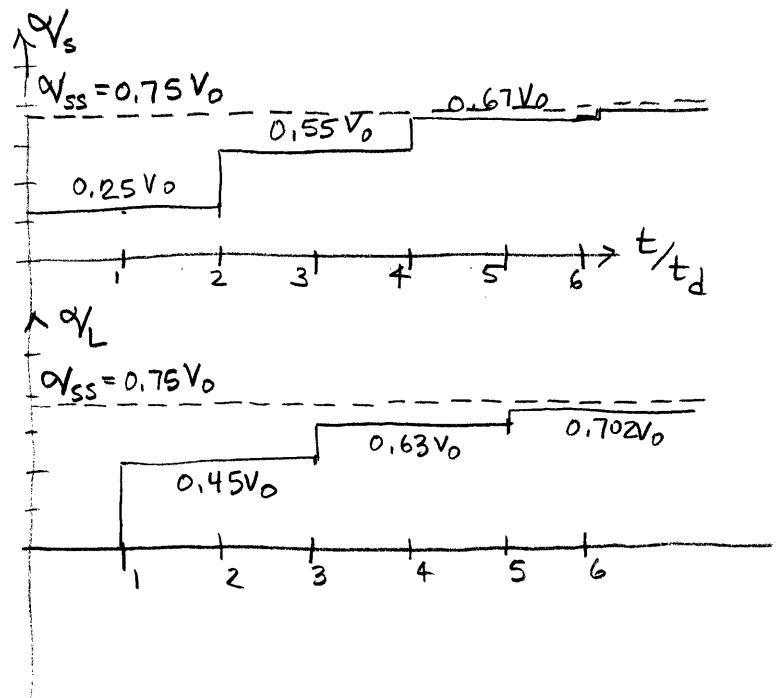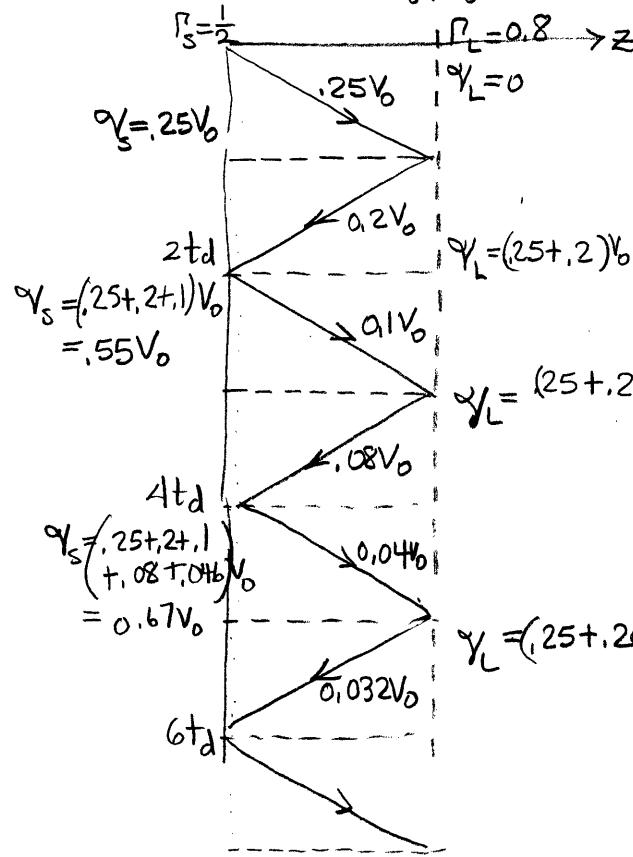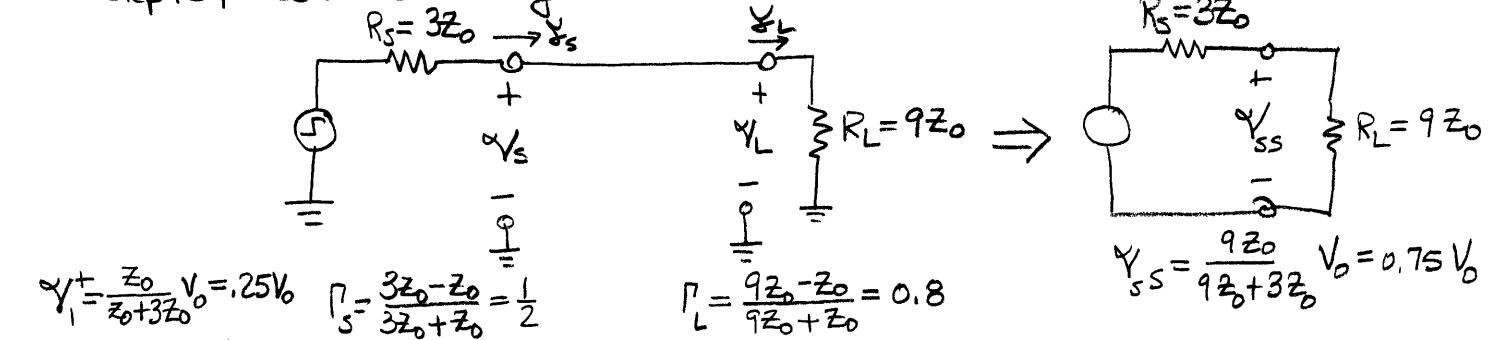

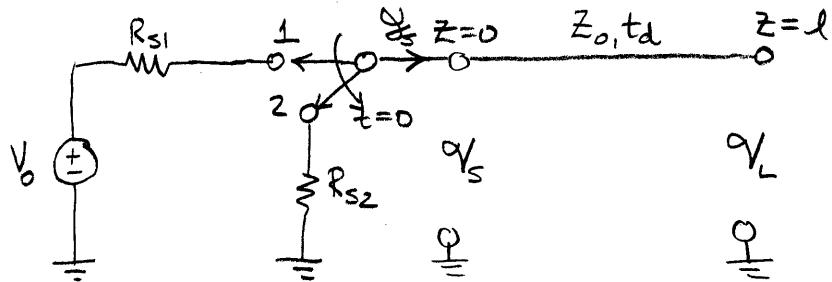Example 2-5 A Charged Line Connected To a Resistor



At $t=0$ the switch is moved from position 1 to position 2

$$(a) \text{ Assume } R_{S2} = \frac{Z_0}{3}$$

The line is initially charged to V_0 volts. $\gamma_s(0^-) = \gamma_L(0^-) = V_0$

The new wave launched on the line is the difference between γ_s at $t=0^-$ and γ_s at $t=0^+$.

$$\gamma_i^+(0,0) = \gamma_s(0^+) - \gamma_s(0^-) = \gamma_s(0^+) - V_0$$

$$\text{where } \gamma_s(0^+) = -R_{S2} \gamma_s(0^+)$$

$$\gamma_s(0^+) = \gamma_i(0,0) = \frac{\gamma_i^+(0,0)}{Z_0}$$

- sign because current will be going to ground and negative wrt γ_s

Substituting gives

$$\gamma_i^+(0,0) = -R_{S2} \frac{\gamma_i^+(0,0)}{Z_0} - V_0$$

solving for $\gamma_i^+(0,0)$

$$\gamma_i^+(0,0) Z_0 = -R_{S2} \gamma_i^+(0,0) - Z_0 V_0$$


$$\gamma_i^+(0,0) = \frac{-Z_0 V_0}{Z_0 + R_{S2}}$$

This is a bit like a voltage divider except it is Z_0 and not R_{S2} in the numerator since this is the wave in the line.

Given this you can construct a bounce diagram

$$\Gamma_{S2} = \frac{R_S - Z_0}{R_L + Z_0} = \frac{\frac{Z_0}{3} - Z_0}{\frac{Z_0}{3} + Z_0} = -\frac{1}{2}$$
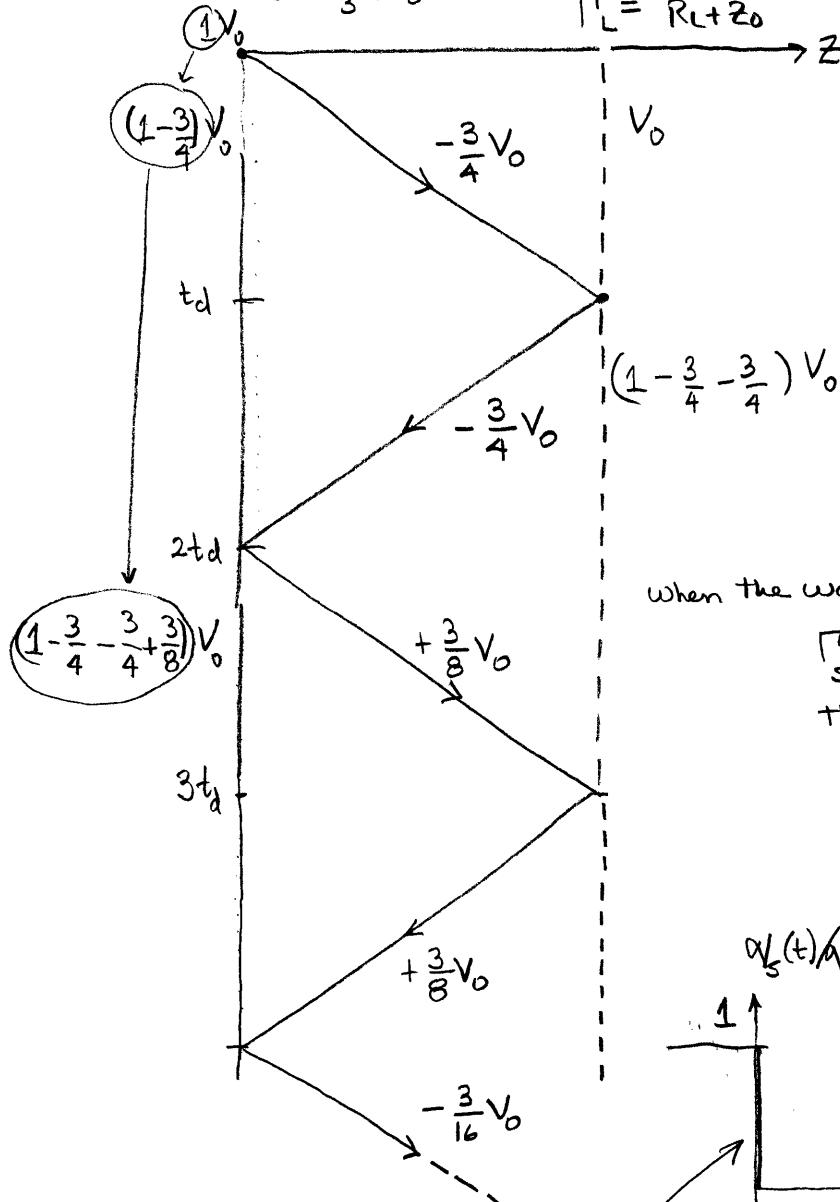
$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = 1 \text{ as } R_L \rightarrow \infty$$




wave launched is $-\frac{Z_0}{Z_0 + R_{S2}} V_0$


$$\Psi^+(0,0) = -\frac{Z_0}{Z_0 + \frac{1}{3}Z_0} V_0 = -\frac{3}{4}V_0$$

when the wave gets to the source end it sees
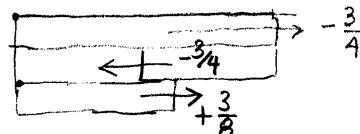
$$\Gamma_{S2} = -\frac{1}{2}, \text{ The reflected wave is}\\ \text{then } -\frac{1}{2}(-\frac{3}{4}V_0) = +\frac{3}{8}V_0$$


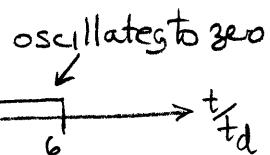
$$1 - \frac{3}{4} - \frac{3}{4} + \frac{3}{8}$$



$$\Psi_s = V_0 - \Psi^+ \\ = 1 - \frac{3}{4}$$


$$\Psi_s = V_0 - \Psi^+ \\ = 1 - \frac{3}{4} - \frac{3}{4} + \frac{3}{8} = -\frac{1}{8}$$

at V_0 until pulse gets there





then goes to $1 - \frac{3}{4} - \frac{3}{4} = -\frac{1}{2}$


Also decays.

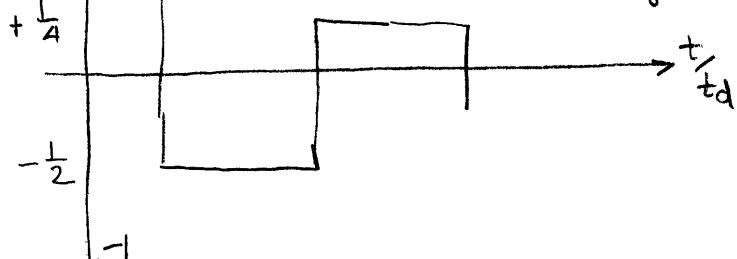

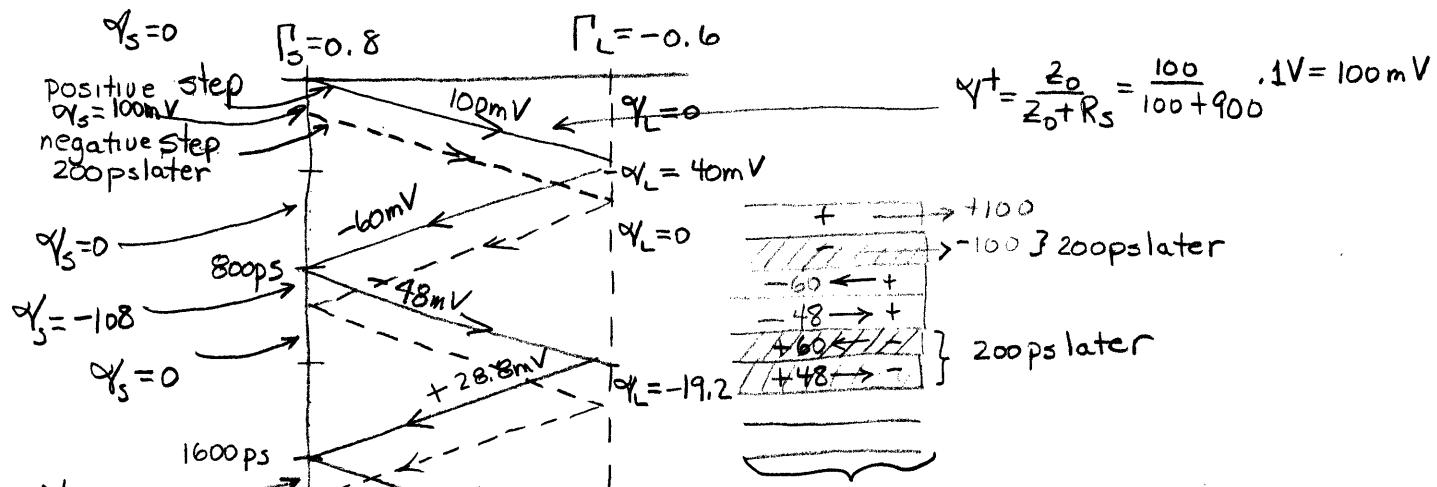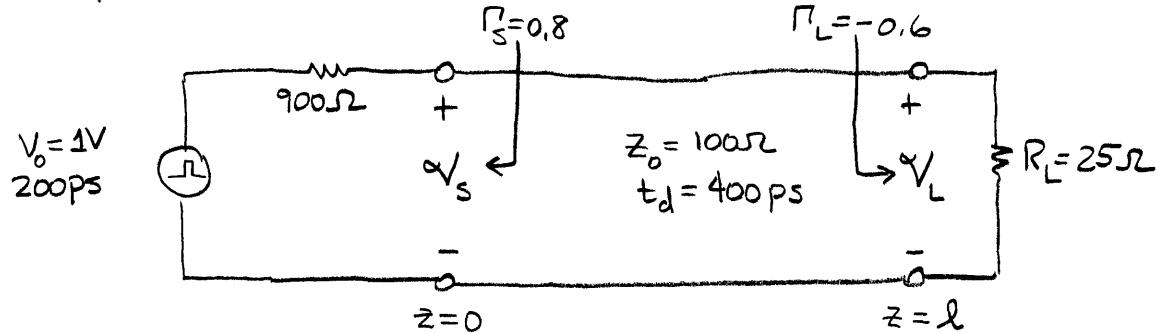
Example 2-6 Pulse Excitation of a Transmission Line



$$\alpha V_L = \frac{Z_0}{Z_0 + R_L} = \frac{100}{100 + 900} \cdot 1V = 100mV$$

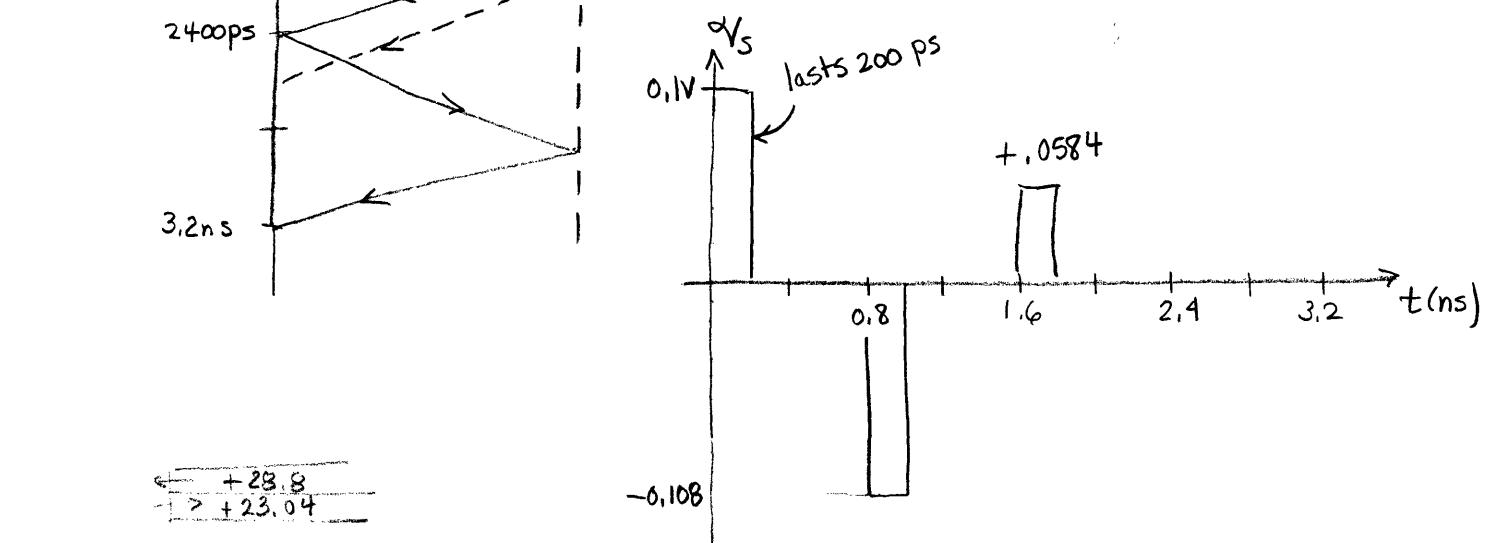

Example 2.8 Cascaded Transmission Lines

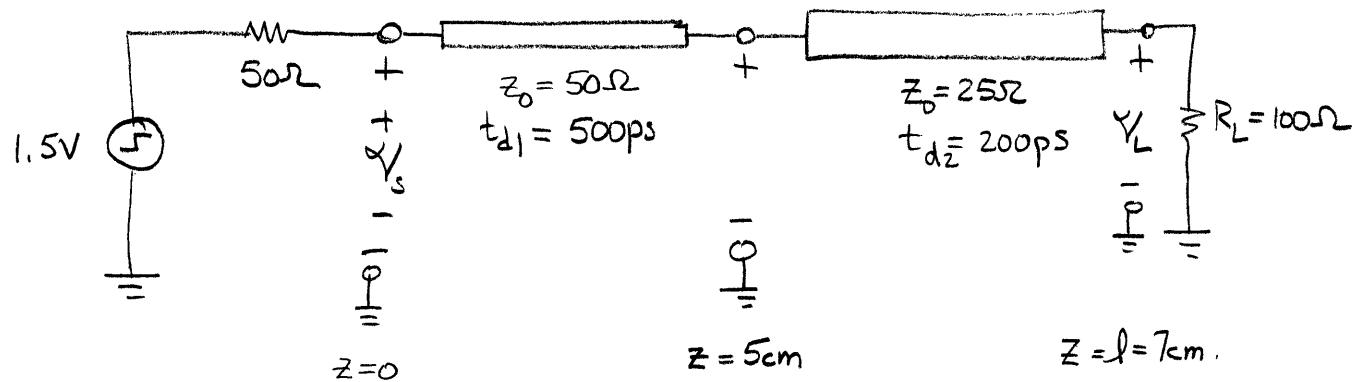

compute the reflection coefficients


$$\Gamma = \frac{R_L - Z_0}{R_L + Z_0}$$

$$\Gamma_s = \frac{50 - 50}{50 + 50} = 0$$



$$\Gamma_{AB} = \frac{25 - 50}{25 + 50} = -\frac{1}{3}, \quad \Gamma_{BA} = \frac{50 - 25}{50 + 25} = +\frac{1}{3}$$

$$\Gamma_L = \frac{100 - 25}{100 + 25} = 0.6$$

we treat the second transmission line as a simple input impedance

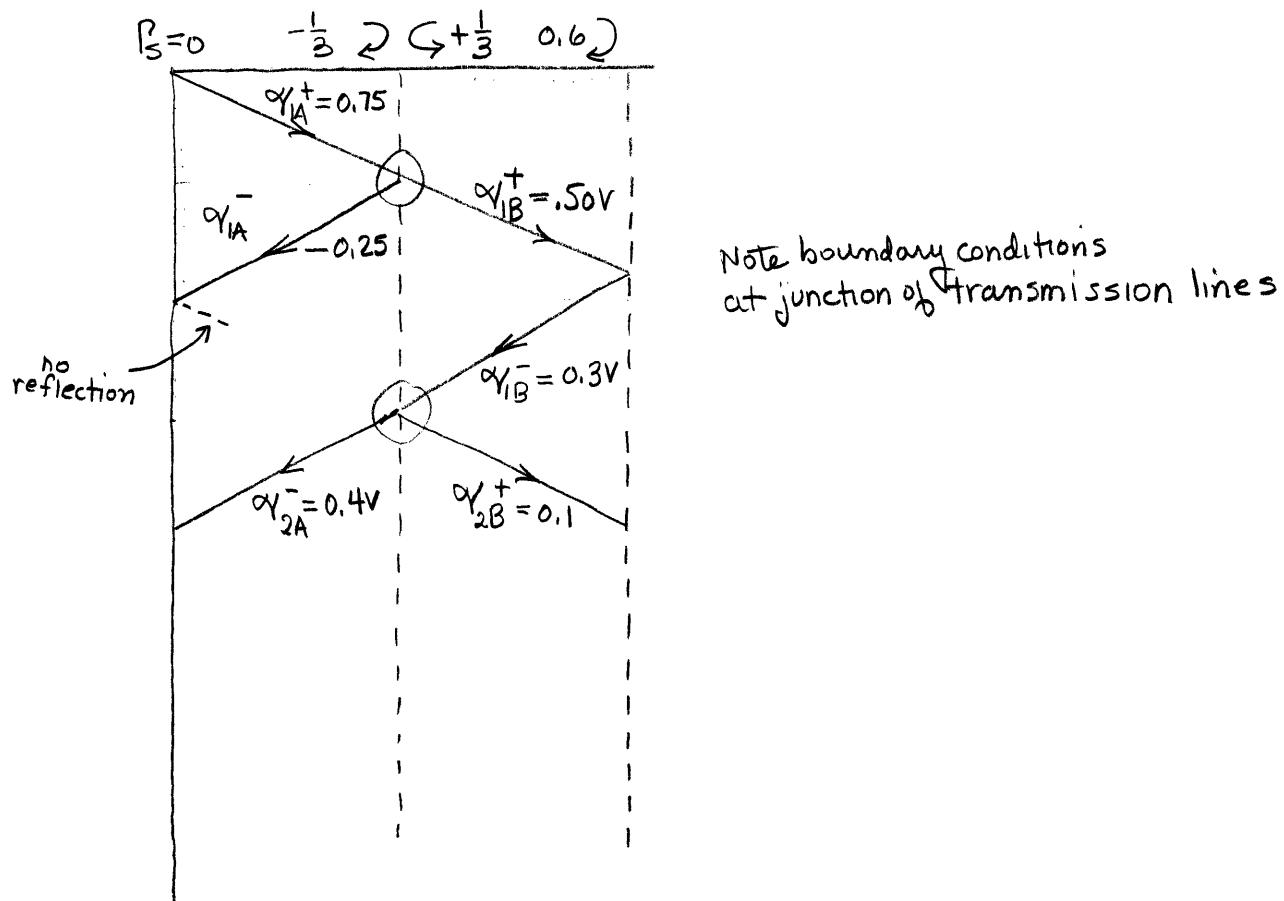

Example 2-9 Three Transmission Lines

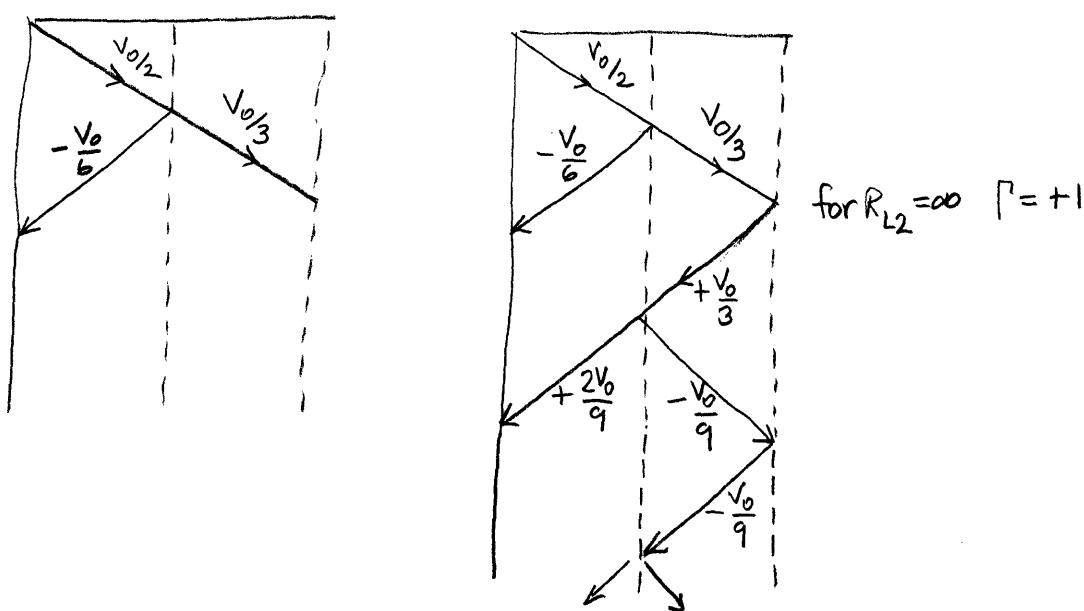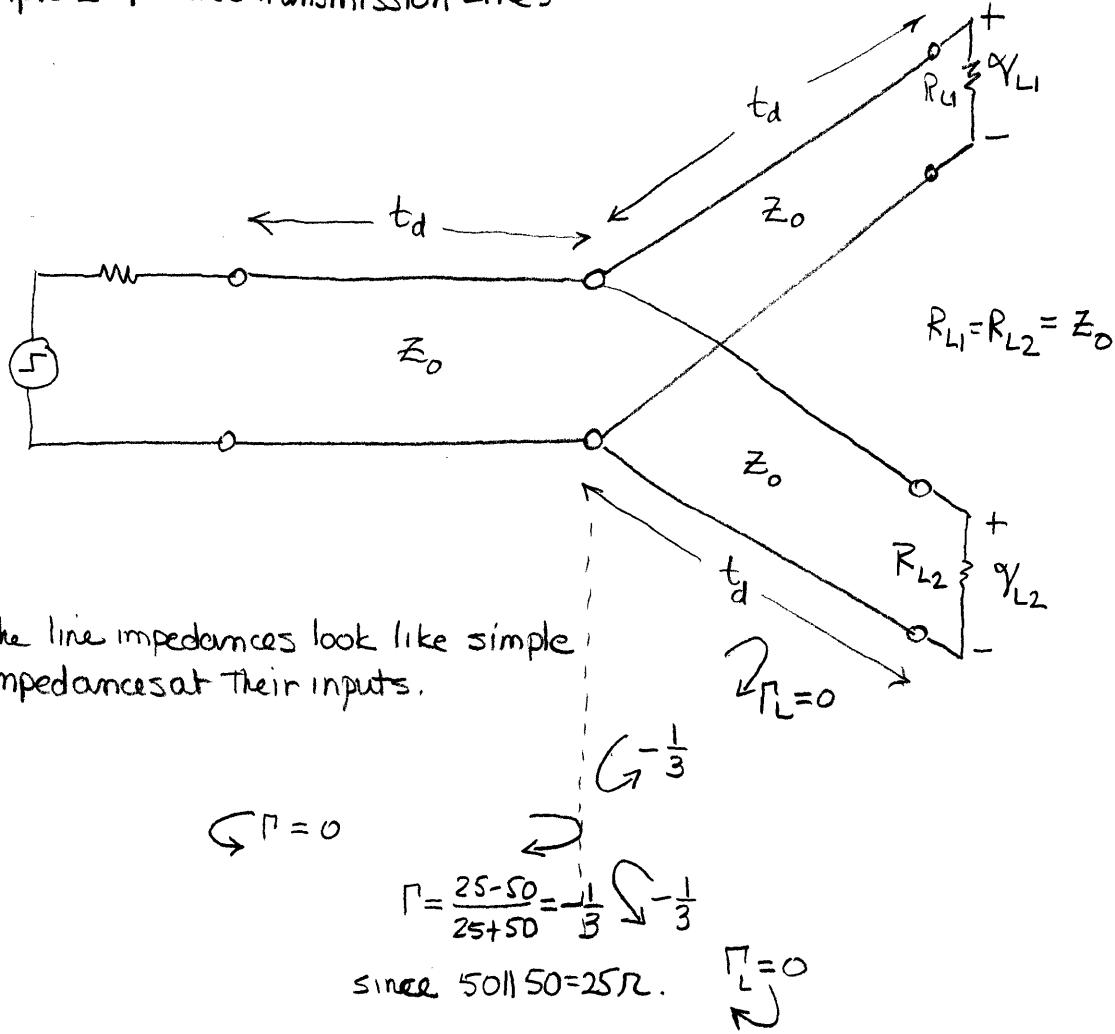


2.5 Reactive & Non-Linear Terminations

Examples:

- capacitive loading by busses
- inductive loading due to bonding wire inductances
- pins on IC packages, PCB vias, and variations in line width create inductances and capacitances

The solution is similar to our previous termination solutions but will involve integrals or derivatives

Analysis:

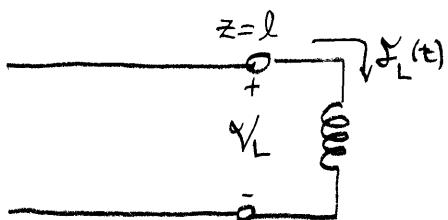

$$\text{For the load} \quad \gamma_L(t) = L \frac{d\mathcal{E}_L(t)}{dt}$$

For the transmission line

$$\begin{aligned} \gamma_L(t) &= \gamma_i^+(l,t) + \gamma_i^-(l,t) \\ \mathcal{E}_L(t) &= \mathcal{E}^+(l,t) + \mathcal{E}^-(l,t) = \frac{\gamma_i^+(l,t)}{Z_0} - \frac{\gamma_i^-(l,t)}{Z_0} \end{aligned}$$

Combining these

$$\gamma_i^+(l,t) + \gamma_i^-(l,t) = L \frac{d}{dt} \left(\frac{\gamma_i^+(l,t)}{Z_0} - \frac{\gamma_i^-(l,t)}{Z_0} \right)$$

Combining the + and - traveling waves gives

$$\frac{L}{Z_0} \frac{d\gamma_i^-(l,t)}{dt} + \gamma_i^-(l,t) = \frac{L}{Z_0} \frac{d\gamma_i^+(l,t)}{dt} - \gamma_i^+(l,t)$$

$$\underbrace{\frac{d\gamma_i^-(l,t)}{dt} + \frac{Z_0}{L} \gamma_i^-(l,t)}_{\text{this is simply a first order D.E. for the reflection.}} = \underbrace{\frac{d\gamma_i^+(l,t)}{dt} - \frac{Z_0}{L} \gamma_i^+(l,t)}_{\text{we assume this is known since it is coming from the source}}$$

this is simply a first order D.E. for the reflection.

we assume this is known since it is coming from the source

Let's assume the incident wave is a step as we have been doing

$$\gamma_i^+(l,t) = V_0$$

The D.E. at the load is then

$$\frac{d\gamma_i^-(l,t)}{dt} + \frac{Z_0}{L} \gamma_i^-(l,t) = -\frac{Z_0}{L} V_0$$


The solution is then the sum of the homogeneous & transient solution

$$\gamma_i^-(l,t) = -V_0 + K e^{-\frac{Z_0 t}{L}}$$



To determine K we note that at $t=0$ $\gamma_i^-(t=0) = 0$. This is equivalent to an open circuit and we know that KCL gives $\gamma_i^-(l,t=0) = V_0$, i.e., it's completely reflected.

$$\text{For } \gamma_i^-(l,t=0) = 0 \quad K = 2V_0$$

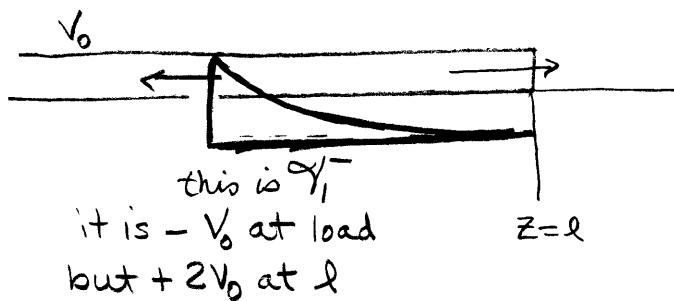
$$\therefore \gamma_i^-(l,t=0) = -V_0 + 2V_0 e^{-\frac{Z_0 t}{L}}$$



Overall, the sum looks like this

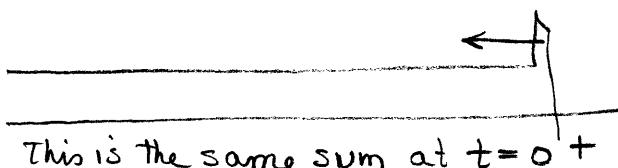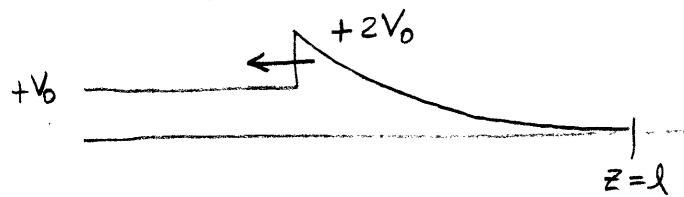

Example 2-10. Lossy capacitative load

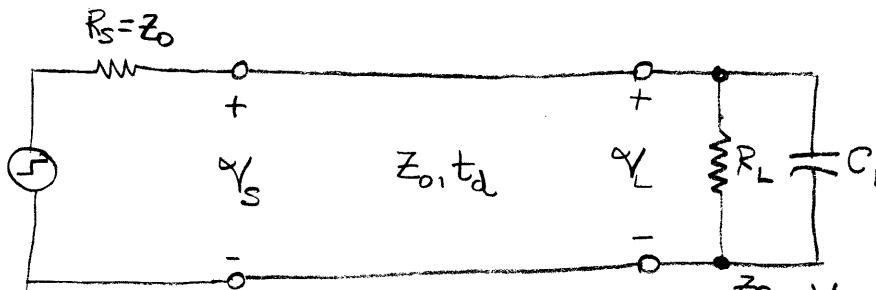

The wave launched on the line is $\mathcal{Y}_i^+(0,0) = \frac{Z_0}{Z_0 + Z_0} V_0 = \frac{1}{2} V_0$
 We write the voltage and current equations at the load.

$$\mathcal{Y}_L(t) = \mathcal{Y}_i^+(l, t) + \mathcal{Y}_i^-(l, t)$$

$$\mathcal{I}_L(t) = \mathcal{Y}_i^+(l, t) + \mathcal{Y}_i^-(l, t) = \frac{\mathcal{Y}_i^+(l, t)}{Z_0} - \frac{\mathcal{Y}_i^-(l, t)}{Z_0}$$

The load equation is given by KCL as

$$\mathcal{I}_L(t) = \frac{\mathcal{Y}_L(t)}{R_L} + C_L \frac{d\mathcal{Y}_L(t)}{dt}$$

We do algebra to get the D.E. at the load.

$$\frac{\mathcal{Y}_i^+(l, t)}{Z_0} - \frac{\mathcal{Y}_i^-(l, t)}{Z_0} = \frac{\mathcal{Y}_i^+(l, t)}{R_L} + \frac{\mathcal{Y}_i^-(l, t)}{R_L} + C_L \frac{d}{dt} [\mathcal{Y}_i^+(l, t) + \mathcal{Y}_i^-(l, t)]$$

$$\frac{1}{C_L} \left[\frac{\mathcal{Y}_i^-(l, t)}{Z_0} + \frac{\mathcal{Y}_i^-(l, t)}{R_L} + C_L \frac{d\mathcal{Y}_i^-(l, t)}{dt} \right] = \frac{\mathcal{Y}_i^+(l, t)}{Z_0} - \frac{\mathcal{Y}_i^+(l, t)}{R_L} - C_L \frac{d\mathcal{Y}_i^+(l, t)}{dt}$$

$$\frac{d\mathcal{Y}_i^-(l, t)}{dt} + \left[\frac{1}{C_L Z_0} + \frac{1}{C_L R_L} \right] \mathcal{Y}_i^-(l, t) = - \frac{d\mathcal{Y}_i^+(l, t)}{dt} + \left[\frac{1}{C_L Z_0} - \frac{1}{C_L R_L} \right] \mathcal{Y}_i^+(l, t)$$

As before we have a step, this time of magnitude $\frac{1}{2} V_0$

Under these conditions it becomes

$$\frac{d\mathcal{Y}_i^-(l, t)}{dt} + \left(\frac{R_L + Z_0}{R_L Z_0} \right) \frac{1}{C_L} \mathcal{Y}_i^-(l, t) = \frac{R_L - Z_0}{R_L Z_0} \frac{1}{C_L} \frac{V_0}{2}$$

the $\frac{d\mathcal{Y}_i^+(l, t)}{dt}$ term disappears because the incident voltage is constant in time
 $- \frac{R_L + Z_0}{R_L Z_0} \frac{1}{C_L} (t - t_d)$

The general solution is $\mathcal{Y}_i^-(l, t) = K_1 + K_2 e^{-\frac{1}{C_L} (t - t_d)}$

↑
 since the wave started at $z=0$ at $t=0$

The capacitor is initially a short circuit giving $\gamma_1^-(l, t_d) + \gamma_1^+(l, t_d) = 0$

$$\text{or } \gamma_1^-(l, t_d) = -\gamma_1^+(l, t_d) = -\frac{V_o}{Z}$$

After a long time the capacitor is fully charged and γ^+ sees only the resistor. This is a resistive termination R_L and

$$\gamma_1^-(l, \infty) = R_L \gamma_1^+(l, \infty) = \frac{R_L - Z_0}{R_L + Z_0} \gamma_1^+(l, \infty) = \frac{R_L - Z_0}{R_L + Z_0} \frac{V_o}{Z}$$

We can use these initial conditions to write the general solution

$$\gamma_1^-(l, \infty) = \frac{R_L - Z_0}{R_L + Z_0} \frac{V_o}{Z} = K_1$$

$$\gamma_1^-(l, t_d) = K_1 + K_2 = -\frac{V_o}{Z}$$

$$\begin{aligned} K_2 &= -\frac{V_o}{Z} - K_1 = -\frac{V_o}{Z} - \frac{R_L - Z_0}{R_L + Z_0} \frac{V_o}{Z} \\ &= -\frac{V_o}{Z} \left[1 + \frac{R_L - Z_0}{R_L + Z_0} \right] = -\frac{V_o}{Z} \left[\frac{R_L + Z_0 + R_L - Z_0}{R_L + Z_0} \right] = -\frac{V_o R_L}{R_L + Z_0} \end{aligned}$$

$$\gamma_1^-(l, t) = \frac{R_L - Z_0}{R_L + Z_0} \frac{V_o}{Z} - \frac{V_o R_L}{R_L + Z_0} e^{-\frac{R_L + Z_0}{R_L Z_0} \frac{1}{C_L} (t - t_d)}$$



However, this is more useful to write in terms of $\gamma^+ = \frac{V_o}{Z}$

$$\gamma_1^-(l, t) = \gamma_1^+(l, t) \left[\frac{R_L - Z_0}{R_L + Z_0} - \frac{2 R_L}{R_L + Z_0} e^{-\frac{R_L + Z_0}{R_L Z_0} \frac{1}{C_L} (t - t_d)} \right]$$


It will look like this



Our book likes to plot both $\alpha V_L(t)$ and $\alpha V_s(t)$

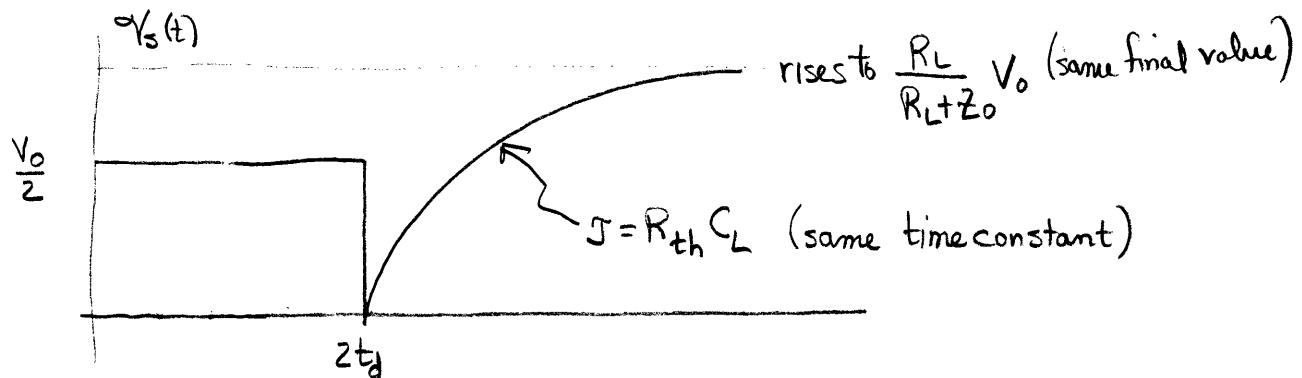
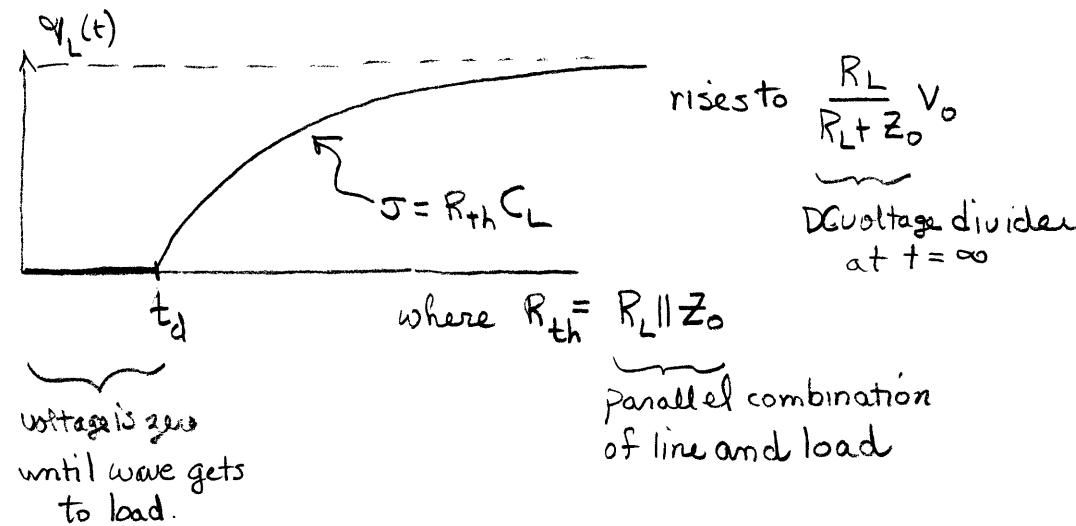


Example 2-11

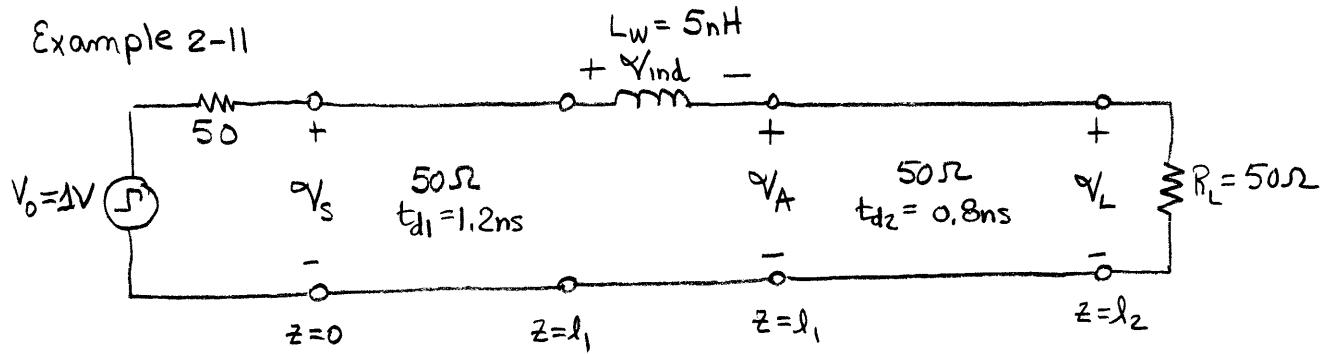

This is an example of how transmission lines might be connected together by a jumper.

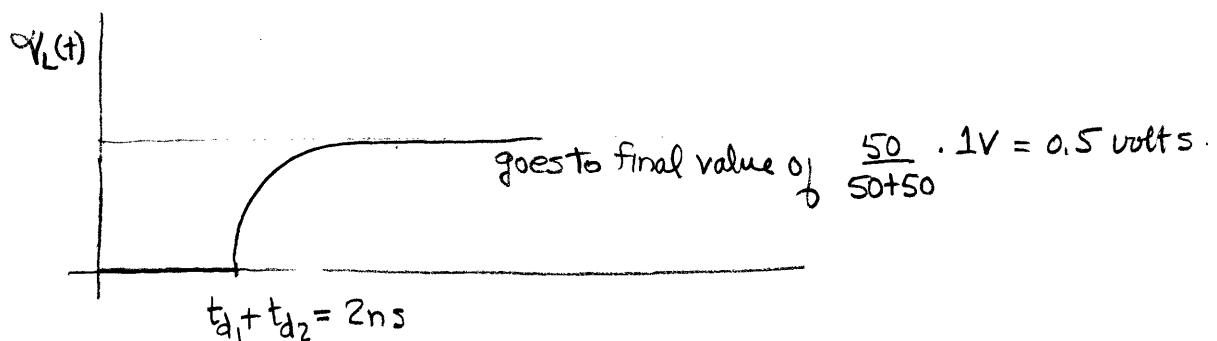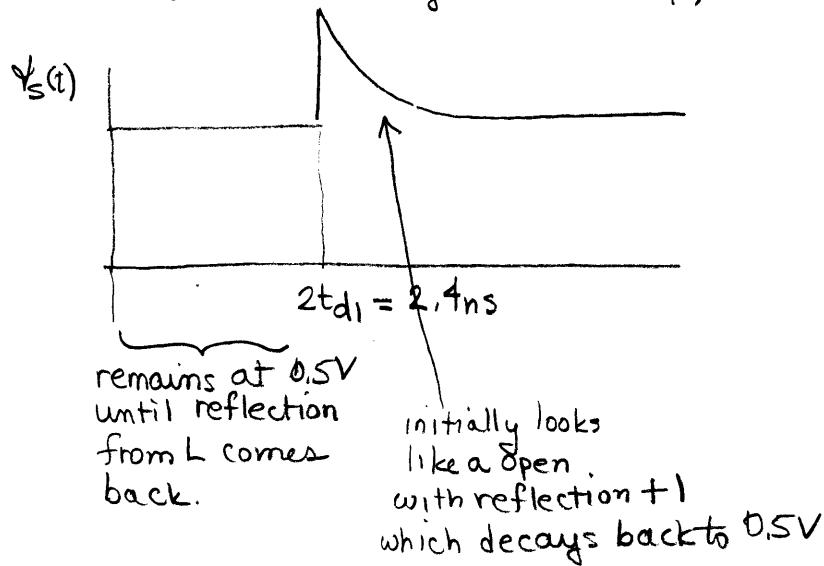
Because $z_0 = 50\Omega$ a voltage wave $\mathcal{V}^+(z,t) = 0.5V$ is launched.



2.5.2 Non-linear Terminations

Bergeron graphical technique

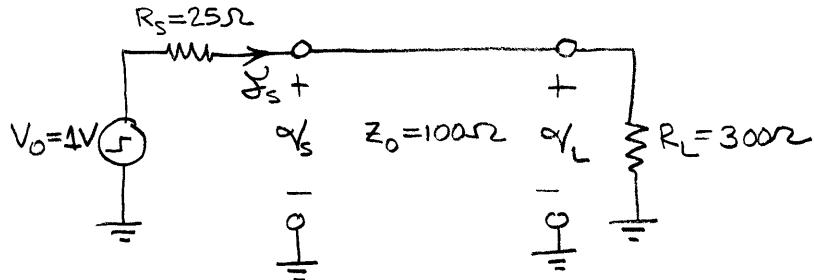
Example 2-13 Graphical solution of resistively terminated line



① Plot $i-v$ characteristics of source and load

$$\text{@ source } \gamma_s = V_0 - R_s \gamma_s = 1 - 25 \gamma_s \quad \gamma_s = -40 \gamma_s + 40 \text{ (mA)}$$
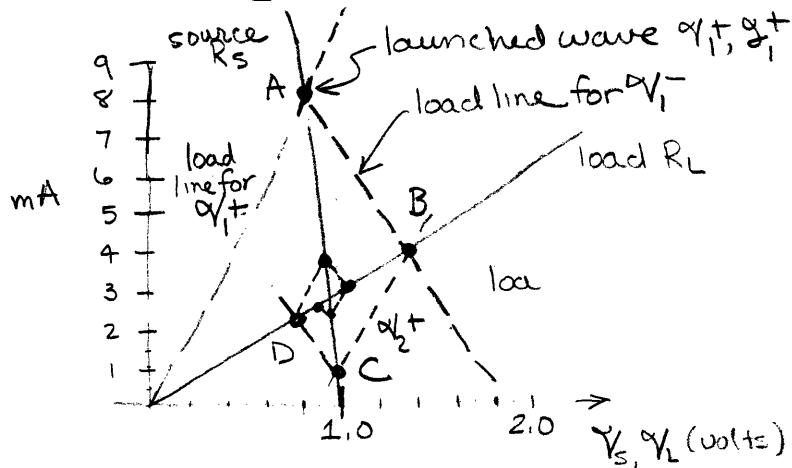
$$\text{@ load } \gamma_L = R_L \gamma_L = 300 \gamma_L \quad I_L = \frac{10}{3} \gamma_L \text{ (mA)}$$



- A: γ_s^+ , γ_s^+ @ $t=0$ (0.8V, 8mA)
- B: γ_L^+ , γ_L^+ @ $t=t_d$ (0.4V, 4mA)
- C: γ_s^+ , γ_s^+ @ $t=2t_d$ (0.96V, 1.6mA)

② Launch γ_1^+ . Since it is in line $\gamma_1^+ = \frac{\gamma_1^+}{Z_0} = \frac{\gamma_1^+}{100} = 10\gamma_1^-$ (mA)

③ Intersection of γ_1^+ and source load lines is wave launched.

This gives what we previously got by voltage divider.

Intersection is $\gamma_1^+ = 0.8V$, $\gamma_1^- = 8\text{mA}$.

④ Add in load line for γ_1^- generated at $t=t_d$.

This load line has slope $-\frac{1}{Z_0} = -\frac{1}{100}$. Negative since -direction.

⑤ Consider reflection back to source. Reflection reaches source at $t=2t_d$ generating γ_2^+ , γ_2^-

$$\text{Total voltage } \gamma_s = \underbrace{\gamma_1^+ + \gamma_1^-}_{\text{This is the voltage } V_B \text{ at the load}} + \gamma_2^+ = V_B + \gamma_2^+$$

This is the voltage V_B at the load

$$\text{total current } \mathcal{I}_s = \underbrace{\mathcal{I}_1^+ + \mathcal{I}_1^-}_{\text{This is } I_B \text{ from load}} + \mathcal{I}_2^+ = I_B + \mathcal{I}_2^+$$

At the line input $\mathcal{I}_2^+ = \frac{\gamma_2^+}{Z_0}$

Substituting results gives

$$\mathcal{I}_s - I_B = \frac{\gamma_s - V_B}{Z_0}$$

This is the equation of a line passing through (V_B, I_B) with slope $\frac{1}{Z_0}$ and described $\gamma_2^+, \mathcal{I}_2^+$. This load line intersects the source load line at C, which is about $\gamma_s = 0.96V$, $\mathcal{I}_s = 1.6mA$

- ⑥ Reflection at source gives γ_2^- back towards load with slope $-\frac{1}{Z_0} = -\frac{1}{100}$


This gives D.

- ⑦ Repeat process until converges.

- Each dashed line is the load line for a + or - z directed traveling wave with slope $\pm \frac{1}{Z_0}$.
- Intersection with source or load load lines defines launch of new wave by reflection.
- Converges to steady state values.

NOTE: You would have to calculate γ_n^+ , γ_n^- from sum of voltages at each reflection

Example 2-14 Nonlinear termination

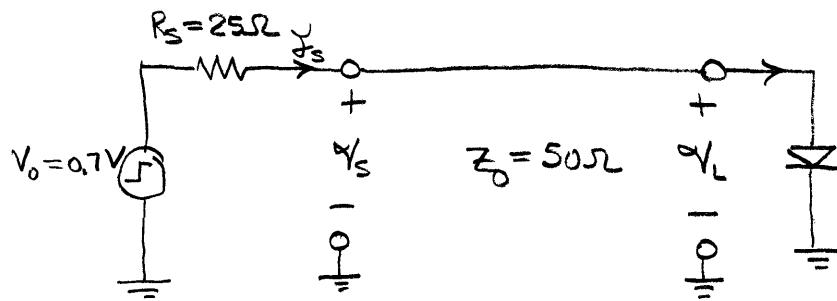


source load line

$$V_o - 25I_s = V_s$$

$$I_s = \frac{V_s - V_o}{-25}$$

$$I_s = -40V_s + 28 \text{ (mA)}$$

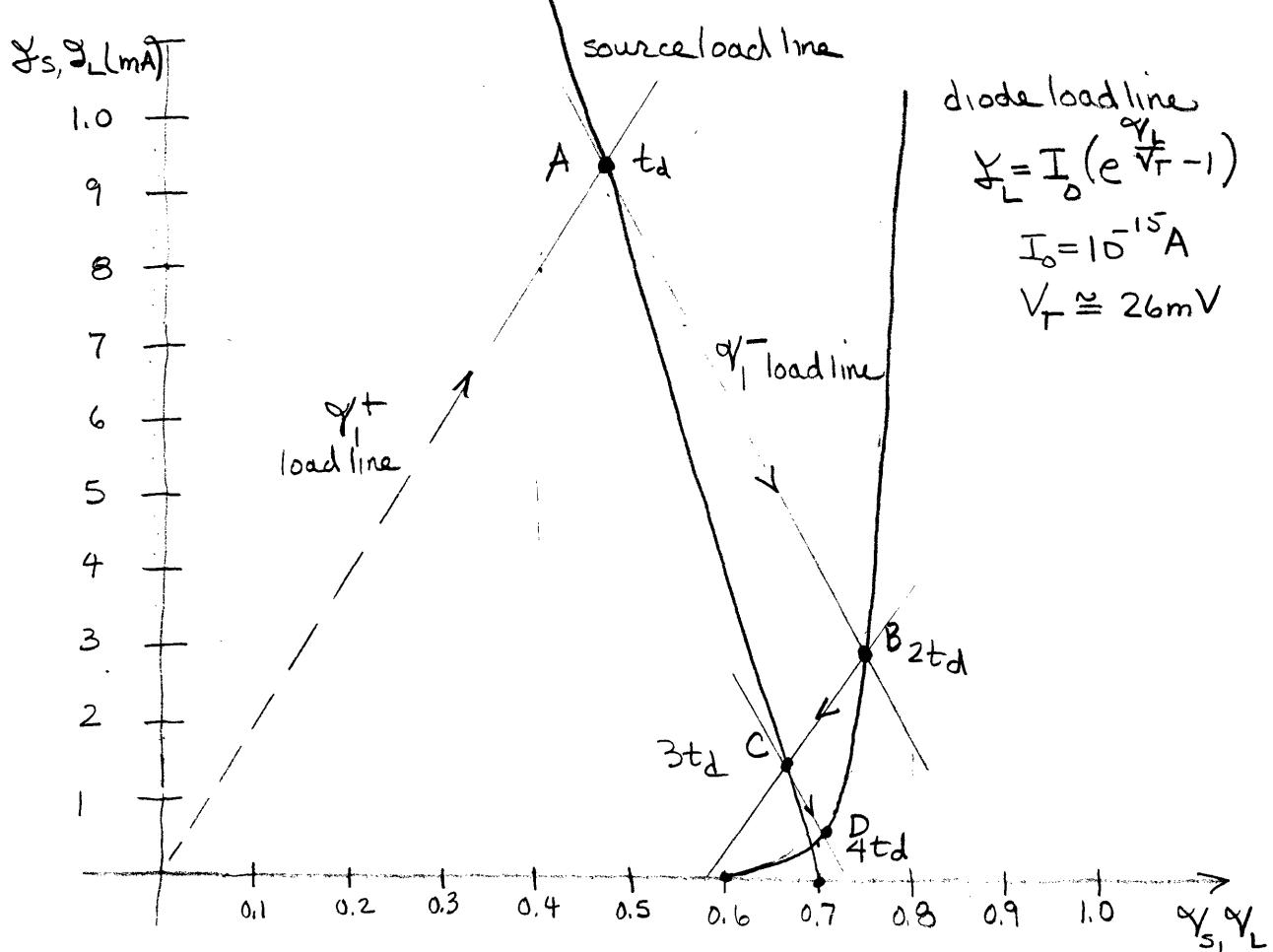


Easy to draw keeping slopes the same $\pm \frac{1}{Z_0} = \pm \frac{1}{50}$







Converges to steady state values $V_s = V_L = 0.6912 \text{ Volts}$
and $I_s = I_L \approx 0.35 \text{ mA}$ in about $4t_d$.

Neglected capacitance of diodes.


2.6.1. Time Domain Reflectometry

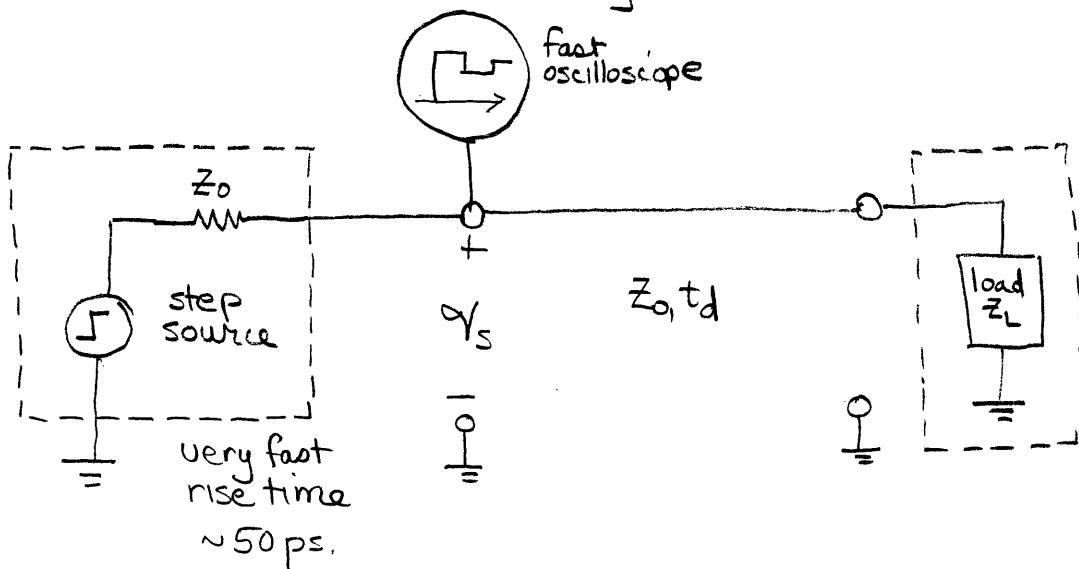

Waveforms will depend upon load

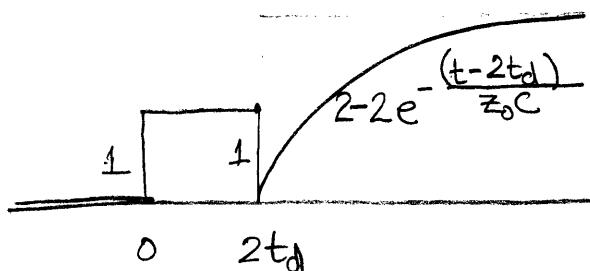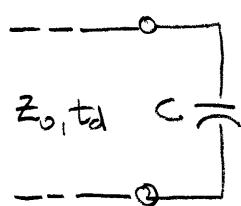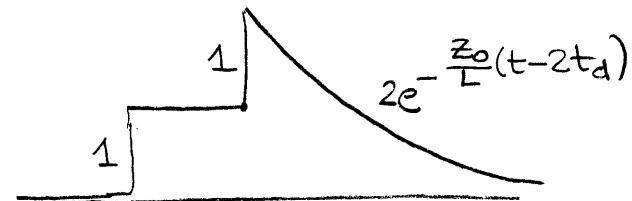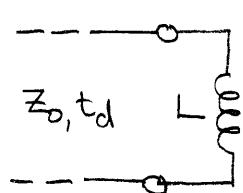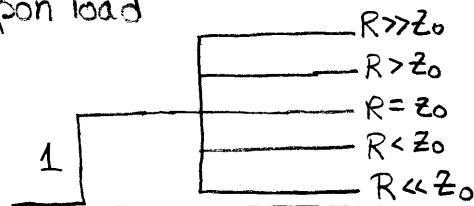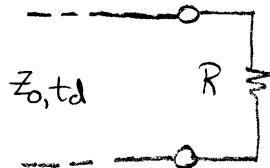

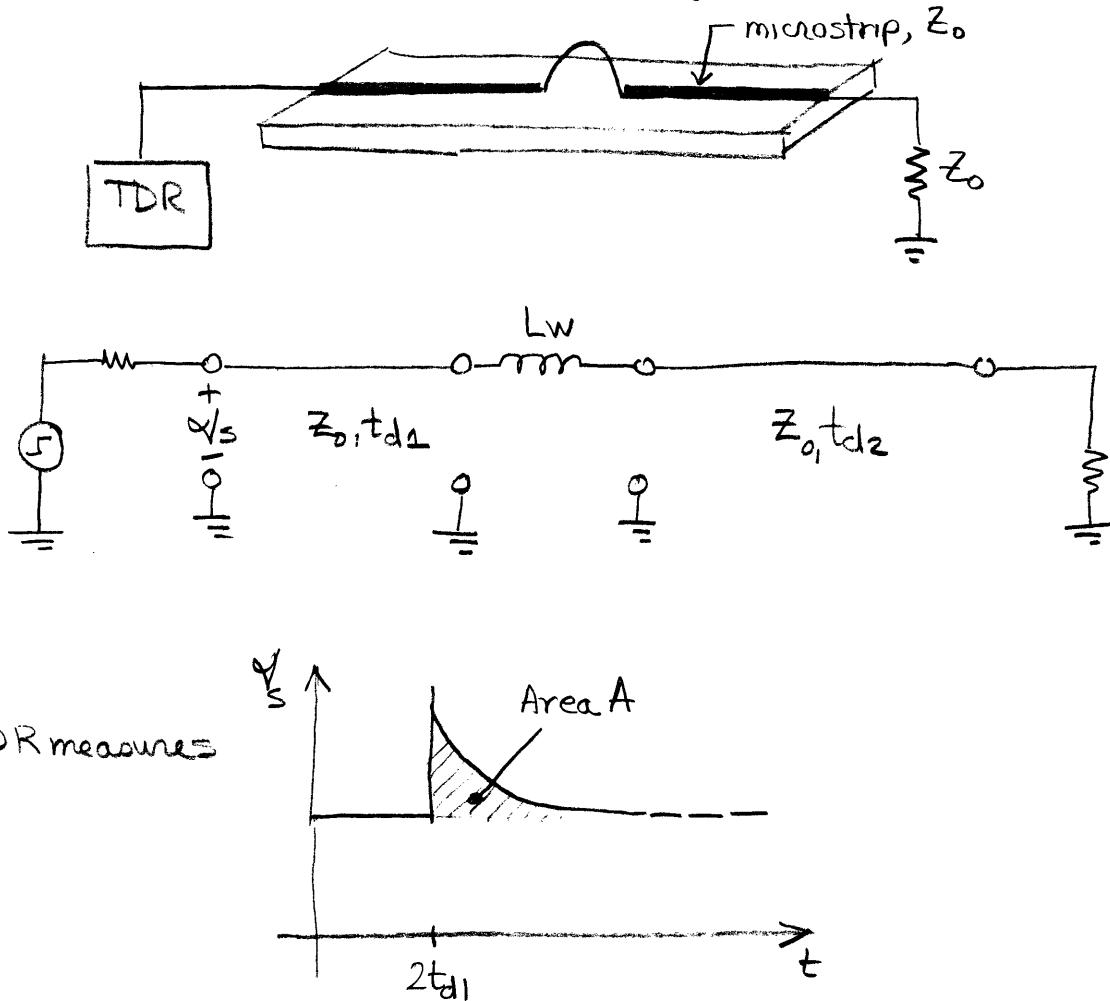Example 2-16 TDR measurement of bonding wire inductance



You would immediately think of fitting exponential to waveform.

Already know V_s from Example 2-11


$$V_s(+)=\begin{cases} \frac{V_0}{2} & 0 < t < 2t_{d1}, \\ \frac{V_0}{2} [1 + e^{-2\frac{Z_0}{L_w}(t-2t_{d1})}] & t \geq 2t_{d1}, \end{cases}$$

More accurate to integrate Area under curve to get A


$$A = \int_{2t_{d1}}^{\infty} \frac{V_0}{2} e^{-2\frac{Z_0}{L_w}(t-2t_{d1})} dt = \underbrace{\frac{V_0}{2} \int_0^{\infty} e^{-2\frac{Z_0}{L_w}t'} dt'}_{\text{use } t' = t - 2t_{d1}} = -\frac{L_w V_0}{4Z_0} \Big|_0^{\infty}$$

$$A = \frac{L_w V_0}{4Z_0} \Rightarrow L_w = \frac{4Z_0 A}{V_0}$$


2.7 Transmission Line Parameters

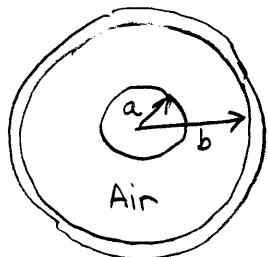

coaxial

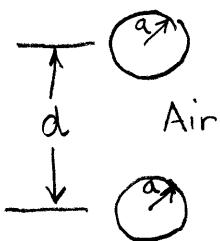

two-line

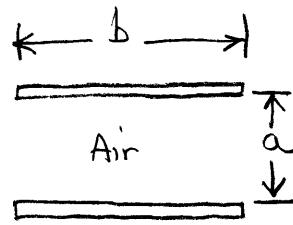Parallel Plate⁺

$$L(\mu\text{H/m}) \quad 0.2 \ln\left(\frac{b}{a}\right) \quad 0.4 \ln\left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1}\right]$$

$$\frac{1.26a}{b}$$

$$c(\text{PF/m}) \quad \frac{55.6}{\ln\left(\frac{b}{a}\right)} \quad \frac{27.8}{\ln\left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1}\right]}$$

$$\frac{8.85b}{a}$$

$$R(\Omega/\text{m}) \quad \frac{4.15 \times 10^8 (a+b)\sqrt{f}}{ab} \quad \frac{8.3 \times 10^{-8} \sqrt{f}}{a} \quad \frac{5.22 \times 10^{-7} \sqrt{f}}{b}$$

$$G^{**}(\text{s/m}) \quad \frac{7.35 \times 10^{-4}}{\ln\left(\frac{b}{a}\right)} \quad \frac{3.67 \times 10^{-4}}{\ln\left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1}\right]} \quad \frac{1.17 \times 10^{-4} b}{a}$$

$$Z_0(\Omega) \quad 60 \ln\left(\frac{b}{a}\right) \quad 120 \ln\left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a}\right)^2 - 1}\right] \quad \frac{377a}{b}$$

* Valid for $b \gg a$

** For polyethylene at 3GHz

Example 2-18 TV antenna twin-lead

$$a \sim 1\text{ mm}$$

$$d \sim 0.7\text{ cm}$$

Assume dielectric constant of plastic approximates air

$$f = 200\text{ MHz}$$

This is a two-wire line.

$$L = 0.4 \ln \left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right] = 0.4 \ln \left[\frac{7}{2} + \sqrt{\left(\frac{7}{2} \right)^2 - 1} \right] \cong 1.05 \mu\text{H/m}$$

$$C = \frac{27.8}{m \left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right]} = \frac{27.8}{m \ln \left[\frac{7}{2} + \sqrt{\left(\frac{7}{2} \right)^2 - 1} \right]} \cong 10.6 \text{ pF/m}$$

$$R = \frac{8.3 \times 10^{-8} \sqrt{f}}{a} = \frac{8.3 \times 10^{-8} \sqrt{200 \times 10^6}}{(1 \times 10^{-3})} \cong 2.35 \Omega/\text{m}$$

$$Z_0 = 120 \ln \left[\frac{d}{2a} + \sqrt{\left(\frac{d}{2a} \right)^2 - 1} \right] = 120 \ln \left[\frac{7}{2} + \sqrt{\left(\frac{7}{2} \right)^2 - 1} \right] \cong 316 \Omega$$

This is often called 300 Ω twin lead even though it is actually 316 Ω .