

## Chapter 3 Steady-State Waves on Transmission Lines

We can still use the lossless transmission line equations.

$$\frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t}$$

use phasors for sinusoidal steady state

assume  $V(z,t) = \operatorname{Re} \{V(z)e^{j\omega t}\}$

$$I(z,t) = \operatorname{Re} \{I(z)e^{j\omega t}\}$$

Substituting

$$\frac{dV(z)}{dz} e^{j\omega t} = -L j\omega I(z) e^{j\omega t}$$

$$\frac{dI(z)}{dz} e^{j\omega t} = -C j\omega V(z) e^{j\omega t}$$

Simplifying  $\frac{dV(z)}{dz} = -j\omega L I(z)$

$$\frac{dI(z)}{dz} = -j\omega C V(z)$$

Combining

$$\frac{d^2V(z)}{dz^2} = -j\omega L \frac{dI(z)}{dz} = -j\omega L (-j\omega C V(z))$$

$$\frac{d^2V(z)}{dz^2} = -\omega^2 L C V(z) = -\beta^2 V(z) \text{ where } \beta = \omega \sqrt{LC}$$

$$\frac{d^2V(z)}{dz^2} = -\beta^2 V(z) \quad \begin{matrix} \text{complex wave equation} \\ \beta = \omega \sqrt{LC} \quad \text{phase constant} \end{matrix}$$

You also get

$$\frac{d^2I(z)}{dz^2} = -\beta^2 I(z)$$

The solutions are

$$V(z) = V^+ e^{-j\beta z} + V^- e^{+j\beta z}$$

$$I(z) = I^+ e^{-j\beta z} + I^- e^{+j\beta z} = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z}$$

$$\text{where } Z_0 = \frac{V^+}{I^+} = -\frac{V^-}{I^-} = \sqrt{\frac{L}{C}}$$

Equivalent time expressions are

$$V(z,t) = \operatorname{Re} \{ V(z) e^{j\omega t} \} = \operatorname{Re} \{ V^+ e^{-j\beta z} e^{j\omega t} + V^- e^{+j\beta z} e^{j\omega t} \}$$

$$V(z,t) = V^+ \cos(\omega t - \beta z) + V^- \cos(\omega t + \beta z)$$

You can also get

$$I(z,t) = \frac{V^+}{Z_0} \cos(\omega t - \beta z) - \frac{V^-}{Z_0} \cos(\omega t + \beta z)$$

Consider an infinitely long transmission line

$$\text{Then } V(z,t) = V^+ \cos(\omega t - \beta z)$$

$$V(z,t) = \frac{V^+}{Z_0} \cos(\omega t - \beta z)$$

The wave propagates in the  $+z$  direction at a velocity  $v_p$

$$\omega t - \beta z = \text{constant}$$


This is the velocity at which each point propagates.

$$\omega dt - \beta dz = 0 \quad \text{or} \quad \omega dt = \beta dz$$

$$v_p = \frac{dz}{dt} = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

The phase velocity is usually NOT a function of the geometry of the transmission line, but is a function of the material.

### 3.2. Open & Short Circuited Lines

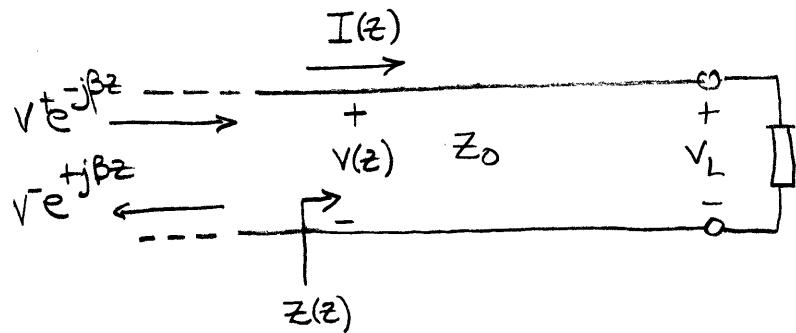

The total voltages and currents on the line are

$$V(z) = V^+ e^{-j\beta z} + V^- e^{+j\beta z}$$


$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z}$$

We can write the line impedance anywhere  $z$  on the line looking towards the load

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V^+ e^{-j\beta z} + V^- e^{+j\beta z}}{V^+ e^{-j\beta z} - V^- e^{+j\beta z}} = R(z) + jX(z)$$
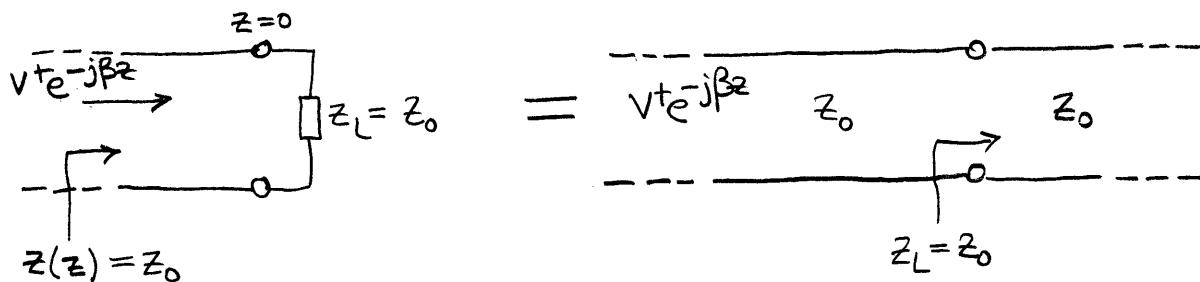
#### Example 3-1 Matched Load

A transmission line is terminated with a load  $Z_L$ . Find the line impedance  $Z(z)$  and the magnitude of the reflected wave  $V^-$




at  $z=0$  the load boundary condition looks just like the input to an infinitely long transmission line of impedance  $Z_0$

the impedance at any point  $Z(z) = Z_0$

there is no reflected wave since the boundary condition at the load is satisfied without it.

### 3.2.1 Short Circuited Line

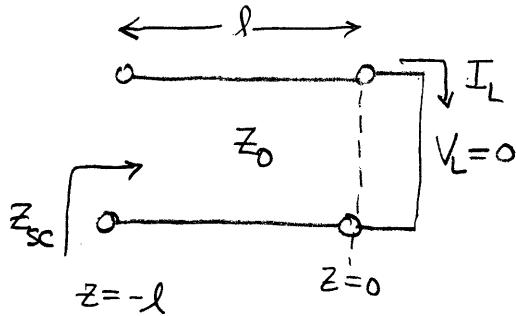

at the load  $V_L = \left[ V^+ e^{-j\beta z} + V^- e^{+j\beta z} \right]_{z=0} = V^+ + V^- = 0 \Rightarrow V^- = -V^+$

at the load  $I_L = \left[ \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z} \right]_{z=0} = \frac{1}{Z_0} V^+ - \frac{V^-}{Z_0} = \frac{2V^+}{Z_0}$

Everywhere else on the line

$$V(z) = V^+ (e^{-j\beta z} - e^{+j\beta z}) = -2V^+ j \sin(\beta z)$$

$$I(z) = \frac{V^+}{Z_0} (e^{-j\beta z} + e^{+j\beta z}) = +\frac{2V^+}{Z_0} \cos(\beta z)$$

where we use the Euler identity  $e^{j\theta} = \cos\theta + j\sin\theta$

The space-time function forms a standing wave

$$\begin{aligned} V(z,t) &= \operatorname{Re} \{ V(z) e^{j\omega t} \} = \operatorname{Re} \{ -2V^+ j \sin(\beta z) e^{j\omega t} \} \\ &= \operatorname{Re} \{ +2V^+ e^{-j\frac{\pi}{2}} \sin(\beta z) e^{j\omega t} \} \end{aligned}$$




$$V(z,t) = 2V^+ \sin(\beta z) \cos(\omega t - \frac{\pi}{2})$$

If  $V^+$  is complex, i.e.  $V^+ = |V^+| e^{j\phi^+}$  this becomes

$$V(z,t) = 2|V^+| \sin(\beta z) \cos(\omega t - \frac{\pi}{2} + \phi^+)$$

You can repeat this for the current to get

$$I(z,t) = \frac{2|V^+|}{Z_0} \cos(\beta z) \cos(\omega t)$$

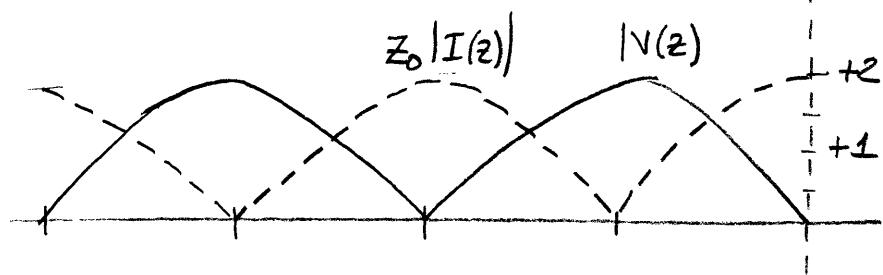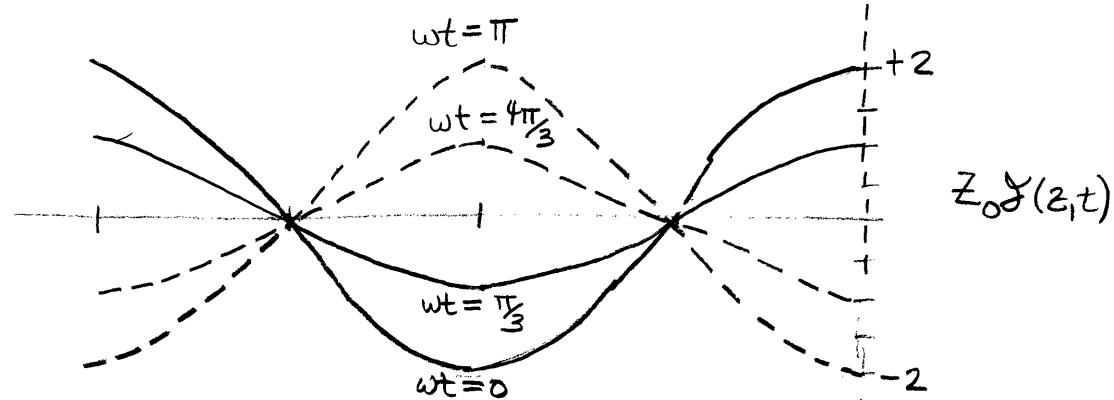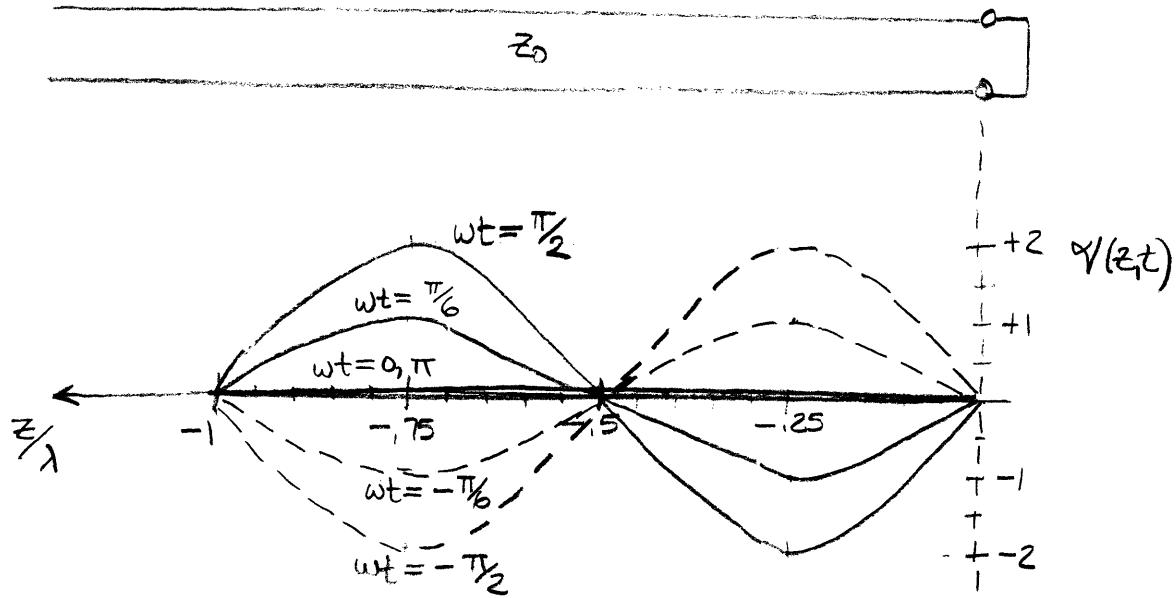


The line impedance is

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{-2jV^+ \sin(\beta z)}{2V^+ \cos(\beta z)} = -jZ_0 \tan(\beta z)$$

The input impedance where  $z = -l$  is given by

$$Z_{sc} = jZ_0 \tan(\beta l) = jX_{sc}$$

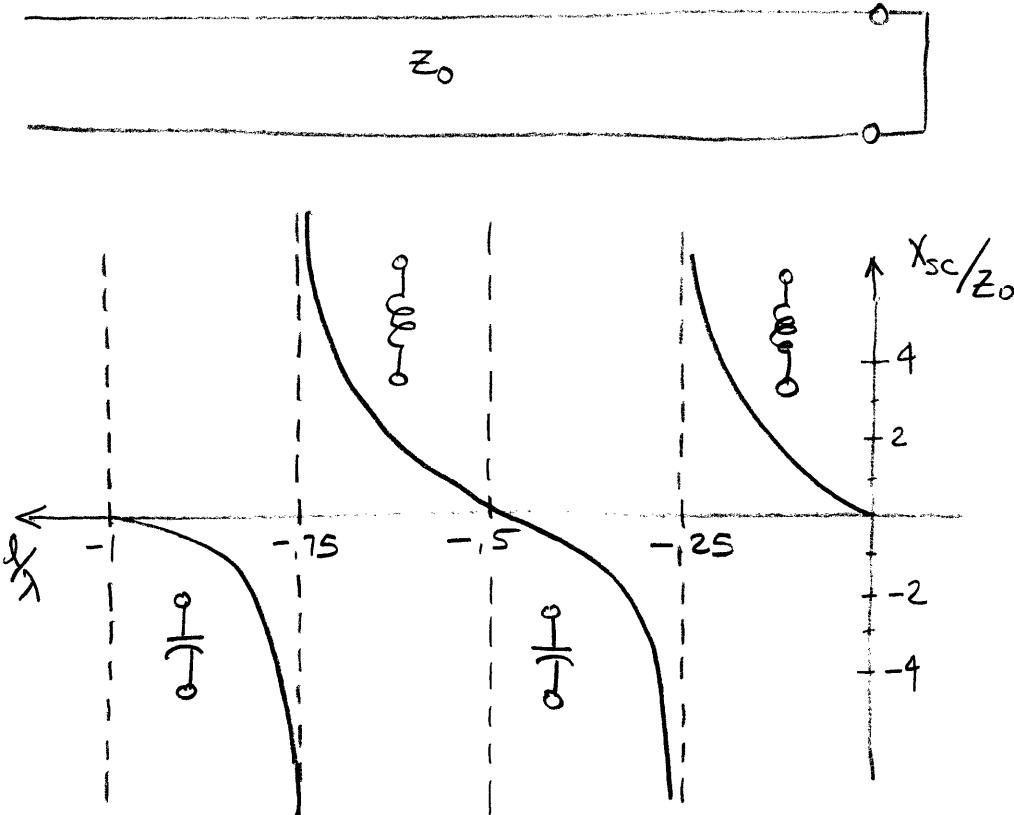

Example 3-2 Short circuit antenna twin-lead

$\lambda = 10\text{cm}$ ,  $Z_0 = 300\Omega$ , shorted at one end

Find the input impedance at 300 MHz

$$\lambda = \frac{v_p}{f} = \frac{3 \times 10^8}{300 \times 10^6} = 1\text{m.}$$

$$\frac{l}{\lambda} = \frac{0.1\text{m}}{1\text{m}} = 0.1$$

$$Z_{sc} = jZ_0 \tan(\beta l) = j(300) \tan\left(\frac{2\pi}{\lambda} \cdot 0.1\lambda\right) \cong j218\Omega$$


The equivalent lumped impedance is

$$X_{sc} = \omega L_{sc} = 218$$

$$L_{sc} = \frac{X_{sc}}{\omega} = \frac{218}{2\pi(300 \times 10^6)} = 0.116\text{ }\mu\text{H}$$

### 3.2.2. Open circuited line

Analysis similar to short circuited line

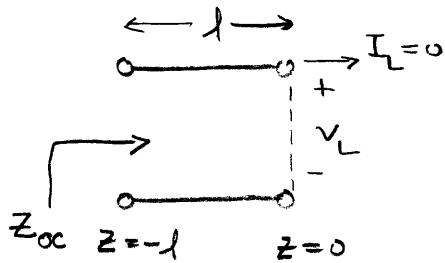

$$\text{at the load } I_L = I(z=0) = \left[ \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{+j\beta z} \right]_{z=0}$$

$$I_L = \frac{V^+ - V^-}{Z_0} = 0 \Rightarrow V^+ = V^-$$

The load voltage can be computed as

$$V_L = V(z=0) = \left[ V^+ e^{-j\beta z} + V^- e^{+j\beta z} \right]_{z=0} = V^+ + V^- = 2V^+$$

We can use  $V^+ = V^-$  to determine  $V$  and  $I$  anywhere along the line

$$V(z) = V^+ e^{-j\beta z} + V^+ e^{+j\beta z} = 2V^+ \cos(\beta z)$$

$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^+}{Z_0} e^{+j\beta z} = -2j \frac{V^+}{Z_0} \sin(\beta z) = +2e^{-j\frac{\pi}{2}} \frac{V^+}{Z_0} \sin(\beta z)$$

In the time domain

$$\Re\{V(z)e^{j\omega t}\} = 2|V^+| \cos(\beta z) \cos(\omega t)$$


$$\Im\{I(z)e^{j\omega t}\} = 2\frac{|V^+|}{Z_0} \sin(\beta z) \cos(\omega t - \frac{\pi}{2})$$

$$\text{where } V^+ = |V^+| e^{j\phi^+}, \text{ Assumed } \phi^+ = 0$$


The line impedance looking towards the open is

$$Z(z) = \frac{V(z)}{I(z)} = +j Z_0 \cot(\beta z)$$
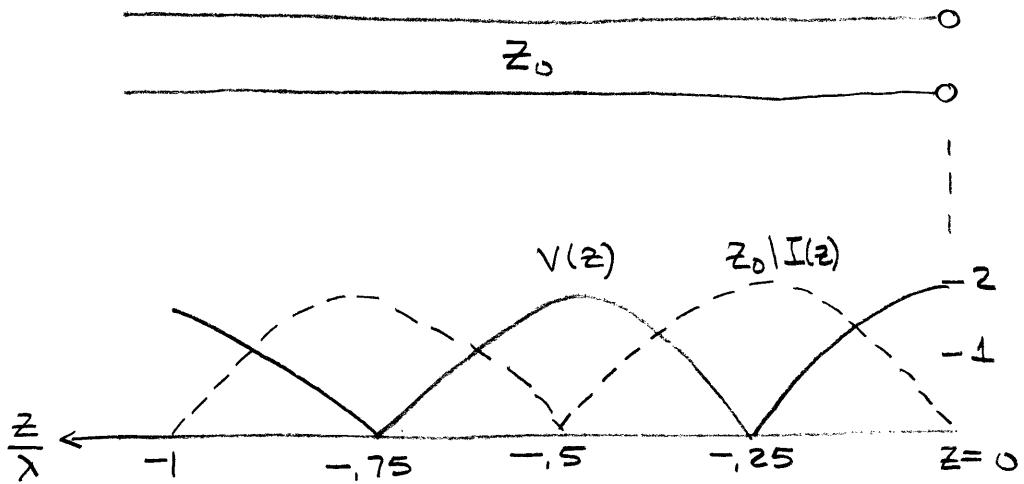
$$Z_{oc} = Z(z=-l) = -j Z_0 \cot(\beta l) = j X_{oc}$$



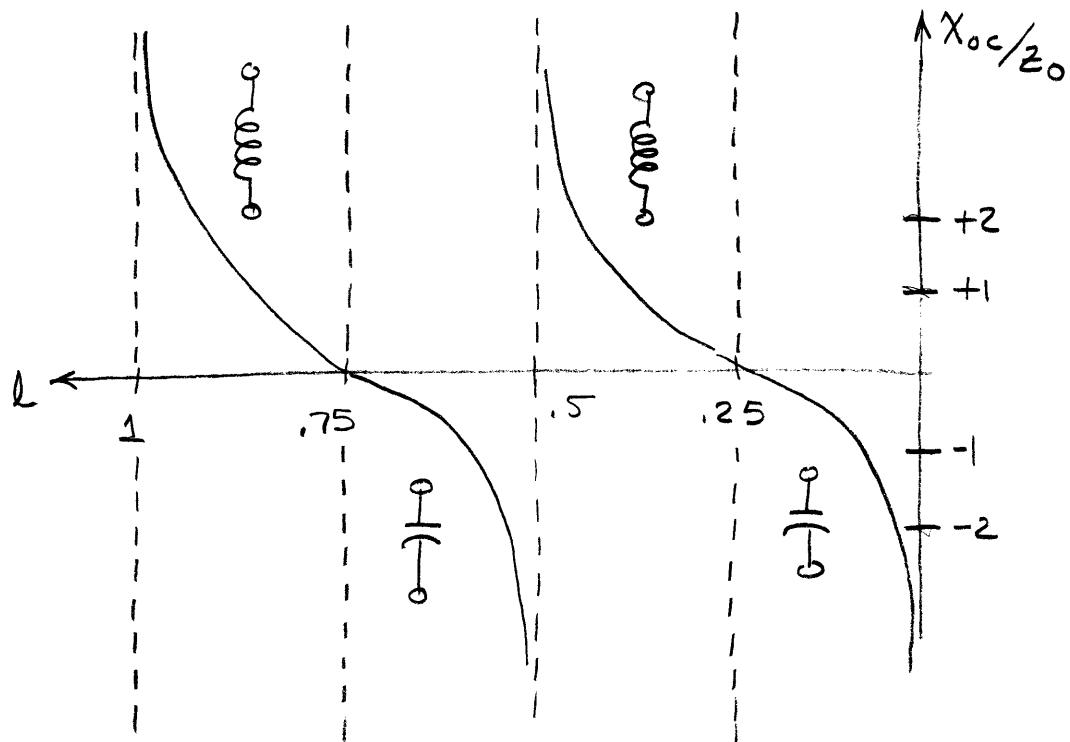This is very similar to the results for the short circuited line, except they are  $90^\circ$  different  
We have  $I(z)=0$  at  $z=0$



Just like for the short circuit, an open circuit can look capacitive or inductive depending upon the length  $l$  of the line.

### Example 3-3

Consider a  $l = 20\text{cm}$  length of television lead-in ( $z_0 = 300\Omega$ )

Assume it is connected to nothing (i.e., open circuit)

What is the input impedance of this line at 300 MHz?

For an open

$$z_{oc} = -j z_0 \cot(\beta l) = -j z_0 \cot\left(\frac{2\pi}{\lambda} l\right)$$

The electrical length is calculated as

$$\lambda = \frac{v_p}{f} = \frac{3 \times 10^8}{300 \times 10^6} = 1\text{m}$$

$$\frac{l}{\lambda} = \frac{0.20\text{m}}{1\text{m}} = 0.2$$

$$\therefore z_{oc} = -j 300 \cot(0.2 \cdot 2\pi) = -j 97,476 \Omega$$

As the frequency increases we can start to use transmission lines to replace lumped inductors and capacitors

Also as  $f$  increases the size of the transmission lines decreases. Typically we can use transmission lines as circuit elements from 1 to 100 GHz.

### Example 3-4

A short-circuited transmission line with  $v_p = 2.07 \times 10^8 \text{ m/s}$  is to be designed to provide a 15 nH inductance at 3 GHz.

(a) Find the shortest possible length  $l$  if  $Z_0 = 50 \Omega$ .

The impedance of a 15 nH inductor at 3 GHz is

$$Z = j\omega L = j 2\pi(3 \times 10^9)(15 \times 10^{-9}) = j 282.75 \Omega$$

The impedance at the input of a short-circuited line is

$$Z_{sc} = j Z_0 \tan \left( \frac{2\pi}{\lambda} l \right)$$

$$\text{The wavelength is } \lambda = \frac{v_p}{f} = \frac{2.07 \times 10^8}{3 \times 10^9} = 0.069 \text{ m}$$

We can then calculate  $l$  as

$$j 282.75 = j 50 \tan(91.061l)$$

$$\tan(91.061l) = 5.655$$

$$91.061l = 1.396$$

$$l = 1.53 \text{ cm}$$

(b) What is the equivalent lumped element at 4 GHz of this line?

$$\text{At } 4 \text{ GHz } \lambda = \frac{v_p}{f} = \frac{2.07 \times 10^8}{4 \times 10^9} = 0.052 \text{ m}$$


$$Z_{sc} = j 50 \tan \left( \frac{2\pi}{0.052} \cdot 0.153 \right) = j 50 (-3.51) = -j 175.26 \Omega$$

The equivalent capacitance is

$$\frac{1}{j\omega C} = -j \frac{1}{2\pi(4 \times 10^9)C} = -j 175.26$$

$$\therefore C = \frac{1}{2\pi(4 \times 10^9)(175.26)} = \frac{1}{4.40 \times 10^9} = 0.227 \text{ pF.}$$
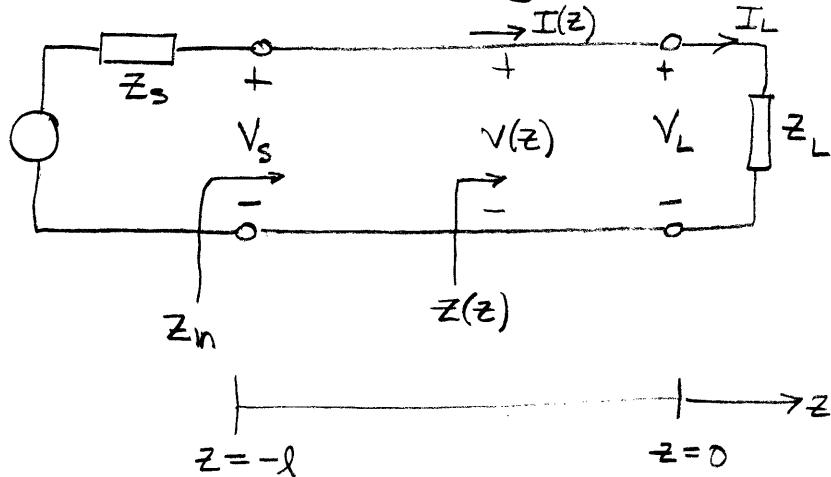
### 3.3 Lines terminated in an arbitrary impedance



The voltage and current anywhere on the line are

$$V(z) = V^+ e^{-j\beta z} + V^- e^{+j\beta z}$$

$$I(z) = \frac{1}{z_0} (V^+ e^{-j\beta z} - V^- e^{+j\beta z})$$

At the load

$$V_L = Z_L I_L$$

$$V(z)|_{z=0} = Z_L I(z)|_{z=0}$$

$$V^+ + V^- = Z_L \frac{1}{z_0} (V^+ - V^-)$$

$$Z_L = Z_0 \frac{V^+ + V^-}{V^+ - V^-}$$

The voltage reflection coefficient at the load is defined as  $\Gamma_L = \frac{V^-}{V^+}$

Solving the load relationship for  $\frac{V^-}{V^+}$  gives

$$Z_L V^+ - Z_L V^- = Z_0 V^+ + Z_0 V^-$$

$$Z_L V^+ - Z_0 V^+ = Z_L V^- + Z_0 V^-$$

$$\frac{Z_L - Z_0}{Z_L + Z_0} = \frac{V^-}{V^+} = \Gamma_L$$

Since  $Z_L$  and  $Z_0$  can be complex,  $\Gamma_L$  is in general complex

We can use  $\Gamma_L$  to re-write the expressions for the phasors on the line as

$$v(z) = V^+ \left( e^{-j\beta z} + \Gamma_L e^{+j\beta z} \right) = V^+ e^{-j\beta z} (1 + \Gamma_L e^{j2\beta z})$$

$$v(z) = V^+ e^{-j\beta z} (1 + \Gamma(z))$$

$$\text{where we define } \Gamma(z) = \frac{V^- e^{j\beta z}}{V^+ e^{-j\beta z}} = \Gamma_L e^{j2\beta z} = \rho e^{j(\psi + 2\beta z)}$$

The current can be written in the same way

$$I(z) = \frac{V^+}{Z_0} \left( e^{-j\beta z} - \Gamma_L e^{+j\beta z} \right) = \frac{V^+}{Z_0} e^{-j\beta z} (1 - \Gamma_L e^{j2\beta z})$$

$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} (1 - \Gamma(z))$$

$$\Gamma(z) = \Gamma_L e^{j2\beta z}$$

is a generalized reflection coefficient which is valid at every point  $z$  on a transmission line.

A very useful relationship exists between the line impedance and the reflection coefficient at any position

$$Z(z) = \frac{V(z)}{I(z)} = \frac{V^+ e^{-j\beta z} (1 + \Gamma(z))}{\frac{V^+ e^{-j\beta z} (1 - \Gamma(z))}{Z_0}} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

This will be useful for understanding Smith Charts.

### 3.3.1 Voltage and current standing wave patterns

$$V(z) = V^+ (e^{-j\beta z} + \Gamma_L e^{+j\beta z})$$

Now let the load be resistive so that  $\Gamma_L = \rho e^{j\phi} \rightarrow \rho$

$$V(z) = V^+ (e^{-j\beta z} \pm \rho e^{j\beta z})$$

↑  
can be positive or negative even with R loads

$$V(z) = V^+ \underbrace{(e^{-j\beta z} \pm \rho e^{-j\beta z} + \rho e^{-j\beta z} \mp \rho e^{j\beta z})}_{\text{add + and - quantities}}$$

Reorganize

$$V(z) = V^+ \left[ e^{-j\beta z} (1 \pm \rho) \pm \rho (-pe^{-j\beta z} + e^{j\beta z}) \right]$$

Multiply by  $e^{j\omega t}$  and convert to time domain

$$V(z,t) = \underbrace{|V^+|(1 \pm \rho) \cos(\omega t - \beta z + \phi^+)}_{\text{This is a traveling}} \pm \underbrace{|V^+|2\rho \sin \beta z \cos(\omega t + \phi^+ + \frac{\pi}{2})}_{\text{This is a standing wave. It is stationary in space.}}$$

(propagating) wave

It is stationary in space.


where we have assumed  $V^+ = |V^+|e^{j\phi^+}$

It is important to consider the maximum and minimum values of  $|V(z)|$   
we can write  $V(z) = V^+ e^{-j\beta z} (1 + \Gamma(z))$  where  $\Gamma(z) = \Gamma_L e^{j2\beta z} = \rho e^{j(\phi + 2\beta z)}$

$$V_{\max} = |V(z)|_{\max} = |V^+|(1 + |\Gamma_L|) = |V^+|(1 + \rho) \quad \left. \right\} \text{since } |\Gamma(z)| = |\Gamma_L| = \rho$$

$$V_{\min} = |V(z)|_{\min} = |V^+|(1 - |\Gamma_L|) = |V^+|(1 - \rho) \quad \left. \right\}$$

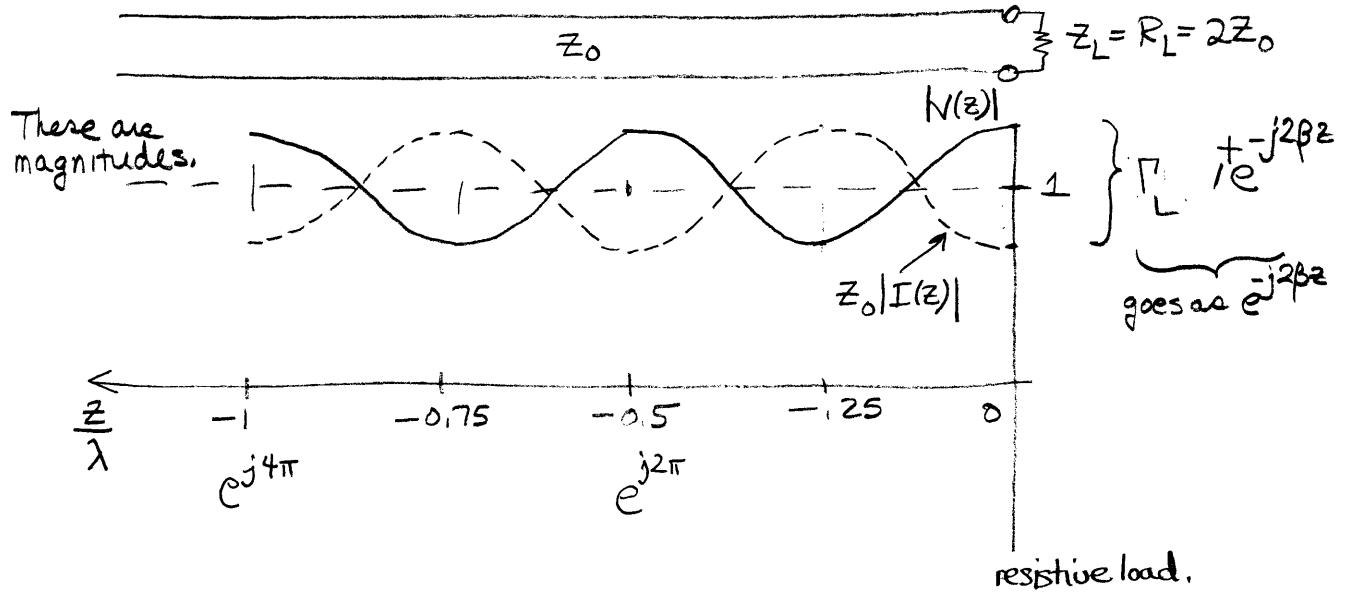The magnitude of  $V$  will vary sinusoidally from the load with a variation  $\pm \rho$



For  $Z_L = 2Z_0 = R_L$  we have

$$\Gamma_L = \frac{2Z_0 - Z_0}{2Z_0 + Z_0} = \frac{Z_0}{3Z_0} = \frac{1}{3} = \rho$$

$$V(z) = V^+ e^{-j\beta z} [1 + \Gamma(z)]$$

$$\Gamma(z) = \Gamma_L e^{j2\beta z} = \frac{1}{3} e^{j2\beta z} \quad \text{where } \psi = 0 \text{ since } Z_L = \text{real}$$

$$e^{j2\frac{2\pi}{\lambda} z} = e^{j\frac{4\pi}{\lambda} z}$$

You can also plot  $I$


$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} \underbrace{[1 - \Gamma(z)]}_{}$$

This has the same variation as  $V(z)$  but the sign of  $\Gamma$  is reversed

Plot  $I(z) Z_0$  since this is to the same scale as  $V(z)$
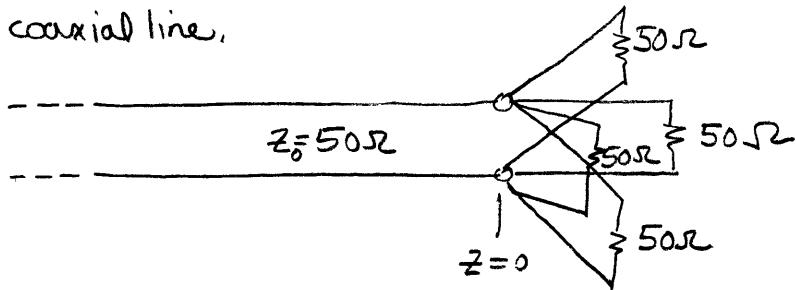
## Example 3-5

Four Yagi antennas with a feed point impedance of  $50\Omega$  are stacked in parallel on an antenna tower and connected to the transmitter by a  $50\Omega$  coaxial line.



(a) Calculate the load reflection coefficient  $\Gamma_L$  put sign in exponent

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{12.5 - 50}{12.5 + 50} = -\frac{37.5}{62.5} = -0.6 = 0.6 e^{j180^\circ}$$

(b) Calculate  $V_{max}$ ,  $V_{min}$ ,  $I_{max}$ ,  $I_{min}$  assuming  $V^+ = 1V$


$$V_{max} = V^+ (1 + \rho) = 1(1 + 0.6) = 1.6V$$

$$V_{min} = V^+ (1 - \rho) = 1(1 - 0.6) = 0.4V$$

$$I_{max} = \frac{V^+}{Z_0} (1 + \rho) = \frac{1(1 + 0.6)}{50} = 32mA$$

$$I_{min} = \frac{V^+}{Z_0} (1 - \rho) = \frac{1(1 - 0.6)}{50} = 8mA$$

(c) Sketch  $|V(z)|$  and  $|I(z)|$  as functions of  $\frac{z}{\lambda}$

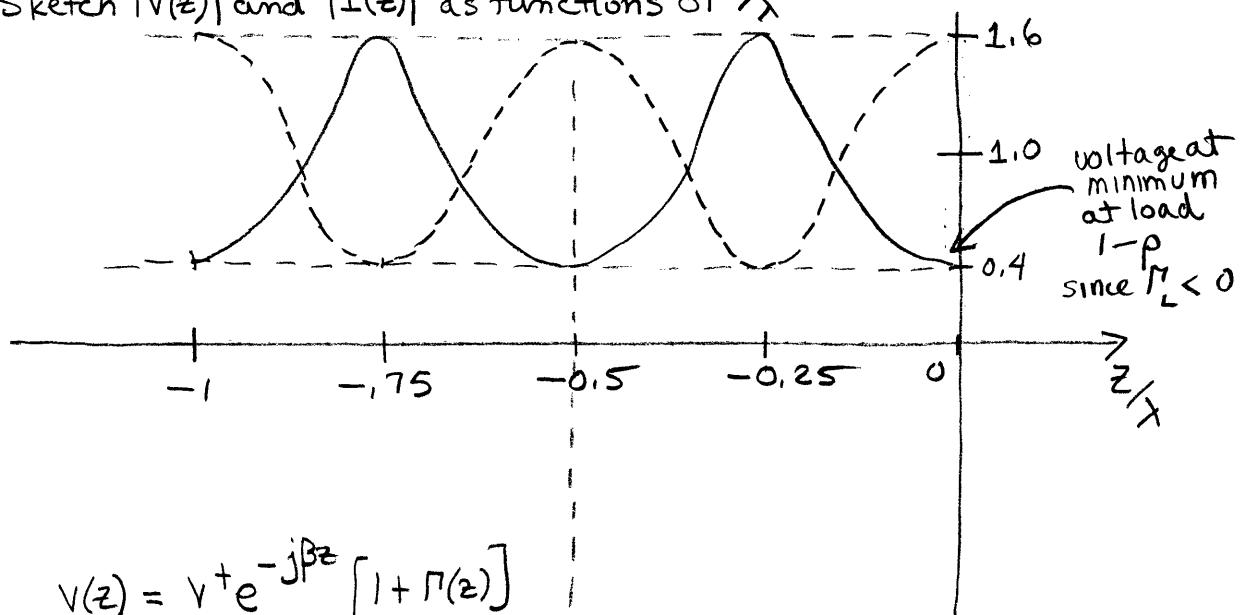

$$V(z) = V^+ e^{-j\beta z} [1 + \Gamma(z)]$$

$$V_L = V(z=0) = 1[1 - 0.6] = 0.4 \text{ Volts.}$$

Current is out of phase so it starts at

$$I_L = I(z=0) = \frac{1}{50} [1 + 0.6] = 32mA$$

$$Z_0 I_L = 1.6$$

### Example 3-6 UHF Blade Antenna

The measured values of the feed point impedance are

$Z_L$	$f$
$22.5 - j51$	225 MHz
$35 - j16$	300
$45 - j2.5$	400

The antenna is fed with a  $50\Omega$  coaxial line.

Calculate the load reflection coefficient and the standing wave ratio  $S$  on the line at

(a) 225 MHz

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{22.5 - j51 - 50}{22.5 - j51 + 50} = \frac{-27.5 - j51}{72.5 - j51} = +0.08 - j0.65$$

$$\Gamma_L = 0.65 e^{-j83.2^\circ}$$

The standing wave ratio is the ratio of  $V_{max}$  to  $V_{min}$  and is given by

$$S = \frac{1+\rho}{1-\rho} = \frac{1+0.65}{1-0.65} = 4.71$$

↑  
magnitude

(b) 300 MHz

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{35 - j16 - 50}{35 - j16 + 50} = \frac{-15 - j16}{85 - j16} = -0.14 - j0.21$$

$$\Gamma_L = 0.25 e^{-j122.5^\circ}$$

$$S = \frac{1+\rho}{1-\rho} = \frac{1+.25}{1-.25} = \frac{1.25}{.75} = 1.67$$

$$(c) \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{45 - j2.5 - 50}{45 - j2.5 + 50} = \frac{-5 - j2.5}{95 - j2.5} = -0.05 - j0.03$$

$$\Gamma_L = 0.06 e^{-j151.93}$$

$$S = \frac{1+\rho}{1-\rho} = \frac{1+.06}{1-.06} = 1.13$$

The standing wave ratio (SWR) or  $S$  is

$$\text{defined as } S = \frac{V_{\max}}{V_{\min}} = \frac{1+\rho}{1-\rho}$$

Inverting this

$$S(1-\rho) = 1+\rho$$

$$S - Sp = 1 + \rho$$

$$S - 1 = Sp + \rho = (S+1)\rho$$

$$\rho = \frac{S-1}{S+1}$$

The standing ratio  $\$$  can be measured. If we can also measure the location of the first minimum we can estimate  $z_L$ .

$$v(z) = V^+ (e^{-j\beta z} + R_L e^{+j\beta z}) = V^+ e^{-j\beta z} (1 + R_L e^{j2\beta z})$$

$$v(z) = V^+ e^{-j\beta z} (1 + \rho e^{j\Psi} e^{j2\beta z})$$

Now think about a minimum for  $v(z)$ . The minimum

$|v(z)| = V_{\min}$  will occur when

$$|v(z)| = |V^+| |1 - \rho|$$

$$\text{or } e^{j\Psi} e^{j2\beta z} = e^{j(\Psi+2\beta z)} = -1$$

This occurs when the exponent is an odd multiple of  $\pi$ , i.e.  $\cos \pi = -1$

$$\Psi + 2\beta z_{\min} = -(2m+1)\pi$$

The location of the first minimum is given by

$$\Psi + 2\beta z_{\min} = -\pi$$

We can write an expression for  $|V(z)|$  as a function of  $\rho$  and  $\psi$

$$V(z) = V^+ e^{-j\beta z} [1 + \Gamma(z)]$$

$$V(z) = V^+ e^{-j\beta z} [1 + \rho e^{j(\psi + 2\beta z)}]$$

$$= V^+ e^{-j\beta z} + \rho V^+ e^{j(\psi + \beta z)}$$

$$V(z) = V^+ \left[ \cos \beta z + j \sin \beta z + \rho \cos(\psi + \beta z) + j \rho \sin(\psi + \beta z) \right]$$

$$|V(z)| = |V^+| \sqrt{[\cos(\beta z) + \rho \cos(\psi + \beta z)]^2 + [\sin(\beta z) + \rho \sin(\psi + \beta z)]^2}$$

This is readily plotted as a function of  $\rho$  and  $\psi$


If  $\psi = 0$  or  $\pi$  (i.e. purely resistive)

$$|V(z)| = |V^+| \sqrt{(1 \pm \rho)^2 \cos^2(\beta z) + \sin^2(\beta z)(1 \mp \rho)^2}$$

lower sign is  $\psi = \pi$

From the plots the load is at a voltage minimum or maximum when  $Z_L = R_L + j0$

For the general case  $Z_L = R_L + jX_L$  the minimum is displaced from  $z=0$ .

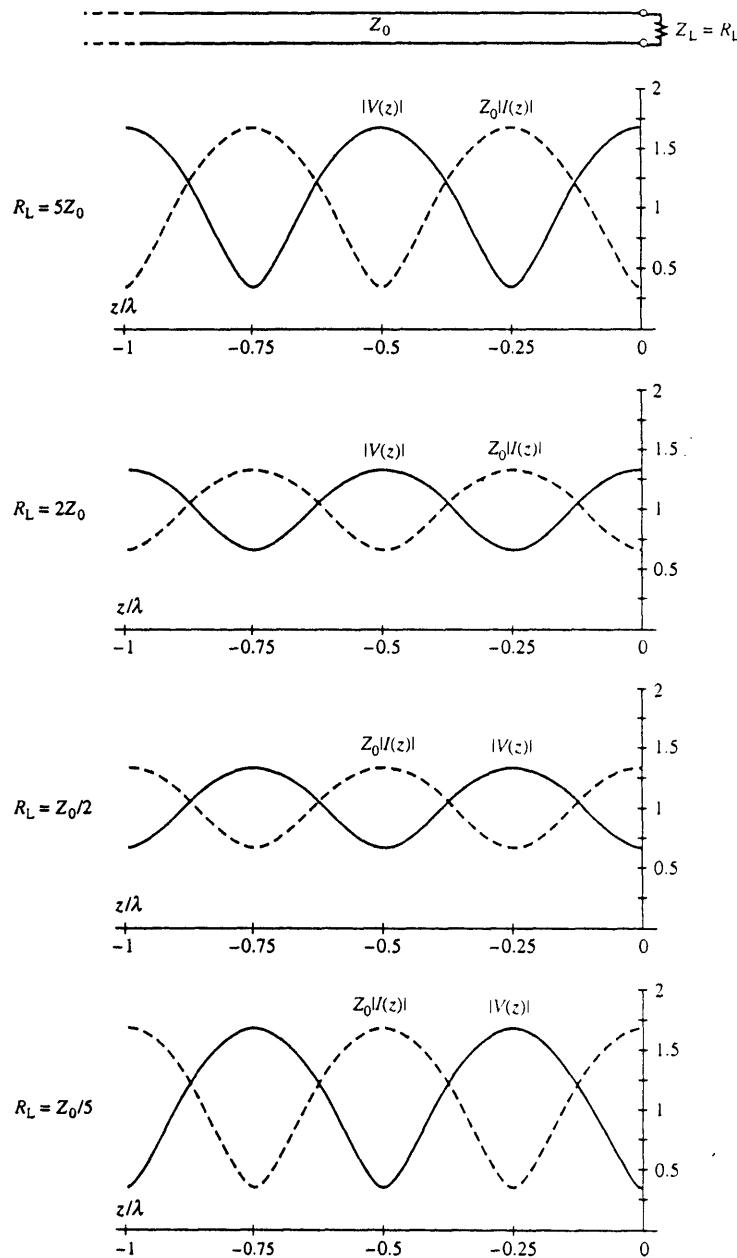

**FIGURE 3.15.** Voltage and current standing-wave patterns for different purely resistive loads. Magnitudes of the voltage and current phasors (i.e.,  $|V(z)|$  and  $Z_0|I(z)|$ ) are shown as functions of electrical distance from the load position  $z/\lambda$ , for  $V^+ = 1$  and for  $R_L = 5Z_0, 2Z_0, Z_0/2$ , and  $Z_0/5$ .

- The key things to observe from these plots are that
- a maxima or a minima occurs at the load for a resistive termination
  - that the S ratio decreases the closer you get to a matched load
  - $V$  has a maximum at the load if  $R_L > Z_0$   
a minimum at the load if  $R_L < Z_0$

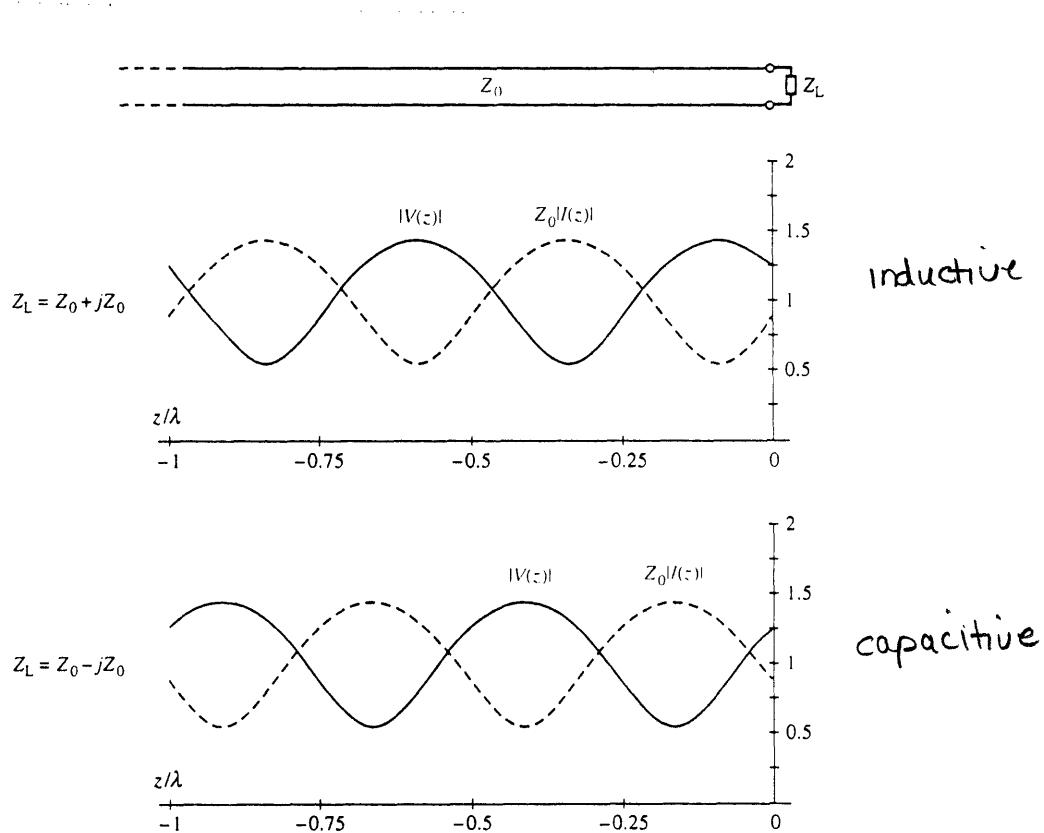


FIGURE 3.16. Voltage and current standing-wave patterns for complex loads. Magnitudes of the voltage and current phasors (i.e.,  $|V(z)|$  and  $Z_0|I(z)|$ ) are shown as functions of electrical distance from the load  $z/\lambda$  for  $V^+ = 1$  and for  $Z_L = Z_0 + jZ_0$  (inductive load) and  $Z_L = Z_0 - jZ_0$  (capacitive load).

Complex loads are harder to analyze. They also have standing wave patterns but you need to locate the first minimum to determine if the load is capacitive or inductive. If  $-z_{\min} < \frac{\lambda}{4}$  the load is capacitive. If  $-z_{\min} > \frac{\lambda}{4}$  then the load is inductive.

We can use  $|H^P|$  to understand the behavior of  $|V|$  near the load.

$$V(z) = V^+ e^{-j\beta z} [1 + \Gamma(z)]$$

$$|V(z)| = |V^+| \underbrace{|1 + \Gamma(z)|}_{\text{constant}} \quad \text{since } |e^{-j\beta z}| = 1$$



behavior of  $|V|$  comes from this vector sum

$$|1 + \Gamma(z)| = |1 + \Gamma_L e^{j2\beta z}| = |1 + pe^{j\psi} e^{j2\beta z}|$$


look at magnitude  
of vector sum

consists of "1" + vector of magnitude  $p$   
and angle  $\psi + 2\beta z$

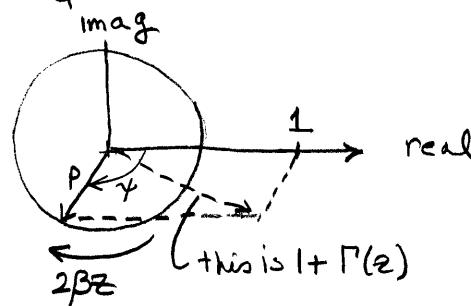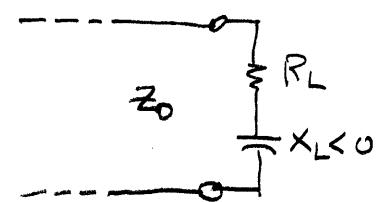We already know  $-\pi < \psi < 0$  for capacitive loads






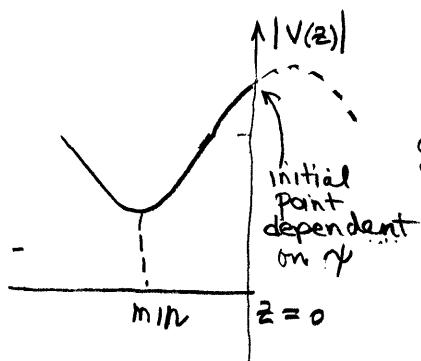Remember  
 $Z$  is negative  
so  $2\beta z$  goes  
clockwise



As  $z$  increases the angle  $\psi + 2\beta z$  increases  
going clockwise. This causes  $|1 + \Gamma(z)|$  to decrease  
to a minimum at  $\psi + 2\beta z = -\pi$

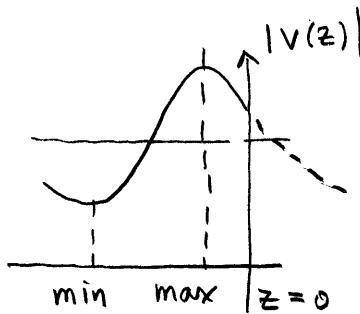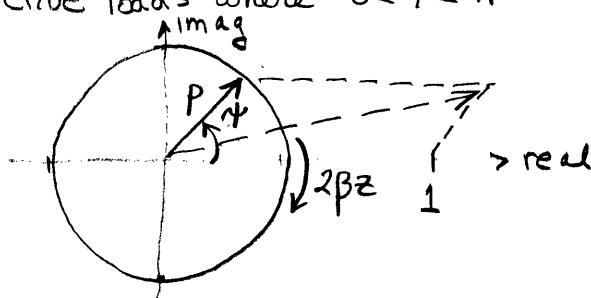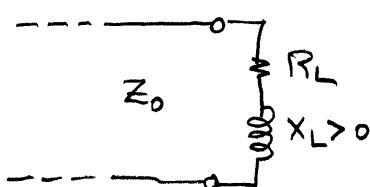We can repeat this for inductive loads where  $0 < \psi < \pi$



As  $z$  increases the angle actually decreases  
(going clockwise) until  $|H^P|$  reaches a maximum  
when  $\psi + 2\beta z = 0$

Note: inductive minima nearer load!

### 3.3.2. Transmission line impedance

$$z(z) = \frac{V(z)}{I(z)} = \frac{V^+ e^{-j\beta z} [1 + \Gamma(z)]}{V^+ e^{-j\beta z} [1 - \Gamma(z)]} = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$\text{but } \Gamma(z) = \frac{V^- e^{+j\beta z}}{V^+ e^{-j\beta z}} = \Gamma_L e^{j2\beta z}$$

$$\therefore z(z) = Z_0 \frac{1 + \Gamma_L e^{j2\beta z}}{1 - \Gamma_L e^{j2\beta z}} = Z_0 \frac{1 + \frac{Z_L - Z_0}{Z_L + Z_0} e^{j2\beta z}}{1 - \frac{Z_L - Z_0}{Z_L + Z_0} e^{j2\beta z}}$$

$$\text{but } \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

gives

$$\begin{aligned} z(z) &= Z_0 \frac{\frac{Z_L + Z_0 + Z_L e^{j2\beta z} - Z_0 e^{j2\beta z}}{Z_L + Z_0 - Z_L e^{j2\beta z} + Z_0 e^{j2\beta z}} \cdot \frac{e^{-j\beta z}}{e^{-j\beta z}}} \\ &= Z_0 \frac{\frac{Z_L e^{-j\beta z} + Z_0 e^{-j\beta z} + Z_L e^{j\beta z} - Z_0 e^{+j\beta z}}{Z_L e^{-j\beta z} + Z_0 e^{-j\beta z} - Z_L e^{+j\beta z} + Z_0 e^{j\beta z}}}{\frac{Z_L (e^{j\beta z} + e^{+j\beta z}) + Z_0 (e^{-j\beta z} e^{+j\beta z})}{Z_L (e^{-j\beta z} - e^{+j\beta z}) + Z_0 (e^{-j\beta z} + e^{j\beta z})}} \end{aligned}$$

$$\text{we know } e^{j\theta} = \cos \theta + j \sin \theta$$

$$\underline{e^{-j\theta} = \cos \theta - j \sin \theta}$$

$$e^{j\theta} + e^{-j\theta} = 2 \cos \theta$$

$$e^{j\theta} - e^{-j\theta} = 2j \sin \theta$$

Using these identities

$$z(z) = Z_0 \frac{Z_L 2 \cos \beta z + Z_0 (-2j \sin \beta z)}{Z_L (-2j \sin \beta z) + Z_0 2 \cos \beta z}$$

$$z(z) = Z_0 \frac{\frac{Z_L \cos \beta z - j Z_0 \sin \beta z}{Z_0 \cos \beta z - j Z_L \sin \beta z} \cdot \frac{1}{\cos \beta z}}{\frac{1}{\cos \beta z}} = Z_0 \frac{Z_L - j Z_0 \tan \beta z}{Z_0 - j Z_L \tan \beta z}$$

It is common to normalize this expression to  $Z_0$

$$\bar{Z}(z) = \frac{Z(z)}{Z_0}$$

$$\bar{Z}_L(z) = \frac{Z_L}{Z_0}$$

The normalized expression becomes

$$\bar{Z}(z) = \frac{\bar{Z}_L - j \tan \beta z}{1 - j \bar{Z}_L \tan \beta z} \quad \text{use with Smith Charts}$$

We would like to be able to determine  $\bar{Z}_L$  from measurements.

From previous page

$$Z(z) = Z_0 \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

$$@ z=0 \quad \bar{Z}_L = Z(z=z=0) = Z_0 \left. \frac{1 + \Gamma_L e^{j2\beta z}}{1 - \Gamma_L e^{j2\beta z}} \right|_{z=0} = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = Z_0 \frac{1 + pe^{j\psi}}{1 - pe^{j\psi}}$$

Normalizing

$$\bar{Z}_L = \frac{Z_L}{Z_0} = \frac{1 + \Gamma_L}{1 - \Gamma_L} = \frac{1 + pe^{j\psi}}{1 - pe^{j\psi}}$$

but  $p = \frac{s-1}{s+1}$  and  $\psi = -\pi - 2\beta z_{\min}$  are known and measurable

$$\bar{Z}_L = \frac{1 + \frac{s-1}{s+1} e^{j\psi}}{1 - \frac{s-1}{s+1} e^{j\psi}} = \frac{(s+1) + (s-1)e^{j\psi}}{(s+1) - (s-1)e^{j\psi}} = \frac{(s+1) + (s-1)e^{-j\pi} e^{-j2\beta z_{\min}}}{(s+1) - (s-1)e^{-j\pi} e^{-j2\beta z_{\min}}}$$

$$\bar{Z}_L = \frac{(s+1) + (s-1)e^{-j2\beta z_{\min}}}{(s+1) + (s-1)e^{-j2\beta z_{\min}}}$$

$$\bar{Z}_L = \frac{(s+1)e^{j\beta z_{\min}} - (s-1)e^{-j\beta z_{\min}}}{(s+1)e^{+j\beta z_{\min}} + (s-1)e^{-j\beta z_{\min}}}$$

$$= \frac{(e^{j\beta z_{\min}} + e^{-j\beta z_{\min}}) + s(e^{j\beta z_{\min}} - e^{-j\beta z_{\min}})}{(e^{j\beta z_{\min}} - e^{-j\beta z_{\min}}) + s(e^{j\beta z_{\min}} + e^{-j\beta z_{\min}})}$$

$$= \frac{2 \cos \beta z_{\min} + s 2 j \sin \beta z_{\min}}{2 j \sin \beta z_{\min} + s 2 \cos \beta z_{\min}} = \frac{1 + j s \tan \beta z_{\min}}{s + j \tan \beta z_{\min}}$$

With Smith charts it is useful to use admittances

$$Y(z) = \frac{1}{Z(z)} = Y_0 \frac{1 - \Gamma_L e^{j2\beta z}}{1 + \Gamma_L e^{j2\beta z}} = Y_0 \frac{Y_L - j Y_0 \tan \beta z}{Y_0 + j Y_L \tan \beta z}$$


These are just inverses of previous expressions.

Using normalized line admittances.

$$\bar{Y}(z) = \frac{\bar{Y}_L - j \tan \beta z}{1 - j \bar{Y}_L \tan \beta z}$$


$$\Gamma_L = \frac{Y_0 - Y_L}{Y_0 + Y_L}$$


Line impedance for resistive loads

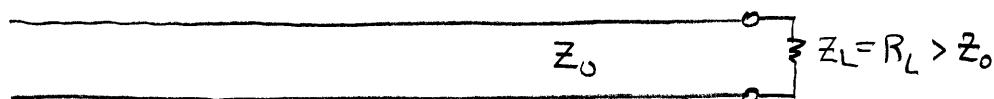


$$\text{Plot } \bar{Z}(z) = \frac{\bar{Z}_L - j \tan \beta z}{1 - j \bar{Z}_L \tan \beta z}$$

↑ normalized impedance.

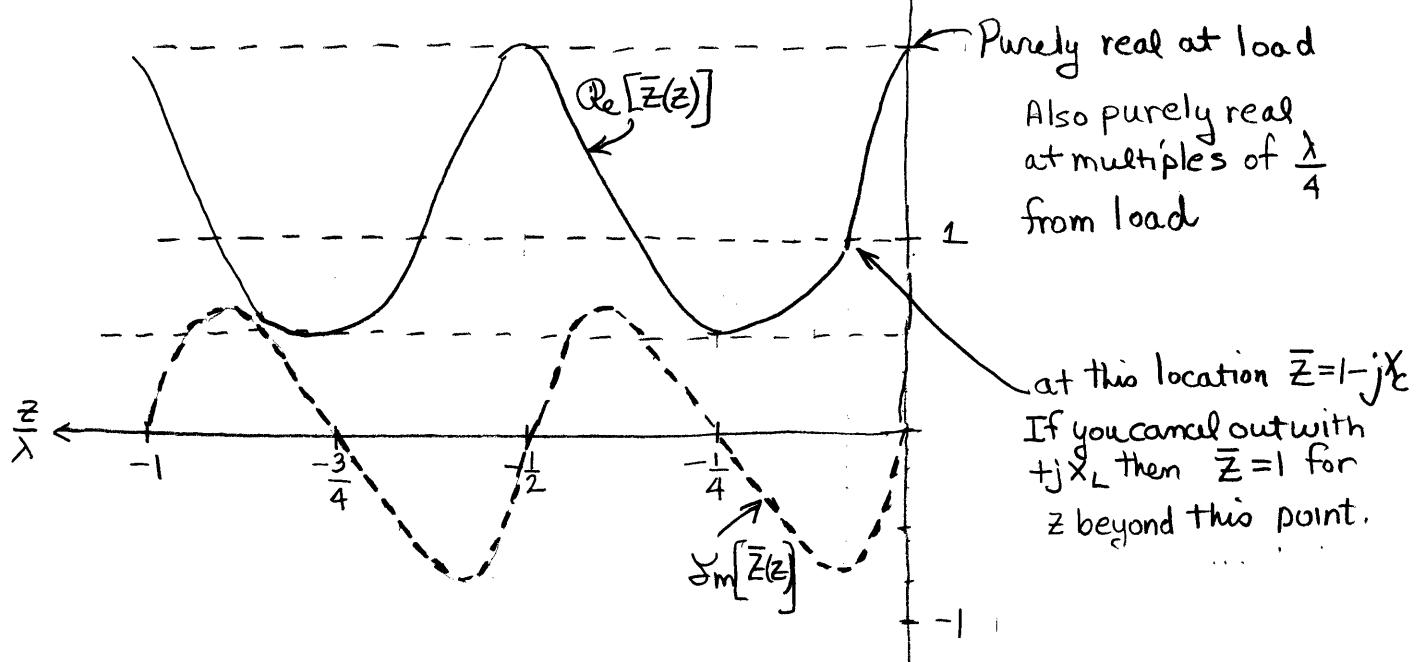

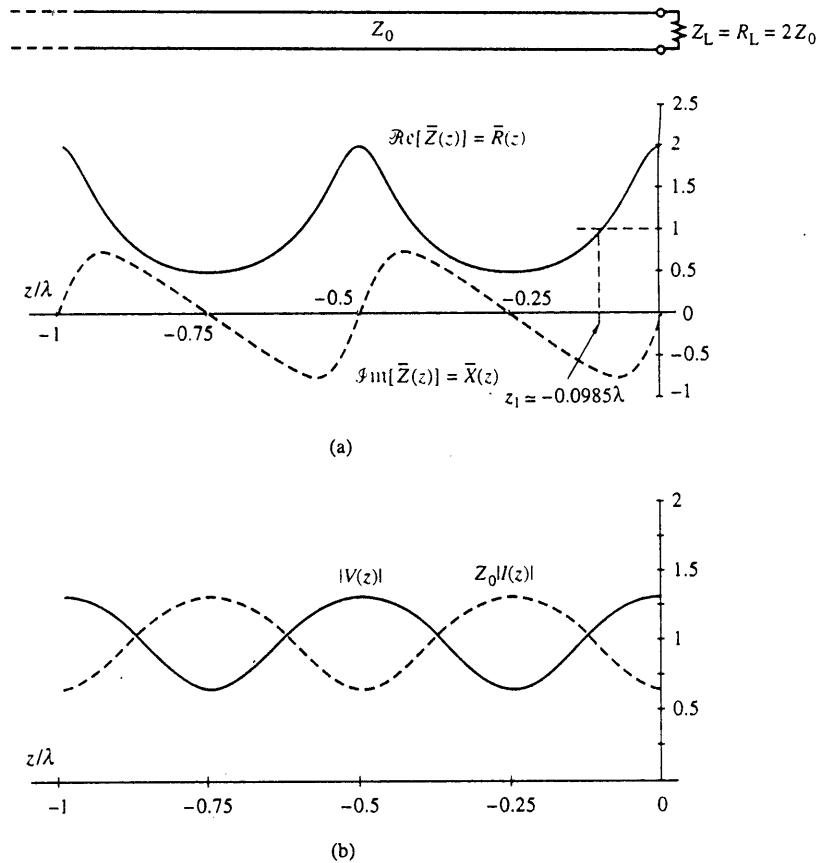

**FIGURE 3.19.** Impedance along a line terminated with  $Z_L = R_L = 2Z_0$ . (a) The real and imaginary parts of the normalized line impedance  $\bar{Z}(z)$  are shown as functions of  $z/\lambda$ . (b) Magnitudes of the voltage and current phasors (i.e.,  $|V(z)|$  and  $Z_0|I(z)|$ ) are shown as functions of electrical distance from the load  $z/\lambda$ , for  $V^+ = 1$ .

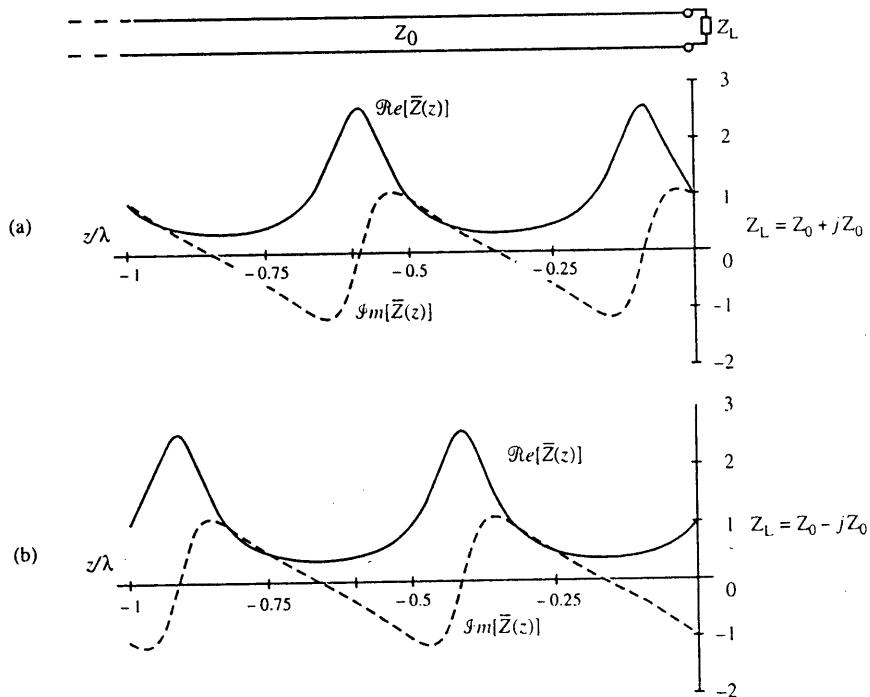

**FIGURE 3.22.** Line impedance for two different complex load impedances. The real and imaginary parts of the normalized line impedance  $\bar{Z}(z)$  are shown as functions of electrical distance  $z/\lambda$  along the line for (a)  $Z_L = Z_0 + jZ_0$  and (b)  $Z_L = Z_0 - jZ_0$ .

Some observations for a resistive load:

line impedance at a voltage maximum is real

$$v(z) = V^+ e^{-j\beta z} \underbrace{[1 + \rho e^{j(\phi + 2\beta z)}]}_{\text{this will be a maximum at}} \rightarrow |V^+|(1+\rho)$$

$$\phi + 2\beta z = -m 2\pi \quad m=0, 1, 2, 3$$

At the same position the current is

$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} \underbrace{[1 - \rho e^{j(\phi + 2\beta z)}]}_{\text{At this point the impedance is}} \rightarrow \frac{|V^+|}{Z_0} (1-\rho)$$

At this point the impedance is

$$|Z(z=voltage\ maximum)| = \frac{|V^+|(1+\rho)}{\frac{|V^+|}{Z_0}(1-\rho)} = Z_0 \frac{1+\rho}{1-\rho} = Z_0 S$$

For a complex load the maxima and minima of the voltage or the line impedance do NOT occur at the load.



Address: http://www.amanogawa.com/StandingWavePattern/StandingWavePattern.tmp.html



go

[IEEE Student Applicants](#) [Kowicki Thesis](#) [Frank Merat](#) [CwRU Bookstore](#) [EECS 311](#) [Carl Merat](#) [Class Schedules](#) [Google Map](#)

Favorites

History


Search

Scrapbook



Page Holder

## Standing Wave Patterns - 1


0.3333

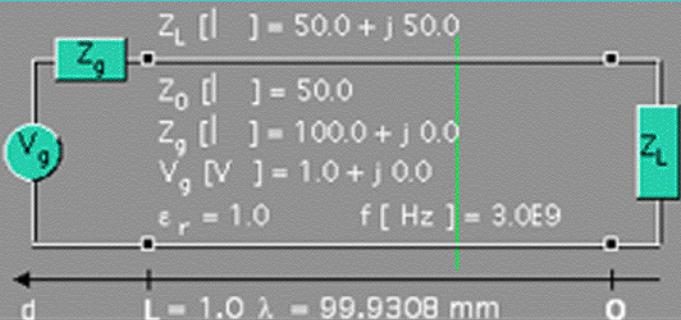

## Standing Wave Patterns

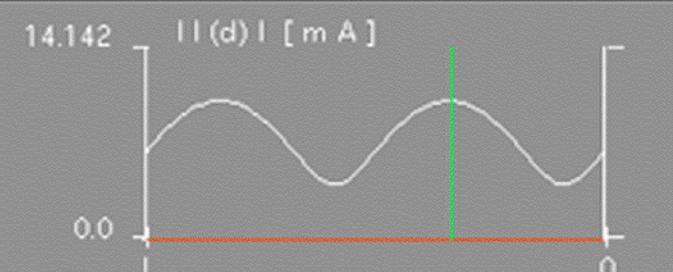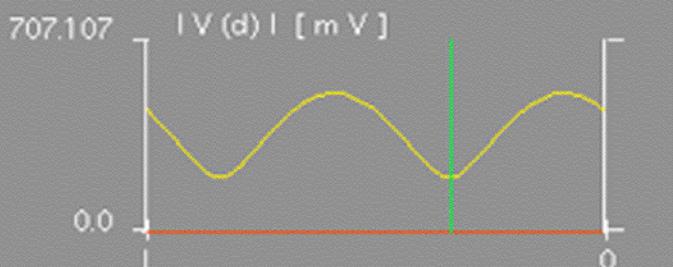

Set: Line Review: Plot

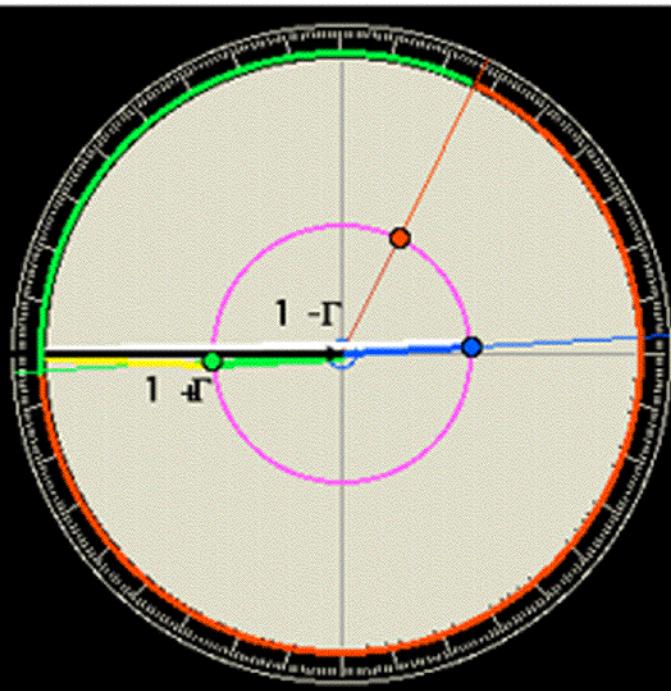

● Load Impedance =  $1.0 + j 1.0$   
● Load Refl. Coef. =  $0.44721 \angle 63.43495^\circ$   
● Cursor Impedance =  $0.38226 - j 0.02579$   
● Cursor Refl. Coef. =  $0.44721 \angle -176.54105^\circ$   
● Cursor Admittance =  $2.60415 + j 0.17566$

●  $d = 0.3333 \lambda \mid 2\beta d = 4.1884 \text{ rad} = 239.976^\circ$   
●  $0.5\lambda - d = 0.1667 \lambda \mid 2\beta(0.5\lambda - d) = 2.0948 \text{ rad} = 12^\circ$

Impedance Grid       Admittance Grid  
 Show Grid       SWR Circle       Cursor Line

Back to  
Index Page



Address: http://www.amanogawa.com/LineImpedance/LineImpedance.tmp.html

go

[IEEE Student Applicants](#) [Kowicki Thesis](#) [Frank Merat](#) [CwRU Bookstore](#) [EECS 311](#) [Carl Merat](#) [Class Schedules](#) [Google Mao](#)

## Line Impedance

0.0881



Set:

Load




Review:

Plot

 $Z_L [ \Omega ] = 50.0 + j 50.0$   
  $Z_0 [ \Omega ] = 50.0$   
 $Z(d) [ \Omega ] = 130.902 + j 0.0080$   
  $\epsilon_r = 1.0$   
  
 $d$     $L = 1.17081\lambda = 100.0 \text{ mm}$     $0$ 

3.51 GHz

## Impedance

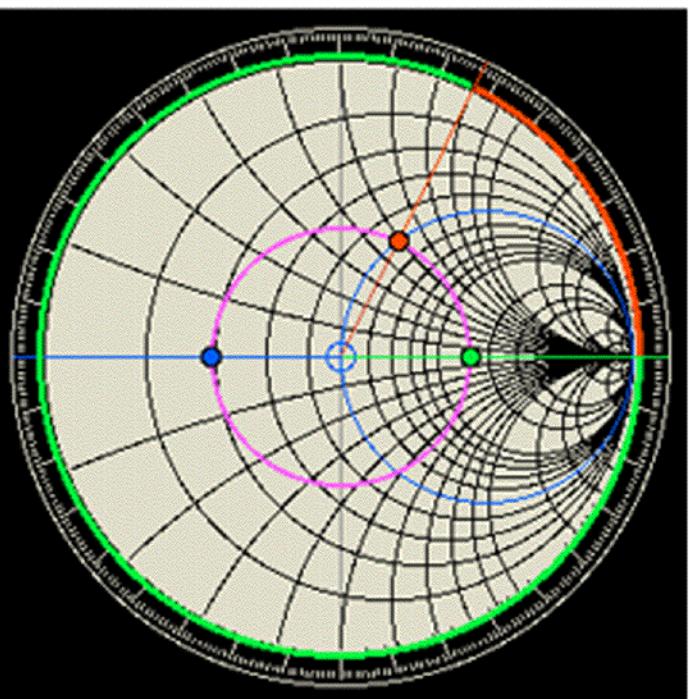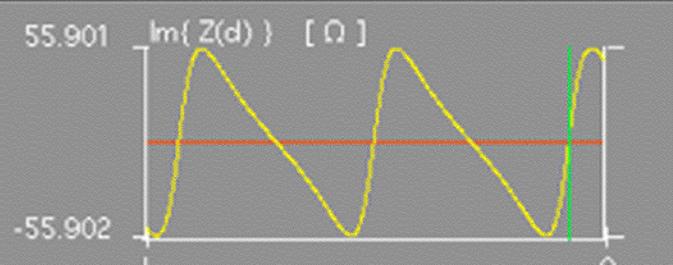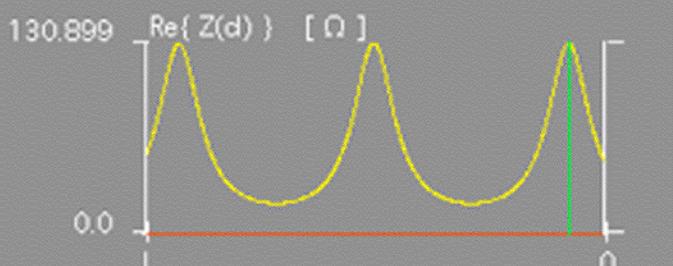

- Load Impedance =  $1.0 + j 1.0$
- Load Refl. Coef. =  $0.44721 \angle 63.43495^\circ$
- Cursor Impedance =  $2.61803 + j 1.5E-4$
- Cursor Refl. Coef. =  $0.44721 \angle 0.00295^\circ$
- Cursor Admittance =  $0.38197 - j 2.0E-5$

- $d = 0.0881 \lambda \mid 2\beta d = 1.1071 \text{ rad} = 63.432^\circ$
- $0.5\lambda-d = 0.4119 \lambda \mid 2\beta(0.5\lambda-d) = 5.1761 \text{ rad} = 29$

 Impedance Grid
 
 Admittance Grid
 
 SWR Circle
 
 Cursor Line
 
[Back to Index Page](#)

### Example 3-7 Input impedance of a line

Find the input impedance of a 75-cm long transmission line where  $Z_0 = 70\Omega$ , terminated with a  $Z_L = 140\Omega$  load at 50, 100, 150 and 200 MHz. Assume the phase velocity  $v_p$  to be equal to the speed of light in free space.

$$(a) f = 50 \text{ MHz} \quad \lambda = \frac{3 \times 10^8 \text{ m/sec}}{50 \times 10^6 / \text{sec}} = 6 \text{ m.}$$

$$\text{the electrical length of the line is } \frac{\lambda}{\lambda} = \frac{0.75 \text{ m}}{6 \text{ m}} = 0.125$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan(\beta l)}{Z_0 + j Z_L \tan(\beta l)}$$

$$\beta l = \frac{2\pi}{\lambda} l = 2\pi(0.125)$$

$$Z_{in} = 70 \frac{140 + j 70 \tan(2\pi \frac{1}{8})}{70 + j 140 \tan(2\pi \frac{1}{8})} = 70 \frac{140 + j 70}{70 + j 140} = 56 - j 42 \Omega$$

capacitive

$$(b) f = 100 \text{ MHz} \quad \lambda = \frac{3 \times 10^8 \text{ m/s}}{100 \times 10^6 / \text{s}} = 3 \text{ m}$$

$$\frac{\lambda}{\lambda} = \frac{0.75}{3} = \frac{1}{4} \quad \tan \beta l = \tan \left( \frac{2\pi}{\lambda} \cdot \frac{1}{4} \lambda \right) = \tan \left( \frac{\pi}{2} \right) = \infty$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \rightarrow Z_0 \frac{j Z_0}{j Z_L} = \frac{(Z_0)^2}{Z_L} = \frac{(70)^2}{140} = 35 \Omega$$

resistive

$$(c) f = 150 \text{ MHz} \quad \lambda = \frac{3 \times 10^8 \text{ m/s}}{150 \times 10^6 / \text{s}} = 2 \text{ m}$$

$$\frac{\lambda}{\lambda} = \frac{0.75}{2} = \frac{3}{8} \quad \tan \beta l = \tan \left( \frac{2\pi}{\lambda} \cdot \frac{3}{8} \lambda \right) = -1$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} = 70 \frac{140 - j 70}{70 - j 140} = 56 + j 42 \Omega$$

inductive

$$(d) f = 200 \text{ MHz} \quad \lambda = \frac{3 \times 10^8 \text{ m/s}}{200 \times 10^6 / \text{s}} = 1.5 \text{ m}$$

$$\frac{\lambda}{\lambda} = \frac{0.75 \text{ m}}{1.5 \text{ m}} = \frac{1}{2} \quad \tan \beta l = \tan \left( \frac{2\pi}{\lambda} \cdot \frac{1}{2} \lambda \right) = 0$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} = 70 \frac{140 + j 0}{70 + j 0} = 140 \Omega$$

resistive  
(equal to load impedance)

**Example 3-8** The following measurements were carried out on a  $100\Omega$  transmission line terminated with an unknown load  $Z_L$ . The voltage standing wave ratio  $S = 5$ , the distance between successive voltage minima is 25cm, and the distance from  $Z_L$  to the first voltage minimum is 8cm.

(a) Determine the load reflection coefficient  $\Gamma_L$ .

From S we can determine the magnitude p of  $\Gamma_L$

$$p = \frac{S-1}{S+1} = \frac{5-1}{5+1} = \frac{4}{6} = 0.667$$

Since the spacing between minima is  $\frac{\lambda}{2}$  we identify  $\frac{\lambda}{2} = 25\text{cm}$  or  $\lambda = 50\text{cm}$ .

Now, we can identify  $\Psi$ , the angle of the load coefficient

Since  $8\text{cm} < \frac{\lambda}{4} = 12.5\text{cm}$  this is a capacitive load

and  $\Psi = -\pi - 2\beta z$  (See pg. 21-22 of these notes).

$$\Psi = -\pi + 2 \frac{2\pi}{\lambda} \frac{8}{50} \lambda = -1.13 \text{ radians} = -64.8^\circ$$

↑  
don't forget z is negative

$$\therefore \Gamma_L = pe^{j\Psi} = 0.667 e^{-j64.8^\circ}$$

(b) Determine the unknown load impedance.

$$\beta z_{\min} = \frac{-2\pi}{\lambda} \frac{8}{50} \lambda = -1.0053 \text{ radians}$$

↑  
again note sign

$$\tan(\beta z_{\min}) = \tan(-1.0053) \cong -1.575$$

$$Z_L = Z_0 \frac{1 + j S \tan(\beta z_{\min})}{S + j \tan(\beta z_{\min})} = 100 \frac{1 + j 5(-1.575)}{5 + j(-1.575)}$$

$$= 100 \frac{1 - j 7.8787}{5 - j 1.575} = 63.35 - j 137.62 \Omega$$

(c) Determine the location of the first voltage maximum with respect to the load.

The first voltage maximum is always  $\frac{\lambda}{4}$  away from the voltage minimum.

$$z_{\max} = z_{\min} - \frac{\lambda}{4} = -8 - 12.5\text{cm} = -20.5\text{cm.}$$

↑ note sign

### Example 3-9 Inverted-V antenna

A  $50\Omega$  coaxial line filled with Teflon ( $v_p = 21 \text{ cm/nsec}$ ) is connected to an inverted-V antenna represented by  $Z_L$  as shown below. At  $f = 29.6 \text{ MHz}$  the feed-point impedance of the antenna is approximately measured to be  $Z_L \approx 75\Omega + j25\Omega$ . Find the two closest positions to the antenna along the line where the real part of the line impedance is equal to the characteristic impedance of the line (i.e.,  $Z_0$ ).

$$Z(z) = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

Define  $\gamma = -\tan \beta l$  and substitute values (We assume  $z = -l$ )

$$Z(z) = 50 \frac{(75+j25)-j50\gamma}{50-j(75+j25)\gamma} = 50 \frac{3+j(1-2\gamma)}{(2+\gamma)-j3\gamma}$$

We want the real part of this. Using old fashioned algebra

$$\begin{aligned} \operatorname{Re}\{Z(z)\} &= \operatorname{Re}\left\{50 \frac{3+j(1-2\gamma)}{(2+\gamma)-j3\gamma} \cdot \frac{(2+\gamma)+j3\gamma}{(2+\gamma)+j3\gamma}\right\} \\ &= \operatorname{Re}\left\{50 \frac{3(2+\gamma) - (1-2\gamma)(3\gamma) + j(1-2\gamma)(2+\gamma) + j9\gamma}{(2+\gamma)^2 + 9\gamma^2}\right\} \\ &= 50 \frac{3(2+\gamma) - 3\gamma(1-2\gamma)}{(2+\gamma)^2 + 9\gamma^2} = 50 \end{aligned}$$

$$3(2+\gamma) - 3\gamma(1-2\gamma) = (2+\gamma)^2 + 9\gamma^2$$

$$6 + 3\gamma - 3\gamma + 6\gamma^2 = 4 + 4\gamma + \gamma^2 + 9\gamma^2$$

$$4\gamma^2 + 4\gamma - 2 = 0$$

$$2\gamma^2 + 2\gamma - 1 = 0$$

$$\gamma = \frac{-2 \pm \sqrt{(2)^2 - 4(-1)(-2)}}{4} = \frac{-2 \pm \sqrt{4+8}}{4} = \frac{-1 \pm \sqrt{3}}{2} =$$

$$\gamma = -1.367, 0.366$$



$$\gamma = \tan(\beta z)$$

$$\lambda = \frac{v_p}{f} = \frac{2.1 \times 10^8 \text{ m/s}}{29.6 \times 10^6 \text{ Hz}} = 7.095 \text{ m}$$

$$\therefore \tan(\beta z) = \tan\left(\frac{2\pi}{\lambda} \cdot \frac{z}{7.095} \lambda\right) = \tan\left(\frac{2\pi z}{7.095}\right)$$

Solving for  $z_1$ ,

$$\tan\left(\frac{2\pi z_1}{\lambda}\right) = -1.367$$

$$\frac{2\pi z_1}{\lambda} = -0.9392$$

$$z_1 = -0.149\lambda = -1.06 \text{ meters}$$

Solving for  $z_2$

$$\tan\left(2\pi\left(\frac{z_2}{\lambda} + \frac{\frac{1}{2}}{\lambda}\right)\right) = .35086$$

↑  
the second real point  
must be  $\frac{\lambda}{2}$  away from the first real point

$$\tan\left(2\pi\left(\frac{z_2}{\lambda} + \frac{1}{2}\right)\right) = .35086$$

$$2\pi\left(\frac{z_2}{\lambda} + \frac{1}{2}\right) = 0.33744$$

$$\frac{z_2}{\lambda} + \frac{1}{2} = 0.05371$$

$$z_2 = -0.4463\lambda = -3.167 \text{ meters.}$$

At  $z = -1.06 \text{ m}$  and  $-3.167 \text{ m}$  the real part of  $z$   
is equal to  $z_0 = 50\sqrt{2}$

### Example 3-10

A radio transmitter is connected to an antenna having a feed-point impedance of  $Z_L = 70 + j100 \Omega$  with a  $50 \Omega$  coaxial line. Find

- (a) the load reflection coefficient

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{70 + j100 - 50}{70 + j100 + 50} = \frac{20 + j100}{120 + j100} = .508 + j0.410$$

$$\Gamma_L = 0.65 e^{j37.41^\circ}$$

- (b) the standing wave ratio

$$S = \frac{1 + \rho}{1 - \rho} = \frac{1 + .653}{1 - .653} = 4.76$$

- (c) the two positions closest to the load along the line where the line impedance is purely real, and their corresponding line impedance values.

This is an inductive load since  $X_L > 0$

The maximum voltage occurs when the line impedance is purely real (See Fig 3.19) At this point the magnitude of  $Z(z)$  is also a maximum.

This then reduces to finding the maximum voltage position

$$\text{i.e. } \Psi + 2\beta z_{\max} = 0$$

$$37.41^\circ = 0.6529 \text{ radians}$$

$$0.6529 + \frac{2\pi}{\lambda} z_{\max} = 0$$

$$z_{\max} = -\frac{0.652}{\frac{2\pi}{\lambda}} = -0.052\lambda$$

At this point  $R(z)$  is a maximum and the impedance is  $Z_0 S$

$$R_{\max} = Z_0 S = (50)(4.76) = 238 \Omega$$

The other point occurs at a voltage minimum.

$$\text{At a minimum } \Psi + 2\beta z_{\min} = -\pi$$

$$2\frac{\pi}{\lambda} z_{\min} = -\pi - 0.6529 = -3.795$$

$$z_{\min} = -0.302\lambda$$

$$\text{at this point } R_{\min} = \frac{Z_0}{S} = \frac{50}{4.76} = 10.5 \Omega$$

### 3.3.3 Calculation of $V^+$

We need to include the source to get actual values for  $V^+$ .

The voltage at the input end of the transmission line is given by

$$V_s = V(z=-l) = V^+ e^{j\beta l} (1 + R_L e^{-j2\beta l})$$

However this voltage can also be given by the input voltage divider.

$$V_s = \frac{Z_{in}}{Z_{in} + Z_s} V_0$$

Equate these two expressions for  $V_s$  and solve for  $V^+$


$$V^+ e^{j\beta l} (1 + R_L e^{-j2\beta l}) = \frac{Z_{in} V_0}{Z_{in} + Z_s}$$

$$V^+ = \frac{Z_{in} V_0}{(Z_{in} + Z_s) e^{j\beta l} (1 + R_L e^{-j2\beta l})}$$
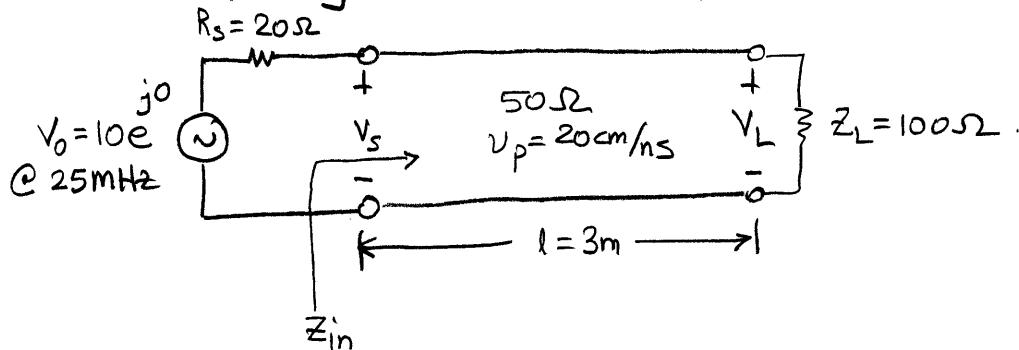
### Example 3-11

A sinusoidal voltage source  $V_0(t) = 10 \cos(5\pi \times 10^7 t)$  volts and  $R_s = 20\Omega$  is connected to an antenna with feed point impedance  $Z_L = 100\Omega$  through a 3-m long, lossless coaxial transmission line filled with polyethylene ( $v_p = 20 \text{ cm/ns}$ ) and with a characteristic impedance  $Z_0 = 50\Omega$  as shown below. Find

- the voltage and current phasors,  $V(z)$  and  $I(z)$ , at any location on the line, and
- the corresponding instantaneous expressions  $V(z,t)$  and  $I(z,t)$



Solution:

$$f = \frac{\omega}{2\pi} = \frac{5\pi \times 10^7}{2\pi} = 25 \times 10^6 \text{ Hz.}$$

$$\lambda = \frac{v_p}{f} = \frac{2 \times 10^8 \text{ m/s}}{25 \times 10^6} = 8 \text{ meters.}$$

The electrical length of the line is then  $\frac{l}{\lambda} = \frac{3 \text{ m}}{8 \text{ m}} = 0.375$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{3}{8}\lambda = \frac{3\pi}{4} \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{8} = \frac{\pi}{4}$$

$$\tan(\beta l) = -1$$

We then compute the input impedance.

$$Z_{in} = Z(z=l) = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} = 50 \frac{100 + j 50(-1)}{50 + j(100)(-1)}$$

$$Z_{in} = 40 + j 30 \Omega$$

We compute the input voltage  $V_s$  from the input voltage divider

$$V_s = \frac{Z_{in}}{R_s + Z_{in}} V_0 = \frac{40 + j 30}{60 + j 30} (10) = 7.45 e^{j 10.3^\circ} = 7.45 e^{j 0.180}$$

But  $V_s$  can also be written as

$$V_s = V(z = -3m) = V^+ e^{j\beta l} \left( 1 + \Gamma_L e^{-j2\beta l} \right)$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$$\text{so } V_s = V^+ e^{j\frac{3\pi}{4}} \left( 1 + \frac{1}{3} e^{-j\frac{3\pi}{2}} \right) = V^+ e^{j\frac{3\pi}{4}} \left( 1 + j\frac{1}{3} \right)$$

Equating the two expressions for  $V_s$  gives  $V^+$

$$V^+ e^{j\frac{3\pi}{4}} \left( 1 + j\frac{1}{3} \right) = 7.45 e^{j10.3^\circ} \cdot e^{-j0.32} \cdot e^{j0.18} \cdot e^{-j\frac{3\pi}{4}} = 7.07 e^{-j2.496}$$

$$V^+ = \frac{7.45}{1+j\frac{1}{3}} e^{j10.3^\circ} e^{-j\frac{3\pi}{4}} = 7.07 e^{-j0.32} e^{j0.18} e^{-j\frac{3\pi}{4}} = 7.07 e^{-j2.496}$$

$$\therefore V(z) = \underbrace{7.07 e^{-j143^\circ}}_{V^+} \underbrace{e^{j\frac{\pi z}{4}}}_{e^{j\beta z}} \underbrace{\left( 1 + \frac{1}{3} e^{j\frac{\pi z}{2}} \right)}_{1 + \Gamma(z)}$$

remember this  
is  $2\beta z$

$$I(z) = \frac{V(z)}{Z_0} = 0.141 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} \left( 1 - \frac{1}{3} e^{j\frac{\pi z}{2}} \right)$$

(b) The corresponding time expressions are

$$V(z,t) = \operatorname{Re} \left\{ V(z) e^{j\omega t} \right\} = \operatorname{Re} \left\{ (7.07 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} + 7.07 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} e^{\frac{j\pi z}{2}}) e^{j\omega t} \right\}$$

$$= \operatorname{Re} \left\{ (7.07 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} + 2.36 e^{-j143^\circ} e^{j\frac{\pi z}{4}}) e^{j\omega t} \right\}$$

$$= 7.07 \cos(5\pi \times 10^7 t - \frac{\pi z}{4} - 143^\circ) + 2.36 \cos(5\pi \times 10^7 t + \frac{\pi z}{4} - 143^\circ)$$

$$Y(z,t) = \operatorname{Re} \left\{ (0.141 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} - 0.141 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} e^{\frac{j\pi z}{2}}) e^{j\omega t} \right\}$$

$$= \operatorname{Re} \left\{ (0.141 e^{-j143^\circ} e^{-j\frac{\pi z}{4}} - 0.047 e^{-j143^\circ} e^{j\frac{\pi z}{4}}) e^{j\omega t} \right\}$$

$$= 0.141 \cos(5\pi \times 10^7 t - \frac{\pi z}{4} - 143^\circ) - 0.047 \cos(5\pi \times 10^7 t + \frac{\pi z}{4} - 143^\circ)$$