

Power Flow on a transmission line

You usually want to maximize the time-average power delivered to the load.

You can calculate time average power as

$$P_{av}(z) = \frac{1}{T_p} \int_0^{T_p} V(z,t) I(z,t) dt$$

where $T_p = \frac{2\pi}{\omega}$ is the period of the signal.

$$\text{In terms of phasors } P_{av}(z) = \frac{1}{2} \operatorname{Re} \{ V(z) I^*(z) \}$$

We can re-write this in terms of transmission line parameters as

$$V(z) = V^+ e^{-j\beta z} + \Gamma_L V^+ e^{+j\beta z}$$

$$I(z) = \frac{V^+}{Z_0} e^{-j\beta z} - \Gamma_L \frac{V^+}{Z_0} e^{+j\beta z}$$

$$\underbrace{+z \text{ traveling wave}}_{P^+} \quad \underbrace{-z \text{ traveling wave}}_{P^-}$$

$$P^+ = \frac{1}{2} \operatorname{Re} \left\{ V^+ e^{-j\beta z} \frac{(V^+ e^{-j\beta z})^*}{Z_0} \right\} = \frac{V^+ (V^+)^*}{2Z_0} = \frac{|V^+|^2}{2Z_0}$$

$$P^- = \frac{1}{2} \operatorname{Re} \left\{ \Gamma_L V^+ e^{+j\beta z} \frac{(-\Gamma_L V^+ e^{+j\beta z})^*}{Z_0} \right\} = -\frac{\Gamma_L \Gamma_L^* V^+ (V^+)^*}{2Z_0} = -\rho^2 \frac{|V^+|^2}{2Z_0}$$

$$\Gamma_L \Gamma_L^* = \rho^2$$

power is going
in opposite direction
to $V(z)$ and $I(z)$

Net power in forward direction

$$P_{av} = P^+ + P^- = \frac{|V^+|^2}{2Z_0} - \rho^2 \frac{|V^+|^2}{2Z_0} = (1-\rho^2) \frac{|V^+|^2}{2Z_0}$$

\Rightarrow you maximize power flow by minimizing ρ .

$$\text{i.e. } Z_L = Z_0$$

$$\Gamma_L = 0$$

$$S = 1$$

Consider what happens if the load is NOT matched to the load.

$$\frac{P_L}{P^+} = \frac{\text{power dissipated in load}}{\text{power delivered to matched load}}$$

$$\begin{aligned} P_L &= \frac{1}{2} \operatorname{Re} \left\{ V_L I_L^* \right\} = \frac{1}{2} \operatorname{Re} \left\{ V^+ (1 + R_L) \cdot \left[\frac{V^+ (1 - R_L^*)}{Z_0} \right]^* \right\} \\ &= \frac{1}{2} \operatorname{Re} \left\{ \frac{V^+ (V^+)^* (1 + R_L) (1 - R_L^*)}{Z_0} \right\} \quad \text{gives twice imaginary part} \\ &= \frac{1}{2} \operatorname{Re} \left\{ |V^+|^2 \frac{[1 + (R_L - R_L^*) - R_L R_L^*]}{Z_0} \right\} \\ &= \frac{1}{2} \frac{|V^+|^2}{Z_0} (1 - \rho^2) \end{aligned}$$

$$\therefore \frac{P_L}{P^+} = \frac{\frac{1}{2} \frac{|V^+|^2}{Z_0} (1 - \rho^2)}{\frac{1}{2} \frac{|V^+|^2}{Z_0}} = 1 - \rho^2$$

$$\frac{P_L}{P^+} = 1 - \rho^2 = 1 - \left(\frac{s-1}{s+1} \right)^2 = \frac{(s+1)^2 - (s-1)^2}{(s+1)^2} = \frac{(s^2 + 2s + 1) - (s^2 - 2s + 1)}{(s+1)^2}$$

$$\frac{P_L}{P^+} = \frac{4s}{(s+1)^2} \quad \text{this is a maximum when } s = 1, \text{i.e. matched.}$$

Example 3-12

A VHF transmitter operating at 125 MHz and developing $V_s = 100 e^{j0^\circ}$ volts with a source resistance of $R_s = 50 \Omega$ feeds an antenna with a feed-point impedance of $Z_L = 100 - j60$ through a 50Ω , polyethylene-filled coaxial line that is 17m long.

(a) Find the voltage $V(z)$ on the line.

$$\lambda = \frac{v_p}{f} = \frac{20 \text{ cm/ns}}{125 \times 10^6} = \frac{20 \times \frac{\text{m}}{100 \text{ cm}} \times \frac{\text{ns}}{10^9 \text{ s}}}{125 \times 10^6} = \frac{2 \times 10^8}{125 \times 10^6} = 1.6 \text{ m}$$


$$l = \frac{17 \text{ m}}{\lambda} = 10.625 \lambda \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{1.6} = \frac{5\pi}{4}$$

$$\tan \beta l = \tan \left(\frac{2\pi}{\lambda} \cdot 10.625 \lambda \right) = 1$$

$$Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} = 50 \frac{(100 - j60) + j50(1)}{50 + j(100 - j60)(1)}$$

$$Z_{in} = 50 \frac{100 - j10}{110 + j100} = 22.62 - j25.1 \Omega$$

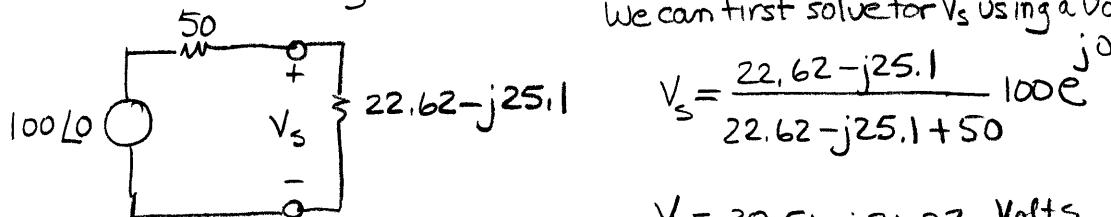We can first solve for V_s using a voltage divider



$$V_s = \frac{22.62 - j25.1}{22.62 - j25.1 + 50} 100 e^{j0^\circ}$$

$$V_s = 38.51 - j21.27 \text{ Volts}$$

$$V_s = 43.99 e^{-j0.504}$$

But V_s also can be written using the wave expressions for $V(z)$

$$V_s = V(z) = V^+ e^{-j\beta z} (1 + \Gamma_L e^{j2\beta z}) \quad \text{remember } z = -l \text{ so this becomes } V^+ e^{+j\beta l} (1 + \Gamma_L e^{-j2\beta l})$$

$$\beta l = \frac{2\pi}{\lambda} \cdot 10.625 \lambda = 21.25\pi = \frac{5}{4}\pi = -\frac{3}{4}\pi \leftarrow \text{note sign change}$$

$$2\beta l = 2 \cdot \frac{2\pi}{\lambda} \cdot 10.625 \lambda = 42.5\pi = \frac{5}{2}\pi = \frac{1}{2}\pi$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 - j60) - 50}{(100 - j60) + 50} = \frac{50 - j60}{150 - j60} = 0.42 - j0.23 = 0.483 e^{-j28.4^\circ}$$

$$V_s = V(z = -17 \text{ m}) = V^+ e^{-j\left(\frac{1}{2}\pi\right)} (1 + (0.42 - j0.23) e^{-j\frac{1}{2}\pi})$$

$$V_s = V^+ e^{-j\frac{3\pi}{4}} (1 + (-0.23 - j0.42)) = V^+ e^{-j\frac{3\pi}{4}} (0.77 - j0.42)$$

These expressions for V_s can be equated and solved for V^+

$$V^+ e^{-j\frac{3\pi}{4}} (0.77 - j0.42) = 43.99 e^{-j0.504}$$

$$V^+ = \frac{43.99 e^{-j0.504}}{(0.77 - j0.42)} e^{j\frac{3\pi}{4}} = (50.15 - j0.23) e^{j\frac{3\pi}{4}}$$

$$V^+ = 50.15 e^{-j0.004} e^{j\frac{3\pi}{4}} \approx 50.1 e^{j\frac{3\pi}{4}}$$

$$\Rightarrow V(z) = V^+ e^{-j\beta z} (1 + R(z))$$

$$V(z) = 50.1 e^{j\frac{3\pi}{4}} e^{-j\frac{5}{4}\pi z} (1 + .483 e^{-j28.4^\circ} e^{-j\frac{5}{2}\pi z})$$

(b) Find the load voltage V_L .

$$V_L = V(z=0) = 50.1 e^{j\frac{3\pi}{4}} (1 + .483 e^{-j28.4^\circ})$$

$$V_L = 50.1 e^{j\frac{3\pi}{4}} (1.426 - j0.23) = 50.1 e^{j\frac{3\pi}{4}} 1.444 e^{-j9.17^\circ} =$$

$$V_L = 72.3 e^{+j125.8} \text{ volts.}$$

(c) Find the time average power absorbed by the VHF antenna.

$$P_L = \frac{1}{2} |I_L|^2 R_L = \frac{1}{2} \left| \frac{V_L}{Z_L} \right|^2 R_L \leftarrow \begin{array}{l} \text{since it is absorbed} \\ -j31.0^\circ \quad \text{use only real part.} \end{array}$$

$$Z_L = 100 - j60 = 116.6 e^{-j31.0^\circ}$$

$$P_L = \frac{1}{2} \frac{(72.3)^2}{(116.6)^2} \cdot (100) = 19.2 \text{ watts.}$$

(d) Find the power absorbed by the source impedance R_s

To find this we need to know I_s

$$I_s = \frac{V_o}{R_s + Z_{in}} = \frac{100 e^{j0^\circ}}{50 + 22.62 - j25.1} = 1.301 e^{j19.1^\circ}$$


$$P_{RS} = \frac{1}{2} |I_s|^2 R_s = \frac{1}{2} (1.301)^2 (50) = 42.3 \text{ watts.}$$

3.5 Impedance matching

Why do impedance matching

- (1) reduce reflections & standing waves that jeopardize the power-handling capabilities of the line
- (b) maximize power delivered to the load
- (c) improve signal-to-noise ratio of system
- (d) reduce amplitude and phase errors of system.

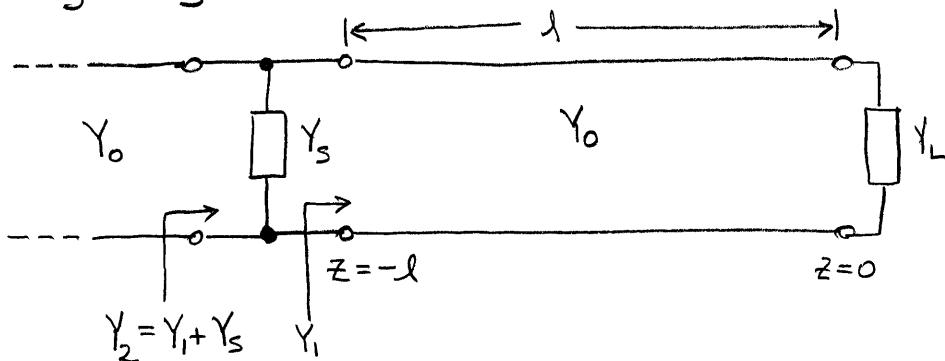3.5.1. Matching using Lumped Reactive Elements



To impedance match connect Y_s @ $z = -l$ such that

$$Y_2(z = -l) = Y_1(z = -l) + Y_s = Y_0$$

Do in terms of normalized admittance

$$\bar{Y}(z) = \frac{Y(z)}{Y_0} = \frac{1 - \bar{Y}_L e^{j2\beta z}}{1 + \bar{Y}_L e^{j2\beta z}}$$

\Rightarrow find $z = -l$ such that $\bar{Y}_1 = \bar{Y}(z = -l) = 1 - j\bar{B}$

\uparrow
want real part to be 1

\bar{B} is whatever Y_L and Y_0 and l cause it to be.

choose $\bar{Y}_s = +j\bar{B}$ so that $\bar{Y}_2 = \bar{Y}_1 + \bar{Y}_s = 1 - j\bar{B} + j\bar{B} = 1$

We can calculate the distance ℓ from the load we wish to place γ_s .

$$\bar{\gamma}_l = \bar{\gamma}(z=-\ell) = \frac{1 - \Gamma_L e^{-j2\beta\ell}}{1 + \Gamma_L e^{-j2\beta\ell}} = 1 - j\bar{B} \quad \text{from the problem}$$

Since $\Gamma_L = \frac{z_L - z_0}{z_L + z_0} = pe^{j\psi}$ we can substitute it into $\bar{\gamma}_l$

$$\bar{\gamma}_l = \frac{1 - pe^{j\psi} e^{-j2\beta\ell}}{1 + pe^{j\psi} e^{-j2\beta\ell}} = \frac{1 - pe^{j\theta}}{1 + pe^{j\theta}}$$

$$\text{where } \theta = \psi - 2\beta\ell$$

We can rationalize this and separate it into real and imaginary parts

$$\bar{\gamma}_l = \frac{1 - pe^{j\theta}}{1 + pe^{j\theta}} \frac{1 + pe^{-j\theta}}{1 + pe^{-j\theta}} = \frac{1 + pe^{-j\theta} - pe^{j\theta} - p^2}{1 + pe^{j\theta} + pe^{-j\theta} + p^2}$$

$$\bar{\gamma}_l = \frac{1 + p(-2j\sin\theta) - p^2}{1 + 2pcos\theta + p^2} = \frac{1 - p^2}{1 + 2pcos\theta + p^2} - j \frac{2psin\theta}{1 + 2pcos\theta + p^2}$$

For matching we want to pick ℓ such that the first term is 1.

$$\frac{1 - p^2}{1 + 2pcos\theta + p^2} = 1$$

$$1 - p^2 = 1 + 2pcos\theta + p^2$$

$$2pcos\theta + 2p^2 = 0$$

$$cos\theta + p = 0$$

$$cos\theta = -p$$

$$\theta = cos^{-1}(-p)$$

$$\theta = \psi - 2\beta\ell = cos^{-1}(-p)$$

Solving for ℓ gives

$$\ell = \frac{\psi - \theta}{2\beta} = \frac{\psi - cos^{-1}(-p)}{2\beta} = \frac{\lambda}{4\pi} [\psi - cos^{-1}(-p)]$$

this will actually have two solutions

This relationship has two solutions $\theta = \cos^{-1}(-\rho)$ since cos is an even function

$$\left. \begin{array}{l} \frac{\pi}{2} \leq \theta_1 \leq \pi \\ \text{and } -\pi \leq \theta_2 \leq -\frac{\pi}{2} \end{array} \right\} \begin{array}{l} \text{since } -\rho < 0 \text{ these solutions must} \\ \text{lie in the 2nd and 3rd quadrants} \\ \text{as shown} \end{array}$$

This specifies l by

$$l = \frac{\lambda}{4\pi} [\psi - \cos^{-1}(-\rho)]$$

Now we assumed that $z = -l$. If l comes out negative add $\frac{\lambda}{2}$ since this simply adds $2\beta(\frac{\lambda}{2}) = 2\left(\frac{2\pi}{\lambda}\right)\left(\frac{\lambda}{2}\right) = 2\pi$ to the argument.

Once the l at which $\Re\{\bar{Y}_2\} = 1$ is determined we can calculate the corresponding susceptance \bar{B}

$$\bar{B} = -\Im\{\bar{Y}_1\} \Big|_{\cos \theta = -\rho} = \frac{2\rho \sin \theta}{1 + 2\rho \cos \theta + \rho^2} \Big|_{\cos \theta = -\rho}$$

$$\cos \theta = -\rho$$

$$\sin \theta = \pm \sqrt{1 - \cos^2 \theta} = \pm \sqrt{1 - \rho^2}$$

$$\bar{B} = \frac{\pm 2\rho \sqrt{1 - \rho^2}}{1 - 2\rho^2 + \rho^2} = \frac{\pm 2\rho \sqrt{1 - \rho^2}}{1 - \rho^2} = \pm \frac{2\rho}{\sqrt{1 - \rho^2}}$$

The sign of \bar{B} comes from the angle θ

if θ in the 2nd quadrant $\sin \theta > 0$ and we use + (capacitor)

if θ in the 3rd quadrant $\sin \theta < 0$ and we use - (inductor)

We did this for parallel (shunt) matching.


You can also do this with series elements except you would calculate $\bar{Z}_1 = \bar{Z}(z = -l) = 1 - j\bar{X}$ and match with a series element.

$$l = \frac{\psi - \cos^{-1}(\rho)}{2\beta} = \frac{\lambda}{4\pi} [\psi - \cos^{-1}(\rho)]$$

$$\bar{X} = \pm \frac{2\rho}{\sqrt{1 - \rho^2}}$$

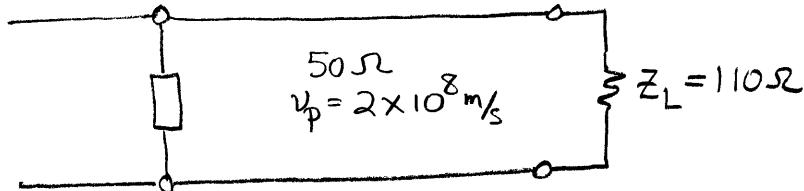Example 3-15

An antenna having a feed-point impedance of 110Ω is to be matched to a 50Ω coaxial line with $v_p = 2 \times 10^8 \text{ m/s}$ using a single shunt lumped reactive element as shown below. Find the position (nearest the load) and the appropriate value of the reactive element for operation at 30 MHz using (a) a capacitor, and (b) an inductor.



$$(a) \Gamma_L = P e^{j\psi} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{110 - 50}{110 + 50} = 0.375 \quad (\text{real})$$

The location of the capacitor will be

$$\lambda_1 = \frac{\psi - \theta}{2\beta} = \frac{\lambda}{4\pi} [\psi^0 - \cos^{-1}(-\rho)] = -\frac{\lambda}{4\pi} \cos^{-1}(0.375) = -\frac{\lambda(1.955)}{4\pi}$$

for a capacitor the sign of B is positive so this is a 2nd quadrant angle. $\frac{\pi}{2} < \theta < \pi$

$$(\text{since } B_c = j\omega C)$$

$$\text{since } \lambda = \frac{v_p}{f} = \frac{2 \times 10^8 \text{ m/s}}{30 \times 10^6 \text{ s}} = 6.67 \text{ m.}$$

Since λ_1 is negative add $+\frac{\lambda}{2}$

$$\lambda_1 = -0.156\lambda + 0.5\lambda = +0.344\lambda = 0.344(6.67 \text{ m}) = 2.29 \text{ m}$$

The capacitance is given by

$$(j\bar{B}_1) = j\omega C (Z_0)$$

$$\bar{B}_1 = +\frac{2\rho}{\sqrt{1-\rho^2}} = \frac{2(0.375)}{\sqrt{1-(0.375)^2}} = 0.809$$

where I chose the + sign to correspond to a shunt capacitance.

$$(0.809) = 2\pi(30 \times 10^6) C (50)$$

$$C = 85.8 \text{ pF.}$$

(b) For an inductor we must choose a 3rd quadrant angle.

$$\text{i.e. } \cos^{-1}(-.375) = -1.955$$

↑
different sign

The corresponding λ is given by

$$\lambda_2 = \frac{\lambda - \theta_2}{2B} = \frac{\lambda}{4\pi} \left[\psi - \cos^{-1}(-p) \right] = -\frac{\lambda}{4\pi} (-1.955) = +0.1555\lambda$$

$$\lambda_2 = +0.1555(6.67) = 1.04\text{m}$$

$$\text{The value of the susceptance is } \bar{B}_2 = -\frac{2p}{\sqrt{1-p^2}} = -0.809$$

The corresponding value is

$$-\frac{j}{\omega L_s} Z_0 = j\bar{B}_2 = -j0.809$$

$$L_s = \frac{-jZ_0}{\omega(-j0.809)} = \frac{50}{2\pi(30 \times 10^6)(0.809)} = 0.328 \mu\text{H}$$


3.5.2 Matching using Series or Shunt Stubs

At microwave frequencies we commonly use open- or short-circuited stubs (short lengths of transmission line) connected in series or parallel to match.


short-circuited stub - used for coax and waveguides
because a short is less sensitive to pick-up and radiates less than an open

open-circuit stub - used for micro strips and striplines because it is easier to fabricate

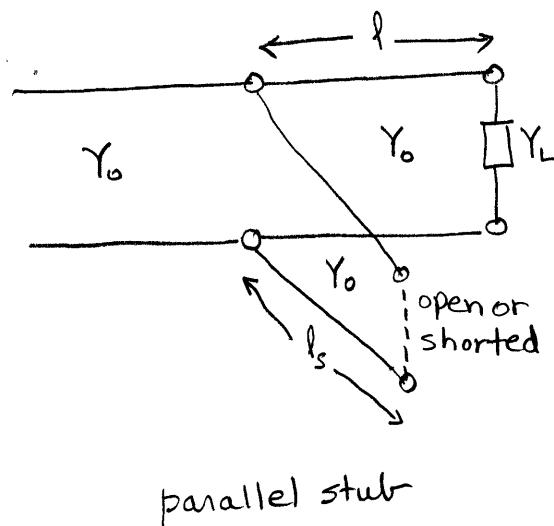A shunt (parallel) stub is usually better than a series stub since breaking the line to add the stub may create discontinuities and lead to reflections.



parallel stub

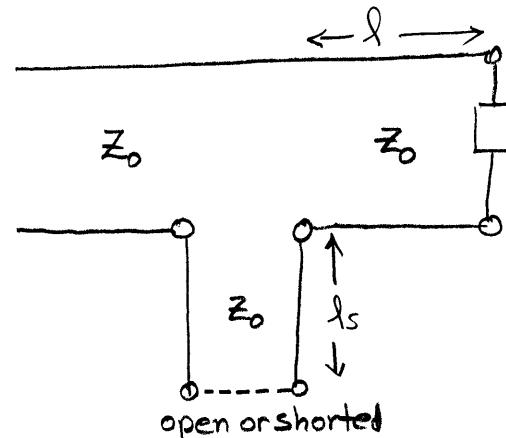

series stub

From the previous expressions for l and \bar{B} we only need to determine l_s of the stub to give $\bar{Y}_s = +j\bar{B}$ at the junction.


For a short circuited line we know

$$Z_m = j Z_0 \tan(\beta l)$$

Inverting

$$\bar{Y}_s = j \bar{B} = \frac{Z_0}{j Z_0 \tan(\beta l_s)} = \frac{1}{j \tan(\beta l_s)}$$

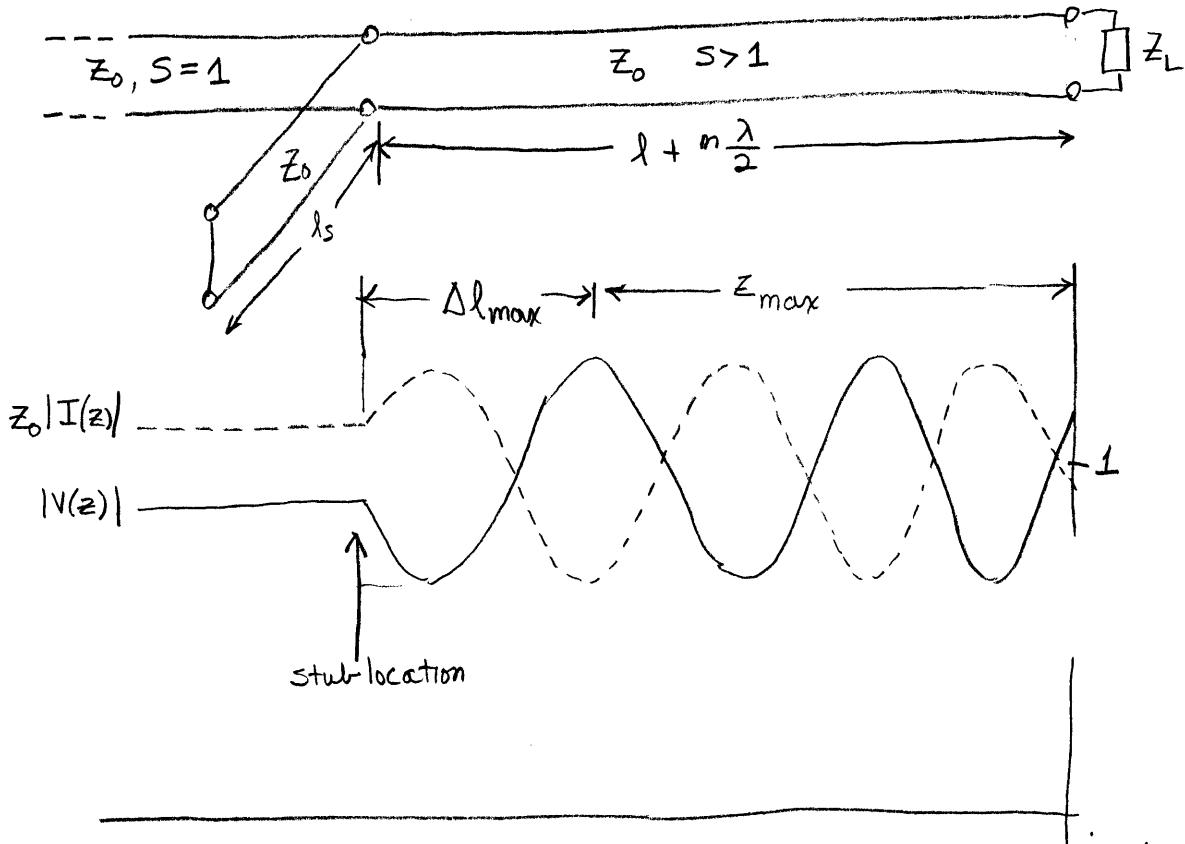so you can readily calculate $\tan(\beta l_s) = -\frac{1}{\bar{B}}$ for a short-circuited stub



You can measure the stub location l relative to the position z_{max} of the nearest voltage maximum toward the load since

$$l + m \frac{\lambda}{2}$$

You can specify

$$\theta = \psi - 2\beta l = \psi + 2\beta z_{max} - 2\beta \Delta l_{max}$$

$$\theta = -m 2\pi - 2\beta \Delta l_{max}$$

$$\Delta l_{max} = -\frac{\theta + m 2\pi}{2\beta} = -\frac{1}{2\beta} [\cos^{-1}(-p) + m 2\pi]$$

↑ can be measured.

Example 3-16

Design a single stub system to match a load consisting of a resistance $R_L = 200\Omega$ in parallel with an inductance $L_L = 200/\pi \text{ nH}$ to a transmission line with characteristic impedance $Z_0 = 100\Omega$ and operating at 500 MHz. Connect the stub in parallel with the line.

Express the load as an admittance

$$Y_L = \frac{1}{R_L} - j \frac{1}{\omega L_L} = \frac{1}{200} - j \frac{1}{2\pi(500 \times 10^6) \left(\frac{200}{\pi} \times 10^{-9}\right)} = .005 - j.005$$

The reflection coefficient at the load is

$$\Gamma_L = \frac{Y_0 - Y_L}{Y_0 + Y_L} = \frac{.01 - (.005 - j.005)}{.01 + (.005 - j.005)} = \frac{.005 + j.005}{.015 - j.005} = \frac{1+j}{3-j} = 0.2 + j0.4$$

$$\Gamma_L = 0.447 e^{j63.43^\circ} = 0.447 e^{j1.107}$$

The location of the stub is given as

$$l = \frac{\lambda}{4\pi} [\psi - \cos^{-1}(-\rho)] = \frac{\lambda}{4\pi} [1.107 \mp 2.034] = \begin{cases} -0.074\lambda + .5\lambda = .426\lambda \\ +0.250\lambda \end{cases}$$

↑
can be 2nd or 3rd
quadrant angle
i.e. C or L

$$\bar{B} = \pm \frac{2\rho}{\sqrt{1-\rho^2}} = \pm \frac{2(0.447)}{\sqrt{1-(0.447)^2}} \cong \pm 1$$

The length of the first stub is $\tan(\beta l_{s1}) = -\frac{1}{B} = -1$ for a short-circuited line

$$\beta l_{s1} = \frac{2\pi}{\lambda} l_{s1} = -0.7853$$



$$l_{s1} = -0.125\lambda + .5\lambda = .375\lambda$$

The length of the second stub is $\tan(\beta l_{s2}) = -\frac{1}{B} = -\frac{1}{1} = +1$

$$\beta l_{s2} = \frac{2\pi}{\lambda} l_{s2} = +0.7854$$

add $\frac{1}{2}\lambda$ since
 $l < 0$

$$l_{s2} = +0.125\lambda$$

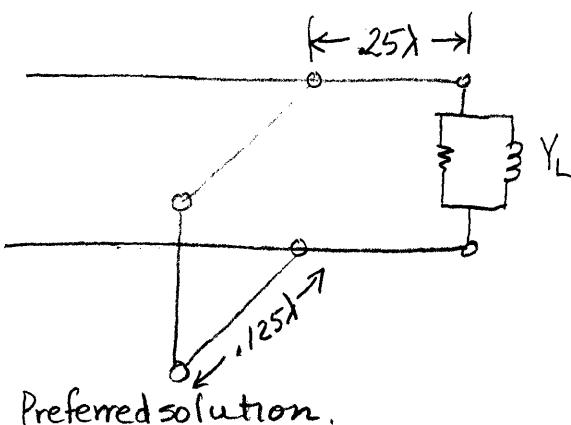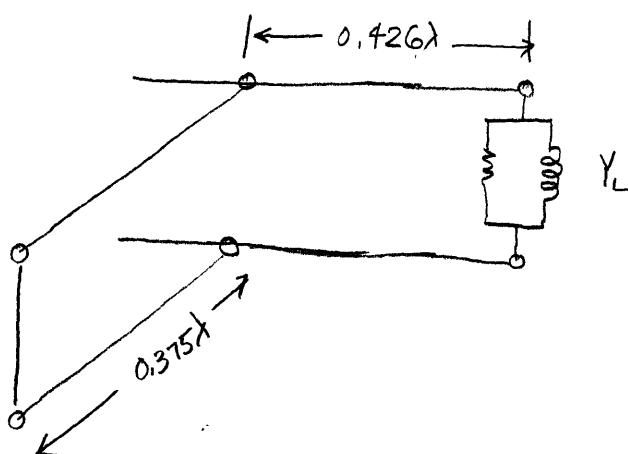

One thing we have NOT discussed is the frequency dependence of a solution.

Consider these two designs

$$Y_L(f) = \frac{1}{200} - j \frac{1}{2\pi f (\frac{200}{\pi} \times 10^{-9})} = \frac{1}{200} - j \frac{10^9}{400f}$$

on the line $\beta l = \frac{2\pi}{\lambda} \cdot l = 2\pi \frac{f}{c} l$

Then just to the right of the stub


$$Y_1(f) = Y_0 \frac{Y_L + j Y_0 \tan(2\pi f l / c)}{Y_0 + j Y_L \tan(2\pi f l / c)}$$

The total line admittance seen just to the left of the stub is then

$$Y_2(f) = Y_s + Y_1 = \frac{-j Y_0}{\tan(2\pi f l / c)} + Y_0 \frac{Y_L + j Y_0 \tan(2\pi f l / c)}{Y_0 + j Y_L \tan(2\pi f l / c)}$$

We can now compute

$$\Gamma_2(f) = \frac{Y_0 - Y_2(f)}{Y_0 + Y_2(f)} \quad \text{and} \quad S_2(f) = \frac{1 + |\Gamma_2(f)|}{1 - |\Gamma_2(f)|}$$

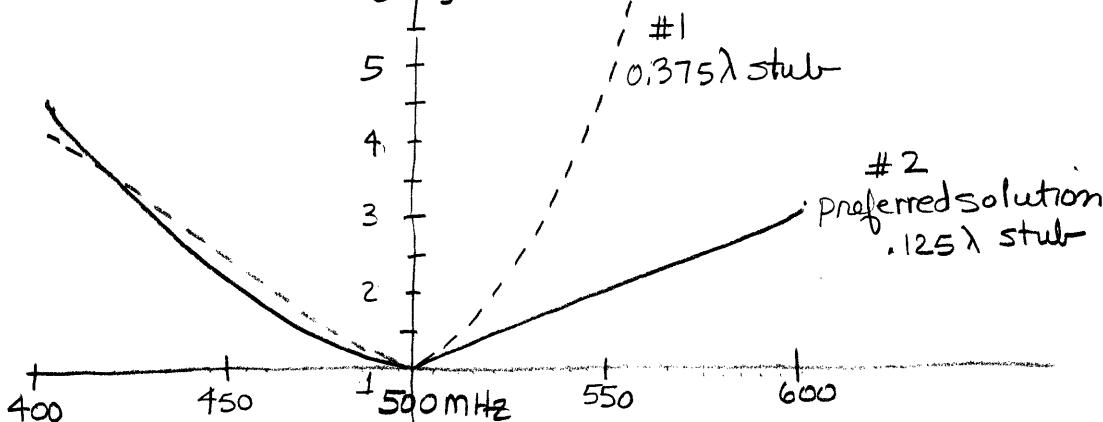

Most engineers would consider solution #2 to be better since it works over a broader range of frequencies.

3.5.3. Quarter Wave Transformer Matching

A common and powerful technique for matching a load to a transmission line is to use a quarter-wave length long transmission line.

For $\lambda = \frac{\lambda}{4}$ the input impedance is

$$Z_{in} \Big|_{\lambda=\frac{\lambda}{4}} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \Big|_{l=\frac{\lambda}{4}} \rightarrow Z_0 \frac{j Z_0 \tan \beta l}{j Z_L \tan \beta l} = \frac{Z_0^2}{Z_L}$$

$$\beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{4} = \frac{\pi}{2}$$

In terms of normalized impedances

$$Z_m = \frac{Z_0^2}{Z_L}$$

$$\text{or } \frac{Z_{in}}{Z_0} = \frac{Z_0}{Z_L}$$

$$\bar{Z}_{in} = \frac{1}{Z_L}$$

we have two cases, $Z_L = R_L$ and $Z_L = R_L + jX_L$

Assume that the impedance of the matching section is Z_Q

$$(a) \text{ For } Z_L = R_L \quad Z_{in} = \frac{Z_Q^2}{R_L}$$

If we want Z_{in} to match R_i (a cable impedance)

$$Z_Q = \sqrt{R_i R_L}$$


$$(b) \text{ for } Z_L = R_L + jX_L$$

$$\text{in this case } Z_{in} = \frac{Z_Q^2}{R_L + jX_L}$$

This is better written in terms of admittances:

$$Y_{in} = \frac{R_L + jX_L}{Z_Q^2} = \frac{R_L}{Z_Q^2} + j \frac{X_L}{Z_Q^2}$$

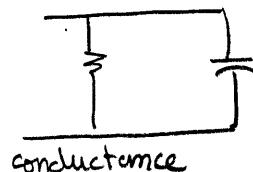
If Z_L is $\begin{cases} \parallel R_L \\ \parallel X_L > 0 \end{cases}$ then Y_{in} is



positive susceptance
which is a capacitance

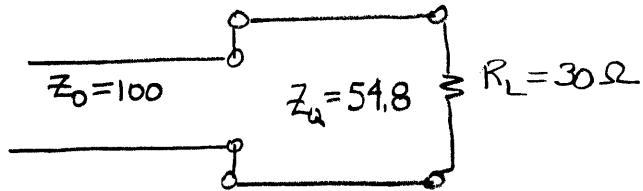Example 3-17

Design a quarter-wavelength section to match a thin monopole antenna of length 0.24λ having a purely resistive feed-point impedance of $R_L = 30\Omega$ to a transmission line having a characteristic impedance of $Z_0 = 100\Omega$.



$$S=1 \quad S=1.82$$

The matching section is $\frac{\lambda}{4}$ so $Z_{in} = \frac{Z_Q^2}{R_L} = 100$
for matching

$$Z_Q = \sqrt{(100)(R_L)} = \sqrt{(100)(30)} = 54.77\Omega$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 - 54.77}{30 + 54.77} = \frac{-24.77}{84.77} = -0.292 = 0.29 e^{j\pi}$$

$$S = \frac{1+\rho}{1-\rho} = \frac{1+0.29}{1-0.29} = \frac{1.29}{0.71} = 1.82$$

Example 3-18


A thin wire half wave dipole antenna has an input impedance of $Z_L = 73 + j42.5 \Omega$. Design a quarter-wave transformer to match this antenna to a transmission line with characteristic impedance $Z_0 = 100 \Omega$.

$$\text{At } z=0 \quad \Gamma_L = pe^{j\psi} = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{73 + j42.5 - 100}{73 + j42.5 + 100} = -0.9 + j.26 = .283 e^{j108.6^\circ}$$

$$\psi = 108.6^\circ = 1.896 \text{ radians}$$

The load is inductive since $j42.5 > 0$

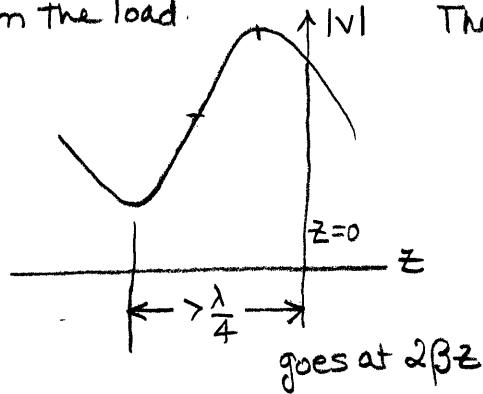For an inductive load the voltage minimum is more than $\frac{\lambda}{4}$ away from the load.



The maximum occurs when

$$\psi + 2\beta z_{\max} = 0 \quad (1+\Gamma \text{ aligns})$$

$$z_{\max} = -\frac{\psi}{2\beta} = -\frac{1.896}{2(2\pi/\lambda)} = -0.151\lambda$$

goes at $2\beta z$

We picked a maximum since $f_m(Z_{in}) = 0$ at a voltage maximum.

We need to calculate $Z(z = -0.151\lambda)$ and switch to normalized impedances


$$\bar{Z}(z = -0.151\lambda) = \frac{\bar{Z}_L - j \tan \beta z}{1 - j \bar{Z}_L \tan \beta z} \Big|_{z = -0.151\lambda} = \frac{(73 + j42.5) + j1.395}{1 - j(73 + j42.5)(-1.395)}$$

$$\tan(\beta z) = \tan\left[\frac{2\pi(-0.151\lambda)}{\lambda}\right] = -\tan(302\pi) = -1.395$$

$$\bar{Z}(z = -0.151\lambda) = \frac{73 + j1.82}{407 + j1.018} = 1.7936$$

We insert a $\frac{1}{4}$ section at $z = -0.151\lambda$. The impedance of this section will be
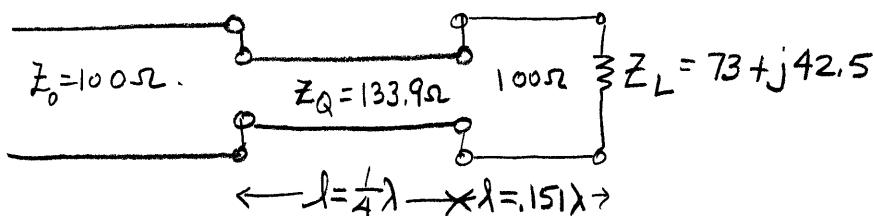
$$\bar{Z}_Q = \sqrt{(1.7936)(1)} = 1.339 \quad Z_Q = 133.9 \Omega$$



3.6 The Smith Chart

$$\bar{Z}(z) = \frac{1 + \Gamma(z)}{1 - \Gamma(z)} \quad \text{where} \quad \Gamma(z) = pe^{j(\psi + 2\beta z)}$$

$$\text{Let } \bar{Z} = \bar{R} + j\bar{X} \text{ and } \Gamma = u + jv$$

The relationship between these variables can be calculated by equating these expressions

$$\bar{Z} = \bar{R} + j\bar{X} = \frac{1 + (u + jv)}{1 - (u + jv)} = \frac{(1+u) + jv}{(1-u) - jv} = \frac{(1-u) + jv}{(1-u) + jv} = \frac{(1-u^2) + jv^2 - v^2}{(1-u)^2 + v^2}$$

$$\bar{R} = \frac{1 - u^2 - v^2}{(1-u)^2 + v^2}$$

$$\bar{X} = \frac{2v}{(1-u)^2 + v^2}$$

$$\bar{R}(1-u^2) + \bar{R}v^2 = 1 - u^2 - v^2$$

$$(1-u)^2 + v^2 = \frac{2v}{\bar{X}}$$

$$-1 + \bar{R}(1-u^2) + u^2 + \bar{R}v^2 + v^2 = 0$$

$$(1-u)^2 + v^2 - 2\frac{v}{\bar{X}} + \frac{1}{\bar{X}^2} = \frac{1}{\bar{X}^2}$$

$$(1-u^2)(\bar{R}-1) + (\bar{R}+1)v^2 = 0$$

$$(u-1)^2 + \left(v - \frac{1}{\bar{X}}\right)^2 = \frac{1}{\bar{X}^2}$$

$$(1-u^2)(\bar{R}-1)(\bar{R}+1) + (\bar{R}+1)^2v^2 = 0$$

$$1 + (1-u^2)(\bar{R}-1)(\bar{R}+1) + (\bar{R}+1)^2v^2 = 1$$

$$\frac{1 + (1-u^2)(\bar{R}^2-1) + v^2}{(\bar{R}+1)^2} = \frac{1}{(\bar{R}+1)^2}$$

$$\frac{1 + (\bar{R}^2 - u^2\bar{R}^2 - 1 + u^2) + v^2}{(\bar{R}+1)^2} = \frac{1}{(\bar{R}+1)^2}$$

$$\frac{-u^2\bar{R}^2 + u^2 + \bar{R}^2}{(\bar{R}+1)^2} + v^2 = \frac{1}{(\bar{R}+1)^2}$$


$$\left(u - \frac{\bar{R}}{\bar{R}+1}\right)^2 + v^2 = \frac{1}{(1+\bar{R})^2}$$

These are equations of circles in uv plane

centered at $u = \frac{\bar{R}}{\bar{R}+1}$, $v = 0$

radius $\frac{1}{1+\bar{R}}$

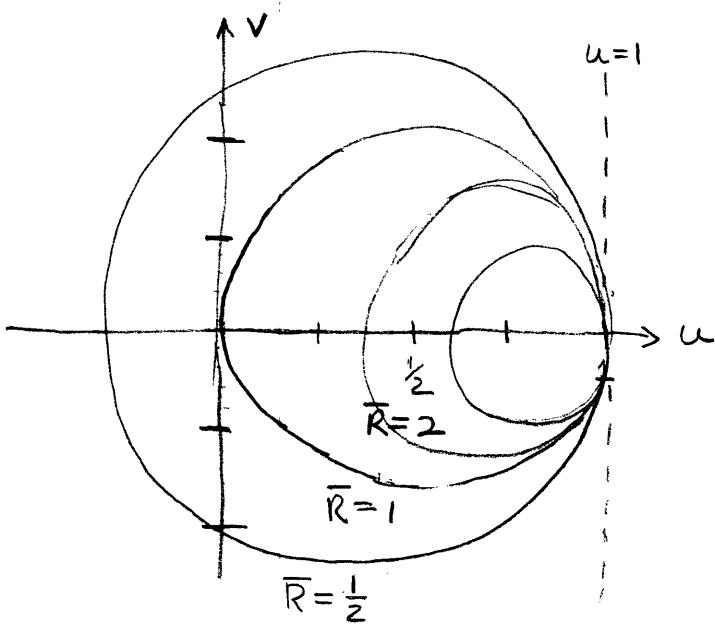
centered at $u = 1$, $v = \frac{1}{\bar{X}}$
radius $\frac{1}{\bar{X}}$



These are the circles of \bar{u} ,
the real part of $\bar{\Gamma}$

$$\left(u - \frac{\bar{R}}{1 + \bar{R}}\right)^2 + v^2 = \left(\frac{1}{1 + \bar{R}}\right)^2$$


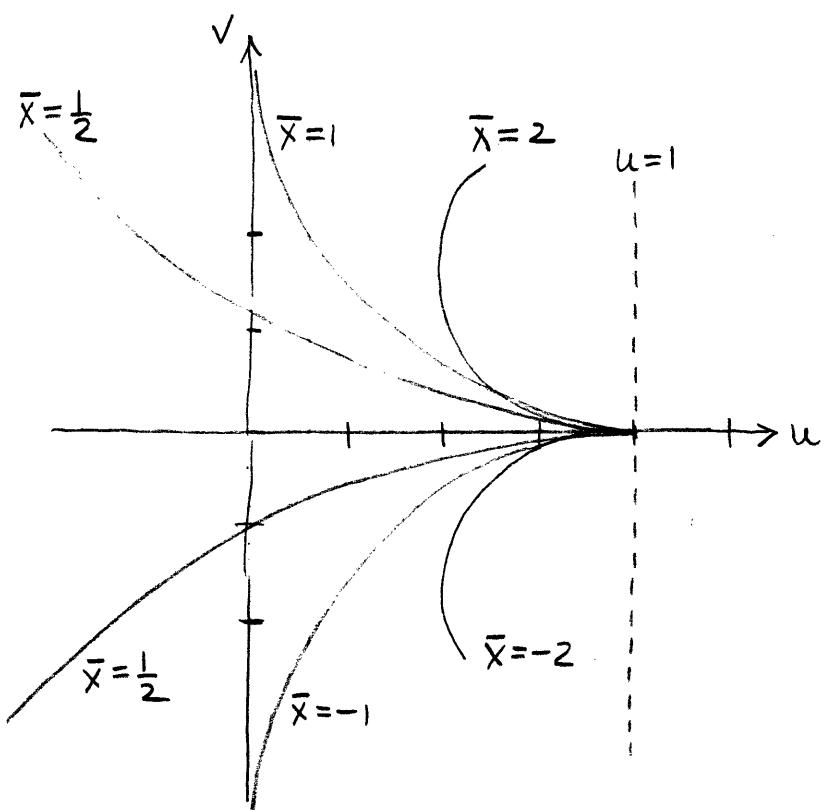
The circles of $\bar{\Gamma}$ given \bar{R} , (constant \bar{R} circles)
The circles are tangent to the $u = 1$ line




$$(u-1)^2 + \left(v - \frac{1}{x}\right)^2 = \frac{1}{x^2}$$

\curvearrowleft
this allows
 $\pm v$ symmetry

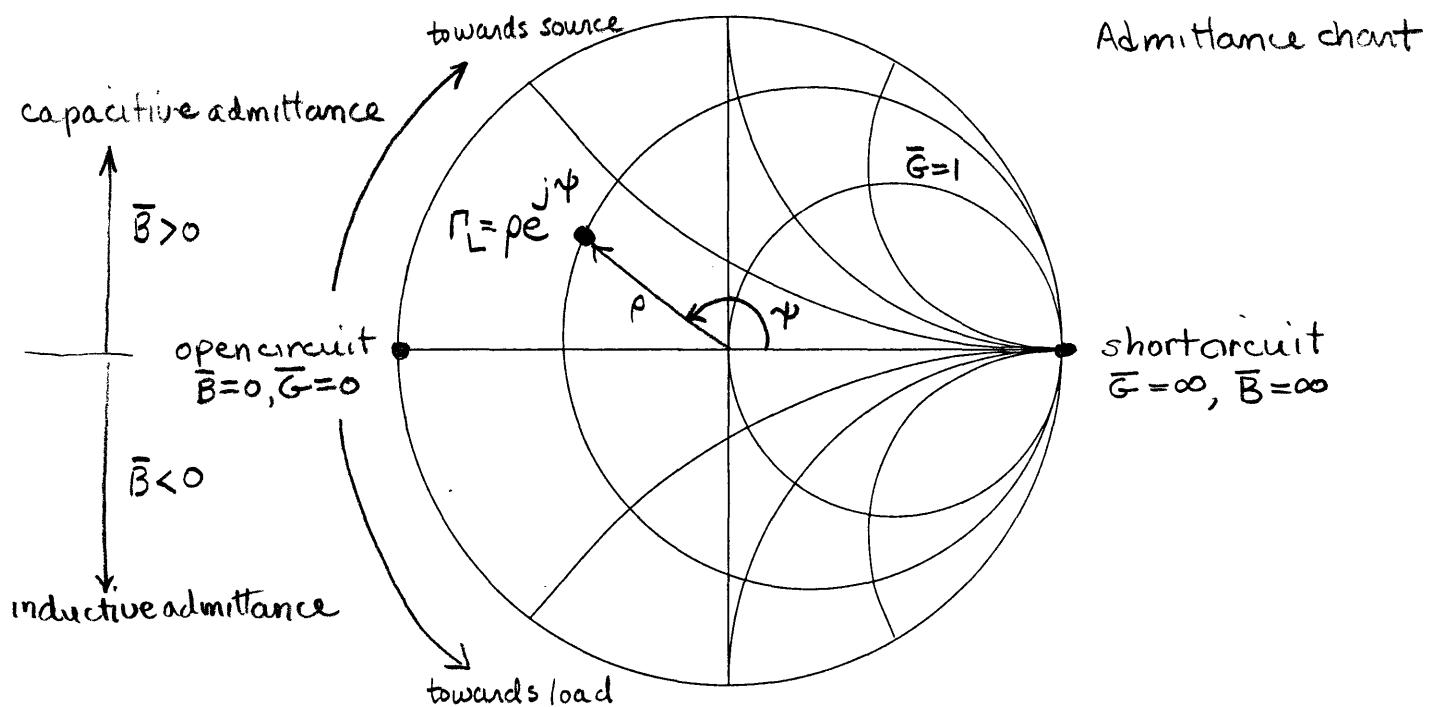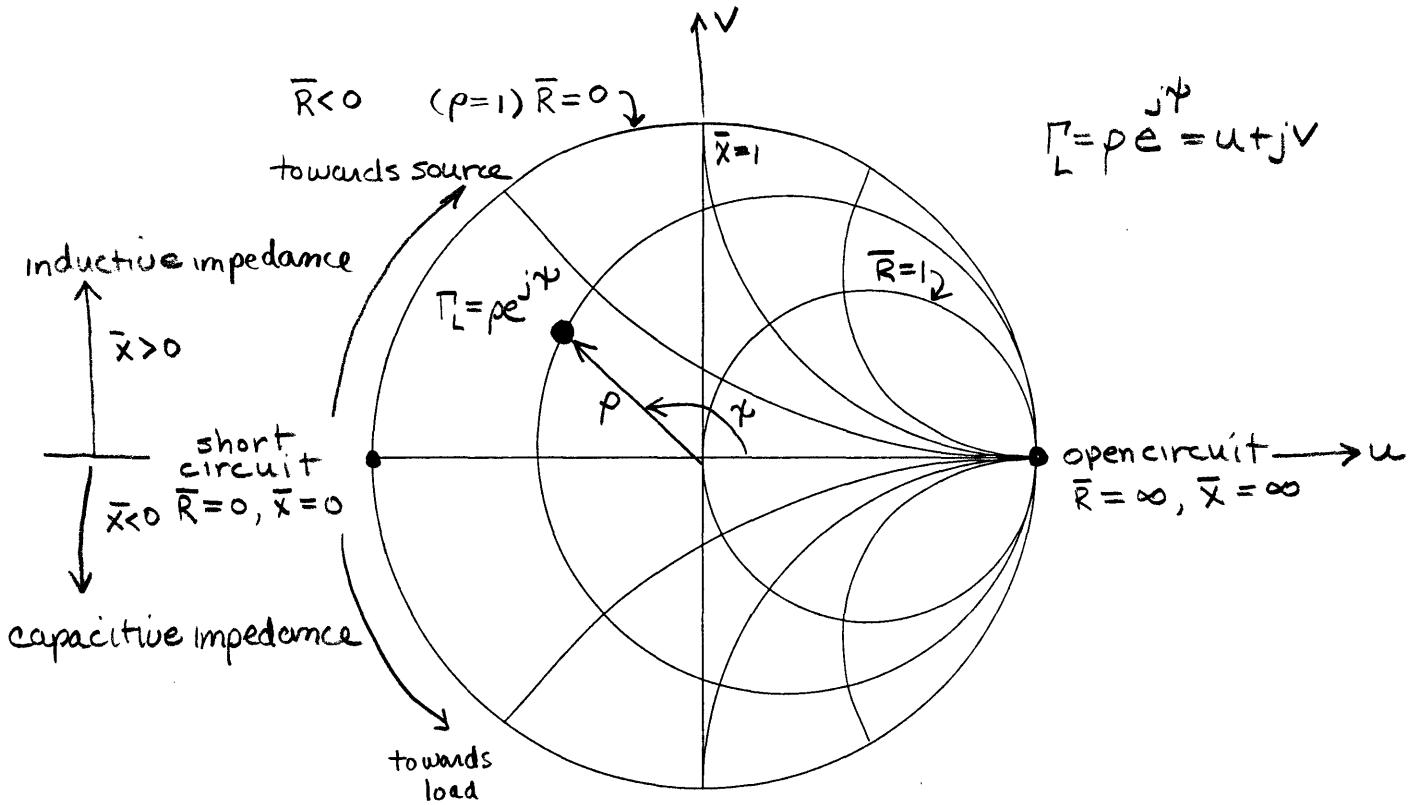The circles of $\bar{\Gamma}$ given \bar{x} , (constant \bar{x} circles)
There are two circles



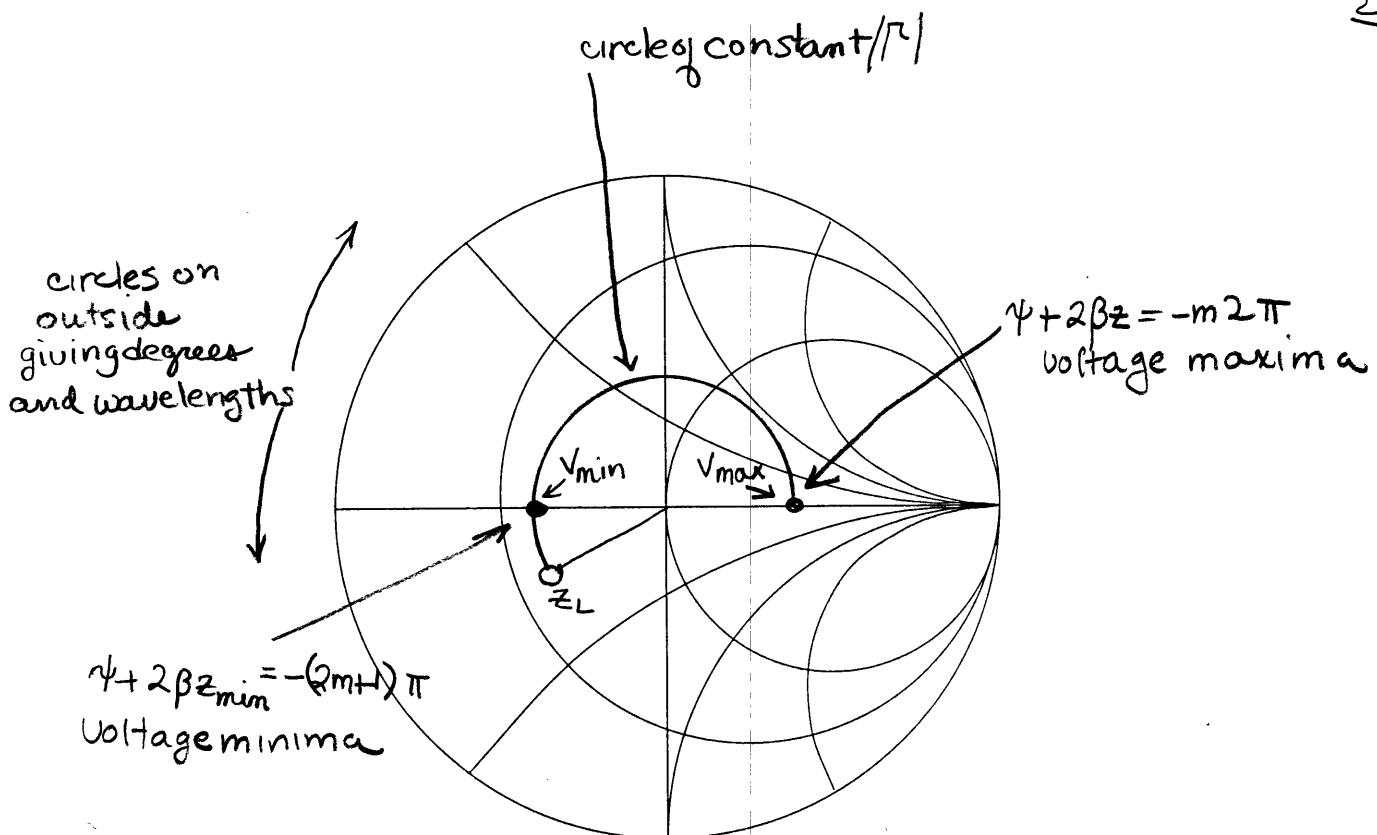rotation is understood by remembering that $\bar{Y} = \bar{Y}_L e^{j2\beta z} - \bar{Y}_L e^{-j2\beta z}$
 as you move away from the load z is increasing negative
 reducing the angle ψ




What is very easy with a Smith chart is locating voltage maxima and minima

$$\text{Recall that } S = \frac{1+\rho}{1-\rho}$$

$$\text{At a voltage maxima } \bar{Z} = \bar{R}_{\max} = S$$

so the S circles are the same as the ρ circles.

Example 3-20

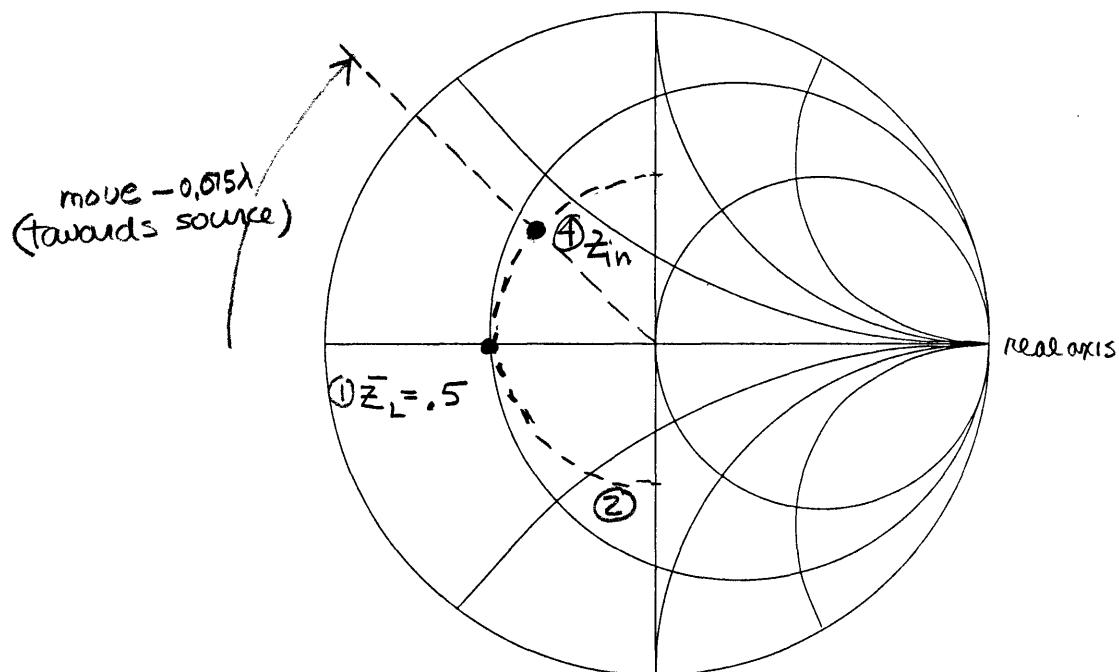

Find the input impedance of a lossless transmission line with the parameters $\bar{Z}_0 = 100\Omega$, $\bar{Z}_L = 50 + j0\Omega$, $l = 86.25\text{cm}$, and $\lambda = 1.5\text{m}$.

$$\text{Electrical length of line is } \frac{0.8625}{1.5} = 0.575\lambda$$

$$\textcircled{1} \quad \bar{Z}_L = \frac{\bar{Z}_L}{\bar{Z}_0} = \frac{50}{100} = 0.5 \text{ and enter on chart}$$


$\textcircled{2}$ draw constant ρ circle

$\textcircled{3}$ impedance goes as $2\beta l$ so a full cycle every $\frac{\lambda}{2}$
so examine line length $0.575\lambda - 0.5\lambda = 0.075\lambda$
move 0.075λ away from load (towards source)

$$\textcircled{4} \quad \text{read off } \bar{Z}_{in} \approx 0.59 + j.36$$

$$Z_{in} = 59 + j36\Omega$$


Example 3-22

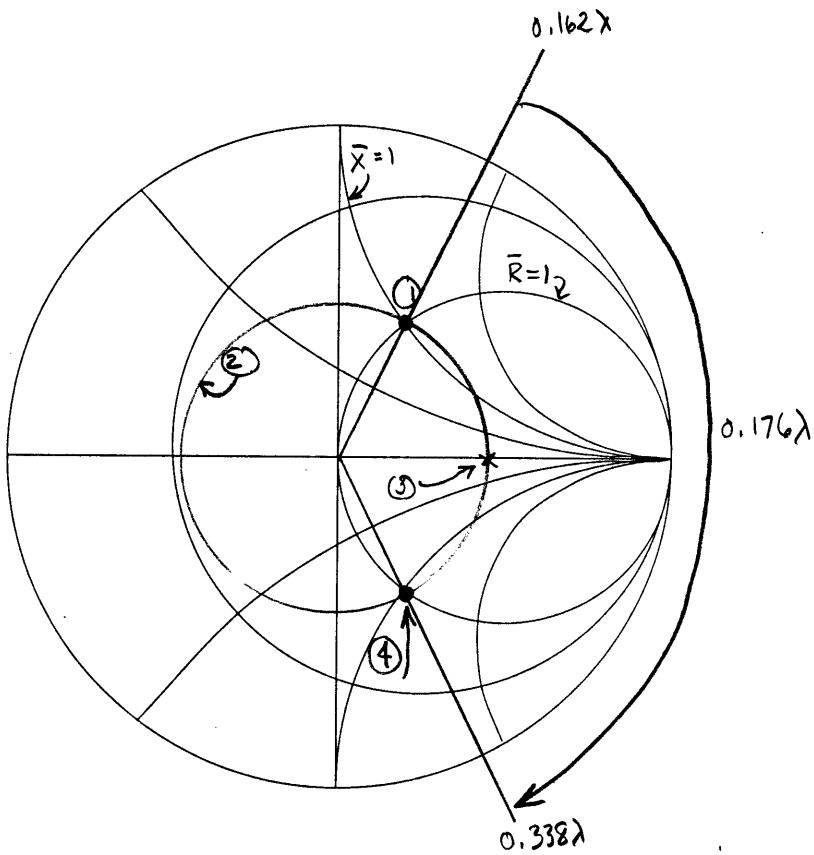

Find the input impedance Z_{in} of a lossless transmission line given the following parameters: $Z_0 = 100\Omega$, $Z_L = 100 + j100$, line length $l = 0.676\lambda$ (i.e., $0.5\lambda + 0.176\lambda$).

- ① The normalized load impedance is $\bar{Z}_L = \frac{100 + j100}{100} = 1 + j1$ enter on chart.
- ② Draw circle of constant ρ (centered at origin) through this point
- ③ Note that the intersection of this circle with the real axis gives $\bar{R} \approx 2.62$. This is also the value of S .
 $S = 2.62$ circle
- ④ To find Z_{in} which goes as $2\beta l$ we move along this circle (clockwise) towards source. Remember that it repeats every $\frac{\lambda}{2}$ so we go 0.176λ . We start at 0.162λ from chart and add 0.176λ to get 0.338λ . This corresponds to $\bar{Z}_{in} = 1 - j1 = 100 - j100$.

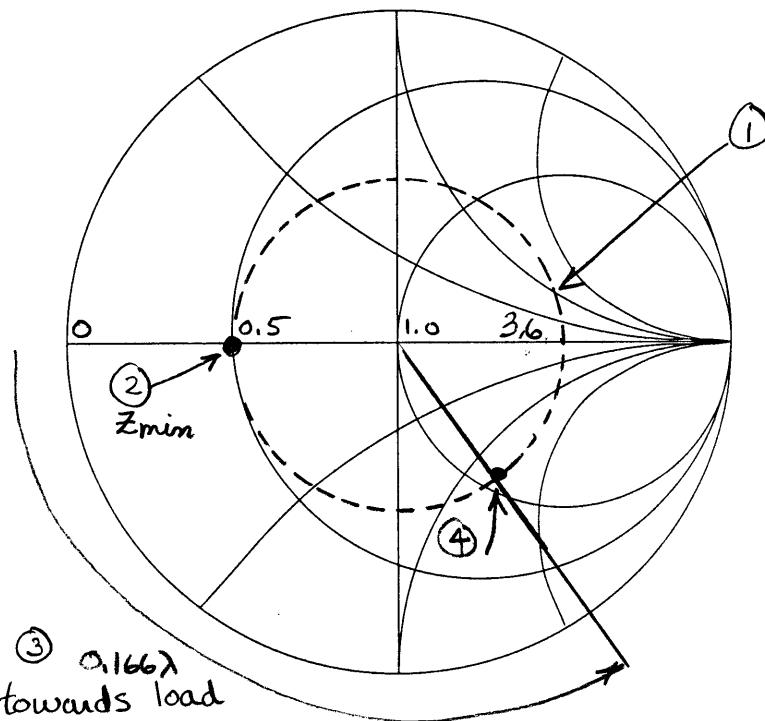
Example 3-23. Find the normalized load impedance on a transmission line with the following measured parameters : standing wave ratio $S = 3.6$ and first voltage minimum $z_{min} = -0.166\lambda$.



- ① Draw constant ρ circle corresponding to $S = 3.6$
- ② z_{min} is where this circle intersects negative u axis.
- ③ Start with z_{min} and move towards load (counterclockwise) a distance $+0.166\lambda$.
- ④ This location gives unknown (now known) load impedance to be $\bar{z}_L = 0.89 - j1.13$

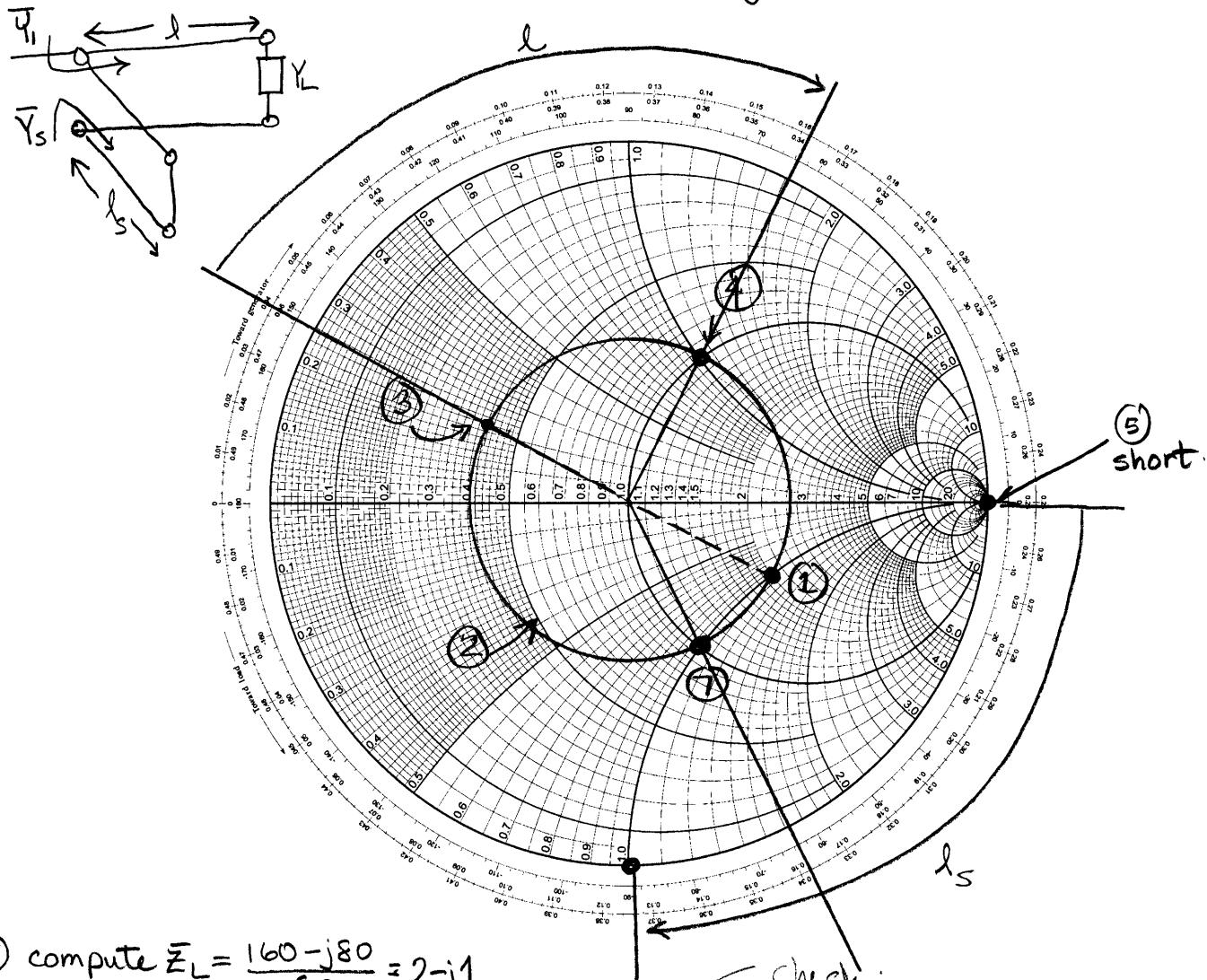Example 3-24

Given a characteristic impedance $Z_0 = 80\Omega$ and a load admittance $\bar{Y}_L = 160 - j80$, match the line to the load by using a short circuited stub.



① compute $\bar{Z}_L = \frac{160 - j80}{80} = 2 - j1$
and plot on chart.

② Draw circle of constant ρ through Z_L .

③ Convert \bar{Z}_L to \bar{Y}_L . $\bar{Y}_L = \frac{1}{\bar{Z}_L} = 0.4 + j1.2$ and plot.

Note: this corresponds to reflection through the origin.

④ Determine $\bar{Y}_{in} = 1 + jB$ by moving on constant ρ circle towards source (clockwise) until you reach $G=1$ ($R=1$) circle.

The amount of rotation determines λ which is $0.162 - 0.04 = 0.122\lambda$

The intersection is at $\bar{Y} = 1 + j1$ so we require stub with $\bar{Y}_s = -j1$



The intersection is at $\bar{Y} = 1 + j1$ so we require stub with $\bar{Y}_s = -j1$

⑤ A short circuit is the right most point on the admittance chart.

⑥ move on circle of constant ρ , i.e. outer edge of chart until you reach $B=1$. This is what you wanted and gives $\lambda = 0.125\lambda$.

⑦ A second solution exists at $\bar{Y} = 1 - j1$. This solution is at $\lambda = .338 - .040 = .298\lambda$. This requires $\bar{Y}_s = +1$ and requires a much longer stub, i.e., $\lambda = .375\lambda$

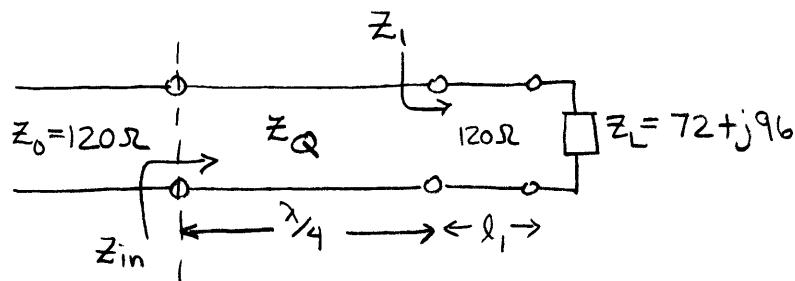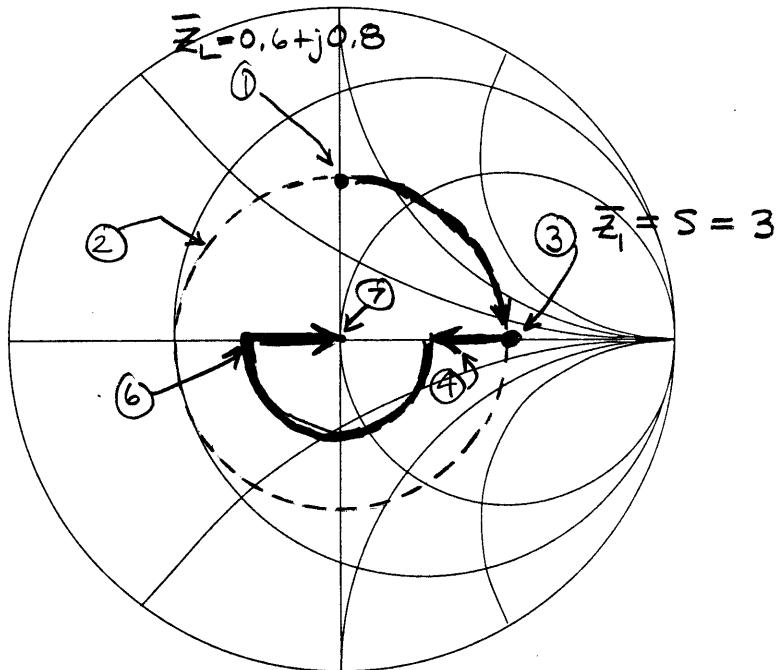3.25 Given a transmission line with a characteristic impedance $Z_0 = 120\Omega$ and line impedance $Z_L = 72 + j96\Omega$ and load impedance $Z_L = 72 + j96\Omega$, match the line to the given load using a quarter-wave transformer.



This is different than stub matching where we find l_1 such that \bar{Y}_1 would be $1 + j\bar{B}$. With quarter-wave transformer find l_1 where \bar{Z}_1 is entirely real, i.e., $X = 0$

$$\textcircled{1} \quad \bar{Z}_L = \frac{72 + j96}{120} = 0.6 + j0.8$$

\textcircled{2} Draw constant ρ circle thru \bar{Z}_L

\textcircled{3} Move along circle away from load (clockwise) to intersection with horizontal axis, i.e. $X = 0$.

At this point $\bar{Z}_1 = S_1 = 3$.

\textcircled{4} Quarter-wave transformer gives $Z_Q = \sqrt{R_1 R_2} = \sqrt{(Z_0)(3Z_0)}$

$Z_Q = 1.732 \times 120 = 207.8$. This moves us from circle of $S = 3$ to circle of $S = 1.732$, i.e. $3/\sqrt{3} = \sqrt{3}$

\textcircled{5} $\lambda/4$ corresponds to a 180° rotation clockwise (towards source).

\textcircled{6} $\bar{Z}_{in} = 0.577$. This is referred to $Z_Q = 207.8$. Converting back to $Z_0 = 120$ we get $Z_{in} = 0.577 \left(\frac{207.8}{120} \right) = 1$ so we are matched.