

INDEX

| | |
|---|---------|
| Index | i-iii |
| History of radio | 1-4 |
| Superheterodyne radio concepts | 5-13 |
| Electrical noise | 37-52 |
| Noise lecture notes | 53-59 |
| Noise examples | 60 |
| <i>Getting Started With Automatic Noise Figure Measurements</i> | 73-79 |
| Gain definitions | 80-86 |
| DC characteristics of BJTs and FETs | 87-93 |
| Amplifier principles | 93-98 |
| Design notes for common emitter BJT amplifiers | 100-109 |
| Bias stabilization | 110-115 |
| Basic small signal models: tee, hybrid-pi and h | 116-121 |
| Reading transistor data sheets/parameter variation .. | 122-128 |
| FET Amplifiers | 129-140 |
| Small signal amplifiers | 141-143 |
| h-parameter formula | 144 |
| cascode amplifier | 145-146 |
| Power amplifiers: | |
| <i>Power amplifiers</i> | 150-160 |
| Biasing the Class B amplifier | 166-174 |
| <i>Heatsinking power amplifiers</i> | 174-179 |
| Power amplifier examples | 180-186 |
| Automatic gain control | 200-202 |
| Two-port networks: | |
| Two-port networks | 211-216 |
| Matrix parameters, definitions & conversions | 217-224 |
| Two-port power gains | 224-231 |
| Two-port interconnections | 232-234 |
| Two-port examples | 235-238 |

| | |
|--|---------|
| Resonant networks | 236-246 |
| Series-parallel conversions | 248-249 |
| Impedance matching networks | 267-270 |
| Impedance matching examples | 271-278 |
| Transformer modeling | 290-296 |
| Tuned transformers | 297-301 |
| Autotransformers | 302-306 |
| Transformer examples | 307-312 |
| RF amplifiers | 330-351 |
| <i>RF Small Signal Design Using Two-Port Parameters</i> . | 352-364 |
| RF amplifier examples | 365-386 |
| Mixers | 390-400 |
| Converters | 401-402 |
| <i>Transistor Mixer Design Using 2-Port Parameters</i> | 403-412 |
| Mixer examples | 413-418 |
| Feedback Amplifiers and Oscillators | 440-471 |
| Oscillator notes | 472-484 |
| Oscillator design problems | 485-499 |
| Phase-locked loops | 550-565 |
| <i>Phase-Locked Loop Design Fundamentals</i> | 566-577 |
| PLL notes | 578-596 |
| PLL examples | 597-607 |
| Total pages actually present: | |
| Reserved pages | |

Appendix A: Transistor Specifications

| | |
|-------------------------|-------|
| 2N2222 NPN BJT | 1-11 |
| 2N2907 PNP BJT | 12-14 |
| 2N3904 NPN BJT | 15-16 |
| 2N3906 PNP BJT | 17-19 |
| 2N5109 NPN RF BJT | 20-25 |
| MPF102 FET | 26 |
| 2N4416 UHF FET | 27-33 |

Appendix B: Grounding and Noise in Electrical Circuits 1-21

Appendix C: Computer Analysis of Electrical Circuits

| | |
|--|-----------------------------------|
| Computer analysis of electrical circuits | 1-6 |
| Network Analysis on the Personal Computer | 7-12 39-44 |
| Transistor Parameter Conversion | 13-15 45-47 |
| BASIC Program Computes Values for 14 Matching Networks | 16-19 48-51 |
| Design of RF Amplifiers: Part I: Using Potentially Unstable Devices | 20-22 52-54 |
| Part II: Using Potentially Stable Devices | 23-25 55-57 |

| | |
|---------------------------------|------|
| # Definitions | C-1 |
| 2 General background | C-1 |
| PSpice commands | C-5 |
| analysis | C-6 |
| i/o commands | C-17 |
| PSpice devices | C-20 |
| PSpice models | C-31 |

STATEMENT

These notes are FOR the students of EEAP 341. They are not a book nor an attempt to write a book. No one is making any money (except Kinko's) on these notes. They are instead an attempt to bring together material and an approach that is not found in any current textbook. Consequently, certain sections of these notes will look like parts of a book but may be difficult to read or use without the accompanying classroom lecture. The hope is that these notes will help explain with theory and examples some of the more difficult aspects of communications circuits.