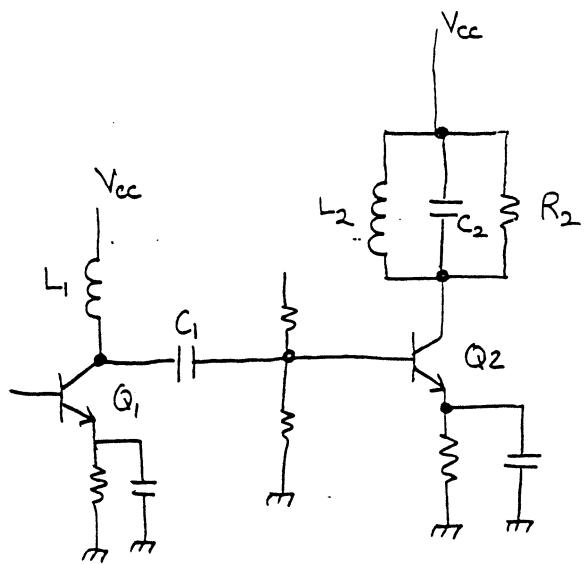


design of a small signal r.f. amplifier:



from data sheets Q_1 & Q_2 are identical

$$y_{ie} = 10 + j10 \text{ mV}$$

$$y_{re} = -j0.001 \text{ mV}$$


$$y_{fe} = 10 \times 10^{-3}$$

$$y_{oe} = 0.1 \times 10^{-3}$$

design for $f_0 = 50 \text{ MHz}$

$$\text{BW} = 0.5 \text{ MHz}$$

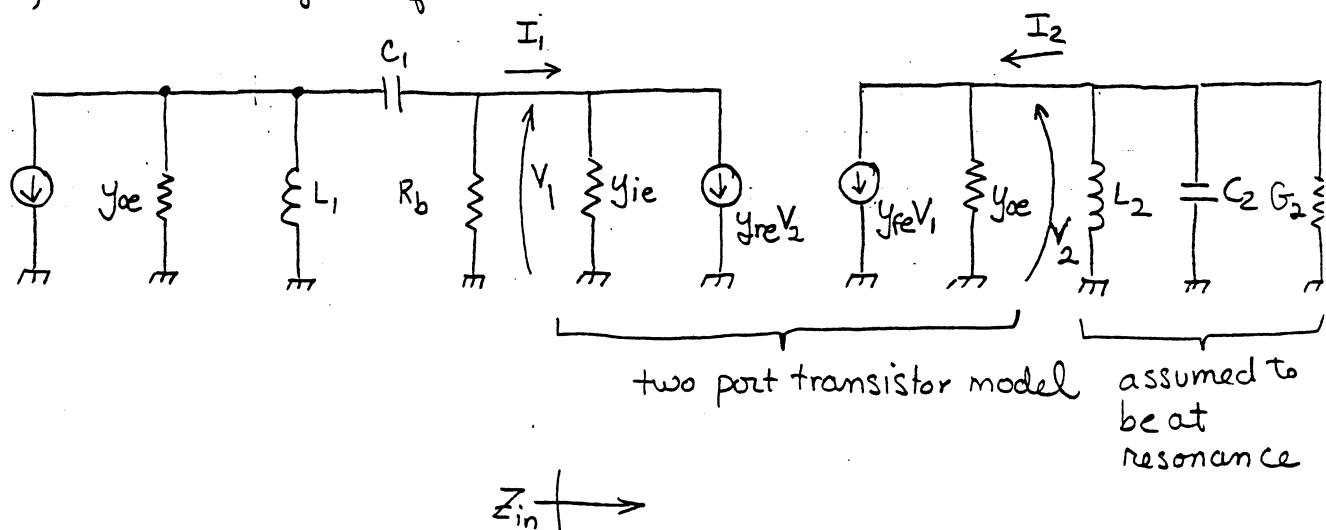First, draw small signal equivalent circuit:



$$Z_{in} = \frac{V_1}{I_1} = \frac{V_1}{y_{ie}V_1 + y_{re}V_2}$$

$$\text{at resonance: } y_{fe}V_1 + g_{oe}V_2 = -G_2V_2$$

$$\therefore V_2 = -\frac{y_{fe}}{g_{oe} + G_2}$$

at resonance.

$$\therefore Z_{in} = \frac{V_1}{Y_{ie}V_1 - \frac{Y_{re}Y_{fe}}{g_{oe} + G_2} V_1} = \frac{1}{Y_{ie} - \frac{Y_{re}Y_{fe}}{g_{oe} + G_2}}$$

$$\text{or } Y_{in} = Y_{ie} - \frac{Y_{re}Y_{fe}}{g_{oe} + G_2}$$

$$= (10 + j10) \times 10^{-3} + \frac{(10 \times 10^{-3})(-j.001 \times 10^{-3})}{0.1 \times 10^{-3} + 10 \times 10^{-3}}$$

use complex number calculator

$$Y_{in} \approx (10 + j10) \text{ m}^{-1} + \frac{j.001 \text{ m}^{-1}}{\text{negligible effect of load}}$$

$$Z_{in} = \frac{1}{Y_{in}} = \frac{1}{10 + j10 \text{ m}^{-1}} = 50 - j50 \Omega$$

$$\begin{aligned} &\text{find } C_{in}: \\ &\text{at } 50 \text{ MHz} \quad \frac{1}{j\omega_0 C_{in}} = -j50 \end{aligned}$$

$$C_{in} = \frac{1}{50 \cdot 2\pi (50 \times 10^6)} = 63.7 \text{ pF}$$

what is A_v at resonance?

$$A_v = \frac{V_2}{V_1}$$

$$I_1 = Y_{ie}V_1 + Y_{re}V_2$$

$$I_2 = Y_{fe}V_1 + g_{oe}V_2$$

$$\text{but } I_2 = -\left(j\omega C_2 + \frac{1}{j\omega L_2} + G_2\right)V_2$$

$$\therefore y_{fe} V_1 + y_{oe} V_2 = (-j\omega C_2 - \frac{1}{j\omega L_2} - G_2) V_2$$

$$V_1 = \frac{(-j\omega C_2 - \frac{1}{j\omega L_2} - G_2 - y_{oe}) V_2}{y_{fe}}$$

$$A_v = \frac{V_2}{V_1} = \frac{V_2}{(-j\omega C_2 - \frac{1}{j\omega L_2} - G_2 - y_{oe}) \frac{V_2}{y_{fe}}}$$

$$= - \frac{y_{fe}}{j\omega C_2 + \frac{1}{j\omega L_2} + G_2 + y_{oe}}$$

\uparrow
 $y_{oe} + j b_{oe} = y_{oe} + j \omega_o C_{oe}$
at resonance

$$= - \frac{y_{fe}}{(G_2 + y_{oe}) + j (\underbrace{\omega_o C_2 + \omega_o C_{oe} - \frac{1}{\omega_o L_2}}_{\text{goes to zero at resonance}})}$$

$$\omega_o^2 = \frac{1}{L_2(C_2 + C_{oe})}$$

at resonance

$$A_v = - \frac{y_{fe}}{G_2 + y_{oe}} \quad \leftarrow \quad y_{fe} = |y_{fe}| e^{j\theta}$$

Since I am only interested in gain use the magnitude

$$|A_v| = - \frac{|y_{fe}|}{G_2 + y_{oe}}$$

to find bandwidth I need to understand how the y-parameters vary with frequency.

For narrow band circuits the y-parameters are usually simple functions of frequency and can be expanded in a Taylor series about ω_0 , i.e.

$$y_{ie} = g_{ie} + j b_{ie}$$

$$\approx g_{ie} + j b_{ie} \Big|_{\omega=\omega_0} + j(\omega-\omega_0) \frac{\partial b_{ie}}{\partial \omega} \Big|_{\omega=\omega_0}$$


In general, b_{ie} will be capacitive at high frequencies and g_{ie} will be independent of frequency (approximately)

For the transistor amplifier

$$A_v(f) = - \frac{y_{fe}}{(G_2 + g_{oe}) + j(\omega C_2 + b_{oe} - \frac{1}{\omega L_2})}$$


Independent of f
only this term is a sharp function near resonance

this term is not involved in resonance

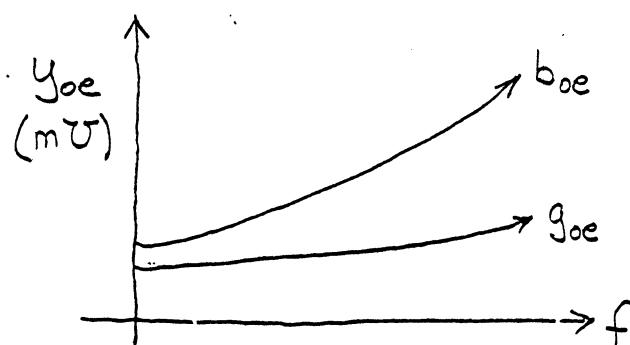

introduction to stability

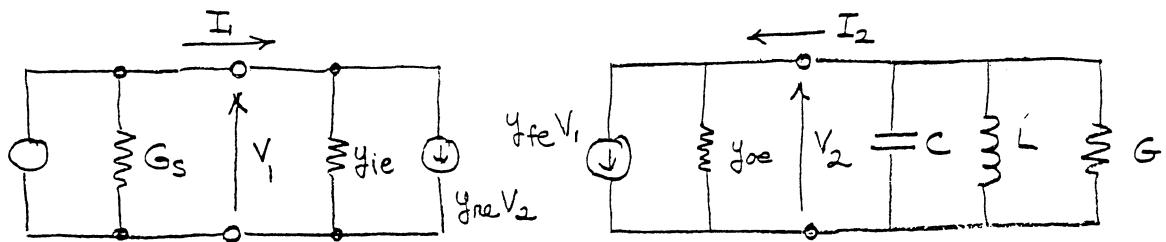consider the small signal tuned amplifier shown below




input admittance can be shown to be


$$Y_{IN} = y_{ie} - \frac{y_{fe} y_{re}}{y_{oe} + G_L}$$

this was the basic result of our last homework problem

input then looks like

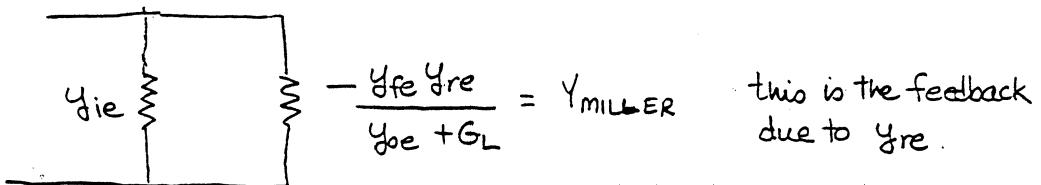

examine this feedback term

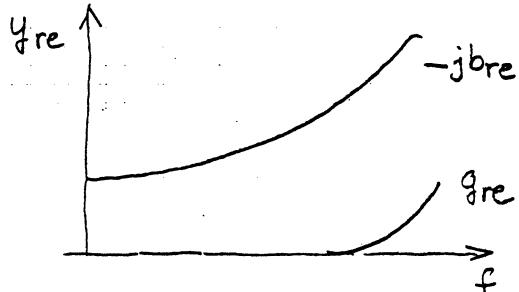

y_{fe} is usually real (for $f < f_T$)

$y_{re} \approx -j\omega C_{re}$ (due to capacitive nature of feed back)

the negative sign is due to the phase inversion between the input and output

$$Y_{MILLER} = -\frac{g_{fe} (-j\omega C_{re})}{y_{oe} + Y_L} = +\frac{j\omega C_{re} g_{fe}}{y_{oe} + Y_L}$$

if $f < f_0$ (the resonant frequency of the tank) Y_L is inductive

$f > f_0$ Y_L is capacitive

$$\text{for } f < f_0 \quad Y_{oe} + Y_L = R - jB$$

$$Y_{MILLER} = \frac{j\omega C_{re} g_{fe}}{R - jB} \quad \frac{R + jB}{R + jB} = - \frac{\omega C_{re} g_{fe} B + j\omega R C_{re} g_{fe}}{R^2 + B^2}$$

note $Y_{MILLER} < 0$ for $f < f_0$

this can give rise to $\text{Re}(Y_{IN}) < 0$ and will result in oscillation. One way to keep an amplifier from oscillating is to add a suitable positive conductance at the input terminals.

stability : what happens to γ_{IN} with different loads

$$\gamma_{IN} = g_{11} - \frac{y_{12} y_{21}}{y_{22} + y_L}$$

$$g_{IN} = g_{11} - \frac{(g_{22} + g_L)^2 + (b_{22} + b_L)^2 - (g_{22} + g_L) \operatorname{Re}(y_{12} y_{21}) - (b_{22} + b_L) \operatorname{Im}(y_{12} y_{21})}{(g_{22} + g_L)^2 + (b_{22} + b_L)^2}$$

consider two cases

I. $g_L = \infty$ a short circuit

$$g_{IN} \rightarrow g_{11} - \frac{g_L^2 - g_L \operatorname{Re}(y_{12} y_{21})}{g_L^2} \rightarrow g_{11}$$

simply require $g_{11} > 0$ for stability

II. $g_L = 0$ open circuit

complicated expression

examine $g_{IN, MIN}$

minimize $g_{IN, MIN}$ by taking $\frac{\partial g_{IN}}{\partial b_L}$ (since $g_L = 0$ don't need it)

result is $g_{11} g_{22}^2 - g_{22} \operatorname{Re}(y_{12} y_{21}) - \frac{\operatorname{Im}(y_{12} y_{21})}{4g_{11}} > 0$

if this is satisfied, $g_{IN, MIN} > 0$

III. general case of $\gamma_L = g_L + jb_L$

minimize g_{IN} by differentiating $\frac{\partial g_{IN}}{\partial g_L}, \frac{\partial g_{IN}}{\partial b_L}$

we get $\begin{cases} g_L = 0 \\ b_L = -b_{22} + \frac{\text{Im}(y_{12}y_{21})}{2g_{11}} \end{cases}$

as worse case

$$\text{evaluate } g_{IN,\min} = \frac{\left[g_{22} - \frac{\text{Re}(y_{12}y_{21})}{2g_{11}} \right]^2 - \frac{|y_{12}y_{21}|^2}{4g_{11}^2}}{(g_{22})^2 + \frac{[\text{Im}(y_{12}y_{21})]^2}{4g_{11}^2}}$$

for stability $g_{22} - \frac{\text{Re}(y_{12}y_{21})}{2g_{11}} > \frac{|y_{12}y_{21}|}{2g_{11}}$

re-write as

$$\frac{|y_{12}y_{21}|}{2g_{11}g_{22} - \underbrace{\text{Re}(y_{12}y_{21})}_{\text{Linivill stability factor}}} < 1$$

Linivill stability factor
usually labeled C.


For $0 < C < 1$ a device is unconditionally stable

$C \geq 1$ device is conditionally stable

in terms of C

$$A_{MAG} = 2 \frac{1 - \sqrt{1 - C^2}}{C^2} G_\infty$$

where $G_\infty = \frac{|y_{21}|^2}{4g_{11}g_{22} - 2\text{Re}(y_{12}y_{21})}$

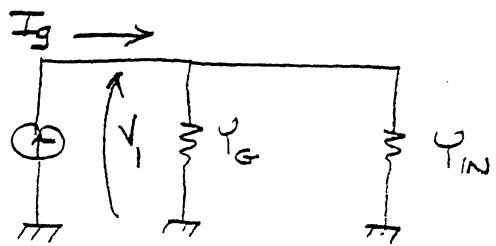

$$I_G = Y_G V_1 + Y_{IN} V_1 \\ = (Y_G + Y_{IN}) V_1$$

$$\therefore A_T = 4 g_G g_L \frac{|V_2|^2}{|Y_G + Y_{IN}|^2 |V_1|^2}$$

$$A_T = \frac{4 g_G g_L}{|Y_G + Y_{IN}|^2} \frac{|Y_{21}|^2}{|Y_{22} + Y_L|}$$

Usually we want to maximize A_T . How?

$$A_T = f(g_G, b_G, g_L, b_L)$$

take partial derivatives with respect to these variables and set all derivatives equal to zero.

$$A_{T, \max} = A_{\text{mag}} = \frac{|Y_{21}|^2}{2 g_{11} g_{22} - \text{Re}(y_{12} y_{21}) + \sqrt{(2 g_{11} g_{22} - \text{Re}(y_{12} y_{21}))^2 - |y_{12} y_{21}|^2}}$$

the necessary terminations are


$$g_{L0} = \frac{1}{2 g_{11}} \sqrt{2 g_{11} g_{22} - \text{Re}(y_{12} y_{21})^2 - |y_{12} y_{21}|^2}$$

$$b_{L0} = -b_{22} + \frac{\text{Im}(y_{12} y_{21})}{2 g_{11}}$$

$$g_{G0} = \frac{g_{11}}{g_{22}} g_{L0}$$

$$b_{G0} = -b_{11} + \frac{\text{Im}(y_{12} y_{21})}{2 g_{22}}$$

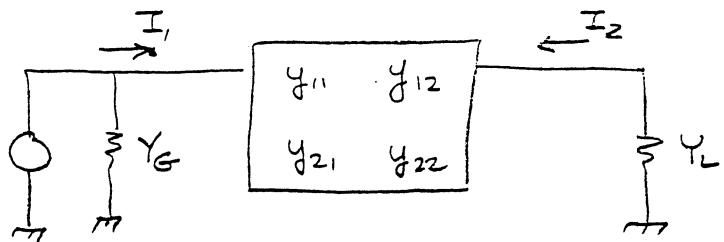p.358 notes amplifier gains in terms of y -parameters



$$Y_{IN} = Y_{11} - \frac{Y_{12} Y_{21}}{Y_{22} + Y_L}$$

$$Y_{OUT} = Y_{22} - \frac{Y_{12} Y_{21}}{Y_{11} + Y_G}$$

$$\left. \begin{array}{l} I_1 = Y_{11} V_1 + Y_{12} V_2 \\ I_2 = Y_{21} V_1 + Y_{22} V_2 \end{array} \right\} \text{from definitions}$$

$$\text{but } I_2 = -V_2 Y_L$$

$$-V_2 Y_L = Y_{21} V_1 + Y_{22} V_2$$

$$\frac{V_2}{V_1} = \frac{-Y_{21}}{Y_{22} + Y_L}$$

simple expression for A_P


$$A_P = \frac{P_L}{P_{IN}} = \frac{|V_2|^2 g_L}{|V_1|^2 g_{IN}} = \left| -\frac{Y_{21}}{Y_{22} + Y_L} \right|^2 \frac{g_L}{g_{11} - \operatorname{Re} \left\{ \frac{Y_{12} Y_{21}}{Y_{22} + Y_L} \right\}}$$

$$A_T = \frac{P_L}{P_{AS}} = \frac{|V_2|^2 g_L}{|I_g|^2} = 4 g_G g_L \left| \frac{V_2}{I_g} \right|^2$$

get I_g by examining input circuit

Unilateralized amplifier :

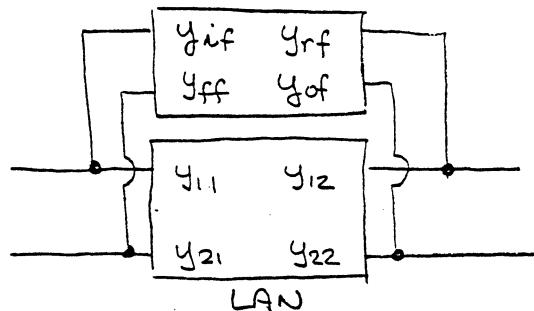- use an external feed back network to make a composite $y_{12} = 0$
- increases input-output isolation




since devices are in parallel.

$$\text{composite } [Y]_c = \underbrace{\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}}_{\text{LAN}} + \underbrace{\begin{bmatrix} y_{if} & y_{rf} \\ y_{ff} & y_{of} \end{bmatrix}}_{\text{feedback}} = \underbrace{\begin{bmatrix} y_{11} + y_{if} & y_{12} + y_{rf} \\ y_{21} + y_{ff} & y_{22} + y_{of} \end{bmatrix}}_{\text{composite}}$$

for unilateralization want $y_{12} + y_{rf} = 0$

typical feedback element

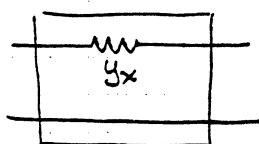


$$[Y]_{\text{feedback}} = \begin{bmatrix} y_x & -y_x \\ -y_x & y_x \end{bmatrix}$$


Neutralization

just cancel $\Im y_{12, \text{composite}}$ for neutralization
 real part remains, usually amplifier is stable with
 just resistive $y_{12, \text{composite}}$

examples of neutralization

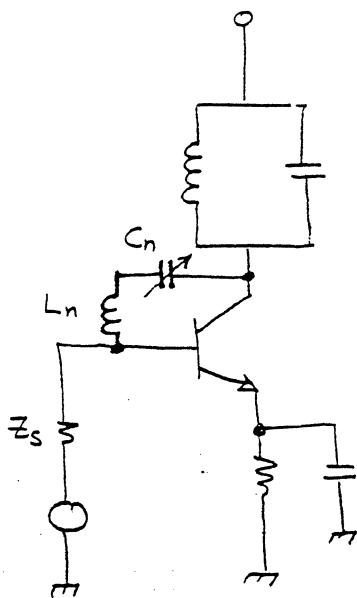

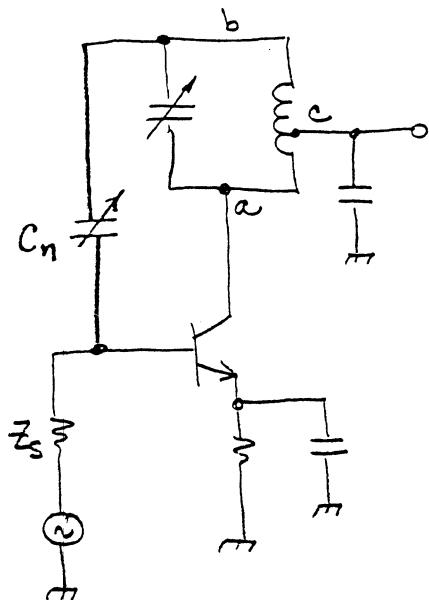tune $L_n - C_n$ to below resonance (inductive) to cancel capacitive feedback from collector to base.




This is a clever circuit. Center-tap of transformer (c) provides ground reference. Points (a) and (c) are 180° out of phase $\Rightarrow C_n$ looks like its phase is inverted, i.e. an inductance to the base of the transistor

few remaining topics

unilateral amplifiers

$y_{12} = 0$ (no feedback)

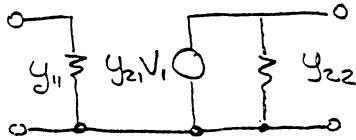

$$A_{MAG} = \frac{|y_{21}|^2}{2g_{11}g_{22} - \operatorname{Re}(y_{12}y_{21}) + \sqrt{(2g_{11}g_{22} - \operatorname{Re}(y_{12}y_{21}))^2 - |y_{12}y_{21}|^2}}$$

If $y_{12} = 0$

$$A_{MAG} \rightarrow \frac{|y_{21}|^2}{2g_{11}g_{22} + \sqrt{(2g_{11}g_{22})^2}} = \frac{|y_{21}|^2}{4g_{11}g_{22}}$$

conjugate matching : $\gamma_L = y_{22}^*$

$$A_P = \frac{|y_{21}|^2 g_L}{\underbrace{|y_{22} + \gamma_L|^2 g_{IN}}_{2g_{22} \text{ since imaginary parts cancel}}} \rightarrow \frac{|y_{21}|^2 g_{22}}{4g_{22}^2 g_{IN}} = \frac{|y_{21}|^2}{4g_{22} g_{IN}} \equiv G_{oo}$$

G_{oo} is the Linvill figure of merit for a transistor

$$\begin{aligned} g_{IN} &= g_{11} - \operatorname{Re} \left[\frac{y_{12} y_{21}}{y_{22} + \gamma_L} \right] = g_{11} - \frac{\operatorname{Re}(y_{12} y_{21})}{2g_{22}} \\ &= \frac{2g_{11}g_{22} - \operatorname{Re}(y_{12} y_{21})}{2g_{22}} \end{aligned}$$

$$G_{oo} = \frac{|y_{21}|^2}{4g_{22} [2g_{11}g_{22} - \operatorname{Re}(y_{12} y_{21})]}$$

maximum
unilateral
gain

Stern stability factor

Suppose we evaluate a transistor for which $C > 1$

$$C = \frac{|y_{12} y_{21}|}{2g_{11} g_{22} - Re(y_{12} y_{21})}$$

We can make this transistor stable by increasing the product $2g_{11} g_{22}$ until $C < 1$. This can be done by external loading, i.e. adding g_L and g_G to get

$$g'_{11} = g_{11} + g_G$$

$$g'_{22} = g_{22} + g_L$$

Note: adding g_L and g_G means lowering R_L and R_G so that the stability criteria becomes:

$$\frac{|y_{12} y_{21}|}{2(g_{11} + g_G)(g_{22} + g_L) - Re(y_{12} y_{21})} < 1$$

cross-multiplying:

$$2(g_{11} + g_G)(g_{22} + g_L) - Re(y_{12} y_{21}) > |y_{12} y_{21}|$$

$$2(g_{11} + g_G)(g_{22} + g_L) > |y_{12} y_{21}| + Re(y_{12} y_{21})$$

$$K \equiv \frac{2(g_{11} + g_G)(g_{22} + g_L)}{|y_{12} y_{21}| + Re(y_{12} y_{21})} > 1$$

This is defined to be the Stern stability factor and the terminated device is stable as long as $K > 1$.

Typical values might be $K = 2$ for a good amplifier

Sensitivity

A final factor is the degree of interaction between the input and output tuned circuits. We define this sensitivity to be

$$S = \frac{\left| \frac{\Delta Y_{IN}}{Y_{IN}} \right|}{\left| \frac{\Delta Y_{OUT}}{Y_{OUT}} \right|} = \frac{\text{fractional change in input}}{\text{fractional change in output}}$$

$$= \frac{\Delta Y_{IN}}{\Delta Y_{OUT}} \frac{Y_{OUT}}{Y_{IN}} = \frac{d Y_{IN}}{d Y_{OUT}} \frac{Y_{OUT}}{Y_{IN}}$$

We can use our prior results that

$$Y_{IN} = Y_{11} - \frac{Re(y_{12} y_{21})}{Y_{22} + Y_L}$$

$$Y_{OUT} = Y_{22} - \frac{Re(y_{12} y_{21})}{Y_{11} + Y_G}$$

The result of evaluating S is

$$S = \frac{|y_{12} y_{21}| |Y_L|}{|Y_{22} + Y_L| |Y_{11}(Y_{22} + Y_L) - y_{12} y_{21}|}$$

A good amplifier will have $S \leq 0.3$. We can always lower S by adding resistance (loading) to the LAN, i.e. let

$$Y'_{11} = Y_{11} + g'_G$$

$$Y'_{22} = Y_{22} + g'_L$$

This can get complicated to analyze as adding g_G and g_L will change C so a change in loading will change C, S and A_{MAG} .

Design with unconditionally stable device

$$Y = \begin{bmatrix} Y_i & \\ & \begin{bmatrix} 8+j6.8 & 0-j0.1 \\ 53-j22 & 0.4+j1.5 \end{bmatrix} \end{bmatrix} \begin{array}{l} Y_r \\ Y_o \end{array}$$

Evaluate Linvill stability factor

$$C = \frac{|Y_f Y_r|}{2g_i g_o - \operatorname{Re}(Y_f Y_r)}$$

$$Y_f Y_r = (-j0.1)(53-j22) = -2.2 - j5.3 = 5.74 \angle -112.5^\circ$$

$$\therefore C = \frac{5.74}{2(8)(0.4) - (-2.2)} = \frac{5.74}{8.6} = 0.67 < 1$$

∴ device is unconditionally stable

MAG is the maximum available gain ($Y_r = 0$
source & load matched)

$$G_T = \frac{4G_s G_L |Y_f|^2}{|(Y_i + Y_s)(Y_o + Y_L) - Y_f Y_r|^2}$$

$$\text{if } Y_i = Y_s^* \quad Y_o = Y_L^* \quad Y_r = 0$$

$$G_T = \frac{4G_s G_L |Y_f|^2}{|(2g_i)(2g_o) - 0|^2} = \frac{4G_s G_L |Y_f|^2}{16(g_i g_o)^2}$$

but $g_i = G_s$, $g_o = G_L$ for conjugate matching

$$\underline{\text{MAG}} \quad G_T = \frac{|Y_f|^2}{4g_i g_o} =$$

$$G_A = \frac{|Y_f|^2 G_s}{\operatorname{Re}[(Y_i Y_o - Y_f Y_r + Y_o Y_s) (Y_i + Y_s)^*]} \quad \leftarrow \text{use other equation}$$

$$= \frac{|Y_f|^2 G_s}{\operatorname{Re} \underbrace{[Y_o (Y_i + Y_s) (Y_i + Y_s)^*]}_{\text{for conjugate match}}}$$

$$\text{for conjugate match} \quad Y_i = G_s - j B_s \\ Y_s = G_s + j B_s$$

$$\therefore Y_i + Y_s = 2G_s$$

$$= \frac{|Y_f|^2 G_s}{\operatorname{Re} [Y_o (2G_s)(2G_s)]} = \frac{|Y_f|^2}{4 G_s g_o} = \frac{|Y_f|^2}{4 g_i g_o}$$

$$\therefore G_{MAG} = \frac{|53-j22|^2}{4(8)(0.4)} = \frac{157.41^2}{12.8} = \frac{3294.8}{12.8} = 257$$

How could we neutralize? Need a feed back element

$$-Y_x + (-j0.1m\omega) = 0 \\ \therefore Y_x = -j0.1m\omega$$

This is an inductance.

composite γ parameters $[\gamma] = \begin{bmatrix} 8+j6.8 & -j0.1 & -j0.1 & +j0.1 \\ 53-j22+j0.1 & 0.4+j1.5 & -j0.1 \end{bmatrix}$

$$= \begin{bmatrix} 8+j6.7 & 0 \\ 53-j21.9 & 0.4+j1.4 \end{bmatrix}$$

Note this is neutralized and unilateralized

since $Y_f = 0$

$$Y_{IN} = 8 + j6.7$$

$$Y_{OUT} = 0.4 + j1.4 \quad 346$$

to maximize gain conjugate match at input & output


$$\text{i.e. } Y_S = 8 - j6.7$$

$$Y_L = 0.4 - j1.4$$

maximum transducer gain

$$G_{T,\max} = \frac{|Y_{f,c}|^2}{4 g_{i,c} g_{o,c}} = \frac{|153 - j21.9|^2}{4(8)(0.4)} = \frac{|157.35|^2}{12.8} = 25$$

pole - zero analysis of tuned amplifiers

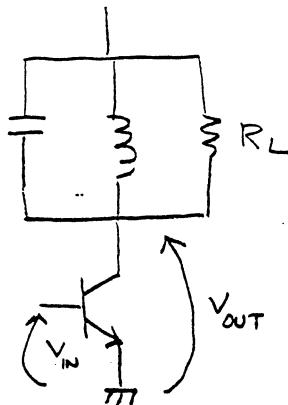

The gain for such a circuit might be written as

$$\text{at resonance } A_V(\omega_0) = -g_m V_{IN} R_L$$

$$\text{off resonance } A_V(s) = -g_m V_{IN} \frac{1}{G + sC + \frac{1}{sL}} \quad \text{where } G = \frac{1}{R_L}$$

in general, an amplifier transfer function can be written as

$$\frac{s}{(s-s_1)(s-s_2)}$$

with a single zero at $s=0$ and poles at $s=s_1, s_2$

If we solve $A_V(s)$ for s_1 and s_2 we get

$$s_1, s_2 = -\frac{G}{2C} \pm \sqrt{\left(\frac{G}{2C}\right)^2 - \frac{1}{LC}}$$

If we recognize


$$\text{Bandwidth } BW = \frac{1}{R_L C} \text{ and } \omega_0^2 = \frac{1}{LC}$$

then, by substitution,

$$s_1, s_2 = -\frac{BW}{2} \pm \sqrt{\left(\frac{BW}{2}\right)^2 - \omega_0^2}$$

if we have a high-Q circuit where $\frac{\omega_0}{BW} \gg 1$

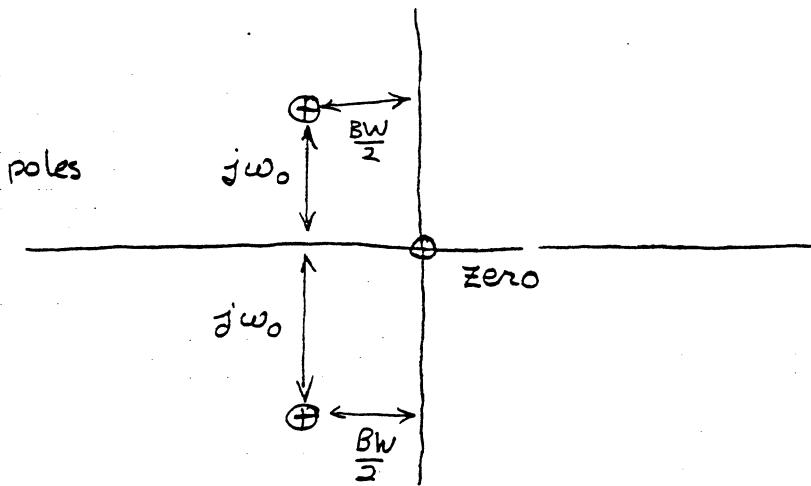
then $s_1, s_2 \approx -\frac{BW}{2} \pm j\omega_0$



If our original transfer function can be re-written

$$A_v(s) = K \frac{Z_1}{(s-s_1)(s-s_2)}$$

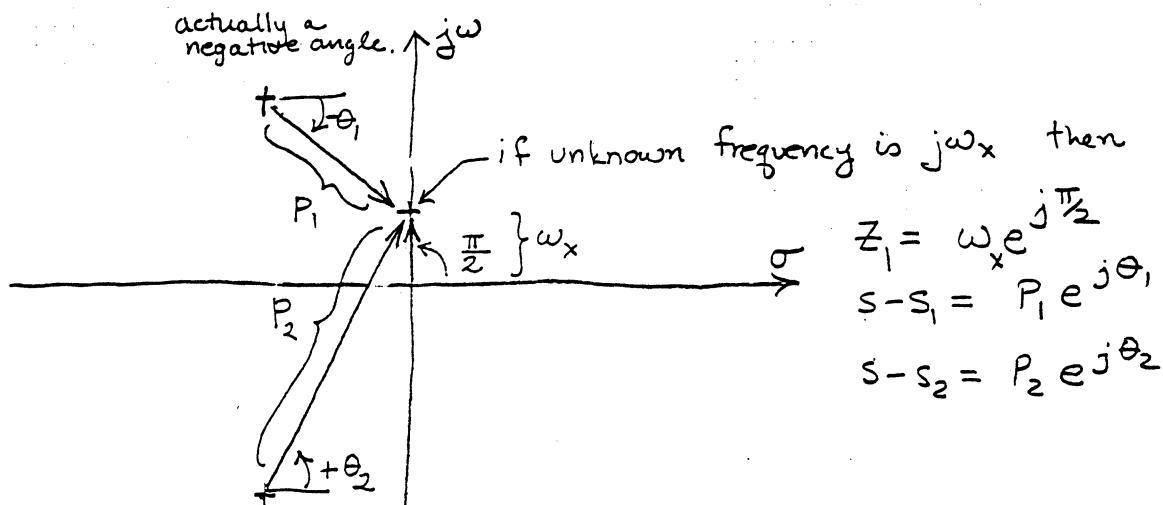where K is a gain constant,
the zero. Then, from the pole-zero diagram.



Then $A_v(j\omega_x) = K \frac{\omega_x e^{j\frac{\pi}{2}}}{P_1 e^{j\theta_1} P_2 e^{j\theta_2}} = \frac{K \omega_x}{P_1 P_2} e^{j\frac{\pi}{2} - \theta_1 - \theta_2}$

Notice that as ω_x approaches ω_0 (one of the poles)
 P_1 (or P_2) will decrease in magnitude increasing $A_v(s)$

and near a pole

$$A_v = \frac{K \omega_x e^{j(\frac{\pi}{2} - \theta_1 - \theta_2)}}{P_1 P_2} \approx \frac{-j K \omega_0}{P_1 2\omega_0} e^{j(\frac{\pi}{2} - \theta_1 - \frac{\pi}{2})} = \frac{K}{2P_1} e^{-j\theta_1}$$

This is called the single pole approximation since everything about the circuit is described by the single pole.

HOW TO ANALYZE TUNED RF AMPLIFIERS

FORMULAS:

Linvill stability factor:

$$C = \frac{|\gamma_{12}\gamma_{21}|}{2g_{11}g_{22} - \operatorname{Re}\{\gamma_{12}\gamma_{21}\}}$$

Stern stability factor:

$$K = \frac{2(g_{11} + G_S)(g_{22} + G_L)}{|\gamma_{12}\gamma_{21}| + \operatorname{Re}\{\gamma_{12}\gamma_{21}\}}$$

Optimum terminations for MAG:

$$g_{LO} = \frac{1}{2g_{11}} \sqrt{2g_{11}g_{22} - [\operatorname{Re}\{\gamma_{12}\gamma_{21}\}]^2 - |\gamma_{12}\gamma_{21}|^2}$$

$$g_{SO} = \frac{g_{11}}{g_{22}} g_{LO}$$

$$b_{LO} = -b_{22} + \frac{\operatorname{Im}\{\gamma_{12}\gamma_{21}\}}{2g_{11}}$$

$$g_{SO} = \frac{g_{11}}{g_{22}} g_{LO}$$

$$b_{SO} = -b_{11} + \frac{\operatorname{Im}\{\gamma_{12}\gamma_{21}\}}{2g_{22}}$$

Transducer gain (general case):

$$G_T = \frac{4G_S G_L |\gamma_{21}|^2}{|(\gamma_{11} + Y_S)(\gamma_{22} + Y_L) - \gamma_{12}\gamma_{21}|^2}$$

Maximum available gain (unilateralized and conjugate matched):

$$\text{MAG} = \frac{|\gamma_{21}|^2}{4g_{11}g_{22}}$$

