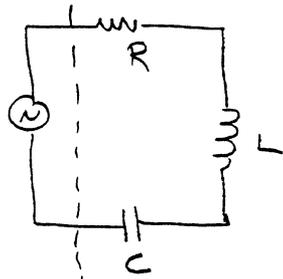


series RLC circuit




$$Z_{in}(j\omega) = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

at  $\omega_0$        $\omega_0 L - \frac{1}{\omega_0 C} = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

from an admittance viewpoint
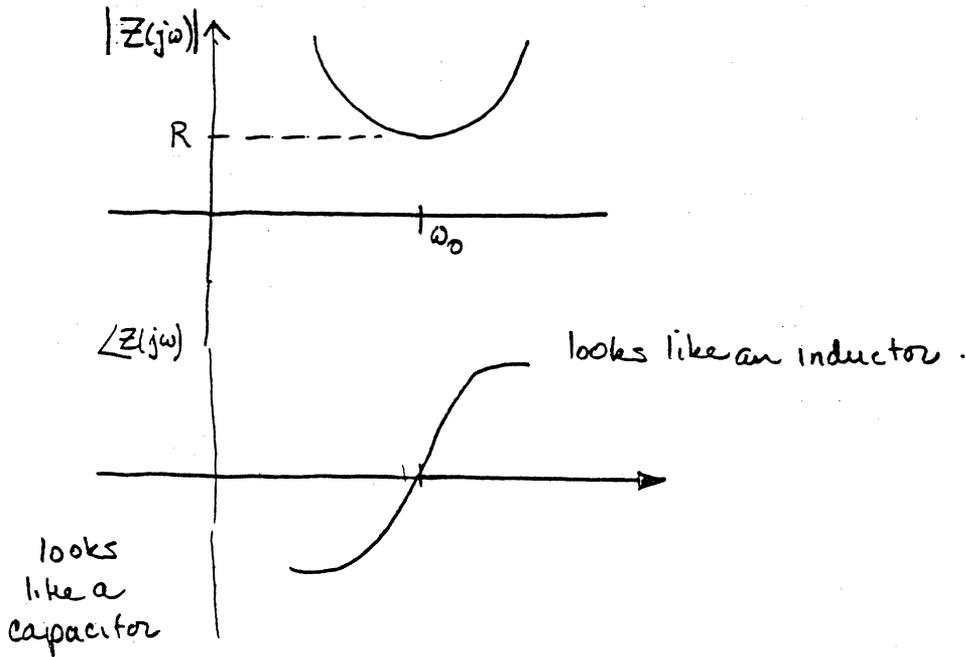
$$Y(j\omega) = G + jB = \frac{1}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \quad \text{multiply top \& bottom} = \frac{R - j\left(\omega L - \frac{1}{\omega C}\right)}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$



just like for filters (3db point) we define

$$Z = R + j(\pm R) \quad \text{i.e. } X = R$$

$$\text{at } |Z| = \sqrt{2} R$$

$$I = \frac{I_{\text{resonance}}}{\sqrt{2}} \quad \text{etc.}$$


in terms of power

at resonance  $P = I I^* R = |I_{\max}|^2 R = P_{\text{res}}$

at  $X = \pm R$   $P = \left| \frac{I_{\max}}{\sqrt{2}} \right|^2 R = \frac{P_{\text{res}}}{2}$

↖ there is a phase factor

-half power points

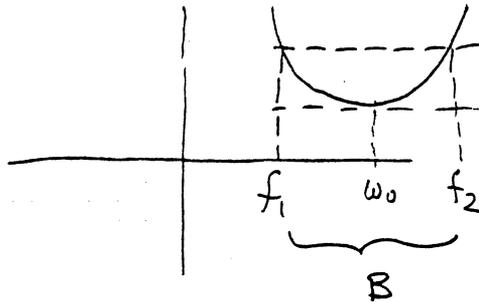

you can see immediately that  $B$  is an indicator of how narrow the resonance is.

We use  $Q = \frac{f_0}{B}$  to denote the

selectivity of the circuit

more generally  $Q = 2\pi \frac{\text{maximum instantaneous energy stored in the circuit}}{\text{energy dissipated per cycle}}$


for circuits with complex impedances

$$Q = \frac{\text{reactance (inductive)}}{\text{resistance}} = \frac{\omega_0 L}{R}$$

use inductive by convention  
we can also use  $C$  as we will see later

Proof that  $Q = \frac{f_0}{B}$  is found in class notes

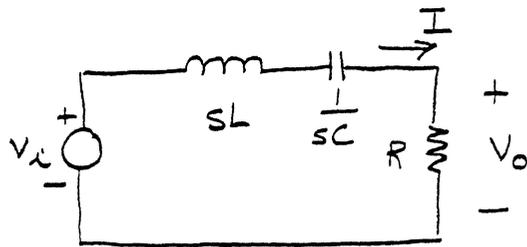transfer function of a series RLC circuit



$$I(s) = \frac{V_i(s)}{sL + \frac{1}{sC} + R} = \frac{V_i(s) \left(\frac{s}{L}\right)}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$


$$V_o(s) = I(s)R = \frac{V_i(s) s \frac{R}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{characteristic equation}$$

$$s_{1,2} = -\frac{R}{2L} \pm \frac{\sqrt{\left(\frac{R}{L}\right)^2 - 4/LC}}{2}$$

in most nf. networks  $\frac{4}{LC} > \frac{R^2}{L^2}$  or  $R^2 < \frac{4L}{C}$   
 (this is known as underdamping)

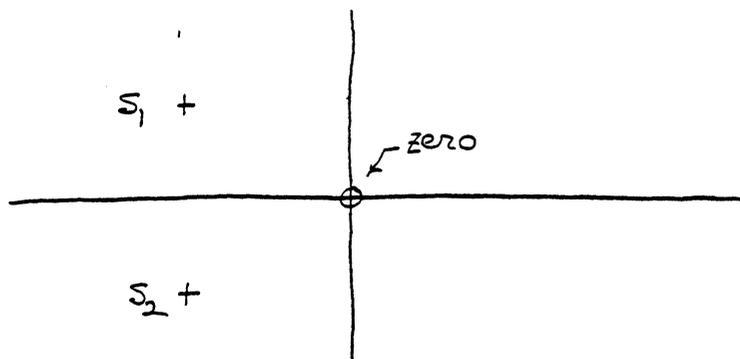so that  $s_{1,2}$  are a complex conjugate pair



Then  $V_o(s)$  can be written

$$V_o(s) = T(s) V_i(s) \quad \text{where } T(s) = \frac{RC s}{\frac{s^2}{\omega_0^2} + \frac{2\zeta}{\omega_0} s + 1}$$

$\uparrow$   
 transfer function 238

where  $\omega_0 = \frac{1}{\sqrt{LC}}$  undamped natural frequency


$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$  damping ratio

there is a reason for this. If  $V_i(s)$  is a unit step

The output is

$$V_o(t) = \frac{2\zeta}{\sqrt{1-\zeta^2}} e^{-\zeta\omega_0 t} \sin(\omega_0 \sqrt{1-\zeta^2} t) u(t)$$




damping
frequency of ringing

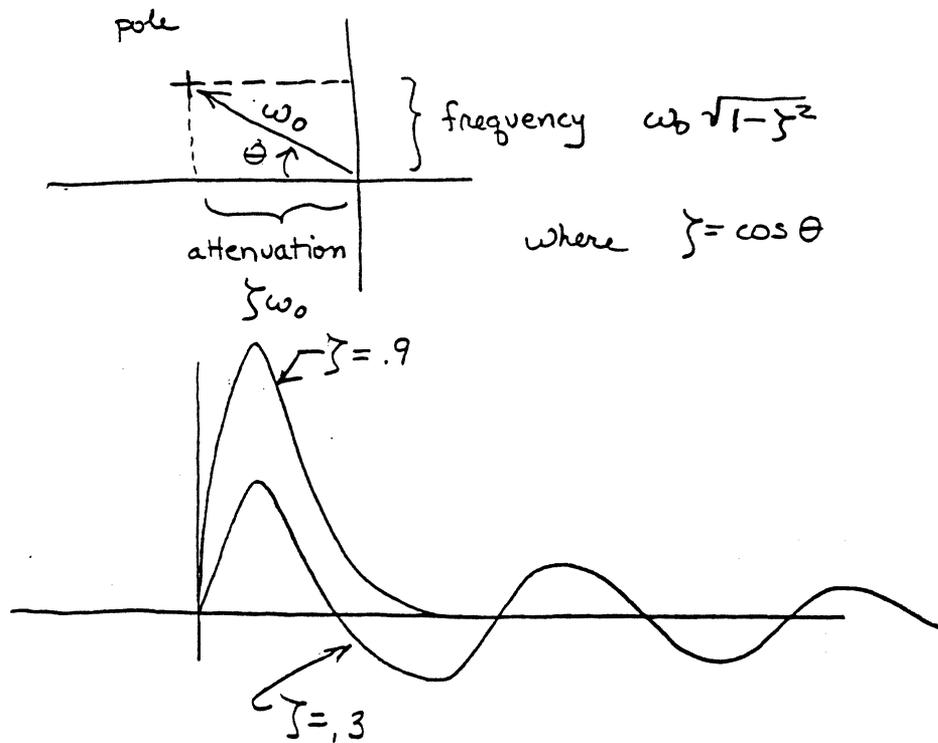

As  $\zeta$  increases the transient increases but decays faster.

For steady state let  $s = j\omega$
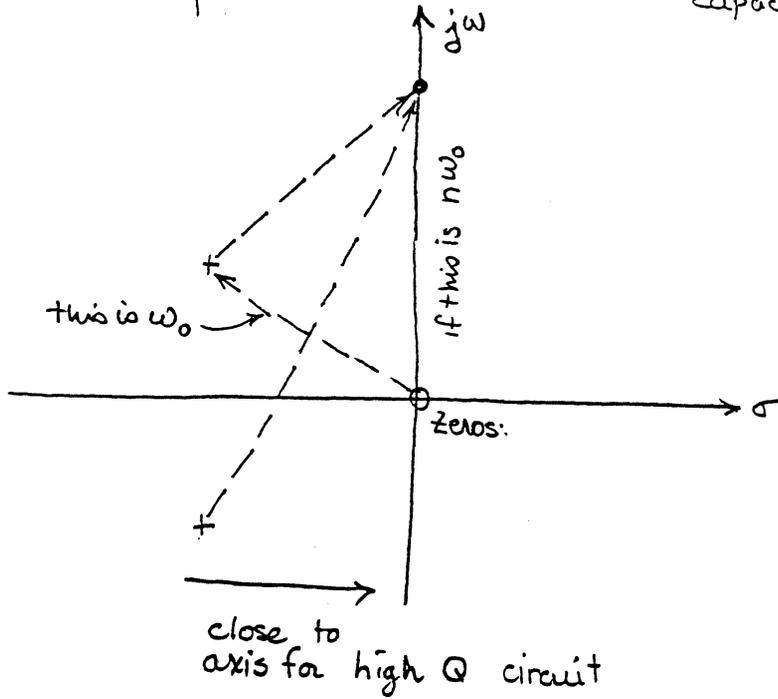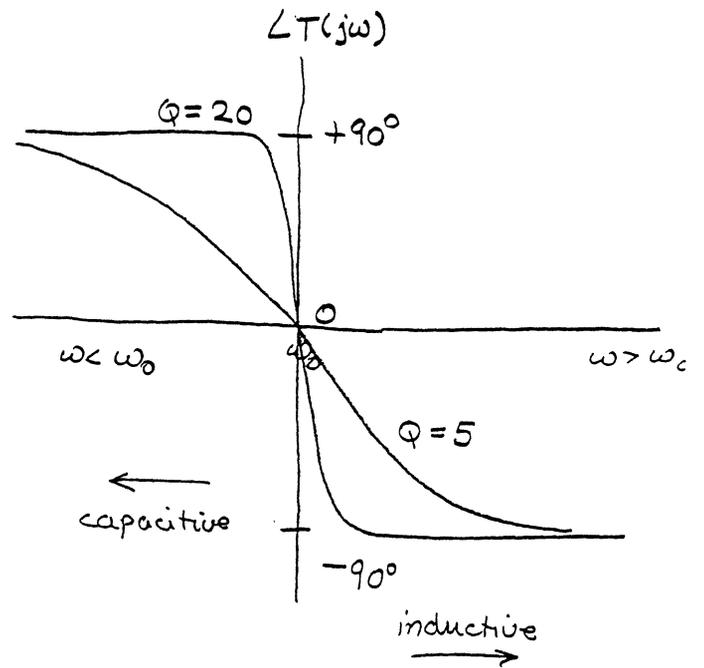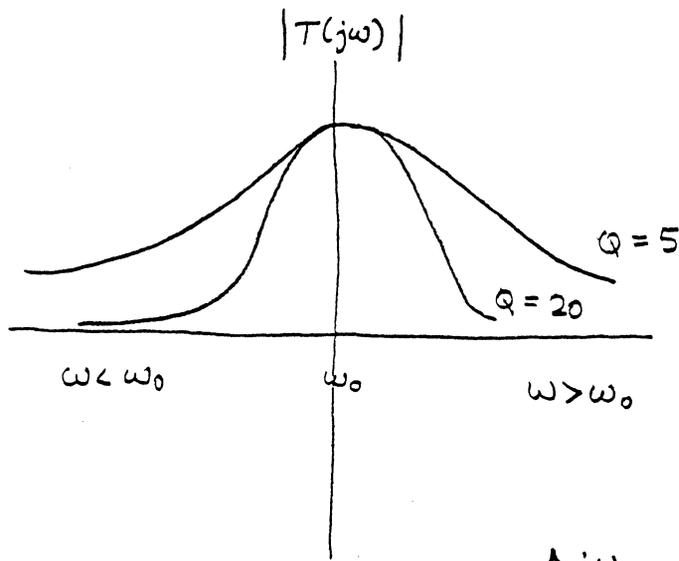
$$T(j\omega) = \frac{1}{1 + jQ \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$



poles close to axis  
so projections  
are essentially  
good estimates  
of their frequency.


without proof: 
$$\text{Gain}(\omega) = \frac{\prod (\omega - \omega_z)}{\prod (\omega - \omega_p)} B = \frac{n\omega_0}{(n-1)\omega_0 (n+1)\omega_0} B$$

$$= \frac{n}{n^2-1} \frac{1}{\omega_0} B = \frac{n}{n^2-1} \frac{1}{Q}$$

attenuation at harmonics

$$\frac{G(n\omega_0)}{G(\omega_0)} = \frac{n}{n^2-1} \frac{1}{Q}$$

parallel RLC circuit

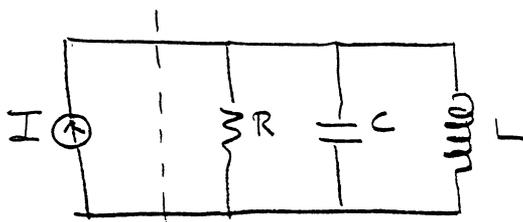


called a "tank" for historical reasons

$$Y(j\omega) = \frac{1}{R} + j\omega C + \frac{1}{j\omega L} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) = G + jB$$

||| G
||| B

at  $\omega_0$   $B=0$

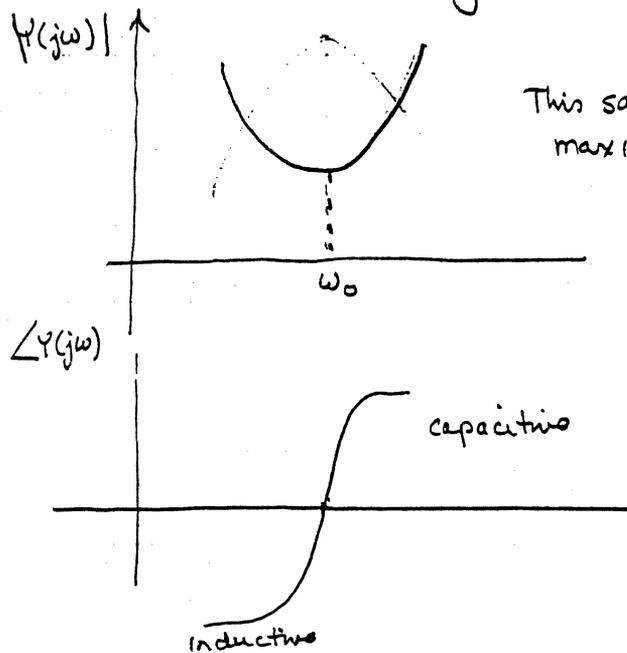this circuit behaves differently at resonance.



This says that impedance is a maximum at  $\omega_0$


As before  $Q = \frac{f_0}{B}$

However now define  $Q$  in terms of reactance (actually admittance)

$$Q = \frac{\omega_0 C}{G}$$

These give us a very useful result  $\frac{f_0}{B} = \frac{\omega_0 C}{G}$  or  $B = \frac{1}{2\pi RC}$

more complex circuit

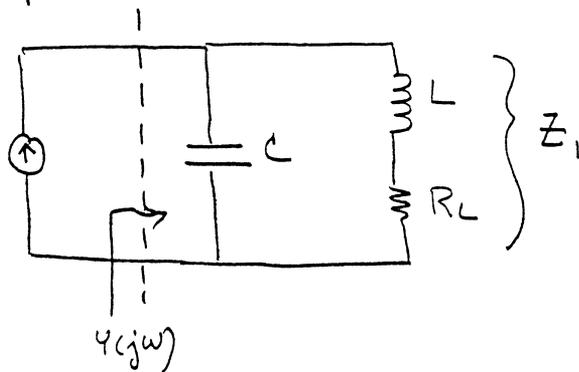

$$Z_1 = j\omega L + R_L$$

$$\frac{1}{Z_1} = \frac{1}{R_L + j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

by inspection  $Y(j\omega) = j\omega C + \frac{1}{Z_1} = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$

$$Y(j\omega) = \frac{R}{R^2 + \omega^2 L^2} + j \left( \omega C - \frac{\omega L}{R^2 + \omega^2 L^2} \right)$$

at resonance  $B \rightarrow 0 \quad \therefore \quad \omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$

$$R^2 + \omega_0^2 L^2 = \frac{\omega_0 L}{\omega_0 C} = \frac{L}{C}$$

$$\therefore \omega_0^2 = \frac{1}{L^2} \left( \frac{L}{C} - R^2 \right) = \frac{1}{LC} - \left( \frac{R}{L} \right)^2$$

$$\omega_0^- = \sqrt{\frac{1}{LC} - \left( \frac{R}{L} \right)^2}$$

resonance frequency is lowered by add resistance.

what we do here is note that

$$Y(j\omega_0) = \frac{R_L}{R_L^2 + (\omega_0 L)^2}$$

$$Z(j\omega_0) = \frac{R_L^2 + (\omega_0 L)^2}{R_L^2} = R_L \left[ 1 + \left( \frac{\omega_0 L}{R_L} \right)^2 \right]$$

this is NOT the Q of the circuit but looks like a Q. We call it  $Q_t$  for transformation Q

$$Z(j\omega_0) = R_t = R_L [1 + Q^2]$$

the resistance at resonance is apparently increased by the  $Q$  of the LR branch.

The bandwidth of this circuit is


$$B = f_2 - f_1 = \frac{1}{2\pi R_t C}$$

Powerful technique to handle unknown configurations

series  $\longleftrightarrow$  parallel conversions



$$Z = R_s + j\omega L_s$$

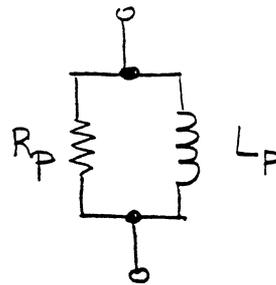

$$Z = j\omega L_p \parallel R_p$$

$$= \frac{j\omega L_p R_p}{R_p + j\omega L_p}$$

$$= \frac{j\omega L_p R_p (R_p - j\omega L_p)}{R_p^2 + \omega^2 L_p^2}$$

$$= \frac{(\omega L_p)^2 R_p + j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

equating real and imaginary parts:

$$R_s = \frac{(\omega L_p)^2 R_p}{R_p^2 + \omega^2 L_p^2}$$

$$j\omega L_s = \frac{j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

Now make some definitions

$$X_s = \omega L_s$$

$$Q_s = \frac{X_s}{R_s} = \frac{\omega L_s}{R_s}$$

$$X_p = \omega L_p$$

$$Q_p = \frac{R_p}{X_p} \left. \vphantom{Q_p} \right\} \begin{array}{l} \text{always inverted} \\ \text{for parallel} \\ \text{circuits} \end{array}$$

then 
$$R_s = \frac{R_p}{1 + Q_p^2}$$


$$R_p = R_s (1 + Q_s^2)$$

$$L_s = L_p \frac{Q_p^2}{Q_p^2 + 1}$$


$$L_p = L_s \left( \frac{Q_s^2 + 1}{Q_s^2} \right)$$

note:  $Q_s = Q_p$

if  $Q \gg 1$

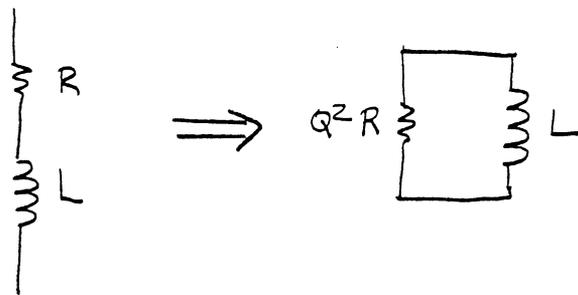


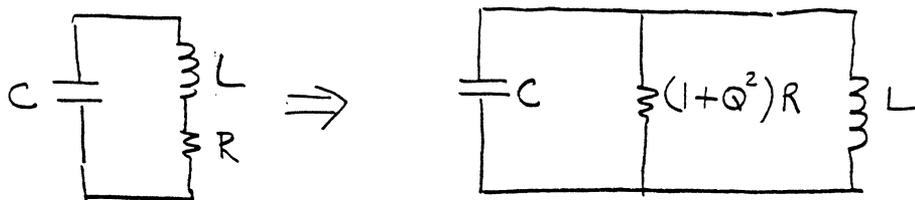Example: high  $Q$  "complicated" circuit



at resonance  $R_t = (1+Q^2)R$   
 $B = \frac{1}{2\pi R_t C}$

Similar results for capacitor circuits

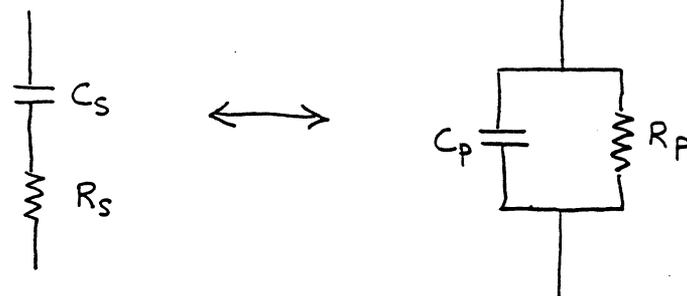

$$X_s = \frac{1}{\omega R_s}$$

$$Q_s = \frac{X_s}{R_s} = \frac{1}{\omega R_s C_s}$$

$$X_p = \frac{1}{\omega C_p}$$

$$Q_p = \frac{R_p}{X_p} = \frac{R_p}{\frac{1}{\omega C_p}} = \omega R_p C_p$$

$$R_s = \frac{R_p}{1+Q_p^2}$$

$$R_p = R_s (1+Q_s^2)$$

$$C_s = C_p \frac{Q_p^2 + 1}{Q_p^2}$$

$$C_p = C_s \frac{Q_s^2}{Q_s^2 + 1}$$


$$Z(j\omega_0) = R_t = R_L [1 + Q_t^2]$$

The resistance at resonance is increased by the "Q" of the L-R branch.

What is the bandwidth of this circuit

$$B = f_2 - f_1 = \frac{1}{2\pi R_t C}$$

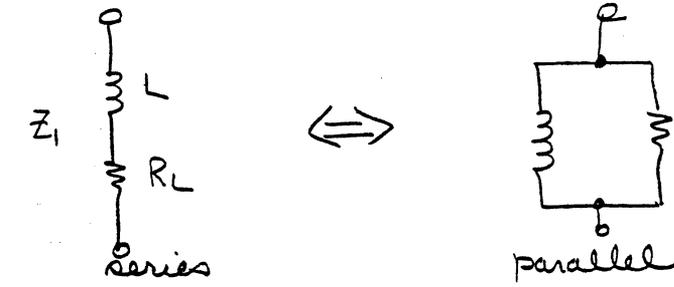Much more powerful general way to solve this circuit



$$Z = R_s + j\omega L_s$$

$$Z = j\omega L_p \parallel R_p = \frac{j\omega L_p R_p}{R_p + j\omega L_p}$$

$$= \frac{j\omega L_p R_p (R_p - j\omega L_p)}{R_p^2 + \omega^2 L_p^2}$$

$$= \frac{(\omega L_p)^2 R_p + j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

equate real & imaginary parts.

$$R_s = \frac{(\omega L_p)^2 R_p}{R_p^2 + \omega^2 L_p^2}$$

$$j\omega L_s = \frac{j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

make some definitions

$$X_s = \omega L_s$$



$$X_p = \omega L_p$$

$$Q_s = \frac{X_s}{R_s} = \frac{\omega L_s}{R_s}$$

$$Q_p = \frac{R_p}{X_p}$$

} always inverted for parallel circuit
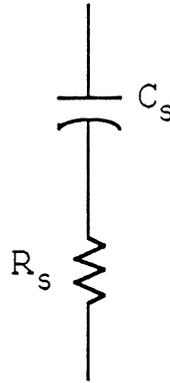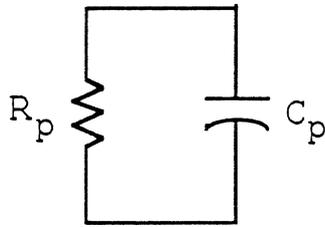
## PARALLEL-SERIES CONVERSION FOR RC NETWORKS



DEFINE	
$X_p = 1/(\omega C_p)$	$X_s = 1/(\omega C_s)$
$Q_p = R_p/X_p$	$Q_s = X_s/R_s = 1/(\omega R_s C_s)$

---

PARALLEL EQUIV OF SERIES      SERIES EQUIV OF PARALLEL

---

### EXACT FORMULA

$$R_{pe} = R_s(1 + Q_s^2)$$

$$R_{se} = R_p/(1 + Q_p^2)$$

$$X_{pe} = X_s(1 + Q_s^2)/Q_s^2$$

$$X_{se} = X_p Q_p^2/(1 + Q_p^2)$$

$$C_{pe} = C_s Q_s^2/(1 + Q_s^2)$$

$$C_{se} = C_p(Q_p^2 + 1)/Q_p^2$$

### APPROXIMATE FORMULA

---

if  $Q_s \geq 10$

if  $Q_p \geq 10$

---

$$R_{pe} \approx R_s Q_s^2$$

$$R_{se} \approx R_p/Q_p^2$$



$$X_{pe} \approx X_s$$

$$X_{se} \approx X_p$$

$$C_{pe} \approx C_s$$

$$C_{se} \approx C_p$$
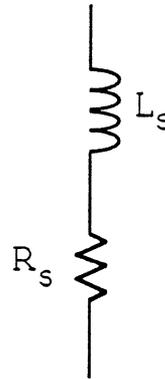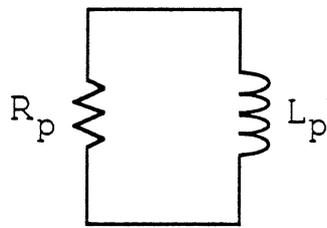
## PARALLEL-SERIES CONVERSION FOR RL NETWORKS



DEFINE	
$X_p = \omega L_p$	$X_s = \omega L_s$
$Q_p = R_p / X_p$	$Q_s = X_s / R_s = \omega L_s / R_s$

PARALLEL EQUIV OF SERIES	SERIES EQUIV OF PARALLEL
--------------------------	--------------------------

### EXACT FORMULA

$$R_{pe} = R_s (1 + Q_s^2)$$

$$R_{se} = R_p / (1 + Q_p^2)$$

$$X_{pe} = X_s (1 + Q_s^2) / Q_s^2$$

$$X_{se} = X_p Q_p^2 / (1 + Q_p^2)$$

$$L_{pe} = L_s (1 + Q_s^2) / Q_s^2$$

$$L_{se} = L_p Q_p^2 / (Q_p^2 + 1)$$

### APPROXIMATE FORMULA

$$\text{if } Q_s \geq 10$$

$$\text{if } Q_p \geq 10$$

$$R_{pe} \approx R_s Q_s^2$$

$$R_{se} \approx R_p / Q_p^2$$

$$X_{pe} \approx X_s$$

$$X_{se} \approx X_p$$


$$L_{pe} \approx L_s$$

$$L_{se} \approx L_p$$

## IMPEDANCE MATCHING NETWORKS


Note that each set of analysis/design formulas has two columns labeled "Exact" and "Approximate". The approximate column is valid when the  $Q_t$  of the network is  $\geq 10$  (the are about 10% accurate when  $3 \leq Q_t \leq 10$ ). This type of network is known as a L network because the basic output element looks like a letter "L" turned on its side. Note that because these networks only have two resonant elements you cannot simultaneously design for a specific bandwidth, resonant frequency and impedance transformation ratio; you can only do that by adding reactive components to the network.

### DESIGN FORMULAS FOR RC "L" NETWORK

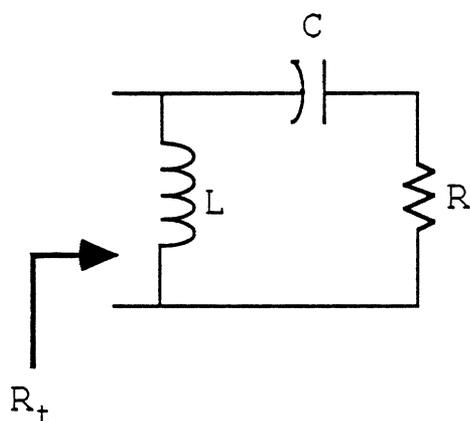

Quantity	Exact	Approximate
$\omega_0$	$= \sqrt{\frac{1}{LC - R^2C^2}}$	$\approx \frac{1}{\sqrt{LC}}$
$Q_t$	$= \frac{1}{\omega_0 CR} = \frac{R_t}{\omega_0 L}$	$\approx \frac{\omega_0 L}{R}$
$\omega_0 L$	$= \frac{1}{\omega_0 C} \frac{Q_t^2 + 1}{Q_t^2}$	$\approx \frac{1}{\omega_0 C}$
$R_t$	$= \frac{L}{CR} = \frac{Q_t}{\omega_0 C} = R(Q_t^2 + 1)$	$\approx Q_t^2 R = \omega_0 L Q_t$
B		$\approx \frac{1}{2\pi CR_t} = \frac{R}{2\pi L} = \frac{f_0}{Q_t}$

DESIGN FORMULAS FOR RL "L" NETWORK:

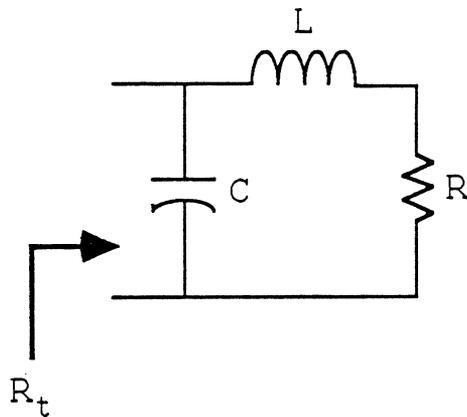

Quantity	Exact	Approximate
$\omega_o$	$= \sqrt{\frac{1}{LC} - \left(\frac{R}{L}\right)^2}$	$\approx \frac{1}{\sqrt{LC}}$
$Q_t$	$= \frac{\omega_o L}{R} = \omega_o C R_t$	$\approx \frac{1}{\omega_o C R}$
$\omega_o L$	$= \frac{1}{\omega_o C} \frac{Q_t^2}{Q_t^2 + 1}$	$\approx \frac{1}{\omega_o C}$
$R_t$	$= \frac{L}{RC} = \frac{Q_t}{\omega_o C} = R (Q_t^2 + 1)$	$\approx Q_t^2 R = \omega_o L Q_t$
B		$\approx \frac{f_o}{Q_t} = \frac{R}{2\pi L} = \frac{1}{2\pi C R_t}$

## DESIGN FORMULAS FOR TAPPED-CAPACITOR MATCHING NETWORK

For  $Q_t \approx \frac{f_o}{B} \geq 10$ ,


$$(1) C \approx \frac{1}{2\pi B R_t}$$

$$(2) L \approx \frac{1}{\omega^2 C}$$

$$(3) Q_t \approx \frac{f_o}{B}$$

$$(4) N = \sqrt{\frac{R_t}{R_2}}$$

$$(5) \frac{Q_t}{N} \approx Q_p$$

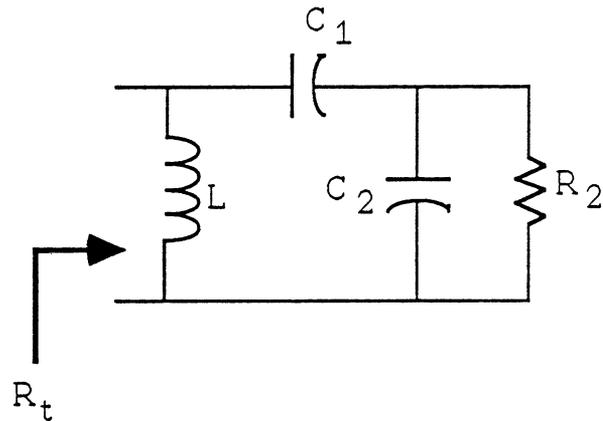

Formulas for  $Q_p \geq 10$

$$(6) Q_p = \frac{Q_t}{N}$$

$$(7) C_2 = N C$$

$$(8) C_1 = \frac{C_2}{N - 1}$$

$Q_p < 10$

$$(6) Q_p = \sqrt{\frac{Q_t^2 + 1}{N^2} - 1}$$

$$(7) C_2 = \frac{Q_p}{\omega_o R_2}$$

$$(8) C_{se} = C_2 \frac{Q_p^2 + 1}{Q_p^2}$$

$$(9) C_1 = \frac{C_{se} C}{C_{se} - C}$$

## DESIGN FORMULAS FOR TAPPED-INDUCTOR MATCHING NETWORK

For  $Q_t \approx \frac{f_o}{B} \geq 10$ ,


$$(1) C \approx \frac{1}{2\pi BR_t}$$

$$(2) L \approx \frac{1}{\omega^2 C}$$

$$(3) Q_t \approx \frac{f_o}{B}$$

$$(4) N = \sqrt{\frac{R_t}{R_2}}$$

$$(5) \frac{Q_t}{N} \approx Q_p$$

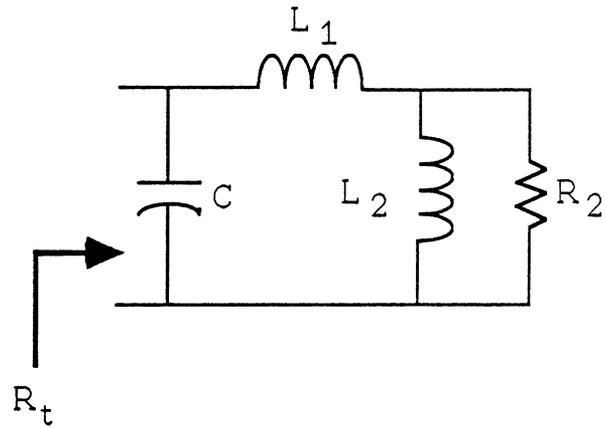

Formulas for  $Q_p \geq 10$

$$(6) Q_p = \frac{Q_t}{N}$$

$$(7) L_2 = \frac{L}{N}$$

$$(8) L_1 = (N - 1) L_2$$

$Q_p < 10$



$$(6) Q_p = \sqrt{\frac{Q_t^2 + 1}{N^2} - 1}$$

$$(7) L_2 = \frac{R_2}{\omega_o Q_p}$$

$$(8) L_{se} = L_2 \frac{Q_p^2}{Q_p^2 + 1}$$

$$(9) L_1 = L - L_{se}$$

Example:

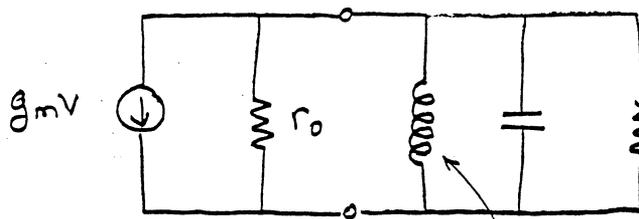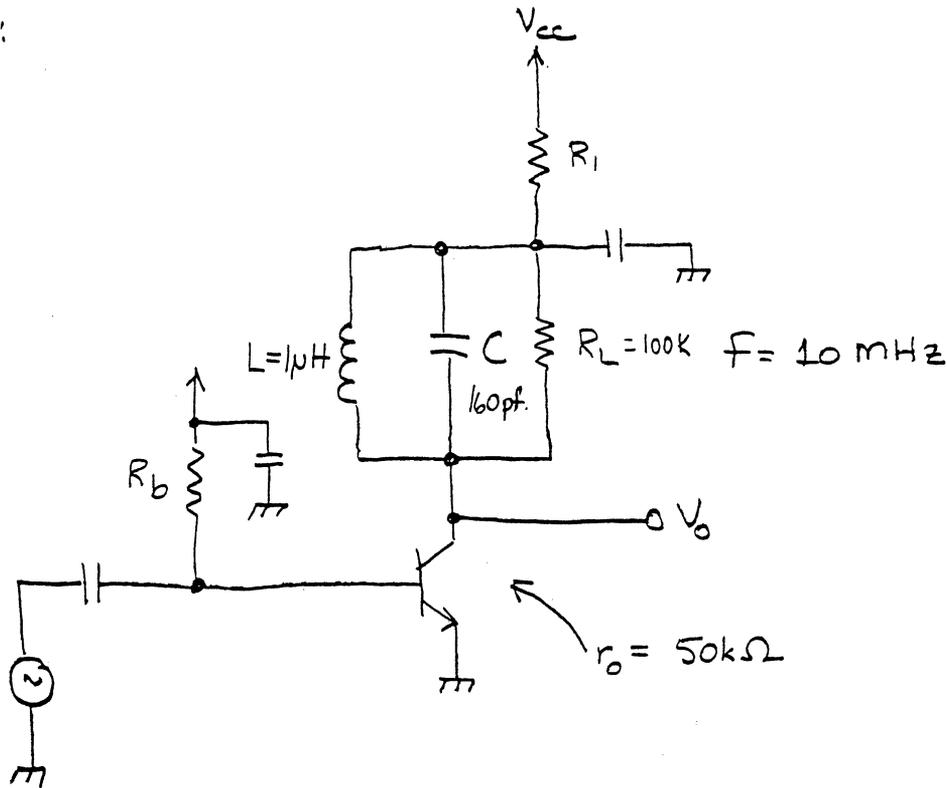

$$Q_p = \frac{R_p}{\omega_0 L} \rightarrow \frac{R_p}{\omega_0 \frac{1}{\omega_0^2 C}} = \omega_0 R_p C$$



$$\omega_0^2 = \frac{1}{LC}$$

parallel RLC circuit  $L=1\mu H, Q_p=100$

using the above result  $B = \frac{\omega_0}{Q} = \frac{\omega_0}{\omega_0 R_p C} = \frac{1}{R_p C}$

$$B = \frac{1}{(r_o \parallel R_L) C}$$

is this really correct

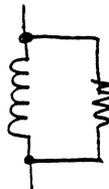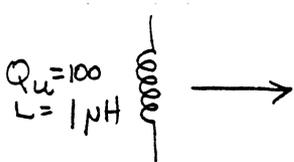

$$Q_u = \frac{R_p}{\omega_0 L}$$


so  $100 = \frac{R_p}{2\pi(10^7)(10^{-6})}$

$$\therefore R_p = 2\pi \cdot 1000 = 6280 \Omega$$

$$R_p \parallel r_o \parallel R_L = 6280 \parallel 50k \parallel 100k = 9.13k\Omega$$

$$B = \frac{1}{(9.13 \times 10^3)(160 \times 10^{-12})} = 0.865 \times 10^6 \text{ rad/sec.}$$


Example:

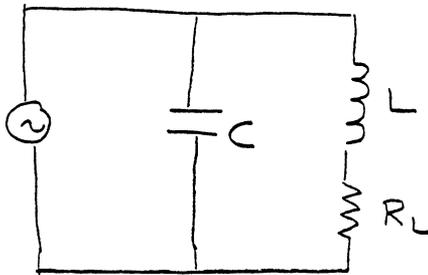

$$C = 1000 \text{ pf}$$


$$L = 10 \mu\text{H}$$

$$R_L = 50 \Omega$$

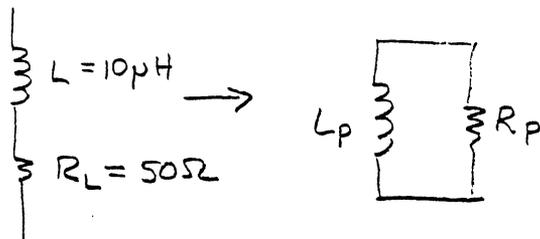

$$Q_s = \frac{\omega L_s}{R_s} \quad \text{what do we do since we don't know } \omega.$$

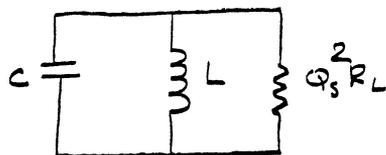Assume  $Q_s \geq 10$  then circuit looks like



$$\omega_0 \approx \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10 \times 10^{-6})(1000 \times 10^{-12})}}$$

$$10^7 \text{ Hz}$$


$$Q_p = \frac{R_p}{\omega L_p} = \frac{Q_s^2 R_s}{\omega L_p}$$

$$\text{but } Q_s = Q_p$$

$$Q_s = \frac{\omega L_p}{R_s} = \frac{(10^7)(10 \times 10^{-6})}{50} = 20$$


so approximation was valid

real circuit

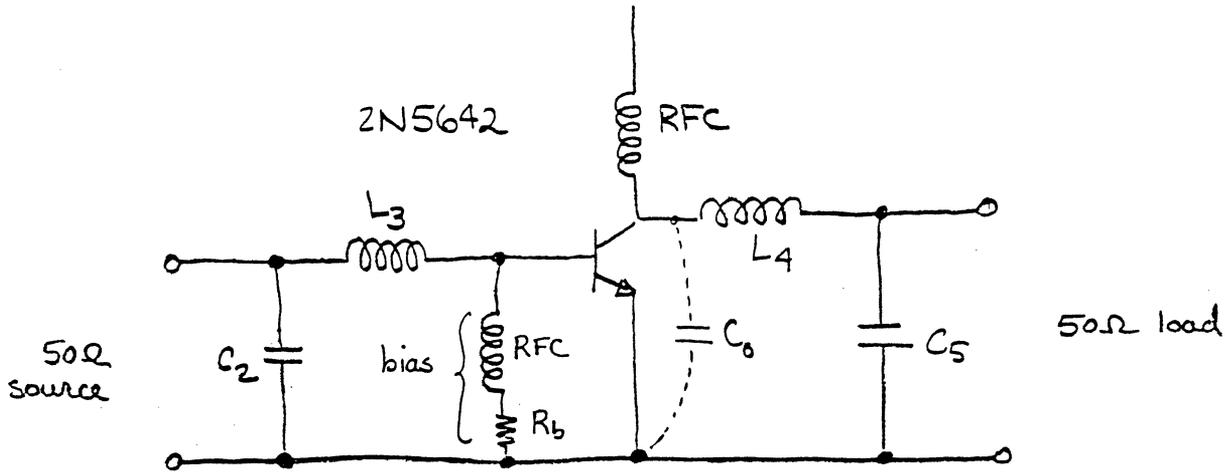

from data sheet for transistor  $Z_o @ 175\text{MHz} = 12.2 - j13.55$  (capacitive)  
 $Z_{in} @ 175\text{MHz} = 1.3 + j1.22$  (inductive)

look at input circuit

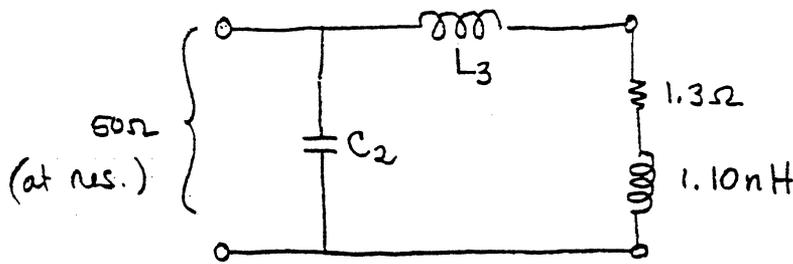


$$\omega L = 1.22\Omega$$

$$2\pi(175 \times 10^6) L = 1.22$$

$$L = 1.10 \times 10^{-9} \text{ H}$$

$$Q = \frac{\omega L}{R} = \frac{1.22}{1.3} = 0.93$$

low Q

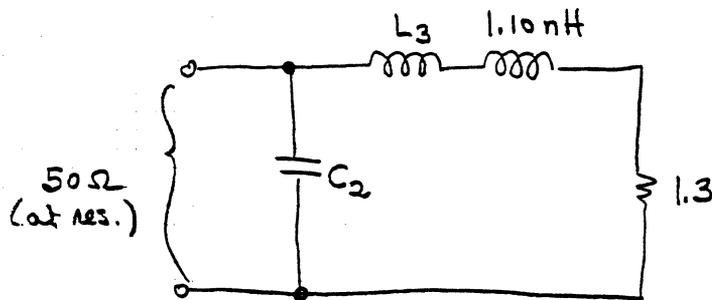

this is resonant RL||C  
 [for  $Q_t \geq 10$  use approximate formula]

① find  $Q_t$

$$R_t = R(Q_t^2 + 1)$$

$$50 = 1.3(Q_t^2 + 1)$$

$$Q_t^2 = \frac{50}{1.3} - 1 = 37.46$$

$$Q_t \approx 6.12$$

$\therefore$  use exact formula

② using  $Q_t$  find  $C$



$$Q_t = \omega_0 C R_t$$

$$6.12 = 2\pi (175 \times 10^6) C (50)$$

$$C = 111.3 \times 10^{-12} = 111.3 \text{ pf.}$$

③ solve for  $L$

$$Q_t = \frac{\omega_0 L}{R}$$



$$6.12 = \frac{2\pi (175 \times 10^6) L}{1.3}$$

$$L = 7.24 \times 10^{-9} = 7.24 \text{ nH}$$

$$\therefore \text{use } L_3 = 7.24 - 1.10 \text{ nH} = 6.14 \text{ nH}$$

Output circuit

*this is incorrect*

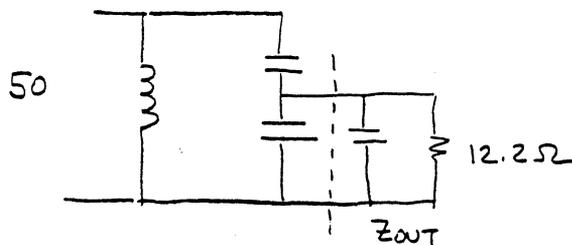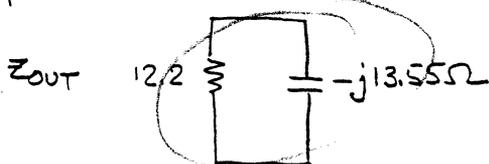

$$-j13.55 = \frac{1}{j2\pi(175 \times 10^6)C}$$

$$C = \frac{1}{2\pi(175 \times 10^6)(13.55)} = 67.1 \text{ pf}$$

Do by capacitive divider  $N = \sqrt{\frac{50}{12.2}} = 2.02$

check for max  $Q_p$   $Q_p = \omega_0 R_2 C_2 = 2\pi(175 \times 10^6)(12.2)(67.1 \times 10^{-9})$   
 $= 900$

$$Q_t \approx N Q_p$$

$\therefore$  pick  $Q_t = 10$  i.e. 17.5 MHz bandwidth.

$$Q_t = \frac{f_0}{B} \quad B = \frac{f_0}{Q} = 17.5 \text{ MHz}$$

$$C = \frac{1}{2\pi R_t B} = \frac{1}{2\pi(50)(17.5 \times 10^6)} = 181.9 \text{ pf.}$$

*181.9 pf*

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi \cdot 175 \times 10^6)^2 (181.9 \times 10^{-9})} = \frac{1}{1.209 \times 10^{18}} = 4.54 \times 10^{-9} \text{ Henrys}$$

$$Q_p \approx \frac{Q_t}{N} = \frac{16}{2.02} = 4.95$$

$$C_2 \approx NC = 49.5 \text{ pf} \quad \text{but } C \text{ of transistor} = 67.1 \text{ pf}$$

how can we make work.

- ① change  $Q_t$
- ② use inductor to cancel out part of  $C_{out}$ .

work backwards. pick  $C_2 = 100 \text{ pf}$   
 $N = 2.02$



$$\therefore C = \frac{C_2}{N} = \frac{100}{2.02} = 49.5 \text{ pf}$$

$$C_1 = \frac{C_2}{N-1} = \frac{49.5 \text{ pf}}{2.02-1} = 48.5 \text{ pf}$$

$$B = \frac{1}{2\pi R_t C} = \frac{1}{2\pi (50)(49.5 \times 10^{-12})} = 64.31 \text{ MHz}$$

$$\therefore \text{restricted to } Q_t = \frac{175}{64.31} = 2.7$$

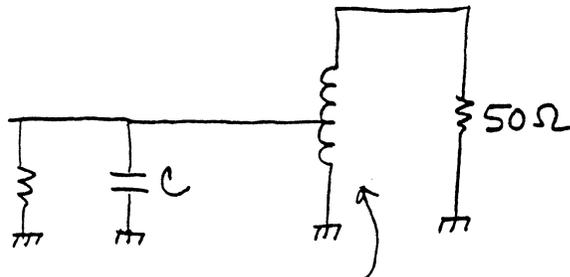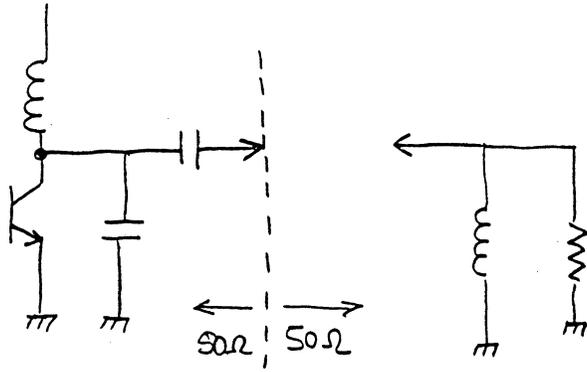Use a more sophisticated design to get a more realistic value of L.




since L goes as turns ratio.

need at least 10:1 to get reasonable value of R

$$10 \times 0.0167 = 0.167 \mu\text{H} \leftarrow L \text{ goes as } n.$$


$$\text{impedance steps down to } \frac{50}{n^2} = \frac{50}{100} = 0.5$$

put in standard form:

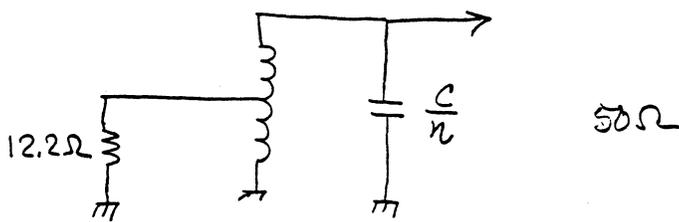

Now use either a tapped inductor or an autotransformer.

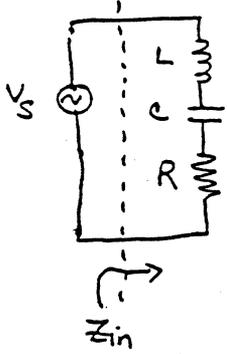What is the voltage across the capacitor (at resonance) in the series R-L-C circuit shown below.




At resonance  $Z_{in}$  is purely resistive, i.e.  $Z_{in}(\omega_0) = R$ .


$$\Rightarrow I_{\text{resonance}} = I_{\text{resistor}} = \frac{V_s}{R}$$

$$V_{\text{capacitor}} = (I_{\text{resistor}}) Z_{\text{capacitor}} = \frac{V_s}{R} \left( -j \frac{1}{\omega C} \right) = -j \frac{V_s}{\omega R C}$$

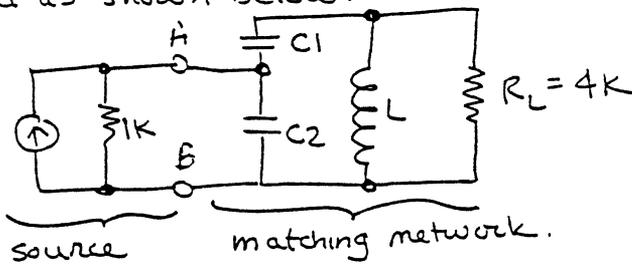A current source with an internal impedance of  $1000\ \Omega$  is used to drive a tapped capacitor impedance matching network terminated into a  $4000\ \Omega$  load as shown below.



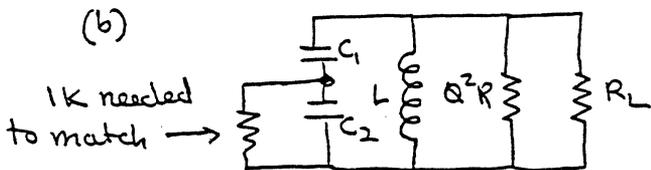- a) For maximum power transfer to the load at resonance what impedance should the network show between points A and B?
- b) Draw the impedance matching network including the resistance of the inductor.
- c) For  $\omega_0 = 10^6$ ,  $B = 10^5$  radians/sec,  $Q_L = 50$  find  $L, C_1$  and  $C_2$ . Is  $R$  negligible?
- (a) in simplest form the network must show  $1000\ \Omega$  there.



(c) Assume  $Q^2 R$  is negligible at first

$$C = \frac{1}{2\pi B R_t} = \frac{1}{10^5 (4 \times 10^3)} = 0.25 \times 10^{-8} = 2500\ \text{pf}$$

$$L = \frac{1}{\omega_0^2 C} = \frac{1}{(10^6)^2 (2.5 \times 10^{-8})} = 4 \times 10^{-4} = 400\ \mu\text{H}$$

$$R = \frac{\omega_0 L}{Q_L} = \frac{(10^6)(400 \times 10^{-6})}{50} = 8\ \Omega$$

$$Q_L^2 R = (50)^2 8\ \Omega = 20\ \text{k}\Omega$$

we can re-calculate this using  $R_t = 20\ \text{k}\Omega \parallel 4\ \text{k}\Omega = 3.33\ \text{k}\Omega$  error in these values is about  $\frac{.6}{4} = 15\%$ .

2nd iteration:

$$C' = \frac{1}{2\pi B R_t'} = \frac{1}{(2\pi B)(3.33 \times 10^3)} = \frac{1}{10^5 \cdot 3.33 \times 10^3} = 3003\ \text{pf}$$

$$L' = \frac{1}{\omega_0^2 C'} = \frac{1}{(10^6)^2 (3.0 \times 10^{-9})} = 333\ \mu\text{H}$$

$$R' = \frac{\omega_0 L'}{Q_L} = \frac{(10^6)(333 \times 10^{-6})}{50} = 6.66\ \Omega$$

$$Q_L^2 R = (50)^2 6.66 = 16.65\ \text{k}\Omega$$

$$R_t'' = 16.65\ \text{k}\Omega \parallel 4\ \text{k}\Omega = 3.23\ \text{k}\Omega$$

error is now about  $\frac{3.33 - 3.23}{3.23} \approx \frac{0.1}{3.23}$  or about 3%.