


TRANSMISSION LINES

- SKIN EFFECT, MOSTLY AN ISSUE AT RF
IMPACTS CURRENT CAPACITY OF LINE.

$$\delta = \frac{1}{\sqrt{\frac{\pi f \mu}{\rho}}}$$

$$\delta = 2.53 \times 10^5 \sqrt{\frac{\rho}{f}}$$

EFFECTIVE AREA:

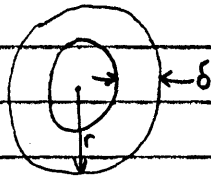

$$A_{eff} = \pi (r^2 - (r - \delta)^2)$$

- SEE FIGURE 6.1, P. 6-3 FOR HANDY GRAPH OF SKIN EFFECT. (R_0 IS D.C. RESISTANCE.)

- INDUCTANCE

INTERNAL - DUE TO CURRENT IN WIRE ACTING ON ITSELF

EXTERNAL - INTERACTION OF FIELDS FROM NEARBY WIRES

$$\text{INTERNAL: } L_i = \frac{\mu}{8\pi} \quad (\text{ALWAYS}) \quad \text{H/m}$$

$$\text{EXTERNAL: } L_e = \frac{\mu}{\pi} \ln\left(\frac{D}{r}\right) \quad \text{H/m}$$

$$\text{TOTAL } L = L_i + L_e \quad \text{H/m}$$

- CAPACITANCE

$$C = \frac{2\pi\epsilon}{\ln\left[\frac{(D-r_1)(D-r_2)}{r_1 r_2}\right]} \quad \text{F/m}$$

POWER TRANSMISSION LINES

- USE TABLES TO GET REQUIRED VALUES.

- CORRECTION FACTOR FOR SPACINGS OTHER THAN 1 FOOT:

$$K_L = 1 + \frac{\ln(D)}{\ln(GMR)}$$

$$K_C = 1 + \frac{\ln(D)}{\ln(\frac{1}{r})}$$

EXAMPLE

FIND X_L OF BLUEBIRD LINE, 10' SPACING.

FROM TABLE, $GMR = 0.0586$,

$$K_L = 1 + \frac{\ln(10)}{\ln(\frac{1}{0.0586})} = 1.81$$

$$X_L = 0.344 \times 1.81 = 0.623 \text{ } \Omega/\text{MILE}$$

↑
FROM
TABLE

THREE PHASE LINES

- USE GEOMETRIC MEAN SPACING

$$d_s = \sqrt[3]{r_{ab} r_{bc} r_{ac}}$$

TO ARRIVE AT SIMPLIFIED EQUATIONS.

$$L = (2 \times 10^7) \ln\left(\frac{d_s}{GMR}\right) \frac{H}{m}$$

$$M_{12} = (2 \times 10^7) \ln\left(\frac{r_1 r_2}{d_s^2}\right) \frac{H}{m}$$

AS LONG AS ALL
3 CONDUCTORS ARE IDENTICAL

PLUG & GO SIMPLE!


MODELING POWER TRANSMISSION LINES

- UNDER FAIRLY BALANCED COND, USE SINGLE LINE ANALYSIS
- MUST USE $\Delta \rightarrow Y$ TRANSFORMATION TO GET EQUIVALENT LINE TO NEUTRAL Z IN CASES OF Δ CONNECTED LOADS:

$$Z_{an} = \frac{Z_{ab} Z_{ac}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

SHORT LINES: (UNDER 50 mi), SHUNT ADMITTANCE NEGLECTABLE.
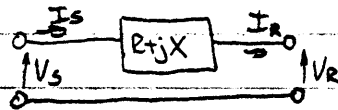
$$Z_L = \left[\frac{R}{\text{MILE}} + j \frac{X_L}{\text{MILE}} \right] \times \text{LENGTH}$$




$$\text{REGULATION} = \frac{|V_{R, \text{NL}}| - |V_{R, \text{FL}}|}{|V_{R, \text{FL}}|} \times 100$$

MEDIUM LINES: (50-150 mi)


- SHUNT COMPONENTS SIGNIFICANT, BUT CAN STILL MODEL WITH LUMPED CKT ELEMENTS:

T MODEL

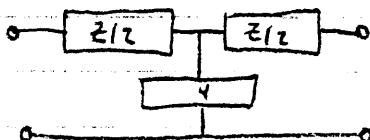

$$\begin{aligned} A &= 1 + \frac{YZ}{2} \\ B &= Z \left(1 + \frac{YZ}{4} \right) \\ C &= Y \\ D &= 1 + \frac{YZ}{2} \end{aligned}$$

PI MODEL

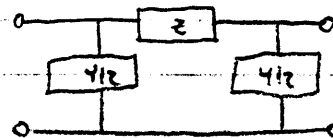

$$\begin{aligned} A &= 1 + \frac{YZ}{2} \\ B &= Z \\ C &= Y \left(1 + \frac{YZ}{4} \right) \\ D &= 1 + \frac{YZ}{2} \end{aligned}$$

REMEMBER THAT
$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

RELATION AS BEFORE.

LONG LINES:

MUST USE DISTRIBUTED CKT ELEMENTS,

Z : SERIES IMPEDANCE/LENGTH

Y : SHUNT ADMITTANCE/LENGTH.

$Z = R + jX_L$ TO GET PROP CONST $\gamma = \sqrt{YZ}$
 $Y = jB_C = \frac{j}{X_C}$ ATT CONST $\alpha = |\gamma| \cos \left[\frac{1}{2} \text{TAN}^{-1} \left(\frac{-R}{X_L} \right) \right]$

PHASE CONST $\beta = |\gamma| \sin \left[\frac{1}{2} \text{TAN}^{-1} \left(\frac{-R}{X_L} \right) \right]$

CHAR IMP $Z_0 = \sqrt{\frac{Z}{Y}}$

REF. COEFF. $\rho = \frac{Z_L - Z_0}{Z_L + Z_0}$ $Z_L = \text{LOAD } Z.$

MOST THINGS YOU NEED TO KNOW
ARE DETAILED IN TEXT EQUATIONS.

RF TRANSMISSION LINES.

AT RF, λ IS SO SHORT EVERY LINE IS A LONG LINE.

BUT $R \rightarrow 0$, SO WE MAY MAKE DRASTIC SIMPLIFICATIONS.

$$Z = j\omega L$$

$$Y = j\omega C$$

$$\gamma = j\omega\sqrt{LC} = j\beta$$


$$Z_0 = \sqrt{\frac{L}{C}}$$

STANDING WAVE RATIO


$$VSWR = \frac{1 + |\rho|}{1 - |\rho|}, \text{ INDICATES DEGREE OF MISMATCH ON LINE.}$$

YOU CAN USE EQUATIONS TO SOLVE TRANSMISSION LINE PROBLEMS, BUT SMITH CHART IS MUCH EASIER
 → CAN NOT OVEREMPHASIZE FACT THAT S.C. IS SIMPLER.

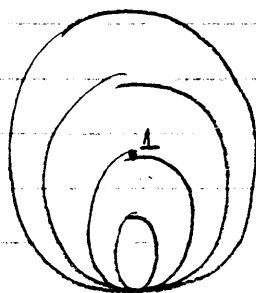SMITH CHART IS A GRAPH OF ALL THE COMPLEX IMPEDANCES (OR ADMITTANCES).



R.

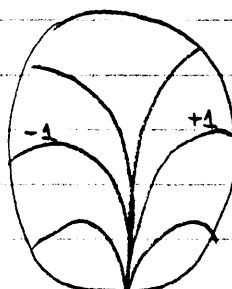


X

NORMALIZE IMPEDANCES TO BASE 1, SO THAT LINE IMPEDANCE IS AT CENTER OF CHART.

Appendix C

The Smith Chart

EXAMPLE #1.

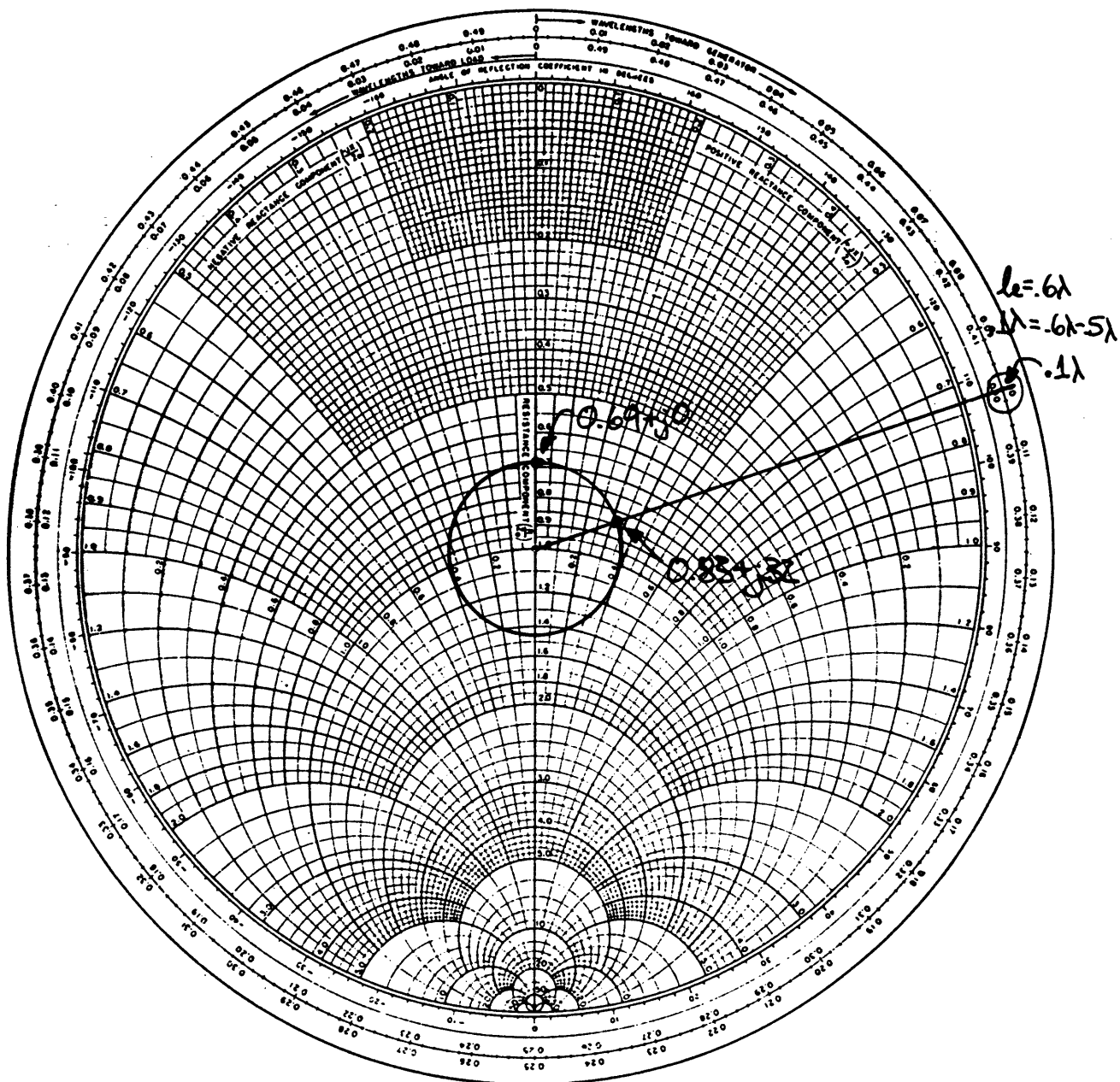

OPEN & SHORTED LINES

NOTE LOCATION OF OPEN CKT: BOTTOM OF CHART

SHORT CKT: TOP OF CHART.

WE CAN USE OPEN & SHORTED LINES TO GENERATE REACTANCES & SUSCEPTANCES WE NEED FOR MATCHING.

EXAMPLE

WE NEEDED SERIES COMPENSATOR $X_c = -160 \Omega$
IN LAST EXAMPLE. REMEMBER, $Z_0 = 100 \Omega$, SO $x_c = -1.6 \Omega$

PLOT $x_c = -1.6 \Omega$, READ VALUES

IF $Z_0 = 250 \Omega$, $x_c = \frac{-160}{250} = -0.64 \Omega$, READ VALUES.

EXAMPLE

WE NEEDED SHUNT COMPENSATOR $B_c = 0.016 S$.

$Y_0 = 0.01 S$

PLOT $B_c = 16 S$, READ THE LENGTHS.

IF $Z_0 = 250 \Omega$, $Y_0 = 0.004 S$,

$B_c = \frac{B_c}{Y_0} = \frac{0.016}{0.004} = 4 S$, READ VALUES.

#1

EX: TRANSMISSION LINE $Z_0 = 72 \Omega$, $\beta = .5 \frac{\text{RAD}}{\text{m}}$, $l = 7.5 \text{ m}$
 TERMINATED IN $Z_L = 50 \Omega$. SOURCE $Z?$

$$z_L = \frac{Z_L}{Z_0} = \frac{50}{72} = .69$$

PLOT THAT POINT.

DRAW CIRCLE OF CONSTANT $|p|$

$$\begin{aligned} \text{ELECTRICAL LENGTH} &= \frac{\beta}{2\pi} l \\ &= \frac{.5}{2\pi} 7.5 = .6\lambda \end{aligned}$$

START FROM LOAD, GO $.6\lambda$ TOWARD GENERATOR.
 POINT LANDS AT $z_i = 0.83 + j0.32$

$$\text{SO } Z_i = z_i Z_0 = 60 + j23 \Omega.$$

ANOTHER EXAMPLE (#2)

$$Z_0 = 100 \Omega \text{ FEEDING } Z_L = 25 + j25 \Omega.$$

FIND LUMPED MATCHING ELEMENTS FOR SERIES SHUNT.

$$\text{SERIES: } Z_L = 25 + j25 \text{ @ } .041\lambda$$

$$\text{SPOT IS } .179\lambda, z = 1 + j1.62$$

$$.179 - .041 = .138\lambda \text{ IS LOCATION FOR } X_c = 160 \Omega$$

$$\text{SHUNT: } y_0 = \frac{1}{Z_0} = .01 \text{ S}$$

$$\text{LOCATE } y_L \text{ ON CHART. } y_L = 2 - j2 \text{ @ } .0291\lambda$$


$$\text{SPOT IS } 0.322\lambda, y = 1 - j1.6 \text{ S}$$

$$0.322 - 0.291 = 0.031\lambda \text{ IS LOCATION FOR } B_c = 0.016 \text{ S.}$$

Appendix C

The Smith Chart

EXAMPLE #2: SERIES

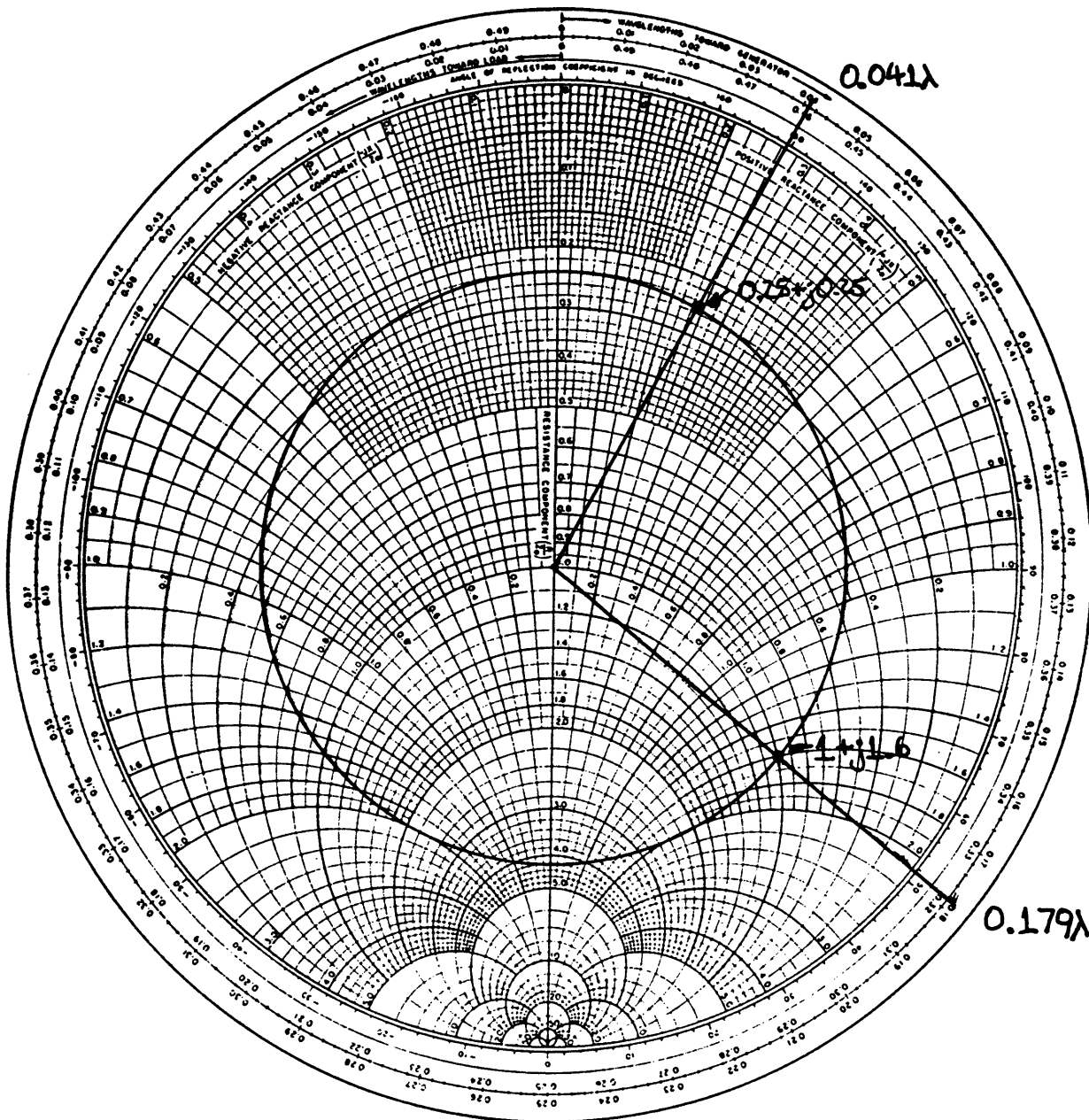


$0.179\lambda - 0.041\lambda = 0.138\lambda$ IS LOCATION FOR X_{comp} .
 $X_{comp} = -1.6\Omega$, so $X_c = Z_0 X_{comp} = -160\Omega$, CAPACITIVE.

Appendix C

The Smith Chart

EXAMPLE #2: SHUNT

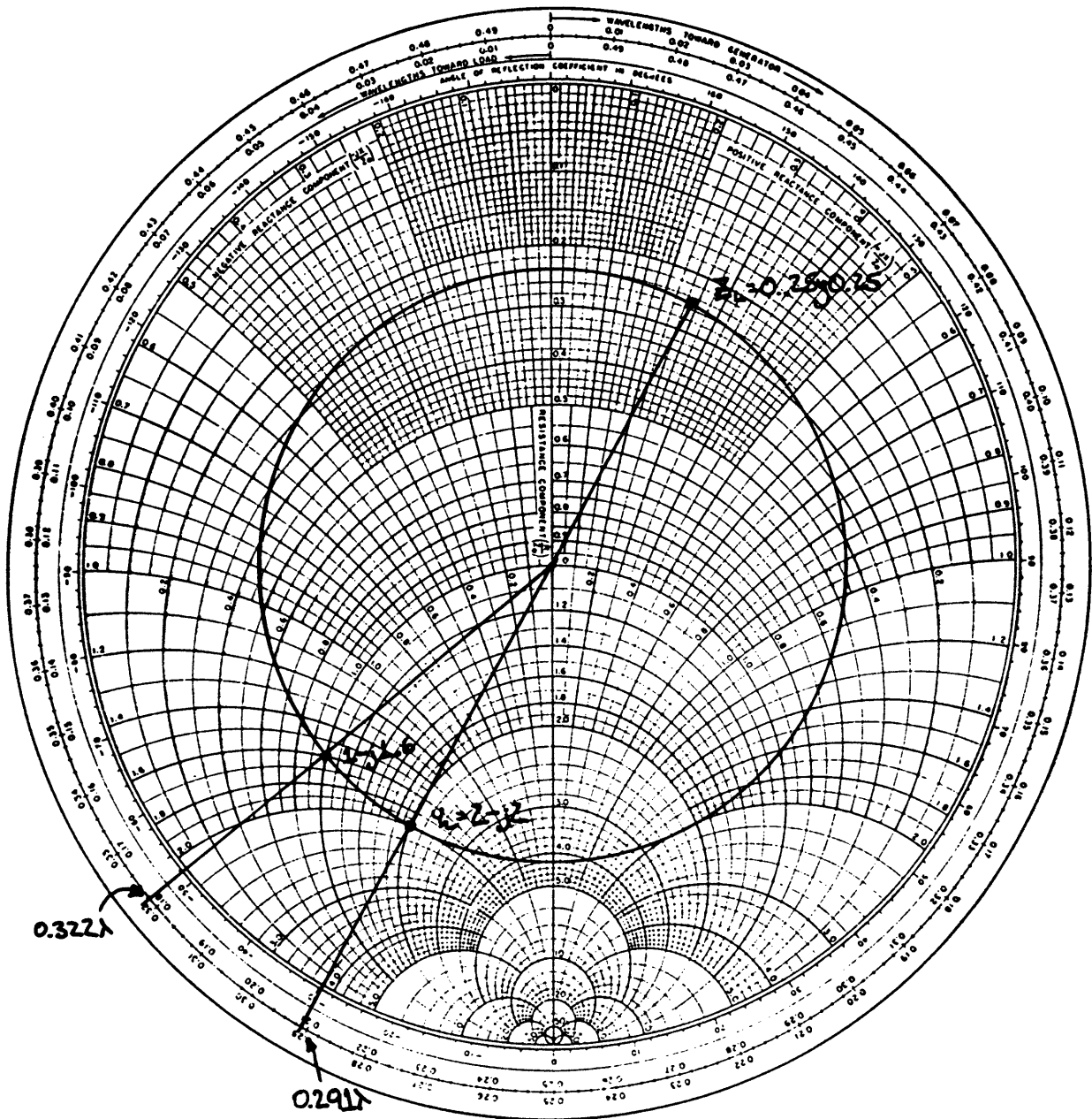


$0.322\lambda - 0.291\lambda = 0.031\lambda$ IS LOCATION FOR B_{comp} .

$B_{\text{comp}} = 1.6$, so $B_c = Y_0 B_{\text{comp}} = .016S$, CAPACITIVE.

Appendix C

The Smith Chart

EXAMPLE #3: SERIES

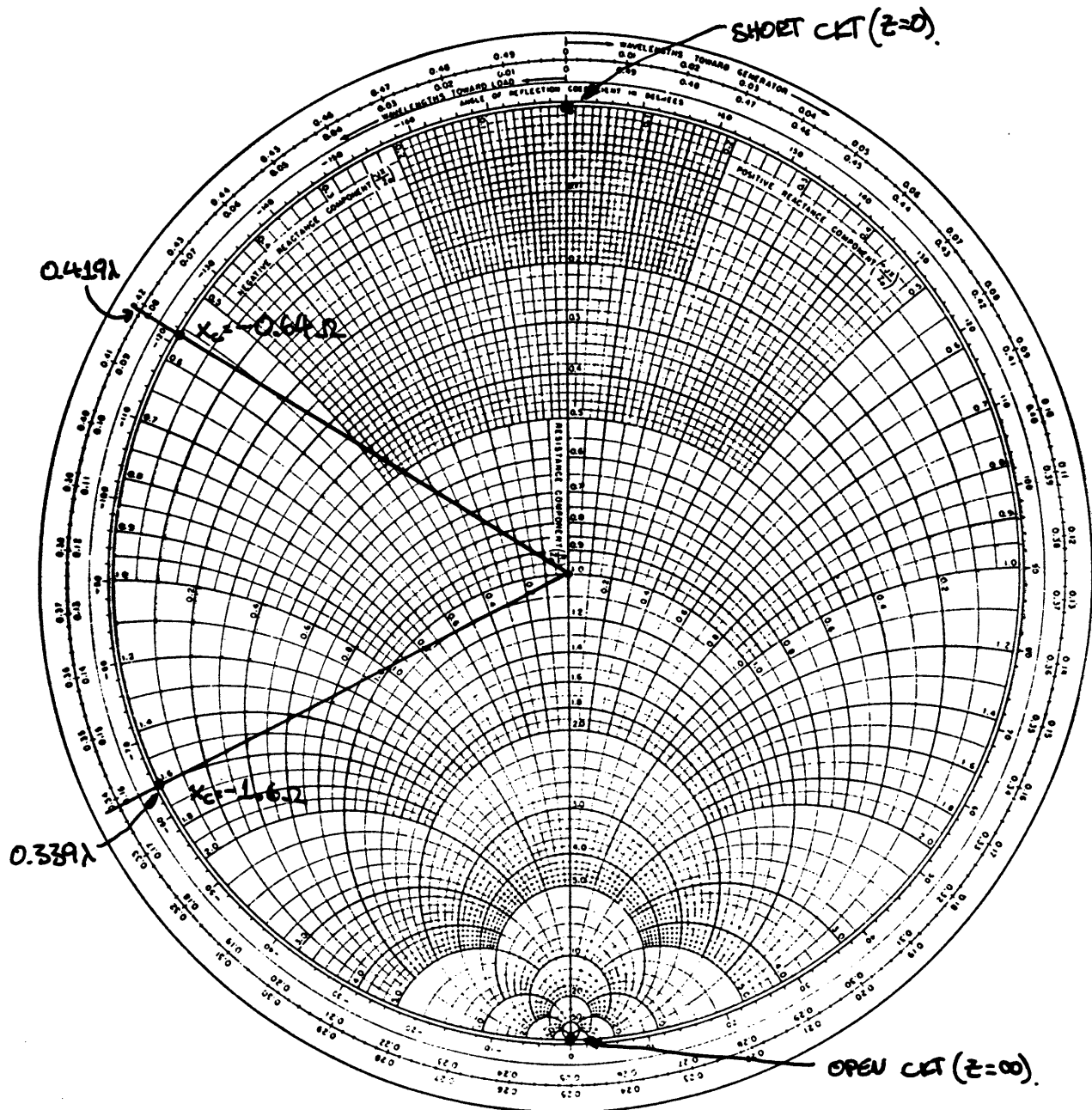

SHORTED LINE: $l = 0.339\lambda$

OPEN LINE: $l = 0.339\lambda - 0.25\lambda = 0.089\lambda$

SHORTED LINE: $l = 0.419\lambda$

OPEN LINE: $l = 0.419\lambda - 0.25\lambda = 0.169\lambda$


$Z_0 = 100\Omega$

$Z_0 = 250\Omega$

Appendix C

The Smith Chart

EXAMPLE #3: SHUNT

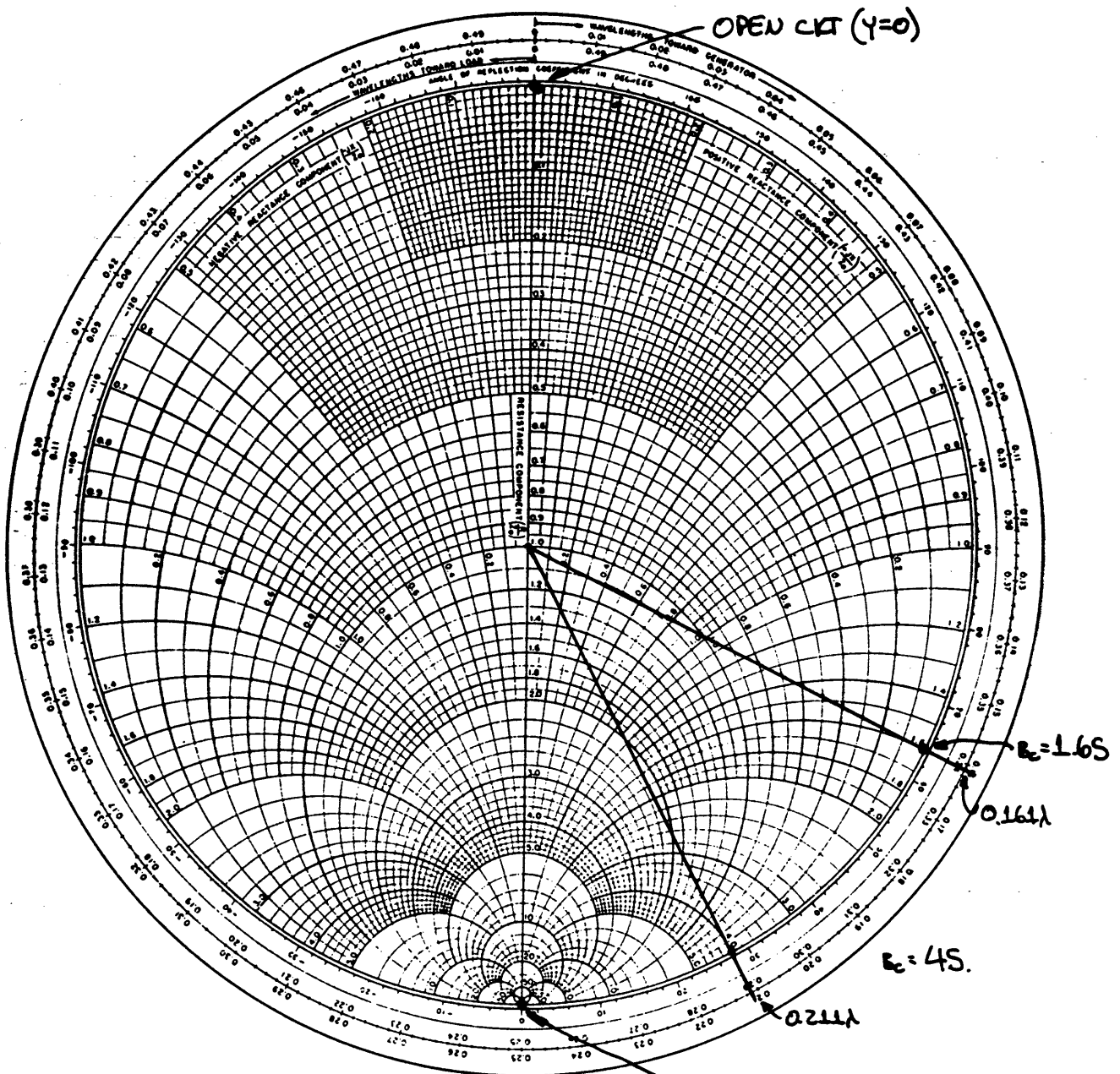


OPEN LINE: $l = 0.161\lambda$
 SHORTED LINE: $l = 0.161\lambda + 0.25\lambda = 0.411\lambda$
 OPEN LINE: $l = 0.211\lambda$
 SHORTED LINE: $l = 0.211\lambda + 0.25\lambda = 0.461\lambda$

$Y_0 = 0.015$
 $Y_0 = 0.004S$ ($Z_0 = 250\Omega$)


Appendix C

The Smith Chart

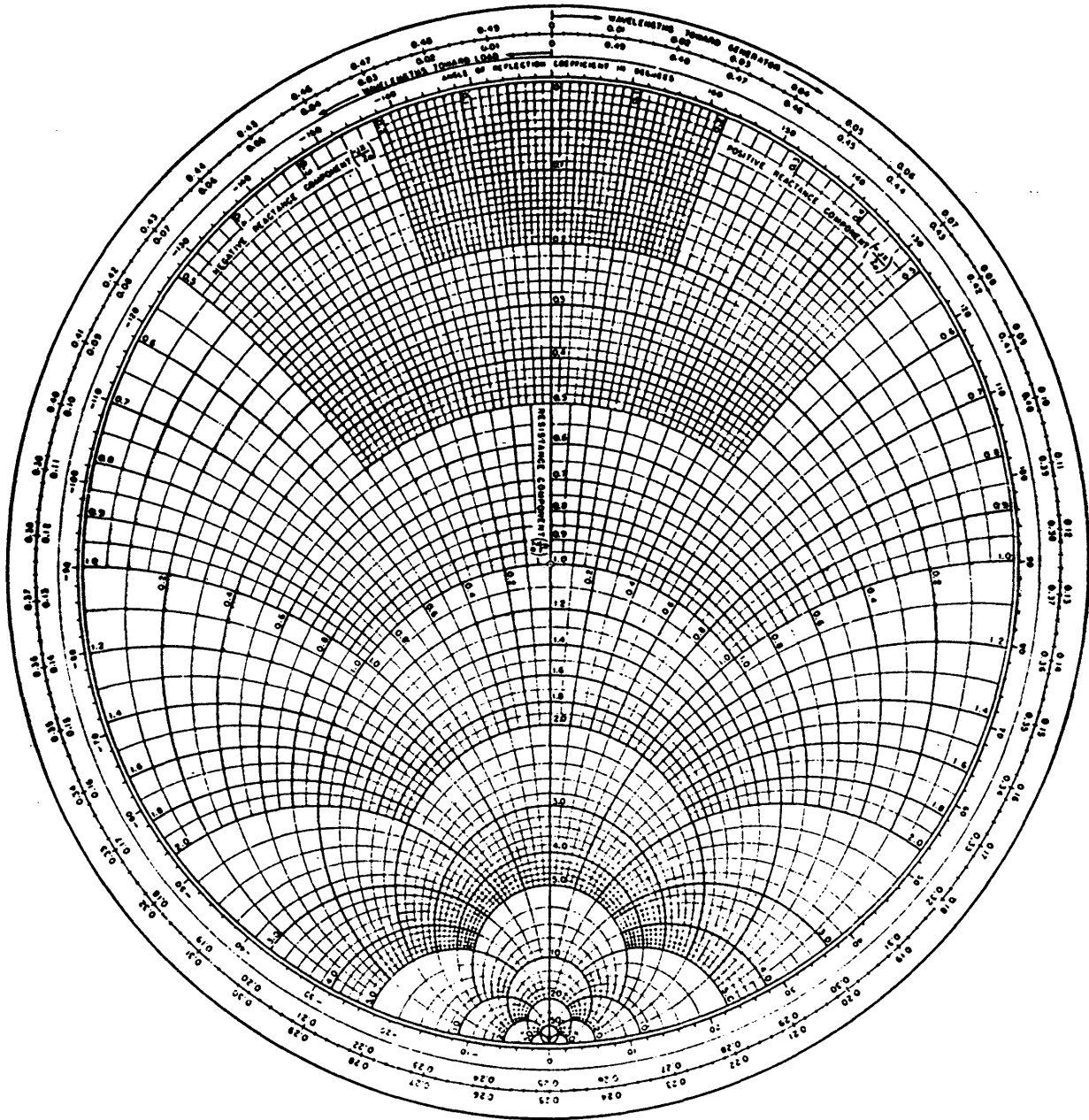

Appendix C

The Smith Chart

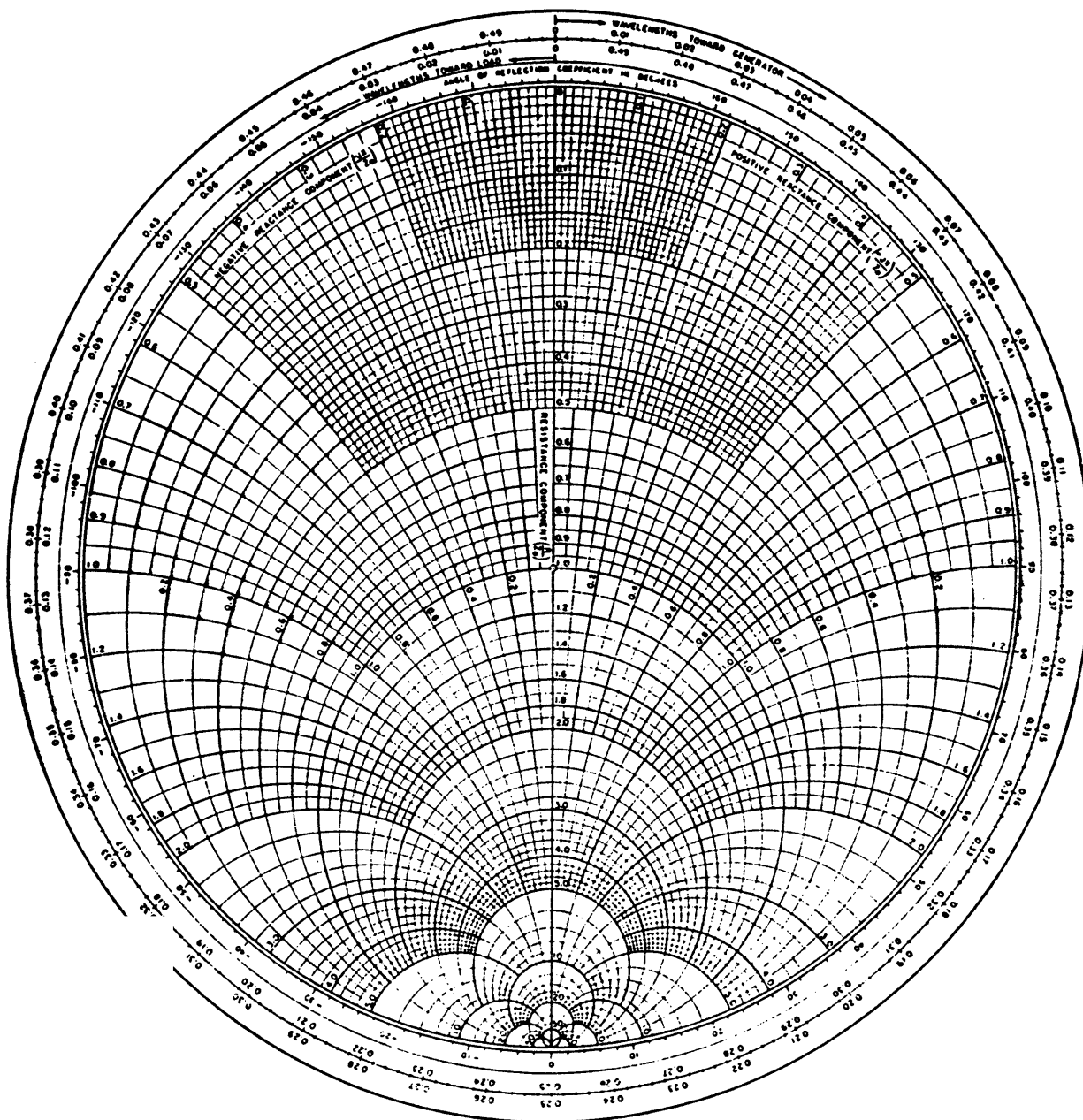

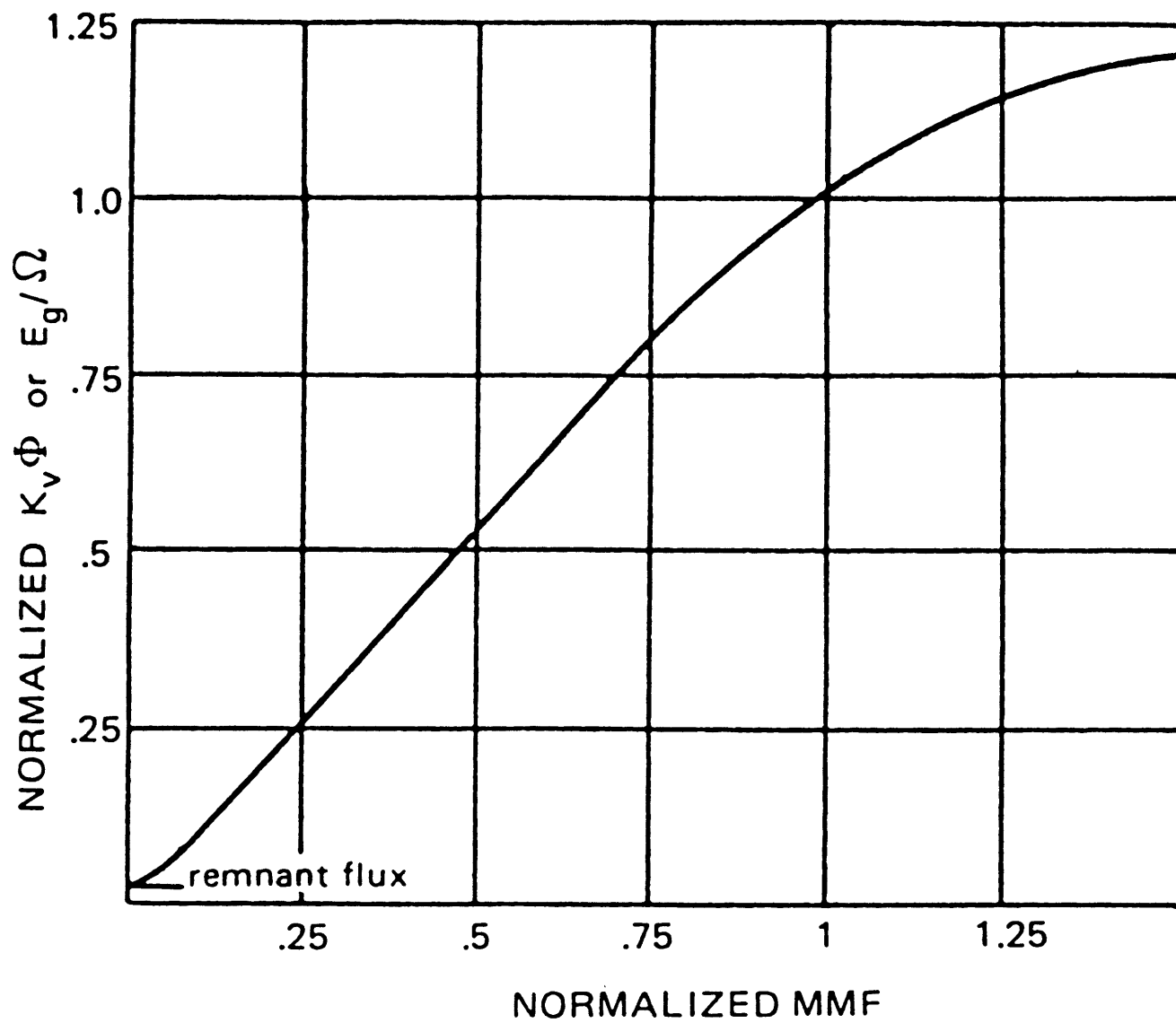


Figure 7.2 Saturation curve

PE REVIEW- TRANSMISSION LINES SECTION



SUPPLEMENTARY NOTES: THE SMITH CHART

P1

THE SMITH CHART IS A GRAPH OF COMPLEX IMPEDANCES OR ADMITTANCES, ARRANGED TO PERMIT RAPID SOLUTION OF WAVE DEPENDENT CIRCUIT PROBLEMS.



IMPEDANCE CHART

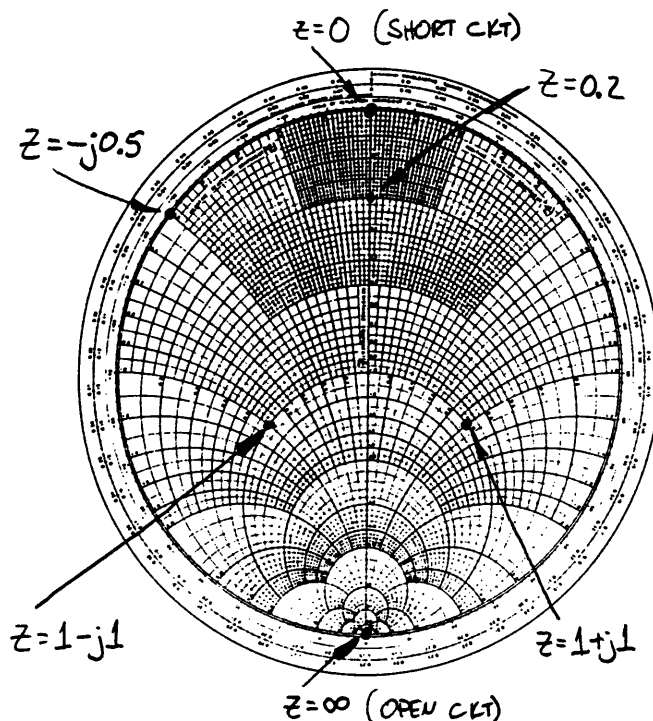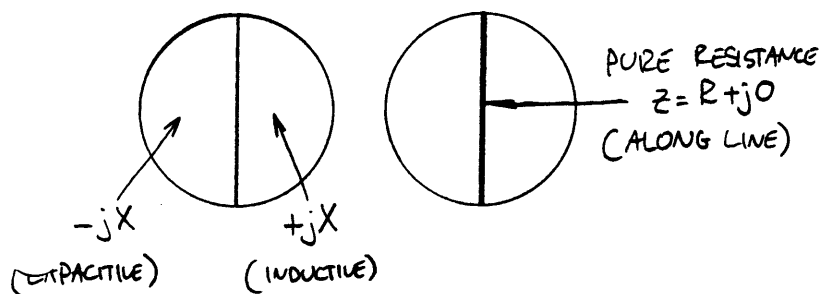THE CHART IS NORMALIZED WITH RESPECT TO THE LINE IMPEDANCE, Z_0 , SO THAT THE CENTER $z = 1$.



ADMITTANCE CHART

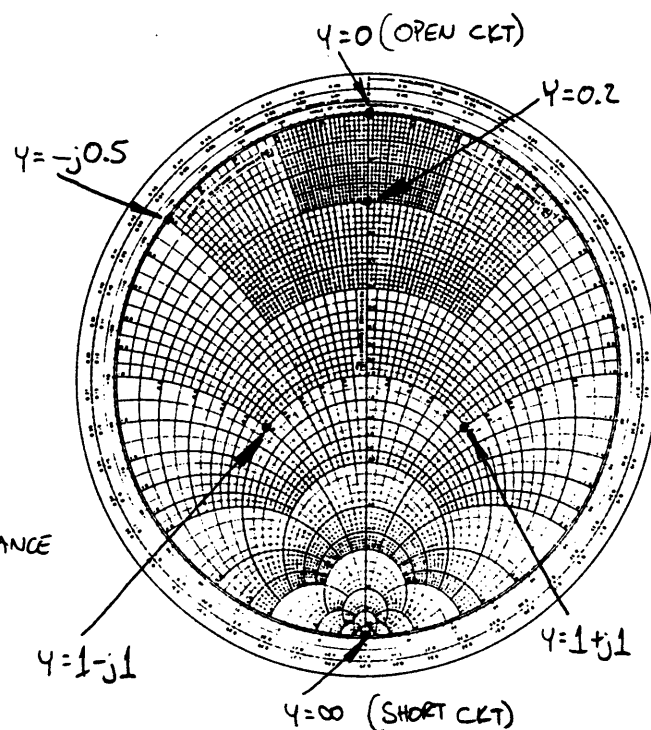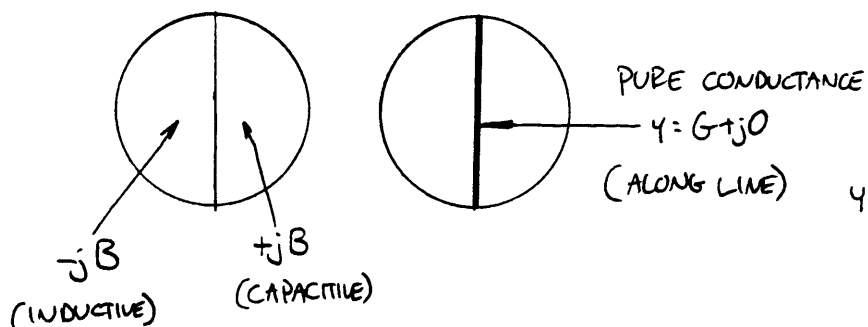THE CHART IS NORMALIZED WITH RESPECT TO THE LINE ADMITTANCE, Y_0 , SO THAT THE CENTER $y = 1$.



EXAMPLE #1: TRANSMISSION LINE $Z_0 = 72 \Omega$, $\beta = .5 \frac{\text{RAD}}{\text{M}}$, $\ell = 7.5 \text{ m}$.
 THE LINE IS TERMINATED IN LOAD $Z_L = 50 \Omega$.
 WHAT IS THE INPUT IMPEDANCE OF THE LINE?

P2

① NORMALIZE Z_L ,

$$z_L = \frac{Z_L}{Z_0} = \frac{50}{72} = .69$$

PLOT z_L .

② DRAW CIRCLE OF CONSTANT $|P|$ THROUGH z_L .


③ ELECTRICAL LENGTH OF LINE

$$\ell_e = \frac{\beta}{2\pi} \ell = \frac{.5}{2\pi} 7.5$$

$$\ell_e = 0.6\lambda$$

④ START AT TOP OF CHART, TRAVEL 0.6λ TOWARD GENERATOR. EACH 360° TRIP IS $.5\lambda$.

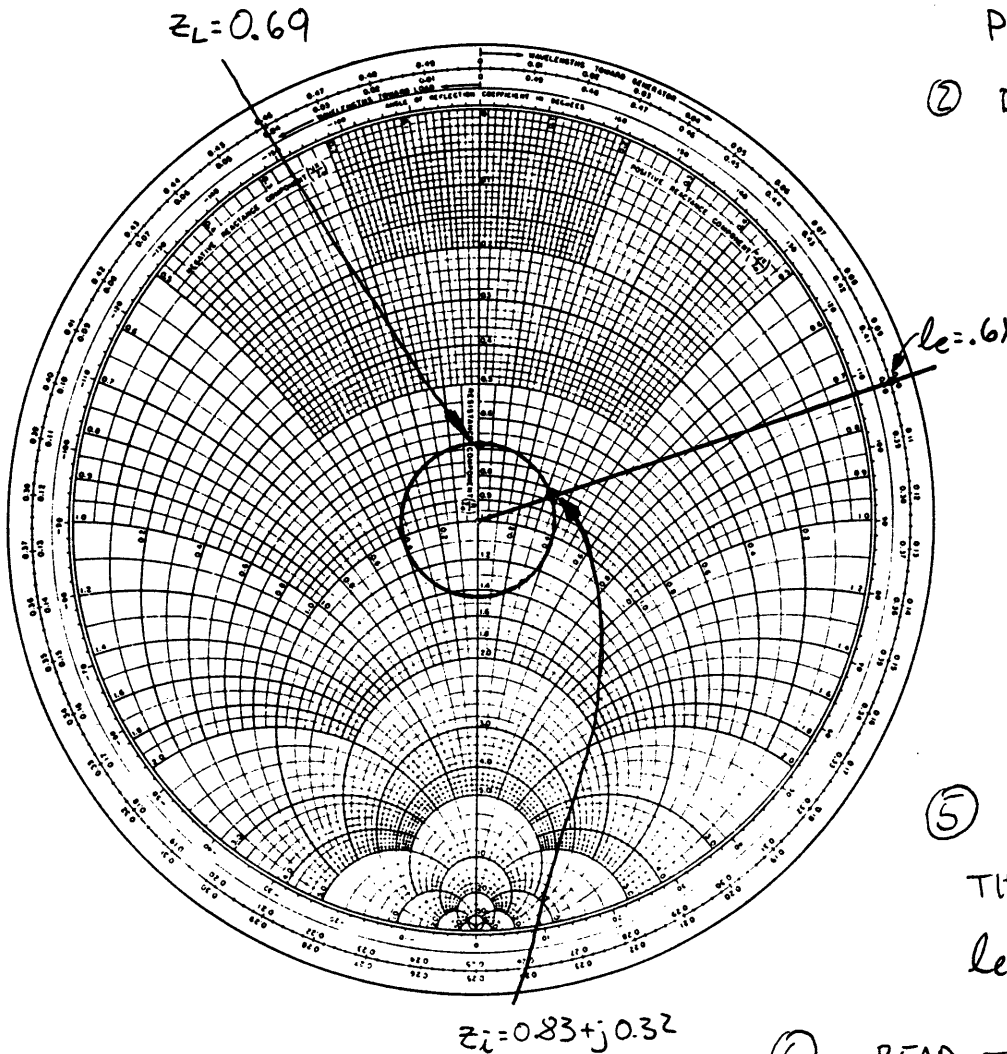⑤ DRAW A LINE FROM THE CENTER THROUGH $\ell_e = .6\lambda$.



⑥ READ THE NORMALIZED WPT z_i FROM THE INTERSECTION.

$$z_i = 0.83 + j0.32$$


⑦ DIMENSION THE ANSWER

$$Z_i = z_i Z_0$$


$$Z_i = 0.83 + j0.32 (72 \Omega)$$

$$Z_i = 60 + j23 \Omega$$

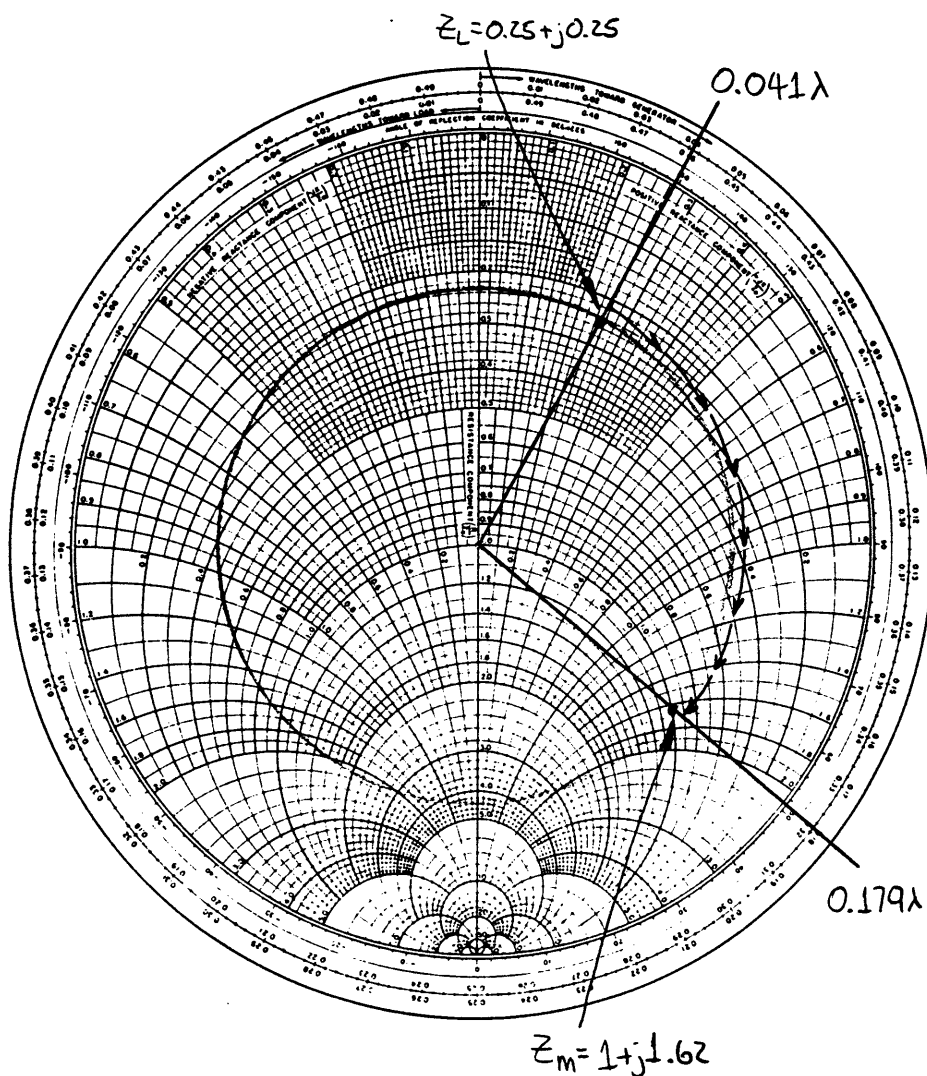EXAMPLE #2: TRANSMISSION LINE $Z_0 = 100\Omega$ FEEDS LOAD $Z_L = 25 + j25\Omega$.
FIND THE COMPONENT VALUES AND LOCATIONS FOR
SERIES CONJUGATE MATCHING.



FINAL CKT:

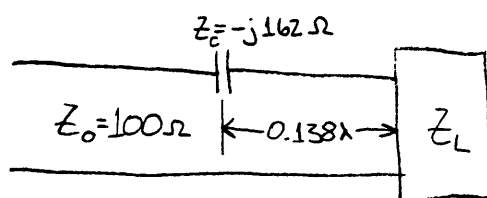

- ① NORMALIZE

$$z_L = \frac{Z_L}{Z_0} = 0.25 + j0.25,$$
 AND PLOT.
- ② PLOT CIRCLE OF CONSTANT $|P|$, DRAW LINE FROM CENTER THROUGH Z_L , AND READ WAVELENGTH, 0.041λ .
- ③ FOLLOW ALONG $|P|$ CIRCLE, IN DIRECTION TO GENERATOR UNTIL $Z_m = 1 + jX$. READ $Z_m = 1 + j1.62$.
 FOR CONJUGATE MATCH

$$1 = Z_m + Z_c$$

$$Z_c = 1 - Z_m = -j1.62.$$
- ④ DIMENSION IT

$$Z_c = z_c Z_0 = -j162\Omega,$$
 OR SINCE $X_c = \frac{1}{Z\pi fC}$,
 THE CAPACITOR


$$C = \frac{1}{Z\pi f(162)}.$$
- ⑤ DRAW A LINE FROM CENTER THROUGH Z_m . READ WAVELENGTH, 0.179λ .
 COMPENSATOR LOCATION

$$l_c = 0.179\lambda - 0.041\lambda$$


$$l_c = 0.138\lambda.$$

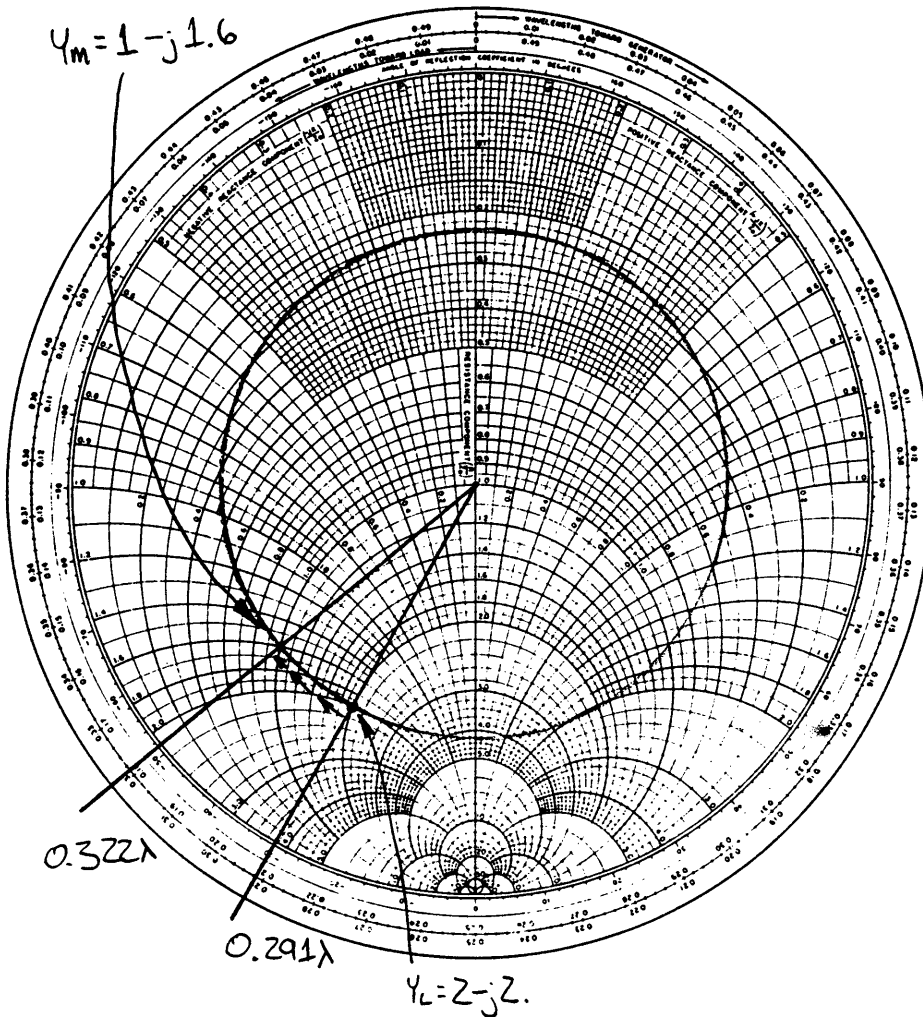EXAMPLE #3: SAME CKT VALUES AS EXAMPLE #2, BUT USE SHUNT CONJUGATE MATCHING.

NOW $Y_o = \frac{1}{Z_o} = .01S$, $Y_L = \frac{1}{Z_L} = .02 - j.02S$.



FINAL CKT:

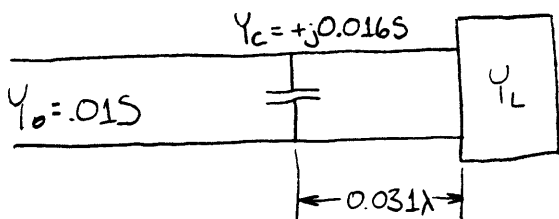

① NORMALIZE
 $Y_L = \frac{Y_L}{Y_o} = Z - jZ,$

PLOT, AND DRAW $|P|$ CIRCLE.

② DRAW LINE, READ WAVELENGTH 0.291λ.

③ MOVE ALONG $|P|$ UNTIL
 $Y_m = 1 + jB.$

READ
 $Y_m = 1 - j1.6$

FOR CONJUGATE MATCH,

$1 = Y_m + Y_c,$
 $Y_c = j1.6.$

④ DIMENSION IT
 $Y_c = Y_o Y_c = j0.016S.$

SINCE $B_c = Z\pi fC,$

$C = \frac{.016}{Z\pi f}$

⑤ DRAW LINE FROM CENTER THROUGH Y_m , READ WAVELENGTH 0.322λ.


COMPENSATOR LOCATION

$l_c = 0.322\lambda - 0.291\lambda.$

$l_c = 0.031\lambda.$

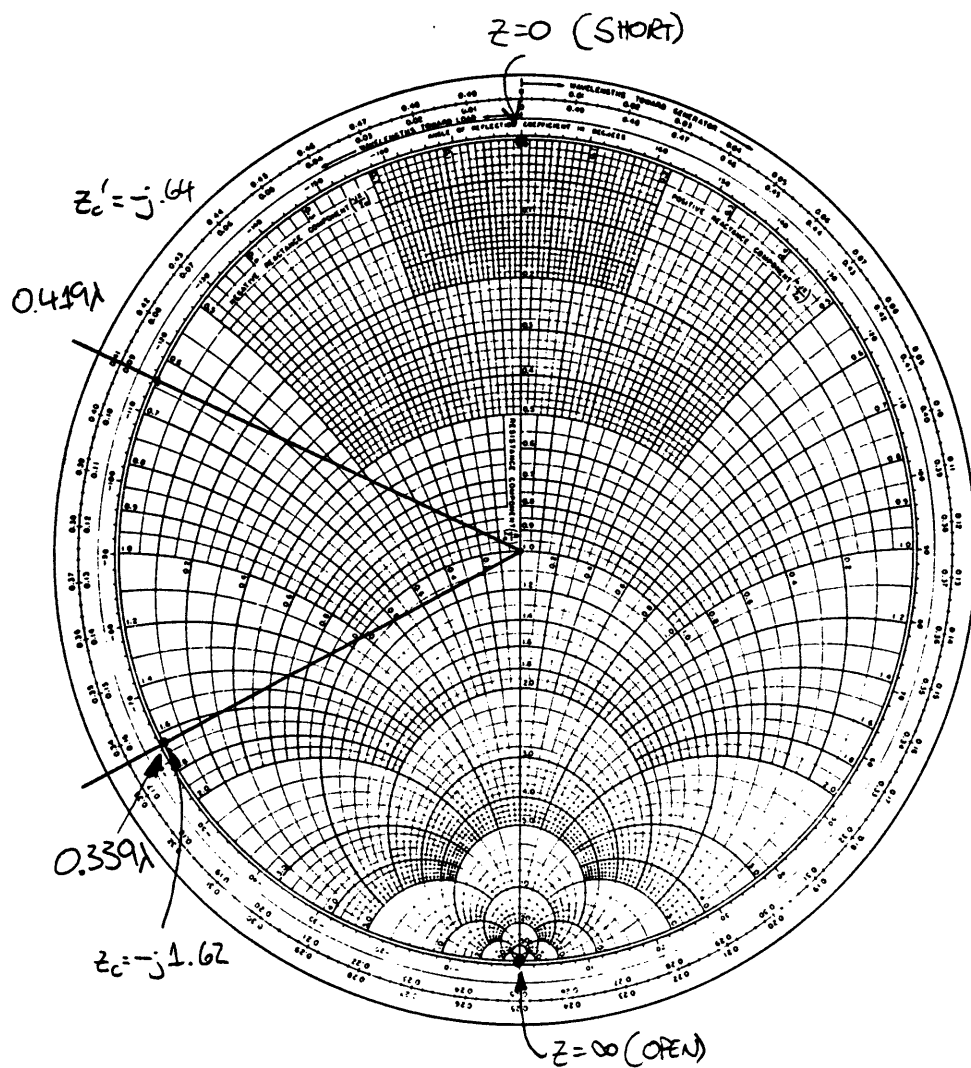EXAMPLE #4: IN EXAMPLE #2, WE NEEDED A SERIES COMPENSATION ELEMENT $Z_c = -j162\Omega$.

DESIGN A SUITABLE COMPENSATOR FROM TRANSMISSION LINE STUBS. USE BOTH OPEN & SHORTED STUBS, WITH $Z_0 = 100\Omega$ AND $Z_0 = 250\Omega$ FOR THE STUB LINE.



① $Z_0 = 100\Omega$.

NORMALIZE

$$z_c = \frac{Z_c}{Z_0} = -j1.62.$$

PLOT z_c , DRAW LINE & READ WAVELENGTH

0.339 λ .

② SHORTED STUB LENGTH JUST 0.339 λ .

OPEN STUB LENGTH IS DISTANCE FROM $z = \infty$ (BOTTOM) TO 0.339 λ , OR 0.339 λ - 0.25 λ = 0.089 λ .

③ $Z_0 = 250\Omega$.

NORMALIZE,

$$z_c' = \frac{Z_c}{Z_0} = -j.64,$$

PLOT, DRAW, READ



0.419 λ .

④ AS ABOVE, JUST READ LENGTHS CLOCKWISE

OPEN: 0.419 λ - 0.25 λ = 0.169 λ

SHORT: 0.419 λ .

FINAL CKT:

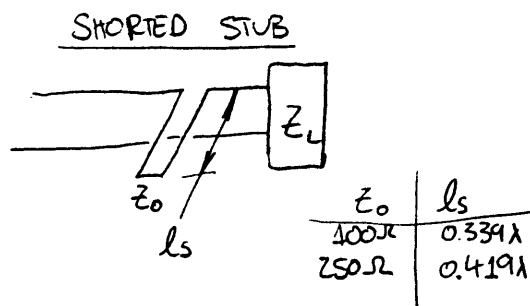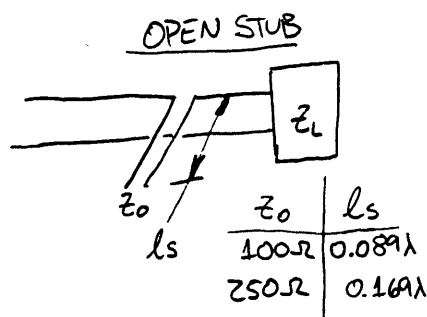

EXAMPLE #5: IN EXAMPLE #3 WE NEEDED A SHUNT COMPENSATOR $Y_c = j0.016S$. DESIGN A SUITABLE SHUNT COMPENSATOR FROM OPEN & SHORTED STUBS, $Z_o = 100\Omega$ AND $Z_o = 250\Omega$.

① $Z_o = 100\Omega$, $Y_o = .01S$.

NORMALIZE,
 $Y_c = \frac{Y_c}{Y_o} = j1.6$.

PLOT, DRAW, READ
 0.161λ .


② OPEN STUB = 0.161λ ,
 SHORTED STUB = $0.161\lambda + .25\lambda$
 $= 0.411\lambda$.

③ $Z_o = 250\Omega$, $Y_o = 0.004S$.

NORMALIZE
 $Y_c' = \frac{Y_c}{Y_o} = j4$.

PLOT, DRAW, READ
 0.211λ .


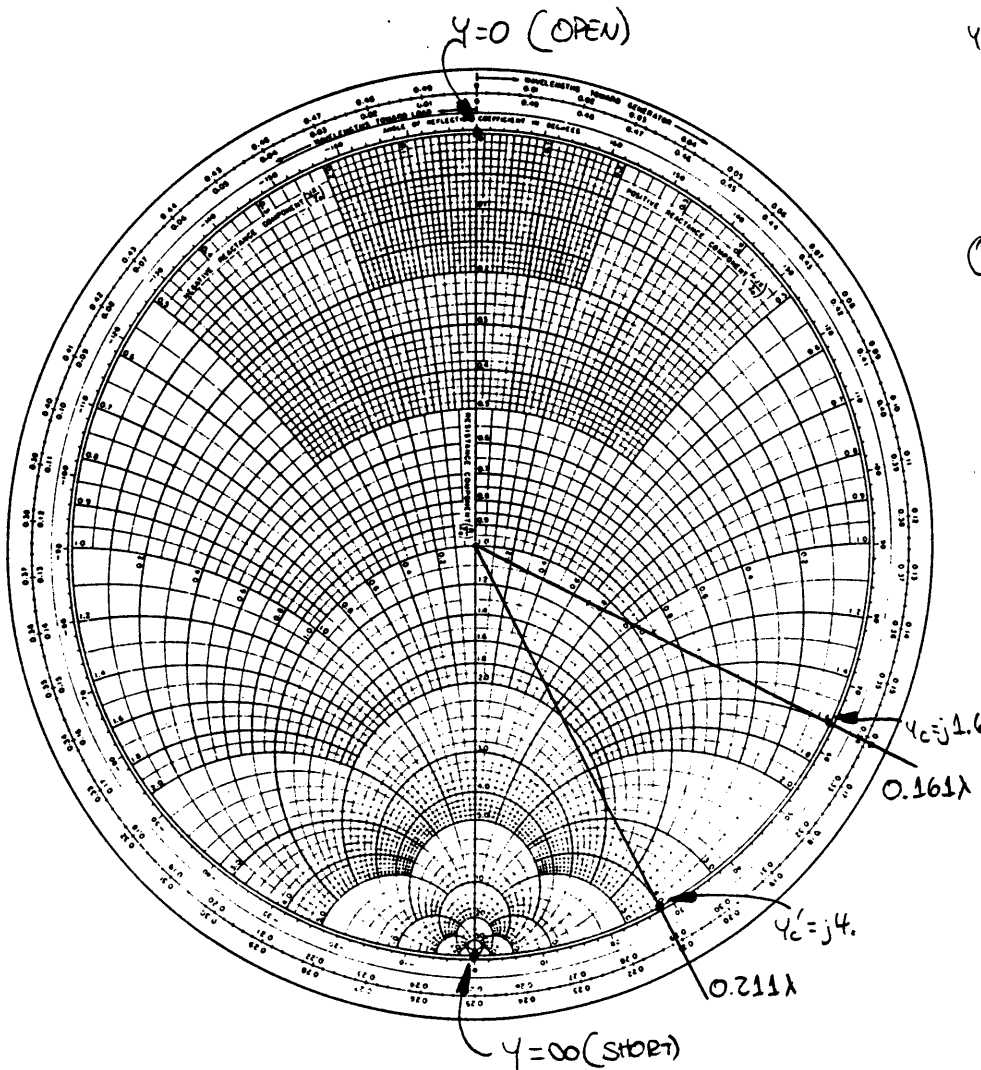
④ OPEN STUB = 0.211λ
 SHORT STUB = $0.211\lambda + .25\lambda$
 $= 0.461\lambda$.



FINAL CKT

OPEN STUB

SHORTED STUB

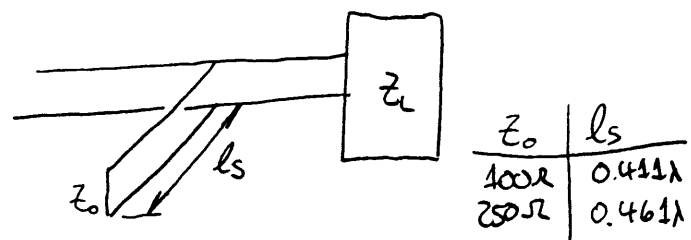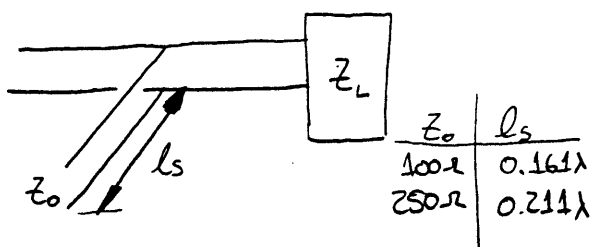

WARMUP 1.



Eq. 6.4 $\delta = \sqrt{\rho / (\pi f \mu)}$

$$\rho = 1.8 \times 10^{-8} \text{ m}$$

$$f = 10^7 \text{ Hz}$$

$$\mu = \mu_0 = 4\pi \times 10^{-7}$$

$$\delta = 21.35 \times 10^{-6} \text{ m}$$

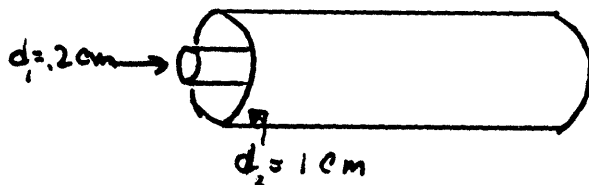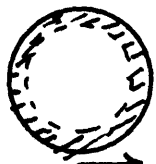INNER CONDUCTOR

conducting area

$$\sim 2\pi r \times \delta$$

in meters²

Approximate width by $2\pi r$

$$r = 0.1 \text{ cm}$$

$$\delta = 0.0021 \text{ cm}$$

OUTER CONDUCTOR

conducting area $2\pi R \times \delta$

From eq. 6.5 the impedance per unit length per unit width.

$$Z = Z_i + Z_o$$

$$= \frac{\rho}{\delta 2\pi r} (1+j) + \frac{\rho}{\delta 2\pi R} (1+j)$$

$$= \frac{1.8 \times 10^{-8} \times 100}{2\pi \times 21.35 \times 10^{-6}} \left[\frac{1}{0.1} + \frac{1}{0.5} \right] [1+j]$$

$$Z = 0.161(1+j)$$

WARMUP 2.

From appendix A, AWG #1 wire has a diameter of 289 mils (1 mil = 0.001 inch).

From example 6.1 it was shown that the skin-depth for copper at 10 kHz is 26 mils. then the

$$\text{ratio: } \frac{R}{\delta} = \frac{289/2}{26} = 5.56$$

Using equation 6.8:

$$\frac{R}{R_0} = 0.25 + 0.5 \frac{R}{\delta} = 3.03$$

Using equation 6.9:

$$\frac{X}{R_0} = 0.5025 \frac{R}{\delta} = 2.79$$

From exercise 6.3:

$$R_0 = 0.124 \Omega / 1000 \text{ ft}$$

$$Z_L = 0.124 [3.03 + j2.79]$$

$$= 0.376 + j0.346$$

ohms / 1000 ft.

WARMUP 3.

From Appendix A $r = 16$ mils

From example 6.2 $\delta = 2.6$ mils

From Appendix A $R_0 = 10.15 \frac{\Omega}{1000 \text{ ft}}$

$$\frac{r}{\delta} = 6.15 \text{ and from eq. 6.9:}$$

$$\frac{X_i}{R_0} = 0.5025 \frac{r}{\delta} = 3.09$$

Then, for each conductor

$$X_i = 3.09 \times 10.15 = 31.36 \frac{\Omega}{1000 \text{ ft}}$$

$$\text{So } X_{i \text{ total}} = 2X_i = 62.73 \frac{\Omega}{1000 \text{ ft.}}$$

$$D/r = \frac{1 \text{ cm}}{16 \text{ mils}} \times \frac{10^3 \text{ mils}}{1 \text{ inch}} \times \frac{1 \text{ inch}}{2.54 \text{ cm}} = 24.61$$

From eq. 6.10

$$L_{\text{ext}} = 4 \times 10^{-7} \ln \frac{D}{r} = 1.281 \times 10^{-6} \frac{\text{H}}{\text{m}}$$

$$X_{\text{ext}} = 2\pi f L_{\text{ext}} = 8.05 \frac{\Omega}{\text{m}}$$

$$= 8.05 \frac{\Omega}{\text{m}} \times \frac{1 \text{ m}}{1000 \text{ cm}} \times \frac{2.54 \text{ cm}}{1 \text{ inch}} \times \frac{12 \text{ inch}}{\text{Foot}}$$

$$= 2.454 \frac{\Omega}{\text{ft}} = 2,454 \frac{\Omega}{1000 \text{ ft}}$$

then:

$$X_{\text{Tot}} = X_i + X_{\text{ext}} = 2,517 \frac{\Omega}{1000 \text{ ft}}$$

WARMUP 4.

From eq. 6.16

$$C_e = \frac{2\pi\epsilon}{\ln \frac{D}{d}}, \text{ where } D \text{ is}$$

the ID of the outer conductor

and d is the diameter of the inner conductor.

$$\epsilon = \epsilon_0 = \frac{1}{36\pi \times 10^9}$$

$$\text{So } C_e = \frac{\frac{2\pi}{36\pi} \times 10^{-9}}{\ln(2/0.2)} = 24.1 \text{ pF/m}$$

WARMUP 5.

From table 6.2:

$$\text{GMR} = 0.0586, X_L(1 \text{ ft}) = 0.344$$

From eq. 6.19:

$$K_L = 1 + \frac{\ln(D)}{\ln \frac{1}{\text{GMR}}} = 1 + \frac{\ln 10}{\ln \frac{1}{\text{GMR}}} = 1.812$$

then

$$X_L = 1.812 \times 0.344 = 0.632 \frac{\Omega}{\text{mile}}$$

WARMUP 6.

From table 6.2: $X_c = 0.0776 \text{ M}\Omega\text{-mi}$

The correction factor K_c is:

$$K_c = 1 + \frac{\ln(\text{separation in feet})}{\ln \frac{1}{\text{wire radius in feet}}}$$

so

$$K_c = 1 + \frac{\ln 20}{\ln \frac{24}{1.762}} = 2.147$$

$X_c = 2.147 \times 0.0776 \text{ M}\Omega\text{-mi/conductor}$
for 2 miles and 2 conductors:

$$X_c \Rightarrow \frac{2.147 \times 0.0776}{2 \text{ cond} \times 2 \text{ mi}} = 0.0417 \text{ M}\Omega = 41.7 \text{ K}\Omega$$

WARMUP 7.

As Outside Diameter (O.D.) is in inches, and the spacing is 1.0 foot:

$$\ln \frac{d}{r} = \ln \frac{d(\text{ft})}{\frac{\text{O.D.}}{2} \times \frac{1}{12}} = \ln \frac{24d(\text{ft})}{\text{O.D.}(\text{in})}$$

Eq. 6.43

$$X_c = 29,668 \ln \left(\frac{d}{r} \right) \Omega\text{-mi}$$

$$= 29,668 \ln \frac{24 d(\text{ft})}{\text{O.D.}(\text{in})}$$

Conductor	CALCULATED $X_c (\text{M}\Omega\text{-mi})$	TABLE 6.2 $X_c (\text{M}\Omega\text{-mi})$
WAXWING	0.1090	0.1090
PARTRIDGE	0.1074	0.1074
BLUEBIRD	0.0775	0.0775

WARMUP 8.

From Chapter 4



Let $a \rightarrow 1$, $b \rightarrow 2$, $c \rightarrow 3$

$$Z_1 = \frac{Z_{12} Z_{13}}{Z_{12} + Z_{23} + Z_{13}}$$

$$Z_2 = \frac{Z_{12} Z_{23}}{Z_{12} + Z_{23} + Z_{13}}$$

$$\text{and } Z_3 = \frac{Z_{13} Z_{23}}{Z_{12} + Z_{13} + Z_{23}}$$

so:

$$Z_{an} = \frac{2 \times 1.8}{2 + 2.5 + 1.8} = \frac{3.6}{6.3} = 0.571 \Omega$$

$$Z_{bn} = \frac{2 \times 2.5}{6.3} = 0.794 \Omega$$

$$Z_{cn} = \frac{2.5 \times 1.8}{6.3} = 0.714 \Omega$$

WARMUP 9.

The VOLT-AMPERE ratings are the same.

The voltage rating for the delta connection is $\sqrt{3}$ times that for the WYE connection.

The current rating for the WYE connection must be $\sqrt{3}$ times that for the delta connection.

WARMUP 10.

The radiation resistance is obtained from eq 6.142.

$$R_r = \frac{\beta^2 d z^2}{6\pi} \sqrt{\frac{\mu_0}{\epsilon_0}}$$

$$\text{where } \beta = \frac{\omega}{c} = \frac{\omega_0}{3 \times 10^8}$$

WARMUP 10 CONTINUED

with $\sqrt{\frac{\mu_0}{\epsilon_0}} = 120\pi$, and

$$\omega = 2\pi \times 60 = 120\pi$$

$$R_e = 3.2 \times 10^{-11} \text{ ohms}$$

From Appendix A

$$R_o = 10.15 \Omega / 1000 \text{ ft}$$

$$= \frac{10.15 \Omega}{1000 \text{ ft}} \times \frac{1 \text{ ft}}{12 \text{ in.}} \times \frac{1 \text{ in.}}{2.54 \text{ cm}} \times \frac{100 \text{ cm}}{\text{m}}$$

$$= 0.0333 \text{ ohms/meter}$$

$$e = \frac{3.2 \times 10^{-11}}{0.0333} \times 100$$

$$= 9.6 \times 10^{-8} \%$$

i.e. not very efficient.

CONCENTRATE 1.

From table 6.2: GMR = 0.0217

$$d_s = \sqrt[3]{10 \times 10 \times 10 \sqrt{2}} = 11.22 \text{ ft.}$$

Eq. 6.33

$$L = 2 \times 10^{-7} \ln \frac{d_s}{\text{GMR}} = 1.25 \mu\text{H/m}$$

$$X_L = 120\pi L = 4.71 \times 10^{-4} \Omega/\text{m}$$

Eq. 6.34

$$M_{bc} = 2 \times 10^{-7} \ln \frac{r_{ab} r_{ac}}{d_s^2}$$

then

$$M_{ab} = M_{ac} = 2 \times 10^{-7} \ln \frac{10 \times 10 \sqrt{2}}{d_s^2} \\ = 2.33 \times 10^{-8} \text{ H/m}$$

$$M_{bc} = 2 \times 10^{-7} \ln \frac{10 \times 10}{d_s^2} \\ = -4.60 \times 10^{-8} \text{ H/m}$$

as there are 1609 meters per mile:

$$X_L = 1609 \times 4.71 \times 10^{-4} = 0.758 \Omega/\text{mi}$$

$$X_{ab} = X_{ac} = 1609 \times 120\pi \times M_{ab} \\ = 0.014 \Omega/\text{mi}$$

$$X_{bc} = 1609 \times 120\pi \times M_{bc} \\ = -0.028 \Omega/\text{mi}$$

CONCENTRATE 2.

For a balanced 3-phase load, the WYE-DELTA TRANSFORMATION is a factor of 3. i.e.

$$Z_{L-n} = \frac{Z_{L-L} \times Z_{L-L}}{Z_{L-L} + Z_{L-L} + Z_{L-L}} \\ = \frac{Z_{L-L}}{3}$$

Converting to an equivalent Wye configuration:

CONCENTRATE 2. CONTINUED

$$Z_{\text{phase}} = 3 + j4 + \frac{20 + j15}{3} = \frac{29 + j27}{3}$$

$$P_{\text{load}} = \frac{30 \text{ KW}}{3 \text{ phases}} = I_{\text{Line}}^2 \times \frac{20}{3}$$

so $I_{\text{Line}} = \sqrt{1500}$

Selecting the a-phase current as a reference:

$$V_s = \sqrt{1500} \left[\frac{29 + j27}{3} \right] \\ = 511.5 \angle 42.95^\circ$$

$$S_{\text{phase}} = V_s I_{\text{Line}} = (14.5 + j13.5) \text{ KVA}$$

(a) $V_s = 511.5 \text{ V l-line}$
 $P = 14.5 \text{ KW/phase}$
 $Q = 13.5 \text{ KVAR/phase}$

OR $V_s = 511.5 \times \sqrt{3} = 886 \text{ V l-l}$

$P = 43.5 \text{ KW}$
 $Q = 40.5 \text{ KVAR}$

(b) Compensation is by means of a parallel capacitance, so the load impedance is converted to admittance

$$Y_L = \frac{3}{20 + j15} = \frac{60 - j45}{625}$$

Compensation requires a parallel capacitor with $B_C = \frac{45}{625}$ or $X_C = -13.89 \Omega$

The compensated load impedance is then:

$$Z_{L-\text{comp}} = \frac{625}{60} = 10.42 \Omega$$

Assuming the load voltage remains the same, the previous value is calculated

$$V_{L/\text{uncomp}} = \sqrt{1500} \left(\frac{20 + j15}{3} \right) \\ = 322.7 \angle 36.87^\circ$$

The current is then

$$I_{\text{Line}} = \frac{322.7}{10.42} = 30.97 \text{ A}$$

$$V_s = 30.97 [13.42 + j14] \\ = 433.7 \angle 16.60^\circ \text{ l-n}$$

$$P_{\text{phase}} = 12.87 \text{ KW}$$

$$Q_{\text{phase}} = 3.84 \text{ KVAR}$$

or

$$V_{l-l} = \sqrt{3} \times 433.7 = 751 \text{ V l-l}$$

$$P = 38.6 \text{ KW}$$

$$Q = 11.5 \text{ KVAR}$$

CONCENTRATE 3.

From table 6.2 the resistance per mile is 0.1943 ohms at 20°C and 0.2134 ohms at 50°C. As example 6.9 found a current of 225 A, which is a current density of about 370 A/in², so the temperature should rise, and so the 50°C value of 0.2134 ohms is used.

From table 6.2 the inductive reactance at 1-ft spacing is 0.432 ohms/mile. With GMR = 0.0284, the correction factor is:

$$K_L = 1 + \frac{\ln 7}{\ln \frac{1}{0.0284}} = 1.5464$$

then

$$X_L = 1.5464 \times 0.432 \times 25 \text{ mi} \\ = 16.70 \Omega / \text{mile}$$

the line impedance is then

$$Z_L = 5.36 + j16.70 \Omega$$

The unknown voltage at the receiving end is

taken as the reference. The current then leads this voltage by 25.8° (cos⁻¹ 0.9). Then:

$$V_S = V_L + 225 \angle 25.84^\circ [Z_L] \\ = V_L + 3.946 \angle 98.01^\circ [\text{KV}]$$

$$V_S = V_L - 0.550 + j3.908 [\text{KV}]$$

but

$$V_S = 11 \cos \theta + j 11 \sin \theta [\text{KV}]$$

$$\text{and } V_L = V_L + j0$$

$$\text{then } 11 \sin \theta = 3.908$$

$$\sin \theta = 0.355$$

$$\theta = 20.81^\circ$$

$$V_L = 11 \cos 20.81^\circ + 0.550 \\ = 10.83 \text{ KV}$$

$$V_S = 11 \cos 20.81^\circ + j 11 \sin 20.81^\circ \\ = 11 \text{ KV}$$

So regulation:

$$\frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = \frac{11 - 10.83}{10.83} \times 100$$

$$\text{Regulation} = 1.57\%$$

CONCENTRATE 4.			1-ft spacing	
OD. INCHES	R/mi 60 Hz 50°C	GMR feet	X_L Ω/mi	X_C MR-mi
1.545	0.0667	0.0523	0.358	0.0814

Table parameters for FALCON
(table 6.2)

Correction factors for 20 ft
spacing:

$$K_L = 1 + \frac{\ln 20}{\ln \frac{1}{0.0523}} = 2.015$$

$$K_C = 1 + \frac{\ln 20}{\ln \frac{24}{1.545}} = 2.092$$

$$X_L = 0.358 \times 2.015 = 0.7214 \frac{\Omega}{\text{mi}}$$

$$X_C = 0.0814 \times 2.092 = 0.1703 \times 10^6 \frac{\Omega}{\text{mi}}$$

then

$$Z = 0.0667 + j0.7214 \frac{\Omega}{\text{mi}}$$

$$Y = j \frac{1}{0.1703 \times 10^6} = j5.8724 \times 10^{-6} \frac{\text{mho}}{\text{mi}}$$

These parameters are converted
to a per meter basis:

There are 1609.3 meters/mile

$$Z = 41.45 \times 10^{-6} + j448.3 \times 10^{-6} \\ = 450.2 \times 10^{-6} \angle 84.72^\circ \frac{\Omega}{\text{m}}$$

$$Y = j3.649 \times 10^{-9} \frac{\text{mhos}}{\text{m}}$$

Then:

$$YZ = 1.643 \times 10^{-12} \angle 174.7^\circ / \text{m}^2$$

$$\sqrt{YZ} = 1.282 \angle 87.36^\circ = \gamma$$

$$(a) \quad \gamma = 59.06 \times 10^{-9} + j1.280 \times 10^{-6}$$

$$(b) \quad \gamma = \alpha + j\beta$$

$$\alpha = 59.06 \times 10^{-9} [\text{meter}]^{-1}$$

$$(c) \quad \beta = 1.280 \times 10^{-6} [\text{meter}]^{-1}$$

$$(d) \quad \gamma_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{450.2 \times 10^{-6} \angle 84.72^\circ}{3.649 \times 10^{-9} \angle 90^\circ}}$$

$$= 351.2 \angle \frac{1}{2}(84.72 - 90)$$

$$= 351.2 \angle -5.28^\circ$$

$$= 349.7 - j32.3$$

$$(e) \quad \rho = \frac{Z_L - \gamma_0}{Z_L + \gamma_0} = \frac{-249.7 + j32.3}{449.7 - j32.3}$$

$$= -0.558 \angle -3.26^\circ$$

$$= 0.558 \angle 176.7^\circ$$

CONCENTRATE 5.

$$\rho = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{70 - 50}{70 + 50} = \frac{1}{6} \quad (a)$$

$$(b) \quad Z_i = Z_0 \frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l}$$

$$= 50 \frac{70 \cos \frac{\pi}{2} + j 50 \sin \frac{\pi}{2}}{50 \cos \frac{\pi}{2} + j 70 \sin \frac{\pi}{2}} = 35.71 \, \Omega$$


$$(c) \quad VSWR = \frac{1 + |\rho|}{1 - |\rho|} = \frac{1 + \frac{1}{6}}{1 - \frac{1}{6}} = 1.40$$

CONCENTRATE 6.

$$\frac{Z_L}{Z_0} = \frac{25 - j25}{50} = \frac{1}{2} - j\frac{1}{2}$$

The load point is shown on the smith chart below.

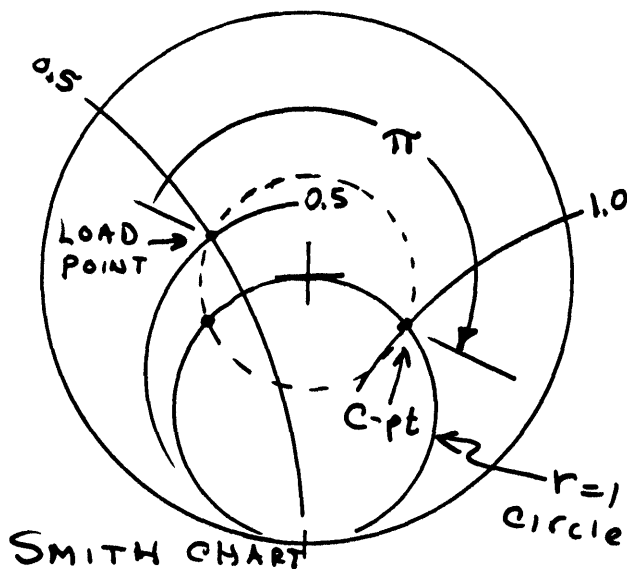Impedance loci is shown as a dashed circle.



The compensation point for series capacitance is where the impedance loci intersects the $r=1$ circle on the right-hand side of the chart.

For this particular load the compensation point is 180° (on the chart) from the load point, at

$$Z_i = 1 + j1$$

180° on the smith chart is $\lambda/4$ or $\pi/2$ radians for βl .

$$\frac{Z_i}{Z_0} = \frac{\frac{Z_L}{Z_0} \cos \beta l + j \sin \beta l}{\cos \beta l + j \frac{Z_L}{Z_0} \sin \beta l}$$

$$= \frac{\frac{1}{2} \cos \beta l + j (\sin \beta l - \frac{1}{2} \cos \beta l)}{\cos \beta l + \frac{1}{2} \sin \beta l + j \frac{1}{2} \sin \beta l}$$

at $\beta l = \pi/2$ $\sin \beta l = 1$, $\cos \beta l = 0$

$$\frac{Z_i}{Z_0} = \frac{j}{\frac{1}{2} + j\frac{1}{2}} = \frac{2}{j+1} = 1 + j$$


So the compensating reactance must be $-j1$ or

$$X_c = -Z_0 = -50 \, \Omega$$

CONCENTRATE 7.

$$a) \frac{Z}{Z_0} = \frac{-j25}{50} = -0.5$$

The bottom of the chart is open.

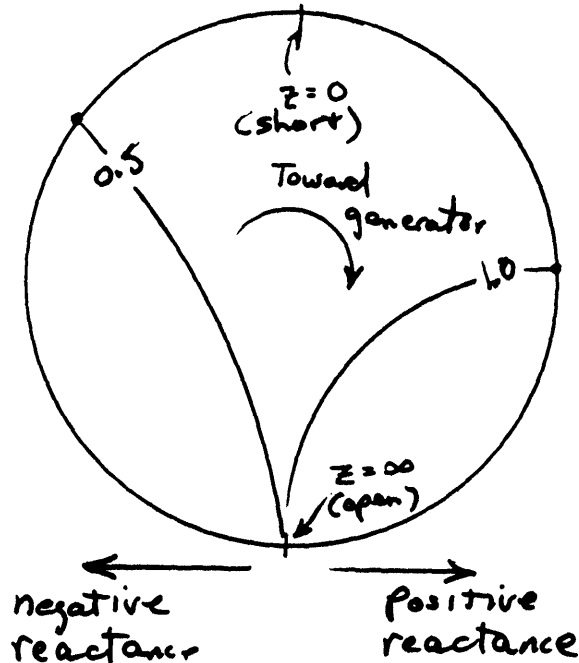

The shortest length to obtain $-j1.5 \times 50$ is to start with an open line. Going clockwise 126.5° to the intersection with $x = 0.5$ on left half of Smith chart. This corresponds to $\beta l = \frac{126.5^\circ}{2 \times 180^\circ}$ or $\beta l = 1.1 \text{ rad} = 0.175\lambda$.

$$(b) \frac{Z}{Z_0} = \frac{j50}{50} = j1$$

The shortest line is found for a shorted line

(short point at top of the Smith chart) going clockwise to intersect the $x=1$ circle (on the right), which is 90 degrees on the chart, corresponding to $\beta l = 45 \times \frac{\pi}{180}$
 $\beta l = 0.785 \text{ radians or } \lambda/8$

CONCENTRATE 8.

$$\text{Assume } c = 3 \times 10^8 \text{ m/s}$$

$$\beta = \frac{2\pi f}{c} = \frac{2\pi \times 10^8}{3 \times 10^8} = \frac{2\pi}{3} \text{ rad/m}$$

$$\beta l = \frac{2\pi}{3} \text{ rad as } l = 1 \text{ m.}$$

$$\tan \beta l = -1.732 = -\sqrt{3}$$

Eq. 6.131

$$\frac{Z_u}{Z_0} = \frac{1 - j VSWR \tan \beta l}{VSWR - j \tan \beta l}$$

$$VSWR = 2$$

$$\frac{Z_u}{Z_0} = \frac{1 + 2\sqrt{3}j}{2 + j\sqrt{3}} = 1.143 + j0.742$$

$$Z_0 = 50 \Omega$$

$$Z_u = 57.14 + j37.12$$

$$R = 57.14 \Omega$$

$$X = 37.12 \Omega$$

CONCENTRATE 9.

Following eq 6.157, the radiated power from a half-wave dipole antenna is:

$$P_r = 73.08 I_m^2$$

The radiation resistance corresponds:

$$P_r = I_m^2 R_r$$

$$R_r = 73.08 \Omega$$

At a frequency of 100 MHz, the wavelength is 3 m, and $h = \lambda/4 = 0.75$ m

The skin depth for copper at 100 MHz is (see example 6.1) 0.26 mils.

AWG #20 wire has a diameter of 32 mils, and a d.c. resistance of 10.15 Ω /1000 feet, so

$$R_0 = \frac{10.15 \Omega}{1000 \text{ ft}} \times \frac{1 \text{ ft}}{12 \text{ in}} \times \frac{1 \text{ in}}{2.54 \text{ cm}} \times \frac{100 \text{ cm}}{\text{m}} \times 75 \text{ m}$$

$$= 0.025 \Omega$$

at high frequencies (see eq. 6.8)

$$R = .025 \left[.25 + \frac{r}{\delta} \right]$$

$$= 0.025 \left[.25 + \frac{.16}{0.26} \right] = 15.93 \Omega$$

The radiation efficiency is

$$e = \frac{R_r}{R_r + R} \times 100 = \frac{73.08 \times 100}{73.08 + 15.93} \%$$

$$e = 82.1 \%$$

CONCENTRATE 10.

From eq. 6.145:

$$g = e \times g_0$$

$$e = \text{efficiency} = 0.90$$

$$g_0 = \text{directivity} = 20$$

$$g = 20 \times 0.9 = 18$$

$$\text{or } g_{\text{db}} = 10 \log_{10} 18 = 12.5 \text{ db}$$

From equation 6.176:

$$\Omega_A = \frac{4\pi}{g_0} = \frac{\pi}{5}$$

TIMED 1.

OD. (in)	R_{AC} 60 Hz 50°C	GMR ft	1-ft spacing reactance/conduct	
			$\frac{X_L}{\Omega/\text{mi}}$	$\frac{X_C}{\text{M}\Omega\text{-mi}}$
0.846	0.2134	0.284	0.432	0.0992

correction factors:

$$K_L = 1 + \frac{\ln 7}{\ln \frac{1}{0.284}} = 1.5464$$

$$K_C = 1 + \frac{\ln 7}{\ln \frac{24}{0.846}} = 1.5817$$

$$X_L = 0.432 K_L = 0.6680 \Omega/\text{mi}$$

$$X_C = -0.0992 K_C = -156.90 \times 10^3 \Omega\text{-mi}$$

TIMED 1 CONTINUED

$$Z = (0.2134 + j0.6680) \times 100$$

$$= 21.34 + j66.8 = 70.126 \angle 72.28^\circ$$

$$X_C = -\frac{157 \times 10^3 \Omega \cdot \text{mi}}{100 \text{ mi}} = -1.57 \text{ k}\Omega$$

$$Y = -\frac{j}{X_C} = 637 \times 10^{-6} \angle 90^\circ$$

$$YZ = 44.67 \times 10^{-3} \angle 162.28^\circ$$

EQ 6.59

$$V_S = \left(1 + \frac{YZ}{2}\right) V_R + Z I_R$$

EQ 6.60

$$I_S = Y \left(1 + \frac{YZ}{4}\right) V_R + \left(1 + \frac{YZ}{2}\right) I_R$$

$$1 + \frac{YZ}{2} = 0.9787 + j0.0068$$

$$1 + \frac{YZ}{4} = 0.9894 + j0.0034$$

$$V_{e-n} = V_R = \frac{86.6}{\sqrt{3}} \text{ kV} = 50 \text{ kV}$$

$$|I_R| = \frac{(8500/3) \text{ kVA}}{50 \text{ kV}} = 56.67 \text{ A}$$

$$\angle I_R = -\cos^{-1} \frac{75}{85} = -28.07^\circ$$

$$I_R = 56.67 \angle -28.07^\circ$$

EQ 6.59

$$V_S = [0.9787 \angle 2.4^\circ] 50 \text{ kV}$$

$$+ [70.126 \angle 72.28^\circ] 56.67 \angle -28.07^\circ$$

Then: $V_S = 51.88 \text{ kV} \angle 3.44^\circ$

When $I_R = 0$, from eq 6.59:

$$51.88 \text{ kV} \angle 3.44^\circ = 0.9787 \angle 2.4^\circ V_R$$

$$\text{or } V_R = 53.00 \angle 3.04^\circ$$

Then:

$$\text{Regulation} = \frac{53 - 50}{50} \times 100 = 6.0\%$$

TIMED 2.

$$Z_0 = 72 \Omega \quad Z_L = 50 \Omega \quad \beta = 0.5$$


$$l = 7.5 \text{ m}$$

$$\frac{Z_L}{Z_0} = \beta_L = \frac{50}{72} = 0.6944$$

$$\beta l = 3.75 \text{ rad} = 214.86^\circ$$

$$2\beta l = 429.72^\circ = 360 + 69.72^\circ$$

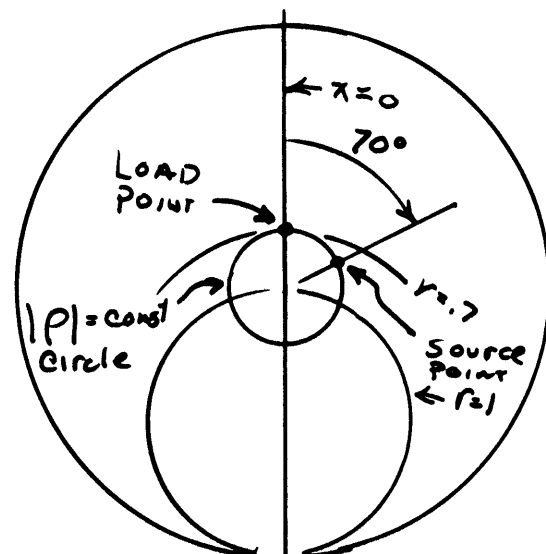The load point as shown
the source point as shown



TIMED 2 CONTINUED
 READING from the enlarged
 chart of appendix C, the
 value is $\frac{Z_i}{Z_o} \approx 0.84 + j0.29$

$$\text{or } Z_i \approx 60 + j21$$

using eq. 6.117

$$\frac{Z_i}{Z_o} = \frac{50 + j \tan 3.75 (\text{rad})}{1 + j 50 \tan 3.75}$$

$$= 0.8358 + j0.2923$$

So


$$Z_L = 60.18 + j21.05$$

TIMED 3.

$$Z_o = 100 \quad Z_L = 25 + j25$$

$$\therefore Z_L = 0.25 + j0.25$$

$$Y_L = 2 - j2$$

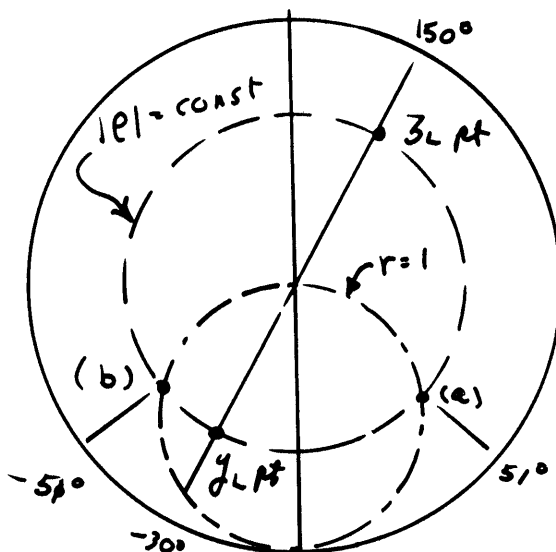

(a) the Z_L pt, $\frac{1}{4} + j\frac{1}{4}$ is at 150° . Following constant $|\Gamma|$ circle toward generator, the compensation point is at 51° where $Z_i = 1 + j1.6$, where series compensation of $-j1.6$ can be added. The line length is $\frac{150^\circ - 51^\circ}{720^\circ} \lambda = 0.1375 \lambda$ from the load. 720°

$$Z_c = j100 \times 1.6 = -j160 \Omega$$

Using a 72Ω line for the compensator, its reactance is $X_c = -\frac{160}{72} = -2.22$

STARTING from the open position (bottom of the smith chart),

The location of -2.22 is at about -48° , for a compensator length of

$$l_{\text{comp}} = \frac{48^\circ}{720^\circ} \lambda = \frac{\lambda}{15}$$

Using eq 6.117 with $Z_L \neq \infty$

$$\frac{Z_i}{Z_o} = \frac{\cos \beta l}{j \sin \beta l} = \frac{-j}{\tan \beta l}$$

$$\text{So } \tan \beta l = \frac{1}{2.22}$$

$$\beta l = \frac{2\pi}{\lambda} l = 0.423$$

$$l = \frac{0.423}{2\pi} \lambda = \frac{\lambda}{14.85}$$

TIMED 3. CONTINUED

(b) The y_L point is 180° from the z_L point on the same $|P| = \text{constant}$ circle.

The parallel compensation point is at -51° , so the distance from the load for compensation is at $\frac{51-30}{270}\lambda = 0.0704\lambda$.

at that point

$$y_L = 1 - j1.6$$

$$y = \frac{z_0}{Z} = z_0 Y \quad \text{so}$$

$$Y_{\text{comp}} = \frac{y}{z_0} = j \frac{1.6}{100}$$

For the 72Ω line

$$y_{\text{comp}} = j \frac{1.6}{100} \times 72 = j1.152$$

1.152 is on the right side of the chart at 82° .

The shortest line is from the top of the chart

($y=0$: open) at 180°

$$\text{so } l = \frac{180-82}{720}\lambda = 0.136\lambda$$

more exactly, using eq 6.117

$$\text{with } Z_L = \infty$$

$$y_c = j \tan \beta l = j1.152$$

$$\text{so } \beta l = \tan^{-1} 1.152 = .8559$$


$$l = \frac{.8559\lambda}{2\pi} = 0.1362\lambda$$

TIMED 4.

$$y_i = Y_{30} = \frac{50}{25 - j25} = 1 + j1$$

This is to be compensated with a shunt capacitance:
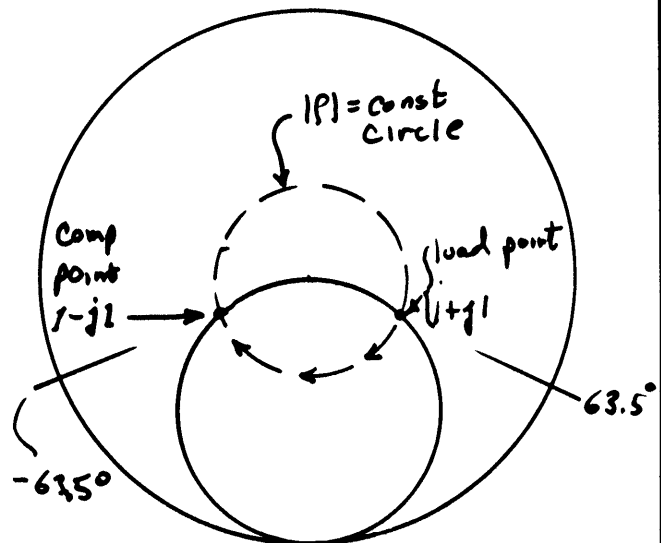
$$y_{\text{comp}} = j b_c \quad B_{30} = b_c$$



the load point is at 63.5° .
traverse the $|P| = \text{const}$ circle clockwise to $1 - j1$ at -63.5°

Distance from load is

$$d = \frac{63.5 - (-63.5)}{720}\lambda = 0.1764\lambda$$

$$B_c = b_c / z_0 = \omega C$$

$$\therefore C = 1/50\omega = 0.02/\omega \text{ F}$$

TIMED 5.

The line-neutral voltage is $220/\sqrt{3}$ KV; Load current

$$I_R = \frac{500 \text{ MW} / (3 \times 10^6)}{220/\sqrt{3} \text{ KV}} \angle -\cos^{-1} 0.9$$


Take $V_R = V_{\text{base}}$, $|I_R| = I_{\text{base}}$

$$\text{then } Z_{\text{base}} = \frac{V_{\text{base}}}{I_{\text{base}}} = \frac{(220/\sqrt{3})^2 \text{ K}^2}{500/(3 \times 10^6) \text{ M}}$$

$$Z_{\text{base}} = 87.12 \Omega$$

$$\text{then } Z_{\text{line}} = Z_L = \frac{40 + j160}{87.12} = 0.4591 + j1.8385$$

$$Y_L = Y Z_{\text{base}} = j0.09261$$

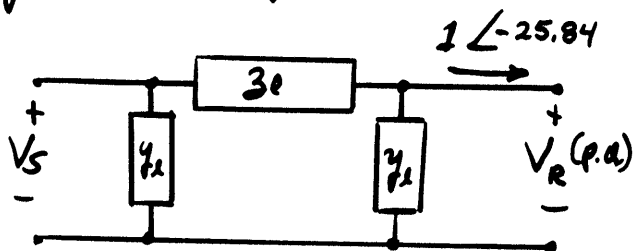

$$V_S = (I_R + Y_L V_R) Z_L + V_R$$

$$= (1 + Y_L Z_L) V_R + I_R Z_L$$

$$V_S = 1 + Y_L Z_L + Z_L \angle -25.84^\circ$$

because $|V_R| = 1$, $|I_R| = 1$

$$V_S = 0.8299 + j0.04252 + 1.2137 + j1.4528$$

$$V_S = 2.0436 + j1.4953 = 2.53 \angle 36.19^\circ \text{ p.u.}$$

Then the line-to-line sending end voltage is:

$$V_S = 220 \times 2.53 = 557 \text{ volts}$$

TIMED 6.

Taking V_R and $|I_R|$ as 1 p.u.,

$$Z_{\text{base}} = \frac{(132 \text{ K})^2}{75 \text{ MVA} / 0.92} = 213.73 \Omega$$

$$Z_{\text{line}} = (0.1 + j0.6) 100$$

$$Z = \frac{Z_{\text{line}}}{Z_{\text{base}}} = 0.2846 \angle 80.54^\circ$$

$$-X_C = \frac{0.15 \times 10^6}{100 \text{ mi}} = 1.5 \times 10^3 \Omega$$

$$Y = j \frac{Z_{\text{base}}}{-X_C} = j0.1425$$

$$1 + YZ = 0.960 + j0.0067$$

as in timed 5:

$$\begin{aligned} V_S &= 1 + YZ + Z \angle -\cos^{-1} 0.92 \\ &= 1 + YZ + 0.1531 + j0.2399 \\ &= 1.113 + j0.247 \text{ p.u.} \\ &= 1.14 \angle 12.5^\circ \text{ p.u.} \end{aligned}$$

The base voltage is 132 KV,
so

$$V_S = 132 \text{ KV} \times 1.14 = 150.5 \text{ KV}$$

TIMED 7.

The power density from an isotropic antenna at a distance r will be:

$$p_r = \frac{e_t P_t}{4\pi r^2} \text{ (isotropic)}$$

where e_t is the transmitting antenna efficiency.

For a directional antenna with a beam solid angle of Ω_T , the maximum power density will be increased over the isotropic case by the directivity:

$$g_D = \frac{4\pi}{\Omega_T}$$

So:

$$p_r = \frac{e_t P_t}{\Omega_T r^2} \text{ (anisotropic)}$$

The receiving antenna will have a power P_r :


$$P_r = e_r p_r A_{\text{eff}}$$

where $A_{\text{eff}} = \frac{\lambda^2}{4\pi} g_D = \frac{\lambda^2}{\Omega_r}$

Thus

$$P_r = \frac{e_r e_t \lambda^2 P_t}{\Omega_T \Omega_r r^2}$$

For a conical beam with half-angle n :

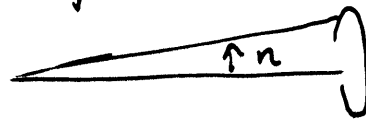

$$\Omega = 2\pi(1 - \cos n)$$

Both antennas have $n = 1.5^\circ$

$$\Omega_T = \Omega_r = 2\pi(1 - \cos 1.5^\circ) = 2.153 \times 10^{-3} \text{ steradians}$$

For $f = 10 \text{ GHz}$ $\lambda = \frac{3 \times 10^8}{10 \times 10^9} = 0.030 \text{ m}$

so for $P_r = 10^{-9} \text{ mW}$

$$P_t = \frac{(2.153 \times 10^{-3})^2 (4 \times 10^5)^2 \times 10^{-9}}{e_r e_t (0.03)^2}$$

$$P_t = \frac{0.8241}{e_r e_t} \text{ mW} \approx 1 \text{ mW}$$

TIMED 8.

For a half-wave dipole:

$$P_r = 73.08 I_m^2$$

For an isotropic antenna

$$P = 120\pi I_m^2$$

so $g_D = \frac{120}{73.08}$

For $f = 50 \text{ MHz}$ $\lambda = 6 \text{ m}$, so the ohmic resistance will be small, and is therefore neglected, which is to assume $e = 1$.

TIMED 8 CONTINUED

Then:

$$P_{\max} = \frac{e g_0 P_t}{4 \pi r^2} = \frac{E^2}{120 \pi}$$

and:

$$r^2 = \frac{120 \pi e g_0 P_t}{4 \pi E^2}$$

$$= 30 \times \frac{120}{73.08} \times 1 \times \frac{100}{(10^{-4})^2}$$

and

$$r = 948.7 \text{ Km}$$

TIMED 9.

$$P_{\text{amp}} = \left(\frac{\lambda}{4 \pi r} \right)^2 g_0 r g_0 r P_T$$

$$g_0 = \frac{4 \pi}{\lambda^2} A_{\text{eff}}$$

$$\begin{aligned} \text{so } P_{\text{amp}} &= \frac{\lambda^2}{4^2 \pi^2 r^2} \left(\frac{4 \pi}{\lambda^2} \right)^2 A_{\text{eff}}^2 P_T \\ &= \frac{A_{\text{eff}}^2}{r^2 \lambda^2} P_T \end{aligned}$$

$$\text{or } r = \frac{A_{\text{eff}}}{\lambda} \sqrt{\frac{P_T}{P_{\text{amp}}}}$$

Assume $A_{\text{eff}} = 50\%$ of physical aperture of 0.2 m^2

$$\lambda = \frac{3 \times 10^8}{3 \times 10^9} = 0.1 \text{ so } \frac{A_{\text{eff}}}{\lambda} = 1$$

$$r = \sqrt{\frac{1}{10^{-9}}} = 31.62 \text{ Km.}$$

TIMED 10.

At the first null of the shorted line we find the half wavelength: $\beta l = \pi$, so $\beta = \pi/3 = 60^\circ$

With the antenna connected to the line, the first minimum occurs at the VSWR condition, which is a purely real impedance.

It was given that $R = 73 \Omega$, and X is small. Then:

$$\frac{Z_i}{Z_0} = \frac{R + jX + j \tan \frac{1.6\pi}{3}}{1 + j \frac{R + jX \tan \frac{1.6\pi}{3}}{Z_0}}$$

$$\frac{1.6\pi}{3} = 1.6 \times 60 = 96^\circ$$

$\frac{Z_i}{Z_0}$ is a real number,

so the angles of the numerator and denominator must be equal:

TIMED 10 CONTINUED

$$\frac{\tan 96^\circ + (X/Z_0)}{(R/Z_0)} = \frac{(R/Z_0) \tan 96^\circ}{1 - (X/Z_0) \tan 96^\circ}$$

From which:

$$\left(\frac{X}{Z_0}\right)^2 + \frac{\tan^2 96^\circ - 1}{\tan 96^\circ} \left(\frac{X}{Z_0}\right) - \left[1 - \left(\frac{R}{Z_0}\right)^2\right] = 0$$

$$\text{with } R/Z_0 = 73/75$$

this is solved using the quadratic formula

$$\frac{X}{Z_0} = 4.7046 \pm \sqrt{4.7046^2 + \left\{1 - \left(\frac{73}{75}\right)^2\right\}}$$

as X was made small by tuning, the minus sign is appropriate and:

$$\frac{X}{Z_0} = -5.5893 \times 10^{-3}$$

In order that the amplifier appear as the complex conjugate of the antenna impedance:

$$\frac{Z_{ant}}{Z_0} = \frac{73}{75} - j5.5893 \times 10^{-3}$$

The amplifier must have the same impedance as the minimum seen from the transmission line:

$$\frac{Z_{min}}{Z_0} = \frac{R/Z_0}{1 - \frac{X}{Z_0} \tan 96^\circ} = 1.028$$

Then with a transmission line of 1.6 meters this impedance seen from the antenna will be:

$$\begin{aligned} \frac{Z}{Z_0} &= \frac{1.028 + j \tan 96^\circ}{1 + j1.028 \tan 96^\circ} \\ &= 0.9733 + j5.589 \times 10^{-3} \end{aligned}$$

$$Z = 73.00 + j0.4192$$

which is the desired complex conjugate.