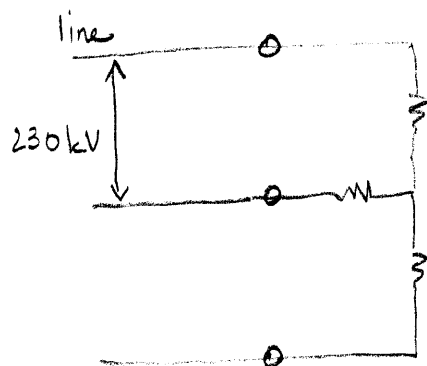


Chapter 5 Power Systems.

Delta

1. A 230 kV (line-to-line), three phase system delivers 200 MVA to a balanced load with a 0.9 power factor (lagging). Determine the line current and the reactance necessary to achieve unity power factor.



$$I_{\text{phase}} = \frac{|S|}{3V} = \frac{(200 \times 10^6)}{3 \times 230 \times 10^3}$$

$$P_{\text{total}} = \sqrt{3} V_{\text{L-L}} |I_L| \cos \theta$$

do single line analysis since balanced.

$$\text{apparent power/phase} = \frac{200 \text{ MVA}}{3}$$

$$\text{line current} = \text{phase current} = \frac{\text{apparent power/phase}}{\text{phase voltage}}$$

(wye)

$$S_{\text{phase}} = \frac{200 \text{ MVA}}{3}$$

$$|I_{\text{phase}}| = \frac{S_{\text{phase}}}{V_{\text{line}}} = \frac{\frac{1}{3}(200 \times 10^6)}{(230 \times 10^3)} = 289.9 \text{ A.}$$

use line-line? Not sure.

$$|I_{\text{line}}| = \sqrt{3} |I_{\text{phase}}| = \sqrt{3} (289.9) = 502 \text{ A.}$$

Correct on a phase basis.

$$I_{\text{phase}} = I_p + j I_q$$

$$I_p = |I_{\text{phase}}| \cos \theta = 289.9 (0.9) = 260.9 \text{ A}$$

$$I_q = |I_{\text{phase}}| \sin \theta = 289.9 \sin(-25.8^\circ) = -126.4 \text{ A}$$

to cancel out reactive current

$$I_{\text{comp}} = +j 126.4 \text{ Amps.}$$

$$= \frac{V}{Z} = \frac{230 \times 10^3}{-j X_c} = \frac{230 \times 10^3}{-j X_c} = +j 126.4$$

$$X_c = \frac{230 \times 10^3}{126.4} = 1820 \Omega.$$



2. A 13.8 kV single phase transformer is subjected to an open circuit test with the following results:

$$P_{in} = 900 \text{ Watts.}$$

$$I_{in} = 0.2 \text{ A.}$$

$$V_{out} = 460 \text{ V (secondary).}$$

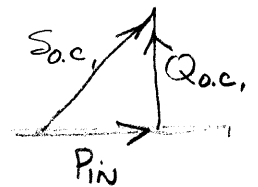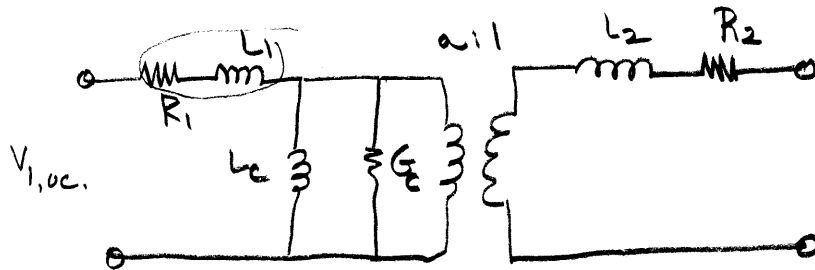Determine the values of the equivalent circuit parameters which can be found from this test.



since open circuit primary winding impedance is negligible, i.e., R_1, L_1 is negligible

apparent power ~~is~~ $S_{oc} = V_{1,oc} I_{1,oc} = (13.8 \times 10^3)(0.2)$

~~reactive power~~

reactive power $Q_{oc}^2 = S_{oc}^2 - P_{oc}^2$ ^{apparent power} _{power, real} $= (13.8 \times 10^3 \times 0.2)^2 - (900)^2 = 2609 \text{ Var.}$

real power dissipated in G_c

$$G_c = \frac{P_{oc}}{V_{1,oc}^2} = \frac{900}{(13800)^2} = 4.73 \times 10^{-6} \text{ S}$$

$$B_c = \frac{\pm Q_{oc}}{V_{1,oc}^2} = \frac{2609}{(13800)^2} = 13.7 \times 10^{-6} \text{ S}$$

technically negative

voltage is easy.

$$\frac{N_P}{N_S} = \frac{V_P}{V_S} = \frac{13800}{460} = 30.$$

3, A 32 kVA single phase transformer is rated at 1.5 kW on the primary, A 60 Hz short circuit test on the primary indicates

$$P_{sc} = 1 \text{ kW}$$

$$I_{sc} = 20 \text{ A}$$

$$I_{sec} = 100 \text{ A}$$

$$V_{pri} = 80 \text{ V}$$

Determine the winding resistances and the leakage inductances,

Conducted at rated current of winding to which voltage is applied.

$$N_p I_p = N_s I_s$$

$$a = \frac{N_p}{N_s} = \frac{I_s}{I_p} = \frac{100 \text{ A}}{20 \text{ A}} = 5$$

$$P_{sc} = I_{sc}^2 (R_p + a^2 R_s)$$

$$\therefore R_p + a^2 R_s = \frac{P_{sc}}{I_{sc}^2} = \frac{1000 \text{ W}}{(20)^2} = 2.5 \Omega$$

for efficiency $R_p = a^2 R_s = \frac{2.5}{5} = 1.25 \Omega$

$$\therefore R_p = 1.25 \Omega$$

$$R_s = \frac{1.25}{5^2} = 0.05 \Omega$$

determine the apparent and reactive power.

$$I_{rated} = \frac{32000 \text{ VA}}{1500}$$

$$|S| = V_p I_p = (80 \text{ V})(20) = 1600 \text{ VA}$$

$$S = P + jQ \quad Q = \sqrt{S^2 - P^2} = \sqrt{(1600)^2 - (1000)^2} = 1249$$

inductive