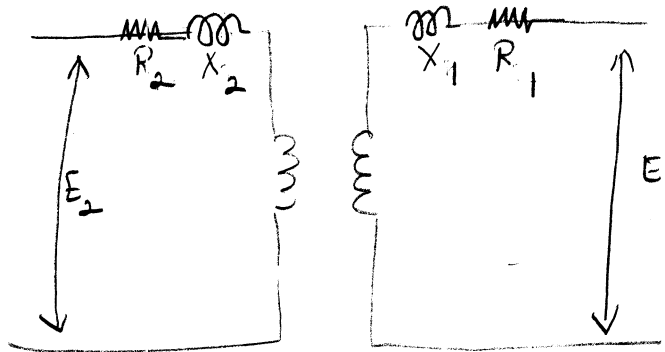




500kVA xfr
 13,200 : 2400
 4% reactance
 1% resistance

leakage reactance 0.250 Ω
 resistance = 0.055 Ω

core loss
 @ rating = 1800 w.

(a) Neglecting xfr losses, unity power factor

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

in this case $\frac{E_2}{E_1} = \frac{13200}{2400} = 5.5,$

$$R_{02} = R_2 + R_1 n^2$$

$$X_{02} = X_2 + X_1 n^2$$

$$Z_{02} = \sqrt{R_{02}^2 + X_{02}^2}$$

$$\frac{Z_{01}}{Z_{02}} = n^2 = \left(\frac{N_1}{N_2} \right)^2$$

$$I_2 = \frac{\text{kva rated} \times 1000}{E_2} = \frac{500 \times 1000}{13200} = 37.9 \text{ amp.}$$


$$R_{02} = .01 \left(\frac{13200 \text{ V}}{37.9 \text{ A}} \right) = 3.48 \Omega$$

$$X_{02} = .04 \left(\frac{13200 \text{ V}}{37.9 \text{ A}} \right) = 13.92 \Omega$$

use load rating
use load rating

500 kVA
11,000 : 2300

Transformers-1
See Constance p.255

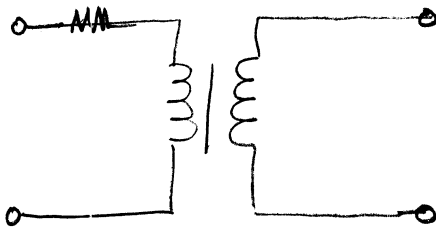

open circuit test $E = 2300$ $I = 2.3 A$, $P = 4000$ watts
short circuit test $E = 600$ $I = 45.4 A$, $P = 6000$ watts.
(secondary shorted) P_{pri} P_{pri} P_{pri}

(a) copper loss

6000 watts.

(b) equivalent resistance referred to the primary

$$R_{01} = \frac{P_{short}}{I_{short}^2} = \frac{6000}{(45.4)^2} = 2.92 \Omega$$

(c) equivalent resistance referred to secondary.

$$R_{02} = 2.92 \times \left(\frac{2300}{11000}\right)^2 = 0.129 \Omega$$

(d) equivalent impedance referred to the primary

$$Z_{01} = \frac{E_1}{I_1} = \frac{600 V}{45.4 A} = 13.2 \Omega$$

(e) equivalent reactance referred to the secondary

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{(13.2)^2 - (2.92)^2} = 12.8 \Omega$$


$$X_{02} = 12.8 \times \left(\frac{2300}{11000}\right)^2 = 0.563 \Omega$$

(f) regulation at 0.8 power factor rating

$$E_1 = \sqrt{\left(\frac{11,000 \times 0.8}{V} + \frac{45.5 \times 2.92}{i} \underbrace{\hspace{1cm}}_{\text{resistance}}\right)^2 + \left(\frac{11,000 \times 0.6}{V} + \frac{45.5 \times 12.8}{i} \underbrace{\hspace{1cm}}_{\text{reactance}}\right)^2}$$

$$E_1 = 11,500$$
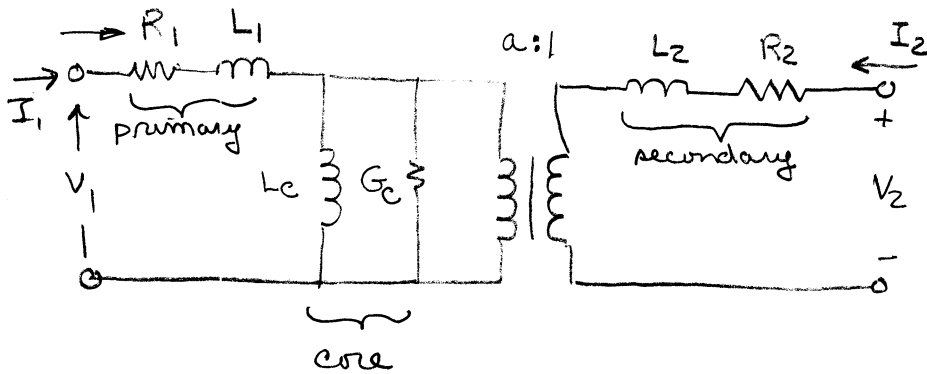
$$\text{Regulation} = \frac{11,500 - 11,000}{11,000} \times 100 = 4.56\%$$



(a) open circuit test

- always performed at rated winding voltage
- transformers with HV primary, LV secondary, usually measure secondary (in this case, put core impedances on secondary)

in open circuit test, primary winding impedance can be neglected

primary V, I, P measurements determine G_c and L_c or X_c

$$Y_{\text{open circuit}} = G_c - jB_c$$

$$\text{The susceptance } B_c = \frac{1}{X_c} = \frac{1}{\omega L_c}$$

open circuit power

$$\text{real power} \rightarrow P_{oc} = V_{oc}^2 G_c \Rightarrow G_c = \frac{P_{oc}}{V_{1,oc}^2}$$


$$S_{oc} = V_{1,oc}^2 Y_c = V_{1,oc}^2 (G_c - jB_c)$$

$$Q_{oc}^2 = S_{oc}^2 - P_{oc}^2 \quad Q_{oc} = V_{1,oc}^2 B_c$$

$$\text{Imaginary power} \Rightarrow B_c = \frac{\sqrt{S_{oc}^2 - P_{oc}^2}}{V_1^2}$$

$$a_{pe} = \frac{V_{1,oc}}{V_{2,oc}} \Big|_{I_2=0}$$

open circuit test example:

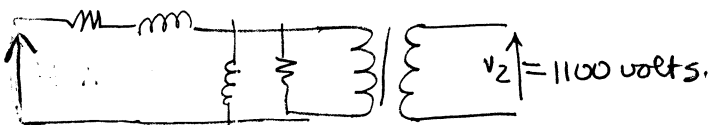

$$P = 100 \text{ watts}$$

$$I = 1 \text{ amp}$$


$$S = (440)(1) = 440 \text{ VA}$$

$$Q^2 = (440)^2 - (100)^2 = (428.5)^2$$

$$G_c = \frac{100}{440^2} = .00052 \text{ S}$$

$$B_c = -\frac{428}{440^2} = -.00221 \text{ S}$$

$$a_{pe} = \frac{440}{1100} = 0.4$$

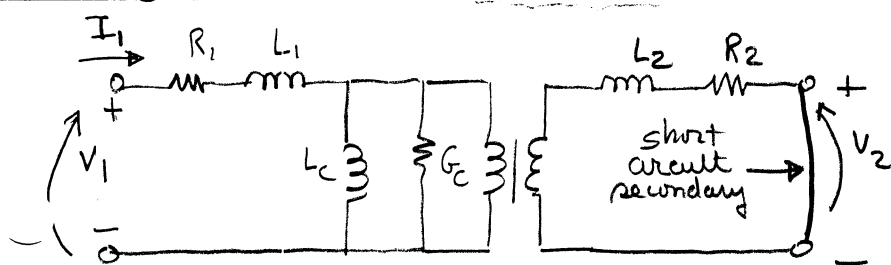

Transformers - 3

SHORT CIRCUIT TEST

- used to determine winding impedances
- always conducted at rated current of winding
- shorting secondary shorts out core effects leaving $Z_{pri} + \text{transformed } Z_{sec}$.

$$Z_{s.c.} = R_1 + jX_1 + a_{ps}^2 (R_2 + jX_2)$$

- measure primary V_{sc}, I_{sc}, P_{sc}

$$V_{sc} I_{sc} = I_{sc}^2 Z = I_{sc}^2 (R_1 + a_{ps}^2 R_2) + j I_{sc}^2 (X_1 + a_{ps}^2 X_2)$$

$$\text{but } P_{sc} = I_{sc}^2 (R_1 + a_{ps}^2 R_2)$$

$$\begin{matrix} \uparrow \\ \text{real} \end{matrix} \Rightarrow R_1 + a_{ps}^2 R_2 = \frac{P_{sc}}{I_{sc}^2}$$

imaginary power,


$$Q_{sc}^2 = S_{sc}^2 - P_{sc}^2 = I_{sc}^2 (X_1 + a_{ps}^2 X_2)$$

$$\Rightarrow X_1 + a_{ps}^2 X_2 = \frac{\sqrt{V_{sc}^2 I_{sc}^2 - P_{sc}^2}}{I_{sc}^2}$$

$$R_1 = a_{ps}^2 R_2 = \frac{P_{sc}}{2 I_{sc}^2} \quad X_1 = a_{ps}^2 X_2 = \frac{Q_{sc}}{2 I_{sc}^2}$$

$$a_{ps} = \frac{I_{2,sc}}{I_{1,sc}}$$

Example:

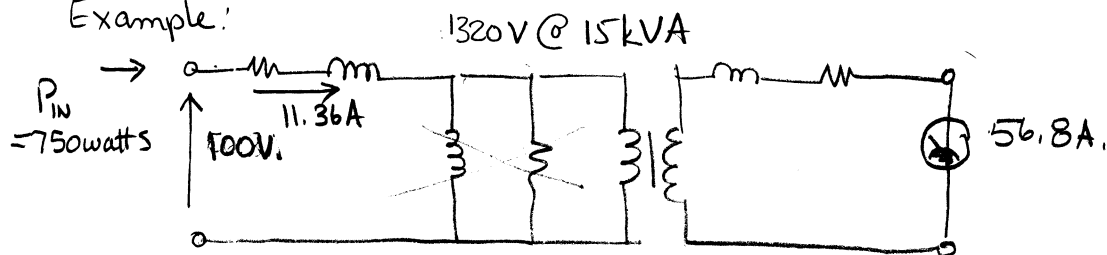

$$I_{rated} = \frac{15 \text{ KVA}}{1.320 \text{ kV}} = 11.36 \text{ A}$$

$$\text{apparent power } S = (11.36 \text{ A})(100 \text{ V}) = 1136 \text{ VA}$$

$$Q = \sqrt{(1136)^2 - (750)^2} = 853 \text{ VAR}$$

$$R_1 = a_{ps}^2 R_2 = \frac{750}{2(11.36)^2} = 2.9 \Omega$$

$$X_1 = a_{ps}^2 X_2 = \frac{853}{2(11.36)^2} = 3.3 \Omega$$

$$a_{ps} = \frac{I_{2,sc}}{I_{1,sc}} = \frac{56.8}{11.36}$$

$$a_{ps} = 5$$