

SOLUTIONS

$$\frac{1}{7-15} \left(\frac{d}{dt} v(t) + 200v(t) = v_s(t) = 25 \cos(100t) \text{ V} \right. \\ \left. v(0) = 0 \text{ V} \right)$$

$$v(t) = v_N(t) + v_F(t) \\ v_N(t) = K e^{-\frac{t}{\tau_c}}$$

rewrite original equation

$$\underset{\substack{\uparrow \\ T_c}}{\frac{1}{200}} \frac{d}{dt} v(t) + v(t) = \underset{\substack{\uparrow \\ V_A}}{\frac{1}{8}} \cos(\underset{\substack{\uparrow \\ \omega}}{100t}) \text{ V}$$

$$v_N = K e^{-200t}$$

$$v_F = \frac{V_A}{1 + (\omega T_c)^2} [\cos(\omega t) + \omega T_c \sin(\omega t)]$$

$$= \frac{\frac{1}{8}}{1 + (\frac{1}{2})^2} [\cos(100t) + \frac{1}{2} \sin(100t)]$$

$$= \frac{1}{8 + 8 \cdot \frac{1}{4}} [\cos(100t) + \frac{1}{2} \sin(100t)]$$

$$= \frac{1}{10} [\cos(100t) + \frac{1}{2} \sin(100t)]$$

$$v(t) = K e^{-200t} + \frac{1}{10} [\cos(100t) + \frac{1}{2} \sin(100t)] \\ v(0) = 0 = K + \frac{1}{10} \\ K = -\frac{1}{10}$$

$$v(t) = -\frac{1}{10} e^{-200t} + \frac{1}{10} [\cos(100t) + \frac{1}{2} \sin(100t)]$$

2
7-18)

2
0 F
5

before $t=0$, inductor behaves as short:



$$i_L(t) = \frac{V}{R} = \frac{5V}{1k\Omega}$$

$$i_L(0) = 5mA$$

after time $t=0$:



as $t \rightarrow \infty$, inductor will again be short:


$$i_L(\infty) = \frac{5V}{5k\Omega} = 1mA$$

$$i_L(t) = FC + (IC - FC)e^{-t/\tau_c}$$

$$= 1mA + (4mA)e^{-\frac{t}{20\mu s}}$$



$$\tau_c = \frac{L}{R} = \frac{100mH}{5k\Omega} = 20\mu s$$

$$i_L(t) = 1mA + 4mA e^{-50,000 t/s}$$

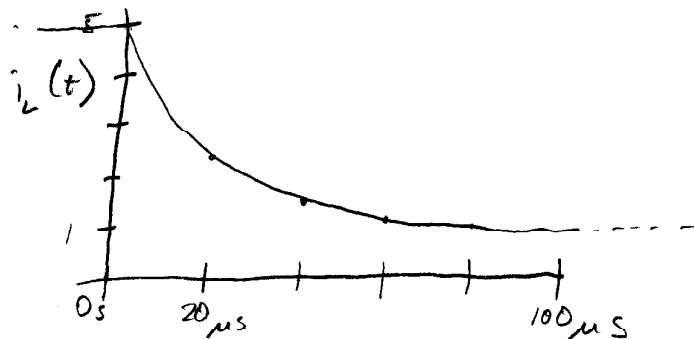

3
7-21) by $t=0$, capacitor is at $V_c(0)=0V$
(can discharge through $15k\Omega$ resistor)

for $0 \leq t \leq 2ms$:

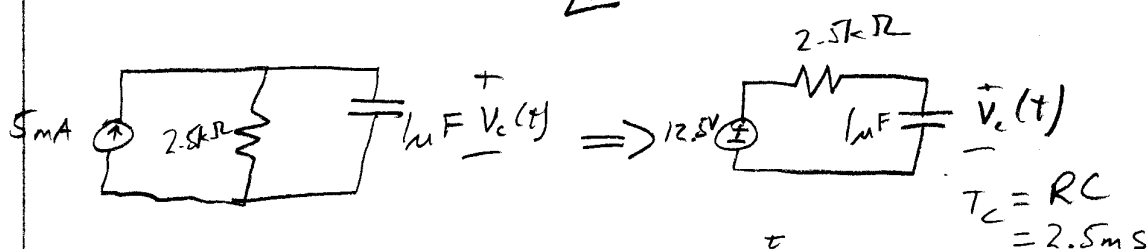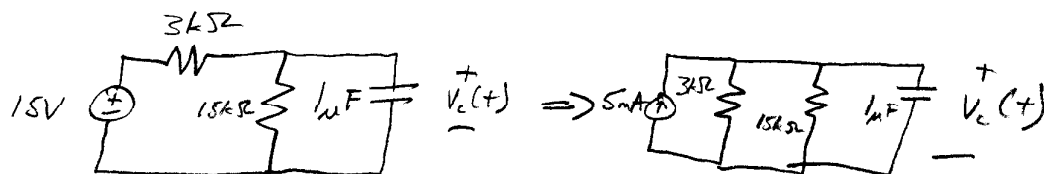

$$V_c(t) = 12.5V + 12.5V e^{-\frac{t}{2.5ms}}$$

at $t=2ms$:

$$V_c(0.002) = 12.5V - 12.5V e^{-\frac{2}{2.5}} \\ \approx 6.88V$$

$t > 2ms$:



$$V_c(t) = \left(12.5V - 12.5V e^{-\frac{2}{2.5}} \right) e^{-\frac{(t-0.002s)}{15ms}}$$

$$V_c(t) = \left(12.5V - 12.5V e^{-0.8} \right) e^{\frac{0.002s - t}{15ms}} \\ \approx 6.88V e^{0.133 - 66.7t/s}$$

4
7-23) a) $T_c = \frac{1}{1000} = 0.001 \text{ s} = \boxed{1 \text{ ms} = T_c}$

b) state variable is $v_c(t)$
 $\boxed{v_c(0) = 10 \text{ V}}$

c) $i_c(t) = C \frac{d}{dt} v_c(t)$
 $-20e^{-1000t} \text{ mA} = C \cdot -1000/s \cdot 10e^{-1000t} \text{ V}$
 $\frac{2}{1000} \frac{\text{mA} \cdot \text{s}}{\text{V}} = C$
 $\boxed{2 \mu\text{F} = C}$
 $R = \frac{T_c}{C} = \frac{1 \text{ ms}}{2 \mu\text{F}} = 500 \Omega$

d) $w_c(t) = \frac{1}{2} C v_c^2(t)$
 $v_c(t) = 10e^{-1000t}$
 $v_c(1 \text{ ms}) = 10e^{-1}$
 $= 3.68 \text{ V}$
 $= \frac{1}{2} \cdot 2 \mu\text{F} \cdot (3.68 \text{ V})^2$
 $\boxed{w_c(1 \text{ ms}) = 13.5 \mu\text{J}}$

5
8-4) $2V_1 + V_2 = 20e^{-j30^\circ} + 60e^{-j220^\circ}$
 $= 20 \cos(30^\circ) - j20 \sin(30^\circ) + 60 \cos(220^\circ) + j60 \sin(220^\circ)$
 $= 28.6 - j28.6 + 60 \cos(220^\circ) + j60 \sin(220^\circ)$
 $= 40.5 e^{j135^\circ}$

$\boxed{2v_1(t) + v_2(t) = 40.5 \cos(10^4 \omega t + 135^\circ)}$

b) $I_1 + 3I_2 = 5e^{j90^\circ} + 3 \cdot 2e^{j270^\circ}$
 $= 5e^{j90^\circ} + 6e^{j270^\circ}$
 $= 5 \cos 90^\circ + j5 \sin 90^\circ + 6 \cos 270^\circ + j6 \sin 270^\circ$
 $= -j5$
 $= e^{-j90^\circ}$

$\boxed{i_1(t) + 3i_2(t) = \cos(200t - 90^\circ)}$

6
8-6)

$$a) \quad V_1 = 10 + j40 \\ = 10\sqrt{17} e^{j76^\circ}$$

$$v_1(t) \approx 41.2 \cos(10t + 76^\circ)$$

$$b) \quad V_2 = (8 - j3) 5 e^{-60^\circ} \\ = \sqrt{73} e^{-j20.6^\circ} \cdot 5 e^{-60^\circ}$$

$$= 5\sqrt{73} e^{-j80.6^\circ}$$

$$v_2(t) = 42.7 \cos(20t - 80.6^\circ)$$

$$c) \quad \underline{H}_1 = 8 - j3 + \frac{3}{j} \\ = 8 - j3 - j3 \\ = 8 - 6j \\ = 10 e^{-j36.9^\circ}$$

$$i_1(t) = 10 \cos(300t - 36.9^\circ)$$

$$d) \quad \underline{H}_2 = \frac{3 + j}{1 - j3} \\ = \frac{\sqrt{10} e^{j18.4^\circ}}{\sqrt{10} e^{-j71.6^\circ}} \\ = e^{j90^\circ}$$

$$i_2(t) = \cos(50t + 90^\circ)$$

5
5
5