
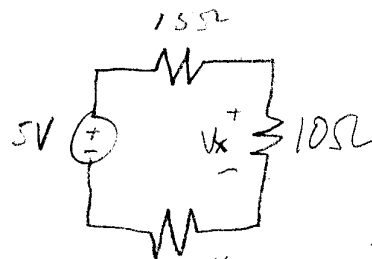


ENGR 210
Fall 2003
Homework #3
SOLUTIONS

1
of
4

1
2-42)

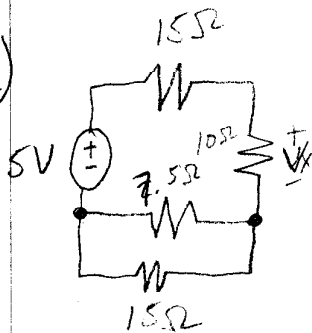

$$7.5\Omega \parallel 15\Omega = \frac{7.5\Omega \cdot 15\Omega}{7.5\Omega + 15\Omega} = 5\Omega$$



by Voltage division:

$$V_x = V_s \frac{R_x}{\Sigma R}$$

$$= 5V \cdot \frac{10\Omega}{15\Omega + 10\Omega + 5\Omega}$$

$$V_x = 1.67V$$

2
2-50)

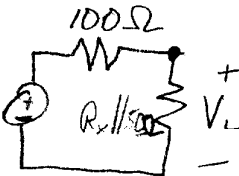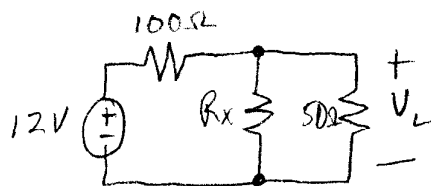

Voltage division: $V_L = 12V \cdot \frac{R_x \parallel 50\Omega}{100\Omega + R_x \parallel 50\Omega}$
need $V_L = 3V$ $3V = 12V \cdot \frac{R_x \cdot 50\Omega}{R_x + 50\Omega} \cdot \frac{1}{100\Omega + \frac{R_x \cdot 50\Omega}{R_x + 50\Omega}}$

$$.25 = \frac{R_x \cdot 50\Omega}{100R_x + 5000(\Omega^2) + R_x \cdot 50\Omega}$$

$$= \frac{R_x}{2R_x + 100\Omega + R_x}$$

$$= \frac{100\Omega + 5R_x}{100\Omega + 5R_x}$$


$$25\Omega + .75R_x = R_x$$

$$25\Omega = .25R_x$$

$$100\Omega = R_x$$


2
of
4

3
2.55)

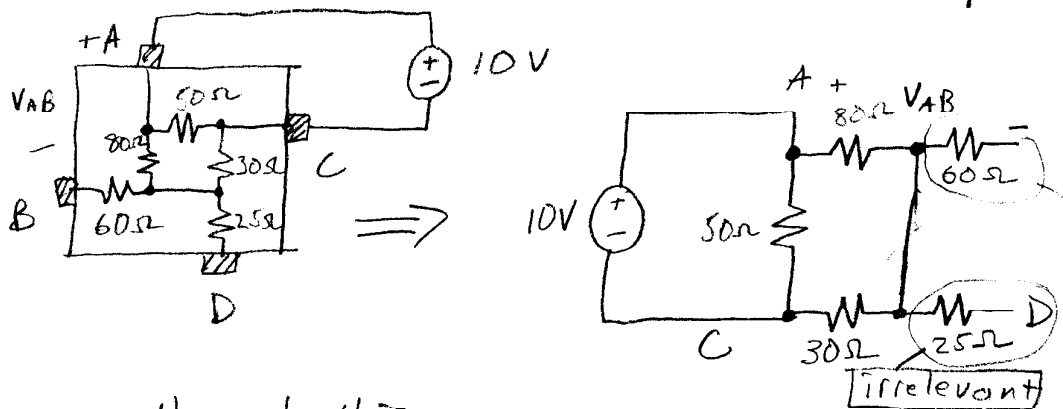

current through this resistor is 0, $\therefore$ voltage across it is also 0,
 $\therefore V_{AB}$ is voltage across 80Ω resistor

redrawn:

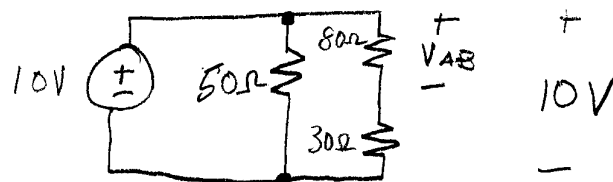


can do voltage division on right branch:

$$V_{AB} = 10V \cdot \frac{80\Omega}{80\Omega + 30\Omega}$$

$$V_{AB} = 7.27V$$

2-62) a)

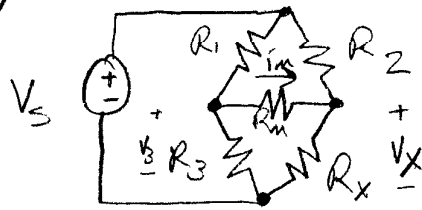

given $i_m = 0$
 $\therefore V_3 = V_x$

voltage division: (ONLY works here since $i_m = 0$!!)

$$V_3 = V_s \frac{R_3}{R_1 + R_3}$$

$$V_x = \frac{R_x}{R_2 + R_x} \cdot V_s$$

$$V_s \frac{R_3}{R_1 + R_3} = V_s \frac{R_x}{R_2 + R_x}$$

$$R_2 R_3 + R_3 R_x = R_1 R_x + R_3 R_x$$

$$R_2 R_3 = R_1 R_x$$

b) given $R_1 = R_2 = R_{upper} = 2.2 \text{ k}\Omega$

$$i_m = 0$$

$$T = 57.5^\circ \text{C}$$

want R_3

$$\rightarrow R_x \approx 2.2 \text{ k}\Omega \text{ (2.15 k}\Omega \text{?)}$$

$$R_2 R_3 = R_1 R_x$$

$$R_{upper} R_3 = R_{upper} \cdot 2.2 \text{ k}\Omega$$

$$R_3 = 2.2 \text{ k}\Omega$$

2-62 continued...

c) given $i_m < 0$
 implies $V_x > V_3$
 R_3 set to $2.2 \text{ k}\Omega$
 implies $R_x > 2.2 \text{ k}\Omega$
 $\therefore \boxed{T > 57.5^\circ\text{C}}$

d) $R_1 = R_2 = R_{\text{upper}} = 2.2 \text{ k}\Omega$
 $R_3 = 2.4 \text{ k}\Omega$

$$R_2 R_3 = R_1 R_x$$

$$R_{\text{upper}} \cdot 2.4 \text{ k}\Omega = R_{\text{upper}} \cdot R_x$$

$$R_x = 2.4 \text{ k}\Omega$$

$$\boxed{T = 62.5^\circ\text{C}}$$

3-2) a) Node A: $V_A \left(\frac{1}{20\Omega} + \frac{1}{10\Omega} + \frac{1}{4\Omega} \right) - V_B \cdot \frac{1}{4\Omega} = 7\text{A}$
 " B: $-V_A \cdot \frac{1}{4\Omega} + V_B \left(\frac{1}{8\Omega} + \frac{1}{4\Omega} \right) = 3.5\text{A} - 7\text{A} = -3.5\text{A}$

V_B rewrite so
 coeff. is 1

$$\begin{aligned} \text{A: } 1.6V_A - V_B &= 28\text{V} \\ \text{B: } -.667V_A + V_B &= -9.33\text{V} \end{aligned}$$

$$\begin{aligned} \text{Sum: } .933V_A &= 18.7\text{V} \\ V_A &= 20\text{V} \end{aligned}$$

$$\begin{aligned} \text{A: } (.4V_A - .25V_B) &= 7\text{A} \\ \text{B: } (-.25V_A + .375V_B) &= -3.5\text{A} \end{aligned}$$

$$\begin{aligned} V_B &= .667V_A - 9.33\text{V} \\ &= 4\text{V} \end{aligned}$$

b) $\bar{I}_x = \frac{V_A}{20\Omega}$
 $\boxed{\bar{I}_x = 1\text{A}}$

$$V_x = V_B$$

$$\boxed{V_x = 4\text{V}}$$