

SOLUTIONS

$$6-2) \quad w(t) = \frac{1}{2} C [v_C(t)]^2$$

$$v_C(t) = 15 \cos(2\pi \cdot 1000t)$$

$$v_C(0.0005) = 15 \cos(2\pi \cdot 0.5)$$

$$= 15 \cos(\pi)$$

$$= -15V$$

$$w(0.0005) = \frac{1}{2} \cdot 3.3 \mu F \cdot (-15V)^2$$

$$w(0.5ms) = 371.25 \mu J$$

$$v_C(0.75ms) = 0V$$

$$w(0.75ms) = 0J$$

$$v_C(1ms) = 15V$$

$$w(1ms) = 371.25 \mu J$$

$$6-8) \quad \text{for inductor: } v_L(t) = L \frac{d}{dt} i_L(t) \quad \tau$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(x) dx$$

$$i_L(0) = 1mA$$

$$v_L(t) = 50e^{-5000t} mV$$

$$= .05e^{-5000t} V$$

$$= 1mA + \frac{1}{10mH} \int_0^t .05e^{-5000x} V dx$$

$$= 1mA - \frac{.05V}{50,000mH} [e^{-5000x}]_0^t$$

$$= 1mA - \frac{.05V}{50H} [e^{-5000t} - 1]$$

$$= 1mA - 1mA [e^{-5000t} - 1]$$

$$i_L(t) = 2mA - [e^{-5000t}] mA$$

$$i_L > 0 \text{ for } t > 0$$

$$v_L > 0 \text{ for all } t$$

$$\therefore p > 0 \Rightarrow \boxed{\text{absorbing power}}$$

$$\begin{aligned} 6-14) \quad i_C(t) &= C \frac{d}{dt} v_C(t) \\ &= 10 \mu F \cdot \frac{d}{dt} [50 - 25e^{-5000t}] V \\ &= 10 \mu F \cdot [125,000e^{-5000t}] \frac{V}{s} \end{aligned}$$

$$\boxed{i_C(t) = 1250e^{-5000t} \text{ mA}}$$

$$\begin{aligned} p_C(t) &= i_C(t) v_C(t) \\ &= 1250e^{-5000t} \text{ mA} \cdot [50 - 25e^{-5000t}] V \end{aligned}$$

$$\boxed{p_C(t) = [62.5e^{-5000t} - 31.25e^{-10,000t}] \text{ W}}$$


for $t > 0$, $p_C(t) > 0$, $\therefore$ capacitor is absorbing power

$$\begin{aligned} 6-20) \quad v_L(t) &= L \frac{d}{dt} i_L(t) & L &= 2 \text{ mH} \\ &= 2 \text{ mH} \frac{d}{dt} [100t \cdot e^{-1000t}] A & i_L(t) &= [100t \cdot e^{-1000t}] A \end{aligned}$$

$$\begin{aligned} &= 2 \text{ mH} [100e^{-1000t} - 100,000te^{-1000t}] A \\ \boxed{v_L(t) = [2e^{-1000t} - 200te^{-1000t}] V} & \frac{A}{s} \end{aligned}$$

t	$i_L(t)$	$v_L(t)$	$p_L(t)$
0.5ms	30.3 mA	60.7 mV	absorbing neither delivering
1ms	38.8 mA	0 V	
2ms	27.1 mA	-27.1 mV	

5
6-21)

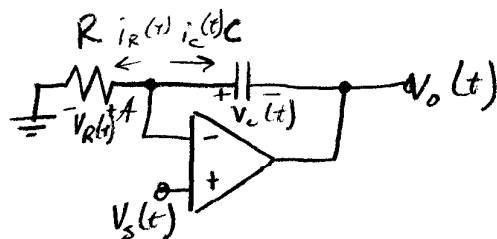

by op-Amp constraints

$$V_A(t) = V_S(t)$$

$$i_R(t) = -i_C(t) \quad (\text{with KCL})$$

$$i_R(t) = \frac{V_A(t)}{R}$$

$$i_R(t) = -i_C(t)$$


$$-\frac{V_A(t)}{R} = C \frac{d}{dt} [V_A(t) - v_o(t)]$$

$$-\frac{V_S(t)}{R} = C \frac{d}{dt} V_A(t) - C \frac{d}{dt} v_o(t)$$

$$\frac{d}{dt} v_o(t) = \frac{d}{dt} V_S(t) + \frac{V_S(t)}{RC}$$

$$v_o(t) - v_o(0) = V_S(t) - V_S(0) + \frac{1}{RC} \int_0^t V_S(x) dx$$

6
6-26)

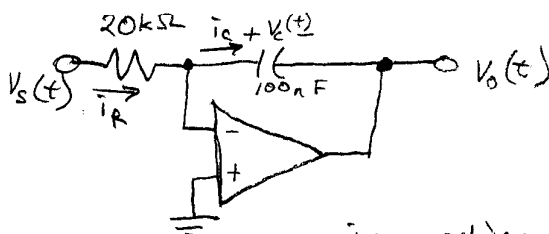

inverting integrator

$$v_o(t) = -\frac{1}{RC} \int_0^t V_S(x) dx$$

$$= -\frac{1}{RC} \int_0^t 5 \sin(\omega x) dx$$

$$= -\frac{5}{\omega RC} [-\cos(\omega x)]_0^t$$

$$= -\frac{5}{\omega RC} [-\cos(\omega t) + 1]$$

$$v_o(t) = -\frac{2500}{\omega} [1 - \cos(\omega t)] V$$

$$\frac{5}{RC} = \frac{5}{20k\Omega \cdot 100nF}$$

$$= \frac{5}{2ms}$$

$$= 2500 s^{-1}$$

largest magnitude occurs when $1 - \cos(\omega t)$
 an extreme, or where $\cos(\omega t) = -1$
 $|v_o(t)|$ must be less than 15V

$$-15V \leq -\frac{2500}{\omega} [1 - (-1)] V \leq 15V$$

$$-15V \leq -5000 s^{-1} V \leq 15V \cdot \omega$$

$$\omega \geq 333 \text{ rad/s}$$

$$\geq -\omega$$

nonsense, ignore