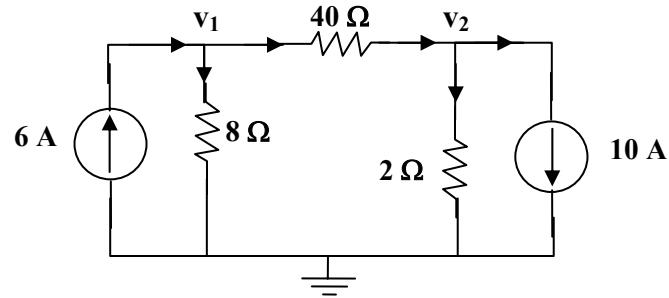


### Chapter 3, Solution 1.



At node 1,

$$6 = v_1/(8) + (v_1 - v_2)/4 \quad 48 = 3v_1 - 2v_2 \quad (1)$$

At node 2,

$$v_1 - v_2/4 = v_2/2 + 10 \quad 40 = v_1 - 3v_2 \quad (2)$$

Solving (1) and (2),

$$v_1 = \underline{9.143} \text{ V}, v_2 = \underline{-10.286} \text{ V}$$

$$P_{8\Omega} = \frac{v_1^2}{8} = \frac{(9.143)^2}{8} = \underline{10.45} \text{ W}$$

$$P_{4\Omega} = \frac{(v_1 - v_2)^2}{4} = \underline{94.37} \text{ W}$$

$$P_{2\Omega} = \frac{v_2^2}{2} = \frac{(-10.286)^2}{2} = \underline{52.9} \text{ W}$$

### Chapter 3, Solution 2

At node 1,

$$\frac{-v_1}{10} - \frac{v_1}{5} = 6 + \frac{v_1 - v_2}{2} \longrightarrow 60 = -8v_1 + 5v_2 \quad (1)$$

At node 2,

$$\frac{v_2}{4} = 3 + 6 + \frac{v_1 - v_2}{2} \longrightarrow 36 = -2v_1 + 3v_2 \quad (2)$$

Solving (1) and (2),

$$v_1 = \underline{0} \text{ V}, v_2 = \underline{12} \text{ V}$$


### Chapter 3, Solution 3

Applying KCL to the upper node,

$$10 = \frac{v_0}{10} + \frac{v_o}{20} + \frac{v_o}{30} + 2 + \frac{v_0}{60} \longrightarrow v_0 = \underline{\underline{40 \text{ V}}}$$

$$i_1 = \frac{v_0}{10} = \underline{\underline{4 \text{ A}}}, i_2 = \frac{v_0}{20} = \underline{\underline{2 \text{ A}}}, i_3 = \frac{v_0}{30} = \underline{\underline{1.33 \text{ A}}}, i_4 = \frac{v_0}{60} = \underline{\underline{67 \text{ mA}}}$$

### Chapter 3, Solution 4

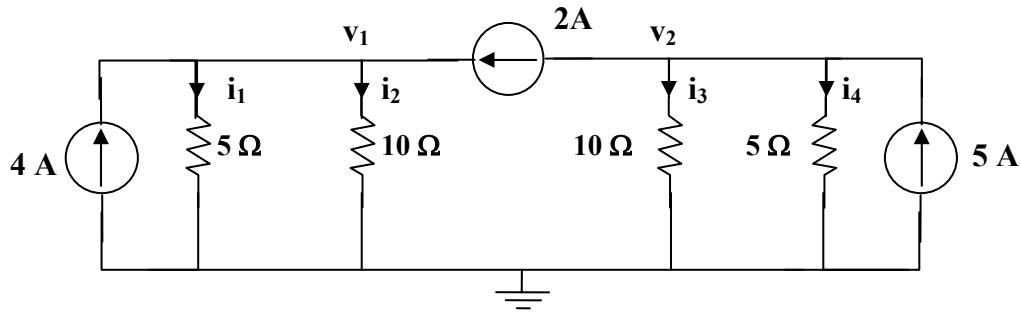

At node 1,

$$4 + 2 = v_1/(5) + v_1/(10) \longrightarrow v_1 = 20$$

At node 2,

$$5 - 2 = v_2/(10) + v_2/(5) \longrightarrow v_2 = 10$$

$$i_1 = v_1/(5) = \underline{\underline{4 \text{ A}}}, i_2 = v_1/(10) = \underline{\underline{2 \text{ A}}}, i_3 = v_2/(10) = \underline{\underline{1 \text{ A}}}, i_4 = v_2/(5) = \underline{\underline{2 \text{ A}}}$$

### Chapter 3, Solution 5

Apply KCL to the top node.

$$\frac{30 - v_0}{2k} + \frac{20 - v_0}{6k} = \frac{v_0}{4k} \longrightarrow v_0 = \underline{\underline{20 \text{ V}}}$$

### Chapter 3, Solution 6

$$i_1 + i_2 + i_3 = 0 \quad \frac{v_2 - 12}{4} + \frac{v_0}{6} + \frac{v_0 - 10}{2} = 0$$

or  $v_0 = \underline{\underline{8.727 \text{ V}}}$

### Chapter 3, Solution 7

At node a,

$$\frac{10 - V_a}{30} = \frac{V_a}{15} + \frac{V_a - V_b}{10} \longrightarrow 10 = 6V_a - 3V_b \quad (1)$$


At node b,

$$\frac{V_a - V_b}{10} + \frac{12 - V_b}{20} + \frac{-9 - V_b}{5} = 0 \longrightarrow 24 = 2V_a - 7V_b \quad (2)$$

Solving (1) and (2) leads to

$V_a = -0.556 \text{ V}, \quad V_b = \underline{\underline{-3.444 \text{ V}}}$

### Chapter 3, Solution 8

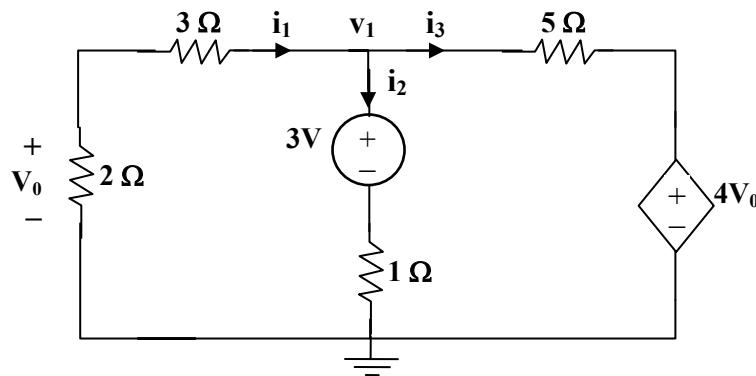


$$i_1 + i_2 + i_3 = 0 \longrightarrow \frac{v_1}{5} + \frac{v_1 - 3}{1} + \frac{v_1 - 4v_0}{5} = 0$$

But  $v_0 = \frac{2}{5}v_1$  so that  $v_1 + 5v_1 - 15 + v_1 - \frac{8}{5}v_1 = 0$

or  $v_1 = 15x5/(27) = 2.778 \text{ V}$ , therefore  $v_0 = 2v_1/5 = \underline{\underline{1.1111 \text{ V}}}$

### Chapter 3, Solution 9

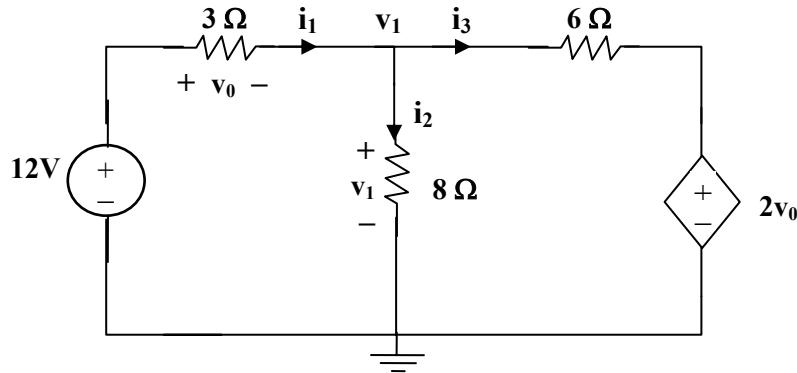

At the non-reference node,

$$\frac{12 - v_1}{3} = \frac{v_1}{8} + \frac{v_1 - 2v_0}{6} \quad (1)$$

But

$$-12 + v_0 + v_1 = 0 \longrightarrow v_0 = 12 - v_1 \quad (2)$$


Substituting (2) into (1),

$$\frac{12 - v_1}{3} = \frac{v_1}{8} + \frac{3v_1 - 24}{6} \longrightarrow v_0 = \underline{\underline{3.652 \text{ V}}}$$
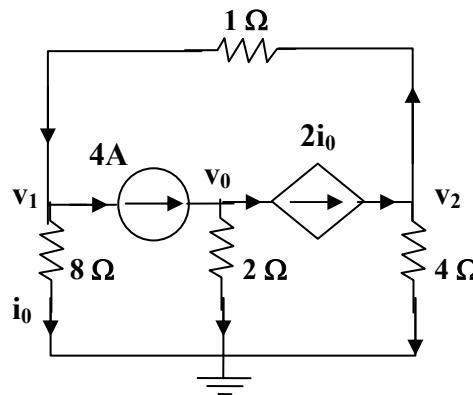
### Chapter 3, Solution 10

At node 1,

$$\frac{v_2 - v_1}{1} = 4 + \frac{v_1}{8} \longrightarrow 32 = -v_1 + 8v_2 - 8v_0 \quad (1)$$



At node 0,

$$4 = \frac{v_0}{2} + 2I_0 \text{ and } I_0 = \frac{v_1}{8} \longrightarrow 16 = 2v_0 + v_1 \quad (2)$$


At node 2,

$$2I_0 = \frac{v_2 - v_1}{1} + \frac{v_2}{4} \text{ and } I_0 = \frac{v_1}{8} \longrightarrow v_2 = v_1 \quad (3)$$

From (1), (2) and (3),  $v_0 = 24$  V, but from (2) we get

$$i_o = \frac{4 - \frac{v_0}{2}}{2} = 2 - \frac{24}{4} = 2 - 6 = \underline{-4 \text{ A}}$$

### Chapter 3, Solution 11

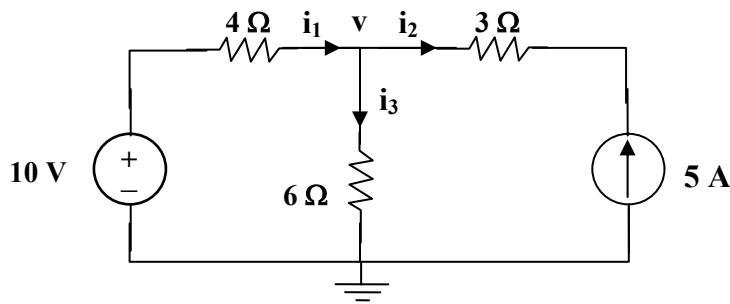


Note that  $i_2 = -5$  A. At the non-reference node

$$\frac{10 - v}{4} + 5 = \frac{v}{6} \longrightarrow v = 18$$

$$i_1 = \frac{10 - v}{4} = \underline{-2 \text{ A}}, i_2 = \underline{-5 \text{ A}}$$

### Chapter 3, Solution 12

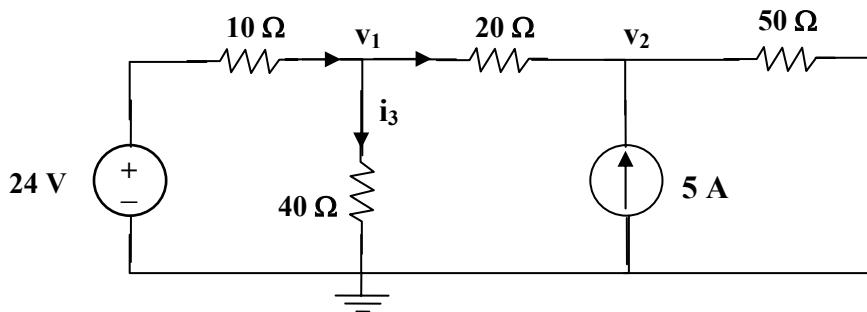

$$\text{At node 1, } \frac{24 - v_1}{10} = \frac{v_1 - v_2}{20} + \frac{v_1 - 0}{40} \longrightarrow 96 = 7v_1 - 2v_2 \quad (1)$$

$$\text{At node 2, } 5 + \frac{v_1 - v_2}{20} = \frac{v_2}{50} \longrightarrow 500 = -5v_1 + 7v_2 \quad (2)$$

Solving (1) and (2) gives,

$$v_1 = 42.87 \text{ V}, v_2 = 102.05 \text{ V}$$


$$i_1 = \frac{v_1}{40} = \underline{\mathbf{1.072 \text{ A}}}, v_2 = \frac{v_2}{50} = \underline{\mathbf{2.041 \text{ A}}}$$

### Chapter 3, Solution 13

At node number 2,  $[(v_2 + 2) - 0]/10 + v_2/4 = 3$  or  $v_2 = \underline{\mathbf{8 \text{ volts}}}$

But,  $I = [(v_2 + 2) - 0]/10 = (8 + 2)/10 = 1 \text{ amp}$  and  $v_1 = 8 \times 1 = \underline{\mathbf{8 \text{ volts}}}$

### Chapter 3, Solution 14

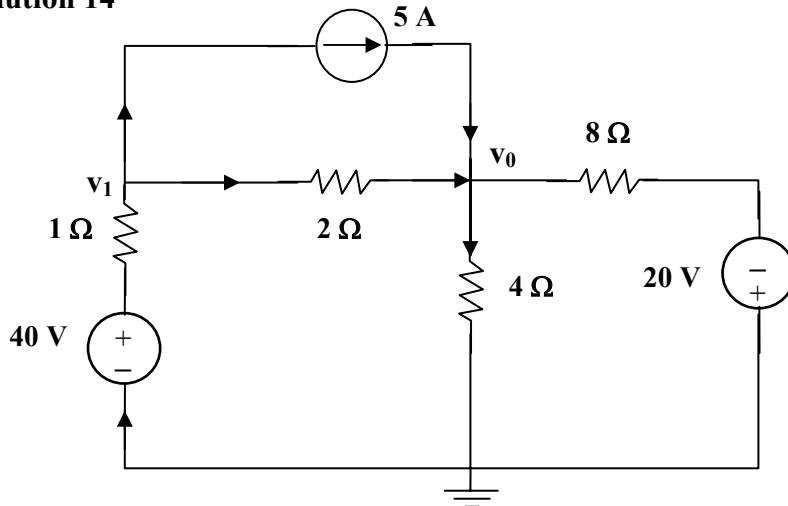


$$\text{At node 1, } \frac{v_1 - v_0}{2} + 5 = \frac{40 - v_0}{1} \longrightarrow v_1 + v_0 = 70 \quad (1)$$

$$\text{At node 0, } \frac{v_1 - v_0}{2} + 5 = \frac{v_0}{4} + \frac{v_0 + 20}{8} \longrightarrow 4v_1 - 7v_0 = -20 \quad (2)$$

Solving (1) and (2),  $v_0 = \underline{\mathbf{20 \text{ V}}}$

**Chapter 3, Solution 15**

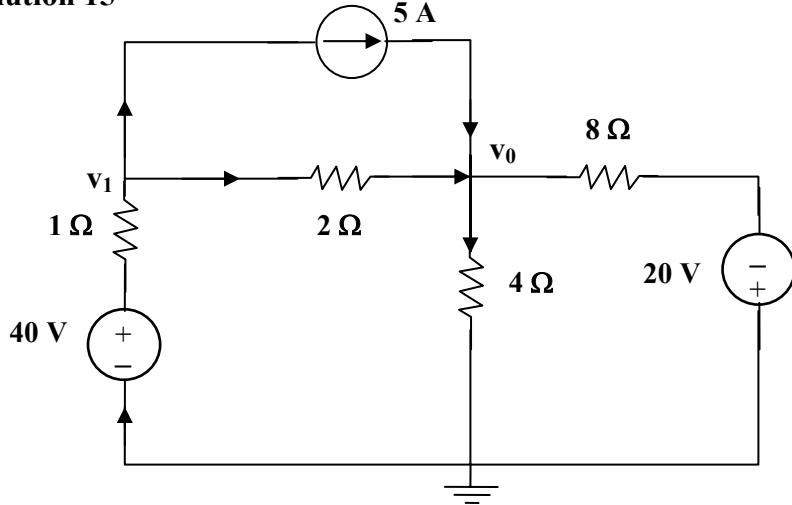

$$\text{Nodes 1 and 2 form a supernode so that } v_1 = v_2 + 10 \quad (1)$$

$$\text{At the supernode, } 2 + 6v_1 + 5v_2 = 3(v_3 - v_2) \longrightarrow 2 + 6v_1 + 8v_2 = 3v_3 \quad (2)$$

$$\text{At node 3, } 2 + 4 = 3(v_3 - v_2) \longrightarrow v_3 = v_2 + 2 \quad (3)$$

Substituting (1) and (3) into (2),

$$2 + 6v_2 + 60 + 8v_2 = 3v_2 + 6 \longrightarrow v_2 = \frac{-56}{11}$$

$$v_1 = v_2 + 10 = \frac{54}{11}$$


$$i_0 = 6v_i = \underline{\underline{29.45 \text{ A}}}$$

$$P_{65} = \frac{v_1^2}{R} = v_1^2 G = \left( \frac{54}{11} \right)^2 6 = \underline{\underline{144.6 \text{ W}}}$$

$$P_{55} = v_2^2 G = \left( \frac{-56}{11} \right)^2 5 = \underline{\underline{129.6 \text{ W}}}$$

$$P_{35} = (v_L - v_3)^2 G = (2)^2 3 = \underline{\underline{12 \text{ W}}}$$

### Chapter 3, Solution 16

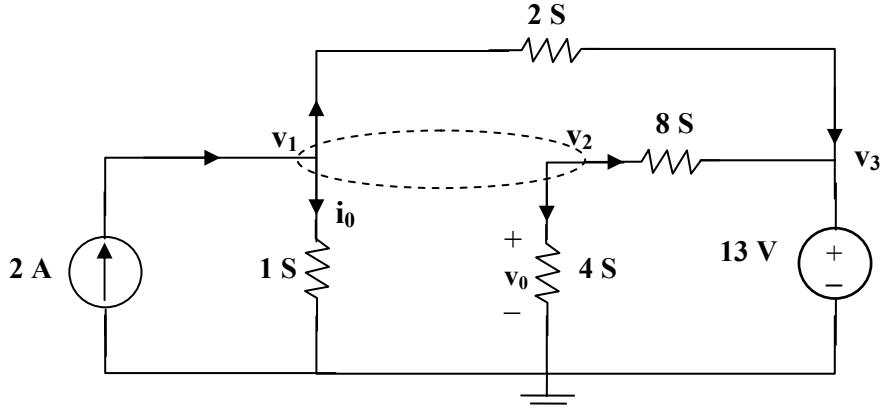

At the supernode,

$$2 = v_1 + 2(v_1 - v_3) + 8(v_2 - v_3) + 4v_2, \text{ which leads to } 2 = 3v_1 + 12v_2 - 10v_3 \quad (1)$$

But

$$v_1 = v_2 + 2v_0 \text{ and } v_0 = v_2.$$

Hence


$$v_1 = 3v_2 \quad (2)$$

$$v_3 = 13V \quad (3)$$

Substituting (2) and (3) with (1) gives,

$$v_1 = \underline{\underline{18.858 \text{ V}}}, \quad v_2 = \underline{\underline{6.286 \text{ V}}}, \quad v_3 = \underline{\underline{13 \text{ V}}}$$

### Chapter 3, Solution 17

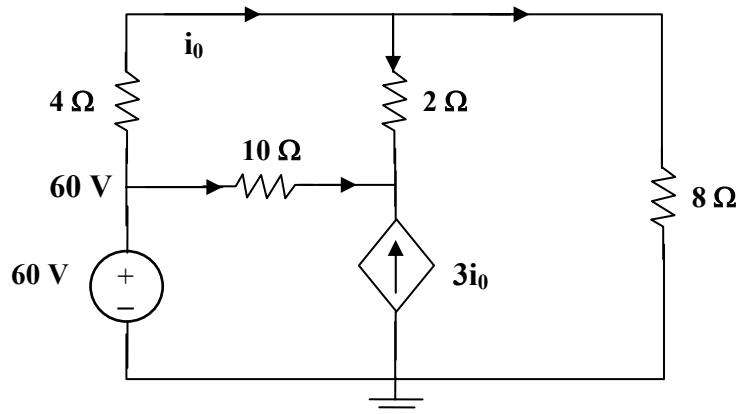

$$\text{At node 1, } \frac{60 - v_1}{4} = \frac{v_1}{8} + \frac{v_1 - v_2}{2} \quad 120 = 7v_1 - 4v_2 \quad (1)$$

$$\text{At node 2, } 3i_0 + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0$$


$$\text{But } i_0 = \frac{60 - v_1}{4}$$

Hence


$$\frac{3(60 - v_1)}{4} + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0 \longrightarrow 1020 = 5v_1 - 12v_2 \quad (2)$$

Solving (1) and (2) gives  $v_1 = 53.08 \text{ V}$ . Hence  $i_0 = \frac{60 - v_1}{4} = \underline{\underline{1.73 \text{ A}}}$

### Chapter 3, Solution 18

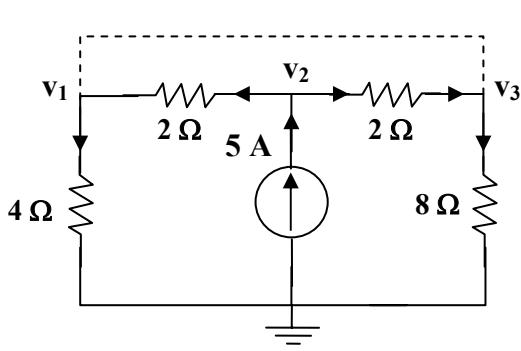

(a)

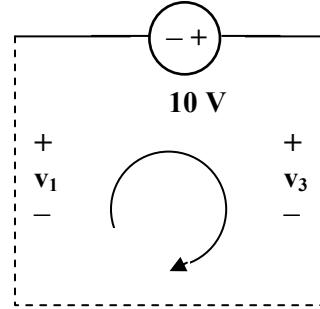

(b)

$$\text{At node 2, in Fig. (a), } 5 = \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{2} \longrightarrow 10 = -v_1 + 2v_2 - v_3 \quad (1)$$

$$\text{At the supernode, } \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{2} = \frac{v_1}{4} + \frac{v_3}{8} \longrightarrow 40 = 2v_1 + v_3 \quad (2)$$

$$\text{From Fig. (b), } -v_1 - 10 + v_3 = 0 \longrightarrow v_3 = v_1 + 10 \quad (3)$$

Solving (1) to (3), we obtain  $v_1 = \underline{\underline{10 \text{ V}}}$ ,  $v_2 = \underline{\underline{20 \text{ V}}} = v_3$

### Chapter 3, Solution 19

At node 1,

$$5 = 3 + \frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{8} + \frac{V_1}{4} \longrightarrow 16 = 7V_1 - V_2 - 4V_3 \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{8} = \frac{V_2}{2} + \frac{V_2 - V_3}{4} \longrightarrow 0 = -V_1 + 7V_2 - 2V_3 \quad (2)$$

At node 3,

$$3 + \frac{12 - V_3}{8} + \frac{V_1 - V_3}{2} + \frac{V_2 - V_3}{4} = 0 \longrightarrow -36 = 4V_1 + 2V_2 - 7V_3 \quad (3)$$

From (1) to (3),

$$\begin{pmatrix} 7 & -1 & -4 \\ -1 & 7 & -2 \\ 4 & 2 & -7 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 16 \\ 0 \\ -36 \end{pmatrix} \longrightarrow AV = B$$


Using MATLAB,

$$V = A^{-1}B = \begin{bmatrix} 10 \\ 4.933 \\ 12.267 \end{bmatrix} \longrightarrow \underline{\underline{V_1 = 10 \text{ V}, V_2 = 4.933 \text{ V}, V_3 = 12.267 \text{ V}}}$$
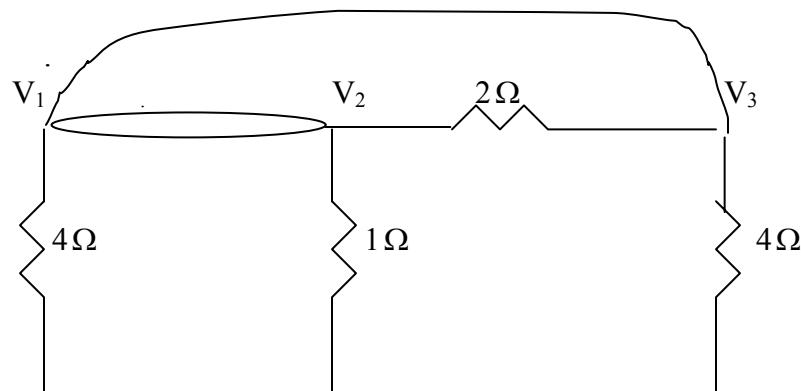
### Chapter 3, Solution 20

Nodes 1 and 2 form a supernode; so do nodes 1 and 3. Hence

$$\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_3}{4} = 0 \longrightarrow V_1 + 4V_2 + V_3 = 0 \quad (1)$$



Between nodes 1 and 3,

$$-V_1 + 12 + V_3 = 0 \longrightarrow V_3 = V_1 - 12 \quad (2)$$

Similarly, between nodes 1 and 2,

$$V_1 = V_2 + 2i \quad (3)$$


But  $i = V_3 / 4$ . Combining this with (2) and (3) gives

$$V_2 = 6 + V_1 / 2 \quad (4)$$

Solving (1), (2), and (4) leads to

$$\underline{V_1 = -3V, V_2 = 4.5V, V_3 = -15V}$$

### Chapter 3, Solution 21

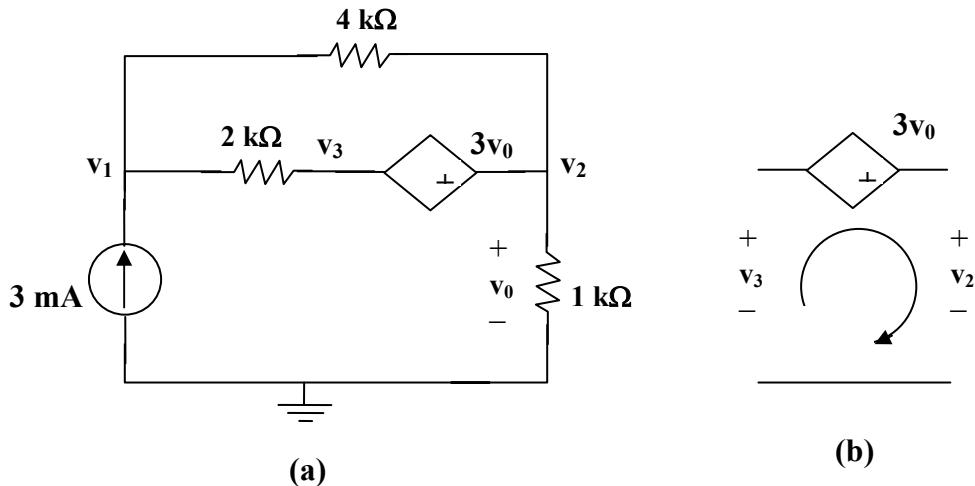

Let  $v_3$  be the voltage between the  $2\text{k}\Omega$  resistor and the voltage-controlled voltage source.

At node 1,

$$3 \times 10^{-3} = \frac{V_1 - V_2}{4000} + \frac{V_1 - V_3}{2000} \longrightarrow 12 = 3V_1 - V_2 - 2V_3 \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_3}{2} = \frac{V_2}{1} \longrightarrow 3V_1 - 5V_2 - 2V_3 = 0 \quad (2)$$

Note that  $v_0 = v_2$ . We now apply KVL in Fig. (b)

$$-v_3 - 3v_2 + v_2 = 0 \longrightarrow v_3 = -2v_2 \quad (3)$$

From (1) to (3),

$$V_1 = \underline{1V}, V_2 = \underline{3V}$$

### Chapter 3, Solution 22

$$\text{At node 1, } \frac{12 - v_0}{2} = \frac{v_1}{4} + 3 + \frac{v_1 - v_0}{8} \rightarrow 24 = 7v_1 - v_2 \quad (1)$$

$$\text{At node 2, } 3 + \frac{v_1 - v_2}{8} = \frac{v_2 + 5v_1}{1}$$

$$\text{But, } v_1 = 12 - v_0$$

$$\text{Hence, } 24 + v_1 - v_2 = 8(v_2 + 60 + 5v_1) = 4 \text{ V}$$

$$456 = 41v_1 - 9v_2 \quad (2)$$

Solving (1) and (2),

$$v_1 = \underline{-10.91 \text{ V}}, \quad v_2 = \underline{-100.36 \text{ V}}$$


### Chapter 3, Solution 23

$$\text{At the supernode, } 5 + 2 = \frac{v_1}{10} + \frac{v_2}{5} \longrightarrow 70 = v_1 + 2v_2 \quad (1)$$


$$\text{Considering Fig. (b), } -v_1 - 8 + v_2 = 0 \longrightarrow v_2 = v_1 + 8 \quad (2)$$

Solving (1) and (2),
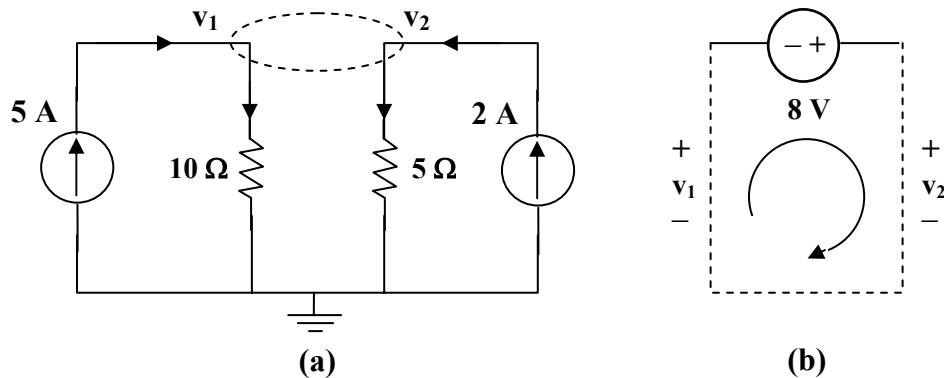
$$v_1 = \underline{18 \text{ V}}, \quad v_2 = \underline{26 \text{ V}}$$



### Chapter 3, Solution 24

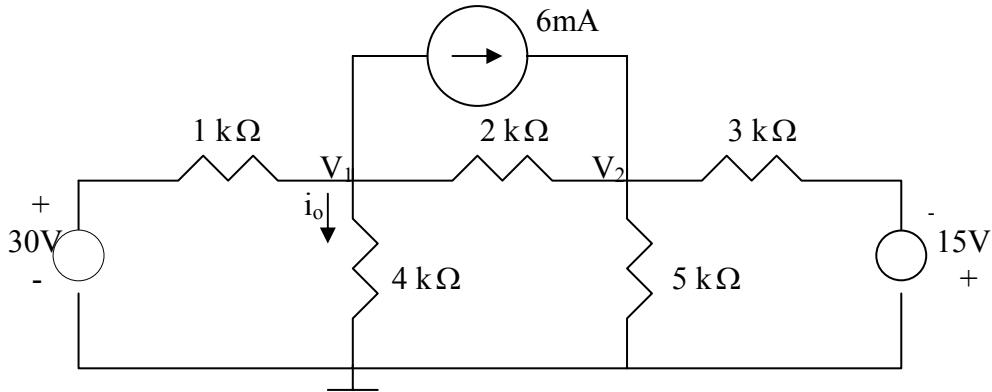

At node 1,

$$\frac{30 - V_1}{1} = 6 + \frac{V_1}{4} + \frac{V_1 - V_2}{2} \longrightarrow 96 = 7V_1 - 2V_2 \quad (1)$$


At node 2,

$$6 + \frac{(-15 - V_2)}{3} = \frac{V_2}{5} + \frac{V_2 - V_1}{2} \longrightarrow 30 = -15V_1 + 31V_2 \quad (2)$$

Solving (1) and (2) gives  $V_1 = 16.24$ . Hence

$$i_o = V_1/4 = 4.06 \text{ mA}$$

### Chapter 3, Solution 25

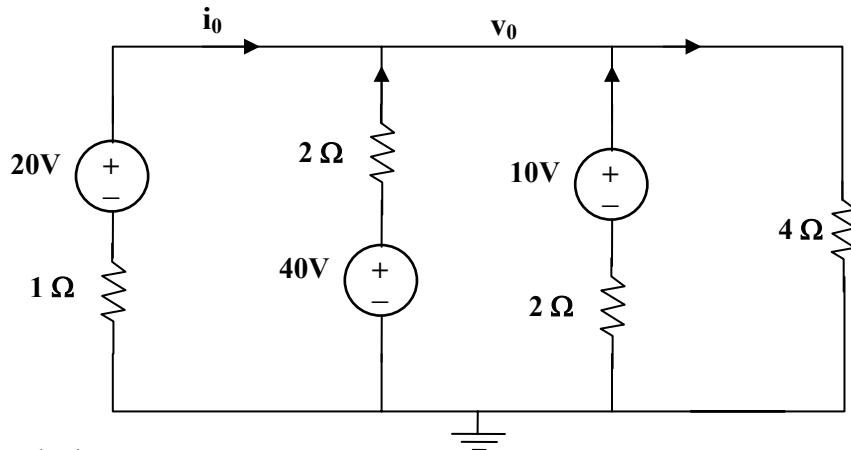

Using nodal analysis,

$$\frac{20 - v_0}{1} + \frac{40 - v_0}{2} + \frac{10 - v_0}{2} = \frac{v_0 - 0}{4} \longrightarrow v_0 = \underline{\underline{20V}}$$

$$i_0 = \frac{20 - v_0}{1} = \underline{\underline{0A}}$$

### Chapter 3, Solution 26

At node 1,

$$\frac{15-V_1}{20} = 3 + \frac{V_1-V_3}{10} + \frac{V_1-V_2}{5} \longrightarrow -45 = 7V_1 - 4V_2 - 2V_3 \quad (1)$$

At node 2,

$$\frac{V_1-V_2}{5} + \frac{4I_o - V_2}{5} = \frac{V_2-V_3}{5} \quad (2)$$

But  $I_o = \frac{V_1-V_3}{10}$ . Hence, (2) becomes

$$0 = 7V_1 - 15V_2 + 3V_3 \quad (3)$$

At node 3,

$$3 + \frac{V_1-V_3}{10} + \frac{-10-V_3}{5} + \frac{V_2-V_3}{5} = 0 \longrightarrow -10 = V_1 + 2V_2 - 5V_3 \quad (4)$$

Putting (1), (3), and (4) in matrix form produces

$$\begin{pmatrix} 7 & -4 & -2 \\ 7 & -15 & 3 \\ 1 & 2 & -5 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} -45 \\ 0 \\ -10 \end{pmatrix} \longrightarrow AV = B$$

Using MATLAB leads to

$$V = A^{-1}B = \begin{pmatrix} -9.835 \\ -4.982 \\ -1.96 \end{pmatrix}$$

Thus,

$$\underline{V_1 = -9.835 \text{ V}, V_2 = -4.982 \text{ V}, V_3 = -1.95 \text{ V}}$$

### Chapter 3, Solution 27

At node 1,

$$2 = 2v_1 + v_1 - v_2 + (v_1 - v_3)4 + 3i_0, \quad i_0 = 4v_2. \quad \text{Hence,}$$

$$2 = 7v_1 + 11v_2 - 4v_3 \quad (1)$$

At node 2,

$$v_1 - v_2 = 4v_2 + v_2 - v_3 \longrightarrow 0 = -v_1 + 6v_2 - v_3 \quad (2)$$

At node 3,

$$2v_3 = 4 + v_2 - v_3 + 12v_2 + 4(v_1 - v_3)$$

or  $-4 = 4v_1 + 13v_2 - 7v_3$

(3)

In matrix form,

$$\begin{bmatrix} 7 & 11 & -4 \\ 1 & -6 & 1 \\ 4 & 13 & -7 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ -4 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 7 & 11 & -4 \\ 1 & -6 & 1 \\ 4 & 13 & -7 \end{vmatrix} = 176, \quad \Delta_1 = \begin{vmatrix} 2 & 11 & -4 \\ 0 & -6 & 1 \\ -4 & 13 & -7 \end{vmatrix} = 110$$

$$\Delta_2 = \begin{vmatrix} 7 & 2 & -4 \\ 1 & 0 & 1 \\ 4 & -4 & -7 \end{vmatrix} = 66, \quad \Delta_3 = \begin{vmatrix} 7 & 11 & 2 \\ 1 & -6 & 0 \\ 4 & 13 & -4 \end{vmatrix} = 286$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{110}{176} = 0.625V, \quad v_2 = \frac{\Delta_2}{\Delta} = \frac{66}{176} = 0.375V$$

$$v_3 = \frac{\Delta_3}{\Delta} = \frac{286}{176} = 1.625V.$$

$$v_1 = \underline{625 \text{ mV}}, \quad v_2 = \underline{375 \text{ mV}}, \quad v_3 = \underline{1.625 \text{ V}}.$$

### Chapter 3, Solution 28

At node c,

$$\frac{V_d - V_c}{10} = \frac{V_c - V_b}{4} + \frac{V_c}{5} \quad \longrightarrow \quad 0 = -5V_b + 11V_c - 2V_d \quad (1)$$

At node b,

$$\frac{V_a + 45 - V_b}{8} + \frac{V_c - V_b}{4} = \frac{V_b}{8} \quad \longrightarrow \quad -45 = V_a - 4V_b + 2V_c \quad (2)$$

At node a,

$$\frac{V_a - 30 - V_d}{4} + \frac{V_a}{16} + \frac{V_a + 45 - V_b}{8} = 0 \quad \longrightarrow \quad 30 = 7V_a - 2V_b - 4V_d \quad (3)$$

At node d,

$$\frac{V_a - 30 - V_d}{4} = \frac{V_d}{20} + \frac{V_d - V_c}{10} \quad \longrightarrow \quad 150 = 5V_a + 2V_c - 7V_d \quad (4)$$

In matrix form, (1) to (4) become

$$\begin{pmatrix} 0 & -5 & 11 & -2 \\ 1 & -4 & 2 & 0 \\ 7 & -2 & 0 & -4 \\ 5 & 0 & 2 & -7 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \\ V_c \\ V_d \end{pmatrix} = \begin{pmatrix} 0 \\ -45 \\ 30 \\ 150 \end{pmatrix} \longrightarrow AV = B$$

We use MATLAB to invert A and obtain

$$V = A^{-1}B = \begin{pmatrix} -10.14 \\ 7.847 \\ -1.736 \\ -29.17 \end{pmatrix}$$

Thus,

$$\underline{V_a = -10.14 \text{ V}, V_b = 7.847 \text{ V}, V_c = -1.736 \text{ V}, V_d = -29.17 \text{ V}}$$

### Chapter 3, Solution 29

At node 1,

$$5 + V_1 - V_4 + 2V_1 + V_1 - V_2 = 0 \longrightarrow -5 = 4V_1 - V_2 - V_4 \quad (1)$$

At node 2,

$$V_1 - V_2 = 2V_2 + 4(V_2 - V_3) = 0 \longrightarrow 0 = -V_1 + 7V_2 - 4V_3 \quad (2)$$

At node 3,

$$6 + 4(V_2 - V_3) = V_3 - V_4 \longrightarrow 6 = -4V_2 + 5V_3 - V_4 \quad (3)$$

At node 4,

$$2 + V_3 - V_4 + V_1 - V_4 = 3V_4 \longrightarrow 2 = -V_1 - V_3 + 5V_4 \quad (4)$$

In matrix form, (1) to (4) become

$$\begin{pmatrix} 4 & -1 & 0 & -1 \\ -1 & 7 & -4 & 0 \\ 0 & -4 & 5 & -1 \\ -1 & 0 & -1 & 5 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{pmatrix} = \begin{pmatrix} -5 \\ 0 \\ 6 \\ 2 \end{pmatrix} \longrightarrow AV = B$$


Using MATLAB,

$$V = A^{-1}B = \begin{pmatrix} -0.7708 \\ 1.209 \\ 2.309 \\ 0.7076 \end{pmatrix}$$

i.e.

$$\underline{V_1 = -0.7708 \text{ V}, V_2 = 1.209 \text{ V}, V_3 = 2.309 \text{ V}, V_4 = 0.7076 \text{ V}}$$

### Chapter 3, Solution 30

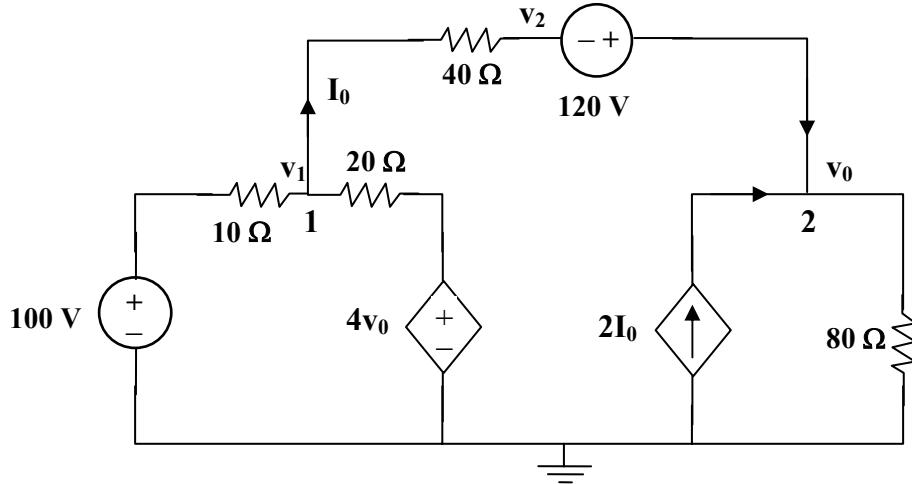

At node 1,

$$\frac{v_1 - v_2}{40} = \frac{100 - v_1}{10} + \frac{4v_o - v_1}{20} \quad (1)$$

But,  $v_o = 120 + v_2 \rightarrow v_2 = v_o - 120$ . Hence (1) becomes

$$7v_1 - 9v_o = 280 \quad (2)$$

At node 2,

$$I_o + 2I_o = \frac{v_o - 0}{80}$$

$$3\left(\frac{v_1 + 120 - v_o}{40}\right) = \frac{v_o}{80}$$

or

$$6v_1 - 7v_o = -720 \quad (3)$$

from (2) and (3),

$$\begin{bmatrix} 7 & -9 \\ 6 & -7 \end{bmatrix} \begin{bmatrix} v_1 \\ v_o \end{bmatrix} = \begin{bmatrix} 280 \\ -720 \end{bmatrix}$$


$$\Delta = \begin{vmatrix} 7 & -9 \\ 6 & -7 \end{vmatrix} = -49 + 54 = 5$$

$$\Delta_1 = \begin{vmatrix} 280 & -9 \\ -720 & -7 \end{vmatrix} = -8440, \quad \Delta_2 = \begin{vmatrix} 7 & 280 \\ 6 & -720 \end{vmatrix} = -6720$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{-8440}{5} = -1688, \quad v_o = \frac{\Delta_2}{\Delta} = \frac{-6720}{5} = -1344V$$

$$I_o = \underline{5.6 \text{ A}}$$

### Chapter 3, Solution 31

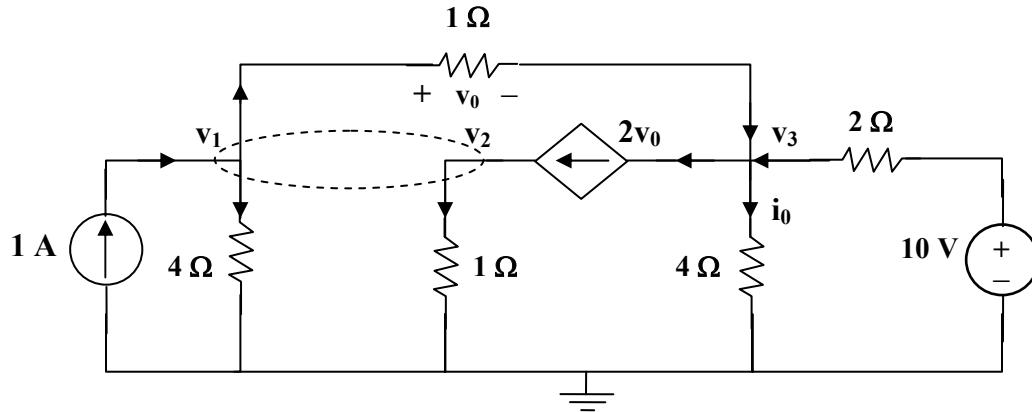

At the supernode,

$$1 + 2v_0 = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} \quad (1)$$

But  $v_0 = v_1 - v_3$ . Hence (1) becomes,

$$4 = -3v_1 + 4v_2 + 4v_3 \quad (2)$$

At node 3,

$$2v_0 + \frac{v_2}{4} = v_1 - v_3 + \frac{10 - v_3}{2}$$

or

$$20 = 4v_1 + v_2 - 2v_3 \quad (3)$$


At the supernode,  $v_2 = v_1 + 4i_o$ . But  $i_o = \frac{v_3}{4}$ . Hence,

$$v_2 = v_1 + v_3 \quad (4)$$

Solving (2) to (4) leads to,

$$v_1 = \underline{4 \text{ V}}, \quad v_2 = \underline{4 \text{ V}}, \quad v_3 = \underline{0 \text{ V}}.$$

Chapter 3, Solution 32

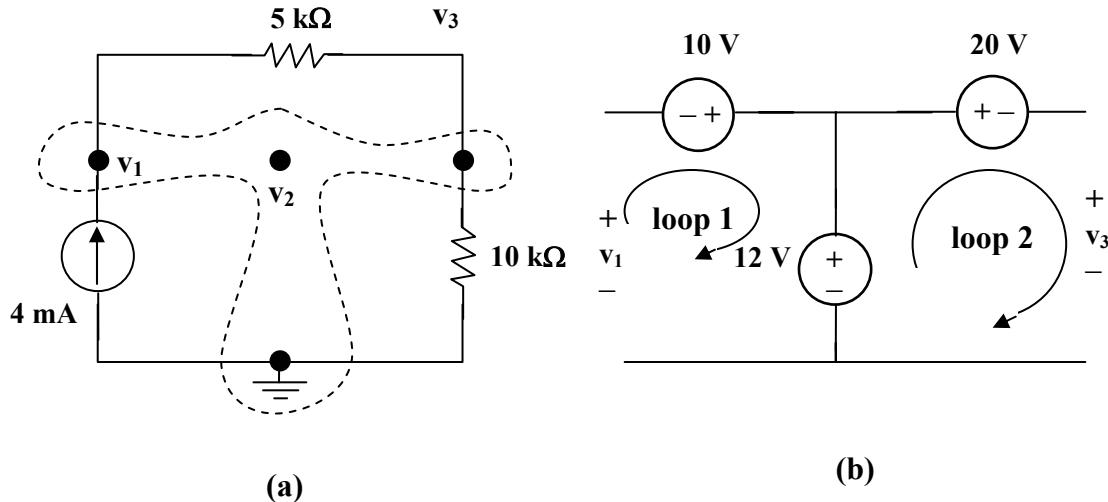

We have a supernode as shown in figure (a). It is evident that  $v_2 = 12$  V. Applying KVL to loops 1 and 2 in figure (b), we obtain,


$$-v_1 - 10 + 12 = 0 \text{ or } v_1 = 2 \text{ and } -12 + 20 + v_3 = 0 \text{ or } v_3 = -8 \text{ V}$$

Thus,  $v_1 = \underline{2V}$ ,  $v_2 = \underline{12V}$ ,  $v_3 = \underline{-8V}$ .

Chapter 3, Solution 33


- (a)** This is a **non-planar** circuit because there is no way of redrawing the circuit with no crossing branches.

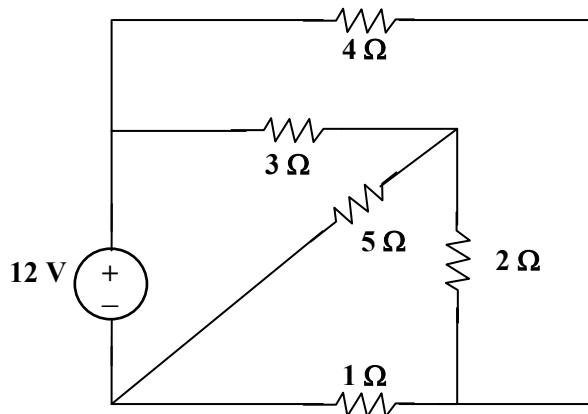**(b)** This is a **planar** circuit. It can be redrawn as shown below.




### Chapter 3, Solution 34

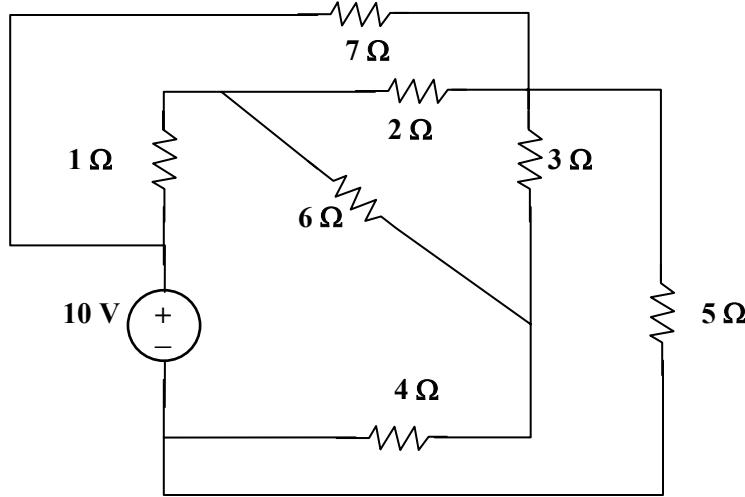(a) This is a planar circuit because it can be redrawn as shown below,



(b) This is a non-planar circuit.

### Chapter 3, Solution 35

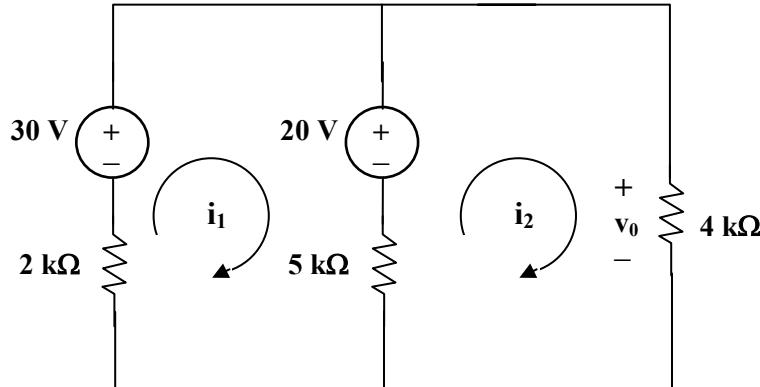

Assume that  $i_1$  and  $i_2$  are in mA. We apply mesh analysis. For mesh 1,

$$-30 + 20 + 7i_1 - 5i_2 = 0 \text{ or } 7i_1 - 5i_2 = 10 \quad (1)$$


For mesh 2,

$$-20 + 9i_2 - 5i_1 = 0 \text{ or } -5i_1 + 9i_2 = 20 \quad (2)$$

Solving (1) and (2), we obtain,  $i_2 = 5$ .

$$v_0 = 4i_2 = \underline{\underline{20 \text{ volts}}}$$

### Chapter 3, Solution 36

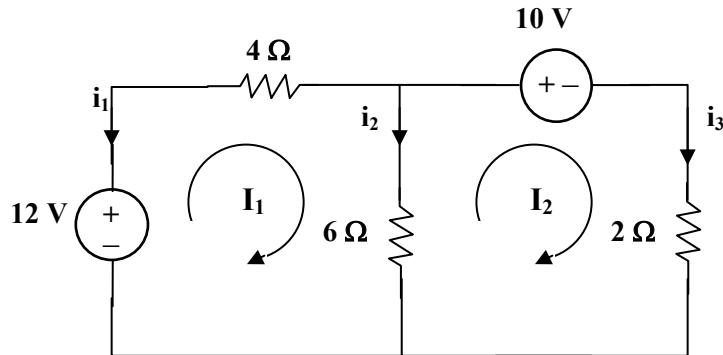

Applying mesh analysis gives,

$$12 = 10I_1 - 6I_2$$

$$-10 = -6I_1 + 8I_2$$

or

$$\begin{bmatrix} 6 \\ -5 \end{bmatrix} = \begin{bmatrix} 5 & -3 \\ -3 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


$$\Delta = \begin{vmatrix} 5 & -3 \\ -3 & 4 \end{vmatrix} = 11, \quad \Delta_1 = \begin{vmatrix} 6 & -3 \\ -5 & 4 \end{vmatrix} = 9, \quad \Delta_2 = \begin{vmatrix} 5 & 6 \\ -3 & -5 \end{vmatrix} = -7$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{9}{11}, \quad I_2 = \frac{\Delta_2}{\Delta} = \frac{-7}{11}$$

$$i_1 = -I_1 = -9/11 = -0.8181 \text{ A}, \quad i_2 = I_1 - I_2 = 10/11 = 1.4545 \text{ A}.$$

$$v_o = 6i_2 = 6 \times 1.4545 = \underline{8.727 \text{ V.}}$$

### Chapter 3, Solution 37

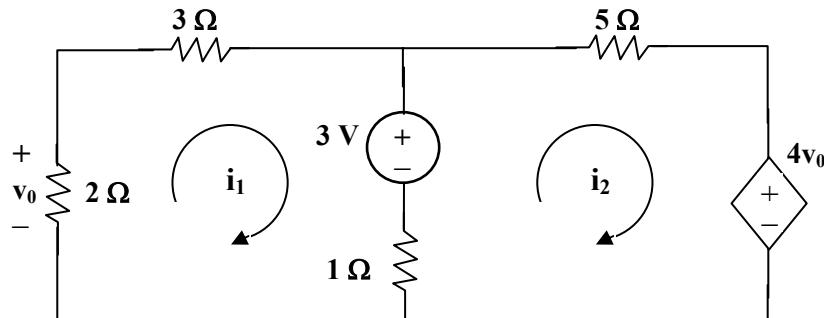

Applying mesh analysis to loops 1 and 2, we get,

$$6i_1 - 1i_2 + 3 = 0 \text{ which leads to } i_2 = 6i_1 + 3 \quad (1)$$


$$-1i_1 + 6i_2 - 3 + 4v_0 = 0 \quad (2)$$

$$\text{But, } v_0 = -2i_1 \quad (3)$$

Using (1), (2), and (3) we get  $i_1 = -5/9$ .

Therefore, we get  $v_0 = -2i_1 = -2(-5/9) = \underline{\underline{1.111 \text{ volts}}}$

### Chapter 3, Solution 38

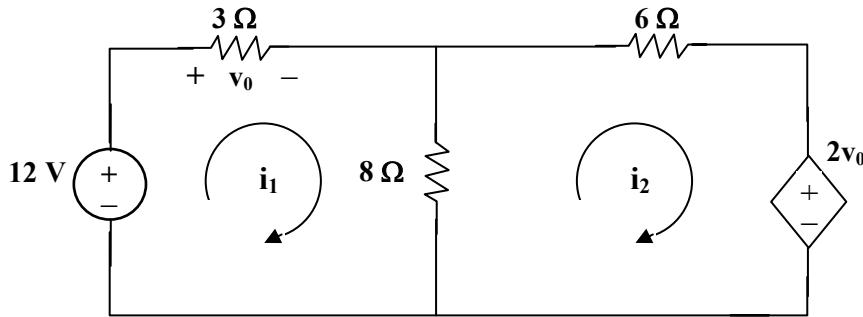

We apply mesh analysis.

$$12 = 3i_1 + 8(i_1 - i_2) \text{ which leads to } 12 = 11i_1 - 8i_2 \quad (1)$$

$$-2v_0 = 6i_2 + 8(i_2 - i_1) \text{ and } v_0 = 3i_1 \text{ or } i_1 = 7i_2 \quad (2)$$

From (1) and (2),  $i_1 = 84/69$  and  $v_0 = 3i_1 = 3 \times 84/69$

$$v_0 = \underline{\underline{3.652 \text{ volts}}}$$

### Chapter 3, Solution 39

For mesh 1,

$$-10 - 2I_x + 10I_1 - 6I_2 = 0$$

But  $I_x = I_1 - I_2$ . Hence,

$$10 = -12I_1 + 12I_2 + 10I_1 - 6I_2 \longrightarrow 5 = 4I_1 - 2I_2 \quad (1)$$


For mesh 2,

$$12 + 8I_2 - 6I_1 = 0 \longrightarrow 6 = 3I_1 - 4I_2 \quad (2)$$

Solving (1) and (2) leads to

$$\underline{\underline{I_1 = 0.8 \text{ A}, \quad I_2 = -0.9 \text{ A}}}$$

### Chapter 3, Solution 40

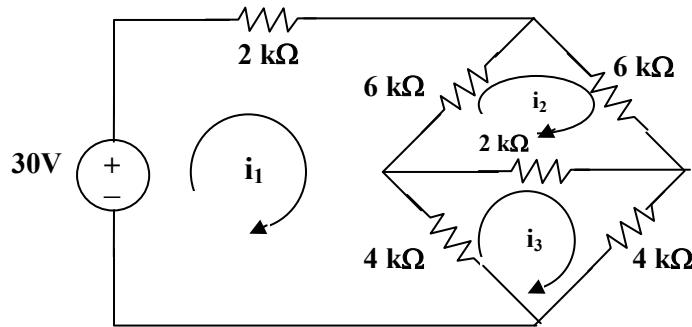

Assume all currents are in mA and apply mesh analysis for mesh 1.

$$30 = 12i_1 - 6i_2 - 4i_3 \quad \rightarrow \quad 15 = 6i_1 - 3i_2 - 2i_3 \quad (1)$$

for mesh 2,

$$0 = -6i_1 + 14i_2 - 2i_3 \quad \rightarrow \quad 0 = -3i_1 + 7i_2 - i_3 \quad (2)$$


for mesh 3,

$$0 = -4i_1 - 2i_2 + 10i_3 \quad 0 = -2i_1 - i_2 + 5i_3 \quad (3)$$

Solving (1), (2), and (3), we obtain,

$$i_o = i_1 = \underline{4.286 \text{ mA}}$$

### Chapter 3, Solution 41

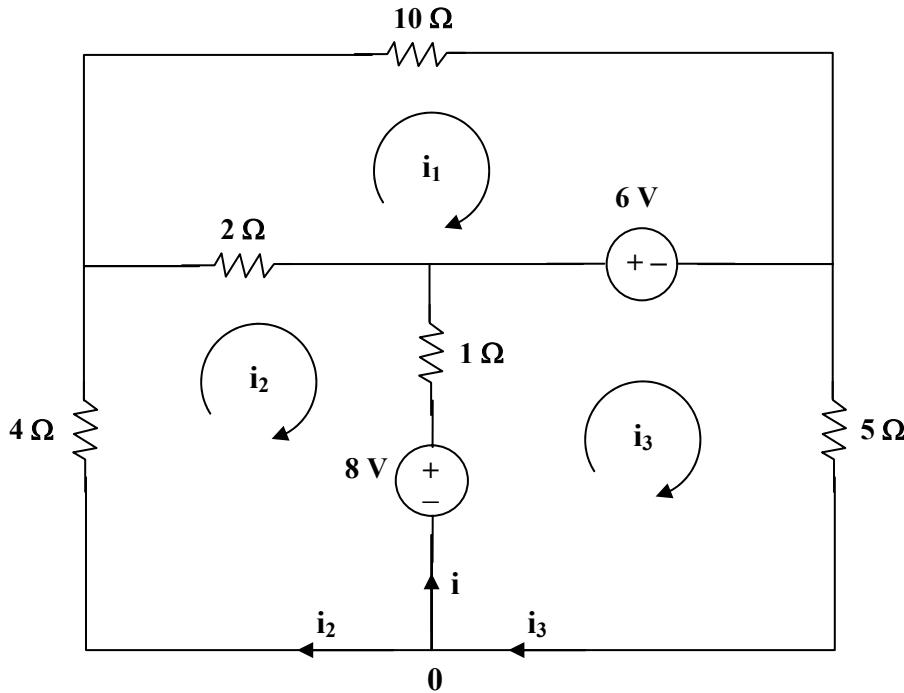

For loop 1,

$$6 = 12i_1 - 2i_2 \quad \longrightarrow \quad 3 = 6i_1 - i_2 \quad (1)$$

For loop 2,

$$-8 = 7i_2 - 2i_1 - i_3 \quad (2)$$

For loop 3,

$$-8 + 6 + 6i_3 - i_2 = 0 \quad \longrightarrow \quad 2 = 6i_3 - i_2 \quad (3)$$

We put (1), (2), and (3) in matrix form,

$$\begin{bmatrix} 6 & -1 & 0 \\ 2 & -7 & 1 \\ 0 & -1 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 8 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -1 & 0 \\ 2 & -7 & 1 \\ 0 & -1 & 6 \end{vmatrix} = -234, \quad \Delta_2 = \begin{vmatrix} 6 & 3 & 0 \\ 2 & 8 & 1 \\ 0 & 2 & 6 \end{vmatrix} = -240$$

$$\Delta_3 = \begin{vmatrix} 6 & -1 & 3 \\ 2 & -7 & 8 \\ 0 & -1 & 2 \end{vmatrix} = -38$$

$$\text{At node 0, } i + i_2 = i_3 \text{ or } i = i_3 - i_2 = \frac{\Delta_3 - \Delta_2}{\Delta} = \frac{-38 - 240}{-234} = \underline{\mathbf{1.188 A}}$$

### Chapter 3, Solution 42

For mesh 1,

$$-12 + 50I_1 - 30I_2 = 0 \longrightarrow 12 = 50I_1 - 30I_2 \quad (1)$$

For mesh 2,

$$-8 + 100I_2 - 30I_1 - 40I_3 = 0 \longrightarrow 8 = -30I_1 + 100I_2 - 40I_3 \quad (2)$$

For mesh 3,

$$-6 + 50I_3 - 40I_2 = 0 \longrightarrow 6 = -40I_2 + 50I_3 \quad (3)$$

Putting eqs. (1) to (3) in matrix form, we get


$$\begin{pmatrix} 50 & -30 & 0 \\ -30 & 100 & -40 \\ 0 & -40 & 50 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 12 \\ 8 \\ 6 \end{pmatrix} \longrightarrow AI = B$$

Using Matlab,

$$I = A^{-1}B = \begin{pmatrix} 0.48 \\ 0.40 \\ 0.44 \end{pmatrix}$$

i.e.  $I_1 = 0.48 \text{ A}$ ,  $I_2 = 0.4 \text{ A}$ ,  $I_3 = 0.44 \text{ A}$

### Chapter 3, Solution 43

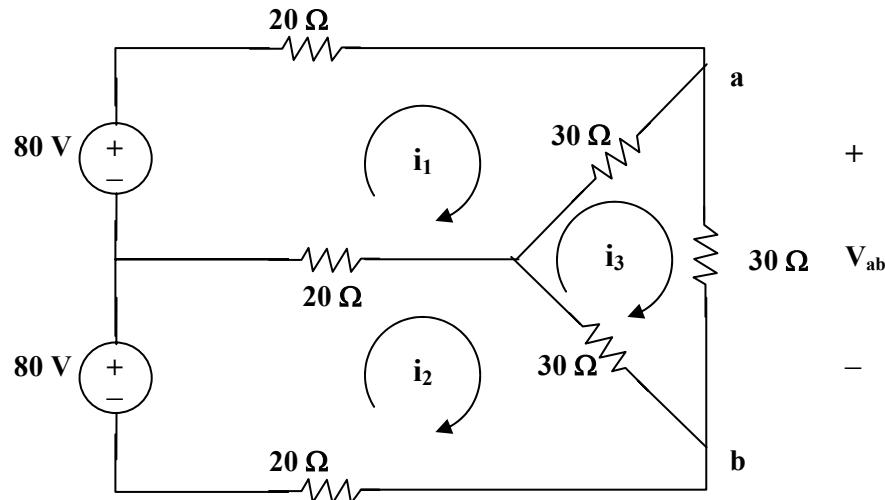

For loop 1,

$$80 = 70i_1 - 20i_2 - 30i_3 \longrightarrow 8 = 7i_1 - 2i_2 - 3i_3 \quad (1)$$

For loop 2,

$$80 = 70i_2 - 20i_1 - 30i_3 \quad \longrightarrow \quad 8 = -2i_1 + 7i_2 - 3i_3 \quad (2)$$

For loop 3,


$$0 = -30i_1 - 30i_2 + 90i_3 \quad \longrightarrow \quad 0 = i_1 + i_2 - 3i_3 \quad (3)$$

Solving (1) to (3), we obtain  $i_3 = 16/9$

$$I_o = i_3 = 16/9 = \underline{\mathbf{1.778 \text{ A}}}$$

$$V_{ab} = 30i_3 = \underline{\mathbf{53.33 \text{ V}}}$$

### Chapter 3, Solution 44

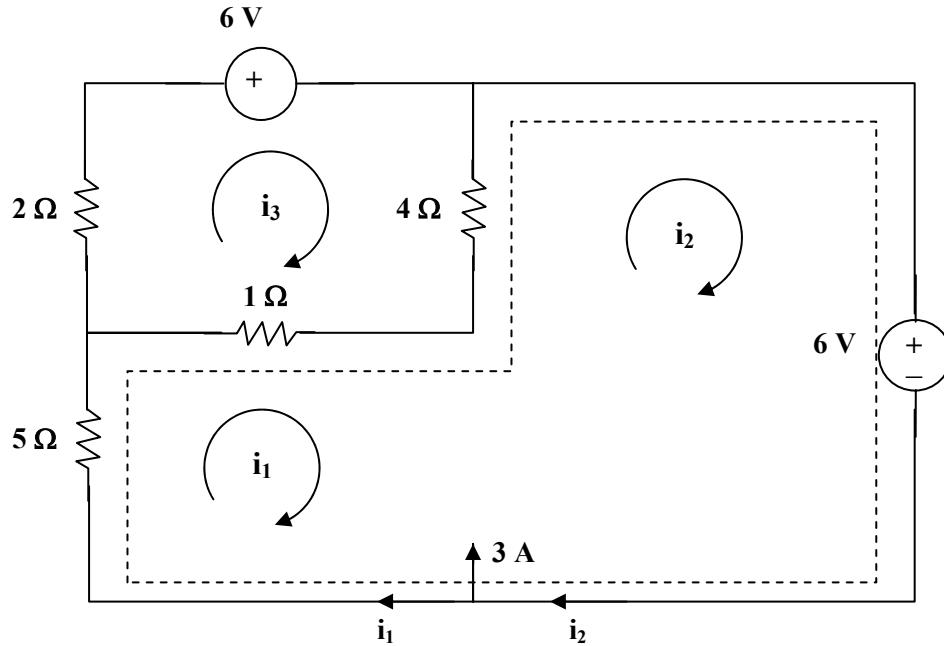

Loop 1 and 2 form a supermesh. For the supermesh,


$$6i_1 + 4i_2 - 5i_3 + 12 = 0 \quad (1)$$

$$\text{For loop 3, } -i_1 - 4i_2 + 7i_3 + 6 = 0 \quad (2)$$

$$\text{Also, } i_2 = 3 + i_1 \quad (3)$$

Solving (1) to (3),  $i_1 = -3.067$ ,  $i_3 = -1.3333$ ;  $i_o = i_1 - i_3 = \underline{\mathbf{-1.7333 \text{ A}}}$

### Chapter 3, Solution 45

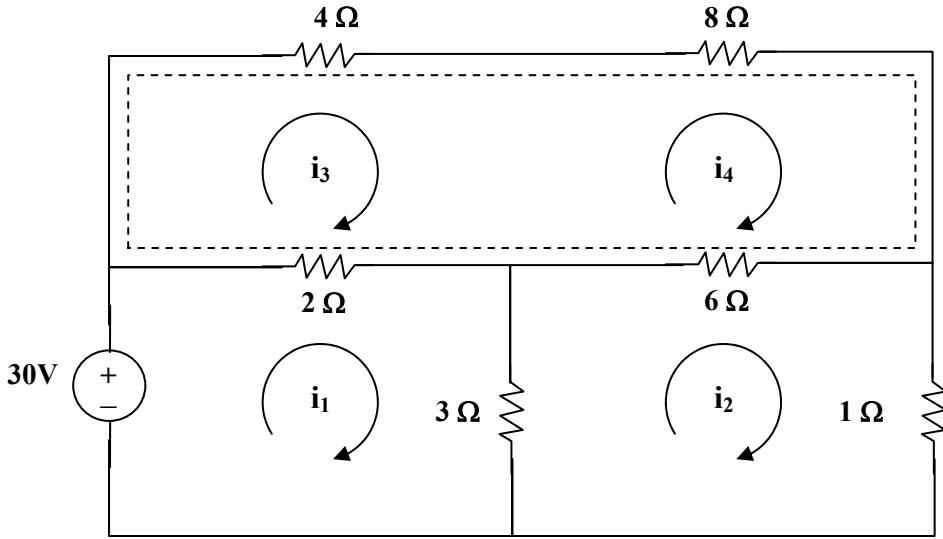

For loop 1,  $30 = 5i_1 - 3i_2 - 2i_3 \quad (1)$

For loop 2,  $10i_2 - 3i_1 - 6i_4 = 0 \quad (2)$

For the supermesh,  $6i_3 + 14i_4 - 2i_1 - 6i_2 = 0 \quad (3)$

But  $i_4 - i_3 = 4$  which leads to  $i_4 = i_3 + 4 \quad (4)$

Solving (1) to (4) by elimination gives  $i = i_1 = \underline{\underline{8.561 \text{ A}}}$ .

### Chapter 3, Solution 46

For loop 1,

$$-12 + 11i_1 - 8i_2 = 0 \longrightarrow 11i_1 - 8i_2 = 12 \quad (1)$$

For loop 2,

$$-8i_1 + 14i_2 + 2v_o = 0$$

But  $v_o = 3i_1$ ,


$$-8i_1 + 14i_2 + 6i_1 = 0 \longrightarrow i_1 = 7i_2 \quad (2)$$

Substituting (2) into (1),

$$77i_2 - 8i_2 = 12 \longrightarrow i_2 = \underline{\underline{0.1739 \text{ A}}} \text{ and } i_1 = \underline{\underline{1.217 \text{ A}}}$$
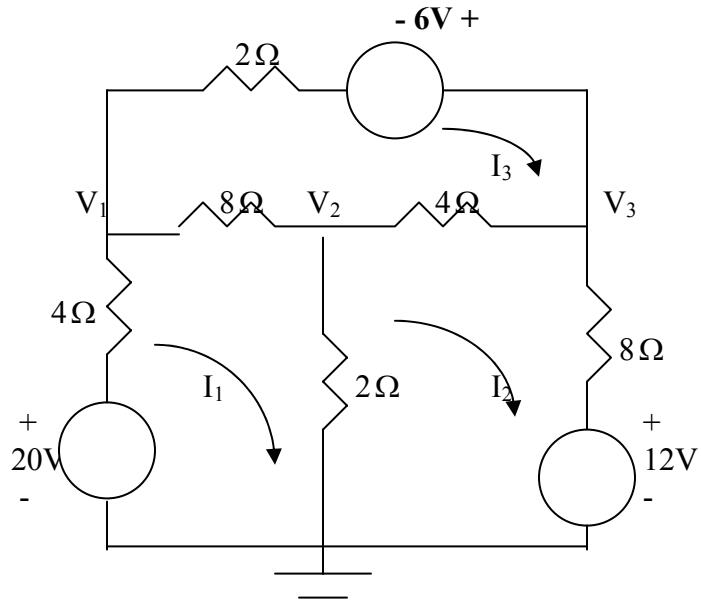
### Chapter 3, Solution 47

First, transform the current sources as shown below.



For mesh 1,

$$-20 + 14I_1 - 2I_2 - 8I_3 = 0 \quad \longrightarrow \quad 10 = 7I_1 - I_2 - 4I_3 \quad (1)$$

For mesh 2,

$$12 + 14I_2 - 2I_1 - 4I_3 = 0 \quad \longrightarrow \quad -6 = -I_1 + 7I_2 - 2I_3 \quad (2)$$

For mesh 3,

$$-6 + 14I_3 - 4I_2 - 8I_1 = 0 \quad \longrightarrow \quad 3 = -4I_1 - 2I_2 + 7I_3 \quad (3)$$

Putting (1) to (3) in matrix form, we obtain

$$\begin{pmatrix} 7 & -1 & -4 \\ -1 & 7 & -2 \\ -4 & -2 & 7 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 10 \\ -6 \\ 3 \end{pmatrix} \quad \longrightarrow \quad AI = B$$

Using MATLAB,

$$I = A^{-1}B = \begin{bmatrix} 2 \\ 0.0333 \\ 1.8667 \end{bmatrix} \quad \longrightarrow \quad I_1 = 2.5, I_2 = 0.0333, I_3 = 1.8667$$

But

$$I_1 = \frac{20 - V_1}{4} \quad \longrightarrow \quad V_1 = 20 - 4I_1 = 10 \text{ V}$$


$$V_2 = 2(I_1 - I_2) = 4.933 \text{ V}$$

Also,

$$I_2 = \frac{V_3 - 12}{8} \quad \longrightarrow \quad V_3 = 12 + 8I_2 = 12.267 \text{ V}$$
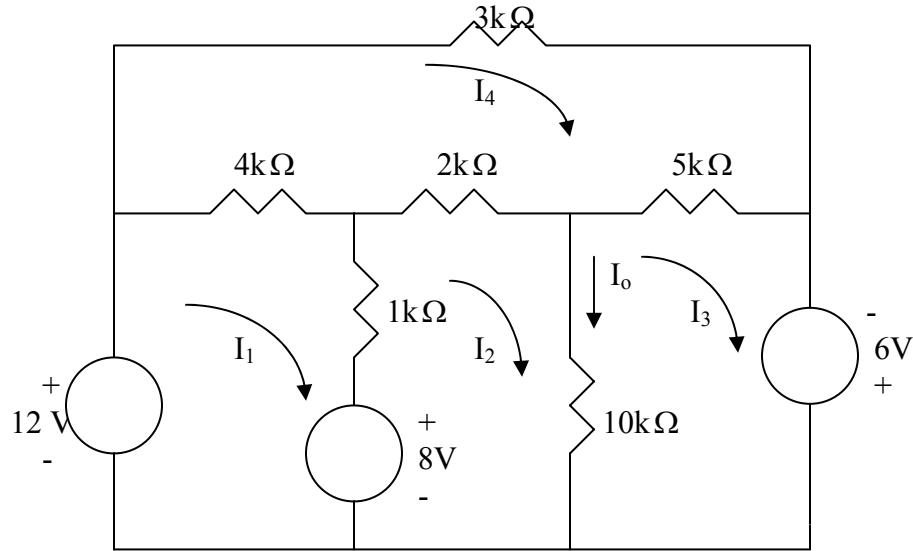
### Chapter 3, Solution 48

We apply mesh analysis and let the mesh currents be in mA.



For mesh 1,

$$-12 + 8 + 5I_1 - I_2 - 4I_4 = 0 \quad \longrightarrow \quad 4 = 5I_1 - I_2 - 4I_4 \quad (1)$$

For mesh 2,

$$-8 + 13I_2 - I_1 - 10I_3 - 2I_4 = 0 \quad \longrightarrow \quad 8 = -I_1 + 13I_2 - 10I_3 - 2I_4 \quad (2)$$

For mesh 3,

$$-6 + 15I_3 - 10I_2 - 5I_4 = 0 \quad \longrightarrow \quad 6 = -10I_2 + 15I_3 - 5I_4 \quad (3)$$

For mesh 4,

$$-4I_1 - 2I_2 - 5I_3 + 14I_4 = 0 \quad (4)$$

Putting (1) to (4) in matrix form gives


$$\begin{pmatrix} 5 & -1 & 0 & -4 \\ -1 & 13 & -10 & -2 \\ 0 & -10 & 15 & -5 \\ -4 & -2 & -5 & 14 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{pmatrix} = \begin{pmatrix} 4 \\ 8 \\ 6 \\ 0 \end{pmatrix} \quad \longrightarrow \quad AI = B$$

Using MATLAB,


$$I = A^{-1}B = \begin{pmatrix} 7.217 \\ 8.087 \\ 7.791 \\ 6 \end{pmatrix}$$

The current through the  $10\text{k}\Omega$  resistor is  $I_o = I_2 - I_3 = 0.2957 \text{ mA}$

**Chapter 3, Solution 49**

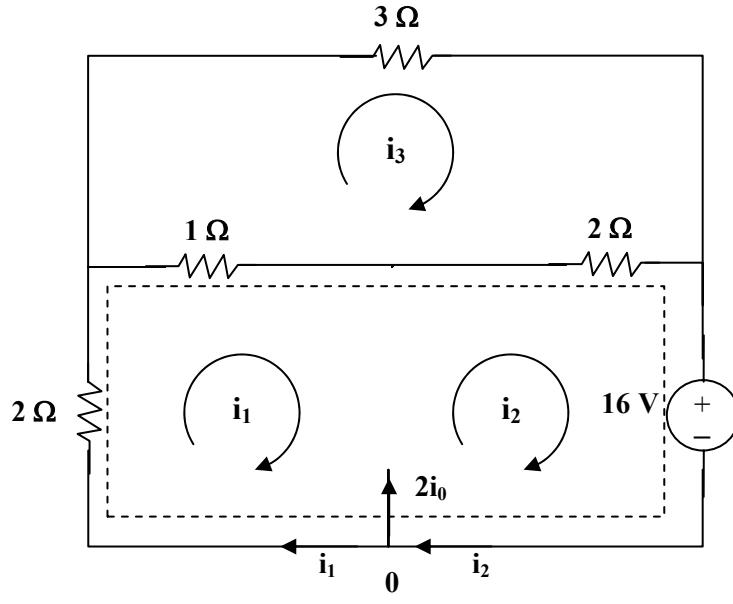

(a)

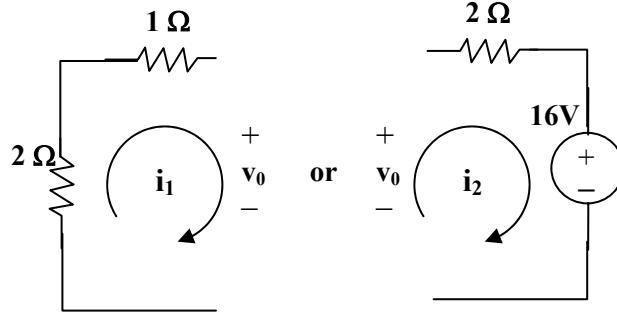

(b)

For the supermesh in figure (a),

$$3i_1 + 2i_2 - 3i_3 + 16 = 0 \quad (1)$$


$$\text{At node 0, } i_2 - i_1 = 2i_0 \text{ and } i_0 = -i_1 \text{ which leads to } i_2 = -i_1 \quad (2)$$

$$\text{For loop 3, } -i_1 - 2i_2 + 6i_3 = 0 \text{ which leads to } 6i_3 = -i_1 \quad (3)$$

Solving (1) to (3),  $i_1 = (-32/3)A$ ,  $i_2 = (32/3)A$ ,  $i_3 = (16/9)A$

$i_0 = -i_1 = \underline{\underline{10.667\text{ A}}}$ , from fig. (b),  $v_0 = i_3 - 3i_1 = (16/9) + 32 = \underline{\underline{33.78\text{ V}}}$ .

### Chapter 3, Solution 50

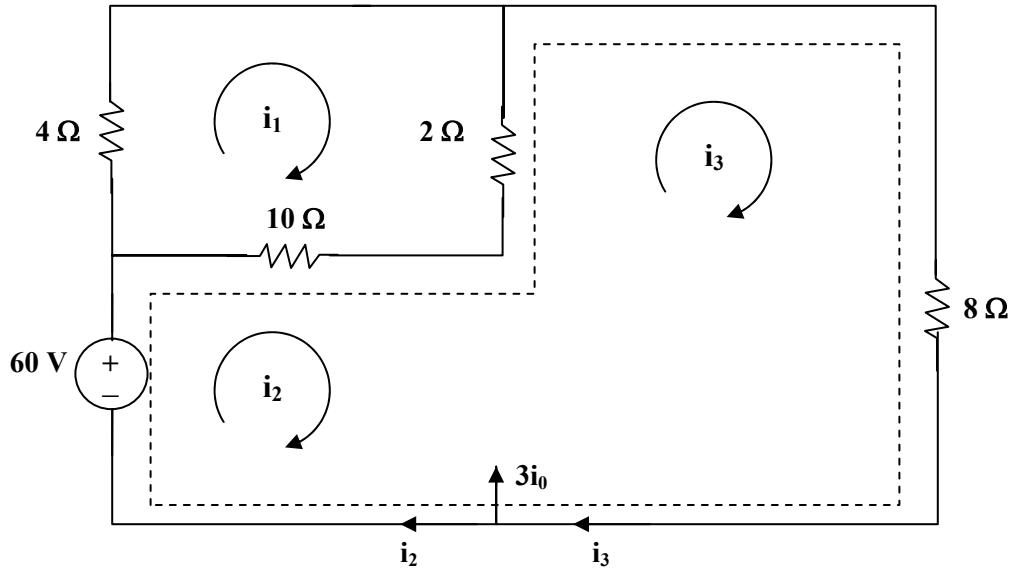

$$\text{For loop 1, } 16i_1 - 10i_2 - 2i_3 = 0 \text{ which leads to } 8i_1 - 5i_2 - i_3 = 0 \quad (1)$$


$$\text{For the supermesh, } -60 + 10i_2 - 10i_1 + 10i_3 - 2i_1 = 0$$

$$\text{or} \quad -6i_1 + 5i_2 + 5i_3 = 30 \quad (2)$$

$$\text{Also, } 3i_0 = i_3 - i_2 \text{ and } i_0 = i_1 \text{ which leads to } 3i_1 = i_3 - i_2 \quad (3)$$

Solving (1), (2), and (3), we obtain  $i_1 = 1.731$  and  $i_0 = i_1 = \underline{\underline{1.731 \text{ A}}}$

### Chapter 3, Solution 51

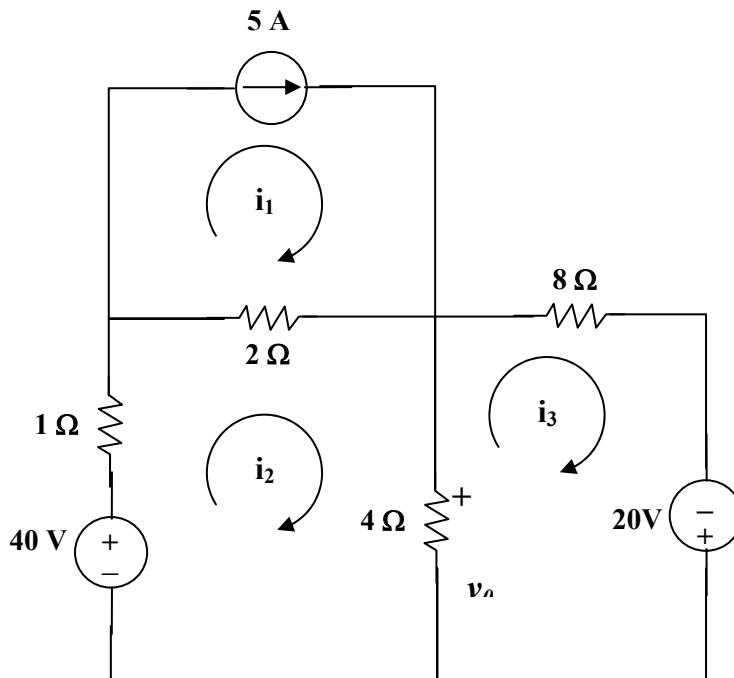

For loop 1,  $i_1 = 5A$  (1)


For loop 2,  $-40 + 7i_2 - 2i_1 - 4i_3 = 0$  which leads to  $50 = 7i_2 - 4i_3$  (2)

For loop 3,  $-20 + 12i_3 - 4i_2 = 0$  which leads to  $5 = -i_2 + 3i_3$  (3)

Solving with (2) and (3),  $i_2 = 10 A$ ,  $i_3 = 5 A$

And,  $v_0 = 4(i_2 - i_3) = 4(10 - 5) = \underline{\underline{20 V}}$ .

### Chapter 3, Solution 52

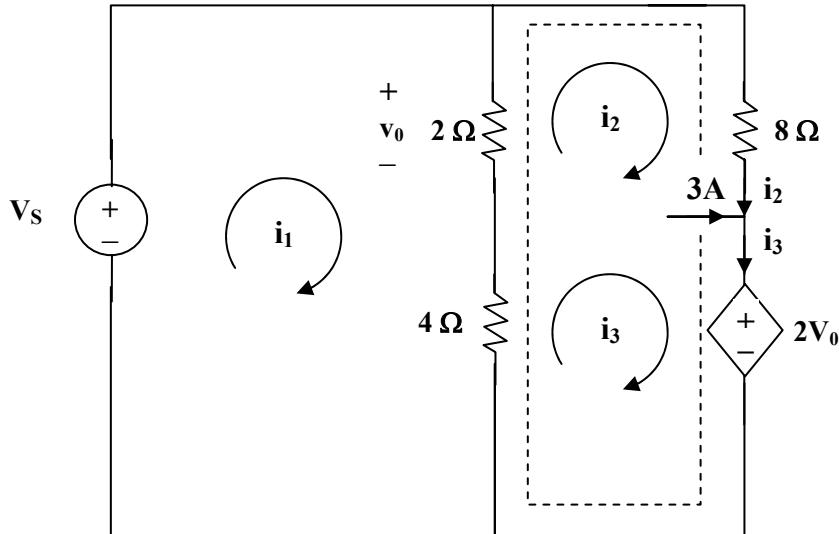

For mesh 1,

$$2(i_1 - i_2) + 4(i_1 - i_3) - 12 = 0 \text{ which leads to } 3i_1 - i_2 - 2i_3 = 6 \quad (1)$$

For the supermesh,  $2(i_2 - i_1) + 8i_2 + 2v_0 + 4(i_3 - i_1) = 0$


But  $v_0 = 2(i_1 - i_2)$  which leads to  $-i_1 + 3i_2 + 2i_3 = 0$  (2)

For the independent current source,  $i_3 = 3 + i_2$  (3)

Solving (1), (2), and (3), we obtain,

$$i_1 = \underline{\underline{3.5 A}}, \quad i_2 = \underline{\underline{-0.5 A}}, \quad i_3 = \underline{\underline{2.5 A}}$$

### Chapter 3, Solution 53

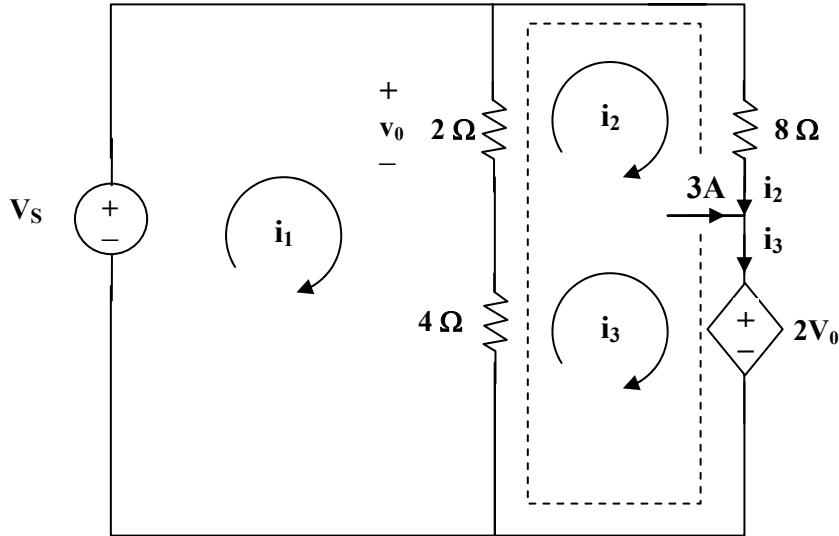

For mesh 1,

$$2(i_1 - i_2) + 4(i_1 - i_3) - 12 = 0 \text{ which leads to } 3i_1 - i_2 - 2i_3 = 6 \quad (1)$$

$$\text{For the supermesh, } 2(i_2 - i_1) + 8i_2 + 2V_0 + 4(i_3 - i_1) = 0$$

$$\text{But } V_0 = 2(i_1 - i_2) \text{ which leads to } -i_1 + 3i_2 + 2i_3 = 0 \quad (2)$$

$$\text{For the independent current source, } i_3 = 3 + i_2 \quad (3)$$

Solving (1), (2), and (3), we obtain,

$$i_1 = \underline{\underline{3.5 \text{ A}}}, \quad i_2 = \underline{\underline{-0.5 \text{ A}}}, \quad i_3 = \underline{\underline{2.5 \text{ A}}}.$$

### Chapter 3, Solution 54

Let the mesh currents be in mA. For mesh 1,

$$-12 + 10 + 2I_1 - I_2 = 0 \longrightarrow 2 = 2I_1 - I_2 \quad (1)$$

For mesh 2,

$$-10 + 3I_2 - I_1 - I_3 = 0 \longrightarrow 10 = -I_1 + 3I_2 - I_3 \quad (2)$$

For mesh 3,

$$-12 + 2I_3 - I_2 = 0 \longrightarrow 12 = -I_2 + 2I_3 \quad (3)$$


Putting (1) to (3) in matrix form leads to

$$\begin{pmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 2 \\ 10 \\ 12 \end{pmatrix} \longrightarrow AI = B$$

Using MATLAB,

$$I = A^{-1}B = \begin{bmatrix} 5.25 \\ 8.5 \\ 10.25 \end{bmatrix} \longrightarrow \underline{\underline{I_1 = 5.25 \text{ mA}, I_2 = 8.5 \text{ mA}, I_3 = 10.25 \text{ mA}}}$$

### Chapter 3, Solution 55

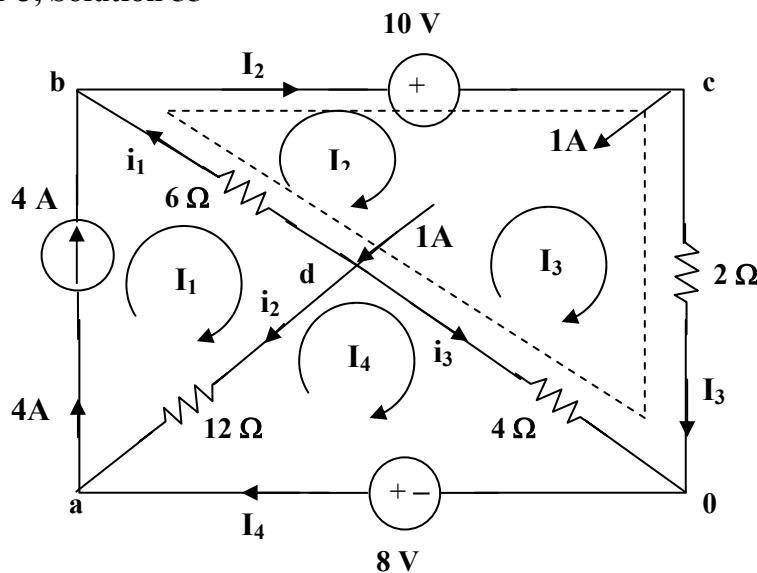

It is evident that  $I_1 = 4$  (1)

For mesh 4,  $12(I_4 - I_1) + 4(I_4 - I_3) - 8 = 0$  (2)

For the supermesh  $6(I_2 - I_1) + 10 + 2I_3 + 4(I_3 - I_4) = 0$   
or  $-3I_1 + 3I_2 + 3I_3 - 2I_4 = -5$  (3)

At node c,  $I_2 = I_3 + 1$  (4)


Solving (1), (2), (3), and (4) yields,  $I_1 = 4A$ ,  $I_2 = 3A$ ,  $I_3 = 2A$ , and  $I_4 = 4A$

At node b,  $i_1 = I_2 - I_1 = \underline{\underline{1A}}$

At node a,  $i_2 = 4 - I_4 = \underline{\underline{0A}}$

At node 0,  $i_3 = I_4 - I_3 = \underline{\underline{2A}}$

### Chapter 3, Solution 56

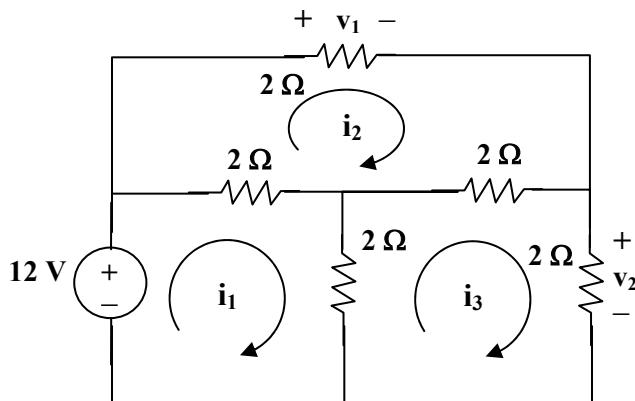

For loop 1,  $12 = 4i_1 - 2i_2 - 2i_3$  which leads to  $6 = 2i_1 - i_2 - i_3$  (1)

For loop 2,  $0 = 6i_2 - 2i_1 - 2i_3$  which leads to  $0 = -i_1 + 3i_2 - i_3$  (2)

For loop 3,  $0 = 6i_3 - 2i_1 - 2i_2$  which leads to  $0 = -i_1 - i_2 + 3i_3$  (3)

In matrix form (1), (2), and (3) become,

$$\begin{bmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 2 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix} = 8, \quad \Delta_2 = \begin{vmatrix} 2 & 6 & -1 \\ -1 & 3 & -1 \\ -1 & 0 & 3 \end{vmatrix} = 24$$

$$\Delta_3 = \begin{vmatrix} 2 & -1 & 6 \\ -1 & 3 & 0 \\ -1 & -1 & 0 \end{vmatrix} = 24, \text{ therefore } i_2 = i_3 = 24/8 = 3A,$$

$$v_1 = 2i_2 = \underline{\underline{6 \text{ volts}}}, \quad v = 2i_3 = \underline{\underline{6 \text{ volts}}}$$

### Chapter 3, Solution 57

Assume R is in kilo-ohms.


$$V_2 = 4k\Omega \times 18mA = \underline{\underline{72V}}, \quad V_1 = 100 - V_2 = 100 - 72 = \underline{\underline{28V}}$$

Current through R is

$$i_R = \frac{3}{3+R} i_o, \quad V_1 = i_R R \quad \longrightarrow \quad 28 = \frac{3}{3+R} (18)R$$

$$\text{This leads to } R = 84/26 = \underline{\underline{3.23 \text{ k}\Omega}}$$

### Chapter 3, Solution 58

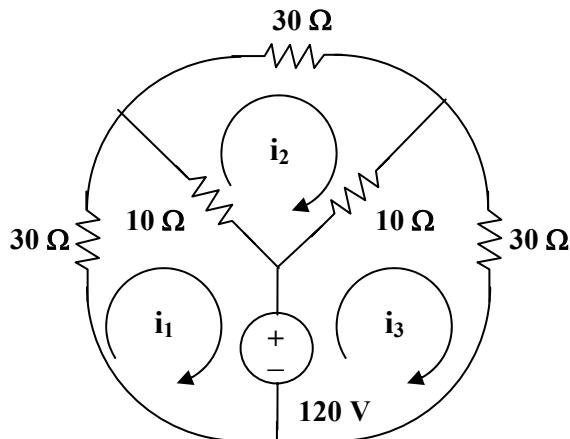


For loop 1,  $120 + 40i_1 - 10i_2 = 0$ , which leads to  $-12 = 4i_1 - i_2$  (1)

For loop 2,  $50i_2 - 10i_1 - 10i_3 = 0$ , which leads to  $-i_1 + 5i_2 - i_3 = 0$  (2)

For loop 3,  $-120 - 10i_2 + 40i_3 = 0$ , which leads to  $12 = -i_2 + 4i_3$  (3)

Solving (1), (2), and (3), we get,  $i_1 = \underline{-3A}$ ,  $i_2 = \underline{0}$ , and  $i_3 = \underline{3A}$

### Chapter 3, Solution 59

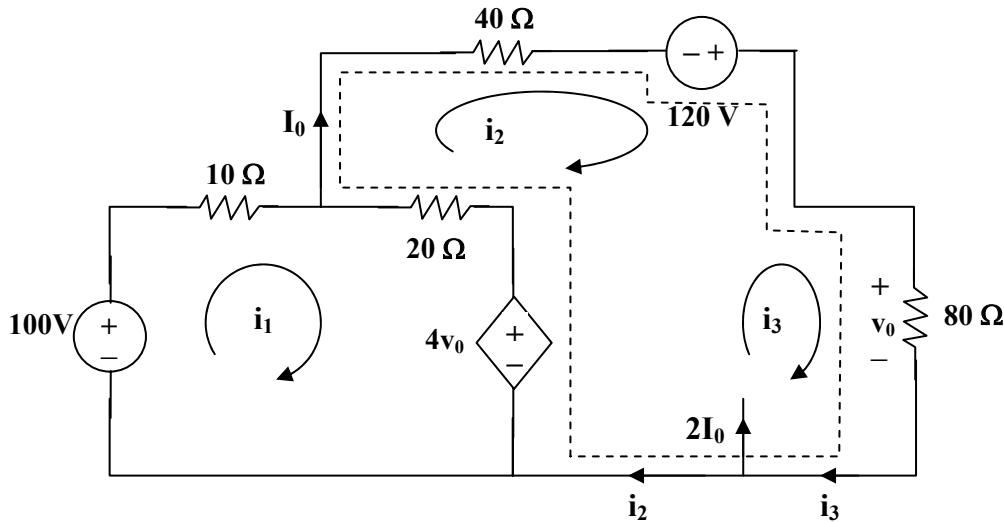

For loop 1,  $-100 + 30i_1 - 20i_2 + 4v_0 = 0$ , where  $v_0 = 80i_3$   
or  $5 = 1.5i_1 - i_2 + 16i_3$  (1)

For the supermesh,  $60i_2 - 20i_1 - 120 + 80i_3 - 4v_0 = 0$ , where  $v_0 = 80i_3$   
or  $6 = -i_1 + 3i_2 - 12i_3$  (2)

Also,  $2I_0 = i_3 - i_2$  and  $I_0 = i_2$ , hence,  $3i_2 = i_3$  (3)

From (1), (2), and (3),


$$\begin{bmatrix} 3 & -2 & 32 \\ -1 & 3 & -12 \\ 0 & 3 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 6 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -2 & 32 \\ -1 & 3 & -12 \\ 0 & 3 & -1 \end{vmatrix} = 5, \quad \Delta_2 = \begin{vmatrix} 3 & 10 & 32 \\ -1 & 6 & -12 \\ 0 & 0 & -1 \end{vmatrix} = -28, \quad \Delta_3 = \begin{vmatrix} 3 & -2 & 10 \\ -1 & 3 & 6 \\ 0 & 3 & 0 \end{vmatrix} = -84$$

$$I_0 = i_2 = \Delta_2 / \Delta = -28/5 = \underline{-5.6 A}$$

$$v_0 = 8i_3 = (-84/5)80 = \underline{-1344 \text{ volts}}$$

### Chapter 3, Solution 60

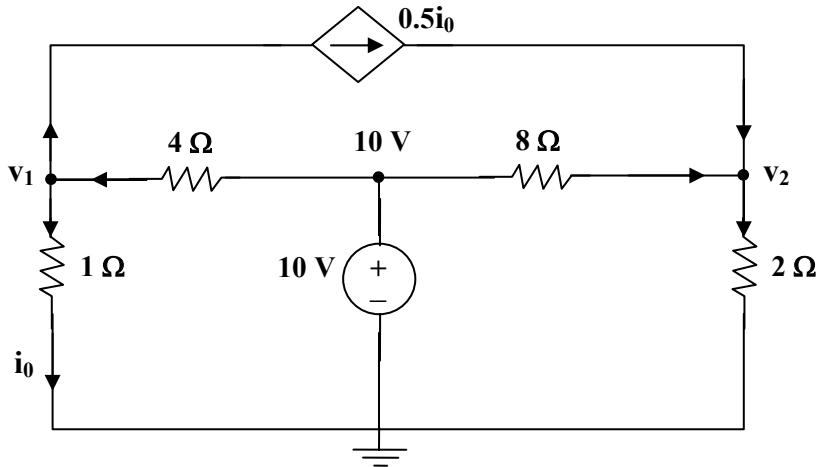


At node 1,  $(v_1/1) + (0.5v_1/1) = (10 - v_1)/4$ , which leads to  $v_1 = 10/7$

At node 2,  $(0.5v_1/1) + ((10 - v_2)/8) = v_2/2$  which leads to  $v_2 = 22/7$

$$P_{1\Omega} = (v_1)^2/1 = \underline{2.041 \text{ watts}}, \quad P_{2\Omega} = (v_2)^2/2 = \underline{4.939 \text{ watts}}$$

$$P_{4\Omega} = (10 - v_1)^2/4 = \underline{18.38 \text{ watts}}, \quad P_{8\Omega} = (10 - v_2)^2/8 = \underline{5.88 \text{ watts}}$$

### Chapter 3, Solution 61

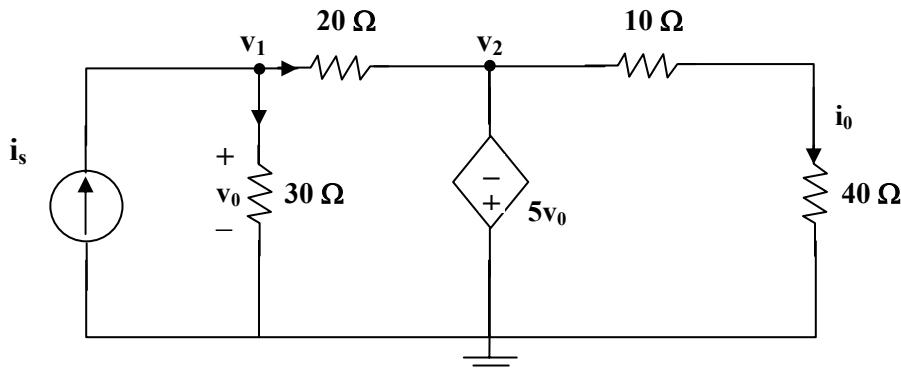


At node 1,  $i_s = (v_1/30) + ((v_1 - v_2)/20)$  which leads to  $60i_s = 5v_1 - 3v_2 \quad (1)$

But  $v_2 = -5v_0$  and  $v_0 = v_1$  which leads to  $v_2 = -5v_1$

Hence,  $60i_s = 5v_1 + 15v_1 = 20v_1$  which leads to  $v_1 = 3i_s, v_2 = -15i_s$

$$i_0 = v_2/50 = -15i_s/50 \text{ which leads to } i_0/i_s = -15/50 = \underline{-0.3}$$

### Chapter 3, Solution 62

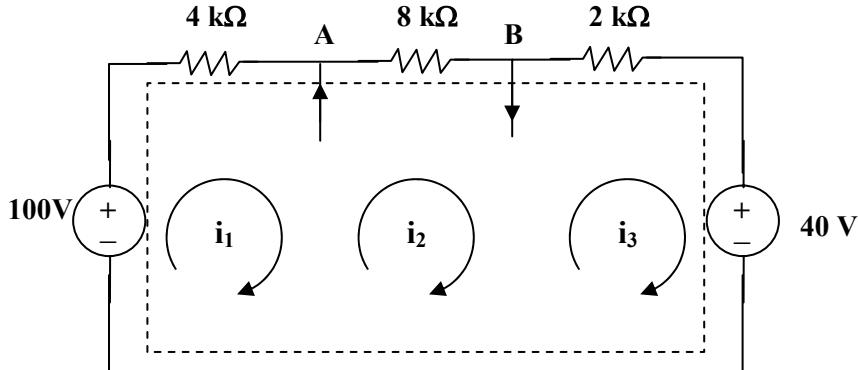

We have a supermesh. Let all R be in  $k\Omega$ , i in mA, and v in volts.


$$\text{For the supermesh, } -100 + 4i_1 + 8i_2 + 2i_3 + 40 = 0 \text{ or } 30 = 2i_1 + 4i_2 + i_3 \quad (1)$$

$$\text{At node A, } i_1 + 4 = i_2 \quad (2)$$

$$\text{At node B, } i_2 = 2i_1 + i_3 \quad (3)$$

Solving (1), (2), and (3), we get  $i_1 = 2 \text{ mA}$ ,  $i_2 = 6 \text{ mA}$ , and  $i_3 = 2 \text{ mA}$ .

### Chapter 3, Solution 63

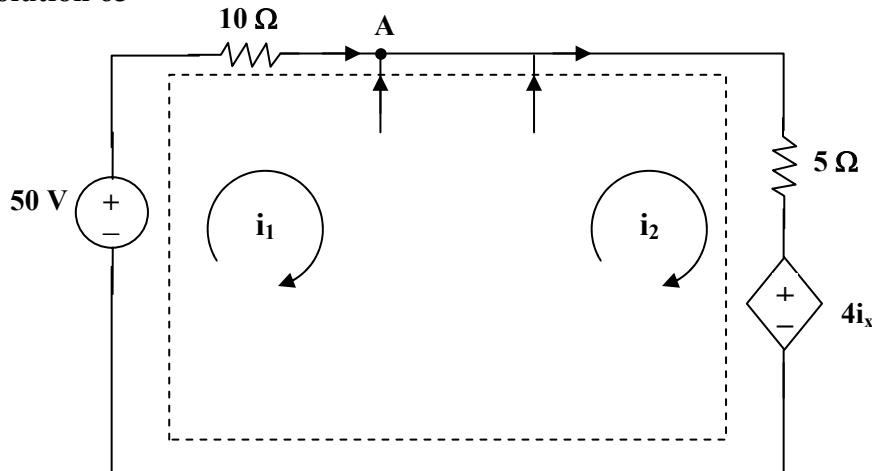

For the supermesh,  $-50 + 10i_1 + 5i_2 + 4i_x = 0$ , but  $i_x = i_1$ . Hence,


$$50 = 14i_1 + 5i_2 \quad (1)$$

$$\text{At node A, } i_1 + 3 + (v_x/4) = i_2, \text{ but } v_x = 2(i_1 - i_2), \text{ hence, } i_1 + 2 = i_2 \quad (2)$$

Solving (1) and (2) gives  $i_1 = 2.105 \text{ A}$  and  $i_2 = 4.105 \text{ A}$

$$v_x = 2(i_1 - i_2) = \underline{\underline{-4 \text{ volts}}} \text{ and } i_x = i_2 - 2 = \underline{\underline{4.105 \text{ amp}}}$$

### Chapter 3, Solution 64

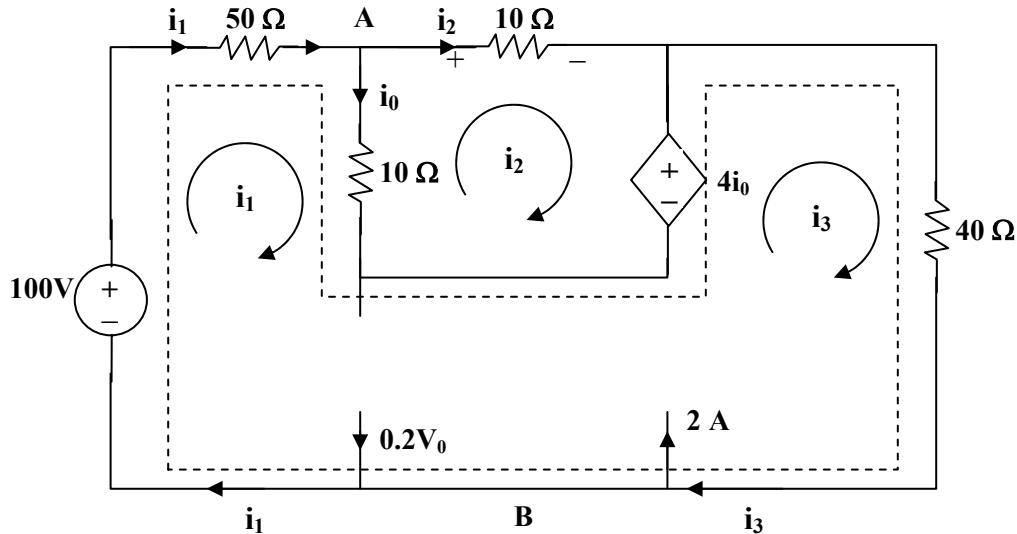

For mesh 2,  $20i_2 - 10i_1 + 4i_0 = 0 \quad (1)$

But at node A,  $i_0 = i_1 - i_2$  so that (1) becomes  $i_1 = (7/12)i_2 \quad (2)$

For the supermesh,  $-100 + 50i_1 + 10(i_1 - i_2) - 4i_0 + 40i_3 = 0$

or  $50 = 28i_1 - 3i_2 + 20i_3 \quad (3)$

At node B,  $i_3 + 0.2v_0 = 2 + i_1 \quad (4)$

But,  $v_0 = 10i_2$  so that (4) becomes  $i_3 = 2 - (17/12)i_2 \quad (5)$

Solving (1) to (5),  $i_2 = -0.674$ ,

$$v_0 = 10i_2 = \underline{\text{-6.74 volts}}, \quad i_0 = i_1 - i_2 = -(5/12)i_2 = \underline{\text{0.281 amps}}$$

### Chapter 3, Solution 65

For mesh 1,  $12 = 12I_1 - 6I_2 - I_4 \quad (1)$

For mesh 2,  $0 = -6I_1 + 16I_2 - 8I_3 - I_4 - I_5 \quad (2)$

For mesh 3,  $9 = -8I_2 + 15I_3 - I_5 \quad (3)$

For mesh 4,  $6 = -I_1 - I_2 + 5I_4 - 2I_5 \quad (4)$

For mesh 5,  $10 = -I_2 - I_3 - 2I_4 + 8I_5 \quad (5)$

Casting (1) to (5) in matrix form gives

$$\begin{pmatrix} 12 & -6 & 0 & 1 & 0 \\ -6 & 16 & -8 & -1 & -1 \\ 0 & -8 & 15 & 0 & -1 \\ -1 & -1 & 0 & 5 & -2 \\ 0 & -1 & -1 & -2 & 8 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \end{pmatrix} = \begin{pmatrix} 12 \\ 0 \\ 9 \\ 6 \\ 10 \end{pmatrix} \longrightarrow AI = B$$

Using MATLAB leads to


$$I = A^{-1}B = \begin{pmatrix} 1.673 \\ 1.824 \\ 1.733 \\ 2.864 \\ 2.411 \end{pmatrix}$$

Thus,

$$\underline{I_1 = 1.673 \text{ A}, I_2 = 1.824 \text{ A}, I_3 = 1.733 \text{ A}, I_4 = 2.864 \text{ A}, I_5 = 2.411 \text{ A}}$$

### Chapter 3, Solution 66

Consider the circuit below.

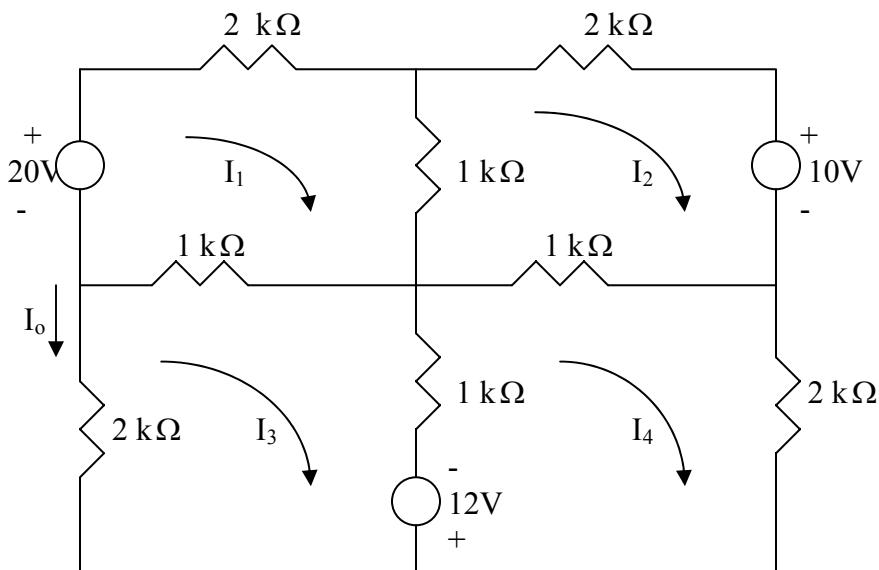

We use mesh analysis. Let the mesh currents be in mA.

$$\text{For mesh 1, } 20 = 4I_1 - I_2 - I_3 \quad (1)$$

$$\text{For mesh 2, } -10 = -I_1 + 4I_2 - I_4 \quad (2)$$

$$\text{For mesh 3, } 12 = -I_1 + 4I_3 - I_4 \quad (3)$$

$$\text{For mesh 4, } -12 = -I_2 - I_3 + 4I_4 \quad (4)$$

In matrix form, (1) to (4) become

$$\begin{pmatrix} 4 & -1 & -1 & 0 \\ -1 & 4 & 0 & -1 \\ -1 & 0 & 4 & -1 \\ 0 & -1 & -1 & 4 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{pmatrix} = \begin{pmatrix} 20 \\ -10 \\ 12 \\ -12 \end{pmatrix} \quad \longrightarrow \quad AI = B$$

Using MATLAB,

$$I = A^{-1}B = \begin{pmatrix} 5.5 \\ -1.75 \\ 3.75 \\ -2.5 \end{pmatrix}$$

Thus,

$$I_o = -I_3 = \underline{-3.75 \text{ mA}}$$

### Chapter 3, Solution 67

$$G_{11} = (1/1) + (1/4) = 1.25, \quad G_{22} = (1/1) + (1/2) = 1.5$$

$$G_{12} = -1 = G_{21}, \quad i_1 = 6 - 3 = 3, \quad i_2 = 5 - 6 = -1$$

Hence, we have,  $\begin{bmatrix} 1.25 & -1 \\ -1 & 1.5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 3 \\ -1 \end{bmatrix}$

$$\begin{bmatrix} 1.25 & -1 \\ -1 & 1.5 \end{bmatrix}^{-1} = \frac{1}{\Delta} \begin{bmatrix} 1.5 & 1 \\ 1 & 1.25 \end{bmatrix}, \text{ where } \Delta = [(1.25)(1.5) - (-1)(-1)] = 0.875$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 1.7143 & 1.1429 \\ 1.1429 & 1.4286 \end{bmatrix} \begin{bmatrix} 3 \\ -1 \end{bmatrix} = \begin{bmatrix} 3(1.7143) - 1(1.1429) \\ 3(1.1429) - 1(1.4286) \end{bmatrix} = \begin{bmatrix} 4 \\ 2 \end{bmatrix}$$

Clearly  $v_1 = \underline{\textbf{4 volts}}$  and  $v_2 = \underline{\textbf{2 volts}}$

### Chapter 3, Solution 68

By inspection,  $G_{11} = 1 + 3 + 5 = 8S$ ,  $G_{22} = 1 + 2 = 3S$ ,  $G_{33} = 2 + 5 = 7S$

$G_{12} = -1$ ,  $G_{13} = -5$ ,  $G_{21} = -1$ ,  $G_{23} = -2$ ,  $G_{31} = -5$ ,  $G_{32} = -2$

$i_1 = 4$ ,  $i_2 = 2$ ,  $i_3 = -1$

We can either use matrix inverse as we did in Problem 3.51 or use Cramer's Rule.  
Let us use Cramer's rule for this problem.

First, we develop the matrix relationships.

$$\begin{bmatrix} 8 & -1 & -5 \\ -1 & 3 & -2 \\ -5 & -2 & 7 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 4 \\ 2 \\ -1 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 & -1 & -5 \\ -1 & 3 & -2 \\ -5 & -2 & 7 \end{vmatrix} = 34, \Delta_1 = \begin{vmatrix} 4 & -1 & -5 \\ 2 & 3 & -2 \\ -1 & -2 & 7 \end{vmatrix} = 85$$

$$\Delta_2 = \begin{vmatrix} 8 & 4 & -5 \\ -1 & 2 & -2 \\ -5 & -1 & 7 \end{vmatrix} = 109, \Delta_3 = \begin{vmatrix} 8 & -1 & 4 \\ -1 & 3 & 2 \\ -5 & -2 & -1 \end{vmatrix} = 87$$

$$v_1 = \Delta_1 / \Delta = 85 / 34 = \underline{\underline{3.5 \text{ volts}}}, v_2 = \Delta_2 / \Delta = 109 / 34 = \underline{\underline{3.206 \text{ volts}}}$$

$$v_3 = \Delta_3 / \Delta = 87 / 34 = \underline{\underline{2.56 \text{ volts}}}$$

### Chapter 3, Solution 69

Assume that all conductances are in mS, all currents are in mA, and all voltages are in volts.

$$\begin{aligned} G_{11} &= (1/2) + (1/4) + (1/1) = 1.75, \quad G_{22} = (1/4) + (1/4) + (1/2) = 1, \\ G_{33} &= (1/1) + (1/4) = 1.25, \quad G_{12} = -1/4 = -0.25, \quad G_{13} = -1/1 = -1, \\ G_{21} &= -0.25, \quad G_{23} = -1/4 = -0.25, \quad G_{31} = -1, \quad G_{32} = -0.25 \end{aligned}$$

$$i_1 = 20, \quad i_2 = 5, \text{ and } i_3 = 10 - 5 = 5$$

The node-voltage equations are:

$$\begin{bmatrix} 1.75 & -0.25 & -1 \\ -0.25 & 1 & -0.25 \\ -1 & -0.25 & 1.25 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \\ 5 \end{bmatrix}$$

---

### Chapter 3, Solution 70

$$\begin{aligned} G_{11} &= G_1 + G_2 + G_4, \quad G_{12} = -G_2, \quad G_{13} = 0, \\ G_{22} &= G_2 + G_3, \quad G_{21} = -G_2, \quad G_{23} = -G_3, \\ G_{33} &= G_1 + G_3 + G_5, \quad G_{31} = 0, \quad G_{32} = -G_3 \end{aligned}$$

$$i_1 = -I_1, \quad i_2 = I_2, \text{ and } i_3 = I_1$$

Then, the node-voltage equations are:

$$\begin{bmatrix} G_1 + G_2 + G_4 & -G_2 & 0 \\ -G_2 & G_1 + G_2 & -G_3 \\ 0 & -G_3 & G_1 + G_3 + G_5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -I_1 \\ I_2 \\ I_1 \end{bmatrix}$$

---

### Chapter 3, Solution 71

$$R_{11} = 4 + 2 = 6, R_{22} = 2 + 8 + 2 = 12, R_{33} = 2 + 5 = 7, \\ R_{12} = -2, R_{13} = 0, R_{21} = -2, R_{23} = -2, R_{31} = 0, R_{32} = -2$$

$$v_1 = 12, v_2 = -8, \text{ and } v_3 = -20$$

Now we can write the matrix relationships for the mesh-current equations.

$$\begin{bmatrix} 6 & -2 & 0 \\ -2 & 12 & -2 \\ 0 & -2 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ -8 \\ -20 \end{bmatrix}$$

Now we can solve for  $i_2$  using Cramer's Rule.

$$\Delta = \begin{vmatrix} 6 & -2 & 0 \\ -2 & 12 & -2 \\ 0 & -2 & 7 \end{vmatrix} = 452, \Delta_2 = \begin{vmatrix} 6 & 12 & 0 \\ -2 & -8 & -2 \\ 0 & -20 & 7 \end{vmatrix} = -408$$

$$i_2 = \Delta_2 / \Delta = -0.9026, P = (i_2)^2 R = \underline{\underline{6.52 \text{ watts}}}$$

### Chapter 3, Solution 72

$$R_{11} = 5 + 2 = 7, R_{22} = 2 + 4 = 6, R_{33} = 1 + 4 = 5, R_{44} = 1 + 4 = 5, \\ R_{12} = -2, R_{13} = 0 = R_{14}, R_{21} = -2, R_{23} = -4, R_{24} = 0, R_{31} = 0, \\ R_{32} = -4, R_{34} = -1, R_{41} = 0 = R_{42}, R_{43} = -1, \text{ we note that } R_{ij} = R_{ji} \text{ for all } i \neq j.$$

$$v_1 = 8, v_2 = 4, v_3 = -10, \text{ and } v_4 = -4$$

Hence the mesh-current equations are:

$$\begin{bmatrix} 7 & -2 & 0 & 0 \\ -2 & 6 & -4 & 0 \\ 0 & -4 & 5 & -1 \\ 0 & 0 & -1 & 5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 8 \\ 4 \\ -10 \\ -4 \end{bmatrix}$$


---

### Chapter 3, Solution 73

$$R_{11} = 2 + 3 + 4 = 9, R_{22} = 3 + 5 = 8, R_{33} = 1 + 4 = 5, R_{44} = 1 + 1 = 2, \\ R_{12} = -3, R_{13} = -4, R_{14} = 0, R_{23} = 0, R_{24} = 0, R_{34} = -1$$

$$v_1 = 6, v_2 = 4, v_3 = 2, \text{ and } v_4 = -3$$

Hence,

$$\begin{bmatrix} 9 & -3 & -4 & 0 \\ -3 & 8 & 0 & 0 \\ -4 & 0 & 6 & -1 \\ 0 & 0 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 6 \\ 4 \\ 2 \\ -3 \end{bmatrix}$$


---

### Chapter 3, Solution 74

$$R_{11} = R_1 + R_4 + R_6, R_{22} = R_2 + R_4 + R_5, R_{33} = R_6 + R_7 + R_8, \\ R_{44} = R_3 + R_5 + R_8, R_{12} = -R_4, R_{13} = -R_6, R_{14} = 0, R_{23} = 0, \\ R_{24} = -R_5, R_{34} = -R_8, \text{ again, we note that } R_{ij} = R_{ji} \text{ for all } i \neq j.$$

$$\text{The input voltage vector is } = \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ -V_4 \end{bmatrix}$$


$$\begin{bmatrix} R_1 + R_4 + R_6 & -R_4 & -R_6 & 0 \\ -R_4 & R_2 + R_4 + R_5 & 0 & -R_5 \\ -R_6 & 0 & R_6 + R_7 + R_8 & -R_8 \\ 0 & -R_5 & -R_8 & R_3 + R_5 + R_8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ -V_4 \end{bmatrix}$$


---
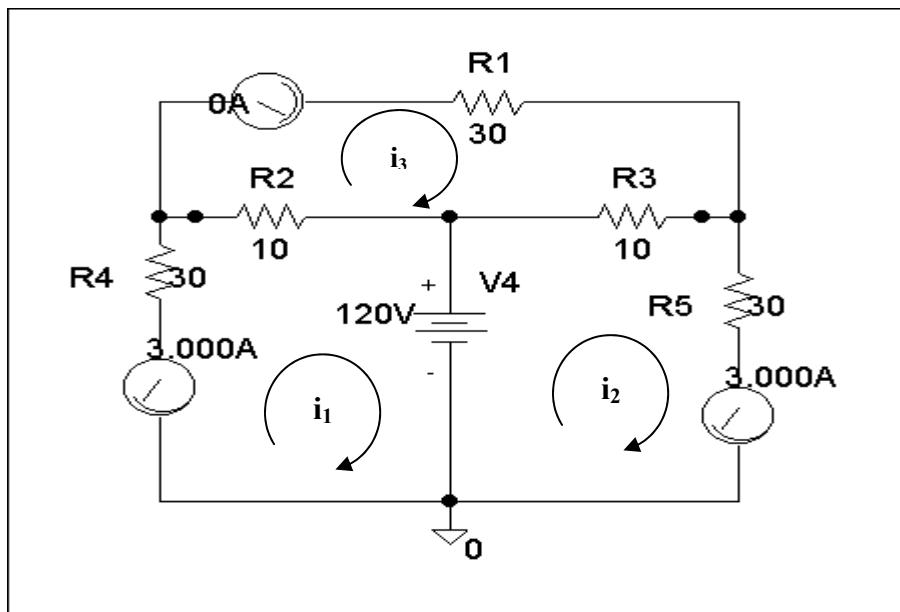
### Chapter 3, Solution 75

\* Schematics Netlist \*

```
R_R4      $N_0002 $N_0001 30
R_R2      $N_0001 $N_0003 10
R_R1      $N_0005 $N_0004 30
R_R3      $N_0003 $N_0004 10
R_R5      $N_0006 $N_0004 30
V_V4      $N_0003 0 120V
v_V3      $N_0005 $N_0001 0
v_V2      0 $N_0006 0
v_V1      0 $N_0002 0
```




Clearly,  $i_1 = \underline{-3 \text{ amps}}$ ,  $i_2 = \underline{0 \text{ amps}}$ , and  $i_3 = \underline{3 \text{ amps}}$ , which agrees with the answers in Problem 3.44.
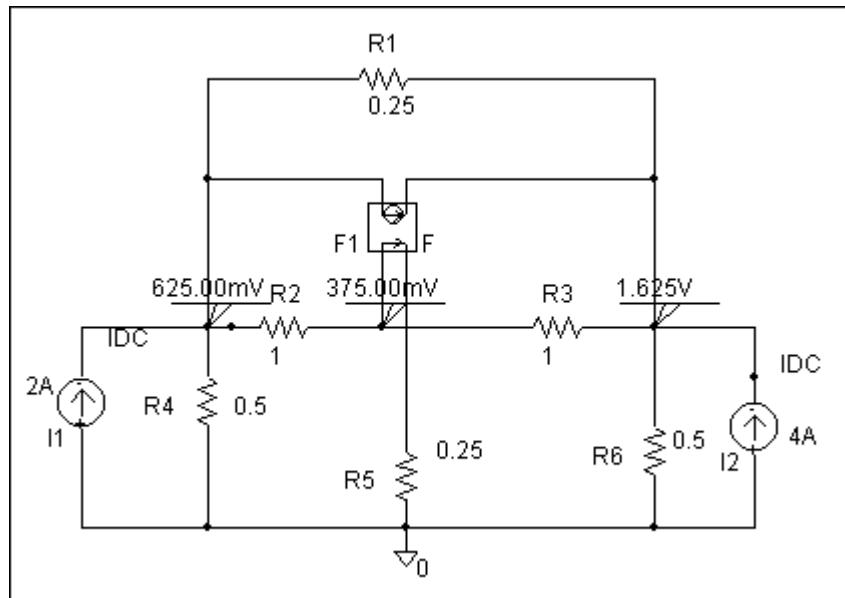
### Chapter 3, Solution 76

\* Schematics Netlist \*

```
I_I2      0 $N_0001 DC 4A
R_R1      $N_0002 $N_0001 0.25
R_R3      $N_0003 $N_0001 1
R_R2      $N_0002 $N_0003 1
F_F1      $N_0002 $N_0001 VF_F1 3
VF_F1     $N_0003 $N_0004 0V
R_R4      0 $N_0002 0.5
R_R6      0 $N_0001 0.5
I_I1      0 $N_0002 DC 2A
R_R5      0 $N_0004 0.25
```




Clearly,  $v_1 = \underline{625 \text{ mVolts}}$ ,  $v_2 = \underline{375 \text{ mVolts}}$ , and  $v_3 = \underline{1.625 \text{ volts}}$ , which agrees with the solution obtained in Problem 3.27.
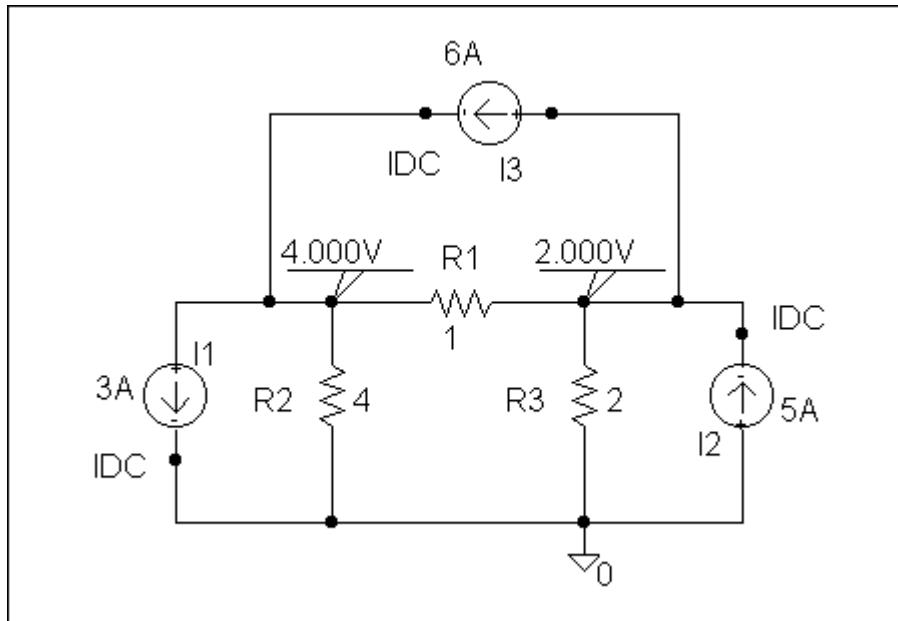
### Chapter 3, Solution 77

\* Schematics Netlist \*

```
R_R2      0 $N_0001 4
I_I1      $N_0001 0 DC 3A
I_I3      $N_0002 $N_0001 DC 6A
R_R3      0 $N_0002 2
R_R1      $N_0001 $N_0002 1
I_I2      0 $N_0002 DC 5A
```




Clearly,  $v_1 = \underline{4 \text{ volts}}$  and  $v_2 = \underline{2 \text{ volts}}$ , which agrees with the answer obtained in Problem 3.51.
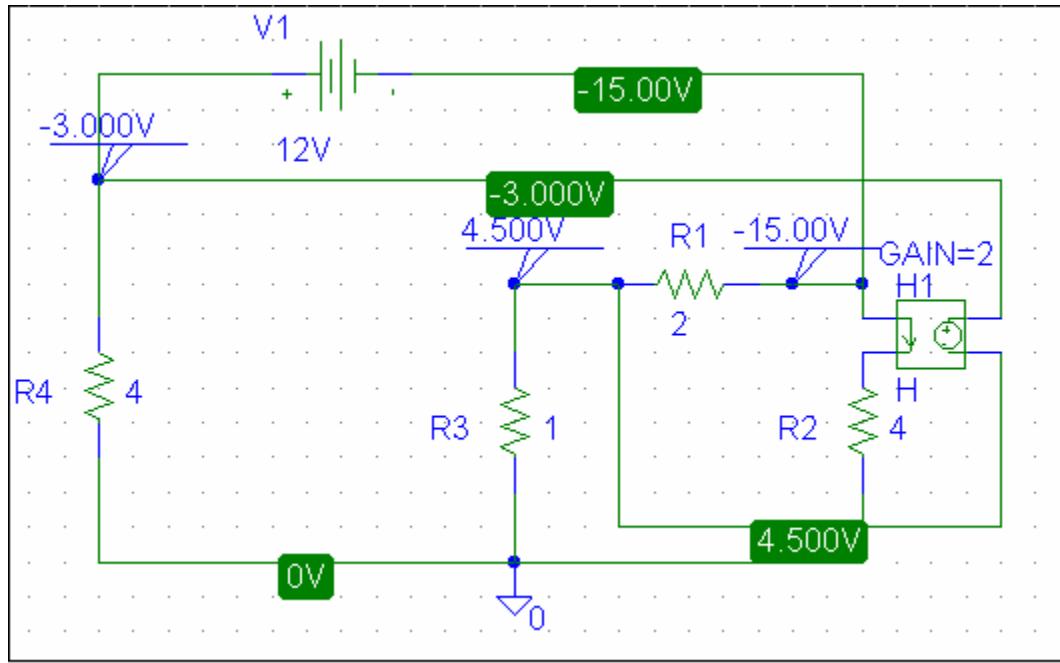
### Chapter 3, Solution 78

The schematic is shown below. When the circuit is saved and simulated the node voltages are displaced on the pseudocomponents as shown. Thus,


$$V_1 = -3V, \quad V_2 = 4.5V, \quad V_3 = -15V,$$


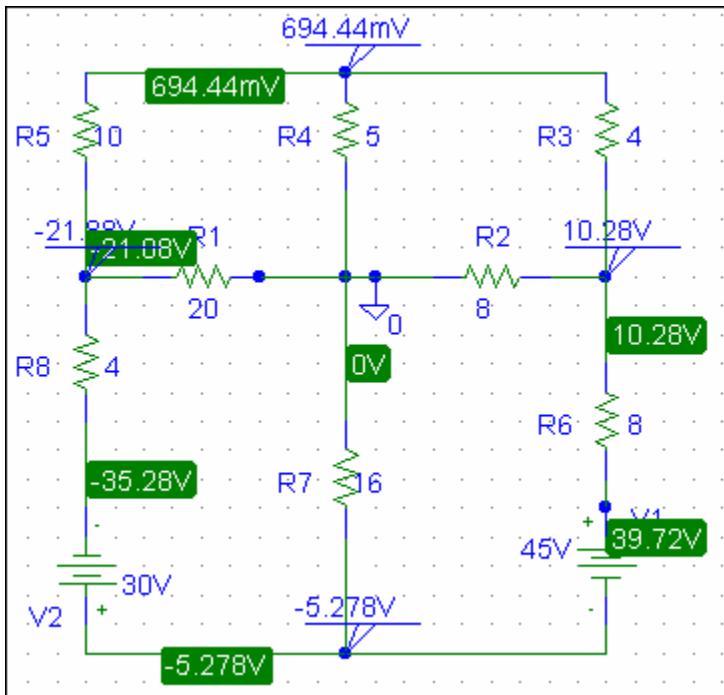
### Chapter 3, Solution 79

The schematic is shown below. When the circuit is saved and simulated, we obtain the node voltages as displayed. Thus,

$$V_a = -5.278 \text{ V}, V_b = 10.28 \text{ V}, V_c = 0.6944 \text{ V}, V_d = -26.88 \text{ V}$$




### Chapter 3, Solution 80

\* Schematics Netlist \*

```


H_H1      $N_0002 $N_0003 VH_H1 6
VH_H1     0 $N_0001 0V
I_I1      $N_0004 $N_0005 DC 8A
V_V1      $N_0002 0 20V
R_R4      0 $N_0003 4
R_R1      $N_0005 $N_0003 10
R_R2      $N_0003 $N_0002 12
R_R5      0 $N_0004 1
R_R3      $N_0004 $N_0001 2

```

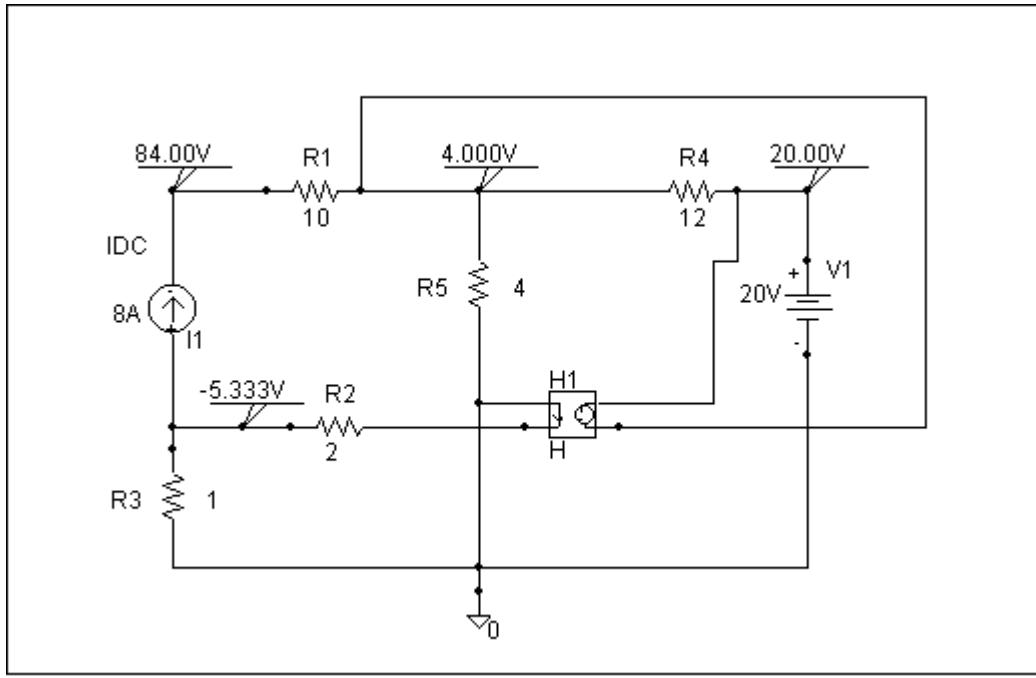

Clearly,  $v_1 = \underline{84 \text{ volts}}$ ,  $v_2 = \underline{4 \text{ volts}}$ ,  $v_3 = \underline{20 \text{ volts}}$ , and  $v_4 = \underline{-5.333 \text{ volts}}$

### Chapter 3, Solution 81

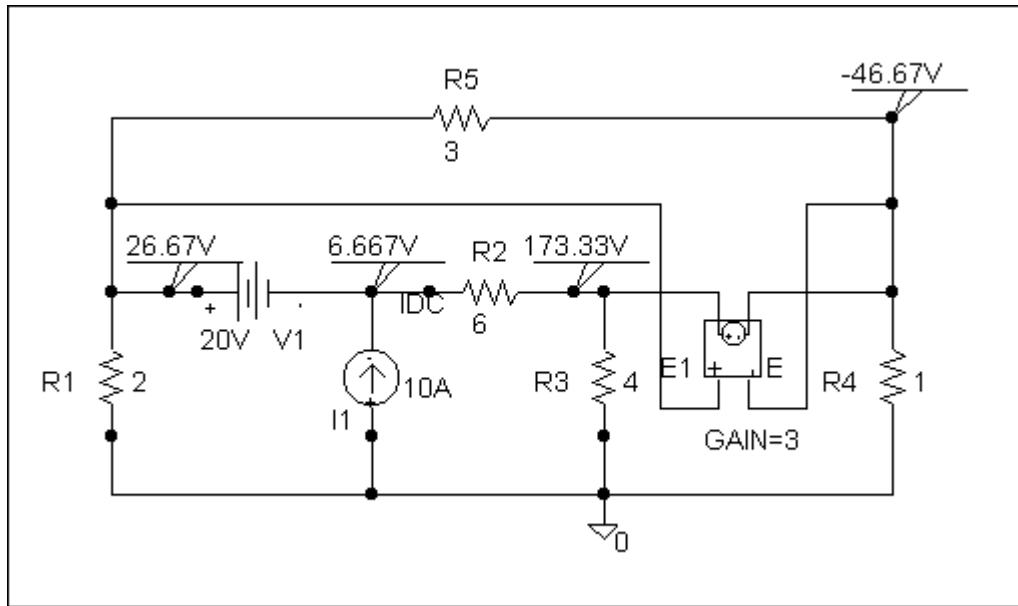


Clearly,  $v_1 = \underline{26.67 \text{ volts}}$ ,  $v_2 = \underline{6.667 \text{ volts}}$ ,  $v_3 = \underline{173.33 \text{ volts}}$ , and  $v_4 = \underline{-46.67 \text{ volts}}$   
which agrees with the results of Example 3.4.

This is the netlist for this circuit.

\* Schematics Netlist \*

```
R_R1      0 $N_0001  2
R_R2      $N_0003 $N_0002  6
R_R3      0 $N_0002  4
R_R4      0 $N_0004  1
R_R5      $N_0001 $N_0004  3
I_I1      0 $N_0003 DC 10A
V_V1      $N_0001 $N_0003 20V
E_E1      $N_0002 $N_0004 $N_0001 $N_0004 3
```


### Chapter 3, Solution 82

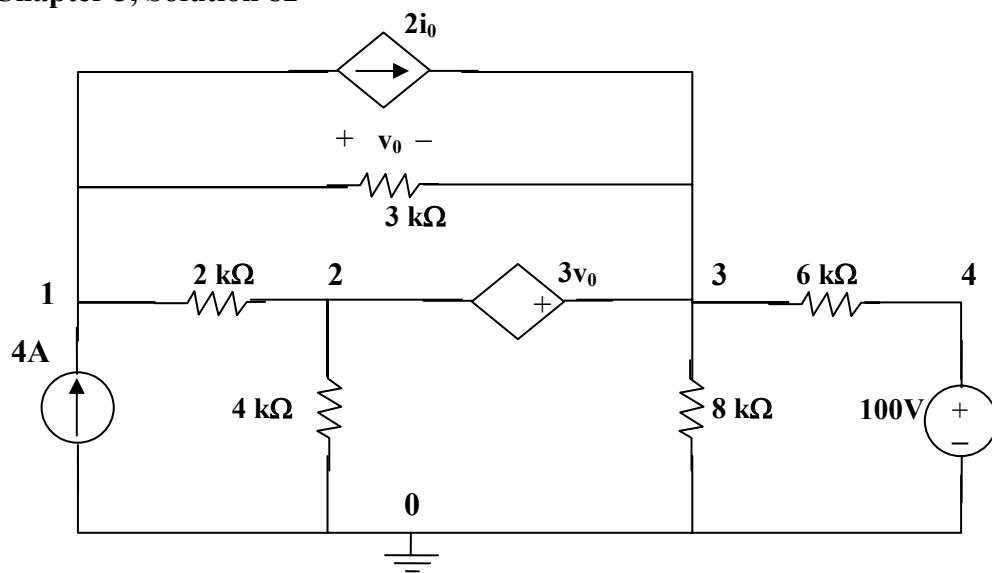

This network corresponds to the Netlist.

### Chapter 3, Solution 83

The circuit is shown below.

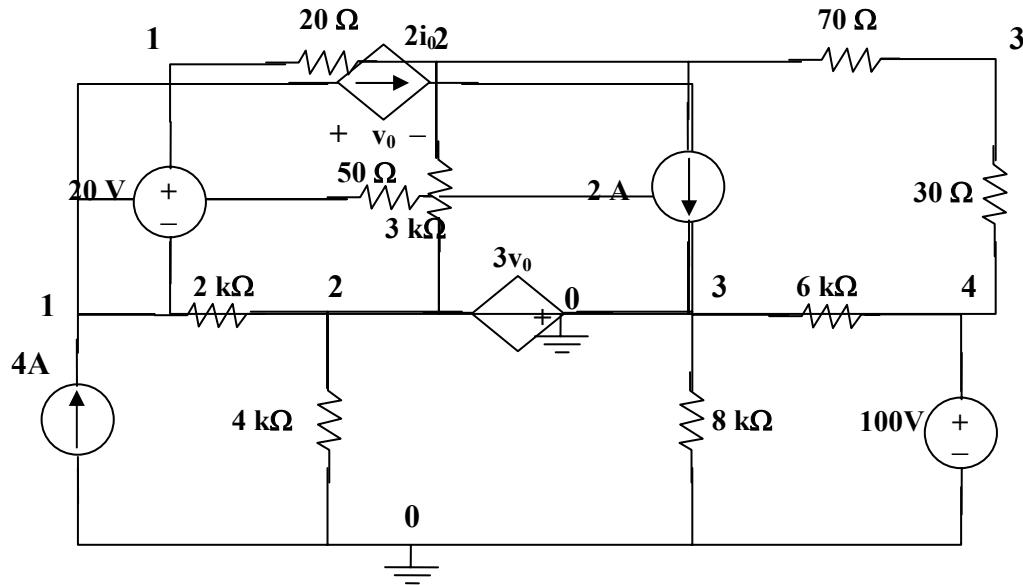

When the circuit is saved and simulated, we obtain  $v_2 = \underline{-12.5 \text{ volts}}$

### Chapter 3, Solution 84


$$\text{From the output loop, } v_0 = 50i_0 \times 20 \times 10^3 = 10^6 i_0 \quad (1)$$

$$\text{From the input loop, } 3 \times 10^{-3} + 4000i_0 - v_0/100 = 0 \quad (2)$$

From (1) and (2) we get,  $i_0 = \underline{0.5\mu\text{A}}$  and  $v_0 = \underline{0.5 \text{ volt}}$ .

### Chapter 3, Solution 85

The amplifier acts as a source.

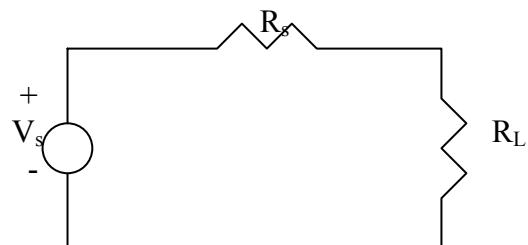

For maximum power transfer,

$$R_L = R_s = \underline{9\Omega}$$

### Chapter 3, Solution 86

Let  $v_1$  be the potential across the 2 k-ohm resistor with plus being on top. Then,

$$[(0.03 - v_1)/1k] + 400i = v_1/2k \quad (1)$$

$$\text{Assume that } i \text{ is in mA. But, } i = (0.03 - v_1)/1 \quad (2)$$

Combining (1) and (2) yields,

$$v_1 = 29.963 \text{ mVolts and } i = 37.4 \text{ nA, therefore,}$$

$$v_0 = -5000 \times 400 \times 37.4 \times 10^{-9} = \underline{\underline{-74.8 \text{ mvolts}}}$$

### Chapter 3, Solution 87

$$v_1 = 500(v_s)/(500 + 2000) = v_s/5$$

$$v_0 = -400(60v_1)/(400 + 2000) = -40v_1 = -40(v_s/5) = -8v_s,$$

$$\text{Therefore, } v_0/v_s = \underline{\underline{-8}}$$

### Chapter 3, Solution 88

Let  $v_1$  be the potential at the top end of the 100-ohm resistor.

$$(v_s - v_1)/200 = v_1/100 + (v_1 - 10^{-3}v_0)/2000 \quad (1)$$

$$\text{For the right loop, } v_0 = -40i_0(10,000) = -40(v_1 - 10^{-3})10,000/2000,$$

$$\text{or, } v_0 = -200v_1 + 0.2v_0 = -4 \times 10^{-3}v_0 \quad (2)$$

Substituting (2) into (1) gives,

$$(v_s + 0.004v_1)/2 = -0.004v_0 + (-0.004v_1 - 0.001v_0)/20$$

$$\text{This leads to } 0.125v_0 = 10v_s \text{ or } (v_0/v_s) = 10/0.125 = \underline{\underline{-80}}$$


### Chapter 3, Solution 89

$$v_i = V_{BE} + 40k I_B \quad (1)$$


$$5 = V_{CE} + 2k I_C \quad (2)$$

If  $I_C = \beta I_B = 75 I_B$  and  $V_{CE} = 2$  volts, then (2) becomes  $5 = 2 + 2k(75 I_B)$  which leads to  $I_B = 20 \mu A$ .

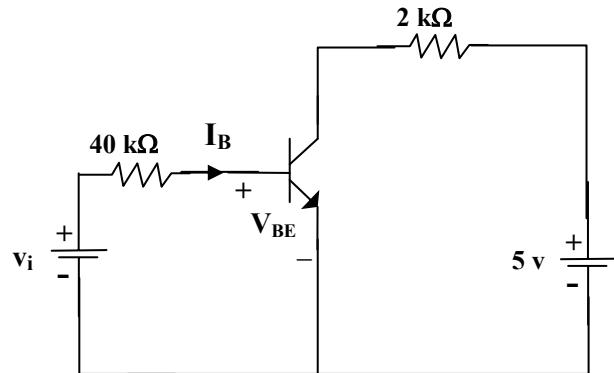Substituting this into (1) produces,  $v_i = 0.7 + 0.8 = \underline{1.5 \text{ volts}}$ .



### Chapter 3, Solution 90

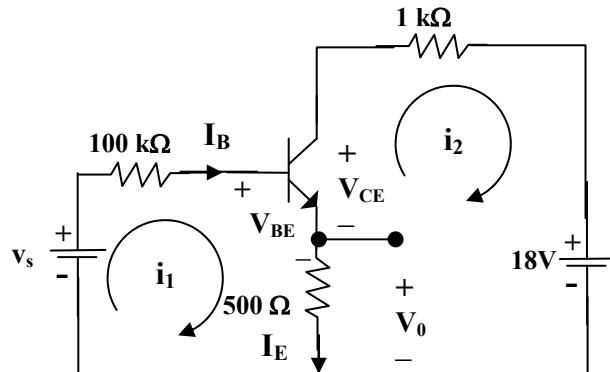

$$\text{For loop 1, } -v_s + 10k(I_B) + V_{BE} + I_E(500) = 0 = -v_s + 0.7 + 10,000I_B + 500(1 + \beta)I_B$$

$$\text{which leads to } v_s + 0.7 = 10,000I_B + 500(151)I_B = 85,500I_B$$


$$\text{But, } v_0 = 500I_E = 500 \times 151I_B = 4 \text{ which leads to } I_B = 5.298 \times 10^{-5}$$

$$\text{Therefore, } v_s = 0.7 + 85,500I_B = \underline{5.23 \text{ volts}}$$
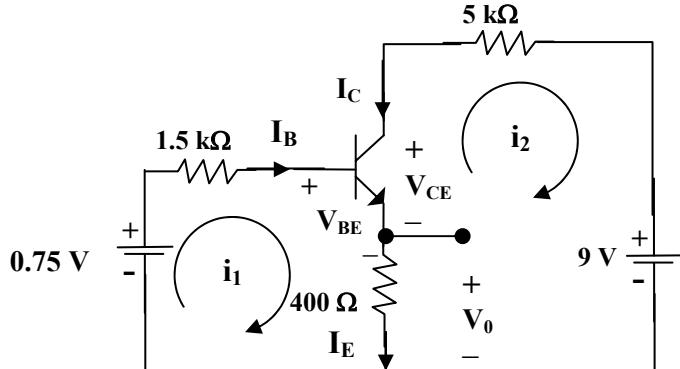
### Chapter 3, Solution 91

We first determine the Thevenin equivalent for the input circuit.

$$R_{Th} = 6\parallel 2 = 6 \times 2 / 8 = 1.5 \text{ k}\Omega \text{ and } V_{Th} = 2(3)/(2+6) = 0.75 \text{ volts}$$



$$\text{For loop 1, } -0.75 + 1.5kI_B + V_{BE} + 400I_E = 0 = -0.75 + 0.7 + 1500I_B + 400(1 + \beta)I_B$$


$$I_B = 0.05/81,900 = \underline{\underline{0.61 \mu A}}$$

$$v_0 = 400I_E = 400(1 + \beta)I_B = \underline{\underline{49 \text{ mV}}}$$

$$\text{For loop 2, } -400I_E - V_{CE} - 5kI_C + 9 = 0, \text{ but, } I_C = \beta I_B \text{ and } I_E = (1 + \beta)I_B$$

$$V_{CE} = 9 - 5k\beta I_B - 400(1 + \beta)I_B = 9 - 0.659 = \underline{\underline{8.641 \text{ volts}}}$$

### Chapter 3, Solution 92

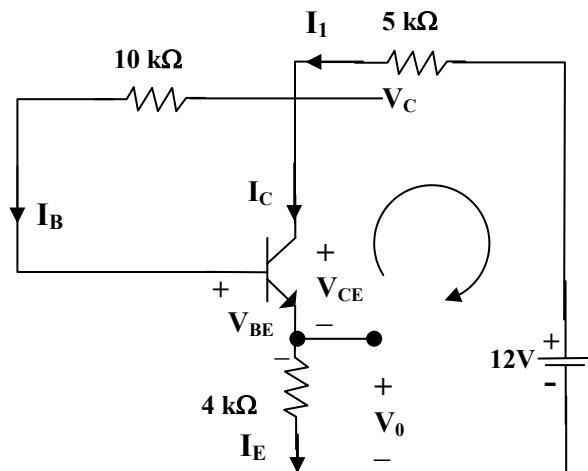

$$I_1 = I_B + I_C = (1 + \beta)I_B \quad \text{and} \quad I_E = I_B + I_C = I_1$$

Applying KVL around the outer loop,


$$4kI_E + V_{BE} + 10kI_B + 5kI_1 = 12$$

$$12 - 0.7 = 5k(1 + \beta)I_B + 10kI_B + 4k(1 + \beta)I_B = 919kI_B$$

$$I_B = 11.3/919k = 12.296 \mu A$$

Also,  $12 = 5kI_1 + V_C$  which leads to  $V_C = 12 - 5k(101)I_B = \underline{\underline{5.791 \text{ volts}}}$

## Chapter 3, Solution 93

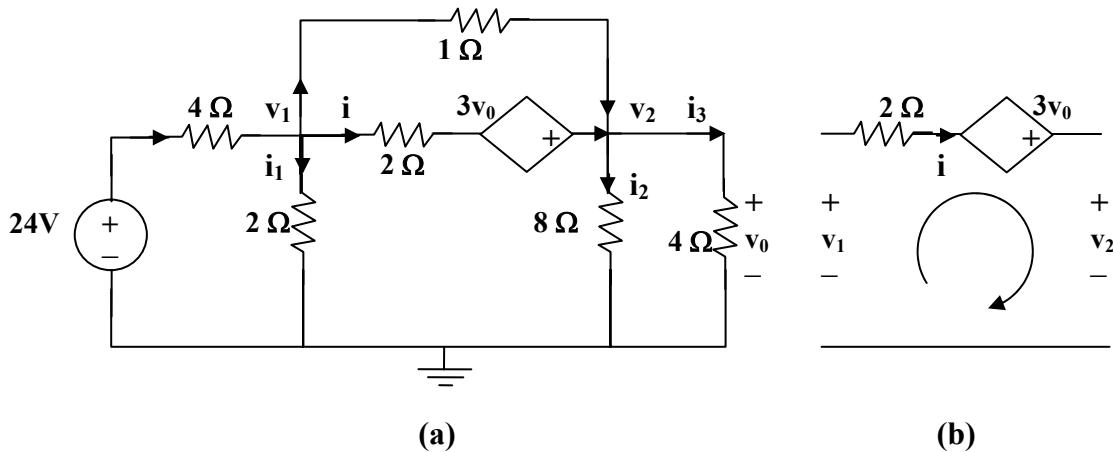

From (b),  $-v_1 + 2i - 3v_0 + v_2 = 0$  which leads to  $i = (v_1 + 3v_0 - v_2)/2$

At node 1 in (a),  $((24 - v_1)/4) = (v_1/2) + ((v_1 + 3v_0 - v_2)/2) + ((v_1 - v_2)/1)$ , where  $v_0 = v_2$

or  $24 = 9v_1$  which leads to  $v_1 = \underline{2.667 \text{ volts}}$

$$\text{At node 2, } ((v_1 - v_2)/1) + ((v_1 + 3v_0 - v_2)/2) = (v_2/8) + v_2/4, \quad v_0 = v_2$$

$$V_2 = 4V_1 = \underline{\underline{10.66 \text{ volts}}}$$

Now we can solve for the currents,  $i_1 = v_1/2 = \underline{1.333\text{ A}}$ ,  $i_2 = \underline{1.333\text{ A}}$ , and

$$i_3 = 2.6667 \text{ A.}$$