

### **Chapter 6, Solution 1.**

$$i = C \frac{dv}{dt} = 5(2e^{-3t} - 6 + e^{-3t}) = \underline{10(1 - 3t)e^{-3t} A}$$

$$p = vi = 10(1-3t)e^{-3t} \cdot 2t e^{-3t} = \underline{20t(1 - 3t)e^{-6t} W}$$

### **Chapter 6, Solution 2.**

$$w_1 = \frac{1}{2} Cv_1^2 = \frac{1}{2}(40)(120)^2$$

$$w_2 = \frac{1}{2} Cv_1^2 = \frac{1}{2}(40)(80)^2$$

$$\Delta w = w_1 - w_2 = 20(120^2 - 80^2) = \underline{160 \text{ kW}}$$

### **Chapter 6, Solution 3.**

$$i = C \frac{dv}{dt} = 40 \times 10^{-3} \frac{280 - 160}{5} = \underline{480 \text{ mA}}$$

### **Chapter 6, Solution 4.**

$$v = \frac{1}{C} \int_0^t idt + v(0)$$

$$= \frac{1}{2} \int 6 \sin 4t dt + 1$$

$$= \underline{1 - 0.75 \cos 4t}$$

### **Chapter 6, Solution 5.**

$$v = \frac{1}{C} \int_0^t idt + v(0)$$

For  $0 < t < 1$ ,  $i = 4t$ ,

$$v = \frac{1}{20 \times 10^{-6}} \int_0^t 4t dt + 0 = 100t^2 \text{ kV}$$

$$v(1) = 100 \text{ kV}$$

For  $1 < t < 2$ ,  $i = 8 - 4t$ ,

$$v = \frac{1}{20 \times 10^{-6}} \int_1^t (8 - 4t) dt + v(1)$$

$$= 100 (4t - t^2 - 3) + 100 \text{ kV}$$

Thus  $v(t) = \begin{cases} 100t^2 \text{kV}, & 0 < t < 1 \\ 100(4t - t^2 - 2) \text{kV}, & 1 < t < 2 \end{cases}$

### Chapter 6, Solution 6.


$$i = C \frac{dv}{dt} = 30 \times 10^{-6} \times \text{slope of the waveform.}$$

For example, for  $0 < t < 2$ ,

$$\frac{dv}{dt} = \frac{10}{2 \times 10^{-3}}$$

$$i = C \frac{dv}{dt} = 30 \times 10^{-6} \times \frac{10}{2 \times 10^{-3}} = 150 \text{ mA}$$

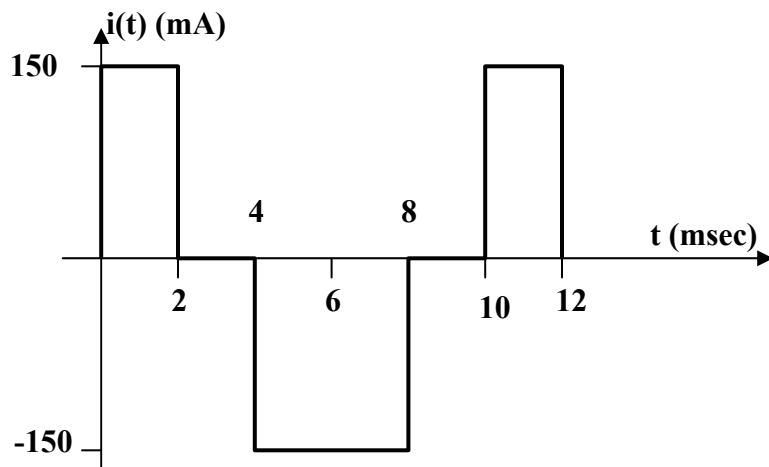Thus the current  $i$  is sketched below.



### Chapter 6, Solution 7.

$$v = \frac{1}{C} \int i dt + v(t_0) = \frac{1}{50 \times 10^{-3}} \int_0^t 4t \times 10^{-3} dt + 10$$

$$= \frac{2t^2}{50} + 10 = \underline{\underline{0.04k^2 + 10 \text{ V}}}$$

### Chapter 6, Solution 8.

$$(a) \quad i = C \frac{dv}{dt} = -100ACe^{-100t} - 600BCe^{-600t} \quad (1)$$

$$i(0) = 2 = -100AC - 600BC \quad \longrightarrow \quad 5 = -A - 6B \quad (2)$$

$$v(0^+) = v(0^-) \quad \longrightarrow \quad 50 = A + B \quad (3)$$

Solving (2) and (3) leads to

$$\underline{A=61, \quad B=-11}$$

$$(b) \quad \text{Energy} = \frac{1}{2} Cv^2(0) = \frac{1}{2} x 4x10^{-3} x 2500 = \underline{5 \text{ J}}$$

(c) From (1),

$$i = -100x61x4x10^{-3}e^{-100t} - 600x11x4x10^{-3}e^{-600t} = \underline{-24.4e^{-100t} - 26.4e^{-600t} \text{ A}}$$

### Chapter 6, Solution 9.

$$v(t) = \frac{1}{1/2} \int_0^t 6(1 - e^{-t}) dt + 0 = 12(t + e^{-t})V$$

$$v(2) = 12(2 + e^{-2}) = \underline{25.62 \text{ V}}$$

$$p = iv = 12(t + e^{-t}) 6(1 - e^{-t}) = 72(t - e^{-2t})$$

$$p(2) = 72(2 - e^{-4}) = \underline{142.68 \text{ W}}$$

### Chapter 6, Solution 10

$$i = C \frac{dv}{dt} = 2x10^{-3} \frac{dv}{dt}$$

$$v = \begin{cases} 16t, & 0 < t < 1 \mu s \\ 16, & 1 < t < 3 \mu s \\ 64 - 16t, & 3 < t < 4 \mu s \end{cases}$$

$$\frac{dv}{dt} = \begin{cases} 16 \times 10^6, & 0 < t < 1 \mu s \\ 0, & 1 < t < 3 \mu s \\ -16 \times 10^6, & 3 < t < 4 \mu s \end{cases}$$


---


$$i(t) = \begin{cases} 32 \text{ kA}, & 0 < t < 1 \mu s \\ 0, & 1 < t < 3 \mu s \\ -32 \text{ kA}, & 3 < t < 4 \mu s \end{cases}$$

### Chapter 6, Solution 11.

$$v = \frac{1}{C} \int_0^t i dt + v(0)$$

For  $0 < t < 1$ ,

$$v = \frac{1}{4 \times 10^{-6}} \int_0^t 40 \times 10^{-3} dt = 10t \text{ kV}$$

$$v(1) = 10 \text{ kV}$$

For  $1 < t < 2$ ,

$$v = \frac{1}{C} \int_1^t v dt + v(1) = 10 \text{ kV}$$

For  $2 < t < 3$ ,

$$v = \frac{1}{4 \times 10^{-6}} \int_2^t (-40 \times 10^{-3}) dt + v(2)$$

$$= -10t + 30 \text{ kV}$$

Thus

$$v(t) = \begin{cases} 10t \cdot \text{kV}, & 0 < t < 1 \\ 10 \text{kV}, & 1 < t < 2 \\ -10t + 30 \text{kV}, & 2 < t < 3 \end{cases}$$


---

### Chapter 6, Solution 12.

$$i = C \frac{dv}{dt} = 3 \times 10^{-3} \times 60 (4\pi) (-\sin 4\pi t)$$

$$= -0.7e \pi \sin 4\pi t \text{ A}$$


$$P = vi = 60(-0.72)\pi \cos 4\pi t \sin 4\pi t = -21.6\pi \sin 8\pi t \text{ W}$$

$$W = \int_0^t P dt = -\int_0^{\frac{1}{8}} 21.6\pi \sin 8\pi t dt$$

$$= \frac{21.6\pi}{8\pi} \cos 8\pi \Big|_0^{1/8} = -5.4 \text{ J}$$
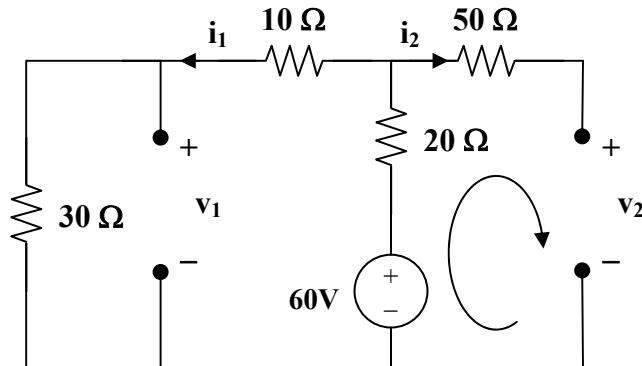
### Chapter 6, Solution 13.

Under dc conditions, the circuit becomes that shown below:



$$i_2 = 0, i_1 = 60/(30+10+20) = 1A$$

$$v_1 = 30i_2 = 30V, v_2 = 60 - 20i_1 = 40V$$

$$\text{Thus, } \underline{v_1 = 30V, v_2 = 40V}$$

### Chapter 6, Solution 14.


$$(a) C_{eq} = 4C = \underline{120 \text{ mF}}$$

$$(b) \frac{1}{C_{eq}} = \frac{4}{C} = \frac{4}{30} \longrightarrow C_{eq} = \underline{7.5 \text{ mF}}$$

### Chapter 6, Solution 15.

In parallel, as in Fig. (a),

$$v_1 = v_2 = 100$$

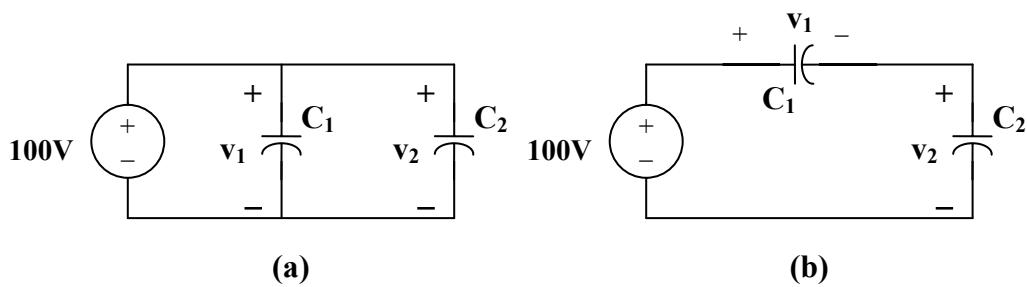

$$w_{20} = \frac{1}{2} C v^2 = \frac{1}{2} \times 20 \times 10^{-6} \times 100^2 = \underline{\underline{0.1J}}$$

$$w_{30} = \frac{1}{2} \times 30 \times 10^{-6} \times 100^2 = \underline{\underline{0.15J}}$$

(b) When they are connected in series as in Fig. (b):

$$v_1 = \frac{C_2}{C_1 + C_2} V = \frac{30}{50} \times 100 = 60, v_2 = 40$$

$$w_{20} = \frac{1}{2} \times 30 \times 10^{-6} \times 60^2 = \underline{\underline{36 mJ}}$$

$$w_{30} = \frac{1}{2} \times 30 \times 10^{-6} \times 40^2 = \underline{\underline{24 mJ}}$$

### Chapter 6, Solution 16

$$C_{eq} = 14 + \frac{Cx80}{C + 80} = 30 \quad \longrightarrow \quad \underline{\underline{C = 20 \mu F}}$$

### Chapter 6, Solution 17.

- (a) 4F in series with 12F =  $4 \times 12 / (16) = 3F$   
 3F in parallel with 6F and  $3F = 3+6+3 = 12F$   
 4F in series with 12F = 3F

i.e.  $C_{eq} = \underline{\underline{3F}}$

- (b)  $C_{eq} = 5 + [6 \parallel (4 + 2)] = 5 + (6 \parallel 6) = 5 + 3 = \underline{\underline{8F}}$   
 (c) 3F in series with 6F =  $(3 \times 6) / 9 = 6F$

$$\frac{1}{C_{eq}} = \frac{1}{2} + \frac{1}{6} + \frac{1}{3} = 1$$

$$C_{eq} = \underline{\underline{1F}}$$

### Chapter 6, Solution 18.

For the capacitors in parallel

$$C_{\text{eq}}^1 = 15 + 5 + 40 = 60 \mu\text{F}$$

Hence  $\frac{1}{C_{\text{eq}}} = \frac{1}{20} + \frac{1}{30} + \frac{1}{60} = \frac{1}{10}$


$$C_{\text{eq}} = \underline{\underline{10 \mu\text{F}}}$$

### Chapter 6, Solution 19.

We combine 10-, 20-, and 30-  $\mu\text{F}$  capacitors in parallel to get  $60 \mu\text{F}$ . The  $60 - \mu\text{F}$  capacitor in series with another  $60 - \mu\text{F}$  capacitor gives  $30 \mu\text{F}$ .

$$30 + 50 = 80 \mu\text{F}, \quad 80 + 40 = 120 \mu\text{F}$$

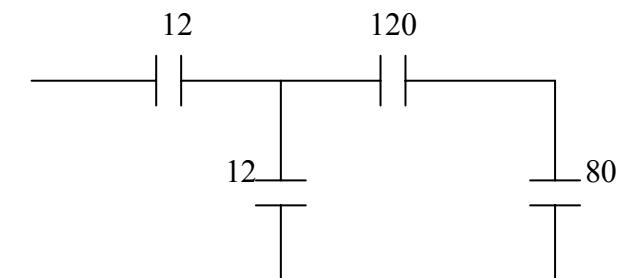The circuit is reduced to that shown below.



$120 - \mu\text{F}$  capacitor in series with  $80 \mu\text{F}$  gives  $(80 \times 120) / 200 = 48$

$$48 + 12 = 60$$

$60 - \mu\text{F}$  capacitor in series with  $12 \mu\text{F}$  gives  $(60 \times 12) / 72 = \underline{\underline{10 \mu\text{F}}}$


### Chapter 6, Solution 20.

$$3 \text{ in series with } 6 = 6x^3/(9) = 2$$

$$2 \text{ in parallel with } 2 = 4$$

$$4 \text{ in series with } 4 = (4 \times 4) / 8 = 2$$

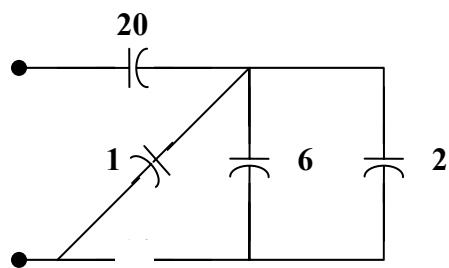The circuit is reduced to that shown below:



6 in parallel with 2 = 8  
 8 in series with 8 = 4  
 4 in parallel with 1 = 5  
 5 in series with 20 =  $(5 \times 20) / 25 = 4$

Thus  $C_{eq} = \underline{4 \text{ mF}}$


### Chapter 6, Solution 21.

$4\mu\text{F}$  in series with  $12\mu\text{F} = (4 \times 12) / 16 = 3\mu\text{F}$   
 $3\mu\text{F}$  in parallel with  $3\mu\text{F} = 6\mu\text{F}$   
 $6\mu\text{F}$  in series with  $6\mu\text{F} = 3\mu\text{F}$   
 $3\mu\text{F}$  in parallel with  $2\mu\text{F} = 5\mu\text{F}$   
 $5\mu\text{F}$  in series with  $5\mu\text{F} = 2.5\mu\text{F}$

Hence  $C_{eq} = \underline{2.5\mu\text{F}}$
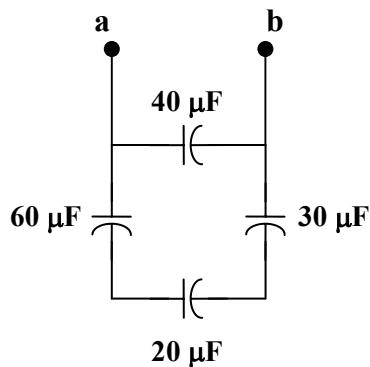
### Chapter 6, Solution 22.

Combining the capacitors in parallel, we obtain the equivalent circuit shown below:



Combining the capacitors in series gives  $C_{eq}^1$ , where

$$\frac{1}{C_{eq}^1} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10} \longrightarrow C_{eq}^1 = 10\mu\text{F}$$

Thus

$$C_{eq} = 10 + 40 = \underline{50\mu\text{F}}$$

### Chapter 6, Solution 23.

(a)  $3\mu F$  is in series with  $6\mu F$        $3 \times 6 / (9) = 2\mu F$

$$v_{4\mu F} = 1/2 \times 120 = \underline{\underline{60V}}$$

$$v_{2\mu F} = \underline{\underline{60V}}$$

$$v_{6\mu F} = \frac{3}{6+3}(60) = \underline{\underline{20V}}$$

$$v_{3\mu F} = 60 - 20 = \underline{\underline{40V}}$$

(b) Hence  $w = 1/2 Cv^2$

$$w_{4\mu F} = 1/2 \times 4 \times 10^{-6} \times 3600 = \underline{\underline{7.2mJ}}$$

$$w_{2\mu F} = 1/2 \times 2 \times 10^{-6} \times 3600 = \underline{\underline{3.6mJ}}$$

$$w_{6\mu F} = 1/2 \times 6 \times 10^{-6} \times 400 = \underline{\underline{1.2mJ}}$$

$$w_{3\mu F} = 1/2 \times 3 \times 10^{-6} \times 1600 = \underline{\underline{2.4mJ}}$$

### Chapter 6, Solution 24.

$20\mu F$  is series with  $80\mu F = 20 \times 80 / (100) = 16\mu F$

$14\mu F$  is parallel with  $16\mu F = 30\mu F$

(a)  $v_{30\mu F} = \underline{\underline{90V}}$

$$v_{60\mu F} = \underline{\underline{30V}}$$

$$v_{14\mu F} = \underline{\underline{60V}}$$

$$v_{20\mu F} = \frac{80}{20+80} \times 60 = \underline{\underline{48V}}$$

$$v_{80\mu F} = 60 - 48 = \underline{\underline{12V}}$$

(b) Since  $w = \frac{1}{2} Cv^2$

$$w_{30\mu F} = 1/2 \times 30 \times 10^{-6} \times 8100 = \underline{\underline{121.5mJ}}$$

$$w_{60\mu F} = 1/2 \times 60 \times 10^{-6} \times 900 = \underline{\underline{27mJ}}$$

$$w_{14\mu F} = 1/2 \times 14 \times 10^{-6} \times 3600 = \underline{\underline{25.2mJ}}$$

$$w_{20\mu F} = 1/2 \times 20 \times 10^{-6} \times (48)^2 = \underline{\underline{23.04mJ}}$$

$$w_{80\mu F} = 1/2 \times 80 \times 10^{-6} \times 144 = \underline{\underline{5.76mJ}}$$

### Chapter 6, Solution 25.

(a) For the capacitors in series,

$$Q_1 = Q_2 \longrightarrow C_1 v_1 = C_2 v_2 \longrightarrow \frac{v_1}{v_2} = \frac{C_2}{C_1}$$

$$v_s = v_1 + v_2 = \frac{C_2}{C_1} v_2 + v_2 = \frac{C_1 + C_2}{C_1} v_2 \quad \longrightarrow \quad \underline{\underline{v_2 = \frac{C_1}{C_1 + C_2} v_s}}$$

Similarly,  $v_1 = \frac{C_2}{C_1 + C_2} v_s$

(b) For capacitors in parallel

$$v_1 = v_2 = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$Q_s = Q_1 + Q_2 = \frac{C_1}{C_2} Q_2 + Q_2 = \frac{C_1 + C_2}{C_2} Q_2$$

or

$$Q_2 = \frac{C_2}{C_1 + C_2}$$

$$Q_1 = \frac{C_1}{C_1 + C_2} Q_s$$

$$i = \frac{dQ}{dt} \longrightarrow \underline{\underline{i_1 = \frac{C_1}{C_1 + C_2} i_s}}, \quad \underline{\underline{i_2 = \frac{C_2}{C_1 + C_2} i_s}}$$

### Chapter 6, Solution 26.

(a)  $C_{eq} = C_1 + C_2 + C_3 = \underline{\underline{35\mu F}}$

(b)  $Q_1 = C_1 V = 5 \times 150\mu C = \underline{\underline{0.75mC}}$

$Q_2 = C_2 V = 10 \times 150\mu C = \underline{\underline{1.5mC}}$

$Q_3 = C_3 V = 20 \times 150 = \underline{\underline{3mC}}$

(c)  $w = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \times 35 \times 150^2 \mu J = \underline{\underline{393.8mJ}}$

### Chapter 6, Solution 27.

$$(a) \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{5} + \frac{1}{10} + \frac{1}{20} = \frac{7}{20}$$

$$C_{eq} = \frac{20}{7} \mu F = \underline{\underline{2.857 \mu F}}$$


(b) Since the capacitors are in series,

$$Q_1 = Q_2 = Q_3 = Q = C_{eq}V = \frac{20}{7} \times 200 \mu V = \underline{\underline{0.5714 mV}}$$

$$(c) \quad w = \frac{1}{2} C_{eq} V^2 = \frac{1}{2} \times \frac{20}{7} \times 200^2 \mu J = \underline{\underline{57.143 mJ}}$$
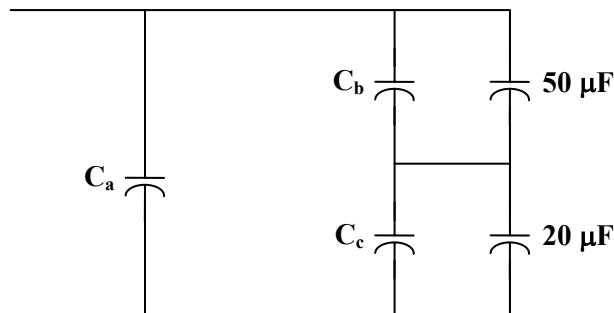
### Chapter 6, Solution 28.

We may treat this like a resistive circuit and apply delta-wye transformation, except that R is replaced by 1/C.



$$\begin{aligned} \frac{1}{C_a} &= \frac{\left(\frac{1}{10}\right)\left(\frac{1}{40}\right)}{\frac{1}{30}} + \frac{\left(\frac{1}{10}\right)\left(\frac{1}{30}\right)}{\frac{1}{30}} + \frac{\left(\frac{1}{30}\right)\left(\frac{1}{40}\right)}{\frac{1}{30}} \\ &= \frac{3}{40} + \frac{1}{10} + \frac{1}{40} = \frac{2}{10} \end{aligned}$$

$$C_a = 5 \mu F$$

$$\begin{aligned} \frac{1}{C_6} &= \frac{1}{400} + \frac{1}{300} + \frac{1}{1200} = \frac{1}{10} \\ C_6 &= 15 \mu F \end{aligned}$$

$$\frac{1}{C_c} = \frac{1}{400} + \frac{1}{300} + \frac{1}{1200} = \frac{1}{40}$$

$$C_c = 3.75\mu F$$

$C_b$  in parallel with  $50\mu F = 50 + 15 = 65\mu F$

$C_c$  in series with  $20\mu F = 23.75\mu F$

$$65\mu F \text{ in series with } 23.75\mu F = \frac{65 \times 23.75}{88.75} = 17.39\mu F$$

$17.39\mu F$  in parallel with  $C_a = 17.39 + 5 = 22.39\mu F$

Hence  $C_{eq} = \underline{\underline{22.39\mu F}}$

### Chapter 6, Solution 29.


(a)  $C$  in series with  $C = C/(2)$

$C/2$  in parallel with  $C = 3C/2$

$$\frac{3C}{2} \text{ in series with } C = \frac{Cx \frac{3C}{2}}{\frac{5C}{2}} = \frac{3C}{5}$$

$\frac{3C}{5}$  in parallel with  $C = C + \frac{3C}{5} = \underline{\underline{1.6 C}}$

(b)

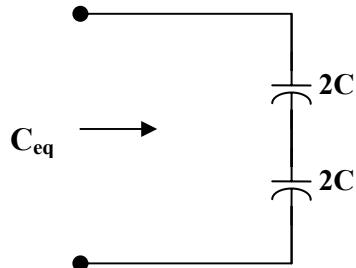

$$\frac{1}{C_{eq}} = \frac{1}{2C} + \frac{1}{2C} = \frac{1}{C}$$

$$C_{eq} = \underline{\underline{C}}$$

### Chapter 6, Solution 30.

$$v_o = \frac{1}{C} \int_0^t i dt + i(0)$$

For  $0 < t < 1$ ,  $i = 60t$  mA,

$$v_o = \frac{10^{-3}}{3 \times 10^{-6}} \int_0^t 60t dt + 0 = 10t^2 \text{kV}$$

$$v_o(1) = 10 \text{kV}$$

For  $1 < t < 2$ ,  $i = 120 - 60t$  mA,

$$\begin{aligned} v_o &= \frac{10^{-3}}{3 \times 10^{-6}} \int_1^t (120 - 60t) dt + v_o(1) \\ &= [40t - 10t^2]_1^t + 10 \text{kV} \end{aligned}$$

$$= 40t - 10t^2 - 20$$

$$v_o(t) = \begin{cases} 10t^2 \text{kV}, & 0 < t < 1 \\ 40t - 10t^2 - 20 \text{kV}, & 1 < t < 2 \end{cases}$$

### Chapter 6, Solution 31.

$$i_s(t) = \begin{cases} 20t \text{mA}, & 0 < t < 1 \\ 20 \text{mA}, & 1 < t < 3 \\ -50 + 10t, & 3 < t < 5 \end{cases}$$

$$C_{eq} = 4 + 6 = 10 \mu\text{F}$$

$$v = \frac{1}{C_{eq}} \int_0^t i dt + v(0)$$

For  $0 < t < 1$ ,

$$v = \frac{10^{-3}}{10 \times 10^{-6}} \int_0^t 20t dt + 0 = t^2 \text{kV}$$

For  $1 < t < 3$ ,

$$v = \frac{10^3}{10} \int_1^t 20 dt + v(1) = 2(t - 1) + 1 \text{kV}$$

$$= 2t - 1 \text{kV}$$

For  $3 < t < 5$ ,

$$v = \frac{10^3}{10} \int_3^t 10(t - 5) dt + v(3)$$

$$= t^2 - 5 + \left| \begin{matrix} t \\ 3 \end{matrix} \right| + 5kV = t^2 - 5t + 11kV$$

$$v(t) = \begin{cases} t^2 kV, & 0 < t < 1 \\ 2t - 1kV, & 1 < t < 3 \\ t^2 - 5t + 11kV, & 3 < t < 5 \end{cases}$$


---

$$i_1 = C_1 \frac{dv}{dt} = 6 \times 10^{-6} \frac{dv}{dt}$$

$$= \begin{cases} 12tmA, & 0 < t < 1 \\ 12mA, & 1 < t < 3 \\ 12 - 30mA, & 3 < t < 5 \end{cases}$$

$$i_1 = C_2 \frac{dv}{dt} = 4 \times 10^{-6} \frac{dv}{dt}$$

$$= \begin{cases} 8tmA, & 0 < t < 1 \\ 8mA, & 1 < t < 3 \\ 8t - 20mA, & 3 < t < 5 \end{cases}$$


---

### Chapter 6, Solution 32.

(a)  $C_{eq} = (12 \times 60) / 72 = 10 \mu F$

$$v_1 = \frac{10^{-3}}{12 \times 10^{-6}} \int_0^t 30e^{-2t} dt + v_1(0) = \frac{-1250e^{-2t}}{12 \times 10^{-6}} \Big|_0^t + 50 = \frac{-1250e^{-2t} + 1300}{12 \times 10^{-6}}$$

$$v_2 = \frac{10^{-3}}{60 \times 10^{-6}} \int_0^t 30e^{-2t} dt + v_2(0) = \frac{250e^{-2t}}{60 \times 10^{-6}} \Big|_0^t + 20 = \frac{250e^{-2t} - 230}{60 \times 10^{-6}}$$

(b) At  $t = 0.5s$ ,

$$v_1 = -1250e^{-1} + 1300 = 840.15, \quad v_2 = 250e^{-1} - 230 = -138.03$$

$$w_{12\mu F} = \frac{1}{2} \times 12 \times 10^{-6} \times (840.15)^2 = 4.235 \text{ J}$$

$$w_{20\mu F} = \frac{1}{2} \times 20 \times 10^{-6} \times (-138.03)^2 = 0.1905 \text{ J}$$

$$w_{40\mu F} = \frac{1}{2} \times 40 \times 10^{-6} \times (-138.03)^2 = 0.381 \text{ J}$$

### **Chapter 6, Solution 33**

Because this is a totally capacitive circuit, we can combine all the capacitors using the property that capacitors in parallel can be combined by just adding their values and we combine capacitors in series by adding their reciprocals.

$$3F + 2F = 5F$$

$$1/5 + 1/5 = 2/5 \text{ or } 2.5F$$

The voltage will divide equally across the two 5F capacitors. Therefore, we get:

$$V_{Th} = \underline{7.5 \text{ V}}, \quad C_{Th} = \underline{2.5 \text{ F}}$$

### **Chapter 6, Solution 34.**

$$i = 6e^{-t/2}$$

$$\begin{aligned} v &= L \frac{di}{dt} = 10 \times 10^{-3} (6) \left( \frac{1}{2} \right) e^{-t/2} \\ &= -30e^{-t/2} \text{ mV} \end{aligned}$$

$$v(3) = -300e^{-3/2} \text{ mV} = \underline{\text{-0.9487 mV}}$$

$$p = vi = -180e^{-t} \text{ mW}$$

$$p(3) = -180e^{-3} \text{ mW} = \underline{\text{-0.8 mW}}$$

### **Chapter 6, Solution 35.**

$$v = L \frac{di}{dt} \quad L = \frac{V}{\Delta i / \Delta t} = \frac{60 \times 10^{-3}}{0.6 / (2)} = \underline{200 \text{ mH}}$$

### **Chapter 6, Solution 36.**

$$v = L \frac{di}{dt} = \frac{1}{4} \times 10^{-3} (12)(2)(-\sin 2t) V$$
$$= \underline{-6 \sin 2t \text{ mV}}$$

$$p = vi = -72 \sin 2t \cos 2t \text{ mW}$$

$$\text{But } 2 \sin A \cos A = \sin 2A$$

$$\underline{p = -36 \sin 4t \text{ mW}}$$

### **Chapter 6, Solution 37.**

$$v = L \frac{di}{dt} = 12 \times 10^{-3} \times 4(100) \cos 100t$$
$$= 4.8 \cos 100t \text{ V}$$

$$p = vi = 4.8 \times 4 \sin 100t \cos 100t = 9.6 \sin 200t$$

$$w = \int_0^t pdt = \int_0^{11/200} 9.6 \sin 200t$$
$$= -\frac{9.6}{200} \cos 200t \Big|_0^{11/200} J$$
$$= -48(\cos \pi - 1)mJ = \underline{96 \text{ mJ}}$$

### **Chapter 6, Solution 38.**

$$v = L \frac{di}{dt} = 40 \times 10^{-3} (e^{-2t} - 2te^{-2t}) dt$$
$$= \underline{40(1 - 2t)e^{-2t} \text{ mV}, t > 0}$$

### Chapter 6, Solution 39

$$v = L \frac{di}{dt} \longrightarrow i = \frac{1}{L} \int_0^t idt + i(0)$$

$$i = \frac{1}{200 \times 10^{-3}} \int_0^t (3t^2 + 2t + 4) dt + 1$$

$$= 5(t^3 + t^2 + 4t) \Big|_0^t + 1$$

$$i(t) = \underline{\underline{5t^3 + 5t^2 + 20t + 1 \text{ A}}}$$

### Chapter 6, Solution 40


$$v = L \frac{di}{dt} = 20 \times 10^{-3} \frac{di}{dt}$$

$$i = \begin{cases} 10t, & 0 < t < 1 \text{ ms} \\ 20 - 10t, & 1 < t < 3 \text{ ms} \\ -40 + 10t, & 3 < t < 4 \text{ ms} \end{cases}$$

$$\frac{di}{dt} = \begin{cases} 10 \times 10^3, & 0 < t < 1 \text{ ms} \\ -10 \times 10^3, & 1 < t < 3 \text{ ms} \\ 10 \times 10^3, & 3 < t < 4 \text{ ms} \end{cases}$$

$$v = \begin{cases} 200 \text{ V}, & 0 < t < 1 \text{ ms} \\ -200 \text{ V}, & 1 < t < 3 \text{ ms} \\ 200 \text{ V}, & 3 < t < 4 \text{ ms} \end{cases}$$

which is sketched below.

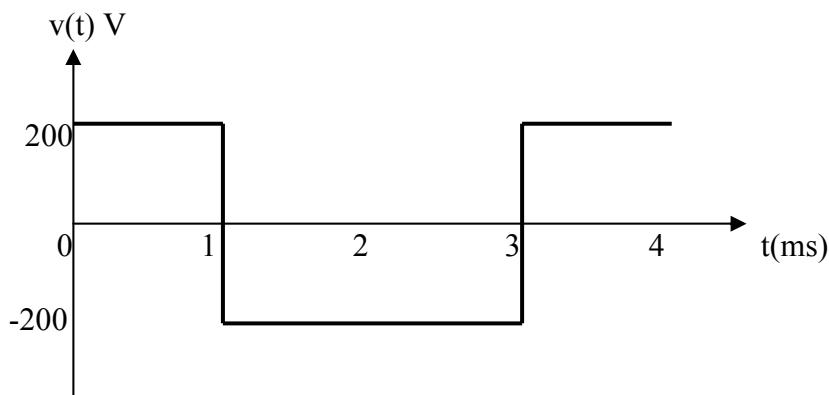

### Chapter 6, Solution 41.

$$\begin{aligned}
 i &= \frac{1}{L} \int_0^t v dt + i(0) = \left( \frac{1}{2} \right) \int_0^t 20(1 - 2^{-2t}) dt + 0.3 \\
 &= 10 \left( t + \frac{1}{2} e^{-2t} \right) \Big|_0^t + 0.3 = 10t + 5e^{-2t} - 4.7 A
 \end{aligned}$$

At  $t = 1s$ ,  $i = 10 - 4.7 + 5e^{-2} = \underline{\underline{5.977 \text{ A}}}$

$$w = \frac{1}{2} L i^2 = \underline{\underline{35.72 \text{ J}}}$$

### Chapter 6, Solution 42.

$$\begin{aligned}
 i &= \frac{1}{L} \int_0^t v dt + i(0) = \frac{1}{5} \int_0^t v(t) dt - 1 \\
 \text{For } 0 < t < 1, \quad i &= \frac{10}{5} \int_0^t dt - 1 = 2t - 1 \text{ A}
 \end{aligned}$$

$$\text{For } 1 < t < 2, \quad i = 0 + i(1) = 1 \text{ A}$$

$$\begin{aligned}
 \text{For } 2 < t < 3, \quad i &= \frac{1}{5} \int 10 dt + i(2) = 2t \Big|_2^3 + 1 \\
 &= 2t - 3 \text{ A}
 \end{aligned}$$

$$\text{For } 3 < t < 4, \quad i = 0 + i(3) = 3 \text{ A}$$

$$\begin{aligned}
 \text{For } 4 < t < 5, \quad i &= \frac{1}{5} \int_4^t 10 dt + i(4) = 2t \Big|_4^t + 3 \\
 &= 2t - 5 \text{ A}
 \end{aligned}$$

$$\text{Thus, } i(t) = \begin{cases} 2t - 1A, & 0 < t < 1 \\ 1A, & 1 < t < 2 \\ 2t - 3A, & 2 < t < 3 \\ 3A, & 3 < t < 4 \\ 2t - 5, & 4 < t < 5 \end{cases}$$

**Chapter 6, Solution 43.**

$$\begin{aligned} w &= L \int_{-\infty}^t i dt = \frac{1}{2} Li(t) - \frac{1}{2} Li^2(-\infty) \\ &= \frac{1}{2} \times 80 \times 10^{-3} \times (60 \times 10^{-3}) - 0 \\ &= \underline{\underline{144 \mu J}} \end{aligned}$$

**Chapter 6, Solution 44.**

$$\begin{aligned} i &= \frac{1}{L} \int_{t_0}^t v dt + i(t_0) = \frac{1}{5} \int_{0}^t (4 + 10 \cos 2t) dt - 1 \\ &= \underline{\underline{0.8t + \sin 2t - 1}} \end{aligned}$$

**Chapter 6, Solution 45.**

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0)$$

For  $0 < t < 1$ ,  $v = 5t$

$$\begin{aligned} i &= \frac{1}{10 \times 10^{-3}} \int_0^t 5t dt + 0 \\ &= 0.25t^2 \text{ kA} \end{aligned}$$


For  $1 < t < 2$ ,  $v = -10 + 5t$

$$\begin{aligned} i &= \frac{1}{10 \times 10^{-3}} \int_1^t (-10 + 5t) dt + i(1) \\ &= \int_1^t (0.5t - 1) dt + 0.25 \text{ kA} \\ &= 1 - t + 0.25t^2 \text{ kA} \end{aligned}$$

$$\underline{\underline{i(t)} = \begin{cases} 0.25t^2 \text{ kA}, & 0 < t < 1 \\ 1 - t + 0.25t^2 \text{ kA}, & 1 < t < 2 \end{cases}}$$
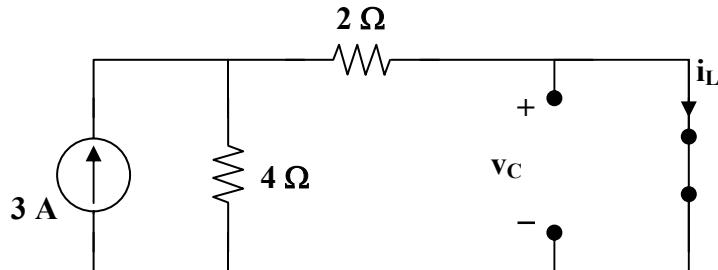
### Chapter 6, Solution 46.

Under dc conditions, the circuit is as shown below:



By current division,


$$i_L = \frac{4}{4+2}(3) = \underline{\underline{2A}}, \quad v_C = \underline{\underline{0V}}$$

$$w_L = \frac{1}{2}L i_L^2 = \frac{1}{2}\left(\frac{1}{2}\right)(2)^2 = \underline{\underline{1J}}$$

$$w_c = \frac{1}{2}C v_c^2 = \frac{1}{2}(2)(0) = \underline{\underline{0J}}$$
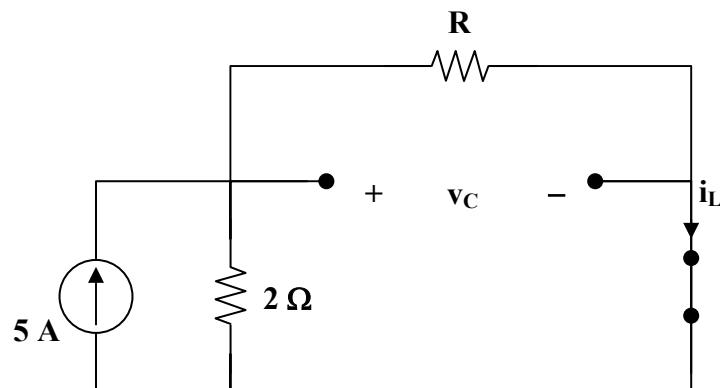
### Chapter 6, Solution 47.

Under dc conditions, the circuit is equivalent to that shown below:



$$i_L = \frac{2}{R+2}(5) = \frac{10}{R+2}, \quad v_C = Ri_L = \frac{10R}{R+2}$$

$$w_c = \frac{1}{2} C v_c^2 = 80 \times 10^{-6} \times \frac{100 R^2}{(R+2)^2}$$

$$w_L = \frac{1}{2} L i_1^2 = 2 \times 10^{-3} \times \frac{100}{(R+2)^2}$$


If  $w_c = w_L$ ,

$$80 \times 10^{-6} \times \frac{100 R^2}{(R \times 2)^2} = \frac{2 \times 10^{-3} \times 100}{(R+2)^2} \longrightarrow 80 \times 10^{-3} R^2 = 2$$

$$R = \underline{\underline{5\Omega}}$$
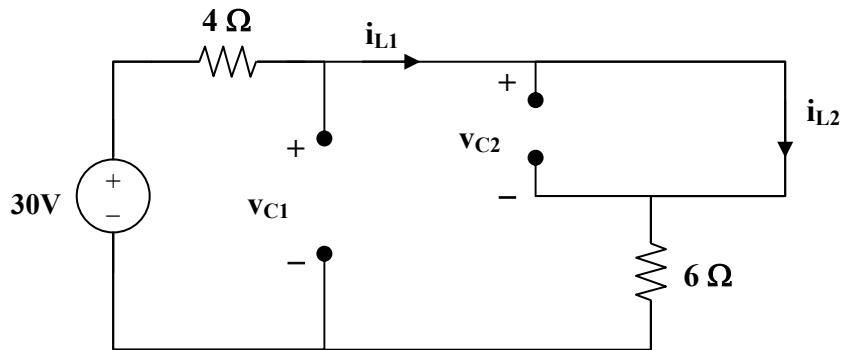
### Chapter 6, Solution 48.

Under dc conditions, the circuit is as shown below:



$$i_{L1} = i_{L2} = \frac{30}{4+6} = \underline{\underline{3A}}$$

$$v_{C1} = 6i_{L1} = \underline{\underline{18V}}$$

$$v_{C2} = \underline{\underline{0V}}$$

### Chapter 6, Solution 49.

$$(a) \quad L_{eq} = 5 + 6 \parallel (1 + 4 \parallel 4) = 5 + 6 \parallel 3 = \underline{\underline{7H}}$$

$$(b) \quad L_{eq} = 12 \parallel (1 + 6 \parallel 6) = 12 \parallel 4 = \underline{\underline{3H}}$$

$$(c) \quad L_{eq} = 4 \parallel (2 + 3 \parallel 6) = 4 \parallel 4 = \underline{\underline{2H}}$$

### Chapter 6, Solution 50.

$$\begin{aligned} L_{eq} &= 10 + 5 \parallel (4 \parallel 12 + 3 \parallel 6) \\ &= 10 + 5 \parallel (3 + 2) = 10 + 2.5 = \underline{\underline{12.5 \text{ mH}}} \end{aligned}$$

### Chapter 6, Solution 51.


$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10} \quad L = 10 \text{ mH}$$

$$\begin{aligned} L_{eq} &= 10 \parallel (25 + 10) = \frac{10 \times 35}{45} \\ &= \underline{\underline{7.778 \text{ mH}}} \end{aligned}$$
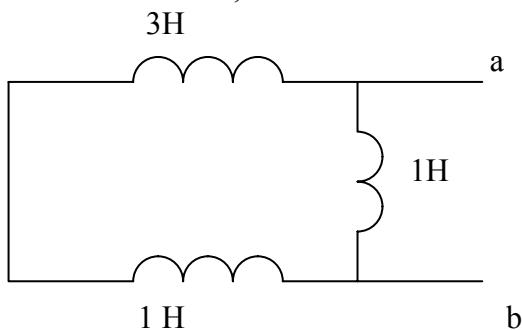
### Chapter 6, Solution 52.

$$3//2//6 = 1\text{H}, \quad 4//12 = 3\text{H}$$

After the parallel combinations, the circuit becomes that shown below.



$$L_{ab} = (3+1)//1 = (4 \times 1)/5 = \underline{\underline{0.8 \text{ H}}}$$

**Chapter 6, Solution 53.**

$$L_{eq} = 6 + 10 + 8 \parallel [5 \parallel (8+12) + 6 \parallel (8+4)]$$

$$= 16 + 8 \parallel (4+4) = 16 + 4$$

$$L_{eq} = \underline{\underline{20 \text{ mH}}}$$

**Chapter 6, Solution 54.**

$$L_{eq} = 4 + (9+3) \parallel (10 \parallel 0 + 6 \parallel 12)$$

$$= 4 + 12 \parallel (0+4) = 4 + 3$$

$$L_{eq} = \underline{\underline{7 \text{ H}}}$$

**Chapter 6, Solution 55.**

(a)  $L//L = 0.5L$ ,  $L + L = 2L$

$$L_{eq} = L + 2L // 0.5L = L + \frac{2L \times 0.5L}{2L + 0.5L} = \underline{\underline{1.4L}}$$


(b)  $L//L = 0.5L$ ,  $L//L + L//L = L$

$$L_{eq} = L//L = \underline{\underline{0.5L}}$$

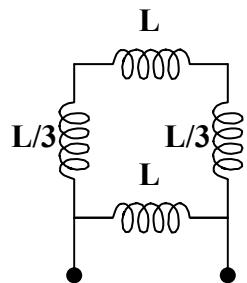**Chapter 6, Solution 56.**

$$L \parallel L \parallel L = \frac{1}{\frac{1}{3} + \frac{1}{3}} = \frac{L}{2}$$

Hence the given circuit is equivalent to that shown below:



$$L_{eq} = L \left( L + \frac{2}{3} L \right) = \frac{Lx \frac{5}{3} L}{L + \frac{5}{3} L} = \frac{5}{8} L$$

### Chapter 6, Solution 57.

$$\text{Let } v = L_{eq} \frac{di}{dt} \quad (1)$$

$$v = v_1 + v_2 = 4 \frac{di}{dt} + v_2 \quad (2)$$

$$i = i_1 + i_2 \longrightarrow i_2 = i - i_1 \quad (3)$$

$$v_2 = 3 \frac{di_1}{dt} \text{ or } \frac{di_1}{dt} = \frac{v_2}{3} \quad (4)$$

and

$$-v_2 + 2 \frac{di}{dt} + 5 \frac{di_2}{dt} = 0$$

$$v_2 = 2 \frac{di}{dt} + 5 \frac{di_2}{dt} \quad (5)$$

Incorporating (3) and (4) into (5),

$$v_2 = 2 \frac{di}{dt} + 5 \frac{di}{dt} - 5 \frac{di_1}{dt} = 7 \frac{di}{dt} - 5 \frac{v_2}{3}$$

$$v_2 \left( 1 + \frac{5}{3} \right) = 7 \frac{di}{dt}$$

$$v_2 = \frac{35}{8} \frac{di}{dt}$$

Substituting this into (2) gives

$$v = 4 \frac{di}{dt} + \frac{35}{8} \frac{di}{dt}$$

$$= \frac{67}{8} \frac{di}{dt}$$


Comparing this with (1),

$$L_{eq} = \frac{67}{8} = \underline{\underline{8.375H}}$$

### Chapter 6, Solution 58.

$$v = L \frac{di}{dt} = 3 \frac{di}{dt} = 3 \times \text{slope of } i(t).$$

Thus  $v$  is sketched below:

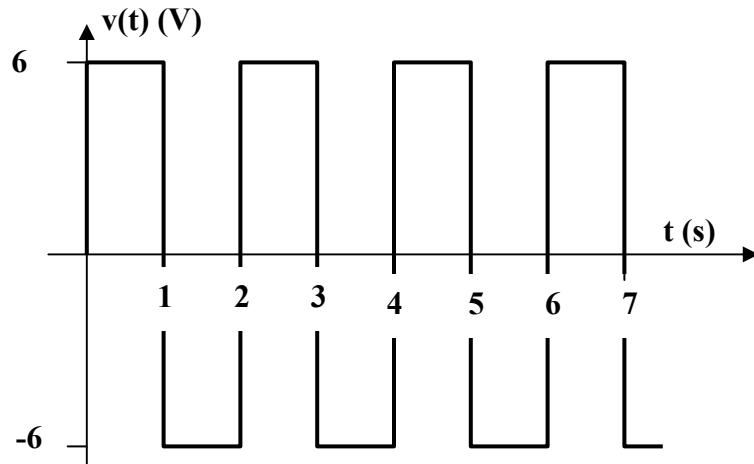

### Chapter 6, Solution 59.

$$(a) \quad v_s = (L_1 + L_2) \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{v_s}{L_1 + L_2}$$

$$v_1 = L_1 \frac{di}{dt}, \quad v_2 = L_2 \frac{di}{dt}$$

$$\underline{v_1 = \frac{L_1}{L_1 + L_2} v_s, \quad v_L = \frac{L_2}{L_1 + L_2} v_s}$$

$$(b) \quad v_i = v_2 = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt}$$

$$i_s = i_1 + i_2$$

$$\frac{di_s}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = \frac{v}{L_1} + \frac{v}{L_2} = v \frac{(L_1 + L_2)}{L_1 L_2}$$

$$\underline{i_1 = \frac{1}{L_1} \int v dt = \frac{1}{L_1} \int \frac{L_1 L_2}{L_1 + L_2} \frac{di_s}{dt} dt = \frac{L_2}{L_1 + L_2} i_s}$$

$$i_2 = \frac{1}{L_2} \int v dt = \frac{1}{L_2} \int \frac{L_1 L_2}{L_1 + L_2} \frac{di_s}{dt} dt = \underline{\underline{\frac{L_1}{L_1 + L_2} i_s}}$$

### Chapter 6, Solution 60

$$L_{eq} = 3//5 = \frac{15}{8}$$

$$v_o = L_{eq} \frac{di}{dt} = \frac{15}{8} \frac{d}{dt} (4e^{-2t}) = \underline{-15e^{-2t}}$$

$$i_o = \frac{I}{L} \int_0^t v_o(t) dt + i_o(0) = 2 + \frac{1}{5} \int_0^t (-15)e^{-2t} dt = 2 + 1.5e^{-2t} \Big|_0^t = \underline{0.5 + 1.5e^{-2t}} A$$

### Chapter 6, Solution 61.

(a)  $i_s = i_1 + i_2$   
 $i_s(0) = i_1(0) + i_2(0)$   
 $6 = 4 + i_2(0)$        $i_2(0) = \underline{2mA}$

(b) Using current division:

$$i_1 = \frac{20}{30+20} i_s = 0.4(6e^{-2t}) = \underline{2.4e^{-2t} mA}$$

$$i_2 = i_s - i_1 = \underline{3.6e^{-2t} mA}$$

(c)  $30\parallel 20 = \frac{30 \times 20}{50} = 12mH$

$$v_1 = L \frac{di}{dt} = 10 \times 10^{-3} \frac{d}{dt} (6e^{-2t}) \times 10^{-3} = \underline{-120e^{-2t} \mu V}$$

$$v_2 = L \frac{di}{dt} = 12 \times 10^{-3} \frac{d}{dt} (6e^{-2t}) \times 10^{-3} = \underline{-144e^{-2t} \mu V}$$

(d)  $w_{10mH} = \frac{1}{2} \times 30 \times 10^{-3} (36e^{-4t} \times 10^{-6})$   
 $= 0.8e^{-4t} \Big|_{t=\frac{1}{2}} \mu J$   
 $= \underline{24.36nJ}$

$$w_{30mH} = \frac{1}{2} \times 30 \times 10^{-3} (5.76e^{-4t} \times 10^{-6}) \Big|_{t=1/2}$$
  
 $= \underline{11.693nJ}$

$$w_{20mH} = \frac{1}{2} \times 20 \times 10^{-3} (12.96e^{-4t} \times 10^{-6}) \Big|_{t=1/2}$$
  
 $= \underline{17.54 nJ}$

### Chapter 6, Solution 62.

$$(a) \quad L_{eq} = 25 + 20 // 60 = 25 + \frac{20 \times 60}{80} = 40 \text{ mH}$$

$$v = L_{eq} \frac{di}{dt} \quad \longrightarrow \quad i = \frac{1}{L_{eq}} \int v(t) dt + i(0) = \frac{10^{-3}}{40 \times 10^{-3}} \int_0^t 12e^{-3t} dt + i(0) = -0.1(e^{-3t} - 1) + i(0)$$

Using current division,

$$i_1 = \frac{60}{80} i = \frac{3}{4} i, \quad i_2 = \frac{1}{4} i$$

$$i_1(0) = \frac{3}{4} i(0) \quad \longrightarrow \quad 0.75i(0) = -0.01 \quad \longrightarrow \quad i(0) = -0.01333$$

$$i_2 = \frac{1}{4}(-0.1e^{-3t} + 0.08667) \text{ A} = -25e^{-3t} + 21.67 \text{ mA}$$

$$i_2(0) = -25 + 21.67 = -3.33 \text{ mA}$$

$$(b) \quad i_1 = \frac{3}{4}(-0.1e^{-3t} + 0.08667) \text{ A} = -75e^{-3t} + 65 \text{ mA}$$

$$i_2 = -25e^{-3t} + 21.67 \text{ mA}$$

### Chapter 6, Solution 63.


We apply superposition principle and let

$$v_o = v_1 + v_2$$


where  $v_1$  and  $v_2$  are due to  $i_1$  and  $i_2$  respectively.

$$v_1 = L \frac{di_1}{dt} = 2 \frac{di_1}{dt} = \begin{cases} 2, & 0 < t < 3 \\ -2, & 3 < t < 6 \end{cases}$$
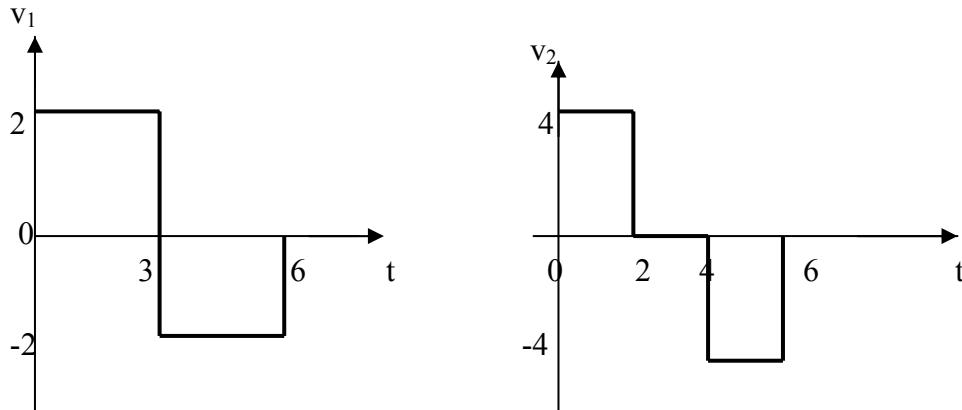
$$v_2 = L \frac{di_2}{dt} = 2 \frac{di_2}{dt} = \begin{cases} 4, & 0 < t < 2 \\ 0, & 2 < t < 4 \\ -4, & 4 < t < 6 \end{cases}$$



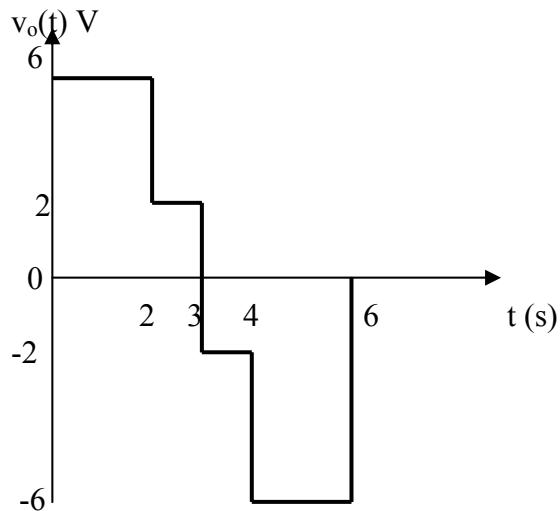Adding  $v_1$  and  $v_2$  gives  $v_o$ , which is shown below.



### Chapter 6, Solution 64.

(a) When the switch is in position A,  
 $i = -6 = i(0)$

When the switch is in position B,

$$i(\infty) = 12 / 4 = 3, \quad \tau = L / R = 1 / 8$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = 3 - 9e^{-8t} \text{ A}$$

$$(b) -12 + 4i(0) + v = 0, \text{ i.e. } v = 12 - 4i(0) = 36 \text{ V}$$

(c) At steady state, the inductor becomes a short circuit so that  
 $v = 0 \text{ V}$

### Chapter 6, Solution 65.

$$(a) \quad w_5 = \frac{1}{2} L_1 i_1^2 = \frac{1}{2} \times 5 \times (4)^2 = \underline{\underline{40 \text{ W}}}$$

$$w_{20} = \frac{1}{2} (20)(-2)^2 = \underline{\underline{40 \text{ W}}}$$

$$(b) \quad w = w_5 + w_{20} = \underline{\underline{80 \text{ W}}}$$

$$(c) \quad i_1 = L_1 \frac{dv}{dt} = 5(-200)(50e^{-200t} \times 10^{-3}) \\ = \underline{\underline{-50e^{-200t} \text{ A}}}$$

$$i_2 = L_2 \frac{dv}{dt} = 20(-200)(50e^{-200t} \times 10^{-3}) \\ = \underline{\underline{-200e^{-200t} \text{ A}}}$$

$$i_2 = L_2 \frac{dv}{dt} = 20(-200)(50e^{-200t} \times 10^{-3}) \\ = \underline{\underline{-200e^{-200t} \text{ A}}}$$

$$(d) \quad i = i_1 + i_2 = \underline{\underline{-250e^{-200t} \text{ A}}}$$

### Chapter 6, Solution 66.

$$L_{\text{eq}} = 20 + 16 + 60 \parallel 40 = 36 + 24 = 60 \text{ mH}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_0^t v dt + i(0)$$

$$= \frac{1}{60 \times 10^{-3}} \int_0^t 12 \sin 4t dt + 0 \text{ mA}$$

$$i = -50 \cos 4t \Big|_0^t = \underline{\underline{50(1 - \cos 4t) \text{ mA}}}$$

$$60 \parallel 40 = 24 \text{ mH}$$

$$v = L \frac{di}{dt} = 24 \times 10^{-3} \frac{d}{dt} (50)(1 - \cos 4t) \text{ mV} \\ = \underline{\underline{4.8 \sin 4t \text{ mV}}}$$

### **Chapter 6, Solution 67.**

$$v_o = -\frac{1}{RC} \int v_i dt, \quad RC = 50 \times 10^3 \times 0.04 \times 10^{-6} = 2 \times 10^{-3}$$

$$v_o = \frac{-10^3}{2} \int 10 \sin 50t dt$$

$$v_o = \underline{\underline{100 \cos 50t \text{ mV}}}$$

### **Chapter 6, Solution 68.**

$$v_o = -\frac{1}{RC} \int v_i dt + v(0), \quad RC = 50 \times 10^3 \times 100 \times 10^{-6} = 5$$

$$v_o = -\frac{1}{5} \int_0^t 10 dt + 0 = -2t$$

The op amp will saturate at  $v_o = \pm 12$

$$-12 = -2t \longrightarrow \underline{\underline{t = 6s}}$$

### **Chapter 6, Solution 69.**

$$RC = 4 \times 10^6 \times 1 \times 10^{-6} = 4$$

$$v_o = -\frac{1}{RC} \int v_i dt = -\frac{1}{4} \int v_i dt$$

$$\text{For } 0 < t < 1, \quad v_i = 20, \quad v_o = -\frac{1}{4} \int_0^t 20 dt = -5t \text{ mV}$$


$$\begin{aligned} \text{For } 1 < t < 2, \quad v_i = 10, \quad v_o &= -\frac{1}{4} \int_1^t 10 dt + v(1) = -2.5(t-1) - 5 \\ &= -2.5t - 2.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 2 < t < 4, \quad v_i = -20, \quad v_o &= +\frac{1}{4} \int_2^t 20 dt + v(2) = 5(t-2) - 7.5 \\ &= 5t - 17.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 4 < t < 5, \quad v_i = -10, \quad v_o &= \frac{1}{4} \int_4^t 10 dt + v(4) = 2.5(t-4) + 2.5 \\ &= 2.5t - 7.5 \text{ mV} \end{aligned}$$

$$\begin{aligned} \text{For } 5 < t < 6, \quad v_i = 20, \quad v_o &= -\frac{1}{4} \int_5^t 20 dt + v(5) = -5(t-5) + 5 \\ &= -5t + 30 \text{ mV} \end{aligned}$$

Thus  $v_o(t)$  is as shown below:

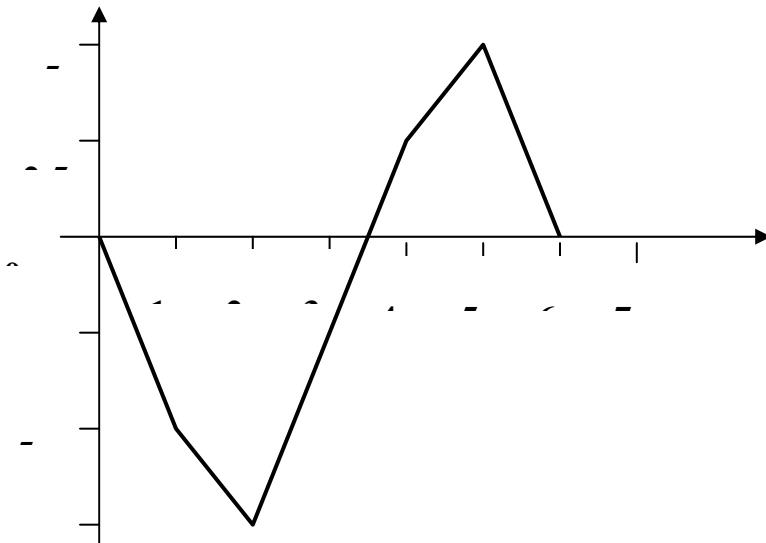

### Chapter 6, Solution 70.


One possibility is as follows:

$$\frac{1}{RC} = 50$$

$$\text{Let } R = 100 \text{ k}\Omega, C = \frac{1}{50 \times 100 \times 10^3} = 0.2 \mu\text{F}$$
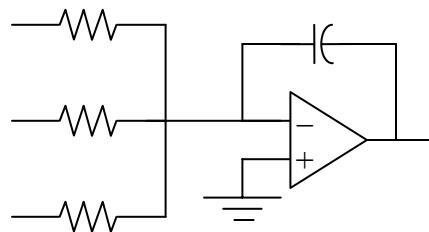
### Chapter 6, Solution 71.

By combining a summer with an integrator, we have the circuit below:



$$v_o = -\frac{1}{R_1 C} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt - \frac{1}{R_2 C} \int v_2 dt$$

For the given problem,  $C = 2 \mu\text{F}$ ,

$$R_1 C = 1 \longrightarrow R_1 = 1/(C) = 100^6/(2) = \underline{\underline{500 \text{ k}\Omega}}$$

$$R_2 C = 1/(4) \longrightarrow R_2 = 1/(4C) = 500 \text{ k}\Omega / (4) = \underline{\underline{125 \text{ k}\Omega}}$$

$$R_3 C = 1/(10) \longrightarrow R_3 = 1/(10C) = \underline{\underline{50 \text{ k}\Omega}}$$

### Chapter 6, Solution 72.

The output of the first op amp is

$$v_1 = -\frac{1}{RC} \int v_i dt = -\frac{1}{10 \times 10^3 \times 2 \times 10^{-6}} \int_0^t idt = -\frac{100t}{2}$$

$$= -50t$$

$$v_o = -\frac{1}{RC} \int v_i dt = -\frac{1}{20 \times 10^3 \times 0.5 \times 10^{-6}} \int_0^t (-50t) dt$$

$$= 2500t^2$$

At  $t = 1.5\text{ms}$ ,


$$v_o = 2500(1.5)^2 \times 10^{-6} = \underline{\underline{5.625 \text{ mV}}}$$

### Chapter 6, Solution 73.

Consider the op amp as shown below:

Let  $v_a = v_b = v$

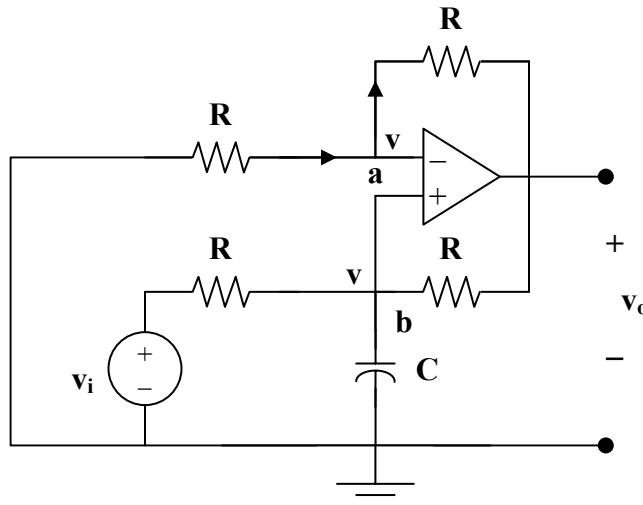At node a,  $\frac{0-v}{R} = \frac{v-v_o}{R} \longrightarrow 2v - v_o = 0$  (1)



At node b,  $\frac{v_i - v}{R} = \frac{v - v_o}{R} + C \frac{dv}{dt}$

$$v_i = 2v - v_o + RC \frac{dv}{dt} \quad (2)$$

Combining (1) and (2),

$$v_i = v_o - v_o + \frac{RC}{2} \frac{dv_o}{dt}$$

or

$$v_o = \frac{2}{RC} \int v_i dt$$

**showing that the circuit is a noninverting integrator.**


### Chapter 6, Solution 74.

$$RC = 0.01 \times 20 \times 10^{-3} \text{ sec}$$

$$v_o = -RC \frac{dv_i}{dt} = -0.2 \frac{dv}{dt} \text{ msec}$$

$$v_o = \begin{cases} -2V, & 0 < t < 1 \\ 2V, & 1 < t < 3 \\ -2V, & 3 < t < 4 \end{cases}$$

Thus  $v_o(t)$  is as sketched below:

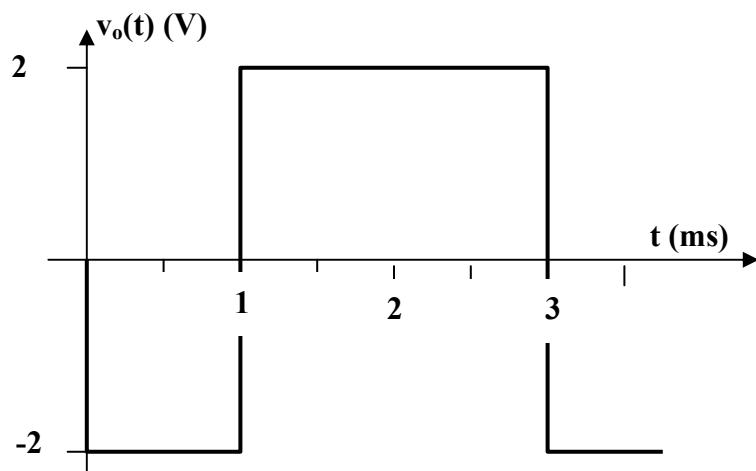

**Chapter 6, Solution 75.**

$$v_o = -RC \frac{dv_i}{dt}, \quad RC = 250 \times 10^3 \times 10 \times 10^{-6} = 2.5$$



$$v_o = -2.5 \frac{d}{dt}(12t) = \underline{-30 \text{ mV}}$$

**Chapter 6, Solution 76.**

$$v_o = -RC \frac{dv_i}{dt}, \quad RC = 50 \times 10^3 \times 10 \times 10^{-6} = 0.5$$

$$v_o = 0.5 \frac{dv_i}{dt} = \begin{cases} -10, & 0 < t < 5 \\ 5, & 5 < t < 15 \end{cases}$$

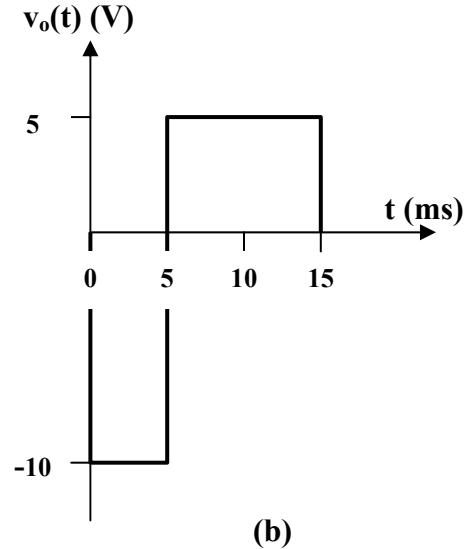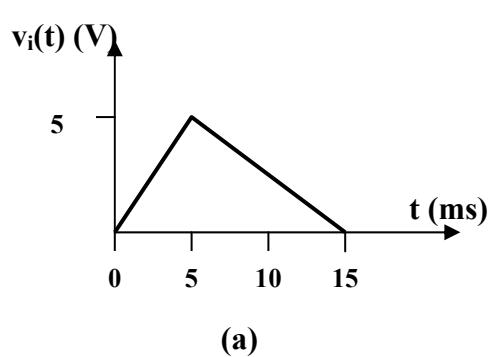The input is sketched in Fig. (a), while the output is sketched in Fig. (b).



**Chapter 6, Solution 77.**


$$i = i_R + i_C$$

$$\frac{v_i - 0}{R} = \frac{0 - v_o}{R_F} + C \frac{d}{dt}(0 - v_o)$$

$$R_F C = 10^6 \times 10^{-6} = 1$$

$$\text{Hence } v_i = -\left(v_o + \frac{dv_o}{dt}\right)$$

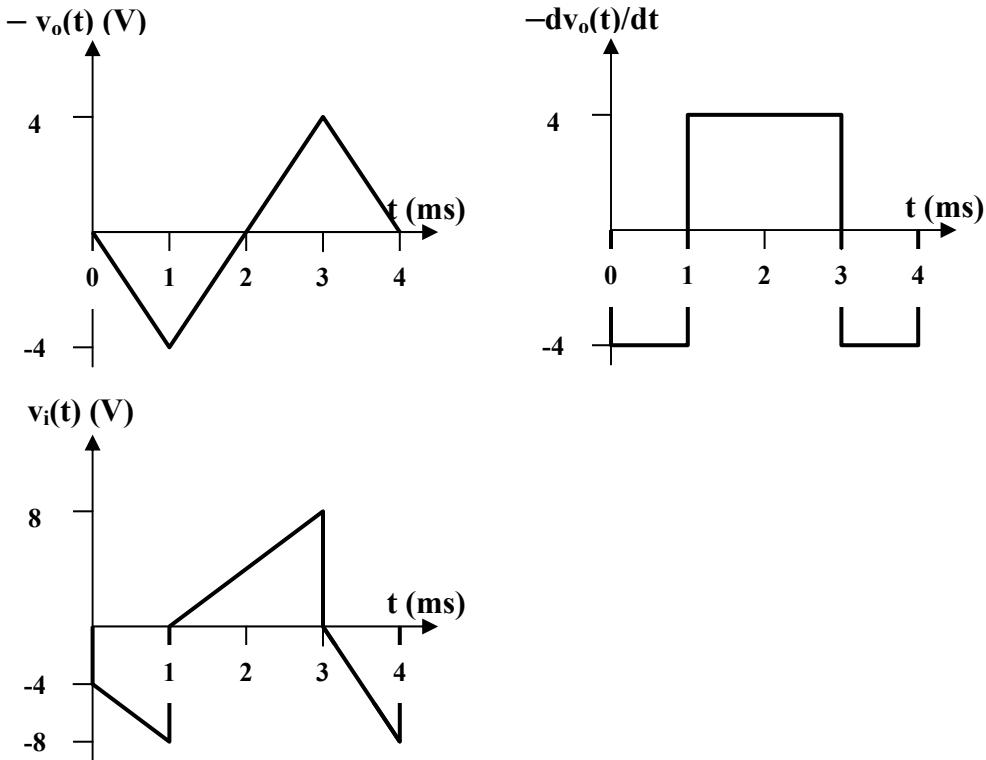
Thus  $v_i$  is obtained from  $v_o$  as shown below:


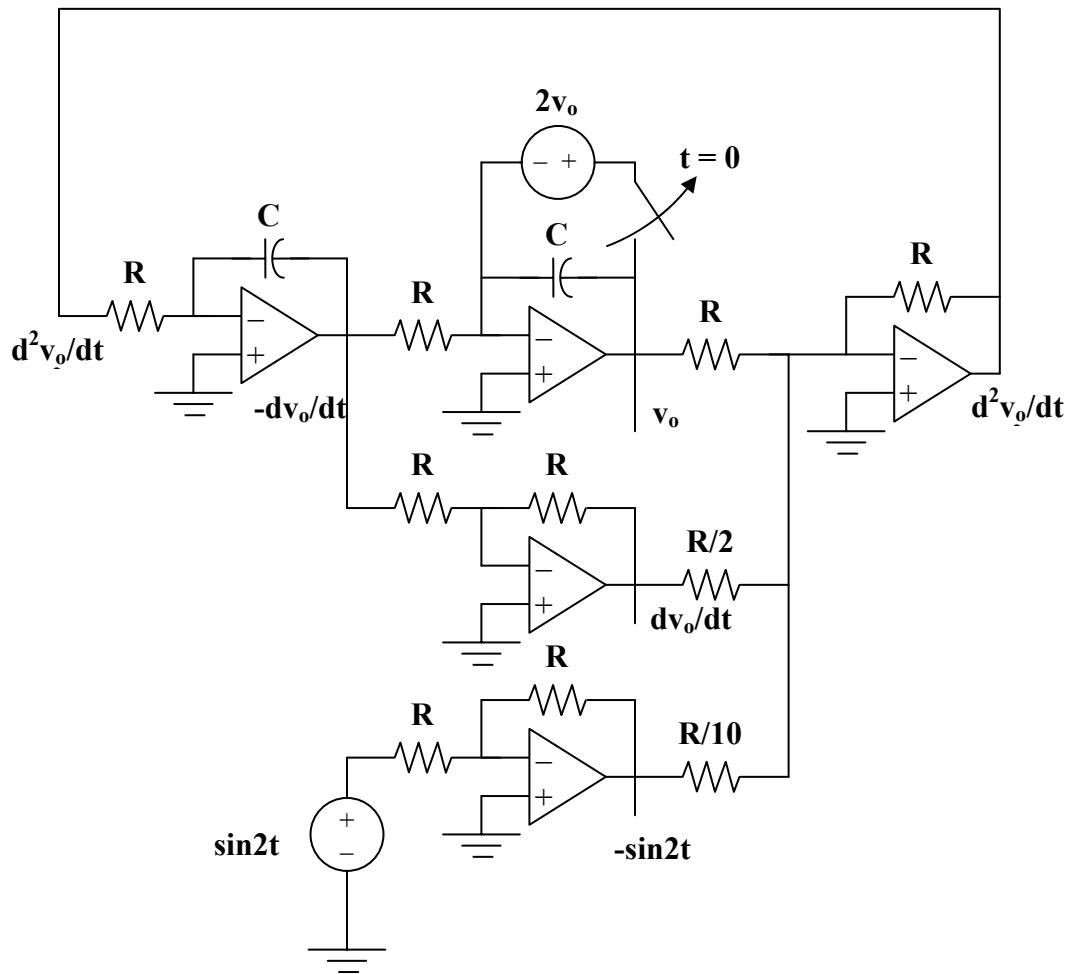
### Chapter 6, Solution 78.

$$\frac{d^2v_o}{dt} = 10 \sin 2t - \frac{2dv_o}{dt} - v_o$$

Thus, by combining integrators with a summer, we obtain the appropriate analog computer as shown below:




### Chapter 6, Solution 79.

We can write the equation as

$$\frac{dy}{dt} = f(t) - 4y(t)$$

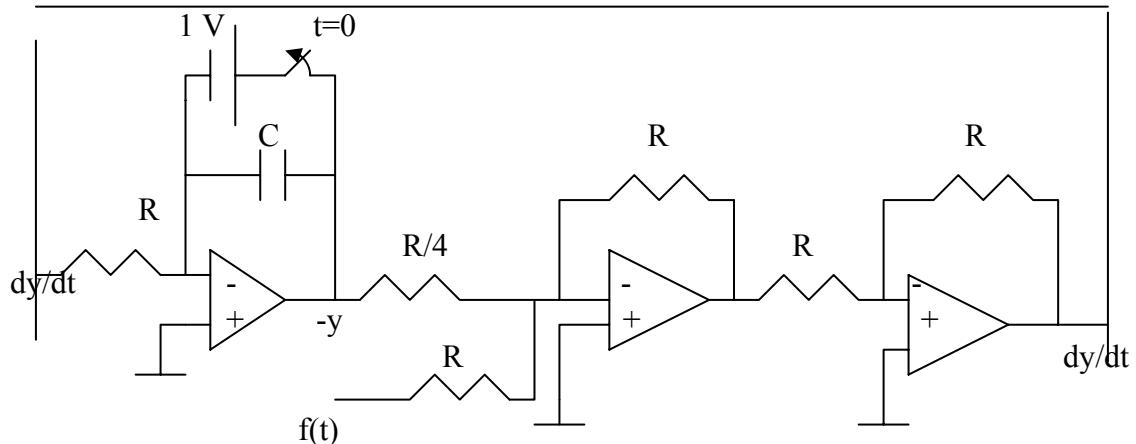which is implemented by the circuit below.



### Chapter 6, Solution 80.

From the given circuit,

$$\frac{d^2v_o}{dt^2} = f(t) - \frac{1000k\Omega}{5000k\Omega} v_o - \frac{1000k\Omega}{200k\Omega} \frac{dv_o}{dt}$$

or


$$\frac{d^2v_o}{dt^2} + 5 \frac{dv_o}{dt} + 2v_o = f(t)$$

### Chapter 6, Solution 81

We can write the equation as


$$\frac{d^2v}{dt^2} = -5v - 2f(t)$$

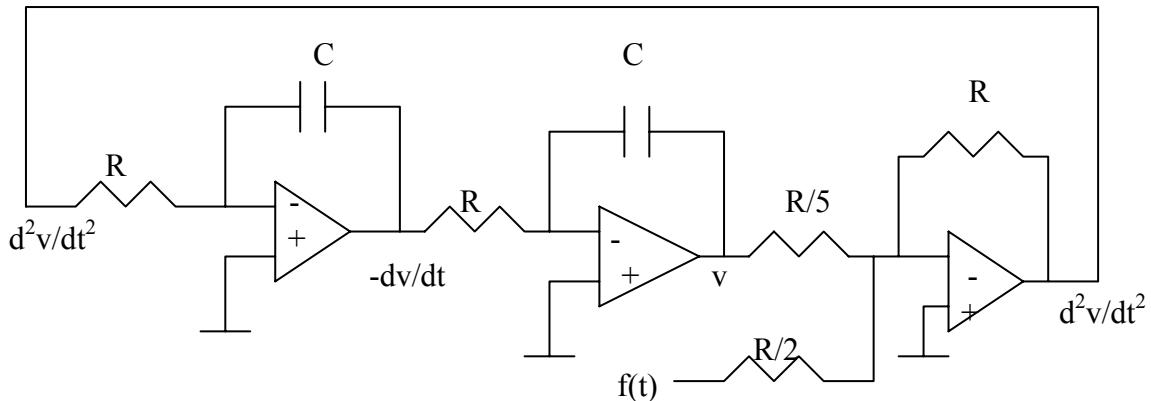which is implemented by the circuit below.



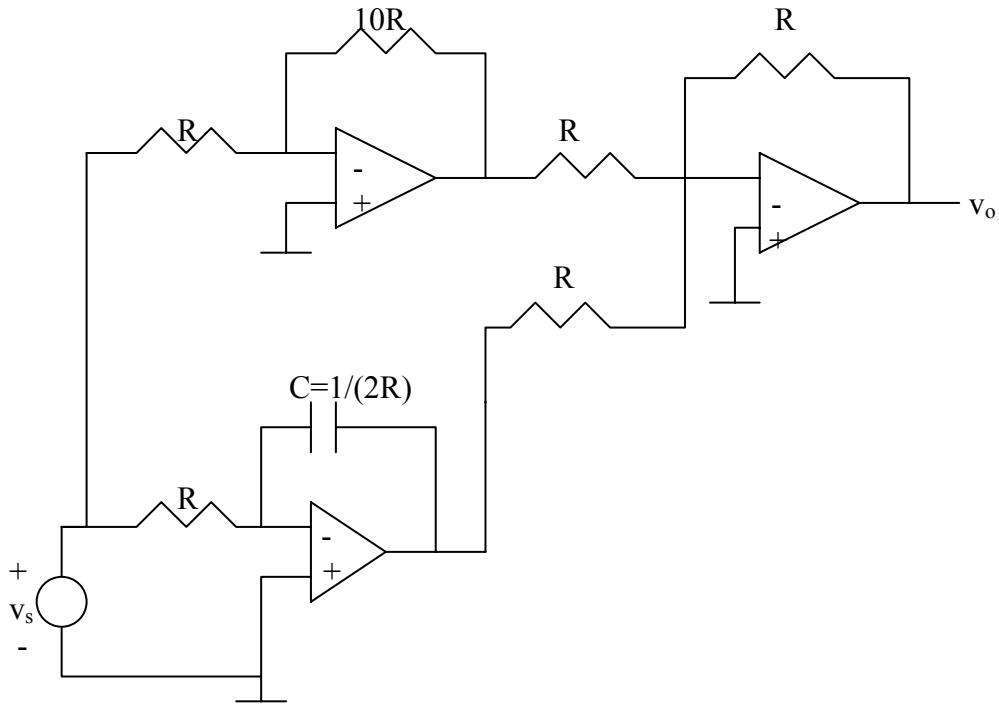
### Chapter 6, Solution 82

The circuit consists of a summer, an inverter, and an integrator. Such circuit is shown below.


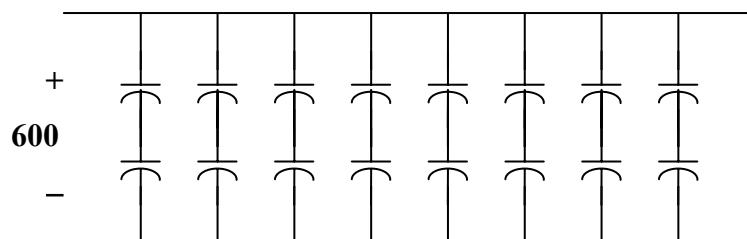
### Chapter 6, Solution 83.

Since two  $10\mu\text{F}$  capacitors in series gives  $5\mu\text{F}$ , rated at 600V, it requires 8 groups in parallel with each group consisting of two capacitors in series, as shown below:



Answer: 8 groups in parallel with each group made up of 2 capacitors in series.

### **Chapter 6, Solution 84.**

$$\Delta I = \frac{\Delta q}{\Delta t} \quad \Delta I \times \Delta t = \Delta q$$

$$\begin{aligned}\Delta q &= 0.6 \times 4 \times 10^{-6} \\ &= 2.4 \mu C\end{aligned}$$

$$C = \frac{\Delta q}{\Delta v} = \frac{2.4 \times 10^{-6}}{(36 - 20)} = \underline{150 nF}$$

### **Chapter 6, Solution 85.**

It is evident that differentiating i will give a waveform similar to v. Hence,

$$v = L \frac{di}{dt}$$

$$i = \begin{cases} 4t, & 0 < t < 1 \\ 8 - 4t, & 1 < t < 2 \end{cases}$$

$$v = L \frac{di}{dt} = \begin{cases} 4L, & 0 < t < 1 \\ -4L, & 1 < t < 2 \end{cases}$$

But,  $v = \begin{cases} 5mV, & 0 < t < 1 \\ -5mV, & 1 < t < 2 \end{cases}$

Thus,  $4L = 5 \times 10^{-3} \longrightarrow L = 1.25 \text{ mH in a } \underline{1.25 \text{ mH inductor}}$

### **Chapter 6, Solution 86.**

(a) For the series-connected capacitor

$$C_s = \frac{1}{\frac{1}{C} + \frac{1}{C} + \dots + \frac{1}{C}} = \frac{C}{8}$$

For the parallel-connected strings,

$$C_{eq} = 10C_s = \frac{10C_s}{8} = 10 \times \frac{1000}{3} \mu F = \underline{1250 \mu F}$$

$$(b) \quad v_T = 8 \times 100V = 800V$$

$$w = \frac{1}{2} C_{eq} v_T^2 = \frac{1}{2} (1250 \times 10^{-6}) (800)^2$$

$$= \underline{\underline{400J}}$$