

Inductance and Capacitance

Drill Exercises

- DE 7.1** [a] $v = L \frac{di}{dt} = -2e^{-200t} + 8e^{-800t}$, $t > 0^+$
 $v(0^+) = -2 + 8 = 6 \text{ V}$
- [b] $v = 0$ when $8e^{-800t} = 2e^{-200t}$ or $t = (\ln 4)/600 = 2.31 \text{ ms}$
- [c] $p = vi = 50e^{-1000t} - 10e^{-400t} - 40e^{-1600t} \text{ W}$
- [d] $\frac{dp}{dt} = 0$ when $e^{1200t} - 12.5e^{600t} + 16 = 0$
 Let $x = e^{600t}$ and solve the quadratic $x^2 - 12.5x + 16 = 0$
 $x = 1.45$, $x = 11.05$, $t = \frac{\ln 1.45}{600} = 616.58 \mu\text{s}$, $t = \frac{\ln 11.05}{600} = 4 \text{ ms}$
 p is maximum at $t = 616.58 \mu\text{s}$
- [e] $p_{\max} = 50e^{-0.61658} - 10e^{-0.4(0.61658)} - 40e^{-1.6(0.61658)} = 4.26 \text{ W}$
- [f] $i_{\max} = 5[e^{-0.2(2.31)} - e^{-0.8(2.31)}] = 2.36 \text{ A}$
 $w_{\max} = (1/2)(2 \times 10^{-3})(2.36)^2 = 5.58 \text{ mJ}$
- [g] W is max when i is max, i is max when di/dt is zero.
 When $di/dt = 0$, $v = 0$, therefore $t = 2.31 \text{ ms}$.
- DE 7.2** [a] $i = C \frac{dv}{dt} = 50 \times 10^{-6} d[e^{-20,000t} \sin 40,000t]$
 $= [2 \cos 40,000t - \sin 40,000t]e^{-20,000t} \text{ A}$, $i(0^+) = 2 \text{ A}$
- [b] $i\left(\frac{\pi}{80} \text{ ms}\right) = -455.94 \text{ mA}$, $v\left(\frac{\pi}{80} \text{ ms}\right) = 45.59 \text{ V}$, $p = vi = -20.79 \text{ W}$
- [c] $w = \left(\frac{1}{2}\right) C v^2 = 519.70 \mu\text{J}$

$$\begin{aligned}
 \text{DE 7.3 [a]} \quad v &= \left(\frac{1}{C}\right) \int_{0^-}^t i \, dx + v(0^-) \\
 &= 2 \times 10^6 \int_{0^-}^t 2 \cos 50,000x \, dx = 80 \sin 50,000t \, \text{V} \\
 \text{[b]} \quad p(t) &= vi = [160 \cos 50,000t] \sin 50,000t \\
 &= 80 \sin 100,000t \, \text{W}, \quad p_{(\max)} = 80 \, \text{W} \\
 \text{[c]} \quad w_{(\max)} &= \left(\frac{1}{2}\right) C v_{\max}^2 = 0.25(80)^2 = 1600 \, \mu\text{J} = 1.6 \, \text{mJ}
 \end{aligned}$$

$$\begin{aligned}
 \text{DE 7.4 [a]} \quad L_{\text{eq}} &= \frac{5(20)}{25} = 4 \, \text{H} \\
 \text{[b]} \quad i(0^+) &= -2 + 4 = 2 \, \text{A}, \quad \text{down} \\
 \text{[c]} \quad i &= 0.25 \int_{0^+}^t (-40e^{-5x}) \, dx + 2 = 2e^{-5t} \, \text{A} \\
 \text{[d]} \quad i_1 &= 0.2 \int_{0^+}^t (-40e^{-5x}) \, dx - 2 = 1.6e^{-5t} - 3.6 \, \text{A} \\
 i_2 &= 0.05 \int_{0^+}^t (-40e^{-5x}) \, dx + 4 = 0.4e^{-5t} + 3.6 \, \text{A} \\
 i_1 + i_2 &= i
 \end{aligned}$$


$$\begin{aligned}
 \text{DE 7.5} \quad v_1 &= 0.5 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 10 = -12e^{-10t} + 2 \, \text{V} \\
 v_2 &= 0.125 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 5 = -3e^{-10t} - 2 \, \text{V} \\
 v_1(\infty) &= 2 \, \text{V}, \quad v_2(\infty) = -2 \, \text{V}, \quad W = \frac{1}{2}(2)(4) + \frac{1}{2}(8)(4) = 20 \, \mu\text{J}
 \end{aligned}$$

Problems

$$\begin{aligned}
 \text{P7.1} \quad p &= vi = 40t[e^{-10t} - 10te^{-20t} - e^{-20t}] \\
 W &= \int_0^\infty p \, dx = \int_0^\infty 40x[e^{-10x} - 10xe^{-20x} - e^{-20x}] \, dx = 0.2 \, \text{J} \\
 &\text{This is energy stored in the inductor at } t = \infty.
 \end{aligned}$$

$$\begin{aligned}
 \text{P7.2 [a]} \quad i &= 0, \quad t \leq 0 \\
 i &= \frac{400 \times 10^{-3}}{5 \times 10^{-3}} t = 80t \, \text{A}, \quad 0 \leq t \leq 5 \, \text{ms} \\
 i(t) &= 0.8 - 80t \, \text{A}, \quad 5 \, \text{ms} \leq t \leq 10 \, \text{ms} \\
 i(t) &= 0, \quad 10 \, \text{ms} \leq t \leq \infty
 \end{aligned}$$

[b]

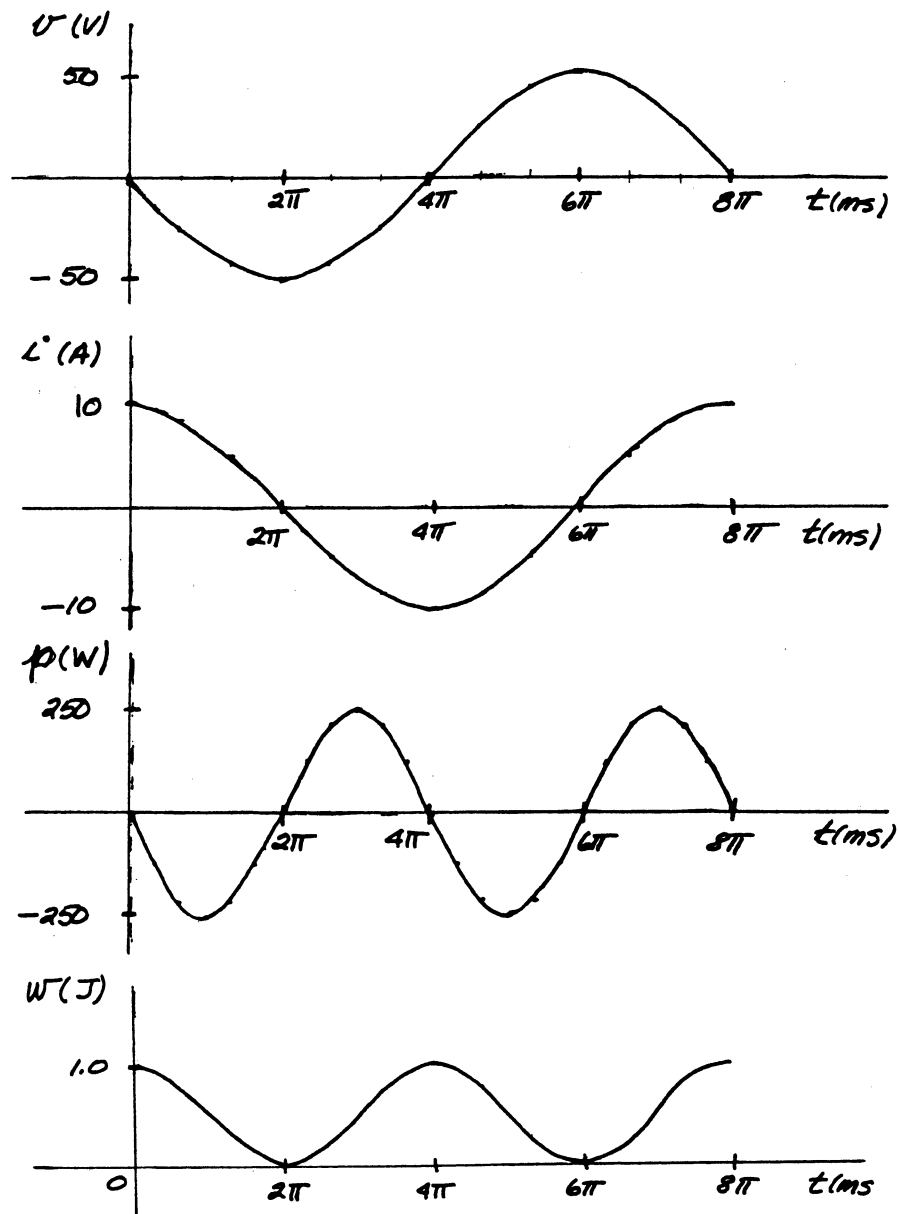

[c] Absorbing power: $2\pi - 4\pi$ ms Delivering power: $0 - 2\pi$ ms
 $6\pi - 8\pi$ ms $4\pi - 6\pi$ ms

P7.6 [a] $v = L \frac{di}{dt}$

$$\begin{aligned}
 v &= -25 \times 10^{-3} \frac{d}{dt} [10 \cos 400t + 5 \sin 400t] e^{-200t} \\
 &= -25 \times 10^{-3} \{ -200 e^{-200t} [10 \cos 400t + 5 \sin 400t] \\
 &\quad + e^{-200t} [-4000 \sin 400t + 2000 \cos 400t] \}
 \end{aligned}$$

$$\begin{aligned}
 v &= -25 \times 10^{-3} e^{-200t} \{-1000 \sin 400t - 4000 \sin 400t\} \\
 &= -25 \times 10^{-3} e^{-200t} \{-5000 \sin 400t\} \\
 &= 125 e^{-200t} \sin 400t \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \frac{dv}{dt} &= 125 \{e^{-200t} \cdot 400 \cos 400t - 200 e^{-200t} \sin 400t\} \\
 &= 25,000 e^{-200t} \{2 \cos 400t - \sin 400t\} \frac{\text{V}}{\text{s}}
 \end{aligned}$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad 2 \cos 400t = \sin 400t$$

$$\therefore \tan 400t = 2, \quad 400t = 1.11, \quad t = 2.77 \text{ ms}$$

$$[b] \quad v(2.77 \text{ ms}) = 125 e^{-0.55} \sin 1.11 = 64.27 \text{ V}$$

$$\begin{aligned}
 \text{P7.7 [a]} \quad v_L &= L \frac{di_L}{dt} = 50 \times 10^{-6} [18] \{e^{-10t} - 10te^{-10t}\} \\
 &= 900 \times 10^{-6} e^{-10t} (1 - 10t) = 900 e^{-10t} (1 - 10t) \mu\text{V}
 \end{aligned}$$

$$[b] \quad i(200 \text{ ms}) = 18(0.2)(e^{-2}) = 487.21 \text{ mA}$$

$$v(200 \text{ ms}) = 900 e^{-2} (1 - 2) = -121.80 \mu\text{V}$$

$$p(200 \text{ ms}) = vi = -59,342.67 \times 10^{-9} = -59.34 \mu\text{W}$$

$$[c] \quad \text{Delivering}$$

$$[d] \quad w = \frac{1}{2} Li^2; \quad w(200 \text{ ms}) = \frac{1}{2} (50 \times 10^{-6}) (0.48721^2) = 5.93 \mu\text{J}$$

$$[e] \quad \text{Energy stored is maximum when } i \text{ is maximum.}$$

$$\frac{di_L}{dt} = 18 [t(-10)e^{-10t} + e^{-10t}] = 18e^{-10t} (1 - 10t)$$

$$\frac{di_L}{dt} = 0, \quad t = 0.1 \text{ s}$$

$$i_L(\text{max}) = 18(0.1)e^{-1} = 662.18 \text{ mA}$$

$$w(\text{max}) = \frac{1}{2} (50 \times 10^{-6}) (0.66218)^2 = 10.96 \mu\text{J}$$

$$\text{P7.8 [a]} \quad v = -100t, \quad 0 \leq t \leq 1 \text{ s}$$

$$i = \frac{1}{5} \int_0^t -100x \, dx + 0 = (-20) \frac{x^2}{2} \Big|_0^t + 0 = -10t^2$$

$$i = -10t^2, \quad 0 \leq t \leq 1 \text{ s}$$

$$i(1) = -10 \text{ A}$$

$$v = -200 + 100t \text{ V}, \quad 1 \text{ s} \leq t \leq 3 \text{ s}$$

$$i = \frac{1}{5} \int_1^t (-200 + 100x) \, dx - 10 = 20 \int_1^t (-2 + x) \, dx - 10$$

$$i = 10t^2 - 40t + 20 \text{ A}, \quad 1 \text{ s} \leq t \leq 3 \text{ s}$$

$$i(3) = 90 - 120 + 20 = -10 \text{ A}$$

$$v = 100 \text{ V}, \quad 3 \text{ s} \leq t \leq 5 \text{ s}$$

$$i = \frac{1}{5} \int_3^t 100 \, dx - 10 = 20(t - 3) - 10$$

$$i = 20t - 70 \text{ A}, \quad 3 \text{ s} \leq t \leq 5 \text{ s}$$

$$i(5) = 100 - 70 = 30 \text{ A}$$

$$v = 600 - 100t \text{ V}, \quad 5 \text{ s} \leq t \leq 6 \text{ s}$$

$$i = \frac{1}{5} \int_5^t (600 - 100x) \, dx + 30$$

$$i = 20 \int_5^t (6 - x) \, dx + 30 = 120(t - 5) - 20 \frac{x^2}{2} \Big|_5^t + 30$$

$$= 120t - 600 - 10t^2 + 250 + 30$$

$$i = 120t - 10t^2 - 320 \text{ A}, \quad 5 \text{ s} \leq t \leq 6 \text{ s}$$

$$i(6 \text{ s}) = 720 - 360 - 320 = 40 \text{ A}$$


$$i = 40 \text{ A}, \quad 6 \text{ s} \leq t \leq \infty$$

[b] $v = 0$ at $t = 2 \text{ s}$ and $t = 6 \text{ s}$

$$i(2) = 10(4) - 40(2) + 20 = -20 \text{ A}$$

$$i(6) = 40 \text{ A}$$

[c]

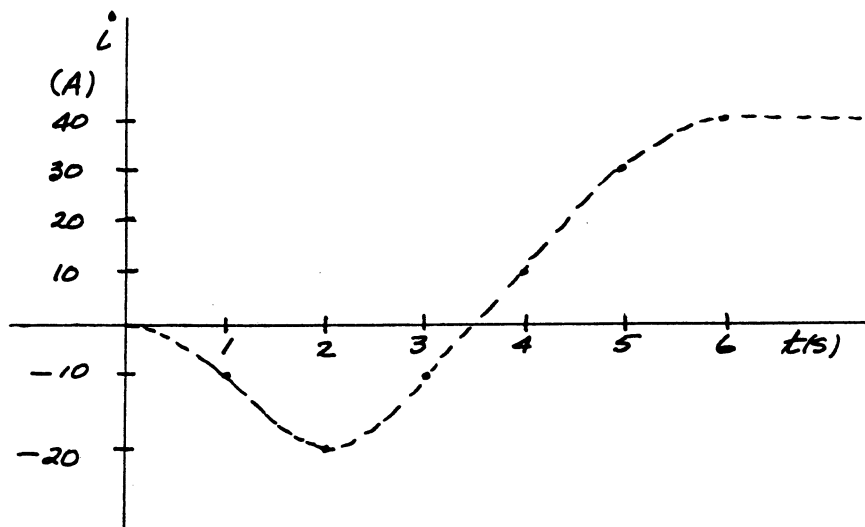

P7.9 $i(0) = B_1 = 10 \text{ A}$

$$\frac{di}{dt} = -0.5e^{-0.5t}(B_1 \cos 4t + B_2 \sin 4t)^{-0.5t} + (-4B_1 \sin 4t + 4B_2 \cos 4t)$$

$$\frac{di}{dt}(0) = -0.5B_1 + 4B_2$$

$$4\frac{di}{dt}(0) = v(0) = 60 = -2B_1 + 16B_2$$

$$\begin{aligned}
\therefore 16B_2 &= 60 + 2(10) = 80; & B_2 &= 5 \\
\therefore i &= (10 \cos 4t + 5 \sin 4t)e^{-0.5t} \text{ A}, & t &\geq 0 \\
\therefore v &= 4[-0.5e^{-0.5t}(10 \cos 4t + 5 \sin 4t) + e^{-0.5t}(-40 \sin 4t + 20 \cos 4t)] \\
&= (60 \cos 4t - 170 \sin 4t)e^{-0.5t} \text{ V} \\
\therefore i(1) &= -6.26 \text{ A}, & v(1) &= 54.25 \text{ V}, & p(1) &= -339.57 \text{ W (delivering)}
\end{aligned}$$

P7.10 [a] $v = 20 \times 10^{-3} \frac{di}{dt} = 20 \times 10^{-3}[-10,000A_1e^{-10,000t} - 40,000A_2e^{-40,000t}]$

$$= -200A_1e^{-10,000t} - 800A_2e^{-40,000t}$$

$$v(0) = -200A_1 - 800A_2 = 28$$

$$\therefore 200A_1 + 800A_2 = -28$$

$$50A_1 + 200A_2 = -7$$

Also $i(0) = 40 \times 10^{-3} = A_1 + A_2$

$$\therefore \Delta = \begin{vmatrix} 50 & 200 \\ 1 & 1 \end{vmatrix} = 50 - 200 = -150$$

$$N_1 = \begin{vmatrix} -7 & 200 \\ 40 \times 10^{-3} & 1 \end{vmatrix} = -7 - 8 = -15$$

$$N_2 = \begin{vmatrix} 50 & -7 \\ 1 & 40 \times 10^{-3} \end{vmatrix} = 2 + 7 = 9$$

$$\therefore A_1 = \frac{-15}{-150} = 0.1 = 100 \times 10^{-3} \text{ A}$$

$$A_2 = \frac{9}{-150} = -0.06 = -60 \times 10^{-3} \text{ A}$$

$$\therefore v = -200 \times 100 \times 10^{-3}e^{-10,000t} - 800(-60 \times 10^{-3})e^{-40,000t}$$

$$v = -20e^{-10,000t} + 48e^{-40,000t} \text{ V}, \quad t > 0$$

[b] From part [a] we have

$$i = 100e^{-10,000t} - 60e^{-40,000t} \text{ mA}, \quad t \geq 0$$

Now note i cannot equal zero for $t > 0$, i.e.,

$$i = 0 \text{ requires } 100e^{-10,000t} = 60e^{-40,000t}$$

$$\text{or } e^{30,000t} = 0.6 \text{ or } t = -17.03 \mu\text{s}$$

From our solution for v we see that v will equal zero when

$$48e^{-40,000t} = 20e^{-10,000t} \text{ or } e^{30,000t} = 2.4$$

$$\therefore t = 29.18 \mu\text{s}$$

Therefore the power at the terminals is zero when $t = 29.18 \mu\text{s}$.

P7.11 [a] From the solution to Problem 7.10 we can write $A_1 + A_2 = 40 \times 10^{-3}$

and $-200A_1 - 800A_2 = -68$ or $50A_1 + 200A_2 = 17$

$$\Delta = \begin{vmatrix} 1 & 1 \\ 50 & 200 \end{vmatrix} = 150$$

$$N_1 = \begin{vmatrix} 40 \times 10^{-3} & 1 \\ 17 & 200 \end{vmatrix} = 8 - 17 = -9$$

$$N_2 = \begin{vmatrix} 1 & 40 \times 10^{-3} \\ 50 & 17 \end{vmatrix} = 17 - 2 = 15$$

$$\therefore A_1 = \frac{N_1}{\Delta} = -60 \times 10^{-3} \text{ A}, \quad A_2 = \frac{N_2}{\Delta} = 100 \times 10^{-3} \text{ A}$$

$$\text{Therefore } i = (-60e^{-10,000t} + 100e^{-40,000t}) \text{ mA}, \quad t \geq 0$$

$$v = L \frac{di}{dt} = 20 \times 10^{-3} [600 \times 10^3 e^{-10,000t} - 4000 \times 10^3 e^{-40,000t}] \times 10^{-3}$$

$$v = 12e^{-10,000t} - 80e^{-40,000t} \text{ V}, \quad t \geq 0$$

[b] Note that $i = 0$ when

$$60e^{-10,000t} = 100e^{-40,000t}$$

$$e^{30,000t} = \frac{100}{60} = \frac{5}{3}; \quad t = 17.03 \mu\text{s}$$

Therefore i is positive for $0 \leq t \leq 17.03 \mu\text{s}$, and i is negative for $17.03 \mu\text{s} \leq t \leq \infty$.


Note that $v = 0$ when

$$12e^{-10,000t} = 80e^{-40,000t}$$

$$e^{30,000t} = \frac{80}{12} = \frac{20}{3}; \quad t = 63.24 \mu\text{s}$$

Therefore v is negative for $0 \leq t \leq 63.24 \mu\text{s}$, and v is positive for $63.24 \mu\text{s} \leq t \leq \infty$. See the following sketches of i and v . From the sketches we conclude

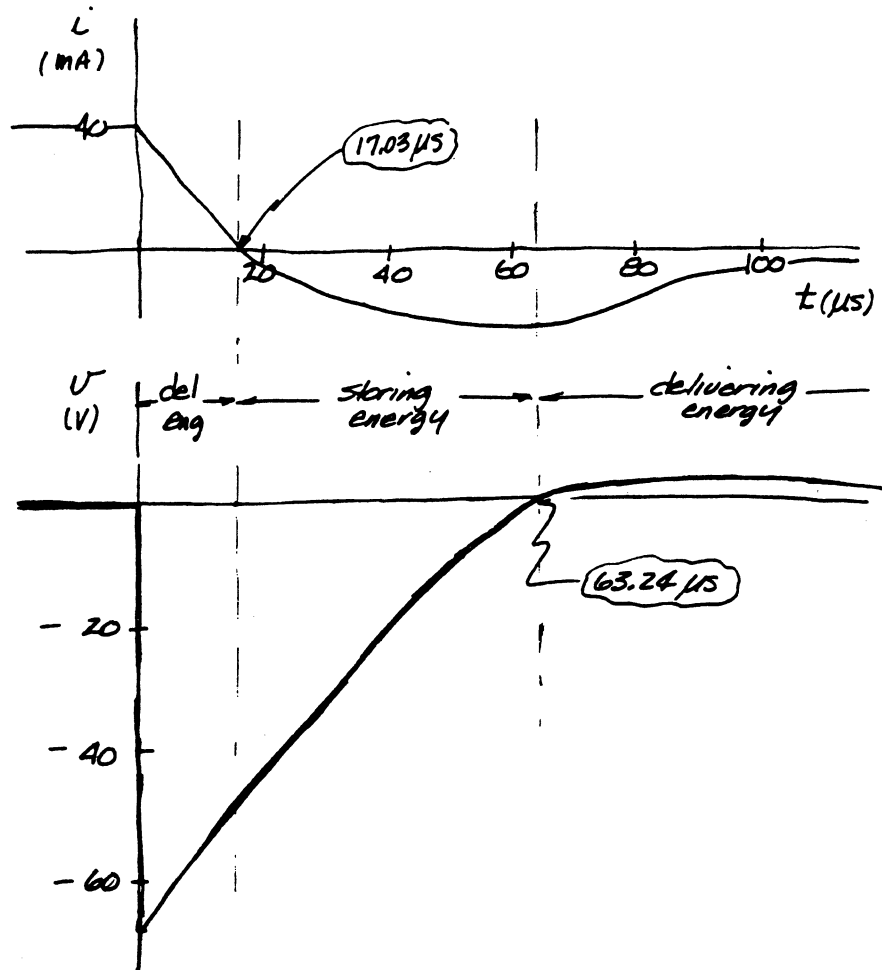- energy is being delivered by the inductor between 0 and $17.03 \mu\text{s}$ and between $63.24 \mu\text{s}$ and infinity.
- the inductor is storing energy between $17.03 \mu\text{s}$ and $63.24 \mu\text{s}$.



[c] The energy stored at $t = 0$ is

$$w(0) = \frac{1}{2} L [i(0)]^2 = \frac{1}{2} (20 \times 10^{-3}) (40 \times 10^{-3})^2 = 16 \times 10^{-6} = 16 \mu\text{J}$$

The energy for $t > 0$ is

$$\begin{aligned} w &= \int_0^{\infty} p \, dt \\ p &= vi = 6e^{-50,000t} - 8e^{-80,000t} - 0.72e^{-20,000t} \text{ W} \\ w &= \int_0^{\infty} 6e^{-50,000t} \, dt - \int_0^{\infty} 8e^{-80,000t} \, dt - \int_0^{\infty} 0.72e^{-20,000t} \, dt \\ &= \left. \frac{6e^{-5 \times 10^4 t}}{-5 \times 10^4} \right|_0^{\infty} - \left. \frac{8e^{-8 \times 10^4 t}}{-8 \times 10^4} \right|_0^{\infty} - \left. \frac{0.72e^{-2 \times 10^4 t}}{-2 \times 10^4} \right|_0^{\infty} \\ &= (1.2 - 1 - 0.36) \times 10^{-4} = -0.16 \times 10^{-4} \text{ J} = -16 \mu\text{J} \end{aligned}$$

Therefore $16 \mu\text{J}$ is extracted from the inductor, hence the energy extracted equals the energy stored.

P7.12 $0 \leq t \leq 1.6 \text{ s}$

$$i_L = \frac{1}{5} \int_0^t 3 \times 10^{-3} dx + 0 = 0.6 \times 10^{-3} t$$

$$i_L(1.6) = (0.6)(1.6) \times 10^{-3} = 0.96 \text{ mA}$$

$$v_{\text{meter}}(1.6 \text{ s}) = (0.96 \times 10^{-3})(20 \times 10^3) = 19.2 \text{ V}$$

P7.13 [a] $w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.2) \times 10^{-6} (150)^2 = 2250 \times 10^{-6} = 2.25 \text{ mJ}$

[b] $v = (A_1 t + A_2) e^{-5000t}$

$$v(0) = A_2 = 150 \text{ V}$$

$$\frac{dv}{dt} = -5000 e^{-5000t} (A_1 t + A_2) + e^{-5000t} (A_1)$$

$$= (-5000 A_1 t - 5000 A_2 + A_1) e^{-5000t}$$

$$\frac{dv}{dt}(0) = A_1 - 5000 A_2$$

$$i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{250 \times 10^{-3}}{0.2 \times 10^{-6}} = 1250 \times 10^3$$

$$\therefore 1.25 \times 10^6 = A_1 - 5000(150)$$

$$A_1 = 1.25 \times 10^6 + 75 \times 10^4 = 2.0 \times 10^6 \frac{\text{V}}{\text{s}}$$

[c] $v = (2 \times 10^6 t + 150) e^{-5000t}$

$$i = C \frac{dv}{dt} = 0.2 \times 10^{-6} \frac{d}{dt} (2 \times 10^6 t + 150) e^{-5000t}$$

$$i = \frac{d}{dt} [(0.4t + 30 \times 10^{-6}) e^{-5000t}]$$

$$= (0.4t + 30 \times 10^{-6}) (-5000) e^{-5000t} + e^{-5000t} (0.4)$$

$$= (-2000t - 150 \times 10^{-3} + 0.4) e^{-5000t}$$

$$= (0.25 - 2000t) e^{-5000t} \text{ A}, \quad t \geq 0$$

P7.14 [a] $i = C \frac{dv}{dt} = 0, \quad t < 0$

[b] $i = (0.4 \times 10^{-6})(-40) \{ (-2000 e^{-2000t})(3 \cos 1000t + \sin 1000t) \\ + e^{-2000t}(-3000 \sin 1000t + 1000 \cos 1000t) \}$

$$= -16 \times 10^{-3} e^{-2000t} \{ -6 \cos 1000t - 2 \sin 1000t - 3 \sin 1000t + \cos 1000t \}$$

$$i = 80 e^{-2000t} [\cos 1000t + \sin 1000t] \text{ mA}, \quad t > 0$$

[c] $v(0) = 100 - 40(1)(3) = -20 \text{ V}$

$$\therefore v = -20 \text{ V for } t \leq 0$$

$$v = -20 \text{ V when } t = 0$$

$$\therefore \text{No instantaneous change in } v \text{ at } t = 0.$$

- [d] $i = 0, \quad t < 0$
 $i = 80 \text{ mA}, \quad t = 0^+$
 $\therefore$ The current jumps instantaneously from 0 to 80 mA at $t = 0$.

[e] $v(\infty) = 100 \text{ V}$
 $w(\infty) = \frac{1}{2}(0.4)(10^{-6})(100)^2 = 2000 \mu\text{J}$

P7.15 [a] $v = \frac{1}{C} \int_0^t -50 \times 10^{-3} dx + 15 = (10^7)(-50 \times 10^{-3})x \Big|_0^t + 15$

$$v = -50 \times 10^4 t + 15, \quad 0 \leq t \leq 10 \mu\text{s}$$

$$v(10 \mu\text{s}) = -50 \times 10^4(10 \times 10^{-6}) + 15 = -5 + 15 = 10 \text{ V}$$

[b] $v = 10^7 \int_{10 \times 10^{-6}}^t 0.1 dx + 10 = 10^6 x \Big|_{10 \times 10^{-6}}^t + 10 = 10^6 t - 10 + 10$

$$v = 10^6 t, \quad 10 \mu\text{s} \leq t \leq 20 \mu\text{s}$$

$$v(20 \mu\text{s}) = 10^6(20 \times 10^{-6}) = 20 \text{ V}$$

[c] $v = 10^7 \int_{20 \times 10^{-6}}^t 0.16 dx + 20 = 10^7(0.16)[t - 20 \times 10^{-6}] + 20$
 $= 1.6 \times 10^6 t - 32 + 20$

$$v = 1.6 \times 10^6 t - 12, \quad 20 \mu\text{s} \leq t \leq 40 \mu\text{s}$$

[d] $v(40 \mu\text{s}) = 64 - 12 = 52 \text{ V}$
 $v(t) = 52, \quad 40 \mu\text{s} \leq t \leq \infty$

P7.16 [a] $q = \int_0^{5 \times 10^{-6}} 8 \times 10^4 x dx + \int_{5 \times 10^{-6}}^{15 \times 10^{-6}} 0.4 dx$
 $= 8 \times 10^4 \frac{x^2}{2} \Big|_0^{5 \times 10^{-6}} + 0.4(15 \times 10^{-6} - 5 \times 10^{-6})$
 $= 4 \times 10^4(25 \times 10^{-12}) + 0.4(10 \times 10^{-6})$
 $q = 10^{-6} + 4 \times 10^{-6} = 5 \mu\text{C}$

[b] $v = 4 \times 10^6 \int_0^{5 \times 10^{-6}} 8 \times 10^4 x dx + 4 \times 10^6 \int_{5 \times 10^{-6}}^{20 \times 10^{-6}} 0.4 dx$
 $+ 4 \times 10^6 \int_{20 \times 10^{-6}}^{30 \times 10^{-6}} (10^4 x - 0.5) dx$
 $= 4 \times 10^6 \left\{ 8 \times 10^4 \frac{x^2}{2} \Big|_0^{5 \times 10^{-6}} + 0.4x \Big|_{5 \times 10^{-6}}^{20 \times 10^{-6}} \right.$
 $\left. + 10^4 \frac{x^2}{2} \Big|_{20 \times 10^{-6}}^{30 \times 10^{-6}} - 0.5x \Big|_{20 \times 10^{-6}}^{30 \times 10^{-6}} \right\}$


$$\begin{aligned}
v &= 4 \times 10^6 \{ 4 \times 10^4 (25 \times 10^{-12}) + 0.4(15 \times 10^{-6}) \\
&\quad + 5000(900 \times 10^{-12} - 400 \times 10^{-12}) - 0.5(10 \times 10^{-6}) \} \\
&= 4 \times 10^6 \{ 10^{-6} + 6 \times 10^{-6} + 2.5 \times 10^{-6} - 5 \times 10^{-6} \} \\
&= 4 \times 10^6 \{ 4.5 \times 10^{-6} \} = 18 \text{ V} \\
v(30 \mu\text{s}) &= 18 \text{ V}
\end{aligned}$$

$$\begin{aligned}
[\text{c}] \quad v(50 \mu\text{s}) &= 4 \times 10^6 \{ 10^{-6} + 6 \times 10^{-6} + 5000(2500 \times 10^{-12} - 400 \times 10^{-12}) \\
&\quad - 0.5(30 \times 10^{-6}) \} \\
&= 4 \times 10^6 \{ 7 \times 10^{-6} + 10.5 \times 10^{-6} - 15 \times 10^{-6} \} \\
v(50 \mu\text{s}) &= 10 \text{ V} \\
w &= \frac{1}{2} C v^2 = \frac{1}{2} (0.25 \times 10^{-6}) (10)^2 = 12.5 \times 10^{-6} \text{ J} \\
w &= 12.5 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
\text{P7.17 [a]} \quad v(400 \mu\text{s}) &= \frac{10^6}{5} \left\{ \int_0^{100 \times 10^{-6}} 500 \times 10^{-3} dx + \int_{100 \times 10^{-6}}^{300 \times 10^{-6}} -250 \times 10^{-3} dx \right. \\
&\quad \left. + \int_{300 \times 10^{-6}}^{400 \times 10^{-6}} 400 \times 10^{-3} dx \right\} - 4 \\
&= \frac{10^3}{5} \{ 500(100 \times 10^{-6}) - 250(200 \times 10^{-6}) + 400(100 \times 10^{-6}) \} \\
&= \frac{10^3}{5} \{ 5 \times 10^{-2} - 5 \times 10^{-2} + 4 \times 10^{-2} \} - 4 = 8 - 4 = 4 \text{ V} \\
w &= \frac{1}{2} (5 \times 10^{-6}) (16) = 40 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
[\text{b}] \quad v(600 \mu\text{s}) &= \frac{10^3}{5} \{ 400(200 \times 10^{-6}) \} - 4 = 16 - 4 = 12 \text{ V} \\
w &= \frac{1}{2} (5 \times 10^{-6}) (144) = 360 \mu\text{J}
\end{aligned}$$
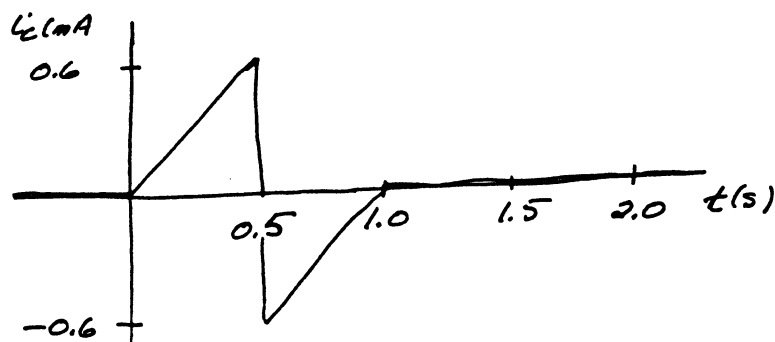
$$\begin{aligned}
\text{P7.18} \quad i_C &= C \frac{dv_C}{dt} = 20 \times 10^{-6} 60t = 1200 \times 10^{-6} t = 1.2t \text{ mA}, \quad 0 \leq t \leq 0.5^- \\
\therefore i_C(0.5^-) &= 0.6 \text{ mA} \\
i_C &= 20 \times 10^{-6} 60(t - 1) = 1.2(t - 1) \text{ mA}, \quad 0.5^+ \leq t \leq 1 \\
\therefore i_C(0.5^+) &= -0.6 \text{ mA} \\
i_C &= 0 \quad \text{elsewhere}
\end{aligned}$$




P7.19 [a] $v(20 \mu\text{s}) = 12.5 \times 10^9 (20 \times 10^{-6})^2 = 5 \text{ V}$ (end of first interval)
 $v(20 \mu\text{s}) = 10^6 (20 \times 10^{-6}) - (12.5)(400) \times 10^{-3} - 10 = 5 \text{ V}$
 (start of second interval)
 $v(40 \mu\text{s}) = 10^6 (40 \times 10^{-6}) - 12.5(1600) \times 10^{-3} - 10 = 10 \text{ V}$
 (end of second interval)

[b] $p(10 \mu\text{s}) = 62.5 \times 10^{12} (10^{-5})^3 = 62.5 \text{ mW}$, $v(10 \mu\text{s}) = 1.25 \text{ V}$,
 $i(10 \mu\text{s}) = 50 \text{ mA}$, $p(10 \mu\text{s}) = vi = 62.5 \text{ mW}$,
 $p(30 \mu\text{s}) = 437.50 \text{ mW}$, $v(30 \mu\text{s}) = 8.75 \text{ V}$, $i(30 \mu\text{s}) = 0.05 \text{ A}$

[c] $w(10 \mu\text{s}) = 15.625 \times 10^{12} (10 \times 10^{-6})^4 = 0.15625 \mu\text{J}$
 $w = 0.5 C v^2 = 0.5 (0.2 \times 10^{-6}) (1.25)^2 = 0.15625 \mu\text{J}$
 $w(30 \mu\text{s}) = 7.65625 \mu\text{J}$
 $w(30 \mu\text{s}) = 0.5 (0.2 \times 10^{-6}) (8.75)^2 = 7.65625 \mu\text{J}$

P7.20 $16 // 24 = 9.6 \text{ H}$ $12 + 8 = 20 \text{ H}$ $10 // 15 = 6 \text{ H}$
 $9.6 + 10.4 = 20 \text{ H}$ $20 // 5 = 4 \text{ H}$ $L_{ab} = 2 + 6 = 8 \text{ H}$
 $20 // 30 = 12 \text{ H}$ $4 + 6 = 10 \text{ H}$

P7.21 [a]

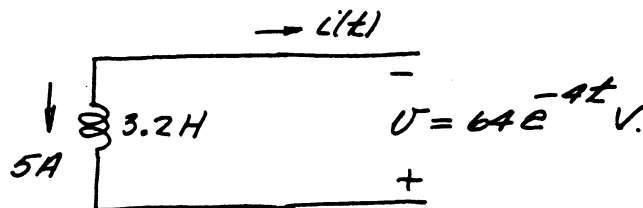

$$3.2 \frac{di}{dt} = 64e^{-4t}; \quad \frac{di}{dt} = 20e^{-4t}$$

$$i = 20 \int_0^t e^{-4x} dx - 5 = 20 \left[\frac{e^{-4x}}{-4} \right]_0^t - 5$$

$$i = -5e^{-4t} \text{ A}, \quad t \geq 0$$

$$[b] \quad 4 \frac{di_1}{dt} = 64e^{-4t}$$

$$\therefore i_1 = 16 \int_0^t e^{-4x} dx - 10 = 16 \left[\frac{e^{-4x}}{-4} \right]_0^t - 10$$

$$i_1 = -4e^{-4t} - 6 \text{ A}, \quad t \geq 0$$

$$[c] \quad 16 \frac{di_2}{dt} = 64e^{-4t}$$

$$\therefore i_2 = 4 \int_0^t e^{-4x} dx + 5$$

$$i_2 = -e^{-4t} + 6 \text{ A}, \quad t \geq 0$$

$$[d] \quad p = -vi = -64e^{-4t}(-5e^{-4t}) = 320e^{-8t} \text{ W}, \quad t \geq 0$$

$$w = 320 \int_0^\infty e^{-8t} dt = 40 \text{ J}$$

$$[e] \quad w(0) = \frac{1}{2}(4)(-10)^2 + \frac{1}{2}(16)(5)^2$$

$$w(0) = 400 \text{ J}$$


$$[f] \quad i_1(\infty) = -6 \text{ A}, \quad i_2(\infty) = 6 \text{ A}$$

$$w(\infty) = \frac{1}{2}(4)(-6)^2 + \frac{1}{2}(16)(6)^2 = 360 \text{ J}$$

$$[g] \quad w_{\text{del}} = w_{\text{init}} - w_{\text{trapped}} = 400 - 360 = 40 \text{ J} \quad (\text{yes})$$

P 7.22 [a] $i_o(0) = -i_1(0) - i_2(0) = 6 - 1 = 5 \text{ A}$


[b]

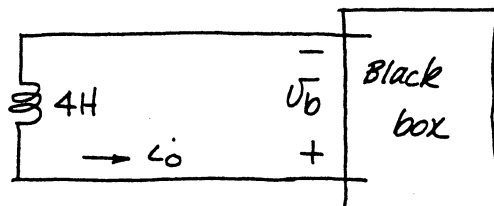

$$i_o = -\frac{1}{4} \int_0^t 2000e^{-100x} dx + 5 = -500 \left[\frac{e^{-100x}}{-100} \right]_0^t + 5$$

$$= 5(e^{-100t} - 1) + 5 = 5e^{-100t} \text{ A}, \quad t \geq 0$$

[c]

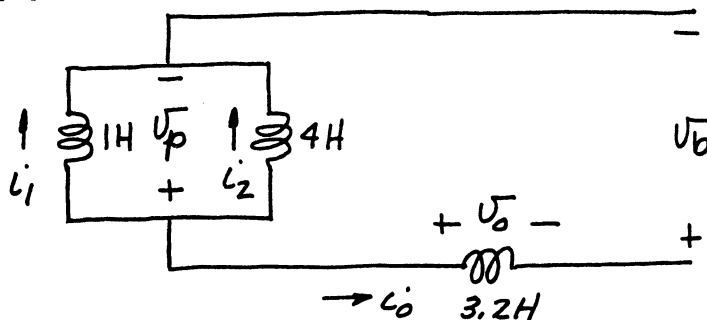

$$v_o = 3.2(-500e^{-100t}) = -1600e^{-100t} \text{ V}$$

$$v_p = v_b + v_o = 400e^{-100t} \text{ V}$$

$$i_1 = \frac{1}{1} \int_0^t 400e^{-100x} dx - 6 = -4(e^{-100t} - 1) - 6$$

$$i_1 = -4e^{-100t} - 2 \text{ A}, \quad t \geq 0$$

$$[d] \quad i_2 = \frac{1}{4} \int_0^t 400e^{-100x} dx + 1$$

$$i_2 = -e^{-100t} + 2 \text{ A}, \quad t \geq 0$$

$$[e] \quad w(0) = \frac{1}{2}(1)(6)^2 + \frac{1}{2}(4)(1)^2 + \frac{1}{2}(3.2)(5)^2 = 60 \text{ J}$$

$$[f] \quad w_{\text{del}} = \frac{1}{2}(4)(5)^2 = 50 \text{ J}$$

$$\text{or } w_{\text{del}} = \int_0^\infty 10,000e^{-200t} dt = -50(e^{-200t}|_0^\infty) = 50 \text{ J}$$

$$[g] \quad w_{\text{trapped}} = 60 - 50 = 10 \text{ J}$$

$$\text{or } w_{\text{trapped}} = \frac{1}{2}(1)(2)^2 + \frac{1}{2}(4)(2)^2 = 10 \text{ J}$$

$$\mathbf{P7.23} \quad w_{\text{del}} = \int_0^{t_o} p dt = \int_0^{t_o} 10^4 e^{-200t} dt = 10,000 \left[\frac{e^{-200t}}{-200} \right]_0^{t_o} = 50(1 - e^{-200t_o})$$

$$\% \text{ delivered} = \frac{50(1 - e^{-200t_o})}{50} \times 100 = 100(1 - e^{-200t_o})$$

$$\therefore 100(1 - e^{-200t_o}) = 80$$

$$200t_o = \ln 5$$

$$e^{-200t_o} = 0.2$$

$$t_o = 5 \ln 5 \text{ ms}$$

$$e^{200t_o} = 5$$

$$t_o = 8.05 \text{ ms}$$

P7.24 From Figure 7.17(a) we have

$$v = \frac{1}{C_1} \int_0^t i + v_1(0) + \frac{1}{C_2} \int_0^t i dx + v_2(0) + \dots$$

$$v = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots \right] \int_0^t i dx + v_1(0) + v_2(0) + \dots$$


Therefore $\frac{1}{C_{\text{eq}}} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \dots \right]$, $v_{\text{eq}}(0) = v_1(0) + v_2(0) + \dots$

P 7.25 From Fig. 7.18(a)


$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots = [C_1 + C_2 + \dots] \frac{dv}{dt}$$

Therefore $C_{\text{eq}} = C_1 + C_2 + \dots$. Because the capacitors are in parallel, the initial voltage on every capacitor must be the same. This initial voltage would appear on C_{eq} .

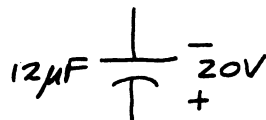
P 7.26 $48 \mu\text{F}$ in series with $16 \mu\text{F}$ is $12 \mu\text{F}$ with an initial voltage of 20 V , i.e.,



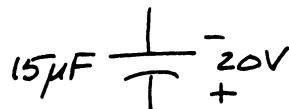
$12 \mu\text{F}$ in parallel with $3 \mu\text{F}$ is $15 \mu\text{F}$ charged to 20 V , i.e.,



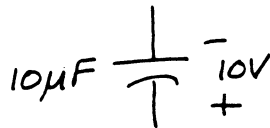
$15 \mu\text{F}$ in series with $30 \mu\text{F}$ is $10 \mu\text{F}$ with a net charge of 10 V , i.e.,



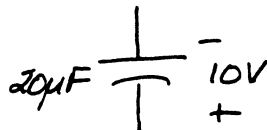
$10 \mu\text{F}$ in parallel with $10 \mu\text{F}$ is $20 \mu\text{F}$ with a charge of 10 V , i.e.,



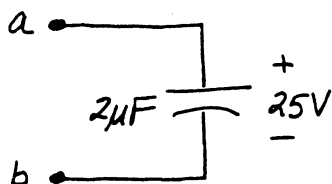$5\ \mu\text{F}$ in series with $20\ \mu\text{F}$ in series with $4\ \mu\text{F}$ is $2\ \mu\text{F}$ with a net charge of $25\ \text{V}$.




P7.27 [a]

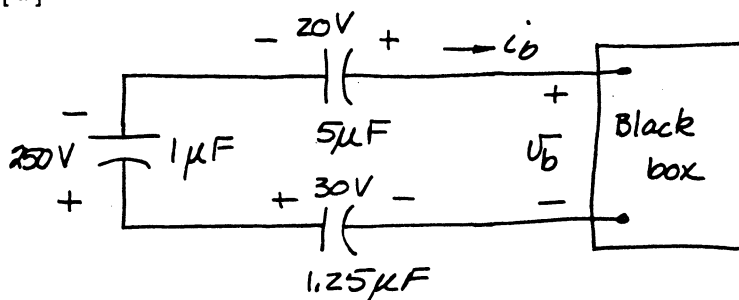

$$\frac{1}{C_e} = \frac{1}{1} + \frac{1}{5} + \frac{1}{1.25} = \frac{10}{5} = 2, \quad \therefore C_e = 0.5\ \mu\text{F}$$
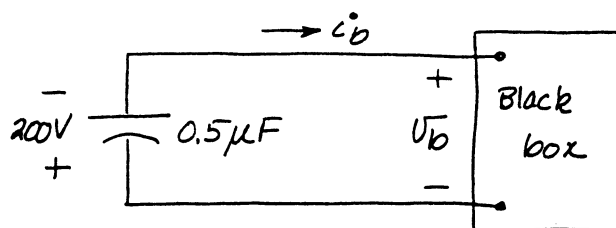
$$v_b(0) = 20 - 250 + 30 = -200\ \text{V}$$



$$\begin{aligned} v_b &= -\frac{10^6}{0.5} \int_0^t (-5 \times 10^{-3}) e^{-50x} dx - 200 = 10^4 \frac{e^{-50x}}{-50} \Big|_0^t - 200 \\ &= -200e^{-50t}\ \text{V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_a &= \frac{10^6}{5} \int_0^t (-5 \times 10^{-3}) e^{-50x} dx - 20 = 20(e^{-50t} - 1) - 20 \\ v_a &= 20e^{-50t} - 40\ \text{V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[c]} \quad v_c &= \frac{10^6}{1.25} \int_0^t (-5 \times 10^{-3}) e^{-50x} dx - 30 = 80(e^{-50t} - 1) - 30 \\ v_c &= 80e^{-50t} - 110\ \text{V}, \quad t \geq 0 \end{aligned}$$

$$[d] \quad v_d = 10^6 \int_0^t (-5 \times 10^{-3}) e^{-50x} dx + 250 = 100(e^{-50t} - 1) + 250$$

$$v_d = 100e^{-50t} + 150 \text{ V}, \quad t \geq 0$$

$$\text{Check: } v_b = -v_c - v_d - v_a = -200e^{-50t} \text{ V}, \quad t \geq 0 \quad (\text{ok})$$

$$[e] \quad i_1 = (0.2 \times 10^{-6}) \frac{dv_d}{dt} = (0.2 \times 10^{-6}) [-5000e^{-50t}]$$

$$i_1 = -e^{-50t} \text{ mA}, \quad t \geq 0$$

$$[f] \quad i_2 = (0.8 \times 10^{-6}) \frac{dv_d}{dt}$$

$$i_2 = -4e^{-50t} \text{ mA}, \quad t \geq 0$$

$$\text{Check: } i_b = i_1 + i_2 = -5e^{-50t} \text{ mA}, \quad t \geq 0 \quad (\text{ok})$$

P 7.28 [a] $w(0) = \frac{1}{2}(0.2 \times 10^{-6})(250)^2 + \frac{1}{2}(0.8 \times 10^{-6})(250)^2 + \frac{1}{2}(5 \times 10^{-6})(20)^2$

$$+ \frac{1}{2}(1.25 \times 10^{-6})(30)^2$$

$$w(0) = 32,812.50 \mu\text{J}$$

[b] $w(\infty) = \frac{1}{2}(5 \times 10^{-6})(1600) + \frac{1}{2}(1.25 \times 10^{-6})(110)^2 + \frac{1}{2}(0.2 \times 10^{-6})(150)^2$

$$+ \frac{1}{2}(0.8 \times 10^{-6})(150)^2$$

$$w(\infty) = 22,812.50 \mu\text{J}$$

[c] $w_{\text{del}} = \frac{1}{2}(0.5 \times 10^{-6})(200)^2 = 10,000 \mu\text{J}$

Check: $w(0) - w(\infty) = 10,000 \mu\text{J}$
--

[d] $\% \text{ delivered} = \frac{10,000}{32,812.50} \times 100 = 30.48\%$

[e] $w = \int_0^{t_o} p dt$

$$p = v_b i_b = (-200e^{-50t})(-5 \times 10^{-3})e^{-50t} = e^{-100t} \text{ W}$$


$$w = \int_0^{t_o} e^{-100t} dt = 10^4(1 - e^{-100t_o}) \mu\text{J}$$

$$10,000(1 - e^{-100t_o}) = 7500$$

$$e^{-100t_o} = 0.25, \quad e^{100t_o} = 4$$

$$t_o = 10 \ln 4 \text{ ms}, \quad t_o = 13.86 \text{ ms}$$

P7.29 [a]

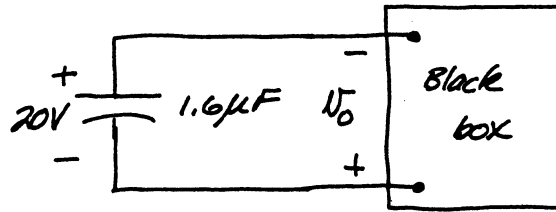

$$\begin{aligned}
 v_o &= \frac{10^6}{1.6} \int_0^t 800 \times 10^{-6} e^{-25x} dx - 20 = 500 \left[\frac{e^{-25x}}{-25} \right]_0^t - 20 \\
 &= -20(e^{-25t} - 1) - 20 \\
 v_o &= -20e^{-25t} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[b]} \quad v_1 &= \frac{10^6}{2} \int_0^t 800 \times 10^{-6} e^{-25x} dx + 5 = 400 \left[\frac{e^{-25x}}{-25} \right]_0^t + 5 \\
 &= -16(e^{-25t} - 1) + 5 \\
 v_1 &= -16e^{-25t} + 21 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad v_2 &= \frac{10^6}{8} \int_0^t 800 \times 10^{-6} e^{-25x} dx - 25 = -4(e^{-25t} - 1) - 25 \\
 v_2 &= -4e^{-25t} - 21 \text{ V}
 \end{aligned}$$

$$\text{Note: } v_1 + v_2 = v_o = -20e^{-25t} \text{ V}$$

$$\begin{aligned}
 \text{[d]} \quad p &= -v_o i = -(-20e^{-25t})(800 \times 10^{-6} e^{-25t}) = 16 \times 10^{-3} e^{-50t} \text{ W} \\
 w &= \int_0^\infty 16 \times 10^{-3} e^{-50t} dt = 16 \times 10^{-3} \left[\frac{e^{-50t}}{-50} \right]_0^\infty \\
 &= -0.32 \times 10^{-3} (0 - 1) = 320 \times 10^{-6} \text{ J} \\
 w &= 320 \mu\text{J}
 \end{aligned}$$

$$\text{[e]} \quad w(0) = \frac{1}{2} (2 \times 10^{-6}) (5)^2 + \frac{1}{2} (8 \times 10^{-6}) (25)^2 = 2525 \mu\text{J}$$

$$\text{[f]} \quad w_{\text{trapped}} = \frac{1}{2} (2 \times 10^{-6}) (21)^2 + \frac{1}{2} (8 \times 10^{-6}) (-21)^2 = 2205 \mu\text{J}$$

$$\text{[g]} \quad \text{Yes; } w(0) - w_{\text{trapped}} = 2525 - 2205 = 320 \mu\text{J}$$

P7.30 Let v_L equal the voltage drop across the 5-H inductor in the direction of i_o , then

$$\begin{aligned}
 v_L &= 5 \frac{di_o}{dt} = 5[60e^{-80t} \cos 60t - 80e^{-80t} \sin 60t] \\
 &= [300 \cos 60t - 400 \sin 60t] e^{-80t} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 v_C &= \frac{10^6}{20} \int_0^t e^{-80x} \sin 60x dx - 300 \\
 &= 5 \times 10^4 \left\{ \frac{e^{-80x}}{(6400 + 3600)} [-80 \sin 60x - 60 \cos 60x]_0^t \right\} - 300 \\
 &= -5 \{ e^{-80t} [80 \sin 60t + 60 \cos 60t] - 60 \} - 300
 \end{aligned}$$

$$v_C = -[400 \sin 60t + 300 \cos 60t]e^{-80t} \text{ V}$$

$$v_o = -(v_C + v_L) = -(-800e^{-80t} \sin 60t)$$

$$v_o = 800e^{-80t} \sin 60t \text{ V}$$

$$\begin{aligned} \text{P 7.31 } \frac{di_o}{dt} &= 5 \{ e^{-2000t} [-8000 \sin 4000t + 4000 \cos 4000t] \\ &\quad - 2000e^{-2000t} [2 \cos 4000t + \sin 4000t] \} \end{aligned}$$

$$\frac{di_o}{dt}(0^+) = 5\{1(4000) - 2000(2)\} = 0$$

$$\therefore 10 \times 10^{-3} \frac{di_o}{dt}(0^+) = 0, \quad \therefore v_2(0^+) = 0$$

$$v_1(0^+) = 40i_o(0^+) + v_2(0^+)$$

$$v_1(0^+) = 40(10) = 400 \text{ V}$$

Response of First-Order *RL* and *RC* Circuits

Drill Exercises

DE 8.1 [a] $i = \left(\frac{100}{1+4} \right) \left(\frac{-20}{25} \right) = -16 \text{ A}$

[b] $w = 0.5(10^{-2})(16)^2 = 1.28 \text{ J}$

[c] $r = \frac{L}{R} = \frac{10^{-2}}{4} = 2.5 \text{ ms}$

[d] $i = -16e^{-400t} \text{ A}, \quad t \geq 0$

[e] $i(5 \text{ ms}) = -2.17 \text{ A}, \quad w(5 \text{ ms}) = (0.5)(10)(2.17)^2 = 23.44 \text{ mJ}$

$w(\text{diss}) = 1280 - 23.44 = 1256.56 \text{ mJ}$

$\% \text{ dissipated} = \left(\frac{1256.56}{1280} \right) 100 = 98.17\%$

DE 8.2 [a] $i_L(0^-) = 6.4 \left(\frac{10}{16} \right) = 4 \text{ A} = i_L(0^+), \quad t > 0$

$R_{\text{eq}} = \frac{(4)(16)}{20} = 3.2 \Omega, \quad r = \frac{0.32}{3.2} = 0.1 \text{ s}$

Therefore $\frac{1}{r} = 10, \quad i_L = 4e^{-10t} \text{ A}$

Let i_1 equal the current in the 10Ω resistor.

Let the reference direction for i_1 be up. Then

$i_1 = \left(\frac{4}{20} \right) i_L = 0.8e^{-10t} \text{ A}, \quad v_o = -10i_1 = -8e^{-10t} \text{ V}, \quad t \geq 0$

$$[b] \quad v_{s4\Omega} = L \frac{di_L}{dt} = 0.32(-40)e^{-10t} = -12.8e^{-10t} \text{ V}, \quad t \geq 0$$

$$p_{4\Omega} = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0$$

$$w_{4\Omega} = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

$$w_i = \frac{1}{2}Li^2 = \frac{1}{2}(0.32)(16) = 2.56 \text{ J}$$

$$\% \text{ dissipated} = \left(\frac{2.048}{2.56} \right) 100 = 80\%$$

$$\text{DE 8.3} [a] \quad v(0) = \left[\frac{15(60)}{90} \right] 20 = 200 \text{ V}$$

$$[b] \quad \tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 10 \text{ ms}$$


$$[c] \quad v = 200e^{-100t} \text{ V}$$

$$[d] \quad w(0) = 0.5(0.5 \times 10^{-6})(200)^2 = 10 \text{ mJ}$$

$$[e] \quad w(t) = 0.5(0.5 \times 10^{-6})(4 \times 10^4)e^{-200t} = 10e^{-200t} \text{ mJ}$$

$$10e^{-200t} = 2.5, \quad t = (\ln 4)/200 = 6.93 \text{ ms}$$
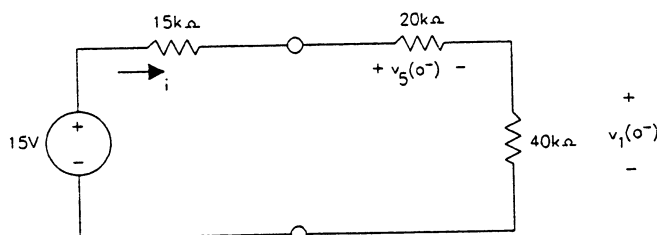
$$\text{DE 8.4} [a] \quad \text{For } t < 0:$$



$$i = \frac{15}{75} = \frac{1}{5} \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}, \quad 1/\tau_5 = 10$$

$$\tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}, \quad 1/\tau_1 = 25$$

$$\text{Therefore } v_5 = 4e^{-10t} \text{ V}, \quad t \geq 0; \quad v_1 = 8e^{-25t} \text{ V}, \quad t \geq 0;$$

$$v_o = v_1 + v_5 = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

$$[b] \quad v_1(60 \text{ ms}) \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) \cong 2.20 \text{ V}$$

$$w_1(60 \text{ ms}) = (1/2)(1)(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = (1/2)(5)(2.20)^2 \cong 12.05 \mu\text{J}$$


$$w_1(0) = (1/2)(1)(64) + (1/2)(5)(16) = 72 \mu\text{J}$$

$$w_{\text{diss}} = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36/72)(100) = 81.05 \%$$

- DE 8.5** [a] $i(0^+) = 24/2 = 12 \text{ A}$
 [b] $v(0^+) = -10(8 + 12) = -200 \text{ V}$
 [c] $\tau = L/R = (200/10) \times 10^{-3} = 20 \text{ ms}$
 [d] $i = -8 + [12 - (-8)]e^{-50t} = [-8 + 20e^{-50t}] \text{ A}, \quad t \geq 0^+$
 [e] $v = 0 + [-200 - 0]e^{-50t} \text{ V} = -200e^{-50t} \text{ V}, \quad t \geq 0^+$

DE 8.6 [a]

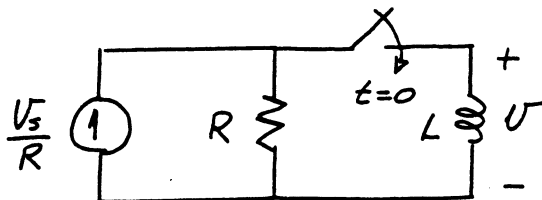

$$\frac{v}{R} + \frac{1}{L} \int_0^t v dx = \frac{V_s}{R}$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0$$

$$\frac{dv}{dt} + \frac{R}{L} v = 0$$

[b] $\frac{dv}{dt} = -\frac{R}{L} v$

$$\frac{dv}{dt} dt = -\frac{R}{L} v dt$$

$$\therefore \frac{dv}{v} = -\frac{R}{L} dt$$

$$\int_{v(0^+)}^{v(t)} \frac{dy}{y} = -\frac{R}{L} \int_{0^+}^t dx$$


$$\ln y \Big|_{v(0^+)}^{v(t)} = -\left(\frac{R}{L}\right) t$$

$$\ln \left[\frac{v(t)}{v(0^+)} \right] = -\left(\frac{R}{L}\right) t$$

$$v(t) = v(0^+) e^{-(R/L)t}; \quad v(0^+) = \left(\frac{V_s}{R} - I_o\right) R = V_s - I_o R$$


$$\therefore v(t) = (V_s - I_o R) e^{-(R/L)t}$$

DE 8.7 [a]

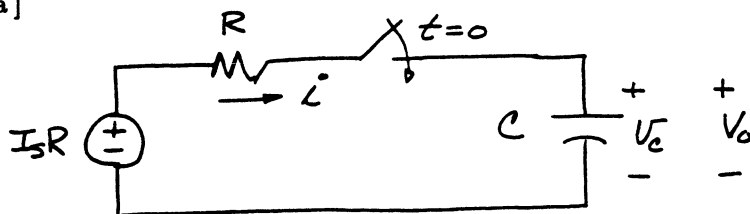

$$\begin{aligned}
 I_s R &= Ri + \frac{1}{C} \int_{0^+}^t i \, dx + V_o \\
 0 &= R \frac{di}{dt} + \frac{i}{C} + 0 \\
 \therefore \frac{di}{dt} + \frac{i}{RC} &= 0 \\
 [b] \quad \frac{di}{dt} &= -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC} \\
 \int_{i(0^+)}^{i(t)} \frac{dy}{y} &= -\frac{1}{RC} \int_{0^+}^t dx \\
 \ln \frac{i(t)}{i(0^+)} &= \frac{-t}{RC} \\
 i(t) &= i(0^+) e^{-t/RC}; \quad i(0^+) = \frac{I_s R - V_o}{R} = \left(I_s - \frac{V_o}{R} \right) \\
 \therefore i(t) &= \left(I_s - \frac{V_o}{R} \right) e^{-t/RC}
 \end{aligned}$$

DE 8.8 [a]

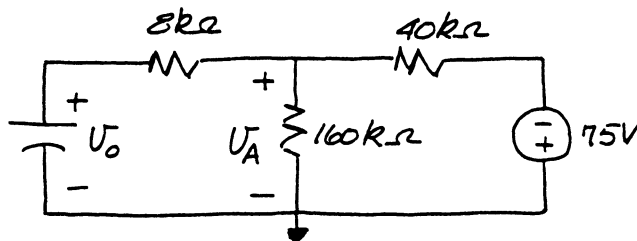

$$\begin{aligned}
 \frac{v_A - v_o}{8} + \frac{v_A}{160} + \frac{v_A + 75}{40} &= 0 \\
 20v_A - 20v_o + v_A + 4v_A + 300 &= 0 \\
 25v_A &= 20v_o - 300 \\
 v_A &= 0.8v_o - 12 \\
 v_A &= -48 + 72e^{-100t} - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+
 \end{aligned}$$

DE 8.9 [a] $v_c(0^+) = 90 \text{ V}$

$$[b] \quad v_c(\infty) = \left(-\frac{40}{80} \right) 60 = -30 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$v_{Th} = -30 \text{ V}, \quad R_{Th} = 20 // 60 = 15 \, \Omega,$$

$$\text{Therefore } \tau = 15(0.5) = 7.5 \, \mu\text{s}$$

$$[d] \quad i(0^+) = -\frac{90 + 30}{15} = -8 \text{ A}$$

$$[e] \quad v_c = -30 + [90 - (-30)]e^{-t/\tau} = -30 + 120e^{-(400,000/3)t} \text{ V}, \quad t \geq 0^+$$

$$[f] \quad i = -8e^{-t/\tau} = -8e^{-(400,000/3)t} \text{ A}, \quad t \geq 0$$

$$\text{Therefore } e^{100t\tau} = 15,000/10 = 1500$$

$$100t\tau = \ln 1500; \quad t\tau = 0.01(\ln 1500); \quad t\tau = 73.13 \text{ ms}$$

$$\text{DE 8.10 [a]} \quad v_c(0^+) = (60/15)(11.5) = 46 \text{ V}$$

$$[b] \quad v_c(\infty) = -8(6.75) = -54 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor,


$$v_{Th} = -54 \text{ V}, \quad R_{Th} = 8 \text{ k}\Omega$$

$$\tau = R_{Th}C = 400 \mu\text{s}$$

$$[d] \quad v_c = -54 + (46 + 54)e^{-2500t} = -54 + 100e^{-2500t}$$

$$\text{Therefore } t = \frac{\ln(100/54)}{2500} = 246.47 \mu\text{s}$$

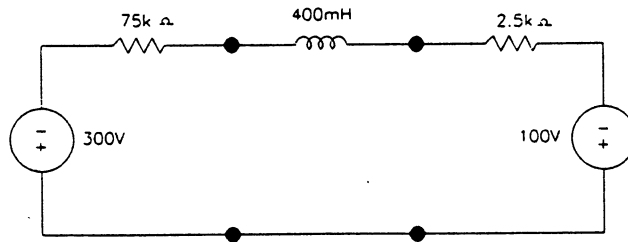
DE 8.11 [a] For $t < 0$, calculate the Thévenin equivalent for the circuit to the left and right of the 400-mH inductor. We get



$$i(0^-) = -200/10 = -20 \text{ mA}$$

$$i(0^-) = i(0^+) = -20 \text{ mA}$$

[b] For $t > 0$, the circuit reduces to

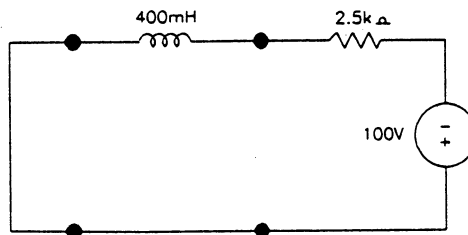

$$\text{Therefore } i(\infty) = 100/2.5 = 40 \text{ mA}$$

$$[c] \quad \tau = (400/2.5) \times 10^{-6} = 160 \mu s$$


$$[d] \quad i(t) = 40 + [-20 - 40]e^{-6250t} \text{ mA}, \quad t > 0^+$$

DE 8.12 [a] For $t < 0$:

$$i = \left(\frac{20}{100} \right) 20 = 4 \text{ mA}$$

$$v_c(0^-) = (4)(50) = 200 \text{ V}$$

$$v_c(0^+) = 200 \text{ V}$$

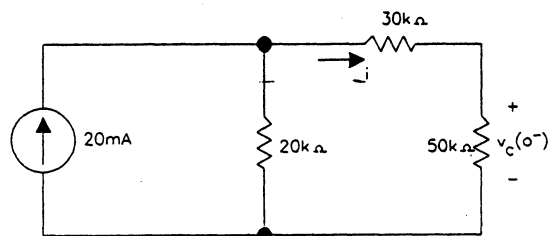


For $0 \leq t \leq 50 \text{ ms}$:

$$\tau = (50)(2.0)10^{-3} = 0.10 \text{ s}$$

$$1/\tau = 10$$

$$v_c = 200e^{-10t} \text{ V}$$

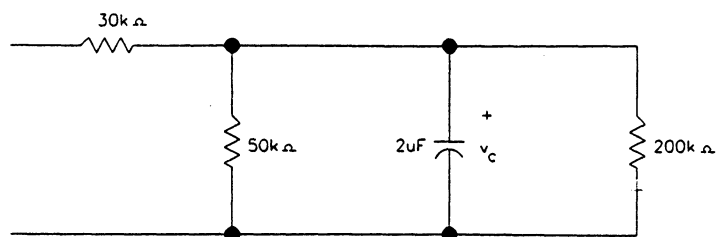

$$[b] \quad v_c(0.05) = 200e^{-0.5} = 121.31 \text{ V.} \quad \text{For } t \geq 50 \text{ ms:}$$

$$R_{eq} = \frac{50(200)}{250} = 40 \text{ k}\Omega, \quad r = (40)(2)10^{-3} = 0.08 \text{ s}$$

$$\frac{1}{\tau} = 12.5$$

$$\text{Therefore } v_c = 121.31e^{-12.5(t-0.05)} \text{ V}, \quad t \geq 0.05 \text{ s}$$

$$[c] \quad w_{50k} = \int_0^{0.05} \frac{[200e^{-10t}]^2}{50,000} dt + \int_{0.05}^{\infty} \frac{[200e^{-0.5}e^{-12.5(t-0.05)}]^2}{50,000} dt = 37.06 \text{ mJ}$$

$$[d] \quad w_{200k\Omega} = \int_{0.05}^{\infty} \frac{[200e^{-0.5}e^{-12.5(t-0.05)}]^2}{200,000} dt = 2.94 \text{ mJ}$$

$$\text{Check: } w_{\text{stored}} = (1/2)(2 \times 10^{-6})(200)^2 = 40 \text{ mJ}$$

$$w_{\text{diss}} = 37.06 + 2.94 = 40 \text{ mJ}$$

DE 8.13 [a] At the instant A is closed, $i(0^+) = 0$. For $0 \leq t \leq 1 \text{ s}$, the Thévenin equivalent with respect to the terminals of the 2-H inductor is $v_{Th} = 3 \text{ V}$, $R_{Th} = 1 \Omega$; therefore in this interval $i(0^+) = 0$ and $i(\infty) = 3 \text{ A}$, also $\tau = 2/1 = 2 \text{ s}$. Thus $i = 3 - 3e^{-0.5t} \text{ A}$, $0^+ \leq t \leq 1$, and $i(1) = 3 - 3e^{-0.5} = 1.18 \text{ A}$.

[b] When $t > 1 \text{ s}$, the Thévenin equivalent w.r.t. the 2-H inductor is $v_{Th} = -12 \text{ V}$, $R_{Th} = 2.5 \Omega$. Therefore $i(\infty) = -12/2.5 = -4.8 \text{ A}$ and $\tau = 2/2.5 = 0.8$, thus $i = 4.8 + (1.18 + 4.8)e^{-1.25(t-1)} \text{ A}$, $1 \leq t \leq \infty$.

DE 8.14 Derivation of Eq. (8.74): Substituting Eq. (8.73) into Eq. (8.72) gives

$$\begin{aligned} v_o &= \frac{V_m R_f}{R_s} + \left\{ -\frac{V_m R_f}{R_s} (1 - e^{-t_1/R_f C_f}) - \frac{V_m R_t}{R_s} \right\} e^{-(t-t_1)/R_f C_f} \\ &= \frac{V_m R_f}{R_s} \left\{ 1 - [1 - e^{-t_1/R_f C_f} + 1]e^{-(t-t_1)/R_f C_f} \right\} \\ &= \frac{V_m R_f}{R_s} \left\{ 1 - [2 - e^{-t_1/R_f C_f}]e^{-(t-t_1)/R_f C_f} \right\} \\ v_o &= \frac{V_m R_f}{R_s} - \frac{V_m R_f}{R_s} (2 - e^{-t_1/R_f C_f})e^{-(t-t_1)/R_f C_f}, \quad t_1 \leq t \leq 2t_1 \end{aligned}$$

Derivation of Eq. (8.75):

$$\begin{aligned} v_o(2t_1) &= \frac{V_m R_f}{R_s} - \frac{V_m R_f}{R_s} (2 - e^{-t_1/R_f C_f})e^{-t_1/R_f C_f} \\ &= \frac{V_m R_f}{R_s} [1 - 2e^{-t_1/R_f C_f} + e^{-2t_1/R_f C_f}] \end{aligned}$$

$$\text{Let } x = e^{-t_1/R_f C_f}; \quad x^2 = e^{-2t_1/R_f C_f}$$

$$v_o(2t_1) = \frac{V_m R_f}{R_s} (1 - 2x + x^2) = \frac{V_m R_f}{R_s} (1 - x)^2 = \frac{V_m R_f}{R_s} [1 - e^{-t_1/R_f C_f}]^2$$

Derivation of Eq. (8.76):

$$v_o(t_o) = 0$$

$$\frac{V_m R_f}{R_s} = \frac{V_m R_f}{R_s} (2 - e^{-t_1/R_f C_f})e^{-(t_o-t_1)/R_f C_f}$$

$$1 = (2 - e^{-t_1/R_f C_f})e^{-(t_o - t_1)/R_f C_f}$$

$$e^{+(t_o - t_1)/R_f C_f} = 2 - e^{-t_1/R_f C_f}$$

$$e^{+t_o/R_f C_f} = 2e^{t_1/R_f C_f} - 1$$

$$\frac{t_o}{R_f C_f} = \ln[2e^{t_1/R_f C_f} - 1]$$

$$t_o = R_f C_f \ln[2e^{t_1/R_f C_f} - 1]$$

DE 8.15 [a] From Eqs. (8.70), (8.74), and (8.79):

$$v_o = -\frac{R_f}{R_s} V_m (1 - e^{-t/R_f C_f}), \quad 0 \leq t \leq t_1$$

$$v_o = \frac{R_f}{R_s} V_m - \frac{R_f}{R_s} V_m (2 - e^{-t_1/R_f C_f}) e^{-(t-t_1)/R_f C_f}, \quad t_1 \leq t \leq 2t_1$$

$$v_o = \frac{V_m R_f}{R_s} (1 - e^{-t_1/R_f C_f})^2 e^{-(t-2t_1)/R_f C_f}, \quad 2t_1 \leq t \leq \infty$$

$$t_o = R_f C_f \ln(2e^{t_1/R_f C_f} - 1)$$

$$\frac{R_f}{R_s} = \frac{50 \times 10^6}{100 \times 10^3} = 500; \quad \frac{R_f}{R_s} V_m = (500)(50 \times 10^{-3}) = 25$$

$$\frac{1}{R_f C_f} = \frac{1}{(50)(0.1)} = 0.20$$

$$v_o = -25(1 - e^{-0.2t}) \text{ V}, \quad 0 \leq t \leq 1$$

$$v_o = 25 - 25(2 - e^{-0.2})e^{-0.2(t-1)}$$

$$v_o = 25 - 29.53e^{-0.2(t-1)} \text{ V}, \quad 1 \leq t \leq 2$$


$$v_o = 25(1 - e^{-0.2})^2 e^{-0.2(t-2)}$$

$$v_o = 0.82e^{-0.2(t-2)} \text{ V}, \quad 2 \leq t \leq \infty$$

[b] $v_o(t_1) = v_o(1) = -25(1 - e^{-0.2}) = -4.53 \text{ V}$

$$v_o(2t_1) = v_o(2) = 0.82$$
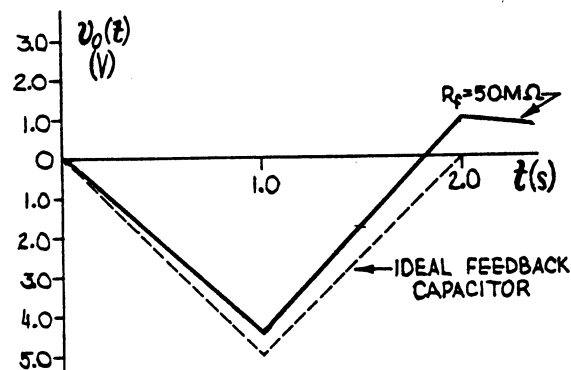
$$t_o = 5 \ln(2e^{0.2} - 1) = 1.83 \text{ s}$$



Problems

P 8.1 [a] $R = \frac{v}{i} = 25 \Omega$

[b] $\frac{1}{\tau} = 10, \quad \tau = 0.10 \text{ s} = 100 \text{ ms}$

[c] $\frac{1}{\tau} = \frac{R}{L} = 10. \quad L = \frac{R}{10} = 2.5 \text{ H}$

[d] $i(0) = 6.4 \text{ A}; \quad w(0) = \frac{1}{2}(2.5)(6.4)^2 = 51.20 \text{ J}$

[e] $w = \int_0^{t_0} vi \, dt = \int_0^{t_0} 1024e^{-20x} dx = 1024 \left[\frac{e^{-20t}}{-20} \right]_0^{t_0}$
 $= -51.20(e^{-20t_0} - 1) = 51.20(1 - e^{-20t_0})$
 $\% \text{ dissipated} = \frac{51.20(1 - e^{-20t_0})}{51.20} \times 100 = 100(1 - e^{-20t_0})$
 $\therefore 100(1 - e^{-20t_0}) = 60; \quad e^{-20t_0} = 0.40; \quad e^{20t_0} = 2.5$
 $t_0 = \frac{1}{20} \ln 2.5 = 50 \ln 2.5 \text{ ms} = 45.81 \text{ ms}$

P 8.2 [a] $i(0) = \frac{24}{12} = 2 \text{ A}$

[b] $\tau = \frac{L}{R} = \frac{1.6}{80} = 0.02 \text{ s} = 20 \text{ ms}$

[c] $i = 2e^{-50t} \text{ A}, \quad t \geq 0$

$v_1 = 1.6 \frac{d}{dt}(2e^{-50t}) = -160e^{-50t} \text{ V}, \quad t \geq 0$

$v_2 = -72i = -144e^{-50t} \text{ V}, \quad t \geq 0$


[d] $w(0) = \frac{1}{2}(1.6)(2)^2 = 3.2 \text{ J}$

$w_{72\Omega} = \int_0^{t_0} 72(4e^{-100x}) dx = 288 \left[\frac{e^{-100x}}{-100} \right]_0^{t_0} = 2.88(1 - e^{-100t_0})$

$w_{72\Omega}(15 \text{ ms}) = 2.88(1 - e^{-1.5}) = 2.24 \text{ J}$

$\% \text{ dissipated} = \frac{2.24}{3.2} \times 100 = 69.92$

P 8.3 [a]

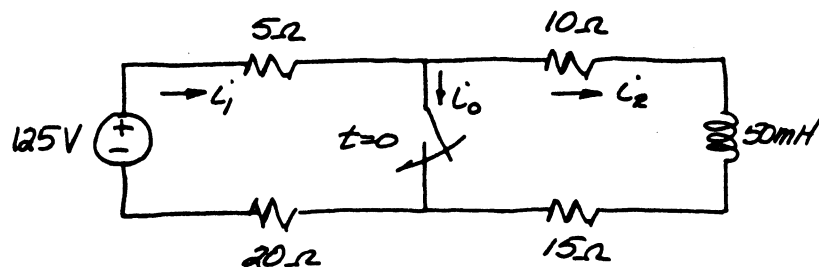

Before the switch is closed, $i_2 = 125/50 = 2.5$ A.

Therefore $i_2(0^-) = i_2(0^+) = 2.5$ A

$i_1(0^-) = 2.5$ A, but $i_1(0^+) = 125/25 = 5$ A

$\therefore i_o(0^+) = i_1(0^+) - i_2(0^+) = 5 - 2.5 = 2.5$ A

$i_o(\infty) = 125/25 = 5$ A

$$[b] \quad i_2 = 2.5e^{-t/\tau} \text{ A}, \quad \tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{25} = 2 \text{ ms}$$

$$\therefore i_2 = 2.5e^{-500t} \text{ A}, \quad t \geq 0$$

$$i_1 = 5 \text{ A}, \quad t \geq 0$$


$$i_o = i_1 - i_2 = 5 - 2.5e^{-500t} \text{ A}, \quad t \geq 0$$

$$[c] \quad 5 - 2.5e^{-500t} = 3 \quad t = (1/500) \ln 1.25$$

$$2.5e^{-500t} = 2 \quad = 2000 \ln 1.25 \mu\text{s}$$

$$e^{500t} = 1.25 \quad t = 446.29 \mu\text{s}$$
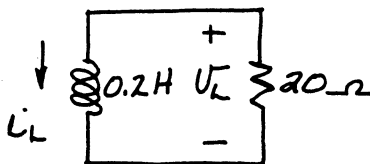
$$\mathbf{P8.4} \quad t > 0: \quad i_L(0) = \left(\frac{80}{20}\right) \left(\frac{50}{80}\right) = 2.5 \text{ A}$$



$$\tau = \frac{0.2}{20} = 0.01 \text{ s}$$

$$\frac{1}{\tau} = 100$$

$$i_L = 2.5e^{-100t} \text{ A}, \quad t \geq 0^+$$

$$v_L = -20i_L = -50e^{-100t} \text{ V}, \quad t \geq 0^+$$

$$v_o = -15i_L = -37.5e^{-100t} \text{ V}, \quad t \geq 0^+$$


$$\mathbf{P8.5} \quad w(0) = \frac{1}{2}(0.2)(2.5)^2 = 625 \text{ mJ}$$

$$p_{2\Omega} = 2i_L^2 = 12.5e^{-200t} \text{ W}$$

$$w_{2\Omega} = \int_0^{0.02} 12.5e^{-200t} dt = 12.5 \frac{e^{-200t}}{(-200)} \bigg|_0^{0.02} = 62.5 \times 10^{-3}(1 - e^{-4}) = 61.36 \text{ mJ}$$



$$\% \text{ dissipated} = \frac{61.36}{625} \times 100 = 9.82\%$$

P8.6 For $t < 0$:

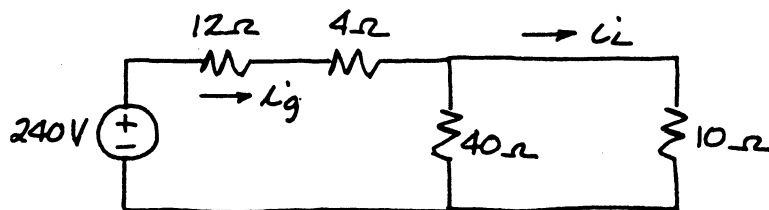

$$i_g = \frac{240}{16 + 8} = 10 \text{ A}; \quad \therefore i_L(0^-) = (10) \frac{40}{50} = 8 \text{ A}$$

For $t \geq 0^+$:

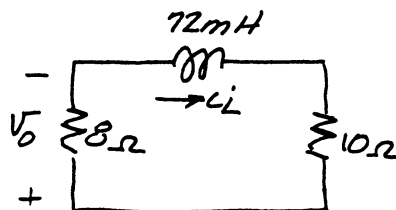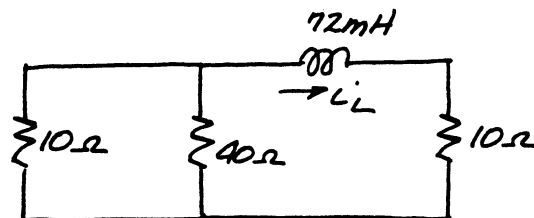

$$\tau = \frac{72 \times 10^{-3}}{18} = 4 \text{ ms}$$

$$\frac{1}{\tau} = 250$$

$$\therefore i_L = 8e^{-250t} \text{ A}, \quad t \geq 0^+$$

$$v_o = - \left[10i_L + 0.072 \frac{di_L}{dt} \right] = - [80e^{-250t} - 144e^{-250t}] = 64e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$\text{or } v_o = 8i_L = 64e^{-250t} \text{ V}, \quad t \geq 0^+$$

P8.7 $w(0) = \frac{1}{2}(72 \times 10^{-3})(8)^2 = 2304 \text{ mJ}$

$$p_{40\Omega} = \frac{v_o^2}{40} = \frac{(64)^2}{40} e^{-500t} = 102.4e^{-500t} \text{ W}$$

$$w_{40\Omega} = \int_0^\infty 102.4e^{-500t} dt = 204.8 \text{ mJ}$$

$$\% \text{ dissipated} = \frac{204.8}{2304} \times 100 = 8.89\%$$

P8.8 [a] When the switch is opened, v_o is the natural response of the inductor voltage, hence

$$v_o = v_o(0^+)e^{-t/\tau}, \quad t \geq 0^+$$

where $\tau = L/R$

By hypothesis $v_o(10^{-3}) = v_o(0^+)e^{-10^{-3}/\tau} = 0.5v_o(0^+)$

It follows that $e^{10^{-3}/\tau} = 2, \quad \frac{10^{-3}}{\tau} = \ln 2$

$$\therefore L = \frac{10}{\ln 2} \times 10^{-3} = 14.43 \text{ mH}$$

[b] $v_o(0^+) = -10i_L(0^+) = -10 \left(\frac{1}{10} \right) (30 \times 10^{-3}) = -30 \text{ mV} = -0.03 \text{ V}$

$$\therefore v_o = -0.03e^{-t/\tau} \text{ V}, \quad t \geq 0^+$$

$$p_{10\Omega} = \frac{v_o^2}{10} = 9 \times 10^{-5} e^{-2t/\tau}$$

$$w_{10\Omega} = \int_{0^+}^{10^{-3}} 9 \times 10^{-5} e^{-2t/\tau} dt = 4.5\tau \times 10^{-5} (1 - e^{-2 \times 10^{-3}/\tau})$$

$$\tau = \frac{1}{1000 \ln 2}$$

$$\therefore w_{10\Omega} = 48.69 \text{ nJ}$$

$$w_L(0) = \frac{1}{2} L i_L^2(0) = \frac{1}{2} (14.43) \times 10^{-3} (3 \times 10^{-3})^2 = 64.92 \text{ nJ}$$

$$\% \text{ dissipated in } 1 \text{ ms} = \frac{48.69}{64.92} \times 100 = 75\%$$

Alternate solution:

$$i_L = 3e^{-t/\tau} \text{ mA}, \quad t \geq 0$$

$$i_L(1 \text{ ms}) = 1.5 \text{ mA}$$


Therefore the energy stored in the inductor at 1 ms is

$$w_L(1 \text{ ms}) = \frac{1}{2} (14.43 \times 10^{-3}) (2.25 \times 10^{-6}) = 16.23 \text{ nJ}$$

$$\therefore w_L(\text{diss}) = w_L(0) - w_L(1 \text{ ms}) = 64.92 - 16.23 = 48.69 \text{ nJ}$$

$$\% \text{ dissipated in } 1 \text{ ms} = \frac{48.69}{64.92} \times 100 = 75\%$$

P8.9 [a] For $t < 0$:

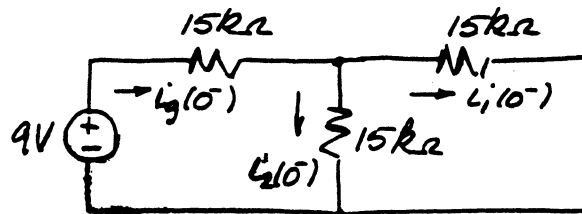


$$i_g(0^-) = \frac{9 \times 10^{-3}}{(15 + 7.5)} = 400 \times 10^{-6} = 400 \mu\text{A}$$

$$i_1(0^-) = \frac{1}{2}(400) = 200 \mu\text{A}$$

$$i_2(0^-) = \frac{1}{2}(400) = 200 \mu\text{A}$$

[b] For $t \geq 0^+$:

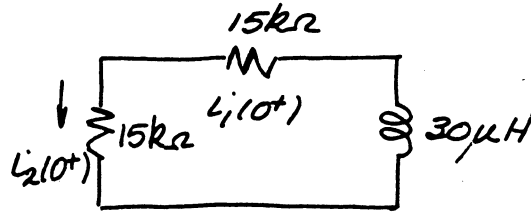

Since i_1 is the inductor branch current, it cannot change instantaneously, thus

$$i_1(0^+) = i_1(0^-) = 200 \mu\text{A}$$

For $t \geq 0^+$: $i_2 = -i_1$, hence $i_2(0^+) = -200 \mu\text{A}$

$$[c] \quad \tau = \frac{L}{R} = \frac{30 \times 10^{-6}}{30 \times 10^3} = 10^{-9} \text{ s}$$

$$\therefore i_1(t) = 200e^{-10^9 t} \mu\text{A}, \quad t \geq 0$$

$$[d] \quad i_2(t) = -200e^{-10^9 t} \mu\text{A}, \quad t \geq 0^+$$

[e] i_1 cannot change instantaneously with time. The switching operation forces

$$i_2(t) = -i_1(t) \quad \text{when} \quad t \geq 0^+$$

Therefore $i_2(0^-) \neq i_2(0^+)$

$$\text{P 8.10} \quad w(0) = \frac{1}{2}(10) \times 10^{-3}(25) = 125 \text{ mJ}$$

$$0.9w(0) = 112.5 \text{ mJ}$$

$$w(t) = \frac{1}{2}(10 \times 10^{-3})i(t)^2$$

$$i(t) = 5e^{-t/\tau} \text{ A}$$

$$\therefore w(t) = 5 \times 10^{-3}(25e^{-2t/\tau}) = 125e^{-2t/\tau} \text{ mJ}$$

$$w(10 \mu\text{s}) = 125e^{-20 \times 10^{-6}/\tau} \text{ mJ}$$


$$\therefore 125e^{-20 \times 10^{-6}/\tau} = 112.5; \quad e^{20 \times 10^{-6}/\tau} = \frac{1}{0.9} = \frac{10}{9}$$

$$\frac{20 \times 10^{-6}}{\tau} = \ln\left(\frac{10}{9}\right)$$


$$\tau = \frac{20 \times 10^{-6}}{\ln(10/9)} = \frac{L}{R}$$

$$\therefore R = \frac{10 \times 10^{-3} \ln(10/9)}{20 \times 10^{-6}} = 500 \ln(10/9) \cong 52.68 \Omega$$

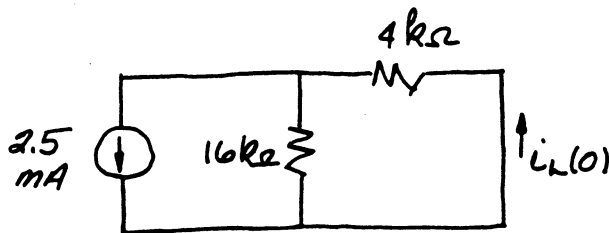P8.11 [a] For $t < 0$: $i_L(0) = (2.5)\frac{16}{20} = 2.0 \text{ mA}$



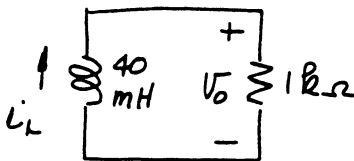For $t > 0$: $L_e = \frac{(120)(60)}{180} = 40 \text{ mH}$



$$\begin{aligned} i_L(0) &= 2 \text{ mA} \\ i_L &= 2e^{-t/\tau} \text{ mA}, \quad t \geq 0 \\ \tau &= L/R = 40 \mu\text{s} \\ 1/\tau &= 25,000 \end{aligned}$$

$$\begin{aligned} \therefore i_L &= 2e^{-25,000t} \text{ mA}, \quad t \geq 0 \\ \therefore v_o &= 2e^{-25,000t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

[b] $p_{1k\Omega} = \frac{v_o^2}{1000} = 4 \times 10^{-3} e^{-50,000t} \text{ W}$

$$\begin{aligned} w_{1k\Omega} &= \int_0^{t_o} 4 \times 10^{-3} e^{-50,000t} dt = 4 \times 10^{-3} \left[\frac{e^{-50,000t}}{-50,000} \right]_0^{t_o} \\ &= 80 \times 10^{-9} (1 - e^{-50,000t_o}) = 80(1 - e^{-50,000t_o}) \text{ nJ} \end{aligned}$$

$$w(0) = \frac{1}{2} (40 \times 10^{-3}) (4 \times 10^{-6}) = 80 \text{ nJ}$$

$$\% \text{ dissipated} = 100(1 - e^{-50,000t_o})$$

$$\therefore 1 - e^{-50,000t_o} = 0.98; \quad e^{-50,000t_o} = 0.02; \quad e^{50,000t_o} = 50$$


$$t_o = \frac{1}{50,000} \ln 50 = 20 \ln 50 \mu\text{s}$$

$$t_o = 78.24 \mu\text{s}$$

$$\therefore \text{Number of time constants} = t_o/\tau = 1.96$$

$$\therefore \text{Number of time constants} < 2$$

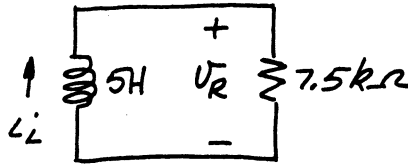P 8.12 [a] $L_e = 1.25 + \frac{60}{16} = 5.0 \text{ H}$



$$i_L = i_L(0)e^{-t/\tau}$$

$$i_L(0) = 2 \text{ A}$$

$$\frac{1}{\tau} = \frac{7500}{5} = 1500$$

$$i_L(t) = 2e^{-1500t} \text{ A}, \quad t \geq 0$$

$$v_R = 15,000e^{-1500t} \text{ V}, \quad t \geq 0^+$$

$$v_o = -3.75 \frac{di_L}{dt} = -3.75(-3000e^{-1500t})$$

$$v_o = 11,250e^{-1500t} \text{ V}, \quad t \geq 0^+$$

[b] $i_o = -\frac{1}{6} \int_0^t 11,250e^{-1500x} dx + 0 = -1875 \frac{e^{-1500x}}{-1500} \Big|_0^t$

$$i_o = 1.25e^{-1500t} - 1.25 \text{ A}, \quad t \geq 0$$

P 8.13 [a] $w_{\text{diss}} = \frac{1}{2} L_e [i_L(0)]^2 = \frac{1}{2} (5)(2)^2 = 10 \text{ J}$

Alternate solution:

$$w_{\text{diss}} = \int_0^\infty [2e^{-1500t}]^2 7500 dt = 30,000 \int_0^\infty e^{-3000t} dt = -10(0 - 1) = 10 \text{ J}$$


[b] $w_{\text{trapped}} = \frac{1}{2} (10)(1.25)^2 + \frac{1}{2} (6)(1.25)^2 = (5 + 3)(1.25)^2 = 12.5 \text{ J}$

Alternate solution:


$$w(0) = \frac{1}{2} (10)(4) + \frac{1}{2} (1.25)(4) = 20 + 2.5 = 22.50 \text{ J}$$

$$w_{\text{trapped}} = w(0) - w_{\text{diss}} = 22.5 - 10 = 12.5 \text{ J}$$

P 8.14 For $t < 0$:

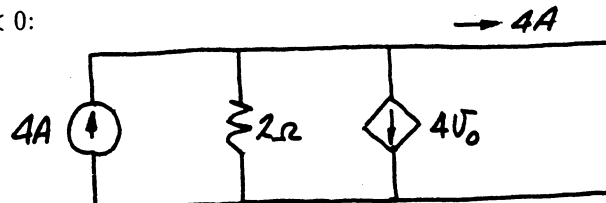

For $t > 0$:

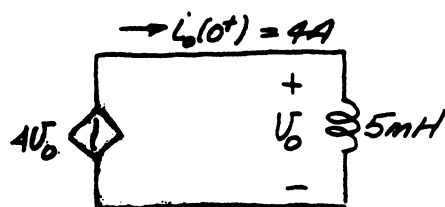

The Thévenin resistance seen by the 5-mH inductor is

$$R_{Th} = \frac{v_o}{4v_o} = 0.25 \Omega$$

$$\tau = \frac{L}{R} = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$

$$\therefore v_o(0^+) = -4(0.25) = -1 \text{ V}$$


$$\therefore v_o = -e^{-50t} \text{ V}, \quad t \geq 0^+$$

Alternate solution:

$$i_o = 4e^{-50t} \text{ A}, \quad t \geq 0$$


$$v_o = L \frac{di_o}{dt} = (5 \times 10^{-3})(-200)e^{-50t} = -e^{-50t} \text{ V}, \quad t \geq 0^+$$

P8.15 [a] For $t < 0$:

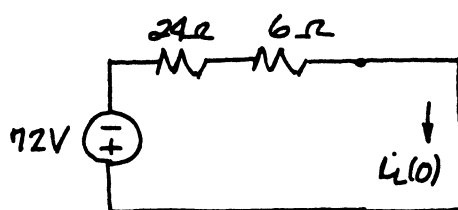


$$i_L(0) = \frac{-72}{30} = -2.4 \text{ A}$$

For $t > 0$:

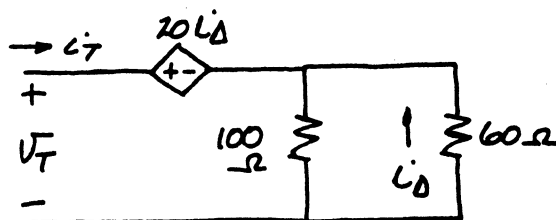

$$v_T = 20i_\Delta + 37.5i_T = 20\left(-\frac{100}{160}i_T\right) + 37.5i_T = (-12.5 + 37.5)i_T = 25i_T$$

$$\frac{v_T}{i_T} = 25 \Omega$$

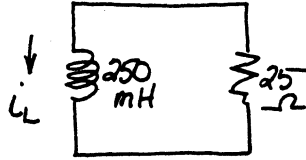

$$\frac{1}{\tau} = \frac{25}{250} \times 10^3 = 100$$

$$i_L(0) = -2.4 \text{ A}$$

$$i_L(t) = -2.4e^{-100t} \text{ A}, \quad t \geq 0$$

$$[b] \quad v_L = (250 \times 10^{-3}) \frac{d}{dt}(-2.4e^{-100t})$$

$$v_L = 60e^{-100t} \text{ V}, \quad t \geq 0^+$$

$$[c] \quad i_\Delta = 0.625i_L = -1.5e^{-100t} \text{ A}, \quad t \geq 0^+$$

$$\text{P 8.16} \quad p_{\text{diss}} = 37.5i_L^2 = 216e^{-200t} \text{ W}$$


$$w_{\text{diss}} = \int_0^\infty 216e^{-200t} dt = 216 \left[\frac{e^{-200t}}{-200} \right]_0^\infty = 1080 \text{ mJ}$$

$$p_{20i_\Delta} = -(20i_\Delta)i_L = -72e^{-200t}$$


$$w_{20i_\Delta} = -72 \left[\frac{e^{-200t}}{-200} \right]_0^\infty = -360 \text{ mJ}; \quad \therefore \text{dependent source delivers 360 mJ}$$

$$\% \text{ supplied by dependent source} = \frac{360}{1080} \times 100 = 33.33\%$$


$$\text{P 8.17} \quad [a] \quad t < 0:$$

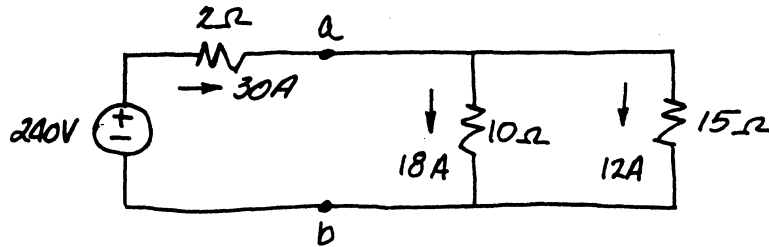

$$t = 0^+:$$

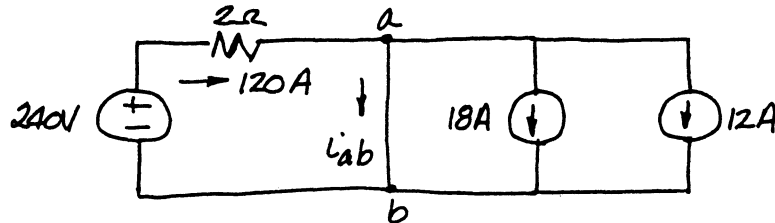


$$120 = i_{ab} + 18 + 12, \quad i_{ab} = 90 \text{ A}, \quad t = 0^+$$

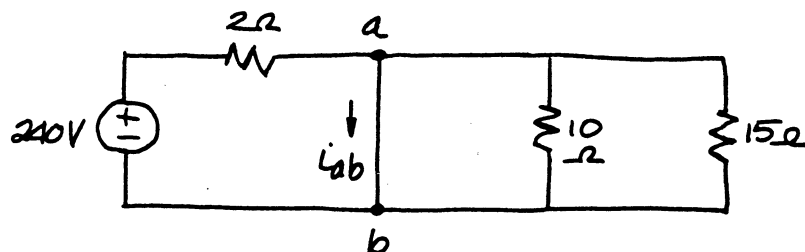[b] At $t = \infty$:

$$i_{ab} = 240/2 = 120 \text{ A}, \quad t = \infty$$

[c]

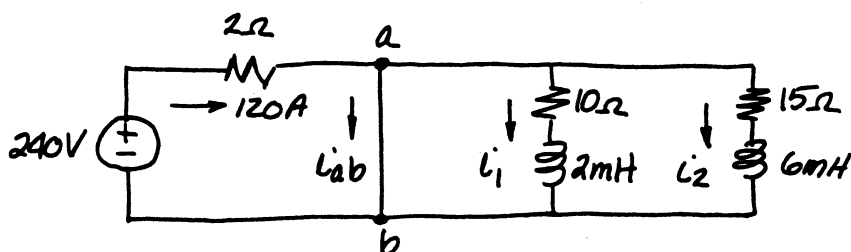

$$i_1(0) = 18, \quad \tau_1 = \frac{2}{10} \times 10^{-3} = 0.2 \text{ ms}$$

$$i_2(0) = 12, \quad \tau_2 = \frac{6}{15} \times 10^{-3} = 0.4 \text{ ms}$$

$$i_1(t) = 18e^{-5000t} \text{ A}, \quad t \geq 0$$

$$i_2(t) = 12e^{-2500t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 120 - 18e^{-5000t} - 12e^{-2500t} \text{ A}, \quad t \geq 0$$

$$120 - 18e^{-5000t} - 12e^{-2500t} = 114$$

$$6 = 18e^{-5000t} + 12e^{-2500t}$$

$$e^{-2500t} = x, \quad \therefore e^{-5000t} = x^2$$

$$\therefore 6 = 18x^2 + 12x$$

$$x^2 + \frac{2}{3}x - \frac{6}{18} = 0$$

$$x = -\frac{1}{3} \pm \sqrt{\frac{1}{9} + \frac{3}{9}}; \quad x = -\frac{1}{3} \pm \frac{2}{3} = \frac{1}{3}$$

$$e^{-2500t} = \frac{1}{3}; \quad e^{2500t} = 3$$

$$t = \frac{1}{2500} \ln 3 = 400 \ln 3 \mu\text{s}; \quad t = 439.44 \mu\text{s}$$

P 8.18 [a] $R = \frac{v}{i} = 8000 \Omega = 8 \text{ k}\Omega$

[b] $\frac{1}{\tau} = \frac{1}{RC} = 500; \quad C = \frac{1}{(500)(8000)} = 0.25 \mu\text{F}$

$$[c] \quad \tau = \frac{1}{500} = 2 \text{ ms}$$

$$[d] \quad w(0) = \frac{1}{2}(0.25 \times 10^{-6})(72)^2 = 648 \mu\text{J}$$

$$[e] \quad W_{\text{diss}} = \int_0^{t_o} \frac{v^2}{R} dt = \int_0^{t_o} \frac{(72)^2 e^{-1000t}}{(8000)} dt = 648 \times 10^{-3} \frac{e^{-1000t}}{-1000} \Big|_0^{t_o}$$

$$= 648 \times 10^{-6}(1 - e^{-1000t_o}) = 648(1 - e^{-1000t_o}) \mu\text{J}$$

$$\therefore \% \text{ dissipated} = 100(1 - e^{-1000t_o})$$

$$\therefore 100(1 - e^{-1000t_o}) = 68$$

$$e^{-1000t_o} = 0.32; \quad e^{1000t_o} = 3.125$$

$$t_o = \frac{1}{1000} \ln 3.125; \quad t_o \cong 1.14 \text{ ms}$$

P 8.19 [a] $v_c(0) = (40)10^{-3} \frac{(2.7)(3.3)}{6} \times 10^3 = 59.4 \text{ V}$

$$\tau = \left[\frac{(3)(6)}{9} \times 10^3 \right] (0.5 \times 10^{-6}) = 1 \text{ ms}$$

$$v_c(t) = 59.4 e^{-1000t} \text{ V}, \quad t \geq 0$$

$$i_o(t) = \left(\frac{59.4}{6} \times 10^{-3} \right) e^{-1000t}$$

$$i_o(t) = 9.90 e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

[b] $W_{\text{diss}} = \int_0^{t_o} \frac{(59.4)^2}{3000} e^{-2000t} dt$


$$W_{\text{diss}} = 1176.12 \times 10^{-3} \left[\frac{e^{-2000t}}{-2000} \Big|_0^{t_o} \right] = 588.06 \times 10^{-6} (1 - e^{-2000t_o})$$

$$w(500 \mu\text{s}) = (588.06)(1 - e^{-1}) \mu\text{J} = 371.72 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.5 \times 10^{-6})(59.4)^2 = 882.09 \mu\text{J}$$

$$\% \text{ dissipated} = \frac{371.72}{882.09} \times 100 = 42.14\%$$

P 8.20 [a] $t < 0$:

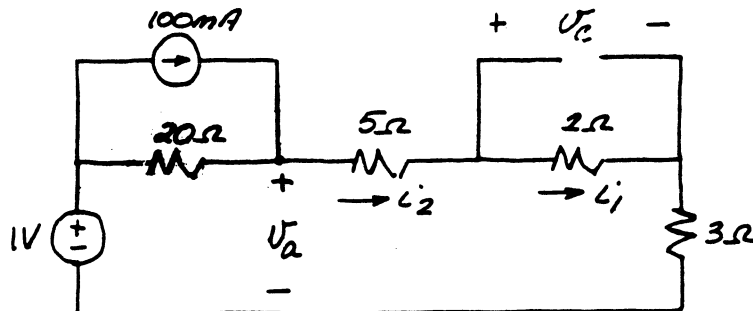


$$\frac{v_a - 1}{20} - 0.1 + \frac{v_a}{10} = 0$$

$$v_a - 1 - 2 + 2v_a = 0, \quad 3v_a = 3, \quad v_a = 1 \text{ V}$$

$$\therefore i_1(0^-) = i_2(0^-) = \frac{1}{10} = 0.1 \text{ A} = 100 \text{ mA}$$

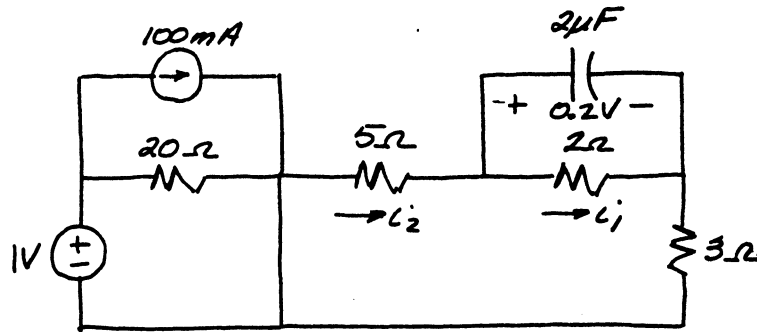- [b] First note that $v_c(0^-) = v_c(0^+) = 2i_1 = 0.2 \text{ V}$; then for $t = 0^+$



$$i_1(0^+) = \frac{0.2}{2} = 0.1 = 100 \text{ mA}; \quad i_2(0^+) = \frac{-0.2}{8} = -25 \text{ mA}$$

- [c] The voltage across the capacitor cannot change instantaneously; therefore the current in the resistor across the terminals of the capacitor cannot change between $t = 0^-$ and $t = 0^+$.
- [d] After the switch closes, i_2 is governed by the capacitor voltage since closing the switch places i_2 in a branch parallel to the $2\text{-}\mu\text{F}$ capacitor. Thus between $t = 0^-$ and $t = 0^+$ i_2 changes instantaneously from 100 mA to -25 mA .
- [e] For $t > 0^+$ the time constant of the circuit is $R_e C$ where

$$R_e = (2)(8)/10 = 1.6 \Omega$$


$$C = 2 \mu\text{F}$$

$$\therefore \tau = 3.2 \mu\text{s} \quad \text{and} \quad \frac{1}{\tau} = 312,500$$

$$\therefore i_1(t) = 100e^{-312,500t} \text{ mA}, \quad t \geq 0$$


[f] $i_2(t) = -25e^{-312,500t} \text{ mA}, \quad t \geq 0^+$

P8.21 [a] For $t < 0$:

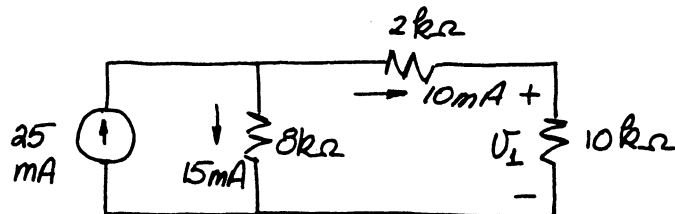


$$\therefore v_o(0) = 120 \text{ V}; \quad v_1(0) = 100 \text{ V}$$

For $t > 0$:

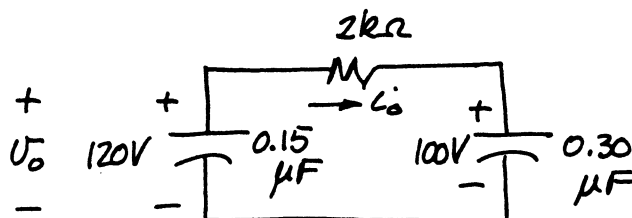
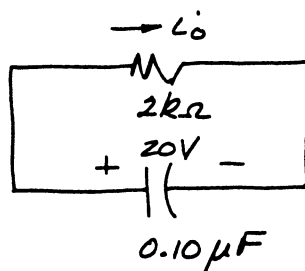
$$\frac{1}{C_e} = \frac{1}{0.15} + \frac{1}{0.30} = \frac{1}{0.10}; \quad C_e = 0.10 \mu\text{F}$$



$$i_o(0^+) = \frac{20}{2} = 10 \text{ mA}$$

$$\tau = (2000)(0.10)10^{-6} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$

$$i_o(t) = 10e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

$$\begin{aligned} \text{[b]} \quad v_o &= \frac{-10^6}{0.15} \int_0^t (10 \times 10^{-3}) e^{-5000x} dx + 120 = \frac{-10,000}{0.15} \left[\frac{e^{-5000x}}{-5000} \right]_0^t + 120 \\ &= \frac{40}{3} e^{-5000t} - \frac{40}{3} + 120 \\ v_o &= \frac{40}{3} e^{-5000t} + \frac{320}{3} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\text{[c]} \quad v_o(\infty) = \frac{320}{3} \text{ V}; \quad \therefore v_1(\infty) = \frac{320}{3} \text{ V}$$


$$w_{\text{trapped}} = \left[\frac{1}{2}(0.15) \left(\frac{320}{3} \right)^2 + \frac{1}{2}(0.30) \left(\frac{320}{3} \right)^2 \right] \mu\text{J} = 2560 \mu\text{J}$$

Check:


$$w(0) = \left[\frac{1}{2}(0.15)(120)^2 + \frac{1}{2}(0.30)(100)^2 \right] \mu\text{J} = 2580 \mu\text{J}$$

$$\begin{aligned}
 w_{\text{diss}} &= \int_0^{\infty} (10 \times 10^{-3})^2 e^{-10,000t} (2000) dt \\
 &= 2000 \times 10^{-4} \left[\frac{e^{-10,000t}}{-10,000} \right]_0^{\infty} = 20 \mu\text{J} \\
 w(0) - w_{\text{diss}} &= 2560 \mu\text{J} = w_{\text{trapped}}
 \end{aligned}$$

P8.22 [a] $t < 0$:

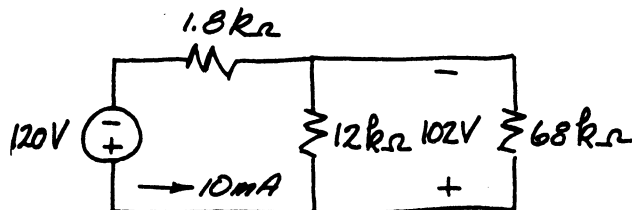

$t > 0$:

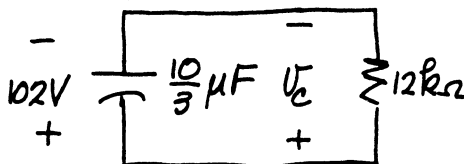

$$\begin{aligned}
 \tau &= RC \\
 &= 12 \times 10^3 \times \frac{10}{3} \times 10^{-6} \\
 &= 40 \text{ ms} \\
 1/\tau &= 25 \\
 v_C &= 102e^{-25t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$W_{\text{diss}} = \int_0^{t_0} \frac{(102)^2 e^{-50t}}{12,000} dt = \frac{10,404}{12,000} \left[\frac{e^{-50t}}{-50} \right]_0^{t_0} = 17.34 \times 10^{-3} (1 - e^{-50t_0})$$

$$W_{\text{diss}}(12 \text{ ms}) = (17.34)(1 - e^{-0.6}) \times 10^{-3} = 7.82 \text{ mJ}$$


[b] % dissipated = $100(1 - e^{-50t_0}) = 75$

$$\therefore 1 - e^{-50t_0} = 0.75$$


$$e^{-50t_0} = 0.25; \quad e^{50t_0} = 4$$

$$t_0 = \frac{1}{50} \ln 4 = 20 \ln 4 \text{ ms}; \quad t_0 = 27.73 \text{ ms}$$

P8.23 [a] $t < 0$:

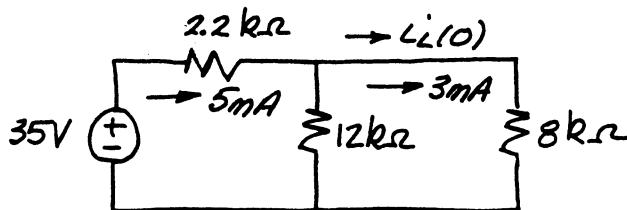

$t > 0$:

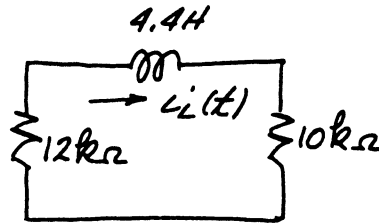

$$\begin{aligned}\tau &= L/R = 4.4/22 \\ &= 0.2 \text{ ms} \\ 1/\tau &= 5000 \\ i_L(t) &= 3e^{-5000t} \text{ mA}, \\ &t \geq 0\end{aligned}$$

$$w(0) = \frac{1}{2}(4.4)(3 \times 10^{-3})^2 = 19.8 \mu\text{J}$$

$$w_{10k} = \int_0^{t_o} (9 \times 10^{-6} e^{-10,000t})(10,000) dt = 9(1 - e^{-10,000t_o}) \mu\text{J}$$

$$\therefore 9(1 - e^{-10,000t_o}) = 0.2(19.8)$$

$$1 - e^{-10,000t_o} = 0.44$$

$$e^{10,000t_o} = \frac{1}{0.56} = \frac{25}{14}$$

$$t_o = 100 \ln \left(\frac{25}{14} \right) \mu\text{s} = 57.98 \mu\text{s}$$


$$\begin{aligned}[\text{b}] \quad W_{\text{diss}}(\text{total}) &= \int_0^{t_o} (9 \times 10^{-6} e^{-10,000t})(22 \times 10^3) dt \\ &= 198 \times 10^{-3} \left[\frac{e^{-10,000t}}{-10^4} \right]_0^{t_o} = 19.8(1 - e^{-10,000t_o}) \mu\text{J}\end{aligned}$$

$$W_{\text{diss}}(\text{total})[57.98 \mu\text{s}] = 8.712 \mu\text{J}$$

$$\% \text{ dissipated @ } 57.98 \mu\text{s} = \left(\frac{8.712}{19.8} \right) 100 = 44$$

P 8.24 For $t < 0$, i_o is zero; therefore the capacitor charges to 15 V, positive at the upper terminal.

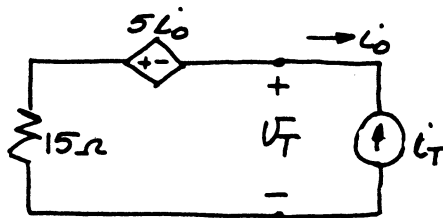For $t > 0$ the Thévenin resistance seen from the terminals of the capacitor is 20Ω , i.e.,




Now $i_o = -i_T$, therefore

$$v_T = 15i_T - 5(-i_T) = 20i_T, \quad R_{\text{Th}} = \frac{v_T}{i_T} = 20 \Omega$$

Therefore the time constant is $\tau = (2 \times 10^{-6})(20) = 40 \mu\text{s}$ and $\frac{1}{\tau} = 25,000$.


$t > 0^+$:

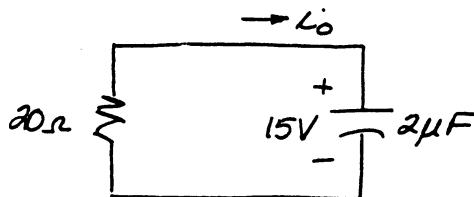

$$i_o(0^+) = -\frac{15}{20} = -0.75 = -750 \text{ mA}$$

$$\therefore i_o(t) = -750e^{-25,000t} \text{ mA}, \quad t \geq 0^+$$

P 8.25 [a]

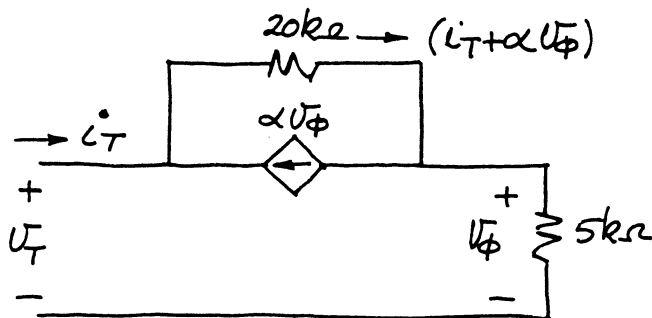

$$v_T = 20 \times 10^3(i_T + \alpha v_\phi) + 5000i_T = 25,000i_T + 20 \times 10^3(\alpha)(5000i_T)$$

$$\frac{v_T}{i_T} = R_{Th} = 25,000 + 100 \times 10^6 \alpha$$

$$\tau = R_{Th}C = 40 \times 10^{-3} = R_{Th}(0.8 \times 10^{-6})$$


$$\therefore R_{Th} = 50 \text{ k}\Omega$$

$$\therefore 25 \times 10^3 + 100 \times 10^6 \alpha = 50 \times 10^3$$


$$\therefore \alpha = \frac{25,000}{100 \times 10^6} = 0.25 \times 10^{-3}$$

$$\alpha = 250 \times 10^{-6} \text{ A/V}$$

[b] $t < 0$:

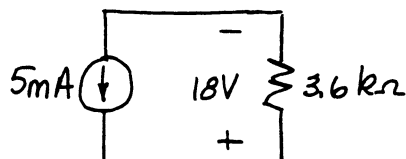

$t > 0$:

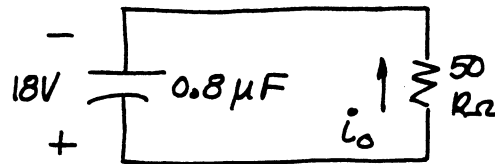

$$\tau = 40 \text{ ms}$$


$$1/\tau = 25$$

$$i_o(0^+) = 0.36 \text{ mA}$$

$$i_o = 0.36e^{-25t} \text{ mA}, \quad t \geq 0^+$$

$$v_\phi = -5000i_o = -1.8e^{-25t} \text{ V}, \quad t \geq 0^+$$

P8.26 [a]

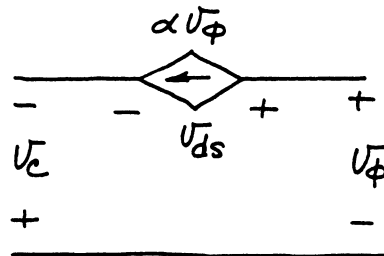

$$v_c = 18e^{-25t} \text{ V}, \quad v_\phi = -1.8e^{-25t} \text{ V}, \quad v_{ds} = v_c + v_\phi = 16.2e^{-25t} \text{ V}$$

$$i_{ds} = \alpha v_\phi = (250 \times 10^{-6})(-1.8e^{-25t}) = -450e^{-25t} \text{ μA}$$

$$p_{ds} = v_{ds} i_{ds} = -7290e^{-50t} \text{ μW}$$

$$w_{ds} = \int_0^\infty -7290 \times 10^{-6} e^{-50t} dt = -145.80 \text{ μJ}$$

$\therefore$ dependent source delivers 145.80 μJ

$$[b] \quad w_{5k\Omega} = \int_0^\infty [0.36 \times 10^{-3} e^{-25t}]^2 5000 dt = 648 \times 10^{-6} \int_0^\infty e^{-50t} dt = 12.96 \text{ μJ}$$



$$w_{20k\Omega} = \int_0^\infty \frac{(16.2e^{-25t})^2}{20,000} dt = 13,122 \times 10^{-6} \int_0^\infty e^{-50t} dt = 262.44 \text{ μJ}$$

$$w(0) = \frac{1}{2}(0.8 \times 10^{-6})(18)^2 = 129.60 \text{ μJ}$$

$$\sum w_{\text{diss}} = 12.96 + 262.44 = 275.40 \text{ μJ}$$

$$\sum w_{\text{del}} = 129.60 + 145.80 = 275.40 \text{ μJ}$$

$$\therefore \sum w_{\text{diss}} = \sum w_{\text{del}}$$

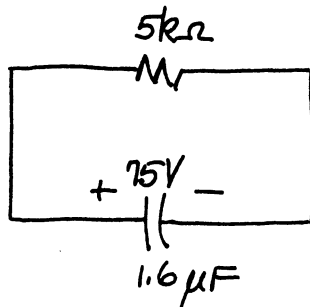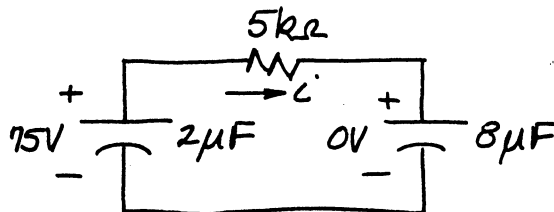P 8.27 [a] $t > 0$:

$$\tau = 8 \times 10^{-3} = 8 \text{ ms}$$

$$1/\tau = 125$$

$$i(0^+) = \frac{75}{5} \times 10^{-3} = 15 \text{ mA}$$

$$i(t) = 15e^{-125t} \text{ mA}, \quad t \geq 0^+$$

$$\begin{aligned} v_1 &= -\frac{10^6}{2} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 75 \\ &= 60(e^{-125t} - 1) + 75 = 60e^{-125t} + 15 \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} v_2 &= \frac{10^6}{8} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 0 \\ &= -15(e^{-125t} - 1) = -15e^{-125t} + 15 \text{ V}, \quad t \geq 0 \end{aligned}$$

$$[b] \quad w(0) = \frac{1}{2}(2 \times 10^{-6})(75)^2 = 5625 \mu\text{J}$$


$$[c] \quad W_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(15)^2 + \frac{1}{2}(8 \times 10^{-6})(15)^2 = 225[10^{-6} + 4 \times 10^{-6}]$$

$$W_{\text{trapped}} = 1125 \mu\text{J}$$

$$W_{\text{diss}} = w(0) - W_{\text{trapped}} = 4500 \mu\text{J}$$

$$\begin{aligned} \text{Check: } W_{\text{diss}} &= \int_0^\infty 225 \times 10^{-6} e^{-250t} (5000) dt \\ &= 1125 \times 10^{-3} \left. \frac{e^{-250t}}{-250} \right|_0^\infty = 4500 \mu\text{J} \end{aligned}$$
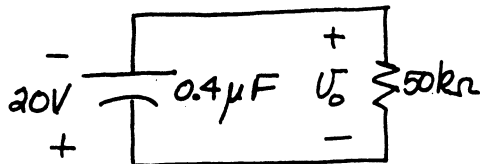
$$\text{P 8.28 [a]} \quad C_e = \frac{(0.6)(1.2)}{1.8} = 0.4 \mu\text{F}$$



$$\tau = (0.4)(50) \times 10^{-3}$$

$$= 20 \text{ ms}$$

$$1/\tau = 50$$

$$v_o = -20e^{-50t} \text{ V}, \quad t \geq 0$$

$$[b] \quad w_{\text{diss}} = \frac{1}{2}(0.4)(400) = 80 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.4)(30)^2 + \frac{1}{2}(0.2)(30^2) + \frac{1}{2}(1.2)(10)^2 = 330 \mu\text{J}$$

$$\therefore \% \text{ dissipated} = \frac{80}{330} \times 100 = 24.24\%$$

$$[c] \quad v_1(t) = \frac{-10^6}{1.2} \int_0^t \frac{-20}{50 \times 10^3} e^{-50x} dx + 10 = \frac{(20)(1000)}{60} \left[\frac{e^{-50x}}{-50} \right]_0^t + 10$$

$$= \frac{-20}{3} e^{-50t} + \frac{20}{3} + 10 = -\frac{20}{3} e^{-50t} + \frac{50}{3} \text{ V}, \quad t \geq 0$$

$$[d] \quad v_2 = \frac{-10^6}{0.6} \int_0^t \frac{-20e^{-50x}}{50 \times 10^3} dx - 30 = -\frac{40}{3}(e^{-50t} - 1) - 30$$

$$= \frac{-40}{3} e^{-50t} - \frac{50}{3} \text{ V}, \quad t \geq 0$$


Note: $v_1 + v_2 = v_o$ as it should

$$[e] \quad w_{\text{trapped}} = \frac{1}{2}(1.2) \left(\frac{50}{3} \right)^2 + \frac{1}{2}(0.6) \left(\frac{50}{3} \right)^2 = 250 \mu\text{J}$$

$$\text{Check: } w_{\text{trapped}} + w_{\text{diss}} = w(0)$$

$$250 + 80 = 330 \quad (\text{ok})$$

P 8.29 [a]

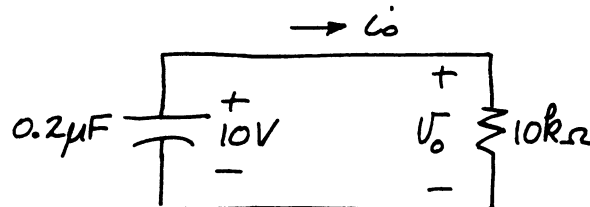

$$\tau = 2 \text{ ms}$$

$$1/\tau = 500$$

$$v_o = 10e^{-500t} \text{ V}, \quad t \geq 0$$

$$i_o = e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{24\text{k}\Omega} = e^{-500t} \left(\frac{16}{40} \right) = 0.40e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{24\text{k}\Omega} = (0.16 \times 10^{-6} e^{-1000t})(24,000) = 3840 \times 10^{-6} e^{-1000t} \text{ W}$$


$$w_{24\text{k}\Omega} = \int_0^\infty 3840 \times 10^{-6} e^{-1000t} dt = -3.84 \times 10^{-6}(0 - 1) = 3.84 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.25)(1600) + \frac{1}{2}(1)(2500) \mu\text{J} = 1450 \mu\text{J}$$

$$\% \text{ diss } (24 \text{ k}\Omega) = \frac{384}{1450} = 0.26\%$$

$$\begin{aligned}
 \text{[b]} \quad p_{400\Omega} &= 400 \times 10^{-6} e^{-1000t} \text{ W} \\
 w_{400\Omega} &= \int_0^{\infty} p_{400} dt = 0.40 \mu\text{J} \\
 \% \text{ diss}(400\Omega) &= \frac{40}{1450} = 0.03\% \\
 p_{16k\Omega} &= (0.36 \times 10^{-6} e^{-1000t})(16,000) = 5760 \times 10^{-6} e^{-1000t} \text{ W} \\
 w_{16k\Omega} &= \int_0^{\infty} 5760 \times 10^{-6} e^{-1000t} dt = 5.76 \mu\text{J} \\
 \% \text{ diss}(16k\Omega) &= 0.40 \\
 \text{[c]} \quad \sum w_{\text{diss}} &= 3.84 + 5.76 + 0.40 = 10 \mu\text{J} \\
 w_{\text{trapped}} &= w(0) - \sum w_{\text{diss}} = 1450 - 10 = 1440 \mu\text{J} \\
 \% \text{ trapped} &= \frac{1440}{1450} \times 100 = 99.31\% \\
 \text{Check: } 0.26 + 0.03 + 0.40 + 99.31 &= 100\%
 \end{aligned}$$

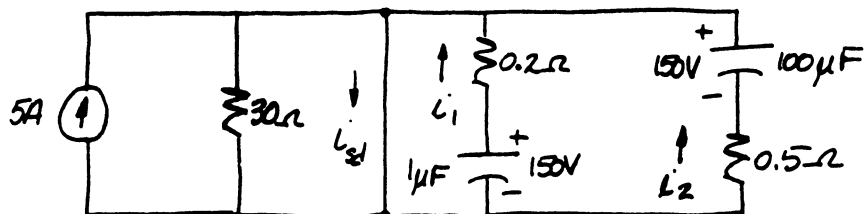P 8.30 [a] At $t = 0^-$ the voltage on each capacitor will be 150 V (5×30), positive at the upper terminal. Hence at $t \geq 0^+$ we have



$$\therefore i_{sd}(0^+) = 5 + \frac{150}{0.2} + \frac{150}{0.5} = 1055 \text{ A}$$

At $t = \infty$, both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 5 \text{ A}$$

$$\begin{aligned}
 \text{[b]} \quad i_{sd}(t) &= 5 + i_1(t) + i_2(t) \\
 \tau_1 &= (0.2)(1) \times 10^{-6} = 0.2 \mu\text{s} \\
 \tau_2 &= (0.5)(100 \times 10^{-6}) = 50 \mu\text{s} \\
 \therefore i_1(t) &= 750 e^{-5 \times 10^6 t} \text{ A}, \quad t \geq 0^+ \\
 i_2(t) &= 300 e^{-20,000 t} \text{ A}, \quad t \geq 0 \\
 \therefore i_{sd} &= 5 + 750 e^{-5 \times 10^6 t} + 300 e^{-20,000 t} \text{ A}, \quad t \geq 0^+
 \end{aligned}$$

P8.31 [a] $v = L \frac{di}{dt} = L(10,000)e^{-400t}$

$$\therefore 10^4 L = 100$$

$$L = 10 \text{ mH}$$

$$\frac{1}{\tau} = \frac{R}{L} = 400, \quad \therefore R = 4 \Omega$$

$$i(\infty) = 25 = \frac{V_s}{R}, \quad \therefore V_s = 25R = 100 \text{ V}$$

[b] $w(\infty) = \frac{1}{2}(10 \times 10^{-3})(25)^2 = 3125 \text{ mJ}$

$$w(t) = \frac{1}{2}(10 \times 10^{-3})[625 - 1250e^{-400t} + 625e^{-800t}]$$

$$= 3125 - 6250e^{-400t} + 3125e^{-800t} \text{ mJ}$$

$$\therefore 3125 - 6250e^{-400t} + 3125e^{-800t} = 0.25(3125)$$

$$1 - 2e^{-400t} + e^{-800t} = 0.25$$

$$x = e^{-400t}$$

$$1 - 2x + x^2 = 0.25$$

$$x^2 - 2x + 0.75 = 0$$

$$x = 1 \pm \sqrt{1 - 0.75} = 1 \pm 0.5$$

$$x_1 = 1.5, \quad x_2 = 0.5$$

Only x_2 has physical significance, i.e., $t > 0$.

$$e^{-400t} = 0.5; \quad e^{400t} = 2$$


$$t = 2.5 \ln 2 \text{ ms} \cong 1.73 \text{ ms}$$

A better way:

$$w = \frac{1}{2}Li^2 = \frac{1}{2}L(25)^2(1 - e^{-400t})^2 = w(\infty)(1 - e^{-400t})^2$$


$$\therefore (1 - e^{-400t})^2 = 0.25; \quad 1 - e^{-400t} = 0.5; \quad t \cong 1.73 \text{ ms}$$

P8.32 [a] $t < 0$:

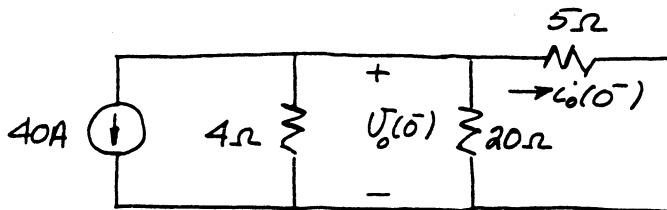

$$\begin{aligned}\frac{v_o(0^-)}{4} + \frac{v_o(0^-)}{20} + \frac{v_o(0^-)}{5} &= -40 \\ 10v_o(0^-) &= -800; \quad v_o(0^-) = -80 \text{ V} \\ \therefore i_o(0^-) &= -80/5 = -16 \text{ A}\end{aligned}$$

$t > 0$:

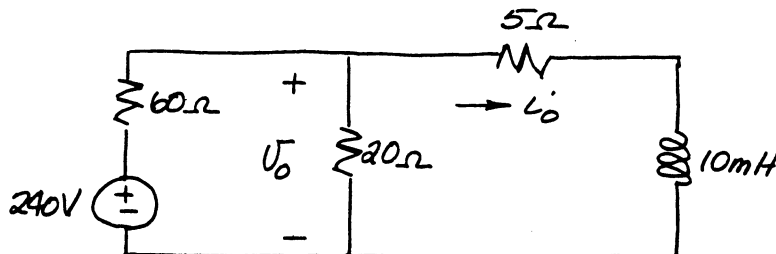


$$\begin{aligned}\frac{v_o}{20} + \frac{v_o - 240}{60} + \frac{v_o}{5} &= 0, \quad t = \infty \\ \therefore 16v_o &= 240, \quad v_o(\infty) = 15 \text{ V} \\ i_o(\infty) &= 15/5 = 3 \text{ A}\end{aligned}$$

Resistance seen from the terminals of the 10-mH inductor:

$$\begin{aligned}R_{Th} &= 5 + \frac{(60)(20)}{80} = 20 \Omega \\ \therefore \tau &= \frac{10}{20} \times 10^{-3} = 0.5 \text{ ms} = 500 \mu\text{s}; \quad 1/\tau = 2000 \\ \therefore i_o(t) &= 3 + (-16 - 3)e^{-2000t} = 3 - 19e^{-2000t} \text{ A}, \quad t \geq 0\end{aligned}$$


$$\begin{aligned}[b] \quad v_o &= 5i_o(t) + 10 \times 10^{-3} \frac{di_o}{dt}(t) = 15 - 95e^{-2000t} + 10 \times 10^{-3}(38,000)e^{-2000t} \\ &= 15 - 95e^{-2000t} + 380e^{-2000t} = 15 + 285e^{-2000t} \text{ V}, \quad t \geq 0\end{aligned}$$

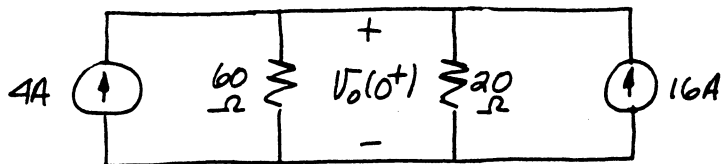Check: $v_o(0^+) = 15 + 285 = 300 \text{ V}$; at $t = 0^+$ the circuit is




$$\begin{aligned}\frac{v_o(0^+)}{60} + \frac{v_o(0^+)}{20} &= 20 \\ 4v_o(0^+) &= 1200 \\ v_o(0^+) &= 300 \text{ V (Checks)}\end{aligned}$$

P 8.33 [a] $t < 0$:

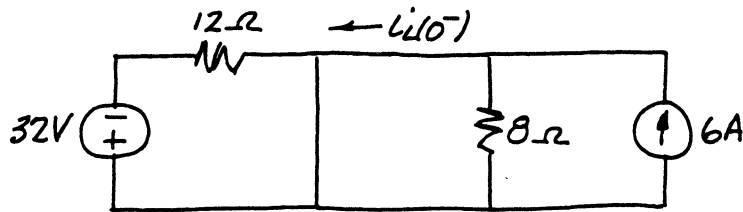

$$i_L(0^-) = 6 \text{ A}$$

$t > 0$:

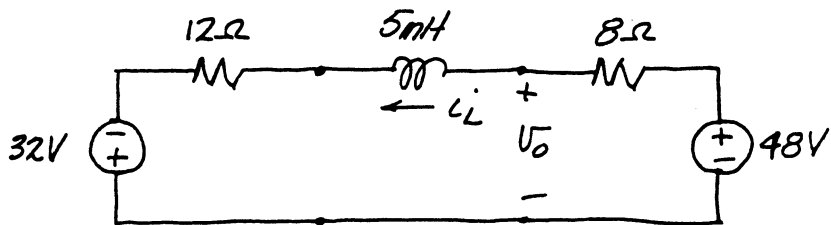

$$i_L(\infty) = \frac{80}{20} = 4 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{20} = 0.25 \times 10^{-3} = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L = 4 + (6 - 4)e^{-4000t} \text{ A} = 4 + 2e^{-4000t} \text{ A}, \quad t \geq 0$$

$$v_o = 48 - 8i_L = 48 - 32 - 16e^{-4000t} = 16 - 16e^{-4000t} \text{ V}, \quad t \geq 0^+$$


[b] $v_L = L \frac{di_L}{dt} = (5 \times 10^{-3})(-8000e^{-4000t}) = -40e^{-4000t} \text{ V}, \quad t \geq 0^+$

$$\therefore v_L(0^+) = -40 \text{ V}$$

$$v_o(0^+) = 0 \text{ V}$$

P 8.34 $i_o(0^-) = i_o(0^+) = 10 \text{ A}$

$t > 0$:

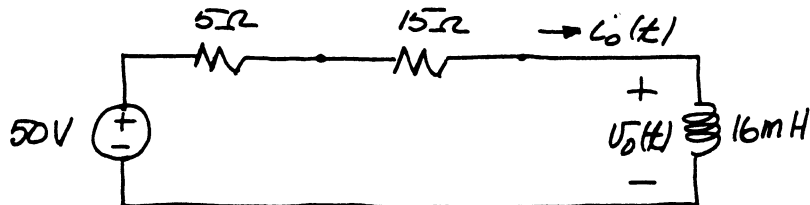

$$i_o(\infty) = \frac{50}{20} = 2.5 \text{ A}$$

$$\tau = \frac{16}{20} \times 10^{-3} = 0.8 \text{ ms} = 800 \mu\text{s}; \quad \frac{1}{\tau} = \frac{1000}{0.8} = 1250 \text{ nepers/s}$$

$$i_o = 2.5 + (10 - 2.5)e^{-1250t}$$

$$i_o(t) = 2.5 + 7.5e^{-1250t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o(t)}{dt} = 16 \times 10^{-3}(-9375)e^{-1250t} = -150e^{-1250t} \text{ V}, \quad t \geq 0$$

P 8.35 [a] $v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-(R_1 + R_2)/L t} \text{ V}, \quad t \geq 0$$

[b] $v_o = -12(20)e^{-(20/8) \times 10^3 t} = -240e^{-2500t} \text{ V}, \quad t \geq 0$

[c] $v_o(0^+) \rightarrow \infty$, and the duration of $v_o(t) \rightarrow \text{zero}$

[d] $v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$

$$\text{Therefore } i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-(R_1 + R_2)/L t}$$


$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-(R_1 + R_2)/L t}$$

$$\text{Therefore } v_{sw} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-(R_1 + R_2)/L t}, \quad t \geq 0$$

[e] $|v_{sw}(0^+)| \rightarrow \infty; \quad \text{duration} \rightarrow 0$


P 8.36 Opening the inductive circuit causes a very large voltage to be induced across the inductor L . This voltage also appears across the switch (part [e] of Problem 8.35) causing the switch to arc over. At the same time, the large voltage across L damages the meter movement.

P 8.37 $t < 0$:

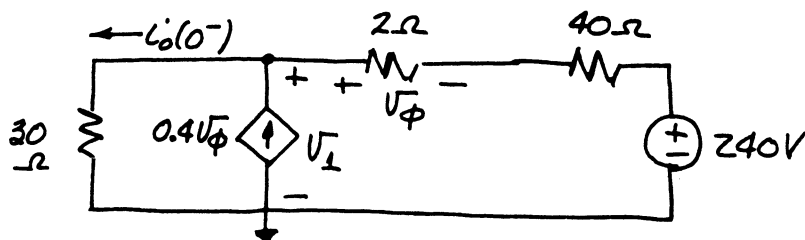


$$\begin{aligned} \frac{v_1}{30} - 0.4v_\phi + \frac{v_1 - 240}{42} &= 0 \\ v_\phi &= \left(\frac{v_1 - 240}{42} \right) (2) = \frac{v_1 - 240}{21} \\ \frac{v_1}{30} - 0.4 \left(\frac{v_1 - 240}{21} \right) + \frac{v_1 - 240}{42} &= 0 \\ 1.4v_1 - 0.8(v_1 - 240) + (v_1 - 240) &= 0 \\ 1.4v_1 + 0.2(v_1 - 240) &= 0 \\ 1.6v_1 = 48; \quad v_1 &= 30 \text{ V} \\ i_o(0^-) = \frac{30}{30} &= 1 \text{ A} = i_o(0^+) \end{aligned}$$

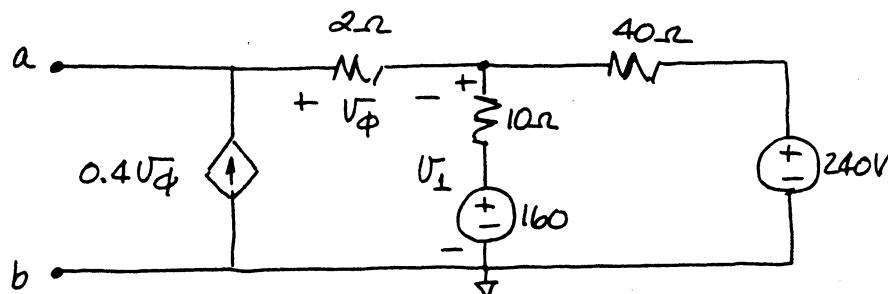For $t < 0$: First find the Thévenin equivalent with respect to the terminals a, b.



$$\begin{aligned} -0.4v_\phi + \frac{v_{ab} - v_1}{2} &= 0 \\ v_{ab} &= v_\phi + v_1, \quad v_\phi = v_{ab} - v_1 \\ \therefore -0.8(v_{ab} - v_1) + (v_{ab} - v_1) &= 0 \\ 0.2(v_{ab} - v_1) &= 0; \quad \therefore v_{ab} = v_1, \quad v_\phi = 0 \\ \therefore \frac{v_1 - 160}{10} + \frac{v_1 - 240}{40} &= 0 \\ 4v_1 - 640 + v_1 - 240 &= 0 \\ 5v_1 = 880, \quad v_1 &= 176 \text{ V} \\ \therefore v_{ab} &= 176 \text{ V} \end{aligned}$$

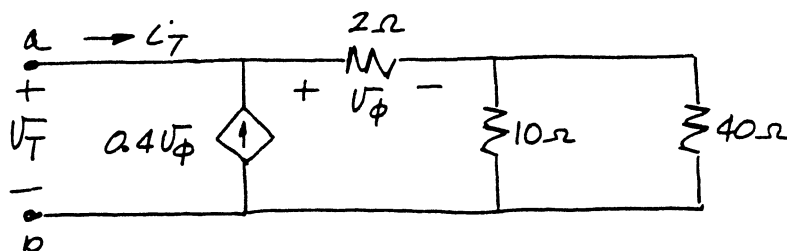Find Thévenin resistance looking into the terminals a, b.



$$v_T = (i_T + 0.4v_\phi)(2 + 8) = 10i_T + 4v_\phi$$

$$v_\phi = (i_T + 0.4v_\phi)2 = 2i_T + 0.8v_\phi$$


$$0.2v_\phi = 2i_T, \quad v_\phi = 10i_T$$

$$\therefore v_T = 10i_T + 40i_T = 50i_T$$

$$R_{Th} = v_T/i_T = 50 \Omega$$



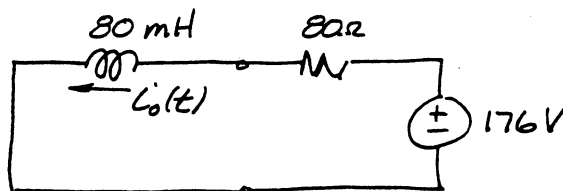It follows that the Thévenin equivalent with respect to the terminals of the 80-mH inductor is




$$\therefore i_o(\infty) = \frac{176}{80} = 2.2 \text{ A}$$

$$\tau = \frac{80}{80} \times 10^{-3} = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$\therefore i_o(t) = 2.2 + (1 - 2.2)e^{-1000t} = 2.2 - 1.2e^{-1000t} \text{ A}, \quad t \geq 0$$

P8.38 [a] For $t > 0$:

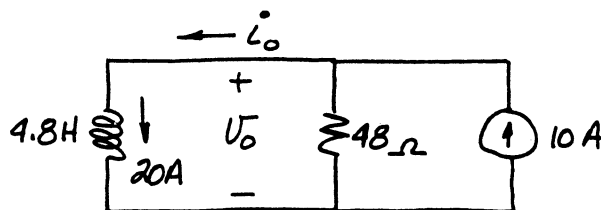

$$i_o(0^-) = i_o(0^+) = 20 \text{ A}$$

$$\tau = \frac{4.8}{4.8} = 0.1 \text{ s}; \quad \frac{1}{\tau} = 10$$

$$i_o(\infty) = 10 \text{ A}$$

$$i_o = 10 + (20 - 10)e^{-10t} = 10 + 10e^{-10t} \text{ A}, \quad t \geq 0$$

$$v_o = 4.8 \frac{di_o}{dt} = 4.8(-100e^{-10t}) = -480e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad i_1(t) = \frac{1}{12} \int_0^t -480e^{-10x} dx + i_1(0)$$

$$i_1(0) = (20) \left(\frac{8}{20} \right) = 8 \text{ A}$$

$$i_1(t) = -40 \left[\frac{e^{-10x}}{-10} \right]_0^t + 8$$

$$\therefore i_1(t) = 4e^{-10t} + 4 \text{ A}, \quad t \geq 0$$


$$[c] \quad i_2(t) = \frac{1}{8} \int_0^t -480e^{-10x} dx + i_2(0)$$

$$i_2(0) = 20 \left(\frac{12}{20} \right) = 12 \text{ A}$$

$$i_2(t) = -60 \left[\frac{e^{-10x}}{-10} \right]_0^t + 12$$

$$\therefore i_2(t) = 6e^{-10t} + 6 \text{ A}, \quad t \geq 0$$


P 8.39 $t < 0$:

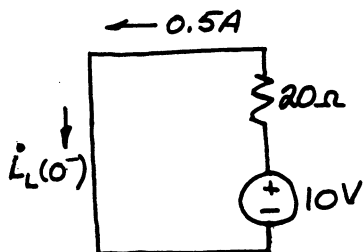


$$i_L(0^-) = 10/20 = 0.5 \text{ A}$$

$$i_L(0^+) = i_L(0^-) = 0.5 \text{ A}$$

For $t > 0$:

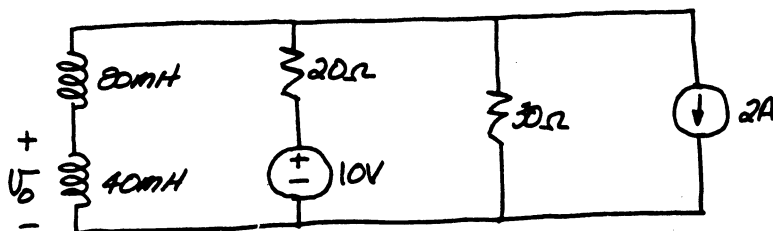


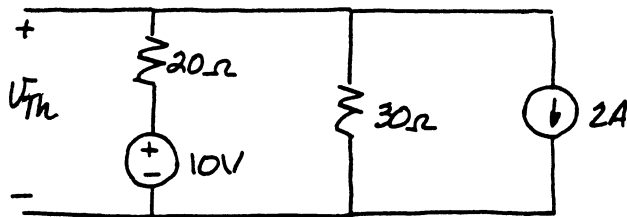Find the Thévenin equivalent with respect to the terminals of the inductors.



$$\begin{aligned}\frac{v_{Th} - 10}{20} + \frac{v_{Th}}{30} + 2 &= 0 \\ 3v_{Th} - 30 + 2v_{Th} + 120 &= 0 \\ 5v_{Th} &= -90 \\ v_{Th} &= -18 \text{ V}\end{aligned}$$
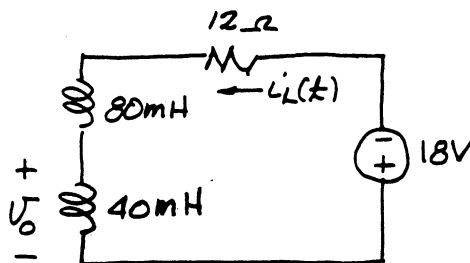
$$\begin{aligned}R_{Th} &= 20 // 30 = 12 \Omega \\ \tau &= \frac{120 \times 10^{-3}}{12} = 10 \text{ ms} \\ \frac{1}{\tau} &= 100\end{aligned}$$




$$i_L(\infty) = \frac{-18}{12} = -1.5 \text{ A}$$

$$\begin{aligned}\therefore i_L(t) &= -1.5 + (0.5 + 1.5)e^{-100t} \text{ A}, \quad t \geq 0 \\ &= -1.5 + 2e^{-100t} \text{ A}, \quad t \geq 0\end{aligned}$$

$$v_o = 40 \times 10^{-3} \frac{di_L}{dt} = (40 \times 10^{-3})[-200e^{-100t}] = -8e^{-100t} \text{ V}, \quad t \geq 0^+$$

Alternate solution:

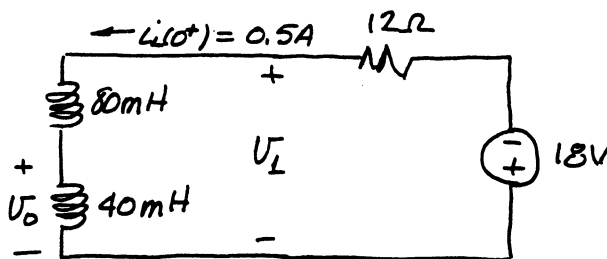

$$v_1(0^+) = -18 - 12(0.5) = -24 \text{ V}$$

$$v_o = \frac{40}{120}v_1 = \frac{1}{3}v_1$$

$$v_1 = -24e^{-100t} \text{ V}, \quad t \geq 0^+$$

$$\therefore v_o = -8e^{-100t} \text{ V}, \quad t \geq 0^+$$

P 8.40 [a] Let v be the voltage drop across the parallel branches, positive at the top node, then

$$-I_g + \frac{v}{R_g} + \frac{1}{L_1} \int_0^t v \, dx + \frac{1}{L_2} \int_0^t v \, dx = 0$$

$$\frac{v}{R_g} + \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t v \, dx = I_g$$

$$\frac{v}{R_g} + \frac{1}{L_e} \int_0^t v \, dx = I_g$$

$$\frac{1}{R_g} \frac{dv}{dt} + \frac{v}{L_e} = 0$$

$$\frac{dv}{dt} + \frac{R_g}{L_e} v = 0$$

$$\text{Therefore } v = I_g R_g e^{-t/\tau}; \quad \tau = L_e/R_g$$

$$\text{Therefore } i_1 = \frac{1}{L_1} \int_0^t I_g R_g e^{-x/\tau} \, dx = \frac{I_g R_g}{L_1} \frac{e^{-x/\tau}}{(-1/\tau)} \bigg|_0^t = \frac{I_g L_e}{L_1} (1 - e^{-t/\tau})$$

$$i_1 = \frac{I_g L_2}{L_1 + L_2} (1 - e^{-t/\tau}) \quad \text{and} \quad i_2 = \frac{I_g L_1}{L_1 + L_2} (1 - e^{-t/\tau})$$

$$[b] \quad i_1(\infty) = \frac{L_2}{L_1 + L_2} I_g; \quad i_2(\infty) = \frac{L_1}{L_1 + L_2} I_g$$

$$\textbf{P 8.41} [a] \quad i = C \frac{dv}{dt} = 10^5 C e^{-500t}$$

$$\therefore 10^5 C = 25 \times 10^{-3}$$

$$C = 25 \times 10^{-8} = 250 \times 10^{-9} = 250 \text{ nF}$$

$$\tau = RC = \frac{1}{500} = 2 \text{ ms}$$

$$R = \frac{1}{500C} = 800 \text{ k}\Omega$$

$$v(\infty) = 200 \text{ V} = I_g R$$

$$\therefore I_g = \frac{200}{800} \times 10^{-3} = 0.25 \text{ mA}$$

$$[b] \quad w(\infty) = \frac{1}{2} (250 \times 10^{-9}) (4 \times 10^4) = 5000 \mu\text{J}$$

$$\begin{aligned} w(t) &= \frac{1}{2} (250 \times 10^{-9}) [4 \times 10^4 - 8 \times 10^4 e^{-500t} + 4 \times 10^4 e^{-1000t}] \\ &= 5000 [e^{-1000t} - 2e^{-500t} + 1] \mu\text{J} \end{aligned}$$

$$\therefore 5000[e^{-1000t} - 2e^{-500t} + 1] = 0.36(5000)$$

$$e^{-1000t} - 2e^{-500t} + 1 = 0.36$$

$$\text{Let } x = e^{-500t} \quad x = 1 \pm \sqrt{1 - 0.64} = 1 \pm 0.6$$

$$x^2 - 2x + 0.64 = 0 \quad x_1 = 1.6, \quad x_2 = 0.4$$

Only x_2 has physical significance:

$$e^{-500t} = 0.4 \quad 500t = \ln 2.5$$

$$e^{500t} = 2.5 \quad t = 2 \ln 2.5 \text{ ms} \cong 1.83 \text{ ms}$$

A better way:


$$w = \frac{1}{2}Cv^2 = \frac{1}{2}Cv^2(\infty)[1 - e^{-500t}]^2 = w(\infty)[1 - e^{-500t}]^2$$

$$w(\infty)(1 - e^{-500t})^2 = 0.36w(\infty)$$

$$\therefore 1 - e^{-500t} = 0.6; \quad e^{-500t} = 0.4; \quad t \cong 1.83 \text{ ms}$$

P 8.42 [a] $v_o(0^-) = v_o(0^+) = 0$

$t > 0:$

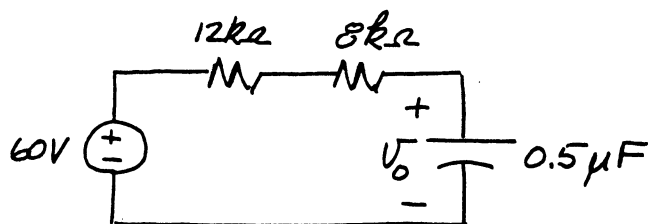

$$C \frac{dv_o}{dt} + \frac{v_o - 60}{20 \times 10^3} = 0$$

$$\frac{dv_o}{dt} + \frac{v_o - 60}{10 \times 10^{-3}} = 0$$

$$\frac{dv_o}{dt} = \frac{-v_o}{10 \times 10^{-3}} + \frac{60}{10 \times 10^{-3}}$$

$$\frac{dv_o}{v_o - 60} = \frac{-dt}{10^{-2}} = -100 dt$$

$$\int_{v_o(0)}^{v_o(t)} \frac{dx}{x - 60} = \int_0^t -100 dy$$

$$\ln[v_o(t) - 60] - \ln[v_o(0) - 60] = -100t$$


$$\ln \frac{[v_o(t) - 60]}{[v_o(0) - 60]} = -100t$$

$$\frac{v_o(t) - 60}{v_o(0) - 60} = e^{-100t}$$

$$v_o(t) - 60 = (v_o(0) - 60)e^{-100t}$$

$$v_o(t) = 60 - 60e^{-100t} \text{ V}, \quad t \geq 0^+$$

[b]

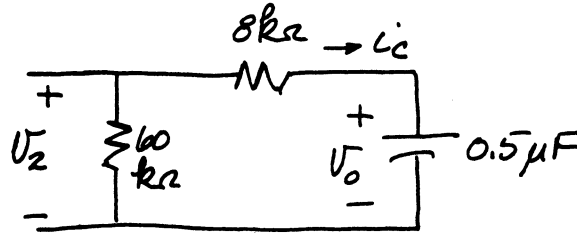

$$i_C = C \frac{dv_o}{dt} = (0.5 \times 10^{-6})(6000e^{-100t}) = 3e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$\therefore v_2 = v_o + 8000i_C = 60 - 60e^{-100t} + 24e^{-100t} = 60 - 36e^{-100t} \text{ V}, \quad t \geq 0^+$$


$$i_o(t) = \frac{v_2}{60} = 1 - 0.6e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$[c] \quad i_1(t) = i_o(t) + i_C = 1 - 0.6e^{-100t} + 3e^{-100t} = 1 + 2.4e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$[d] \quad i_2(t) = \frac{v_2(t)}{15} = 4i_o(t) = 4 - 2.4e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$[e] \quad i_1(0^+) = 3.4 \text{ mA}$$

Check: at $t = 0^+$ we have:

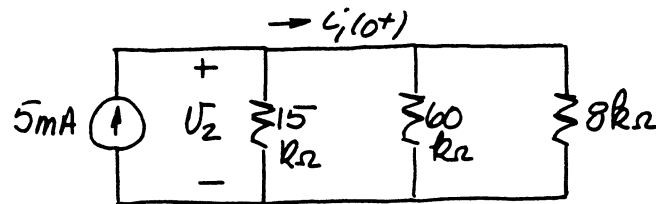

$$\frac{1}{R_e} = \frac{1}{15} + \frac{1}{60} + \frac{1}{8} = \frac{25}{120} \text{ mmhos}$$

$$\therefore R_e = \frac{120}{25} = 4.8 \text{ k}\Omega$$

$$\therefore v_2(0^+) = (5)(4.8) = 24 \text{ V}$$

$$\therefore i_1(0^+) = \frac{24}{60} + \frac{24}{8} = 0.4 + 3 = 3.4 \text{ mA (ok)}$$

P 8.43 [a] $v_o(0^-) = v_o(0^+) = 120 \text{ V}; \quad v_o(\infty) = -4(37.5) = -150 \text{ V}$

$$\tau = (37.5 + 12.5)10^3(0.04 \times 10^{-6}) = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$


$$\therefore v_o(t) = -150 + 270e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad i_o(t) = -C \frac{dv_o}{dt} = -0.04 \times 10^{-6}(-135,000e^{-500t}) = 5.4e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$[c] \quad v_g(t) = v_o - 12.5i_o(t) = -150 + 270e^{-500t} - 67.5e^{-500t} \\ = -150 + 202.5e^{-500t} \text{ V}, \quad t \geq 0^+$$

[d] $v_g(0^+) = 52.50 \text{ V}$

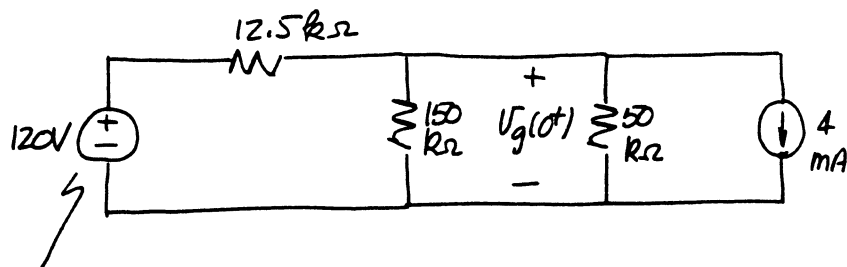
We can check $v_g(0^+)$ as follows. At $t = 0^+$ we have:



Capacitor acts like a voltage source at $t = 0^+$.

$$\begin{aligned} \frac{v_g(0^+) - 120}{12.5} + \frac{v_g(0^+)}{150} + \frac{v_g(0^+)}{50} + 4 &= 0 \\ 12v_g(0^+) - 1440 + v_g(0^+) + 3v_g(0^+) + 600 &= 0 \\ 16v_g(0^+) &= 840 \\ v_g(0^+) &= 52.50 \text{ V (ok)} \end{aligned}$$

P8.44 [a] $t = 0^+$:

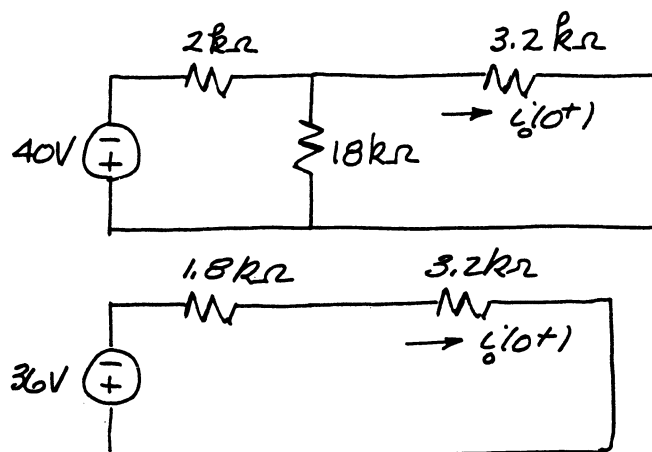


$$i_o(0^+) = \frac{-36}{5} = -7.2 \text{ mA}$$

[b] $i_o(\infty) = 0$

[c] $\tau = (5 \times 10^3)(0.8 \times 10^{-6}) = 4 \text{ ms}$

[d] $i_o(t) = 0 - 7.2e^{-250t} \text{ mA}, \quad t \geq 0^+$


[e]

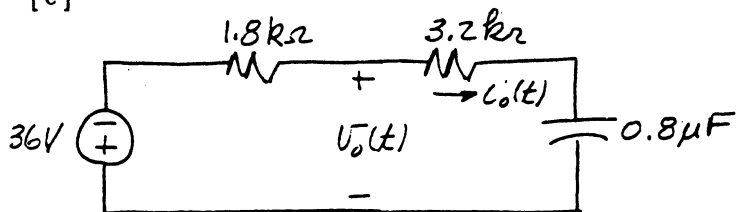

$$\begin{aligned} v_o(t) &= -36 - 1.8i_o(t) = -36 - 1.8(-7.2)e^{-250t} \\ &= -36 + 12.96e^{-250t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

P 8.45 $t < 0$:

$$i_o(0^-) = (10) \frac{20}{100} = 2 \text{ mA}; \quad v_o(0^-) = (2)(50) = 100 \text{ V}$$

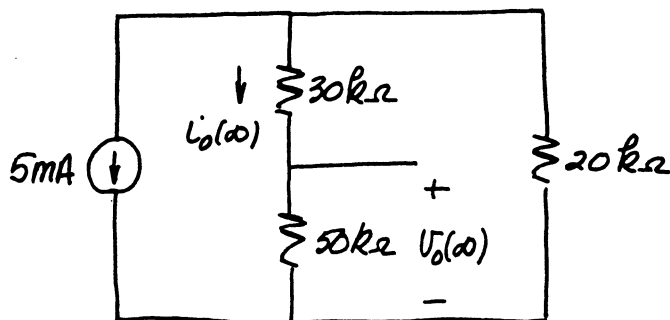
 $t = \infty$:


$$i_o(\infty) = -5 \left(\frac{20}{100} \right) = -1 \text{ mA}; \quad v_o(\infty) = i_o(\infty)(50) = -50 \text{ V}$$

$$R_{Th} = 50 \text{ k}\Omega // 50 \text{ k}\Omega = 25 \text{ k}\Omega; \quad C = 0.016 \mu\text{F}$$

$$\tau = (25)(0.016) = 0.4 \text{ ms}; \quad \frac{1}{\tau} = 2500$$
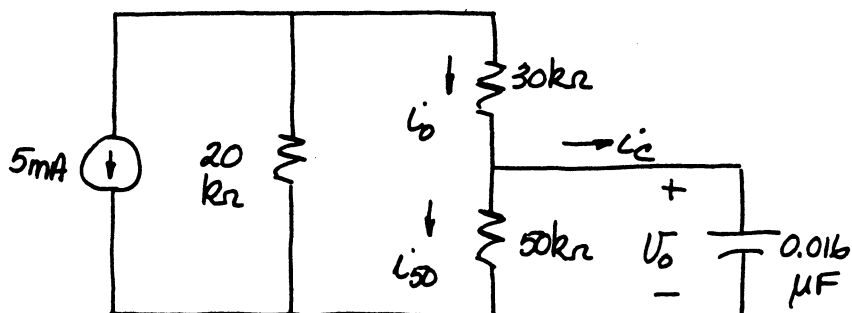
$$\therefore v_o(t) = -50 + 150e^{-2500t} \text{ V}, \quad t \geq 0^+$$




$$i_C = C \frac{dv_o}{dt} = -6e^{-2500t} \text{ mA}, \quad t \geq 0^+$$


$$i_{50} = \frac{v_o}{50} = -1 + 3e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_o = i_C + i_{50} = -(1 + 3e^{-2500t}) \text{ mA}, \quad t \geq 0^+$$


P8.46 $t < 0$:

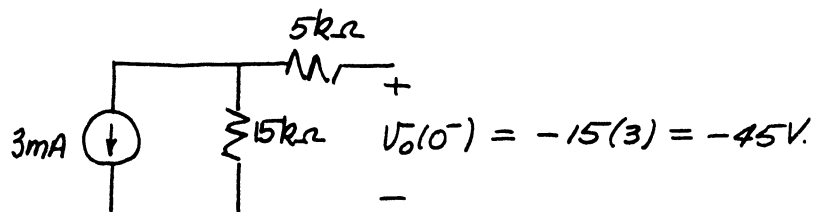

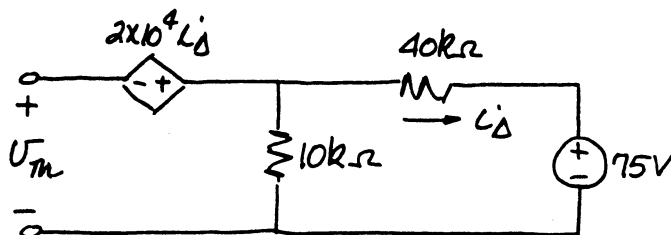$t > 0$: Find the Thévenin equivalent with respect to the capacitor.


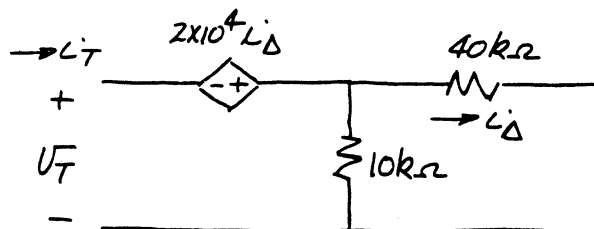
$$v_{Th} = -2 \times 10^4 i_D + \frac{75}{50}(10) = -2 \times 10^4 \left(\frac{-75}{50 \times 10^3} \right) + 15 = 30 + 15 = 45 \text{ V}$$




$$v_T = -2 \times 10^4 i_D + 8000 i_T$$

$$i_D = i_T \frac{(10)}{(50)} = 0.2 i_T$$

$$v_T = (-0.4 \times 10^4 + 8000) i_T = 4000 i_T$$

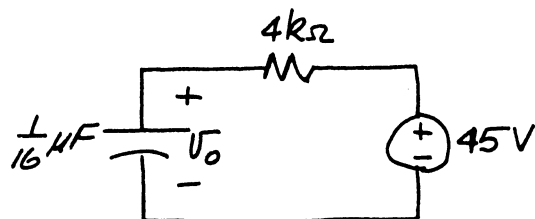
$$\therefore R_{Th} = \frac{v_T}{i_T} = 4 \text{ k}\Omega$$



$$\therefore v_o(\infty) = 45 \text{ V}; \quad \tau = \left(\frac{1}{16}\right)(4)10^{-3} = 0.25 \text{ ms}; \quad \frac{1}{\tau} = 4000$$

$$v_o(t) = 45 + (-45 - 45)e^{-4000t} = 45 - 90e^{-4000t} \text{ V}, \quad t \geq 0$$


P8.47 $t < 0$:

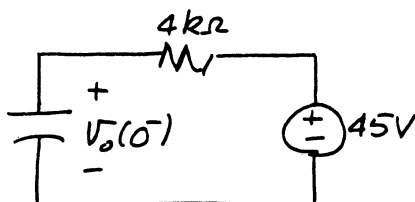

$$v_o(0^-) = 45 \text{ V}$$

$$v_o(0^+) = 45 \text{ V}$$

$t > 0$:

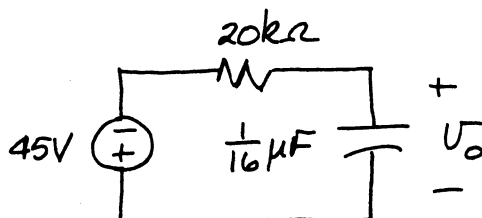

$$v_o(\infty) = -45 \text{ V}$$


$$\tau = (20) \left(\frac{1}{16}\right) \times 10^{-3}$$


$$= 1.25 \text{ ms}$$

$$\frac{1}{\tau} = 800$$




$$\therefore v_o = -45 + (45 + 45)e^{-800t} = -45 + 90e^{-800t} \text{ V}, \quad t \geq 0$$

P8.48 $t < 0$:

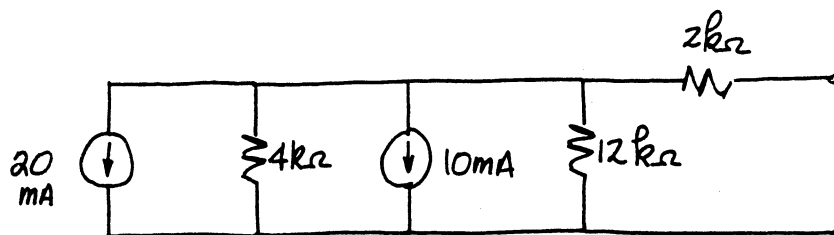

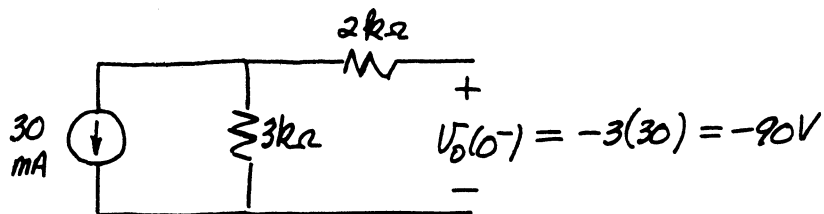

$t > 0$:

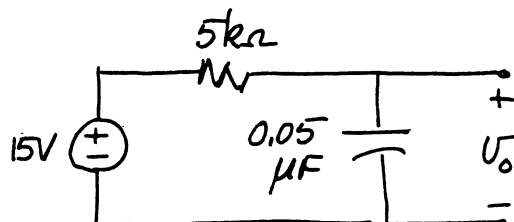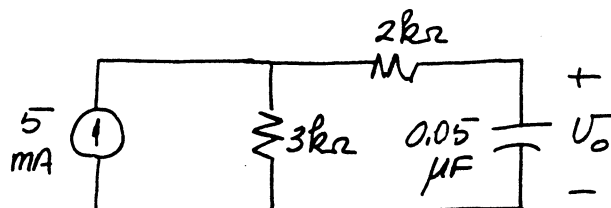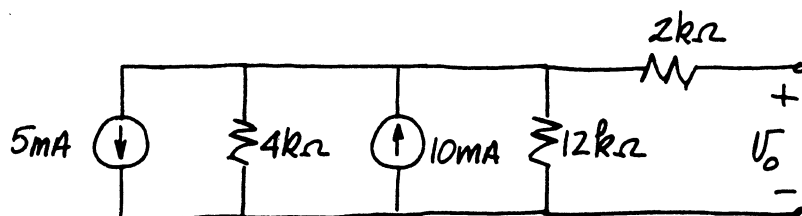

$$v_o(\infty) = 15\text{ V}; \quad \tau = 0.25\text{ ms}; \quad \frac{1}{\tau} = 4000$$

$$v_o = 15 + (-90 - 15)e^{-4000t}$$

$$v_o = 15 - 105e^{-4000t}\text{ V}, \quad t \geq 0$$

P 8.49 [a] Let i be the current in the clockwise direction around the circuit. Then

$$\begin{aligned} V_g &= iR_g + \frac{1}{C_1} \int_0^t i \, dx + \frac{1}{C_2} \int_0^t i \, dx \\ &= iR_g + \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int_0^t i \, dx = iR_g + \frac{1}{C_e} \int_0^t i \, dx \end{aligned}$$

Now differentiate the equation

$$0 = R_g \frac{di}{dt} + \frac{i}{C_e} \quad \text{or} \quad \frac{di}{dt} + \frac{1}{R_g C_e} i = 0$$

Therefore $i = \frac{V_g}{R_g} e^{-t/R_g C_e} = \frac{V_g}{R_g} e^{-t/\tau}; \quad \tau = R_g C_e$

$$v_1(t) = \frac{1}{C_1} \int_0^t \frac{V_g}{R_g} e^{-x/\tau} dx = \frac{V_g}{R_g C_1} \left. \frac{e^{-x/\tau}}{-1/\tau} \right|_0^t = -\frac{V_g C_e}{C_1} (e^{-t/\tau} - 1)$$

$$v_1(t) = \frac{V_g C_2}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$


$$v_2(t) = \frac{V_g C_1}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

[b] $v_1(\infty) = \frac{C_2}{C_1 + C_2} V_g; \quad v_2(\infty) = \frac{C_1}{C_1 + C_2} V_g$

P 8.50 [a] It follows from Problem 8.49 that

$$v_1(0) = \left(\frac{0.6}{0.9} \right) (60) = 40 \text{ V}; \quad v_2(0) = \left(\frac{0.3}{0.9} \right) (60) = 20 \text{ V}$$

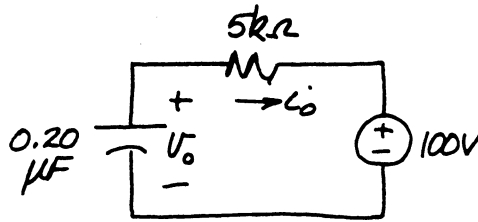We also have $C_e = \frac{(0.3)(0.6)}{0.90} = 0.2 \mu\text{F}$



$$\begin{aligned} \tau &= (0.2)(5) \times 10^{-3} \\ &= 1 \text{ ms} \\ 1/\tau &= 1000 \\ v_o(0) &= 60 \text{ V} \\ v_o(\infty) &= 100 \text{ V} \end{aligned}$$

$$v_o = 100 + (60 - 100)e^{-1000t}$$

$$v_o(t) = 100 - 40e^{-1000t} \text{ V}, \quad t \geq 0$$

[b] $i_o(t) = -C_e \frac{dv_o}{dt} = -0.2 \times 10^{-6} (40,000 e^{-1000t}) = -8e^{-1000t} \text{ mA}, \quad t \geq 0^+$

[c]
$$\begin{aligned} v_1(t) &= -\frac{10^6}{0.3} \int_0^t (-8 \times 10^{-3}) e^{-1000x} dx + 40 = \frac{8000}{0.3} \left[\frac{e^{-1000x}}{-1000} \right]_0^t + 40 \\ &= \frac{-80}{3} [e^{-1000t} - 1] + 40 = \frac{-80}{3} e^{-1000t} + \frac{200}{3} \text{ V}, \quad t \geq 0 \end{aligned}$$

[d]
$$\begin{aligned} v_2(t) &= \frac{-10^6}{0.6} \int_0^t (-8 \times 10^{-3}) e^{-1000x} dx + 20 = \frac{8000}{0.6} \left[\frac{e^{-1000x}}{-1000} \right]_0^t + 20 \\ &= \frac{-80}{6} [e^{-1000t} - 1] + 20 = \frac{-80}{6} e^{-1000t} + \frac{200}{6} \\ &= \frac{-40}{3} e^{-1000t} + \frac{100}{3} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\text{Check: } v_1 + v_2 = \frac{-120}{3}e^{-1000t} + \frac{300}{3} = -40e^{-1000t} + 100 \quad (\text{ok})$$


$$[e] \quad v_1(\infty) = \frac{200}{3} \text{ V}; \quad v_2(\infty) = \frac{100}{3} \text{ V}$$

$$\begin{aligned} w(\infty) &= \frac{1}{2}(0.3 \times 10^{-6}) \left(\frac{4 \times 10^4}{9} \right) + \frac{1}{2}(0.6 \times 10^{-6}) \left(\frac{10^4}{9} \right) \\ &= \frac{(2 \times 10^4)(10^{-6})}{30} + \frac{10^4(10^{-6})}{30} = \frac{10^{-2}}{30}(3) = 10^{-3} = 1 \text{ mJ} \end{aligned}$$

$$\mathbf{P\ 8.51} \quad i_b = \frac{120(33)}{80} = 49.5 \mu\text{A}$$

$$v_{\text{Th}} = -25i_b(16 \times 10^3) - 400 \times 10^3 i_b = -19,800 \times 10^{-3} = -19.8 \text{ V}$$

$$R_{\text{Th}} = 16 \text{ k}\Omega$$

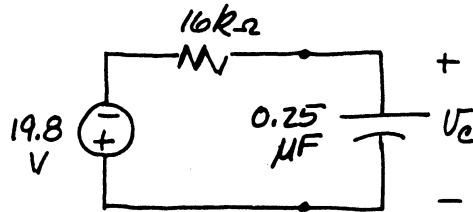

$$\tau = (16)(0.25) \times 10^{-3} = 4 \text{ ms}$$

$$1/\tau = 250$$

$$v_C(0) = 0$$

$$v_C(\infty) = -19.8 \text{ V}$$

$$v_C = -19.8 + 19.8e^{-250t} \text{ V}, \quad 0 \leq t \leq \infty$$

$$w = \frac{1}{2}Cv_C^2 = 0.125 \times 10^{-6}[392.04 - 784.08e^{-250t} + 392.04e^{-500t}] \text{ J}$$

$$w(\infty) = 0.125 \times 10^{-6}(392.04)$$

$$\therefore 0.125 \times 10^{-6}v_C^2 = 0.36[0.125 \times 10^{-6}]392.04$$

$$\therefore 392.04 - 784.08e^{-250t} + 392.04e^{-500t} = 0.36(392.04)$$

$$\therefore 1 - 2e^{-250t} + e^{-500t} = 0.36$$

$$\therefore e^{-500t} - 2e^{-250t} + 0.64 = 0$$

$$x^2 - 2x + 0.64 = 0, \quad x = e^{-250t}$$

$$x = 1 \pm \sqrt{1 - 0.64} = 1 \pm 0.6$$

$$x_1 = 1.6, \quad x_2 = 0.4$$

Only x_2 has physical significance.

$$0.4 = e^{-250t}; \quad e^{250t} = 2.5$$

$$250t = \ln 2.5; \quad t = 4 \ln 2.5 \text{ ms} \cong 3.67 \text{ ms}$$


A better way:

$$w(t) = w(\infty)[1 - e^{-250t}]^2$$

$$\therefore (1 - e^{-250t})^2 = 0.36; \quad 1 - e^{-250t} = 0.6$$

$$t \approx 3.67 \text{ ms}$$


P 8.52 $t < 0$:

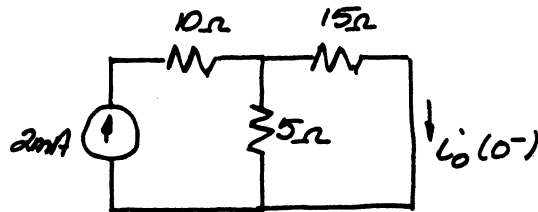

$$i_o(0^-) = 2 \left(\frac{5}{20} \right) = 0.5 \text{ mA}$$

$$i_o(0^+) = i_o(0^-) = 0.5 \text{ mA}$$

$t = 0^+$:

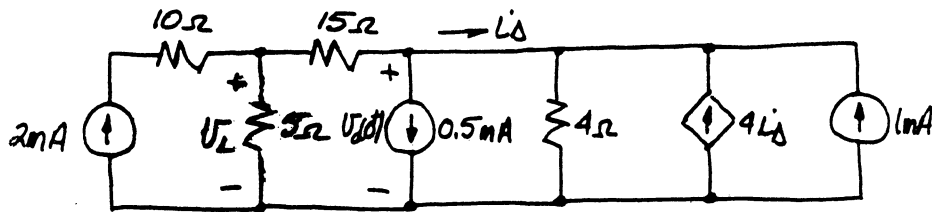

$$0.5 \times 10^{-3} + \frac{v_o(0^+) - v_1}{15} + \frac{v_o(0^+)}{4} - 4i_\Delta - 10^{-3} = 0$$

$$\text{or } 19v_o(0^+) - 4v_1 - 240i_\Delta = 30 \times 10^{-3}$$

$$\frac{v_1}{5} + \frac{v_1 - v_o(0^+)}{15} - 2 \times 10^{-3} = 0$$

$$\text{or } 8v_1 - 2v_o(0^+) = 60 \times 10^{-3}; \quad \therefore v_1 = 0.25v_o(0^+) + 7.5 \times 10^{-3}$$

$$i_\Delta = \frac{v_1 - v_o(0^+)}{15} - 0.5 \times 10^{-3}$$

$$\therefore 240i_\Delta = 16v_1 - 16v_o(0^+) - 120 \times 10^{-3}$$

$$\therefore 19v_o(0^+) - 4v_1 - 16v_1 + 16v_o(0^+) + 120 \times 10^{-3} = 30 \times 10^{-3}$$

$$\therefore 35v_o(0^+) - 20v_1 = -90 \times 10^{-3}$$


$$35v_o(0^+) - 5v_o(0^+) - 150 \times 10^{-3} = -90 \times 10^{-3}$$

$$30v_o(0^+) = 60 \times 10^{-3}$$

$$v_o(0^+) = 2 \text{ mV}$$

We know $v_o(\infty) = 0 \text{ V}$

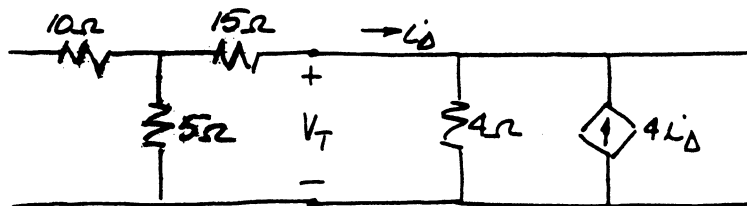To find the time constant find the Thévenin resistance with respect to the terminals of the inductor.



$$i_T = \frac{V_T}{20} + \frac{V_T}{4} - 4i_\Delta$$

$$i_\Delta = \frac{V_T}{4} - 4i_\Delta$$

$$\therefore 5i_\Delta = \frac{V_T}{4}; \quad i_\Delta = \frac{V_T}{20}; \quad 4i_\Delta = \frac{V_T}{5}$$

$$\therefore i_T = \frac{V_T}{20} + \frac{V_T}{4} - \frac{V_T}{5} = \left(\frac{1}{20} + \frac{5}{20} - \frac{4}{20} \right) V_T$$

$$\frac{i_T}{V_T} = \frac{1}{10}$$

$$\therefore R_{Th} = \frac{V_T}{i_T} = 10 \Omega$$

$$\tau = \frac{L}{R_{Th}} = 0.2 \text{ ms}; \quad \frac{1}{\tau} = 5000$$

$$\therefore v_o(t) = 0 + (2 - 0)e^{-5000t} \text{ mV} = 2e^{-5000t} \text{ mV}, \quad t \geq 0^+$$

P 8.53 [a] $i(0^+) = \left[\frac{240}{(1.6 + 6.4)} \right] \left(\frac{8}{40} \right) = 6 \text{ A}$

[b] $0 \leq t \leq 800 \mu\text{s}$

$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{32 + 4.8} = \frac{20 \times 10^{-3}}{36.8}; \quad \frac{1}{\tau} = 1840$$

$$i = 6e^{-1840t} \text{ A}, \quad 0 \leq t \leq 800 \mu\text{s}$$

$$i(300 \mu\text{s}) = 6e^{-0.552} \approx 3.45 \text{ A}$$


[c] $i(800 \mu\text{s}) = 6e^{-1.472} \approx 1.38 \text{ A}, \quad 800 \mu\text{s} \leq t \leq \infty$

$$i = 1.38e^{-(t-0.0008)/\tau}; \quad \tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{32}; \quad \frac{1}{\tau} = 1600$$

$$i = 1.38e^{-1600(t-0.0008)}$$


$$i(1 \text{ ms}) = 1.38e^{-1600(2 \times 10^{-4})} = 1.38e^{-0.32} \approx 1.0 \text{ A}$$

[d] $t = 800^- \mu\text{s}$

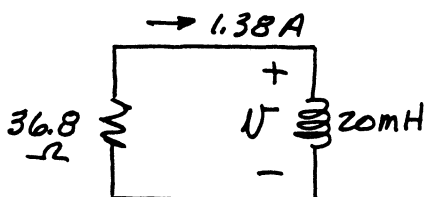


$$v(800^- \mu\text{s}) = -36.8(1.38) = -50.67 \text{ V}$$

[e] $t = 800^+ \mu\text{s}$

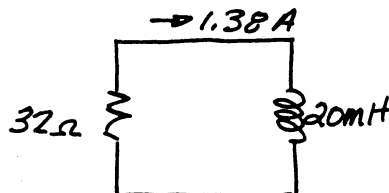


$$v(800^+ \mu\text{s}) = -32(1.38) = -44.06 \text{ V}$$

P8.54 For $t < 0$:

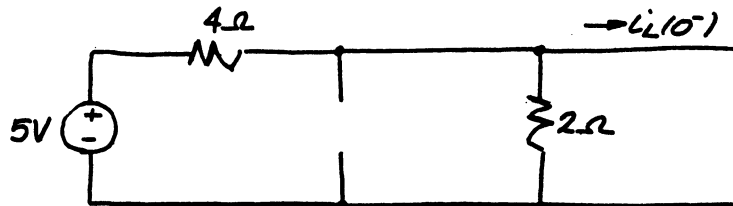

$$i_L(0^-) = \frac{5}{4} = 1.25 \text{ A}; \quad \therefore i_L(0^+) = 1.25 \text{ A}$$

$0 \leq t \leq 1\text{s}$:

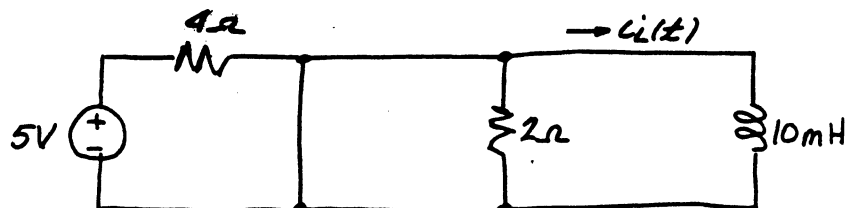


In this interval the voltage across the inductor is zero, hence $i_L(t)$ stays at 1.25 A. Also note the Thévenin resistance seen from the terminals of the inductor is zero, hence the time constant is infinite and the exponential function is unity, that is

$$e^{-t/\infty} = 1 \quad \text{for all finite values of } t.$$

$$\text{Thus } i_L = 1.25e^0 = 1.25 \text{ A}, \quad 0 \leq t \leq 1\text{s}$$


For $1 \leq t \leq \infty$:

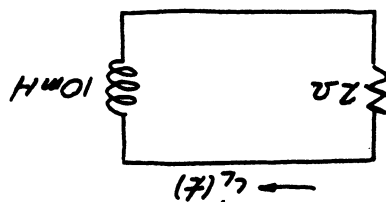


$$\tau = L/R = 5 \text{ ms}$$

$$1/\tau = 200$$

$$\therefore i_L(t) = 1.25e^{-200(t-1)} \text{ A}, \quad 1 \leq t \leq \infty$$

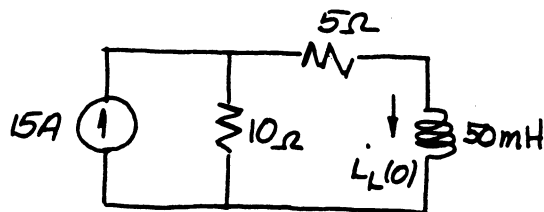P 8.55 $t < 0$:

$$i_L(0) = \frac{15(10)}{15} = 10 \text{ A}$$

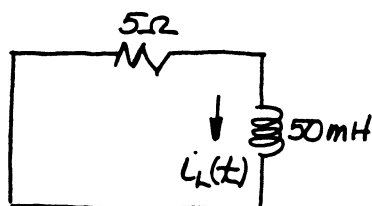
 $0 \leq t \leq 10 \text{ ms}$:

$$\tau = \frac{50}{5} \times 10^{-3} = 10 \text{ ms}$$

$$1/\tau = 100$$

$$i_L(t) = 10e^{-100t} \text{ A}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$i_L(10 \text{ ms}) = 10e^{-1} \text{ A}$$

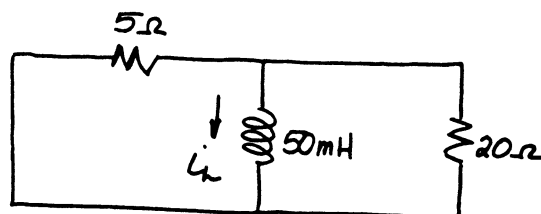 $10 \text{ ms} \leq t \leq 20 \text{ ms}$:


$$R_e = \frac{(20)(5)}{25} = 4 \Omega$$

$$\tau = \frac{50}{4} = 12.5 \text{ ms}$$

$$1/\tau = 80$$

$$i_L(t) = [10e^{-1}]e^{-80(t-0.01)} \text{ A}, \quad 10 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$i_L(20 \text{ ms}) = (10e^{-1})(e^{-80(0.01)}) = 10e^{-1.8}$$

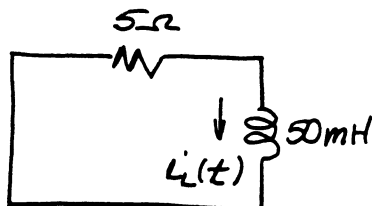 $20 \text{ ms} \leq t \leq \infty$:

$$\tau = 10 \text{ ms}$$

$$1/\tau = 100$$

$$\begin{aligned}
 i_L(t) &= (10e^{-1.8})e^{-100(t-20 \times 10^{-3})} \\
 i_L(25 \text{ ms}) &= (10e^{-1.8})e^{-0.5} = 10e^{-2.3} \text{ A} \\
 v_o &= -5i_L = -50e^{-2.3} = -5.01 \text{ V}
 \end{aligned}$$

P 8.56 $w(0) = \frac{1}{2}(50 \times 10^{-3})(10)^2 = 2.5 \text{ J}$

$$0.04w(0) = 0.10 \text{ J}$$

$$\therefore \frac{1}{2}50 \times 10^{-3}i_L^2 = 0.10; \quad i_L^2 = 4; \quad i_L = 2 \text{ A}$$

From the solution to Problem 8.55 we note t must lie between 10 and 20 ms, i.e.,

$$i_L(10 \text{ ms}) = 10e^{-1} \cong 3.68 \text{ A}$$

$$i_L(20 \text{ ms}) = 10e^{-1.8} \cong 1.65 \text{ A}$$

$$\therefore (10e^{-1})e^{-80(t-0.01)} = 2$$

$$e^{-80(t-0.01)} = 0.2e^1$$

$$80(t - 0.01) = \ln [0.2e^1]^{-1}$$

$$t = \frac{1}{80} \ln [(0.2e^1)]^{-1} + 0.01$$

$$t = 17.62 \text{ ms}$$

Note $[0.2e^1]^{-1} = 5e^{-1}$

P 8.57 $0 \leq t \leq 5 \text{ s}$:

$$v_o(0^-) = v_o(0^+) = -5 \text{ V}$$

Since the capacitor does not discharge while the switch is in position (b), v_o is constant at -5 V :

$$v_o = -5 \text{ V}, \quad 0 \leq t \leq 5 \text{ s}$$

$$5 \text{ s} \leq t \leq \infty:$$

$$\tau = RC = 100 \times 10^3 \times 100 \times 10^{-6} = 10 \text{ s}; \quad 1/\tau = 0.1$$

$$\therefore v_o = -5e^{-0.1(t-5)} \text{ V}, \quad 5 \text{ s} \leq t \leq \infty$$

P 8.58 $0 \leq t \leq 3 \mu\text{s}$:


$$v_o(0) = 0 \quad \tau = (2000)(5 \times 10^{-9}) = 10 \mu\text{s}$$

$$v_o(\infty) = 6 \text{ V} \quad 1/\tau = 100,000$$

$$v_o = 6 - 6e^{-100,000t} \text{ V}, \quad 0 \leq t \leq 3 \mu\text{s}$$

$$v_o(3 \mu\text{s}) = 6 - 6e^{-0.3} = 1.56 \text{ V}$$

$$3\mu\text{s} \leq t \leq \infty:$$

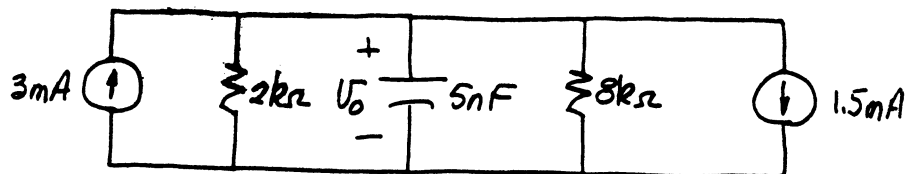

$$2\text{k}\Omega // 8\text{k}\Omega = 1.6\text{k}\Omega$$

$$v_o(\infty) = (1.5)(1.6) = 2.40\text{ V}$$

$$\tau = (1.6)(5) \times 10^{-6} = 8\mu\text{s}; \quad 1/\tau = 125,000$$

$$\therefore v_o = 2.40 + (1.56 - 2.40)e^{-125,000(t-3 \times 10^{-6})}$$


$$v_o = 2.4 - 0.84e^{-125,000(t-3 \times 10^{-6})}\text{ V}, \quad 3\mu\text{s} \leq t \leq \infty$$

Summary:

$$v_o = 6 - 6e^{-100,000t}\text{ V}, \quad 0 \leq t \leq 3\mu\text{s}$$

$$v_o = 2.4 - 0.84e^{-125,000(t-3 \times 10^{-6})}\text{ V}, \quad 3\mu\text{s} \leq t \leq \infty$$

P 8.59 $0 \leq t \leq 200\mu\text{s}$:

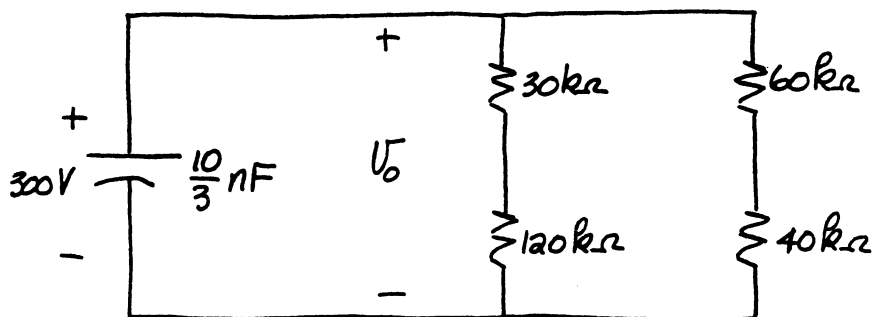


$$R = 150\text{k}\Omega // 100\text{k}\Omega = 60\text{k}\Omega$$

$$\tau = (60,000) \left(\frac{10}{3} \right) \times 10^{-9} = 2 \times 10^{-4}\text{ s}; \quad \frac{1}{\tau} = 5000$$

$$v_o = 300e^{-5000t}\text{ V}, \quad 0 \leq t \leq 200\mu\text{s}$$

$$v_o(200) = 300e^{-5000(200)10^{-6}} = 300e^{-1}$$

$$200 \mu\text{s} \leq t \leq \infty:$$

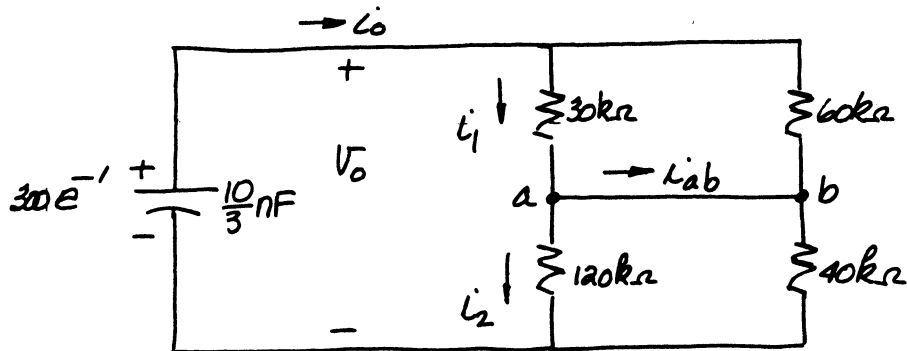

$$R = 30 \text{ k}\Omega // 60 \text{ k}\Omega + 120 \text{ k}\Omega // 40 \text{ k}\Omega = 20 \text{ k}\Omega + 30 \text{ k}\Omega = 50 \text{ k}\Omega$$

$$\tau = \left(\frac{10}{3} \times 10^{-9} \right) (50,000) = \frac{5}{3} \times 10^{-4} \text{ s}; \quad \frac{1}{\tau} = 6000$$

$$v_o = (300e^{-1})e^{-6000(t-200 \times 10^{-6})} \text{ V}, \quad 200 \mu\text{s} \leq t \leq \infty$$

$$v_o(300 \mu\text{s}) = 300e^{-1}e^{-0.6} = (300e^{-1.6})$$


$$i_o(300 \mu\text{s}) = \frac{300e^{-1.6}}{50} \times 10^{-3} = 6e^{-1.6} \text{ mA}$$

$$i_1 = \frac{60}{90}i_o = \frac{2}{3}i_o; \quad i_2 = \frac{40}{160}i_o = \frac{1}{4}i_o$$

$$i_{ab} = i_1 - i_2 = \left(\frac{2}{3} - \frac{1}{4} \right) i_o = \frac{5}{12}i_o = \left(\frac{5}{12} \right) (6e^{-1.6}) \text{ mA} = 2.5e^{-1.6} \text{ mA}$$


$$i_{ab} = 504.74 \mu\text{A} \quad (\text{left-to-right in the switch})$$

P 8.60 $t < 0$:

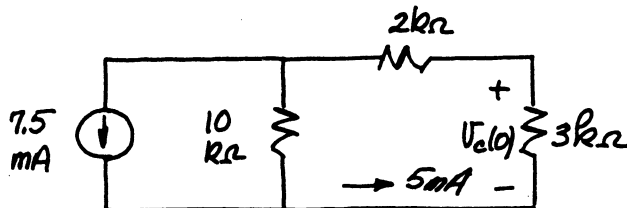

$$v_c(0) = -5(3) = -15 \text{ V}$$

$$0 \leq t \leq 800 \mu\text{s}:$$

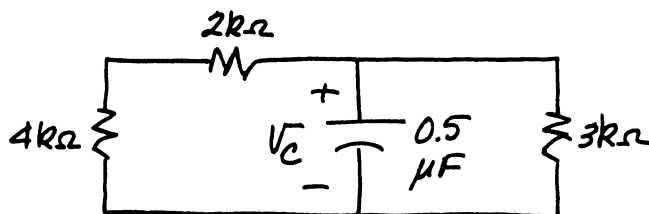


$$R_e = 3 \text{ k}\Omega // 6 \text{ k}\Omega = 2 \text{ k}\Omega$$

$$\tau = 2000(0.5 \times 10^{-6}) = 10^{-3} = 1 \text{ ms}; \quad 1/\tau = 1000$$

$$v_C = -15e^{-1000t} \text{ V}, \quad 0 \leq t \leq 800 \mu\text{s}$$

$$v_C(800 \mu\text{s}) = -15e^{-0.8} \text{ V}$$

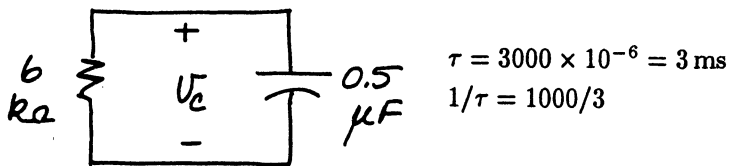
$$800 \mu\text{s} \leq t \leq 1100 \mu\text{s}:$$



$$v_C = (-15e^{-0.8})e^{-(1000/3)(t-800 \times 10^{-6})} \text{ V}, \quad 800 \mu\text{s} \leq t \leq 1100 \mu\text{s}$$

$$v_C(1100 \mu\text{s}) = (-15e^{-0.8})(e^{(-1000/3)(300 \times 10^{-6})}) = -15e^{-0.8}e^{-0.1} = (-15e^{-0.90}) \text{ V}$$

$$1100 \mu\text{s} \leq t \leq \infty:$$

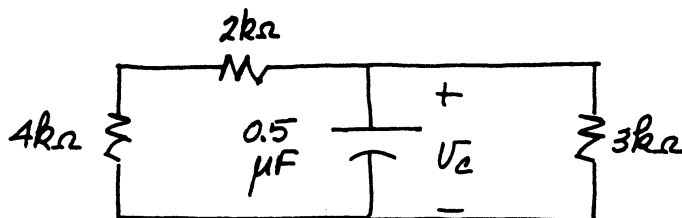

$$\tau = 1 \text{ ms}; \quad 1/\tau = 1000$$

$$v_C = (-15e^{-0.9})e^{-1000(t-1100 \mu\text{s})}; \quad v_C(1500 \mu\text{s}) = -15e^{-0.9}e^{-0.4} = -15e^{-1.3} \text{ V}$$

$$v_o = \frac{2}{3}v_C; \quad v_o(1500 \mu\text{s}) = -10e^{-1.3} \approx -2.73 \text{ V}$$

P8.61 $0 \leq t \leq 800 \mu\text{s}$:

$$p_{3k} = \frac{v_C^2}{3000} = \frac{225e^{-2000t}}{3000} = 75 \times 10^{-3} e^{-2000t} \text{ W}$$

$$w_{3k} = 75 \times 10^{-3} \int_0^{800 \times 10^{-6}} e^{-2000t} dt = (75 \times 10^{-3}) \left. \frac{e^{-2000t}}{-2000} \right|_0^{800 \times 10^{-6}}$$

$$= 37.5 \times 10^{-6} (1 - e^{-1.6}) \text{ J} = 37.5(1 - e^{-1.6}) \mu\text{J}$$

$800 \mu\text{s} \leq t \leq 1100 \mu\text{s}$:

$$w_{3k} = 0$$

$1100 \mu\text{s} \leq t \leq \infty$:

$$p = \frac{225e^{-1.8}}{3000} e^{-2000(t-1100 \times 10^{-6})}$$

$$w_{3k} = 75 \times e^{-1.8} \times 10^{-3} \int_{1100 \times 10^{-6}}^{\infty} e^{-2000(t-1100 \times 10^{-6})} dt$$

$$= 37.5e^{-1.8} \times 10^{-6} = 37.5e^{-1.8} \mu\text{J}$$


$$w_{3k} = w_{3k}(0 - 800 \mu\text{s}) + w_{3k}(1100 \mu\text{s} - \infty)$$

$$= 37.5(1 - e^{-1.6}) + 37.5e^{-1.8} = 37.5(1 + e^{-1.8} - e^{-1.6}) \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.5)(15)^2 = 56.25 \mu\text{J}$$

$$\% \text{ dissipated} = \frac{37.5}{56.25}(1 + e^{-1.8} - e^{-1.6})(100) = 64.23\%$$

P8.62 [a]

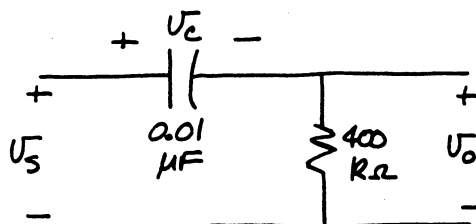

$$v_s = v_C + v_o; \quad \therefore v_o = v_s - v_C$$

$0 \leq t \leq 1 \text{ ms}$:

$$v_C(0) = 0 \text{ V}; \quad v_C(\infty) = 50 \text{ V}$$

$$\tau = (0.01)(400) \times 10^{-3} = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_C(t) = 50 - 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$$\therefore v_o(t) = 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$1 \text{ ms} \leq t \leq \infty$; $v_s = 0 \text{ V}$


$$v_C(1 \text{ ms}) = 50 - 50e^{-0.25} \cong 11.06 \text{ V}$$

$$v_C(\infty) = 0; \quad \tau = 4 \text{ ms}; \quad 1/\tau = 250$$


$$v_C = 0 + (11.06 - 0)e^{-250(t-0.001)} = 11.06e^{-250(t-0.001)} \text{ V}, \quad 1 \text{ ms} \leq t \leq \infty$$

$$\therefore v_o = 0 - 11.06e^{-250(t-0.001)} = -11.06e^{-250(t-0.001)} \text{ V}, \quad 1 \text{ ms} \leq t \leq \infty$$

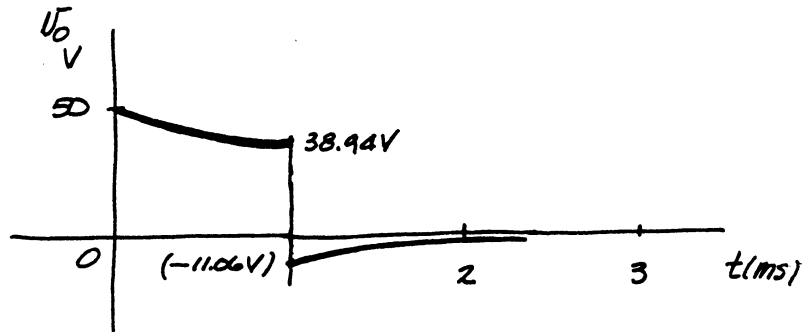[b] $v_o(1 \text{ ms}) = 50e^{-0.25} \cong 38.94 \text{ V}$



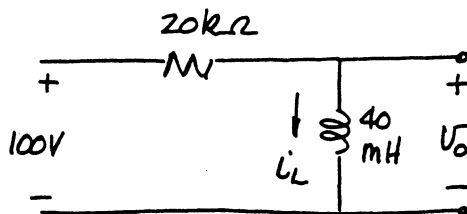P 8.63 [a] $0 \leq t \leq 2 \mu\text{s}$:




$$\begin{aligned} i_L(0) &= 0 \\ i_L(\infty) &= 5 \text{ mA} \\ \tau &= (40/20) \times 10^{-6} \\ &= 2 \mu\text{s} \end{aligned}$$

$$\therefore i_L = 5 - 5e^{-500,000t} \text{ mA}, \quad 0 \leq t \leq 2 \mu\text{s}$$

$$\begin{aligned} v_o &= 40 \times 10^{-3} [2,500,000 \times 10^{-3} e^{-500,000t}] = (40)(2.5)e^{-500,000t} \\ &= 100e^{-500,000t} \text{ V}, \quad 0^+ \leq t < 2 \mu\text{s} \end{aligned}$$

$$2 \mu\text{s} \leq t \leq \infty$$
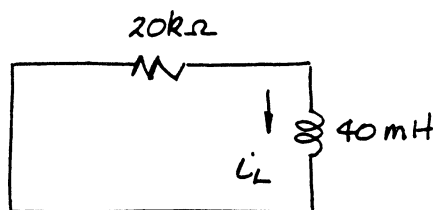
$$i_L(2 \mu\text{s}) = 5 - 5e^{-1} \cong 3.16 \text{ mA}$$



$$i_L(\infty) = 0; \quad \tau = 2 \mu\text{s}; \quad 1/\tau = 500,000$$

$$i_L = 0 + (3.16 - 0)e^{-500,000(t - 2 \times 10^{-6})} \text{ mA} = 3.16e^{-500,000(t - 2 \times 10^{-6})} \text{ mA},$$


$$2 \mu\text{s} \leq t \leq \infty$$

$$v_o = L \frac{di_L}{dt} = 40 \times 10^{-3} (3.16 \times 10^{-3}) (-5 \times 10^5) e^{-500,000(t - 2 \mu\text{s})}$$

$$= (-5)(4)(3.16)e^{-500,000(t - 2 \times 10^{-6})} \text{ V}$$

$$= -63.21e^{-500,000(t - 2 \times 10^{-6})} \text{ V}, \quad 2 \mu\text{s} < t \leq \infty$$

[b]

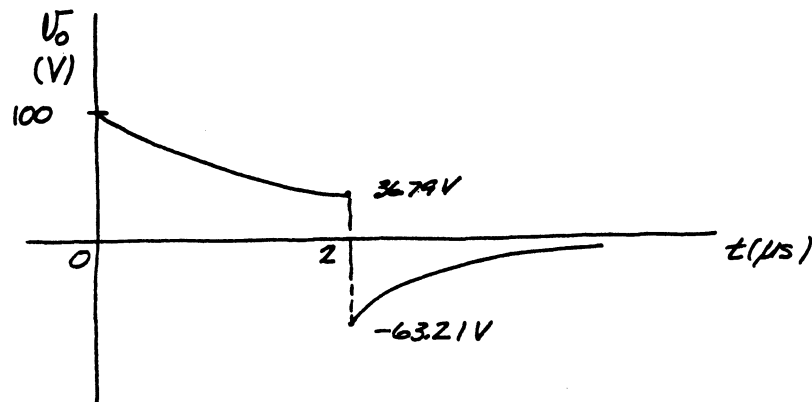

P 8.64 [a] $t < 0$; $v_o = 0$; $0 < t < 75 \mu s$:

$$i_o(0) = 0 \quad \tau = 125 \mu s$$

$$i_o(\infty) = 25 \text{ mA} \quad 1/\tau = 8000$$

$$i_o = 25 - 25e^{-8000t} \text{ mA}, \quad 0 \leq t \leq 75 \mu s$$

$$v_o = L \frac{di_o}{dt} = 0.25 \times (+200,000 \times 10^{-3})e^{-8000t}$$

$$= 50e^{-8000t} \text{ V}, \quad 0 < t < 75 \mu s$$

$75 \mu s < t < \infty$:

$$i_o(75 \mu s) = 25(1 - e^{-0.6}) \cong 11.28 \text{ mA}$$

$$i_o(\infty) = 0$$

$$\therefore i_o = 11.28e^{-8000(t-75 \times 10^{-6})} \text{ mA}, \quad 75 \mu s \leq t < \infty$$

$$v_o = 0.25(-90.24)e^{-8000(t-75 \times 10^{-6})}$$

$$= -22.56e^{-8000(t-75 \times 10^{-6})} \text{ V}, \quad 75 \mu s < t < \infty$$

[b] $v_o(75^-) = 50e^{-0.6} = 27.44 \text{ V}$


$$v_o(75^+) = -22.56 \text{ V}$$

[c] $i_o(75^-) = 11.28 \text{ mA}$

$$i_o(75^+) = 11.28 \text{ mA}$$

P 8.65 [a] $t < 0$; $i_o(t) = 0$; $v_o(t) = 0$

$0 \leq t \leq 2 \text{ ms}$:

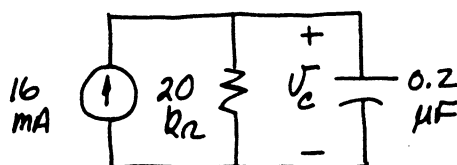

$$v_c(0^-) = 0$$

$$v_c(\infty) = 320 \text{ V}$$

$$\tau = 4 \text{ ms}$$

$$1/\tau = 250$$

$$\therefore v_C = 320 - 320e^{-250t} \text{ V}, \quad 0 \leq t \leq 2 \text{ ms}$$


$$i_o = C \frac{dv_C}{dt} = (0.2 \times 10^{-6})[80,000e^{-250t}] = 16e^{-250t} \text{ mA}, \quad 0 < t < 2 \text{ ms}$$

$$v_o = 4i_o + v_C = 64e^{-250t} + 320 - 320e^{-250t}$$

$$= 320 - 256e^{-250t} \text{ V}, \quad 0 < t < 2 \text{ ms}$$

$$2 \text{ ms} \leq t < \infty:$$
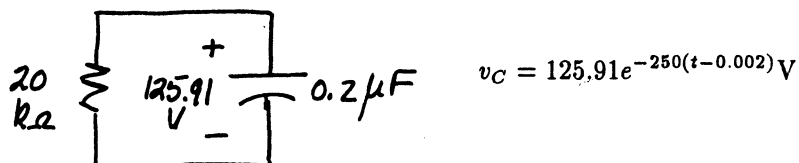
$$v_C(2 \text{ ms}) = 320 - 320e^{-0.5} \cong 125.91 \text{ V}$$



$$i_o = C \frac{dv_C}{dt} = (0.2 \times 10^{-6})(-31,477.55)e^{-250(t-0.002)}$$

$$= -6.30e^{-250(t-0.002)} \text{ mA}, \quad 2 \text{ ms} < t < \infty$$

$$v_o = 4i_o + v_C = (-25.18 + 125.91)e^{-250(t-0.002)}$$

$$= 100.73e^{-250(t-0.002)} \text{ V}, \quad 2 \text{ ms} < t < \infty$$

[b] $i_o(0^-) = 0; \quad i_o(0^+) = 16 \text{ mA}$

$$i_o(0.002^-) = 16e^{-0.5} = 9.7 \text{ mA}$$

$$i_o(0.002^+) = -6.30 \text{ mA}$$


[c] $v_o(0^+) = (16 \times 10^3)(4 \times 10^{-3}) = 64 \text{ V}$


$$v_o(0^-) = 0 \text{ V}$$

$$v_o(0.002^-) = 320 - 256e^{-0.5} = 164.73 \text{ V}$$

$$v_o(0.002^+) = 100.73 \text{ V}$$

[d]

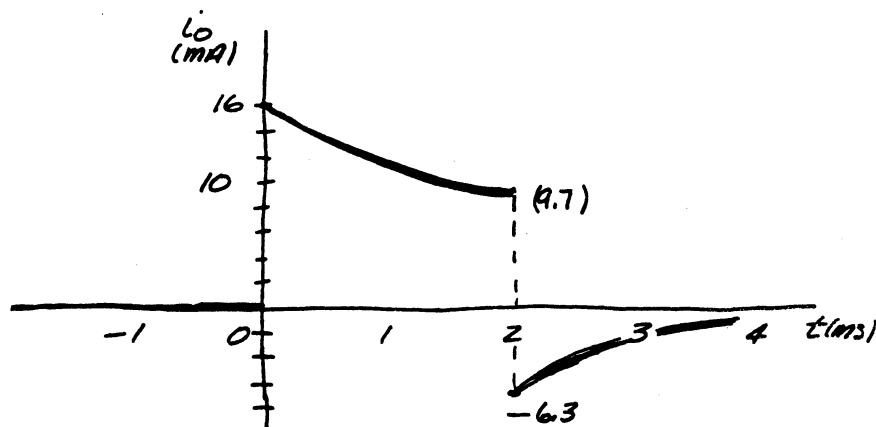

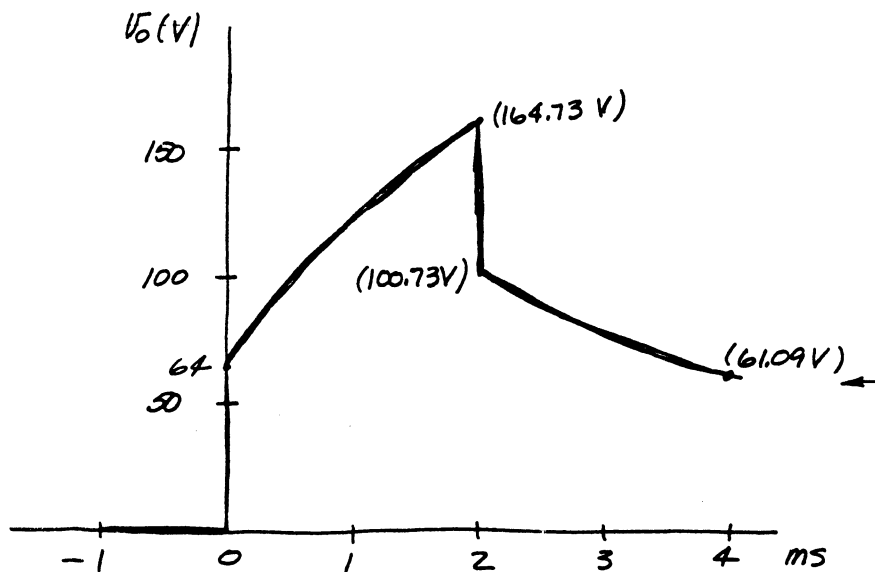

P8.66 [a] $t < 0$: $v_o = 0$

$0 \leq t \leq 4$ ms:

$$\tau = (200)(0.025) \times 10^{-3} = 5 \text{ ms}; \quad 1/\tau = 200$$

$$v_o = 100 - 100e^{-200t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100(1 - e^{-0.8}) = 55.07 \text{ V}$$

$4 \text{ ms} \leq t \leq 8 \text{ ms}$:


$$v_o = -100 + 155.07e^{-200(t-0.004)} \text{ V}$$

$$v_o(8 \text{ ms}) = -100 + 155.07e^{-0.8} = -30.32 \text{ V}$$

$8 \text{ ms} \leq t \leq \infty$:

$$v_o = -30.32e^{-200(t-0.008)} \text{ V}$$

[b]

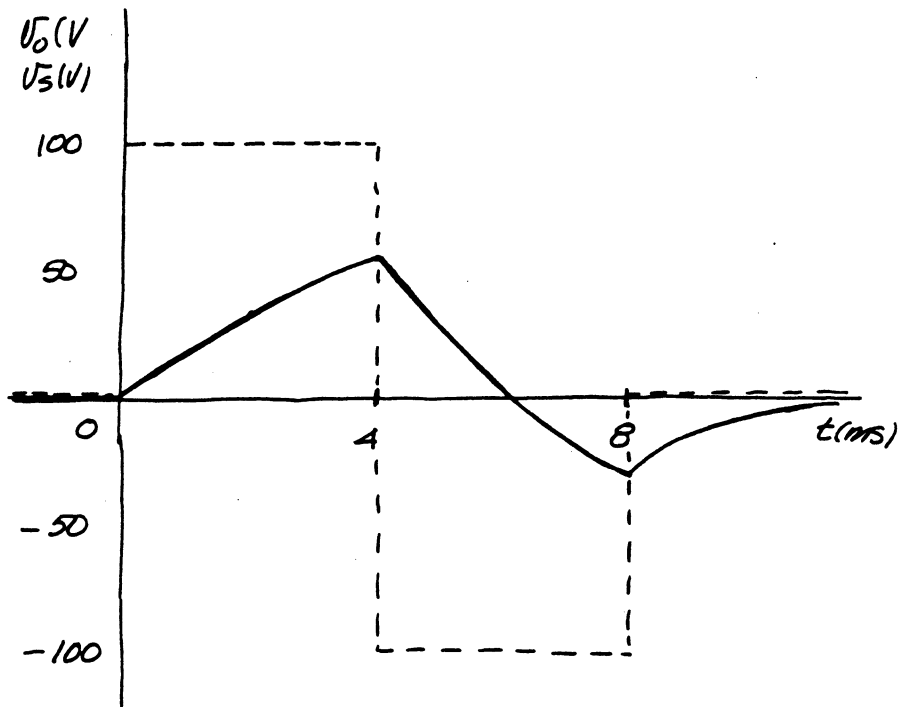[c] $t \leq 0$: $v_o = 0$ $0 \leq t \leq 4$ ms:

$$v_o = 100 - 100e^{-800t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100 - 100e^{-3.2} = 95.92 \text{ V}$$


 $4 \text{ ms} \leq t \leq 8$ ms:

$$v_o = -100 + 195.92e^{-800(t-0.004)} \text{ V}, \quad 4 \text{ ms} \leq t \leq 8 \text{ ms}$$


$$v_o(8 \text{ ms}) = -100 + 195.92e^{-3.2} = -92.01 \text{ V}$$

 $8 \text{ ms} \leq t \leq \infty$:
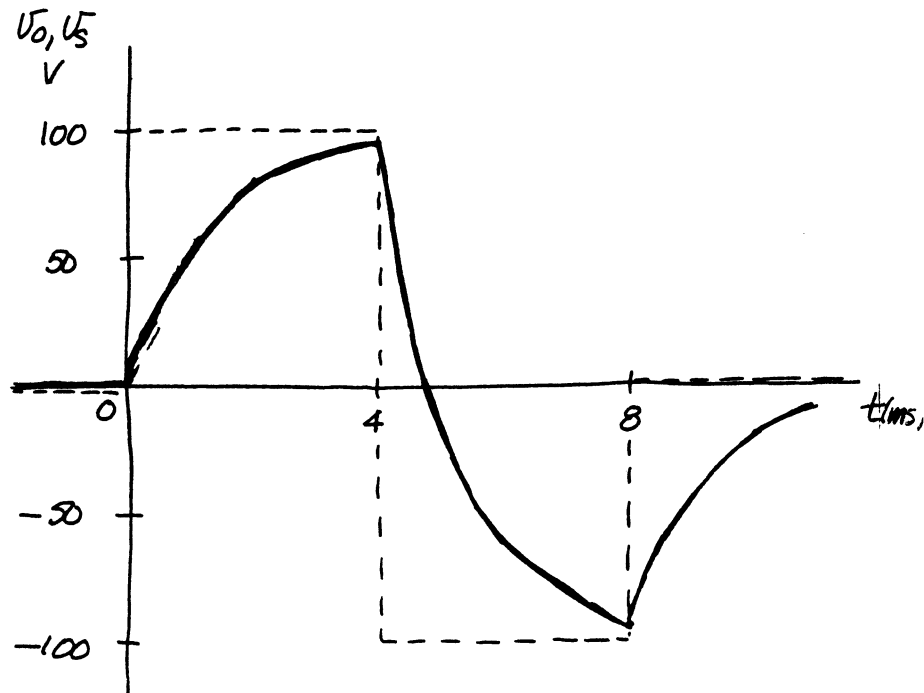
$$v_o = -92.01e^{-800(t-0.008)} \text{ V}, \quad 8 \text{ ms} \leq t \leq \infty$$



P8.67 [a]

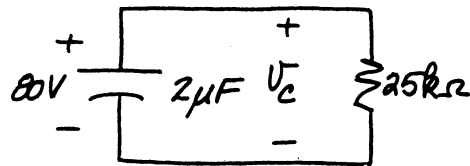


$$\begin{aligned}\tau &= (25)(2) \times 10^{-3} \\ &= 50 \text{ ms} \\ 1/\tau &= 20 \\ v_C(0^+) &= 80 \text{ V} \\ v_C(\infty) &= 0\end{aligned}$$

$$v_C = 80e^{-20t} \text{ V}$$

$$\therefore 80e^{-20t} = 5; \quad e^{20t} = 16; \quad t = 50 \ln 16 \text{ ms} = 138.63 \text{ ms}$$

[b] $0^+ < t < 138.63 \text{ ms}$:

$$i = (2 \times 10^{-6})(-1600e^{-20t}) = -3.2e^{-20t} \text{ mA}, \quad 0^+ \leq t < 138.63 \text{ ms}$$

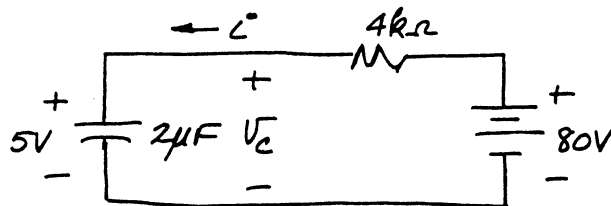 $138.63^+ \text{ ms} < t \leq \infty$:

$$\tau = (2)(4) \times 10^{-3} = 8 \text{ ms}; \quad 1/\tau = 125$$

$$v_C(138.63^+ \text{ ms}) = 5 \text{ V}; \quad v_C(\infty) = 80 \text{ V}$$

$$v_C = 80 - 75e^{-125(t-0.13863)} \text{ V}, \quad 138.63^+ \text{ ms} \leq t \leq \infty$$

$$i = 2 \times 10^{-6}(9375)e^{-125(t-0.13863)}$$


$$= 18.75e^{-125(t-0.13863)} \text{ mA}, \quad 138.63^+ \text{ ms} \leq t \leq \infty$$

$$[c] \quad 80 - 75e^{-125\Delta t} = 0.85(80) = 68$$

$$80 - 68 = 75e^{-125\Delta t} = 12$$

$$e^{125\Delta t} = 6.25; \quad \Delta t = 8 \ln 6.25 \text{ ms} \cong 14.66 \text{ ms}$$

P 8.68 [a] At $t = 0$ we have

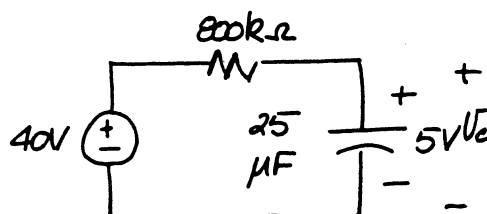

$$\begin{aligned} \tau &= (800)(25) \times 10^{-3} \\ &= 20 \text{ sec} \\ 1/\tau &= 0.05 \end{aligned}$$

$$v_C(\infty) = 40 \text{ V}; \quad v_C(0) = 5 \text{ V}$$


$$v_C = 40 - 35e^{-0.05t} \text{ V}, \quad 0 \leq t \leq t_o$$

$$40 - 35e^{-0.05t_o} = 15$$


$$\therefore e^{0.05t_o} = 1.4$$

$$t_o = 20 \ln 1.4 \text{ s} = 6.73 \text{ s}$$

At $t = t_o$ we have

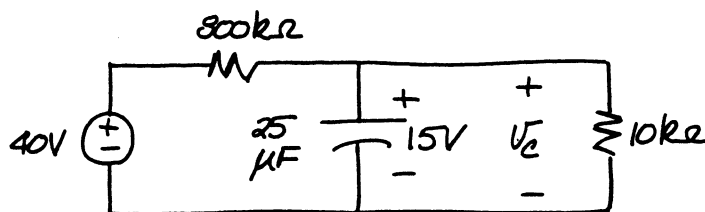

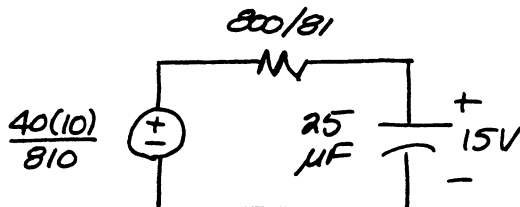The Thévenin equivalent with respect to the capacitor is



$$\tau = \left(\frac{800}{81}\right)(25) \times 10^{-3} = \frac{20}{81} \text{ s}; \quad \frac{1}{\tau} = \frac{81}{20} = 4.05$$

$$v_C(t_0) = 15 \text{ V}; \quad v_C(\infty) = \frac{40}{81} \text{ V}$$


$$v_C(t) = \frac{40}{81} + \left(15 - \frac{40}{81}\right)e^{-4.05(t-t_0)} \text{ V} = \frac{40}{81} + \frac{1175}{81}e^{-4.05(t-t_0)}$$

$$\therefore \frac{40}{81} + \frac{1175}{81}e^{-4.05(t-t_0)} = 5$$

$$\frac{1175}{81}e^{-4.05(t-t_0)} = \frac{365}{81}$$

$$e^{4.05(t-t_0)} = \frac{1175}{365} = 3.22$$

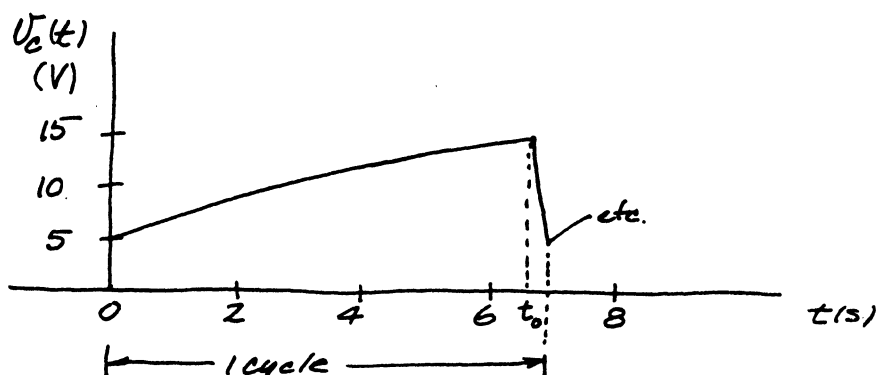
$$t - t_0 = \frac{1}{4.05} \ln 3.22 \cong 0.29 \text{ s}$$



One cycle = 7.02 seconds.

[b] $N = 60/7.02 = 8.55$ flashes per minute

[c] At $t = 0$ we have

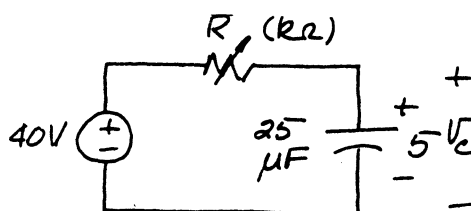

$$\tau = 25R \times 10^{-3}$$


$$1/\tau = 40/R$$

$$v_C = 40 - 35e^{-(40/R)t}$$

$$40 - 35e^{-(40/R)t_0} = 15$$

$$\therefore t_0 = \frac{R}{40} \ln 1.4, \quad R \text{ in } \text{k}\Omega$$

At $t = t_o$:

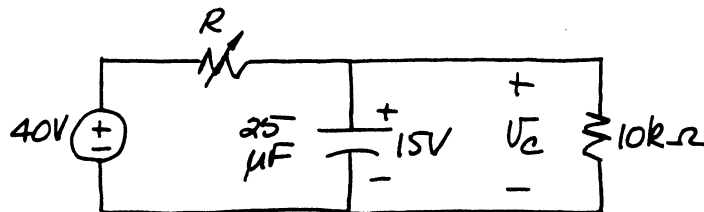

$$v_{Th} = \frac{10}{R+10}(40) = \frac{400}{R+10}; \quad R_{Th} = \frac{10R}{R+10} \text{ k}\Omega$$

$$\tau = \frac{(25)(10R) \times 10^{-3}}{R+10} = \frac{0.25R}{R+10}; \quad \frac{1}{\tau} = \frac{4(R+10)}{R}$$

$$v_C = \frac{400}{R+10} + \left(15 - \frac{400}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)}$$

$$\therefore \frac{400}{R+10} + \left[\frac{15R-250}{R+10}\right] e^{-\frac{4(R+10)}{R}(t-t_o)} = 5$$

$$\text{or } \left(\frac{15R-250}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)} = \frac{5R-350}{(R+10)}$$

$$\therefore e^{\frac{4(R+10)}{R}(t-t_o)} = \frac{3R-50}{R-70}$$

$$\therefore t - t_o = \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70} \right)$$

At 12 flashes per minute $t_o + (t - t_o) = 5 \text{ s}$

$$\therefore \underbrace{\frac{R}{40} \ln 1.4}_{\text{dominant term}} + \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70} \right) = 5$$

dominant
term


Start the trial-and-error procedure by setting $(R/40) \ln 1.4 = 5$, then $R = 200/(\ln 1.4)$ or $594.40 \text{ k}\Omega$. If $R = 594.40 \text{ k}\Omega$ then $t - t_o \cong 0.29 \text{ s}$.

Second trial set $(R/40) \ln 1.4 = 4.7 \text{ s}$ or $R = 558.74 \text{ k}\Omega$.

With $R = 558.74 \text{ k}\Omega$, $t - t_o \cong 0.30 \text{ s}$

$\therefore R = 558.74 \text{ k}\Omega$

P8.69

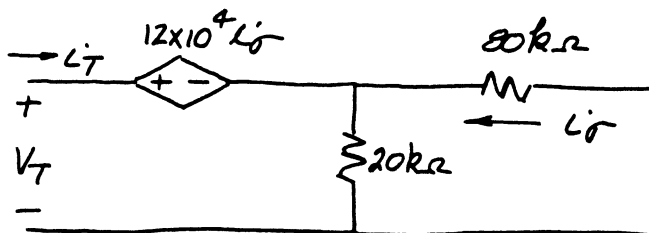

$$v_T = 12 \times 10^4 i_\sigma + 16 \times 10^3 i_T; \quad i_\sigma = -\frac{20}{100} i_T = -\frac{1}{5} i_T$$

$$v_T = -2.4 \times 10^4 i_T + 16 \times 10^3 i_T$$


$$\frac{v_T}{i_T} = R_{Th} = 16 \times 10^3 - 24 \times 10^3 = -8000 \Omega$$

$$\tau = (-8000)(2.5 \times 10^{-6}) = -20 \times 10^{-3}; \quad \frac{1}{\tau} = \frac{-1000}{20} = -50$$

$$v_C = 20e^{50t} \text{ V}, \quad t \geq 0$$

$$20e^{50t} = 20,000; \quad e^{50t} = 1000; \quad t = 20 \ln 1000 \text{ ms} = 138.16 \text{ ms}$$

P 8.70

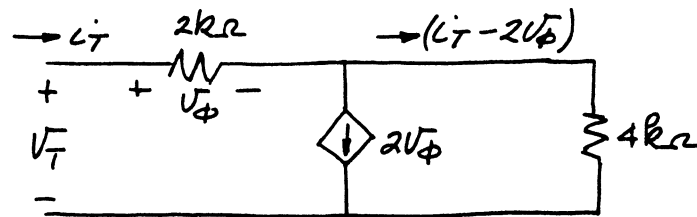

$$v_T = 2i_T + 4(i_T - 2v_\phi) = 6i_T - 8v_\phi = 6i_T - 8(2i_T) = -10i_T$$


$$R_{Th} = \frac{v_T}{i_T} = -10 \text{ k}\Omega$$

$$\tau = \frac{-10}{10 \times 10^3} = -10^{-3} = -1 \text{ ms}; \quad \frac{1}{\tau} = -1000$$

$$i_L(t) = 25e^{1000t} \text{ mA}, \quad t \geq 0$$

$$25e^{1000t} \times 10^{-3} = 5; \quad e^{1000t} = 200; \quad 1000t = \ln 200; \quad t = \ln 200 \text{ ms} = 5.30 \text{ ms}$$


P 8.71

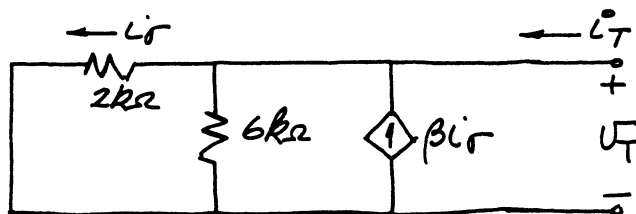

$$i_T = -\beta i_\sigma + \frac{v_T}{6} + \frac{v_T}{2} = -\beta \frac{v_T}{2} + \frac{v_T}{6} + \frac{v_T}{2} = \left[\left(\frac{1-\beta}{2} \right) + \frac{1}{6} \right] v_T = \left(\frac{4-3\beta}{6} \right) v_T$$

$$\therefore \frac{v_T}{i_T} = \frac{6}{4-3\beta} = -3$$

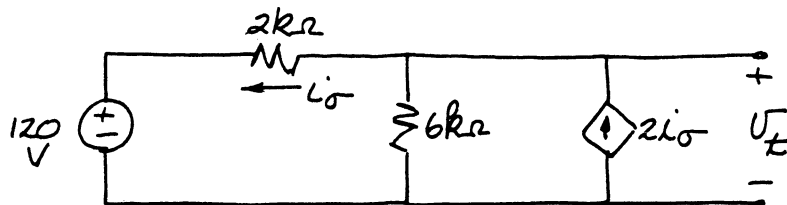
$$6 = -12 + 9\beta, \quad 9\beta = 18, \quad \beta = 2$$



$$\frac{v_T - 120}{2} + \frac{v_T}{6} - 2 \left(\frac{v_T - 120}{2} \right) = 0$$

$$3v_T - 360 + v_T - 6v_T + 720 = 0$$
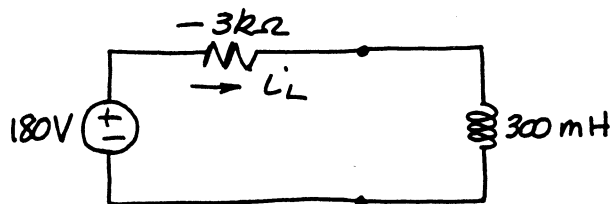
$$-2v_T + 360 = 0; \quad v_T = 180 \text{ V}$$



$$180 = -3000i_L + 0.3 \frac{di_L}{dt}$$

$$\frac{di_L}{dt} - 10^4 i_L = 600$$

$$\frac{di_L}{dt} = 10^4 (i_L + 0.06)$$

$$\frac{di_L}{i_L + 0.06} = 10^4 dt$$

$$\int_{i_L(0)}^{i_L(t)} \frac{dx}{x + 0.06} = \int_0^t 10^4 dy$$

$$\ln(x + 0.06) \Big|_{i_L(0)}^{i_L(t)} = 10^4 t$$

$$\ln \frac{[i_L(t) + 0.06]}{[i_L(0) + 0.06]} = 10^4 t$$

$$[i_L(t) + 0.06] = [i_L(0) + 0.06] e^{10^4 t}$$


$$i_L(t) = -0.06 + 0.06 e^{10^4 t}$$

$$v_L = 0.3 \frac{di_L}{dt} = 0.3 [600 e^{10^4 t}] = 180 e^{10^4 t} \text{ V}, \quad 0^+ \leq t \leq \infty$$

$$180 e^{10^4 t} = 36,000; \quad e^{10^4 t} = 200; \quad 10^4 t = \ln 200;$$

$$t = 10^{-4} \ln 200 = 100 \ln 200 \mu\text{s} \cong 529.83 \mu\text{s}$$

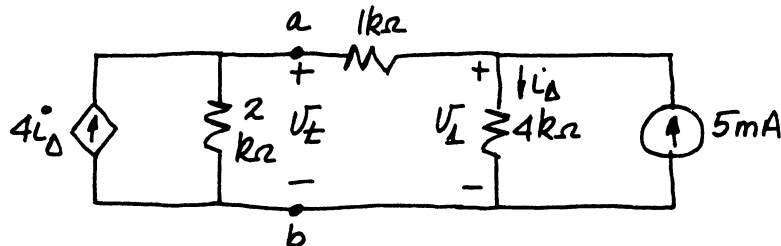P 8.72 First find the Thévenin equivalent with respect to the capacitor terminals.



$$-4\left(\frac{v_1}{4}\right) + \frac{v_{Th}}{2} + \frac{v_{Th} - v_1}{1} = 0$$

$$-4v_1 + 2v_{Th} + 4v_{Th} - 4v_1 = 0$$

$$6v_{Th} - 8v_1 = 0$$


$$\Delta = \begin{vmatrix} 6 & -8 \\ -4 & 5 \end{vmatrix} = 30 - 32 = -2$$

$$\frac{v_1}{4} + \frac{v_1 - v_{Th}}{1} = 5$$

$$N_{Th} = \begin{vmatrix} 0 & -8 \\ 20 & 5 \end{vmatrix} = 160$$

$$-4v_{Th} + 5v_1 = 20$$

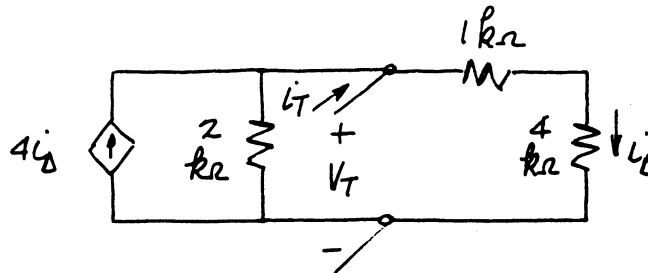
$$v_{Th} = \frac{N_{Th}}{\Delta} = -80 \text{ V}$$



$$i_T = \frac{v_T}{2} + \frac{v_T}{5} - 4\frac{v_T}{5}$$

$$\frac{i_T}{v_T} = \frac{1}{2} + \frac{1}{5} - \frac{4}{5} = \frac{1}{2} - \frac{3}{5} = \frac{5}{10} - \frac{6}{10} = -\frac{1}{10} \text{ millimho}$$
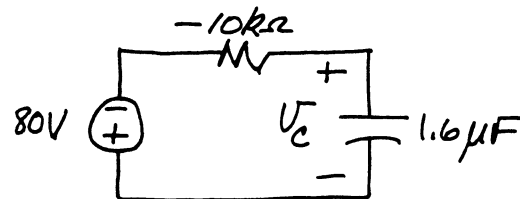
$$R_{Th} = \frac{v_T}{i_T} = -10 \text{ k}\Omega$$



$$1.6 \times 10^{-6} \frac{dv_C}{dt} + \frac{v_C + 80}{-10,000} = 0$$

$$\frac{dv_C}{dt} - 62.5v_C - 5000 = 0$$

$$\frac{dv_C}{dt} = 62.5(v_C + 80)$$

$$\frac{dv_C}{v_C + 80} = 62.5 dt$$

$$\therefore v_C = -80 + 80e^{62.5t} \text{ V}, \quad 0 \leq t \leq \infty$$

$$\therefore -80 + 80e^{62.5t} = 14,400; \quad 80e^{62.5t} = 14,400; \quad e^{62.5t} = 181;$$

$$62.5t = \ln 181; \quad t = 16 \ln 181 \text{ ms} \cong 83.18 \text{ ms}$$

$$\begin{aligned}\text{P 8.73} \quad v_o &= -\frac{10^6}{0.5R} \int_0^t 4 \, dx + 0 = (-10^6) \frac{8}{R} t \\ \therefore -10 &= \frac{-8 \times 10^6}{R} (15) \times 10^{-3}; \quad \therefore R = (8)(15) \times 10^2 = 12 \, \text{k}\Omega\end{aligned}$$

$$\begin{aligned}\text{P 8.74} \quad v_o &= \frac{-8 \times 10^6 t}{R} - 6 \\ \therefore -10 &= \frac{-8 \times 10^6 (40) \times 10^{-3}}{R} - 6; \quad \therefore \frac{32 \times 10^4}{R} = 4; \quad R = 8 \times 10^4 = 80 \, \text{k}\Omega\end{aligned}$$

$$\begin{aligned}\text{P 8.75} \quad v_o &= \frac{-10^3}{200(0.2)} \int_0^t -10 \, dx + 0 = 250t \\ v_o(32 \, \text{ms}) &= (250)(32) \times 10^{-3} = 8 \, \text{V} \\ v_o &= \frac{-10^3}{(250)(0.2)} \int_{32 \times 10^{-3}}^t 5 \, dx + 8 = -100t + 11.2 \, \text{V} \\ \therefore -15 &= -100t + 11.2; \quad t = 262 \, \text{ms}\end{aligned}$$

$$\begin{aligned}\text{P 8.76} \quad v_2 &= \frac{-45}{100}(80) = -36 \, \text{V} = v_1 \\ \frac{-36 - 14}{80 \times 10^3} + 2.5 \times 10^{-6} \frac{d}{dt}(-36 - v_o) &= 0 \\ \therefore -2.5 \times 10^{-6} \frac{dv_o}{dt} &= 6.25 \times 10^{-4}; \quad \frac{dv_o}{dt} = -2.5 \times 10^2 = -250; \quad dv_o = -250 \, dt \\ \int_{v_o(0)}^{v_o(t)} dx &= -250 \int_0^t dy; \quad v_o(t) - v_o(0) = -250t; \quad v_o(0) = -36 + 56 = 20 \, \text{V} \\ \therefore v_o(t) &= -250t + 20; \quad 0 = -250t + 20; \quad 250t = 20; \quad t = 80 \, \text{ms}\end{aligned}$$

$$\begin{aligned}\text{P 8.77} \quad [\text{a}] \quad \frac{v_1}{10} + \frac{v_1 - v_o}{40} &= 0 \\ 5v_1 = v_o = 5v_2; \quad v_2 &= -2 + 2e^{-625t} \, \text{V} \\ \therefore v_o &= -10 + 10e^{-625t} \, \text{V}, \quad 0 \leq t \leq t_{\text{sat}} \\ \therefore -5 &= -10 + 10e^{-625t_{\text{sat}}} \\ \therefore e^{625t_{\text{sat}}} &= 2; \quad t_{\text{sat}} = 1.6 \ln 2 \, \text{ms} = 1.11 \, \text{ms}\end{aligned}$$

$$\begin{aligned}[\text{b}] \quad v_2 &= -2 + 3e^{-625t} \\ v_o = 5v_2 &= -10 + 15e^{-625t}, \quad 0 \leq t \leq t_{\text{sat}} \\ -5 &= -10 + 15e^{-625t_{\text{sat}}} \\ t_{\text{sat}} &= 1.6 \ln 3 \, \text{ms} = 1.76 \, \text{ms}\end{aligned}$$

$$\begin{aligned}\text{P 8.78} \quad [\text{a}] \quad \frac{C dv_2}{dt} + \frac{v_2 - v_b}{R} &= 0; \quad \text{therefore} \quad \frac{dv_2}{dt} + \frac{1}{RC} v_2 = \frac{v_b}{RC} \\ \frac{v_1 - v_a}{R} + C \frac{d(v_1 - v_o)}{dt} &= 0; \quad \text{therefore} \quad \frac{dv_o}{dt} = \frac{dv_1}{dt} + \frac{v_1}{RC} - \frac{v_a}{RC}\end{aligned}$$

But $v_1 = v_2$

$$\text{Therefore } \frac{dv_1}{dt} + \frac{v_1}{RC} = \frac{dv_2}{dt} + \frac{v_2}{RC} = \frac{v_b}{RC}$$

$$\text{Therefore } \frac{dv_o}{dt} = \frac{1}{RC}(v_b - v_a); \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy$$

[b] The output is the integral of the difference between v_b and v_a and then scaled by a factor of $1/RC$.

$$[c] \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx$$

$$RC = (40) \times 10^3 (25) \times 10^{-9} = 1000 \times 10^{-6} = 10^{-3}$$

$$v_b - v_a = (60 - 10)10^{-3} = 50 \times 10^{-3}$$

$$v_o = 50 \int_0^t dx = 50t; \quad 50t_{\text{sat}} = 12; \quad t_{\text{sat}} = 0.24 \text{ s} = 240 \text{ ms}$$

$$\mathbf{P 8.79} \quad RC = (100 \times 10^3)(0.05 \times 10^{-6}) = 5 \times 10^{-3}; \quad \frac{1}{RC} = 200; \quad v_o(0) = -4 + 12 = 8 \text{ V}$$

$$v_o = 200 \int_0^t (-15 + 7) dx + v_o(0) = -1600t + 8 \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

$$v_2 = -15 + (-4 + 15)e^{-200t} = -15 + 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

$$v_f + v_2 = v_o$$

$$v_f = v_o - v_2 = -1600t + 8 + 15 - 11e^{-200t}$$

$$v_f = 23 - 11e^{-200t} - 1600t \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

$$\text{Note: } -1600t_{\text{sat}} + 8 = -20; \quad \therefore t_{\text{sat}} = \frac{-28}{-1600} = 17.5 \text{ ms}$$

$$\mathbf{P 8.80} \quad 0 \leq t \leq 20 \text{ ms:}$$

$$RC = (25 \times 10^3)(0.8 \times 10^{-6}) = 20 \times 10^{-3}; \quad \frac{1}{RC} = 50; \quad v_o(0) = 0$$

$$v_o = -50 \int_0^t -10 dx + 0 = 500t, \quad 0 \leq t \leq 20 \text{ ms}$$

$$v_o(20 \text{ ms}) = (500)(20) \times 10^{-3} = 10 \text{ V}$$

$$20 \text{ ms} \leq t \leq t_{\text{sat}}:$$

$$RC = (100)(0.80) \times 10^{-3} = 80 \text{ ms}; \quad \frac{1}{RC} = 12.5$$

$$v_o = -12.5 \int_{20 \text{ ms}}^t 20 dx + 10 = -250(t - 0.02) + 10$$

$$= -250t + 15 \text{ V}, \quad 20 \text{ ms} \leq t \leq t_{\text{sat}}$$

$$-250t_{\text{sat}} + 15 = -20; \quad -250t_{\text{sat}} = -35; \quad t_{\text{sat}} = 140 \text{ ms}$$

$$v_o = -250t + 15 \text{ V}, \quad 20 \text{ ms} \leq t \leq 140 \text{ ms}$$

P 8.81 $R_f C_f = (24) \left(\frac{1}{3} \right) \times 10^{-3} = 8 \text{ ms}; \quad \frac{1}{R_f C_f} = 125$

$$v_o(0) = -5 \text{ V}; \quad v_o(\infty) = -\frac{24}{3}(-4) = 32 \text{ V}$$

$$v_o(t) = 32 - 37e^{-125t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

$$12 = 32 - 37e^{-125t_{\text{sat}}}$$

$$\therefore e^{125t_{\text{sat}}} = \frac{37}{20} = 1.85; \quad t_{\text{sat}} = 8 \ln 1.85 \text{ ms} = 4.92 \text{ ms}$$

P 8.82 [a] $RC = 25(0.4) \times 10^{-3} = 10 \text{ ms}; \quad \frac{1}{RC} = 100; \quad v_o = 0, \quad t < 0$

[b] $0 \leq t \leq 250 \text{ ms}:$

$$v_o = -100 \int_0^t -0.20 \, dx = 20t \text{ V}$$

[c] $250 \text{ ms} \leq t \leq 500 \text{ ms}:$


$$v_o(0.25) = 20(0.25) = 5 \text{ V}$$

$$v_o(t) = -100 \int_{0.25}^t 0.20 \, dx + 5 = -20(t - 0.25) + 5 = -20t + 10 \text{ V}$$

[d] $500 \text{ ms} \leq t \leq \infty:$

$$v_o(0.5) = -10 + 10 = 0 \text{ V}$$

$$v_o(t) = 0 \text{ V}$$

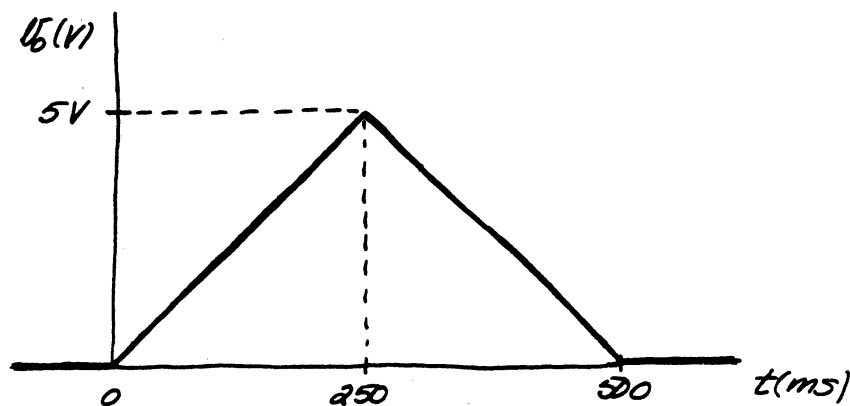


P 8.83 [a] $v_o = 0, \quad t < 0$

[b] $R_f C_f = (5 \times 10^6)(0.4 \times 10^{-6}) = 2; \quad \frac{1}{R_f C_f} = 0.5$

$$v_o = \frac{-5 \times 10^6}{25 \times 10^3}(-0.2)[1 - e^{-0.5t}] = 40(1 - e^{-0.5t}) \text{ V}, \quad 0 \leq t \leq 250 \text{ ms}$$

$$\begin{aligned}
 [c] \quad v_o(0.25) &= 40(1 - e^{-0.125}) \cong 4.70 \text{ V} \\
 v_o &= \frac{-V_m R_f}{R_s} + \frac{V_m R_f}{R_s} (2 - e^{-0.125}) e^{-0.5(t-0.25)} \\
 &= -40 + 40(2 - e^{-0.125}) e^{-0.5(t-0.25)} \\
 &= -40 + 44.70 e^{-0.5(t-0.25)} \text{ V}, \quad 250 \text{ ms} \leq t \leq 500 \text{ ms} \\
 [d] \quad v_o(0.50) &= -40 + 44.70 e^{-0.125} \cong -0.55 \text{ V} \\
 v_o &= -0.55 e^{-0.5(t-0.5)} \text{ V}, \quad 500 \text{ ms} \leq t \leq \infty
 \end{aligned}$$

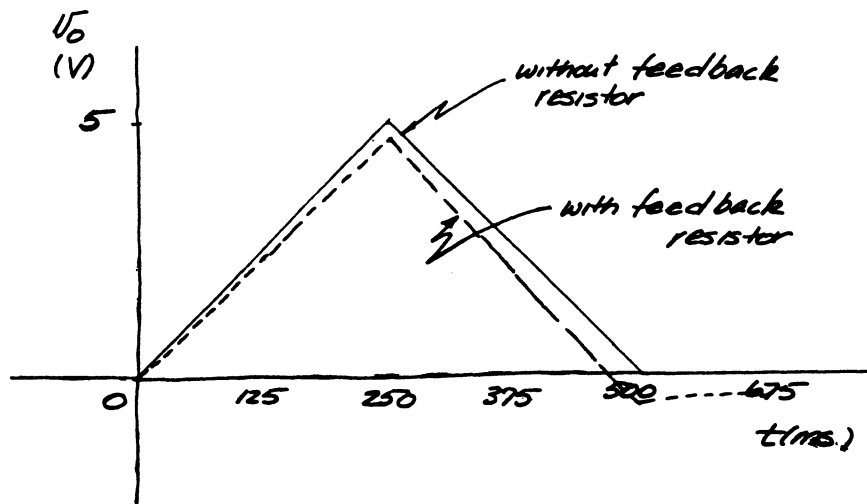

P 8.84 [a] $R_f C_f = (400 \times 10^3)(0.05 \times 10^{-6}) = 20 \text{ ms}; \quad \frac{1}{R_f C_f} = 50; \quad \frac{R_f}{R_s} = 12.5$

$$0 \leq t \leq 2 \text{ ms:}$$

$$v_o = -125(1 - e^{-50t}) \text{ V}, \quad 0 \leq t \leq 2 \text{ ms}$$

$$v_o(2 \text{ ms}) = -125(1 - e^{-0.10}) \cong -11.90 \text{ V}$$

$$2 \text{ ms} \leq t \leq \infty:$$

$$v_o(\infty) = -(-8)(12.5) = 100 \text{ V}$$

$$\therefore v_o = 100 - 111.90 e^{-50(t-0.002)} \text{ V}$$

$$\therefore v_o = 0 \text{ when } 100 = 111.90 e^{-50(t_o-0.002)}$$

$$\text{or } e^{50(t_o-0.002)} = 1.119$$

$$50(t_o - 0.002) = \ln 1.119$$

$$t_o = 0.002 + 0.02 \ln 1.119$$

$$t_o = 2 + 20 \ln 1.119 \text{ ms} = 4.25 \text{ ms}$$

[b] Saturation will occur when $v_o = 15 \text{ V}$.

$$\therefore 100 - 111.90 e^{-50(t_{\text{sat}}-0.002)} = 15$$

$$\therefore 111.90 e^{-50(t_{\text{sat}}-0.002)} = 85; \quad e^{50(t_{\text{sat}}-0.002)} = \frac{111.90}{85}; \quad t_{\text{sat}} = 7.5 \text{ ms}$$

P 8.85 [a] $0 \leq t \leq 1 \mu\text{s}$:

$$RC = (1000)(800) \times 10^{-12} = 8 \times 10^{-7}$$

$$\frac{1}{RC} = 1,250,000 = 125 \times 10^4$$

$$v_g = 2 \times 10^6 t, \quad 0 \leq t \leq 1 \mu\text{s}$$

$$\begin{aligned} \therefore v_o &= -125 \times 10^4 \int_0^t 2 \times 10^6 x \, dx + 0 = -250 \times 10^{10} \frac{x^2}{2} \Big|_0^t \\ &= -125 \times 10^{10} t^2, \quad 0 \leq t \leq 1 \mu\text{s} \end{aligned}$$

$1 \mu\text{s} \leq t \leq 3 \mu\text{s}$:

$$v_g = 4 - 2 \times 10^6 t \, \text{V}, \quad 1 \mu\text{s} \leq t \leq 3 \mu\text{s}$$

$$v_o(1 \mu\text{s}) = -125 \times 10^{10} \times 10^{-12} = -1.25 \, \text{V}$$

$$\begin{aligned} \therefore v_o &= -125 \times 10^4 \int_{10^{-6}}^t (4 - 2 \times 10^6 x) \, dx - 1.25 \\ &= -125 \times 10^4 \left[4x \Big|_{10^{-6}}^t - 2 \times 10^6 \frac{x^2}{2} \Big|_{10^{-6}}^t \right] - 1.25 \\ &= -125 \times 10^4 [4t - 4 \times 10^{-6} - 10^6(t^2 - 10^{-12})] - 1.25 \\ &= -500 \times 10^4 t + 500 \times 10^{-2} + 125 \times 10^{10} t^2 - 1.25 - 1.25 \\ &= 125 \times 10^{10} t^2 - 5 \times 10^6 t + 2.5 \, \text{V}, \quad 1 \mu\text{s} \leq t \leq 3 \mu\text{s} \end{aligned}$$

$3 \mu\text{s} \leq t \leq 4 \mu\text{s}$:

$$v_g = -8 + 2 \times 10^6 t \, \text{V}, \quad 3 \mu\text{s} \leq t \leq 4 \mu\text{s}$$

$$v_o(3 \mu\text{s}) = 125 \times 10^{10} (9 \times 10^{-12}) - 5 \times 10^6 (3 \times 10^{-6}) + 2.5 = -1.25 \, \text{V}$$

$$\begin{aligned} \therefore v_o &= -125 \times 10^4 \int_{3 \times 10^{-6}}^t [-8 + 2 \times 10^6 x] \, dx - 1.25 \\ &= -125 \times 10^4 \left[-8x \Big|_{3 \times 10^{-6}}^t + 10^6 x^2 \Big|_{3 \times 10^{-6}}^t \right] - 1.25 \\ &= -125 \times 10^4 [-8(t - 3 \times 10^{-6}) + 10^6(t^2 - 9 \times 10^{-12})] - 1.25 \\ &= 1000 \times 10^4 t - 30 - 125 \times 10^{10} t^2 + 11.25 - 1.25 \\ v_o &= -125 \times 10^{10} t^2 + 10^7 t - 20, \quad 3 \mu\text{s} \leq t \leq 4 \mu\text{s} \end{aligned}$$

[b]

$$v_o(0) = 0$$

$$v_o(0.5 \mu\text{s}) = -0.3125 \, \text{V}$$

$$v_o(1.0 \mu\text{s}) = -1.25 \, \text{V}$$

$$v_o(1.5 \mu\text{s}) = -2.1875 \, \text{V}$$


$$v_o(2.0 \mu\text{s}) = -2.50 \, \text{V}$$

$$v_o(2.5 \mu\text{s}) = -2.1875 \, \text{V}$$

$$v_o(3 \mu\text{s}) = -1.25 \, \text{V}$$


$$v_o(3.5 \mu\text{s}) = -0.3125 \, \text{V}$$

$$v_o(4.0 \mu\text{s}) = 0$$

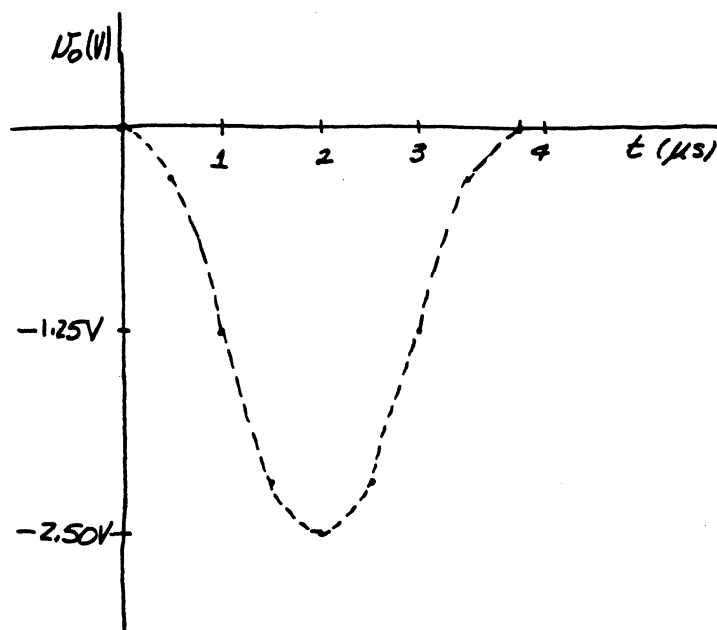


- [c] The output voltage will also repeat. This follows from the observation that at $t = 4 \mu s$ the output voltage is zero, hence there is no energy stored in the capacitor. This means the circuit is in the same state at $t = 4 \mu s$ as it was at $t = 0$, thus as v_g repeats itself so will v_o .

P 8.86 [a] While T_2 has been ON, C_2 is charged to V_{CC} , positive on the left terminal. At the instant T_1 turns ON the capacitor C_2 is connected across $b_2 - e_2$, thus $v_{be2} = -V_{CC}$. This negative voltage snaps T_2 OFF. Now the polarity of the voltage on C_2 starts to reverse, that is, the right-hand terminal of C_2 starts to charge toward $+V_{CC}$. At the same time, C_1 is charging toward V_{CC} , positive on the right. At the instant the charge on C_2 reaches zero, v_{be2} is zero, T_2 turns ON. This makes $v_{be1} = -V_{CC}$ and T_1 snaps OFF. Now the capacitors C_1 and C_2 start to charge with the polarities to turn T_1 ON and T_2 OFF. This switching action repeats itself over and over as long as the circuit is energized. At the instant T_1 turns ON, the voltage controlling the state of T_2 is governed by the following circuit:

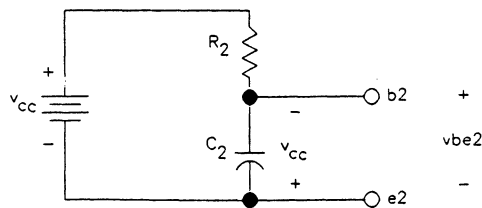


It follows that $v_{be2} = V_{CC} - 2V_{CC}e^{-t/R_2C_2}$.

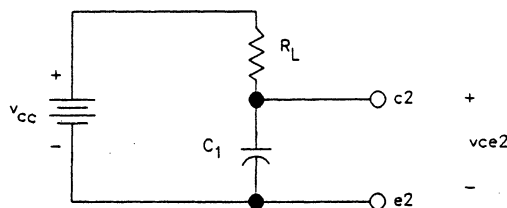- [b] While T_2 is OFF and T_1 is ON, the output voltage v_{ce2} is the same as the voltage across C_1 , thus



It follows that $v_{ce2} = V_{CC} - V_{CC}e^{-t/R_L C_1}$.

- [c] T_2 will be OFF until v_{be2} reaches zero. As soon as v_{be2} is zero, i_{b2} will become positive and turn T_2 ON. $v_{be2} = 0$ when $V_{CC} - 2V_{CC}e^{-t/R_2 C_2} = 0$, or when $t = R_2 C_2 \ln 2$.
- [d] When $t = R_2 C_2 \ln 2$, we have
- $$v_{ce2} = V_{CC} - V_{CC}e^{-[(R_2 C_2 \ln 2)/(R_L C_1)]} = V_{CC} - V_{CC}e^{-10 \ln 2} \cong V_{CC}$$
- [e] Before T_1 turns ON, i_{b1} is zero. At the instant T_1 turns ON, we have

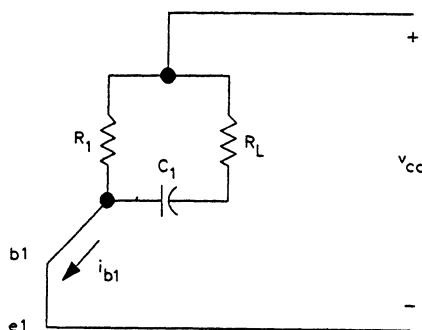


$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L} e^{-t/R_L C_1}$$

- [f] At the instant T_2 turns back ON, $t = R_2 C_2 \ln 2$; therefore


$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L} e^{-10 \ln 2} \cong \frac{V_{CC}}{R_1}$$

When T_2 turns OFF, i_{b1} drops to zero instantaneously.

- [g]

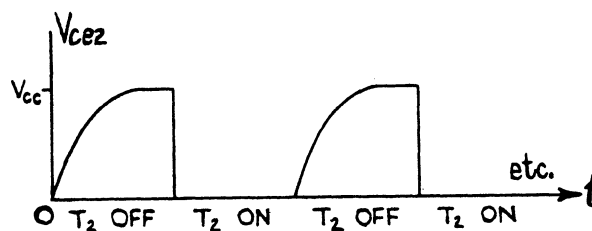

[h]

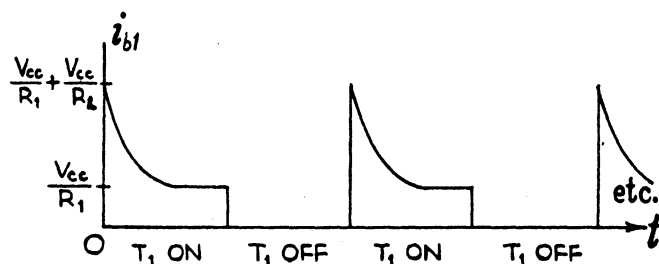

P 8.87 [a] $t_{\text{OFF}2} = R_2 C_2 \ln 2 = 14.43 \times 10^3 (10^{-9}) \ln 2 \cong 10 \mu\text{s}$

[b] $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

[c] $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

[d] $t_{\text{ON}1} = R_2 C_2 \ln 2 \cong 10 \mu\text{s}$

[e] $i_{b1} = \frac{10}{1} + \frac{10}{14.43} = 10.693 \text{ mA}$

[f] $i_{b1} = \frac{10}{14.43} + \frac{10}{1} e^{-10} \cong 0.693 \text{ mA}$

[g] $v_{ce2} = 10 - 10e^{-10} \cong 10 \text{ V}$

P 8.88 [a] $t_{\text{OFF}2} = R_2 C_2 \ln 2 = (14.34 \times 10^3)(0.8 \times 10^{-9}) \ln 2 \cong 8 \mu\text{s}$

[b] $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

[c] $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 10 \mu\text{s}$

[d] $t_{\text{ON}1} = R_2 C_2 \ln 2 = 8 \mu\text{s}$

[e] $i_{b1} = 10.693 \text{ mA}$

[f] $i_{b1} = \frac{10}{14.43} + 10e^{-8} \cong 0.693 \text{ mA}$

[g] $v_{ce2} = 10 - 10e^{-8} \cong 10 \text{ V}$

Note in this circuit T_2 is OFF $8 \mu\text{s}$ and ON $10 \mu\text{s}$ of every cycle, whereas T_1 is ON $8 \mu\text{s}$ and OFF $10 \mu\text{s}$ every cycle.

P 8.89 If $R_1 = R_2 = 50R_L = 100 \text{ k}\Omega$, then

$$C_1 = \frac{48 \times 10^{-6}}{100 \times 10^3 \ln 2} = 692.49 \text{ pF}; \quad C_2 = \frac{36 \times 10^{-6}}{100 \times 10^3 \ln 2} = 519.37 \text{ pF}$$

If $R_1 = R_2 = 6R_L = 12 \text{ k}\Omega$, then

$$C_1 = \frac{48 \times 10^{-6}}{12 \times 10^3 \ln 2} = 5.77 \text{ nF}; \quad C_2 = \frac{36 \times 10^{-6}}{12 \times 10^3 \ln 2} = 4.33 \text{ nF}$$


Therefore $692.49 \text{ pF} \leq C_1 \leq 5.77 \text{ nF}$ and $519.37 \text{ pF} \leq C_2 \leq 4.33 \text{ nF}$

- P 8.90** [a] T_2 is normally ON since its base current i_{b2} is greater than zero, i.e., $i_{b2} = V_{CC}/R$ when T_2 is ON. When T_2 is ON, $v_{ce2} = 0$, therefore $i_{b1} = 0$. When $i_{b1} = 0$, T_1 is OFF. When T_1 is OFF and T_2 is ON, the capacitor C is charged to V_{CC} , positive at the left terminal. This is a stable state; there is nothing to disturb this condition if the circuit is left to itself.
- [b] When S is closed momentarily, v_{be2} is changed to $-V_{CC}$ and T_2 snaps OFF. The instant T_2 turns OFF, v_{ce2} jumps to $V_{CC}R_1/(R_1 + R_L)$ and i_{b1} jumps to $V_{CC}/(R_1 + R_L)$, which turns T_1 ON.
- [c] As soon as T_1 turns ON, the charge on C starts to reverse polarity. Since v_{be2} is the same as the voltage across C , it starts to increase from $-V_{CC}$ toward $+V_{CC}$. However, T_2 turns ON as soon as $v_{be2} = 0$. The equation for v_{be2} is $v_{be2} = V_{CC} - 2V_{CC}e^{-t/RC}$. $v_{be2} = 0$ when $t = RC \ln 2$, therefore T_2 stays OFF for $RC \ln 2$ seconds.


- P 8.91** [a] For $t < 0$, $v_{ce2} = 0$. When the switch is momentarily closed, v_{ce2} jumps to

$$v_{ce2} = \left(\frac{V_{CC}}{R_1 + R_L} \right) R_1 = \frac{6(5)}{25} = 1.2 \text{ V}$$

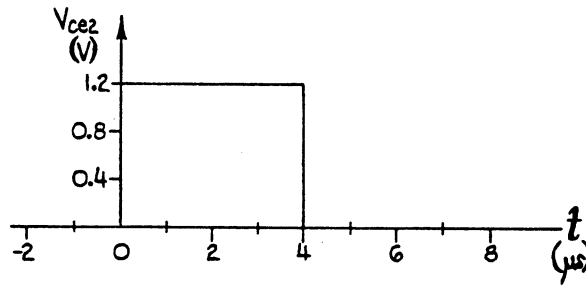T_2 remains open for $(23,083)(250) \times 10^{-12} \ln 2 \cong 4 \mu\text{s}$.



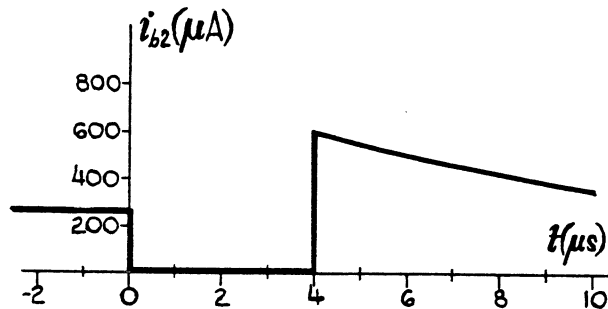- [b] $i_{b2} = \frac{V_{CC}}{R} = 259.93 \mu\text{A}, \quad -5 \leq t \leq 0 \mu\text{s}$
 $i_{b2} = 0, \quad 0 < t < RC \ln 2$
 $i_{b2} = \frac{V_{CC}}{R} + \frac{V_{CC}}{R_L} e^{-(t - RC \ln 2)/R_L C}$
 $= 259.93 + 300e^{-0.2 \times 10^6 (t - 4 \times 10^{-6})} \mu\text{A}, \quad RC \ln 2 < t$



Natural and Step Responses of RLC Circuits

Drill Exercises

DE 9.1 [a] $\frac{1}{(2RC)^2} = \frac{1}{LC}$, therefore $C = 62.5 \text{ nF}$

[b] $\alpha = 10^4 = \frac{1}{2RC}$, therefore $C = 0.25 \mu\text{F} = 250 \text{ nF}$
 $s_{1,2} = -10^4 \pm \sqrt{10^8 - \frac{(10^3)(10^6)}{2.5}} = (-10^4 \pm j17,320.51) \text{ rad/s}$

[c] $\frac{1}{\sqrt{LC}} = 50,000$, therefore $C = 0.04 \mu\text{F} = 40 \text{ nF}$
 $s_{1,2} = [-62.5 \pm \sqrt{(62.5)^2 - 50^2}] 10^3$,
 $s_1 = -25 \text{ krad/s}$, $s_2 = -100 \text{ krad/s}$

DE 9.2 $i_L = \frac{1000}{50} \int_0^t [-14e^{-5000x} + 26e^{-20,000x}] dx + 30 \times 10^{-3}$
 $= 20 \left\{ \frac{-14e^{-5000x}}{-5000} \Big|_0^t + \frac{26e^{-20,000x}}{-20,000} \Big|_0^t \right\} + 30 \times 10^{-3}$
 $= 56 \times 10^{-3}(e^{-5000t} - 1) - 26 \times 10^{-3}(e^{-20,000t} - 1) + 30 \times 10^{-3}$
 $= [56e^{-5000t} - 56 - 26e^{-20,000t} + 26 + 30] \text{ mA}$
 $= 56e^{-5000t} - 26e^{-20,000t} \text{ mA}, \quad t \geq 0$

DE 9.3 From the given values of R , L , and C , $s_1 = -10 \text{ krad/s}$ and $s_2 = -40 \text{ krad/s}$.

[a] $v(0^-) = v(0^+) = 0$, therefore $i_R(0^+) = 0$

[b] $i_C(0^+) = 4 \text{ A}$

$$\begin{aligned}
[\text{c}] \quad & C \frac{dv_C(0^+)}{dt} = 4, \quad \text{therefore} \quad \frac{dv_C(0^+)}{dt} = 8 \times 10^7 \text{ V/s} \\
[\text{d}] \quad & v = [A_1 e^{-10,000t} + A_2 e^{-40,000t}] \text{ V}, \quad t \geq 0^+ \\
& v(0^+) = A_1 + A_2, \quad \frac{dv(0^+)}{dt} = -10,000A_1 - 40,000A_2 \\
& \text{Therefore} \quad A_1 + A_2 = 0, \quad -A_1 - 4A_2 = 8000, \quad A_1 = 8000/3 \\
[\text{e}] \quad & A_2 = -8000/3 \\
[\text{f}] \quad & v = [8000/3][e^{-10,000t} - e^{-40,000t}] \text{ V}, \quad t \geq 0^+
\end{aligned}$$

DE 9.4 [a] $\frac{1}{2RC} = 8000$, therefore $R = 62.5 \Omega$

$$\begin{aligned}
[\text{b}] \quad & i_R(0^+) = \frac{10}{62.5} = 160 \text{ mA} \\
& i_C(0^+) = -80 - 160 = -240 \text{ mA}, \quad i_C(0^+) = C \frac{dv(0^+)}{dt} \\
& \text{Therefore} \quad \frac{dv(0^+)}{dt} = -240 \text{ kV/s} \\
[\text{c}] \quad & B_1 = v(0^+) = 10 \text{ V}, \quad \frac{dv_C(0^+)}{dt} = \omega_d B_2 - \alpha B_1 \\
& \text{Therefore} \quad 6000B_2 - 8000B_1 = -240,000, \quad B_2 = (-80/3) \text{ V} \\
[\text{d}] \quad & i_L = -(i_R + i_C); \quad i_R = v/R; \quad i_C = C \frac{dv}{dt} \\
& v = e^{-8000t} [10 \cos 6000t - \frac{80}{3} \sin 6000t] \text{ V} \\
& \text{Therefore} \quad i_R = e^{-8000t} [160 \cos 6000t - \frac{1280}{3} \sin 6000t] \text{ mA} \\
& i_C = e^{-8000t} [-240 \cos 6000t + \frac{460}{3} \sin 6000t] \text{ mA} \\
& i_L = 10e^{-8000t} [8 \cos 6000t + \frac{82}{3} \sin 6000t] \text{ mA}, \quad t \geq 0^+
\end{aligned}$$

DE 9.5 [a] $\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = \frac{10^6}{4}$, therefore $\frac{1}{2RC} = 500$, $R = 100 \Omega$

$$\begin{aligned}
[\text{b}] \quad & 0.5CV_0^2 = 12.5 \times 10^{-3}, \quad \text{therefore} \quad V_0 = 50 \text{ V} \\
[\text{c}] \quad & 0.5LI_0^2 = 12.5 \times 10^{-3}, \quad I_0 = 250 \text{ mA} \\
[\text{d}] \quad & D_2 = v(0^+) = 50, \quad \frac{dv(0^+)}{dt} = D_1 - \alpha D_2 \\
& i_R(0^+) = \frac{50}{100} = 500 \text{ mA} \\
& \text{Therefore} \quad i_C(0^+) = -(500 + 250) = -750 \text{ mA}
\end{aligned}$$

$$\text{Therefore } \frac{dv(0^+)}{dt} = -750 \times \frac{10^{-3}}{C} = -75,000 \text{ V/s}$$

$$\text{Therefore } D_1 - \alpha D_2 = -75,000; \quad \alpha = \frac{1}{2RC} = 500, \quad D_1 = -50,000$$

$$\begin{aligned} [e] \quad v &= [50e^{-500t} - 50,000te^{-500t}] \text{ V} \\ i_R &= \frac{v}{R} = [0.5e^{-500t} - 500te^{-500t}] \text{ A}, \quad t \geq 0^+ \end{aligned}$$

$$\text{DE 9.6 } [a] \quad i_R(0^+) = \frac{V_0}{R} = \frac{80}{250} = 0.32 \text{ A}$$

$$[b] \quad i_C(0^+) = I - i_R(0^+) - i_L(0^+) = -1.5 - 0.32 - 0.5 = -2.32 \text{ A}$$

$$[c] \quad \frac{di_L(0^+)}{dt} = \frac{80}{.32} = 250 \text{ A/s}$$

$$[d] \quad \alpha = \frac{1}{2RC} = 1000; \quad \frac{1}{LC} = 1,562,500; \quad s_{1,2} = -1000 \pm j750$$

$$[e] \quad i_L = i_f + D_1 e^{-\alpha t} \cos \omega_d t + D_2 e^{-\alpha t} \sin \omega_d t, \quad i_f = -1.5 \text{ A}$$

$$i_L(0^+) = 0.5 = i_f + D_1, \quad \text{therefore } D_1 = 2 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = 250 = -\alpha D_1 + \omega_d D_2, \quad \text{therefore } D_2 = 3 \text{ A}$$

$$\text{Therefore } i_L(t) = -1.5 + 2e^{-1000t}[\cos 750t + 1.5 \sin 750t] \text{ A}, \quad t \geq 0^+$$

$$\text{DE 9.7 } [a] \quad i(0^+) = 0$$

$$[b] \quad v_C(0^+) = v_C(0^-) = \left(\frac{50}{32}\right)(12.8) = 20 \text{ V}$$

$$[c] \quad 20 + L \frac{di(0^+)}{dt} = 100, \quad \frac{di(0^+)}{dt} = 8000 \text{ A/s}$$

$$[d] \quad \alpha = 5000; \quad \frac{1}{LC} = 5 \times 10^6; \quad s_{1,2} = -5000 \pm j5000$$

$$[e] \quad i = i_f + e^{-\alpha t}[D_1 \cos \omega_d t + D_2 \sin \omega_d t]; \quad i_f = 0, \quad i(0^+) = 0$$

$$\text{Therefore } D_1 = 0; \quad \frac{di(0^+)}{dt} = 8000 = -\alpha D_1 + \omega_d D_2$$

$$\text{Therefore } D_2 = 1.6 \text{ A}; \quad i = 1.6e^{-5000t} \sin 5000t \text{ A}, \quad t \geq 0^+$$

$$\text{DE 9.8 } v_C(t) = v_f + e^{-\alpha t}[D_1 \cos \omega_d t + D_2 \sin \omega_d t], \quad v_f = 100 \text{ V}$$

$$v_C(0^+) = 20 \text{ V}; \quad \frac{dv_C(0^+)}{dt} = 0; \quad \text{therefore } 20 = 100 + D_1$$

$$D_1 = -80 \text{ V}; \quad 0 = -\alpha D_1 + \omega_d D_2$$


$$\text{Therefore } D_2 = \frac{\alpha}{\omega_d} D_1 = \left(\frac{5000}{5000} \right) (-80) = -80 \text{ V}$$

$$\text{Therefore } v_C(t) = 100 - 80e^{-5000t}[\cos 5000t + \sin 5000t] \text{ V}, \quad t \geq 0^+$$

DE 9.9 At $t = 0$ the voltage across each capacitor is zero. It follows that since the operational amplifiers are ideal, the current in the $500\text{-k}\Omega$ is zero. Therefore there cannot be an instantaneous change in the current in the $1\text{-}\mu\text{F}$ capacitor. Since the capacitor current equals $C(dv_o/dt)$, the derivative must be zero.

DE 9.10 [a] From Example 9.13 $\frac{d^2 v_o}{dt^2} = 2$; therefore $\frac{dg(t)}{dt} = 2$, $g(t) = \frac{dv_o}{dt}$
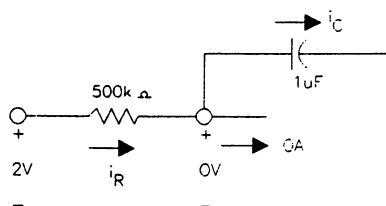
$$g(t) - g(0) = 2t; \quad g(t) = 2t + g(0); \quad g(0) = \frac{dv_o(0)}{dt}$$



$$i_R = \frac{2}{500} \times 10^{-3} = 4 \mu\text{A} = i_C = -C \frac{dv_o(0)}{dt}$$

$$\frac{dv_o(0)}{dt} = \frac{-4 \times 10^{-6}}{1 \times 10^{-6}} = -4 = g(0)$$

$$\frac{dv_o}{dt} = 2t - 4$$

$$dv_o = 2t dt = 4 dt$$

$$v_o - v_o(0) = t^2 - 4t; \quad v_o(0) = 8 \text{ V}$$

$$v_o = t^2 - 4t + 8, \quad 0 \leq t \leq (2 + \sqrt{5}) \text{ s}$$

[b] $t^2 - 4t + 8 = 9$

$$t^2 - 4t - 1 = 0$$

$$t = 2 \pm \sqrt{4 + 1} = 2 \pm \sqrt{5}$$

$$= 4.24 \text{ s} \quad (\text{Negative value has no physical significance.})$$

$$t \cong 4.24 \text{ s}$$

DE 9.11 [a] $R_a = 100 \text{ k}\Omega$; $C_1 = 0.1 \mu\text{F}$; $R_b = 25 \text{ k}\Omega$; $C_2 = 1 \mu\text{F}$

$$\frac{d^2 v_o}{dt^2} = \left(\frac{1}{R_a C_1} \right) \left(\frac{1}{R_b C_2} \right) v_g; \quad \frac{1}{R_a C_1} = 100 \quad \frac{1}{R_b C_2} = 40$$

$$v_g = 250 \times 10^{-3}; \quad \text{therefore } \frac{d^2 v_o}{dt^2} = 1000$$

[b] Since $v_o(0) = 0 = \frac{dv_o(0)}{dt}$, our solution is $v_o = 500t^2$

The second op-amp will saturate when

$$v_o = 6 \text{ V}, \text{ or } t_{\text{sat}} = \sqrt{6/500} \cong 0.1095 \text{ s}$$

[c] $\frac{dv_{o1}}{dt} = -\frac{1}{R_a C_1} v_g = -25$


[d] Since $v_{o1}(0) = 0$, $v_{o1} = -25t \text{ V}$

At $t = 0.1095 \text{ s}$, $v_{o1} \cong -2.74 \text{ V}$

Therefore the second amplifier saturates before the first amplifier saturates. Our expressions are valid for $0 \leq t \leq 0.1095 \text{ s}$. Once the second op-amp saturates, our linear model is no longer valid.

DE 9.12 [a] Initial conditions will not change the differential equation; hence the equation is the same as Example 9.14.

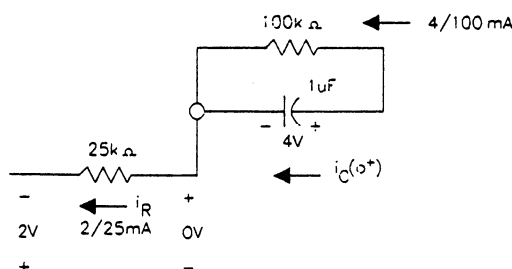[b] $v_o = 5 + A'_1 e^{-10t} + A'_2 e^{-20t}$ (from Example 9.14)
 $v_o(0) = 4 = 5 + A'_1 + A'_2$



$$\frac{4}{100} + i_C(0^+) - \frac{2}{25} = 0$$

$$i_C(0^+) = \frac{4}{100} \text{ mA} = C \frac{dv_o(0^+)}{dt}$$

$$\frac{dv_o(0^+)}{dt} = \frac{0.04 \times 10^{-3}}{10^{-6}} = 40 \text{ V/s}$$

$$\frac{dv_o}{dt} = -10A'_1 e^{-10t} - 20A'_2 e^{-20t}$$

$$\frac{dv_o}{dt}(0^+) = -10A'_1 - 20A'_2 = 40; \quad \text{therefore} \quad \begin{cases} -A'_1 - 2A'_2 = 4 \\ A'_1 + A'_2 = -1 \end{cases} \quad \begin{cases} A'_1 = 2 \\ A'_2 = -3 \end{cases}$$

$$v_o = 5 + 2e^{-10t} - 3e^{-20t} \text{ V}$$

[c] Same as Example (9.14): $\frac{dv_{o1}}{dt} + 20v_{o1} = -25$

[d] From Example (9.14): $v_{o1}(\infty) = -1.25 \text{ V}$, $v_{o1}(0) = -2 \text{ V}$ (given)

$$\begin{aligned}\text{Therefore } v_{o1} &= -1.25 + (-2 + 1.25)e^{-20t} \text{ V} \\ v_{o1} &= -1.25 - 0.75e^{-20t} \text{ V}\end{aligned}$$

Problems

P 9.1 [a] $s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$

$$\frac{1}{2RC} = \frac{10^6}{(2000)(2)} = 250; \quad \frac{1}{LC} = \frac{10^6}{25} = 40,000$$

$$s_{1,2} = -250 \pm \sqrt{62,500 - 40,000} = -250 \pm 150$$

$$s_1 = -100 \text{ rad/s}; \quad s_2 = -400 \text{ rad/s}$$

[b] Overdamped

[c] $\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2} = 120$

$$40,000 - \left(\frac{1}{2RC}\right)^2 = 14,400$$

$$\left(\frac{1}{2RC}\right)^2 = 25,600; \quad \frac{1}{2RC} = 160; \quad R = \frac{10^6}{(4)(160)} = 1562.50 \, \Omega$$

[d] $\frac{1}{2RC} = \frac{10^6}{4(1562.50)} = 160$

$$\therefore s_{1,2} = -160 \pm \sqrt{(160)^2 - 40,000} = -160 \pm j120 \text{ rad/s}$$

$$s_1 = -160 + j120 \text{ rad/s}; \quad s_2 = -160 - j120 \text{ rad/s}$$

[e] $\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = 40,000; \quad \frac{1}{2RC} = 200$

$$\therefore R = \frac{10^6}{800} = 1250 \, \Omega$$

P 9.2 [a] $-\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -250$

$$-\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -1000$$

$$\therefore \frac{-1}{RC} = -1250; \quad R = \frac{1}{1250C} = \frac{10^6}{125} = 8000 \, \Omega$$

$$2\sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = 750; \quad 4\left[\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}\right] = (750)^2; \quad \frac{1}{2RC} = 625$$

$$\therefore 1,562,500 - \frac{4}{LC} = 562,500; \quad \frac{4}{LC} = 10^6; \quad L = 40 \text{ H}$$

$$\alpha = \frac{1}{2RC} = 625 \text{ neper/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{4}; \quad \omega_o = 500 \text{ rad/s}$$

$$[b] \quad i_R = \frac{v(t)}{R} = -e^{-250t} + 4e^{-1000t} \text{ mA}$$

$$i_C = C \frac{dv(t)}{dt} = (0.1 \times 10^{-6})[2000e^{-250t} - 32,000e^{-1000t}]$$

$$= 0.2e^{-250t} - 3.2e^{-1000t} \text{ mA}$$

$$i_L(t) = -i_R(t) - i_C(t) = e^{-250t} - 4e^{-1000t} - 0.2e^{-250t} + 3.2e^{-1000t}$$

$$= 0.8e^{-250t} - 0.8e^{-1000t} \text{ mA}$$

P9.3 [a] $i_C(0) = -1.2 \text{ mA}; \quad i_R(0) = 0; \quad i_L(0) = 1.2 \text{ mA}$

$$[b] \quad \alpha = \frac{1}{2RC} = \frac{10^6}{2(20,000)(0.02)} = \frac{100}{0.08} = 1250 \text{ neper/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(50)(0.02)} = 10^6$$

$$\omega_o = 1000 \text{ rad/s}$$

$$s_{1,2} = -1250 \pm \sqrt{1,562,500 - 10^6} = -1250 \pm \sqrt{562,500} = -1250 \pm 750$$

$$s_1 = -500 \text{ rad/s}; \quad s_2 = -2000 \text{ rad/s}$$

$$v(t) = A_1 e^{-500t} + A_2 e^{-2000t}$$

$$v(0) = 0 = A_1 + A_2; \quad \therefore A_1 = -A_2$$

$$C \frac{dv(0)}{dt} = 0.02 \times 10^{-6}[-500A_1 - 2000A_2]$$

$$10^{-6}(-10A_1 - 40A_2) = -1.2 \times 10^{-3}$$

$$10A_1 + 40A_2 = 1200$$

$$30A_2 = 1200$$

$$A_2 = 40, \quad A_1 = -40$$

$$\therefore v(t) = -40e^{-500t} + 40e^{-2000t} \text{ V}, \quad t \geq 0$$

$$[c] \quad i_R(t) = \frac{v}{R} = -2e^{-500t} + 2e^{-2000t} \text{ mA}, \quad t \geq 0$$

$$i_C(t) = (0.02 \times 10^{-6})[20,000e^{-500t} - 80,000e^{-2000t}]$$

$$= 0.4e^{-500t} - 1.6e^{-2000t} \text{ mA}, \quad t \geq 0$$

$$i_L(t) = -i_R(t) - i_C(t) = 2e^{-500t} - 2e^{-2000t} - 0.4e^{-500t} + 1.6e^{-2000t}$$

$$i_L(t) = 1.6e^{-500t} - 0.4e^{-2000t} \text{ mA}, \quad t \geq 0$$

P9.4 $-\alpha + \sqrt{\alpha^2 - \omega_o^2} = -100; \quad -\alpha - \sqrt{\alpha^2 - \omega_o^2} = -900$

$$2\alpha = -1000; \quad \alpha = 500$$

$$\frac{1}{2RC} = 500; \quad R = \frac{1}{1000C} = \frac{1000}{2.5} = 400 \Omega$$

$$v(0) = 3(1 + 1) = 6 \text{ V}$$

$$i_C(0) = C \frac{dv(0)}{dt} = 2.5 \times 10^{-6}(-300 - 2700) = -7.5 \text{ mA}$$

$$i_R(0) = \frac{v(0)}{R} = \frac{6}{400} = 15 \text{ mA}$$

$$i_L(0^+) = -i_R(0^+) - i_C(0^+) = -15 + 7.5 = -7.5 \text{ mA}$$

P 9.5 [a] $\alpha = -20,000 = -\frac{1}{2RC}$; $\therefore R = \frac{1}{4 \times 10^4 \times 0.04 \times 10^{-6}} = 625 \Omega$

[b] $\omega_o^2 = \frac{1}{LC}$, $L = \frac{1}{\omega_o^2 C}$

$$\omega_o^2 - \alpha^2 = 225 \times 10^6$$

$$\omega_o^2 = 2.25 \times 10^8 + 4 \times 10^8 = 6.25 \times 10^8$$

$$L = \frac{1}{(6.25 \times 10^8)(0.04) \times 10^{-6}} = \frac{1}{25}$$

$$L = 40 \text{ mH}$$

[c] $V_0 = v(0) = 100 \text{ V}$

[d] $I_0 = i_L(0^+) = -i_R(0^+) - i_C(0^+)$

$$i_R(0^+) = \frac{100}{625} = 0.16 = 160 \text{ mA}$$

$$i_C(0^+) = C \frac{dv(0^+)}{dt}$$

$$\frac{dv}{dt} = 100 \{ e^{-20,000t}(-15,000 \sin 15,000t - 30,000 \cos 15,000t)$$

$$+ (\cos 15,000t - 2 \sin 15,000t)(-20,000e^{-20,000t}) \}$$

$$= 100e^{-20,000t}[25,000 \sin 15,000t - 50,000 \cos 15,000t]$$

$$= 25 \times 10^5 e^{-20,000t}[\sin 15,000t - 2 \cos 15,000t]$$

$$\frac{dv}{dt}(0) = -50 \times 10^5 = -5 \times 10^6$$

$$i_C(0^+) = (0.04 \times 10^{-6})(-5 \times 10^6) = -0.20 = -200 \text{ mA}$$

$$\therefore i_L(0^+) = I_0 = -160 + 200 = 40 \text{ mA}$$

[e] $i_R(t) = \frac{v}{R} = 160e^{-20,000t}[\cos 15,000t - 2 \sin 15,000t] \text{ mA}$

$$i_C = C \frac{dv}{dt} = 100e^{-20,000t}[\sin 15,000t - 2 \cos 15,000t] \text{ mA}$$

$$i_L(t) = -i_R(t) - i_C(t) = -e^{-20,000t}[160 \cos 15,000t - 320 \sin 15,000t]$$

$$- e^{-20,000t}[100 \sin 15,000t - 200 \cos 15,000t]$$

$$i_L(t) = e^{-20,000t}[220 \sin 15,000t + 40 \cos 15,000t] \text{ mA}, \quad t \geq 0$$

P9.6 [a] $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -40$; $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_o^2} = -160$

$$\therefore -2\alpha = -200; \quad \alpha = 100 \text{ rad/s}$$

$$s_1 - s_2 = 2\sqrt{\alpha^2 - \omega_o^2} = 120$$

$$\therefore \sqrt{\alpha^2 - \omega_o^2} = 60; \quad \alpha^2 - \omega_o^2 = 3600$$

$$\omega_o^2 = 6400; \quad \omega_o = 80 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC}; \quad C = \frac{1}{2R\alpha} = 25 \mu\text{F}$$

$$\omega_o^2 = \frac{1}{LC}; \quad L = \frac{1}{\omega_o^2 C} = 6.25 \text{ H}$$

$$i_C(0^+) = A_1 + A_2 = 15 \times 10^{-3}$$

$$i_L + i_C + i_R = 0; \quad \frac{di_L}{dt} + \frac{di_R}{dt} + \frac{di_C}{dt} = 0$$

$$\text{At } t = 0^+ \quad \frac{di_L}{dt}(0^+) = 0 \quad \text{since } v(0^+) = 0$$

$$\therefore \frac{di_C}{dt}(0^+) = -\frac{di_R(0^+)}{dt} = -\frac{1}{R} \frac{dv}{dt}(0^+)$$

$$\frac{dv(0^+)}{dt} = \frac{i_C(0^+)}{C}$$

$$\therefore \frac{di_C}{dt}(0^+) = -\frac{1}{R} \frac{i_C(0^+)}{C} = \frac{-15 \times 10^{-3}}{(200)(25)} \times 10^6 = -3 \text{ A/s}$$

$$\frac{di_C}{dt}(0^+) = -160A_1 - 40A_2$$

$$\therefore 160A_1 + 40A_2 = 3; \quad 4A_1 + A_2 = 75 \times 10^{-3}$$

$$\text{Also } A_1 + A_2 = 15 \times 10^{-3}; \quad \therefore A_1 = 20 \text{ mA}, \quad A_2 = -5 \text{ mA}$$

$$\therefore i_C = 20e^{-160t} - 5e^{-40t} \text{ mA}, \quad t \geq 0^+$$

[b] We know that the solution for v will also be of the form

$$v = A_3e^{-160t} + A_4e^{-40t}, \quad t \geq 0$$

By hypothesis

$$v(0^+) = A_3 + A_4 = 0$$

$$\frac{dv(0^+)}{dt} = -160A_3 - 40A_4 = \frac{+15 \times 10^{-3}}{25 \times 10^{-6}}$$


$$\therefore 4A_3 + A_4 = -15; \quad \therefore A_3 = -5 \text{ V}, \quad A_4 = 5 \text{ V}$$

$$v = -5e^{-160t} + 5e^{-40t} \text{ V}, \quad t \geq 0$$

[c] $i_R = \frac{v}{R} = \frac{v}{200} = -25e^{-160t} + 25e^{-40t} \text{ mA}, \quad t \geq 0$

[d] $i_L = -i_R - i_C = 25e^{-160t} - 25e^{-40t} - 20e^{-160t} + 5e^{-40t}$
 $= 5e^{-160t} - 20e^{-40t} \text{ mA}, \quad t \geq 0$

P9.7 [a]

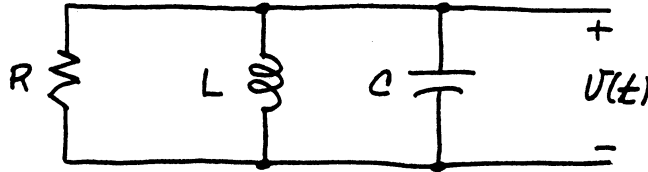

$$\alpha = 500 = \frac{1}{2RC}$$

$$\omega_o = 500, \quad \omega_o^2 = 25 \times 10^4 = \frac{1}{LC}$$

$$\therefore C = \frac{1}{4(25 \times 10^4)} = 1 \mu\text{F}$$

$$R = \frac{1}{1000C} = 1000 \Omega$$

$$v(0) = D_2 = 8 \text{ V}$$

$$i_R(0^+) = \frac{8}{1000} = 8 \text{ mA}; \quad i_L(0^+) = -10 \text{ mA}$$

$$\therefore i_C(0^+) = -i_R(0^+) - i_L(0^+) = 2 \text{ mA}$$

$$\frac{dv}{dt}(0^+) = \frac{2 \times 10^{-3}}{1 \times 10^{-6}} = 2000 \text{ V/s}$$

$$\frac{dv}{dt} = D_1 e^{-500t} - 500 e^{-500t} [D_1 t + D_2]$$

$$\frac{dv}{dt}(0^+) = D_1 - 500 D_2 = 2000$$

$$\therefore D_1 = 2000 + 500(8) = 6000 \text{ V/s}$$

$$\therefore v = (6000t + 8)e^{-500t} \text{ V}, \quad t \geq 0$$

[b] $i_C = C \frac{dv}{dt}$

$$\therefore i_C = 10^{-6} [(6000t + 8)(-500e^{-500t}) + 6000e^{-500t}]$$

$$= -3te^{-500t} + 2 \times 10^{-3} e^{-500t}$$

$$i_C = -3000te^{-500t} + 2e^{-500t} \text{ mA}, \quad t \geq 0^+$$

P9.8 [a] $\alpha = \frac{1}{2RC} = \frac{1}{2} = 0.5$

$$\omega_o^2 = \frac{1}{LC} = \frac{101}{4} = 25.25$$

$$\omega_d = \sqrt{25.25 - 0.25} = 5 \text{ rad/s}$$

$$\therefore v = B_1 e^{-0.5t} \cos 5t + B_2 e^{-0.5t} \sin 5t$$

$$v(0) = B_1 = 0; \quad v = B_2 e^{-0.5t} \sin 5t$$

$$\frac{dv}{dt} = B_2 [e^{-0.5t}(5 \cos 5t) - 0.5e^{-0.5t} \sin 5t] = 0.5B_2 e^{-0.5t} [10 \cos 5t - \sin 5t]$$

$$C \frac{dv}{dt}(0) = 0.04B_2(10) = 0.4B_2$$

$$\therefore 0.4B_2 = -(-4) = 4; \quad B_2 = 10$$

$$\therefore v = 10e^{-0.5t} \sin 5t \text{ V}, \quad t \geq 0$$

$$[b] \quad \frac{dv}{dt} = 5e^{-0.5t}(10 \cos 5t - \sin 5t)$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad 10 \cos 5t = \sin 5t \quad \text{or} \quad \tan 5t = 10$$

$$\therefore 5t_1 = 1.47, \quad t_1 = 294.23 \text{ ms}$$

$$5t_2 = 1.47 + \pi, \quad t_2 = 922.54 \text{ ms}$$

$$5t_3 = 1.47 + 2\pi, \quad t_3 = 1550.86 \text{ ms}$$

$$[c] \quad t_3 - t_1 = 1256.64 \text{ ms}; \quad T_d = \frac{2\pi}{\omega_d} = \frac{2\pi}{5} = 1256.64 \text{ ms}$$


$$[d] \quad t_2 - t_1 = 628.32 \text{ ms}; \quad \frac{T_d}{2} = \frac{1256.64}{2} = 628.32 \text{ ms}$$

$$[e] \quad v(t_1) = 10e^{-0.5(0.29423)} \sin 5(0.29423) = 8.59 \text{ V}$$

$$v(t_2) = 10e^{-0.5(0.92254)} \sin 5(0.92254) = -6.27 \text{ V}$$

$$v(t_3) = 10e^{-0.5(1.55086)} \sin 5(1.55086) = 4.58 \text{ V}$$

[f]

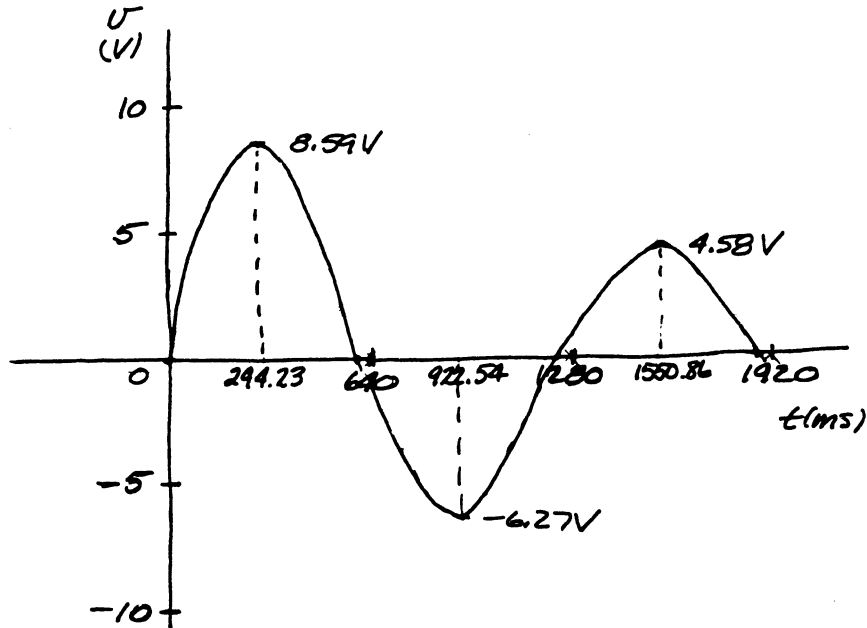

P9.9 [a] $\alpha = 0; \quad \omega_d = \omega_o = \sqrt{25.25} = 5.02 \text{ rad/s}$

$$v = B_1 \cos \omega_o t + B_2 \sin \omega_o t; \quad v(0) = B_1 = 0; \quad v = B_2 \sin \omega_o t$$

$$\frac{dv}{dt} = \omega_o B_2 \cos \omega_o t; \quad C \frac{dv}{dt}(0) = \omega_o C B_2 = -i_L(0) = 4$$

$$\therefore B_2 = \frac{4}{0.08\sqrt{25.25}} = \frac{50}{\sqrt{25.25}} = 9.95$$

$$v = 9.95 \sin 5.02t \text{ V}, \quad t \geq 0$$

$$[b] \quad 2\pi f = 5.02; \quad f = \frac{5.02}{2\pi} \cong 0.80 \text{ Hz}$$

$$[c] \quad 9.95 \text{ V}$$

$$\begin{aligned} \text{P 9.10 } [a] \quad \omega_o^2 &= \frac{1}{LC} = \frac{10^9}{(12.5)(3.2)} = 25 \times 10^6 \\ \alpha^2 &= 25 \times 10^6, \quad \alpha = 5000 = \frac{1}{2RC} \\ \therefore R &= \frac{10^9}{10,000}(3.2) = \frac{10^5}{3.2} = 31.25 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} [b] \quad v(t) &= (D_1 t + D_2)e^{-5000t} \\ v(0) &= D_2 = 100 \text{ V}; \quad v(t) = (D_1 t + 100)e^{-5000t} \\ i_C(0^+) &= i_L(0^+) - i_R(0^+); \quad i_R(0^+) = \frac{100}{31.25} = 3.2 \text{ mA} \\ \therefore i_C(0^+) &= -6.4 - 3.2 = -9.6 \text{ mA} \\ \frac{dv}{dt} &= (D_1 t + 100)(-5000e^{-5000t}) + D_1 e^{-5000t} \\ &= (-5000D_1 t - 5 \times 10^5 + D_1)e^{-5000t} \\ \frac{dv}{dt}(0) &= D_1 - 5 \times 10^5 = \frac{-9.6 \times 10^{-3}}{3.2 \times 10^{-9}} \\ \therefore D_1 &= 5 \times 10^5 - 3 \times 10^6 = (5 - 30)10^5 = -25 \times 10^5 \\ \therefore v(t) &= [-25 \times 10^5 t + 100]e^{-5000t} \text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} [c] \quad i_C(t) &= 0 \quad \text{when} \quad \frac{dv(t)}{dt} = 0 \\ \frac{dv}{dt} &= [-25 \times 10^5 t + 100](-5000e^{-5000t}) - 25 \times 10^5 e^{-5000t} \\ &= (125 \times 10^8 t - 30 \times 10^5)e^{-5000t} \\ \frac{dv}{dt} &= 0 \quad \text{when} \quad 125 \times 10^8 t = 30 \times 10^5 \quad \text{or} \quad t = \frac{30 \times 10^{-3}}{125} = 240 \mu\text{s} \\ v(240 \mu\text{s}) &= [-25 \times 10^5(240) \times 10^{-6} + 100]e^{-1.2} \\ &= (-600 + 100)e^{-1.2} = -500e^{-1.2} \cong -150.60 \text{ V} \end{aligned}$$

$$[d] \quad w(0) = \frac{1}{2}(12.5)(6.4 \times 10^{-3})^2 + \frac{1}{2}(3.2 \times 10^{-9})(100)^2 = 256 + 16 = 272 \mu\text{J}$$

$$\text{When } i_C(t) = 0, \quad t = 240 \mu\text{s}$$

$$\therefore i_L(240 \mu\text{s}) = -i_R(240 \mu\text{s})$$

$$i_R(240 \mu\text{s}) = \frac{v(240 \mu\text{s})}{31.25 \times 10^3} = \frac{-500e^{-1.2}}{31.25 \times 10^3} = -16e^{-1.2} \text{ mA}$$

$$\therefore i_L(240 \mu\text{s}) = 16e^{-1.2} \text{ mA}$$

$$\begin{aligned}\therefore w(240 \mu\text{s}) &= \frac{1}{2}(3.2 \times 10^{-9})(25 \times 10^4)e^{-2.4} + \frac{1}{2}(12.5)(256 \times 10^{-6}e^{-2.4}) \\ &= 2000e^{-2.4} \mu\text{J} \\ \% &= \frac{2000e^{-2.4}}{272} \times 100 = 66.70\%\end{aligned}$$

P9.11 [a] $\alpha = \frac{1}{2RC} = 1250$, $\omega_o = 10^3$, therefore overdamped

$s_1 = -500$, $s_2 = -2000$, therefore $v = A_1 e^{-500t} + A_2 e^{-2000t}$


$v(0^+) = 0 = A_1 + A_2$; $\left[\frac{dv(0^+)}{dt} \right] = \frac{i_C(0^+)}{C} = 98,000 \text{ V/s}$

Therefore $-500A_1 - 2000A_2 = 98,000$; $A_1 = \frac{+980}{15}$, $A_2 = \frac{-980}{15}$

$v(t) = \left[\frac{980}{15} \right] [e^{-500t} - e^{-2000t}] \text{ V}, \quad t \geq 0^+$

[b]

$t(\text{ms})$	0	1	2	3	4	5	6	7
$v(t)(\text{V})$	0.0	30.78	22.84	14.42	8.82	5.36	3.25	1.97

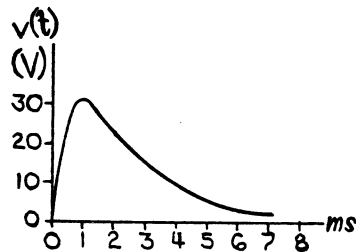


Example 9.4: $v_{\max} \cong 74 \text{ V}$ at 1.4 ms

Example 9.5: $v_{\max} \cong 36 \text{ V}$ at 1.0 ms

Problem 9.11: $v_{\max} \cong 30.8$ at 0.92 ms

P9.12 For $t > 0$:

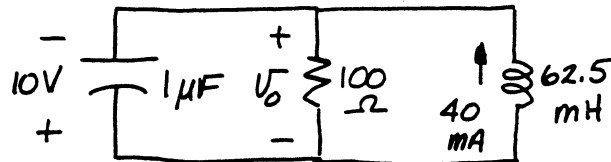

$$\alpha = \frac{1}{2RC} = \frac{10^6}{200} = 5000; \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{62.5} = 16 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 16 \times 10^6} = -5000 \pm 3000$$

$$s_1 = -2000 \text{ rad/s}, \quad s_2 = -8000 \text{ rad/s}; \quad \therefore \text{overdamped}$$

$$v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$v_o(0) = A_1 + A_2 = -10; \quad \frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2$$

$$i_R(0) = \frac{-10}{100} = -0.10 \text{ A}; \quad i_L(0) = -40 \times 10^{-3} = -0.04 \text{ A}$$

$$i_C(0) + i_R(0) + i_L(0) = 0$$

$$\therefore i_C(0) = 0.14 \text{ A}; \quad i_C(0) = C \frac{dv_o}{dt}(0)$$

$$\therefore \frac{dv_o}{dt}(0) = \frac{0.14}{1} \times 10^6 = -2000A_1 - 8000A_2$$

$$\therefore -2A_1 - 8A_2 = 140; \quad -A_1 - 4A_2 = 70; \quad A_1 + A_2 = -10$$

$$\therefore -3A_2 = 60; \quad A_2 = -20$$

$$\therefore A_1 = -10 - (-20) = 10$$

$$\therefore v_o(t) = 10e^{-2000t} - 20e^{-8000t} \text{ V}, \quad t \geq 0$$

P9.13 $\alpha = \frac{1}{2RC} = \frac{10^6}{500} = 2000; \quad \omega_o^2 = \frac{1}{LC} = 16 \times 10^6$

$$\omega_o^2 > \alpha^2; \quad \therefore \text{underdamped}$$

$$s_{1,2} = -2000 \pm j\sqrt{16 \times 10^6 - 4 \times 10^6} = -2000 \pm j2000\sqrt{3} \text{ rad/s}$$

$$v_o(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\alpha = 2000; \quad \omega_d = 2000\sqrt{3}$$

$$v_o(0) = B_1 = -10 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -\alpha B_1 + \omega_d B_2 = \frac{i_C(0)}{C} = 10^6 i_C(0)$$

$$i_R(0) = \frac{-10}{250} = -0.04 \text{ A}; \quad i_L(0) = -0.04 \text{ A}$$

$$\therefore i_C(0) = -(-0.04 - 0.04) = 0.08 \text{ A}$$

$$10^6 i_C(0) = 80,000$$

$$\therefore -2000B_1 + 2000\sqrt{3} B_2 = 80,000$$

$$-B_1 + \sqrt{3} B_2 = 40; \quad 10 + \sqrt{3} B_2 = 40; \quad B_2 = \frac{30}{\sqrt{3}} = 10\sqrt{3}$$

$$\therefore v_o(t) = -10e^{-2000t} \cos 2000\sqrt{3} t + 10\sqrt{3} e^{-2000t} \sin 2000\sqrt{3} t$$

$$v_o(t) = 10 \left[\sqrt{3} \sin 2000\sqrt{3} t - \cos 2000\sqrt{3} t \right] e^{-2000t} \text{ V}, \quad t \geq 0$$

P9.14 $\alpha = \frac{10^6}{250} = 4000, \quad \alpha^2 = 16 \times 10^6$

$$\omega_o^2 = \frac{1}{LC} = 16 \times 10^6; \quad \alpha^2 = \omega_o^2 \quad \text{critical damping}$$

$$\therefore v_o(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}, \quad \alpha = 4000$$

$$v_o(0) = D_2 = -10 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -4000 D_2 + D_1 = \frac{i_C(0)}{C} = 10^6 i_C(0)$$

$$i_R(0) = \frac{-10}{125} = -0.08 \text{ A}; \quad i_L(0) = -0.04 \text{ A}$$


$$\therefore i_C(0) = 0.12 \text{ A}$$

$$\therefore -4000 D_2 + D_1 = 120 \times 10^3; \quad \therefore D_1 = (120 - 40) \times 10^3 = 8 \times 10^4 \text{ V/s}$$

$$v_o = (8 \times 10^4 t - 10) e^{-4000 t} \text{ V}, \quad t \geq 0$$

P9.15 $v_o(0) = \frac{3}{5}(50) = 30 \text{ V}$

Thévenin resistance:

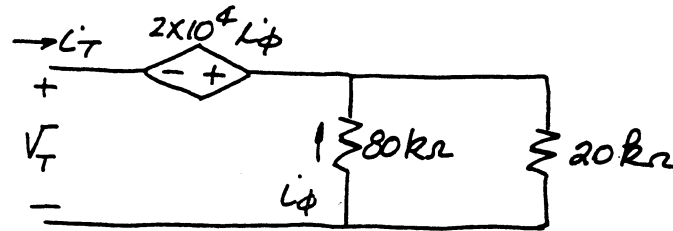


$$V_T = -2 \times 10^4 i_\phi + i_T \frac{(80)(20)}{100} \times 10^3 = -2 \times 10^4 i_\phi + 16 \times 10^3 i_T$$

$$i_\phi = \frac{-i_T(20)}{100} = -\frac{i_T}{5}$$

$$V_T = -20 \times 10^3 \left(\frac{-i_T}{5} \right) + 16 \times 10^3 i_T$$

$$R_{Th} = \frac{V_T}{i_T} = 20 \times 10^3 = 20 \text{ k}\Omega$$

$t \geq 0$:

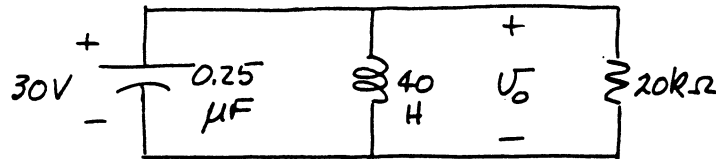

$$\alpha = \frac{1}{2RC} = \frac{10^6}{40 \times 10^3(0.25)} = 100; \quad \alpha^2 = 10^4$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(40)(0.25)} = 10^5$$

$$\omega_o^2 > \alpha^2; \quad \therefore \text{underdamped}$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{10 \times 10^4 - 10^4} = 300 \text{ rad/s}$$

$$v_o(t) = (B_1 \cos 300t + B_2 \sin 300t)e^{-100t}$$

$$i_R(0) = \frac{30}{20} = 1.5 \text{ mA}; \quad i_L(0) = 0$$

$$\therefore i_C(0) = -1.5 \text{ mA} = C \frac{dv_o}{dt}(0)$$

$$\therefore \frac{dv_o}{dt}(0) = \frac{-1.5}{0.25} \times 10^3 = -6 \times 10^3 \text{ V/s}$$

$$\begin{aligned} \frac{dv_o}{dt} &= (B_1 \cos 300t + B_2 \sin 300t)(-100e^{-100t}) \\ &\quad + (-300B_1 \sin 300t + 300B_2 \cos 300t)e^{-100t} \end{aligned}$$

$$\frac{dv_o}{dt}(0) = -100B_1 + 300B_2 = -6 \times 10^3$$

$$v_o(0) = B_1 = 30$$

$$\therefore -B_1 + 3B_2 = -6 \times 10$$

$$\therefore 3B_2 = -60 + 30 = -30; \quad B_2 = -10$$

$$\therefore v_o = [30 \cos 300t - 10 \sin 300t]e^{-100t} \text{ V}, \quad t \geq 0$$

P 9.16 [a] $v = L \left(\frac{di_L}{dt} \right) = 16[e^{-20,000t} - e^{-80,000t}] \text{ V}, \quad t \geq 0^+$

[b] $i_R = \frac{v}{R} = 40[e^{-20,000t} - e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$

[c] $i_C = I - i_L - i_R = [-8e^{-20,000t} + 32e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$

P 9.17 [a] $v = L \left(\frac{di_L}{dt} \right) = 40e^{-32,000t} \sin 24,000t \text{ V}, \quad t \geq 0^+$


[b] $i_C(t) = I - i_R - i_L$
 $= [24e^{-32,000t} \cos 24,000t - 32e^{-32,000t} \sin 24,000t] \text{ mA}, \quad t \geq 0^+$

P 9.18 $v = L \left(\frac{di_L}{dt} \right) = 960,000te^{-40,000t} \text{ V}, \quad t \geq 0^+$

P 9.19 For $t < 0$:

$$i_L(0^-) = \frac{9}{3000} = 3 \text{ mA} = i_L(0^+); \quad v_C(0^-) = 0 = v_C(0^+)$$

For $t > 0$:

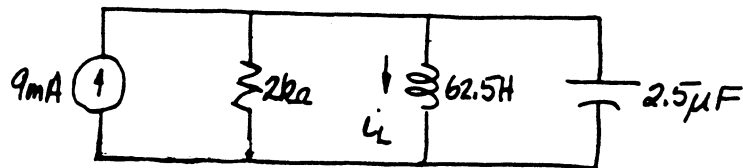

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(2000)(2.5)} = 100; \quad \omega_o^2 = \frac{1}{LC} = \frac{10^6}{(62.5)(2.5)} = 6400$$

$$\alpha^2 = 10,000; \quad \therefore \alpha^2 > \omega_o^2 \text{ overdamped}$$

$$s_1 = -100 + 60 = -40 \text{ rad/s}; \quad s_2 = -100 - 60 = -160 \text{ rad/s}$$

$$\therefore i_L = i_F + A'_1 e^{-40t} + A'_2 e^{-160t}, \quad i_F = 9 \text{ mA}$$

$$i_L = 9 + A'_1 e^{-40t} + A'_2 e^{-160t} \text{ mA}, \quad t \geq 0$$

$$i_L(0) = 3 = 9 + A'_1 + A'_2; \quad \therefore A'_1 + A'_2 = -6 \times 10^{-3}$$


$$\frac{di_L}{dt}(0^+) = 0 = -40A'_1 - 160A'_2$$

$$\therefore A'_1 = -4A'_2$$

$$-3A'_2 = -6 \text{ mA}; \quad A'_2 = 2 \text{ mA}; \quad A'_1 = -8 \text{ mA}$$


$$i_L = 9 - 8e^{-40t} + 2e^{-160t} \text{ mA}, \quad t \geq 0$$

P9.20 $t < 0$:

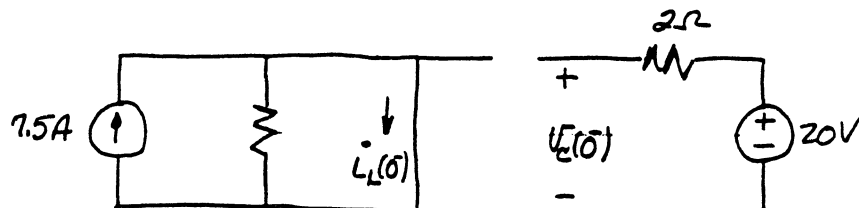

$$i_L(0^-) = 7.5 \text{ A} = i_L(0^+); \quad v_C(0^-) = 20 \text{ V} = v_C(0^+)$$

$t > 0$:

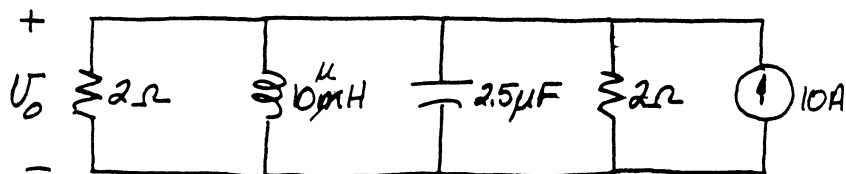

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(2)(1)(2.5)} = 20 \times 10^4; \quad \omega_o^2 = \frac{1}{LC} = \frac{10^{12}}{25} = 4 \times 10^{10}$$


$$\alpha^2 = \omega_o^2 \text{ critically damped}$$

$$v_o = v_F + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t}, \quad v_F = 0$$

$$v_o = (D'_1 t + D'_2) e^{-200,000t}$$

$$v_o(0^+) = 20 = D'_2$$

At $t = 0^+$:

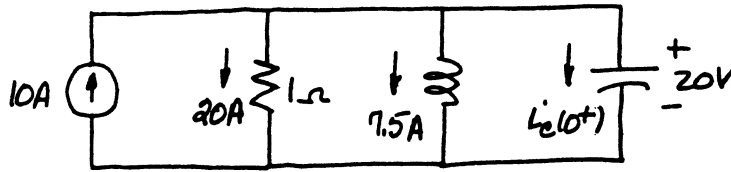

$$\therefore i_C(0^+) = 10 - 20 - 7.5 = -17.5 \text{ A}$$

$$\frac{dv_o}{dt}(0^+) = \frac{-17.5}{2.5} \times 10^6 = -7 \times 10^6$$

$$\frac{dv_o}{dt}(0^+) = -2 \times 10^5 D'_2 + D'_1 = -7 \times 10^6$$

$$-2 \times 10^5(20) + D'_1 = -7 \times 10^6; \quad D'_1 = -3 \times 10^6 \text{ V/s}$$

$$\therefore v_o = -3 \times 10^6 t e^{-2 \times 10^5 t} + 20 e^{-2 \times 10^5 t} \text{ V}, \quad t \geq 0^+$$

P9.21 From the solution of Problem 9.20 we know i_L will be of the form

$$i_L = i_F + D'_3 t e^{-2 \times 10^5 t} + D'_4 e^{-2 \times 10^5 t}$$

We also have from the Problem 9.20 solution

$$i_L(0^-) = i_L(0^+) = 7.5 \text{ A}$$

and

$$L \frac{di_L}{dt}(0^+) = 20 \text{ V} \quad \text{or} \quad \frac{di_L}{dt}(0^+) = 2 \times 10^6 \text{ A/s}$$

The final value of i_L is 10 A, hence we have

$$i_L = 10 + D'_3 t e^{-2 \times 10^5 t} + D'_4 e^{-2 \times 10^5 t}$$


$$i_L(0^+) = 7.5 = 10 + D'_4; \quad D'_4 = -2.5 \text{ A}$$

$$\frac{di_L}{dt}(0^+) = 2 \times 10^6 = -200,000 D'_4 + D'_3$$

$$\therefore D'_3 = 2 \times 10^6 - 0.5 \times 10^6 = 1.5 \times 10^6 \text{ A/s}$$

$$\therefore i_L = 10 + [1.5 \times 10^6 t - 2.5] e^{-200,000 t} \text{ A}, \quad t \geq 0$$

P9.22 For $t > 0$:

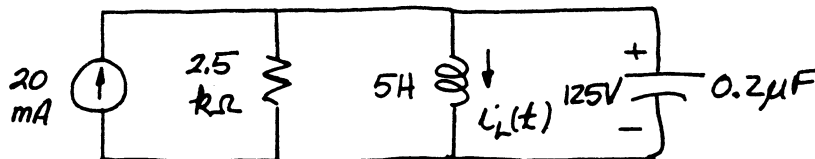

$$\alpha = \frac{1}{2RC} = \frac{10^6}{5000(0.2)} = 10^3 = 1000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(5)(0.2)} = 10^6; \quad \therefore \alpha^2 = \omega_o^2 \quad \text{critical damping}$$

$$i_L(t) = 20 \times 10^{-3} + D'_1 t e^{-1000t} + D'_2 e^{-1000t}$$

$$i_L(0) = 0 = 20 \times 10^{-3} + D'_2; \quad \therefore D'_2 = -20 \times 10^{-3}$$

$$L \frac{di_L(0)}{dt} = 125, \quad \frac{di_L(0)}{dt} = \frac{125}{5} = 25$$

$$\frac{di_L(t)}{dt} = (D'_1 t + D'_2)(-1000e^{-1000t}) + e^{-1000t}(D'_1)$$

$$\frac{di_L(0)}{dt} = -1000D'_2 + D'_1 = 25$$

$$\therefore D'_1 = 25 + 1000D'_2 = 25 + 1000(-20 \times 10^{-3}) = 5$$

$$i_L(t) = 20 \times 10^{-3} + 5te^{-1000t} - 20 \times 10^{-3}e^{-1000t}$$

$$i_L(t) = 20 + (5000t - 20)e^{-1000t} \text{ mA}, \quad t \geq 0$$

P9.23 [a] $i_L(0^+) = 0$

[b] $\frac{di_L}{dt}(0^+) = 0$

[c] $\alpha = \frac{1}{2RC} = \frac{1}{(4)(0.25)} = 1 \text{ rad/s}, \quad \alpha^2 = 1$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(0.8)(0.25)} = 5, \quad \omega_o^2 > \alpha^2 \quad \text{underdamped}$$

$$s_{1,2} = -1 \pm \sqrt{1-5} = -1 \pm j2 \text{ rad/s}$$

$$\therefore i_L(t) = -16 + B'_1 e^{-t} \cos 2t + B'_2 e^{-t} \sin 2t$$

$$i_L(0) = -16 + B'_1 = 0, \quad B'_1 = 16 \text{ A}$$

$$\frac{di_L}{dt} = (B'_1 \cos 2t + B'_2 \sin 2t)(-e^{-t}) + e^{-t}(-2B'_1 \sin 2t + 2B'_2 \cos 2t)$$

$$\frac{di_L}{dt}(0^+) = -B'_1 + 2B'_2 = 0$$

$$B'_2 = \frac{B'_1}{2} = \frac{16}{2} = 8 \text{ A}$$

$$\therefore i_L(t) = -16 + 16e^{-t} \cos 2t + 8e^{-t} \sin 2t \text{ A}, \quad t \geq 0$$

P9.24 [a] Let v_C be the voltage across the capacitor, positive at the top terminal. Then note

$$5 \frac{di}{dt} + 20 \frac{di}{dt} = v_C$$

$$\frac{1}{4} v_o + v_o = v_C$$

$$1.25 v_o = v_C; \quad v_o = 0.8 v_C$$

Now $v_C(0^+) = 0; \quad \therefore v_o(0^+) = 0$


[b] $\frac{dv_o}{dt} = 0.8 \frac{dv_C}{dt}$
 $C \frac{dv_C}{dt}(0^+) = -15 \times 10^{-3}; \quad \frac{dv_C}{dt}(0^+) = \frac{-15 \times 10^{-3}}{0.25 \times 10^{-6}} = -60,000 \text{ V/s}$
 $\therefore \frac{dv_o}{dt}(0^+) = 0.8(-60,000) = -48,000 \text{ V/s}$

[c] $R = 20 \text{ k}\Omega // 5 \text{ k}\Omega = 4 \text{ k}\Omega$
 $\alpha = \frac{10^6}{8000(0.25)} = \frac{1000}{2} = 500 \text{ rad/s}, \quad \alpha^2 = 25 \times 10^4$
 $\omega_o^2 = \frac{10^6}{(25)(0.25)} = \frac{400 \times 10^4}{25} = 16 \times 10^4$
 $\alpha^2 > \omega_o^2$ overdamped
 $\therefore v_C = V_f + A'_1 e^{s_1 t} + A'_2 e^{-s_2 t}; \quad v_C(\infty) = V_f = 0$
 $s_{1,2} = -500 \pm \sqrt{(25 - 16)10^4} = -500 \pm 300$
 $s_1 = -200 \text{ rad/s}, \quad s_2 = -800 \text{ rad/s}$
 $\therefore v_C = A'_1 e^{-200t} + A'_2 e^{-800t}$
 $v_C(0) = 0 = A'_1 + A'_2; \quad \therefore A'_1 = -A'_2$
 $\frac{dv_C}{dt}(0) = -200A'_1 - 800A'_2 = -60,000$
 $-200A'_1 + 800A'_1 = -60,000; \quad 6A'_1 = -600; \quad A'_1 = -100$
 $v_C(t) = -100e^{-200t} + 100e^{-800t} \text{ V}$
 $\therefore v_o(t) = 80e^{-800t} - 80e^{-200t} \text{ V}, \quad t \geq 0$
 $= 80[e^{-800t} - e^{-200t}] \text{ V}, \quad t \geq 0$

P9.25 [a] $v_o(0^+) = 0$

[b] $20 \times 10^{-6} \frac{dv_o}{dt}(0^+) = 60 \times 10^{-3}; \quad \frac{dv_o(0^+)}{dt} = \frac{60,000}{20} = 3000 \text{ V/s}$

[c]

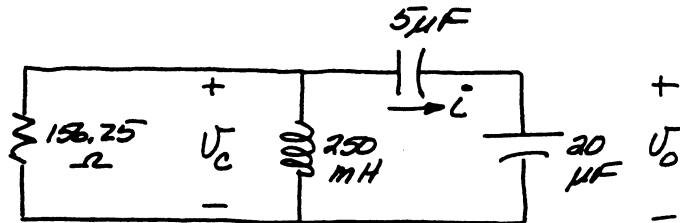

$\alpha = \frac{1}{2RC_e} = \frac{10^6}{(312.5)(4)} = 800; \quad \text{Note: } C_e = \frac{(5)(20)}{25} = 4 \mu\text{F}$
 $\omega_o^2 = \frac{1}{LC_e} = \frac{10^6}{(0.250)(4)} = 10^6$

$$\alpha^2 = 64 \times 10^4 = 0.64 \times 10^6$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}; \quad \omega_d = 600 \text{ rad/s}$$

$$\therefore v_C = V_f + B'_1 e^{-800t} \cos 600t + B'_2 e^{-800t} \sin 600t$$

$$V_f = 0, \quad v_C(0^+) = 0, \quad \therefore B'_1 = 0$$

$$\therefore v_C = B'_2 e^{-800t} \sin 600t$$

$$\frac{dv_C}{dt} = B'_2 [e^{-800t}(600) \cos 600t - 800e^{-800t} \sin 600t]$$

$$= B'_2 e^{-800t} [600 \cos 600t - 800 \sin 600t]$$

$$\frac{dv_C}{dt}(0^+) = 600B'_1$$

$$C_e \frac{dv_C}{dt}(0^+) = 60 \times 10^{-3}$$

$$\frac{dv_C(0^+)}{dt} = \frac{60,000}{4} = 15,000 \text{ V/s}$$

$$\therefore 600B'_2 = 15,000, \quad B'_2 = 25$$

$$v_C(t) = 25e^{-800t} \sin 600t \text{ V}$$

$$v_C = \frac{10^6}{5} \int_0^t i \, dt + \frac{10^6}{20} \int_0^t i \, dt = 4v_o + v_o = 5v_o$$

$$\therefore v_o(t) = \frac{1}{5} v_C(t)$$

$$v_o(t) = 5e^{-800t} \sin 600t \text{ V}, \quad t \geq 0$$

P9.26 [a] $\alpha = \frac{1}{2RC} = \frac{10^6}{20 \times 10^3(2.5)} = 20$

$$\alpha^2 = 400, \quad \omega_o^2 = \frac{1}{LC} = 20,000$$

$$\omega_o^2 > \alpha^2, \quad \therefore \text{underdamped}$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{19,600} = 140 \text{ rad/s}$$

$$\therefore i_L(t) = I_g + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$i_L(0) = I_g + B'_1$$

$$\frac{di_L(0)}{dt} = -\alpha B'_1 + \omega_d B'_2$$

$$\frac{1}{2}(2.5 \times 10^{-6})(56)^2 + \frac{1}{2}(20)i_L(0)^2 = 11.76 \times 10^{-3}$$

$$10i_L(0)^2 = 11.76 \times 10^{-3} - 3.92 \times 10^{-3} = 7.84 \times 10^{-3}$$

$$i_L(0)^2 = 7.84 \times 10^{-4}; \quad i_L(0) = \pm 2.8 \times 10^{-2} = \pm 28 \text{ mA}$$

$$\therefore B'_1 = \pm 28 - 7 \text{ mA}$$

$$\frac{di_L(0)}{dt} = \frac{v(0)}{L} = \frac{56}{20} = 2.8$$

$$\therefore -20B'_1 + 140B'_2 = 2.8$$

$$-B'_1 + 7B'_2 = 0.14$$

$$\therefore 7B'_2 = 0.14 + B'_1$$

$$\text{When } B'_1 = 21 \text{ mA, } 7B'_2 = 140 + 21; \quad B'_2 = 20 + 3 = 23 \text{ mA}$$

$$\text{When } B'_1 = -35 \text{ mA, } B'_2 = \frac{140 - 35}{7} = 15 \text{ mA}$$

$$\therefore i_L(t) = 7 + 21e^{-20t} \cos 140t + 23e^{-20t} \sin 140t \text{ mA, } t \geq 0$$

$$i_L(t) = 7 - 35e^{-20t} \cos 140t + 15e^{-20t} \sin 140t \text{ mA, } t \geq 0$$

$$[b] \quad v = L \frac{di_L}{dt} = 20 \frac{di_L}{dt}$$

$$\frac{di_L}{dt} = \frac{d}{dt}[-35 \cos 140t + 15 \sin 140t]e^{-20t} \times 10^{-3}$$

$$= 10^{-3}[-35 \cos 140t + 15 \sin 140t](-20e^{-20t})$$

$$+ 10^{-3}e^{-20t}[4900 \sin 140t + 2100 \cos 140t]$$

$$= 10^{-3}[700 \cos 140t - 300 \sin 140t + 4900 \sin 140t + 2100 \cos 140t]e^{-20t}$$

$$= (4.6 \sin 140t + 2.8 \cos 140t)e^{-20t}$$

$$v = (92 \sin 140t + 56 \cos 140t)e^{-20t} \text{ V, } t \geq 0$$

$$\frac{di_L}{dt} = \frac{d}{dt}[21 \cos 140t + 23 \sin 140t][e^{-20t}] \times 10^{-3}$$

$$= 10^{-3}[21 \cos 140t + 23 \sin 140t][-20e^{-20t}]$$

$$+ 10^{-3}[-2940 \sin 140t + 3220 \cos 140t]e^{-20t}$$

$$= 10^{-3}[-420 \cos 140t - 460 \sin 140t - 2940 \sin 140t + 3220 \cos 140t]e^{-20t}$$

$$= [2.8 \cos 140t - 3.4 \sin 140t]e^{-20t}$$

$$v = (56 \cos 140t - 68 \sin 140t)e^{-20t} \text{ V, } t \geq 0$$

$$\therefore \text{When } i = 7 + 21e^{-20t} \cos 140t + 23e^{-20t} \sin 140t \text{ mA}$$

$$v = (56 \cos 140t - 68 \sin 140t)e^{-20t} \text{ V}$$

$$\text{When } i = 7 - 35e^{-20t} \cos 140t + 15e^{-20t} \sin 140t \text{ mA}$$

$$v = (92 \sin 140t + 56 \cos 140t)e^{-20t} \text{ V}$$

$$[c] \quad \text{When } v = (56 \cos 140t - 68 \sin 140t)e^{-20t} \text{ V}$$

$$\frac{dv}{dt} = -20e^{-20t}(56 \cos 140t - 68 \sin 140t)$$

$$+ e^{-20t}(-7840 \sin 140t - 9520 \cos 140t)$$

$$= (-1120 \cos 140t + 1360 \sin 140t - 9520 \cos 140t - 7840 \sin 140t)e^{-20t}$$

$$= (-10,640 \cos 140t - 6480 \sin 140t)e^{-20t}$$

$$\frac{dv}{dt} = 0; \quad 10,640 \cos 140t + 6480 \sin 140t = 0$$

$$\tan 140t = -\frac{10,640}{6480} = -1.64$$

$$140t = -1.02 + \pi; \quad t = 15.13 \text{ ms}$$


$$v(15.13 \text{ ms}) = [56 \cos(2.12) - 68 \sin(2.12)]e^{-0.30} = -64.44 \text{ V}$$

$$\text{When } 140t = -1.02 + 2\pi, \quad t = 37.57 \text{ ms}$$

$$v(37.57) = 41.14 \text{ V}$$

$$\therefore v(t)_{\max} = 56 \text{ V}$$
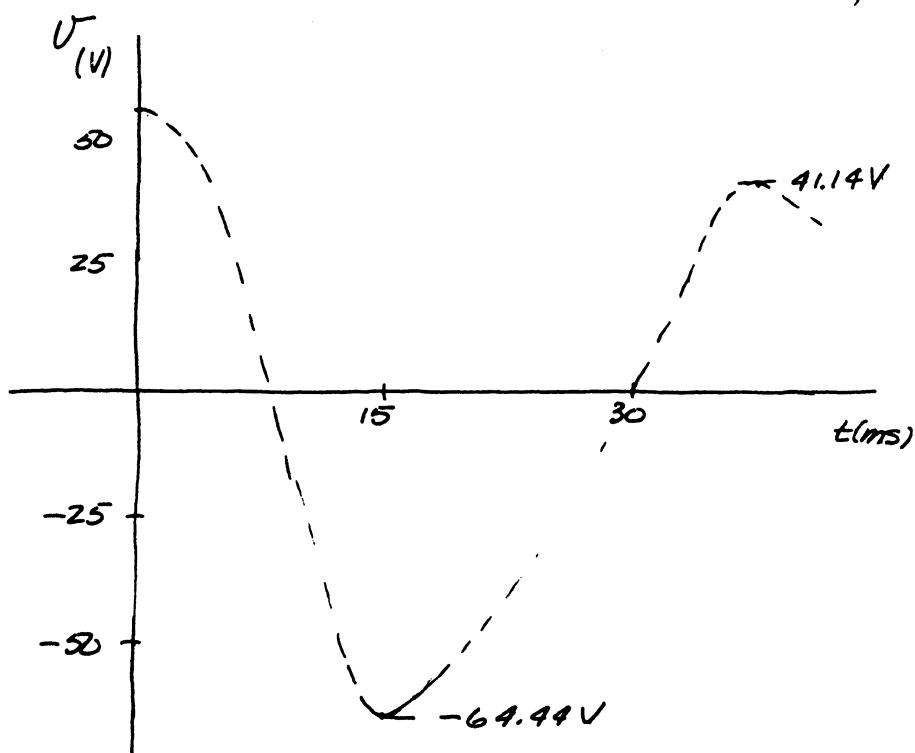
$$v = (56 \cos 140t - 68 \sin 140t)e^{-20t} \text{ V}$$



$$\text{When } v = (92 \sin 140t + 56 \cos 140t)e^{-20t} \text{ V}$$

$$\frac{dv}{dt} = (92 \sin 140t + 56 \cos 140t)(-20e^{-20t})$$

$$+ e^{-20t}(12,880 \cos 140t - 7840 \sin 140t)$$

$$= [12,880 \cos 140t - 1120 \cos 140t - 1840 \sin 140t - 7840 \sin 140t]e^{-20t}$$

$$= [11,760 \cos 140t - 9680 \sin 140t]e^{-20t}$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad \tan 140t = \frac{11,760}{9680} = 1.21$$


$$\therefore 140t = 0.88; \quad t = 6.30 \text{ ms}$$

$$v(6.30 \text{ ms}) = (92 \sin 0.88 + 56 \cos 0.88)e^{-0.13} = 94 \text{ V}$$

$$\text{When } 140t = 0.88 + \pi, \quad t = 28.74 \text{ ms}$$

$$v(28.74 \text{ ms}) = (92 \sin 4.02 + 56 \cos 4.02)e^{-0.57} = -60.01 \text{ V}$$

$$\therefore v_{\max} = 94 \text{ V}$$

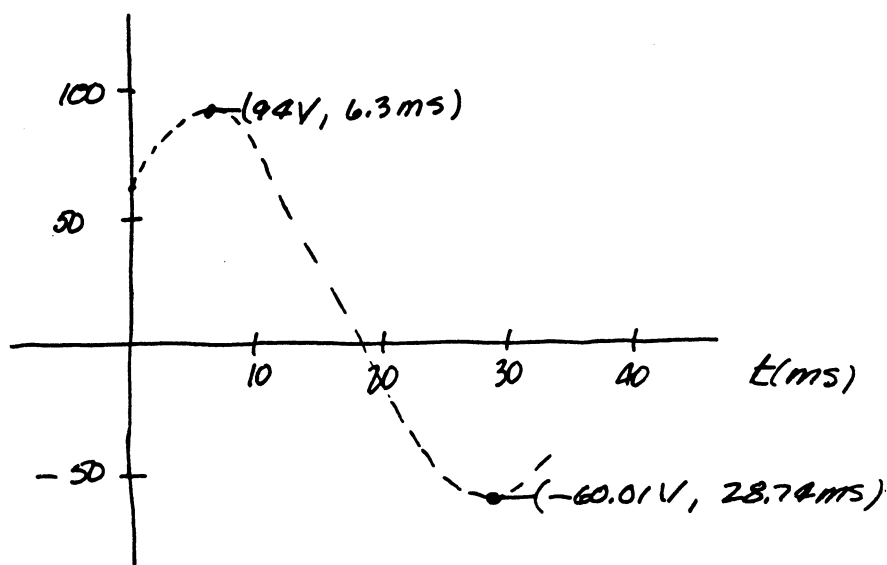

P 9.27 [a] $-\alpha + \sqrt{\alpha^2 - \omega_o^2} = -4000; \quad -\alpha - \sqrt{\alpha^2 - \omega_o^2} = -16,000$

$$\therefore \alpha = 10,000$$

$$\therefore \omega_o^2 = 64 \times 10^6$$

$$\therefore \frac{1}{LC} = 64 \times 10^6, \quad L = \frac{10^3}{(64)(31.25)} = 0.5 \text{ H}$$

$$\frac{R}{2L} = 10,000, \quad R = (2)(0.5)(10^4) = 10 \text{ k}\Omega$$

[b] $i(0^+) = 0$

$$\frac{1}{2}(31.25)[v_C(0^+)]^2 = 9 \times 10^{-6} \times 10^9$$


$$[v_C(0^+)]^2 = \frac{18,000}{31.25} = 576$$

$$v_C(0^+) = \sqrt{576} = 24 \text{ V}$$

$$\therefore 0.5 \frac{di(0^+)}{dt} = 24; \quad \frac{di(0^+)}{dt} = 48 \text{ A/s}$$

- [c] $i(t) = A_1 e^{-4000t} + A_2 e^{-16,000t}$
 $\therefore i(0^+) = A_1 + A_2 = 0, \quad A_2 = -A_1$
 $i(t) = A_1 [e^{-4000t} - e^{-16,000t}]$
 $\frac{di(t)}{dt} = A_1 [-4000e^{-4000t} + 16,000e^{-16,000t}]$
 $\frac{di(0^+)}{dt} = A_1 (12,000) = 48$
 $\therefore A_1 = 4 \times 10^{-3} = 4 \text{ mA}$
 $i(t) = 4[e^{-4000t} - e^{-16,000t}] \text{ mA}, \quad t \geq 0$
- [d] $\frac{di(t)}{dt} = 0$ when $16,000e^{-16,000t} = 4000e^{-4000t}$
 $\therefore 4 = e^{12,000t}; \quad 12,000t = \ln 4; \quad t = \frac{\ln 4}{0.012} \mu\text{s} = 115.52 \mu\text{s}$
- [e] $i_{\max} = 4[e^{-0.46} - e^{-1.85}] = 1.89 \text{ mA}$
- [f] $v_L(t) = 0.5(4 \times 10^{-3})[-4000e^{-4000t} + 16,000e^{-16,000t}]$
 $= 32e^{-16,000t} - 8e^{-4000t} \text{ V}, \quad t \geq 0$

P 9.28

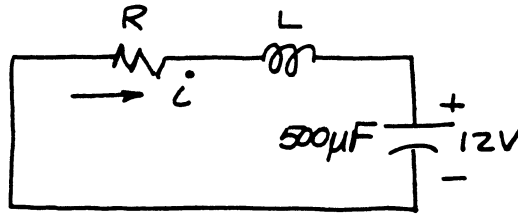

$$\frac{R}{2L} = 800 \quad \omega_d = 600 = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore 36 \times 10^4 = \omega_o^2 - (800)^2$$

$$\therefore \omega_o^2 = 10^6, \quad \omega_o = 1000 \text{ rad/s}$$

$$\therefore L = \frac{1}{10^6 C} = 2 \text{ mH}; \quad R = 1600(2 \times 10^{-3}) = 3.2 \Omega$$

$$i(0^+) = 0 = B_1$$

$$\frac{di(0^+)}{dt} = \frac{-12}{2 \times 10^{-3}} = -6000$$

$$\frac{di}{dt} = e^{-800t}[-B_1 600 \sin 600t + 600B_2 \cos 600t]$$

$$- 800e^{-800t}[B_1 \cos 600t + B_2 \sin 600t]$$

$$\frac{di(0^+)}{dt} = 600B_2 - 800B_1 = 600B_2$$

$$\therefore B_2 = \frac{-6000}{600} = -10 \text{ A}$$

P 9.29 From the solution to Problem 9.28 we know i is $i = -10e^{-800t} \sin 600t$ A, $t \geq 0$

$$\text{From the circuit we have } v_C = -iR - L \frac{di}{dt} = -3.2i - 2 \times 10^{-3} \frac{di}{dt}$$

$$\frac{di}{dt} = [-6000 \cos 600t + 8000 \sin 600t]e^{-800t}$$

$$\therefore v_C = 32e^{-800t} \sin 600t + [12 \cos 600t - 16 \sin 600t]e^{-800t}$$

$$= [12 \cos 600t + 16 \sin 600t]e^{-800t} \text{ V}, \quad t \geq 0$$

P 9.30 [a] $\omega_o^2 = \frac{1}{LC} = \frac{2 \times 10^6}{80 \times 10^{-3}} = 25 \times 10^6$

$$\therefore \alpha^2 = \omega_o^2 = 25 \times 10^6$$

$$\alpha = 5000 = \frac{R}{2L}, \quad R = (5000)(160) \times 10^{-3} = 800 \Omega$$

[b] $i(0) = 30 \text{ mA}$

$$v_C(0) = 800i(0) = 80 \times 10^{-3} \frac{di(0)}{dt}$$

$$\therefore \frac{20 - 800(30 \times 10^{-3})}{0.08} = \frac{di(0)}{dt}$$

$$\therefore \frac{di(0)}{dt} = \frac{20 - 24}{0.08} = -50 \text{ A/s}$$

[c] $v_C(t) = 800i + 0.08 \frac{di}{dt}$

$$i = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$i(0) = D_2 = 30 \times 10^{-3} = 30 \text{ mA}$$

$$\frac{di}{dt} = (D_1 t + D_2)(-5000e^{-5000t}) + e^{-5000t}(D_1)$$

$$\frac{di}{dt}(0) = -5000D_2 + D_1 = -50$$

$$\therefore D_1 = -50 + 5000(30 \times 10^{-3}) = 100$$

$$\therefore i = 10^5 t e^{-5000t} + 30e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$800i = 8 \times 10^7 t e^{-5000t} + 24,000e^{-5000t} \text{ mV} = 8 \times 10^4 t e^{-5000t} + 24e^{-5000t} \text{ V}$$

$$0.08 \frac{di}{dt} = 0.08 [(100t + 0.03)(-5000e^{-5000t}) + 100e^{-5000t}]$$

$$= -4 \times 10^4 t e^{-5000t} - 4e^{-5000t} \text{ V}$$

$$\therefore v_C(t) = 4 \times 10^4 t e^{-5000t} + 20e^{-5000t} \text{ V}$$

Alternate solution: Solve for $v_C(t)$ directly.

$$v_C(t) = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v_C(0) = D_2 = 20 \text{ V}$$


$$\frac{dv_C}{dt}(0) = -5000D_2 + D_1 = \frac{-30 \times 10^{-3}}{0.5 \times 10^{-6}}$$

$$\therefore -5000D_2 + D_1 = -60,000; \quad D_1 = -60,000 + 100,000 = 40,000$$

$$\therefore v_c(t) = 4 \times 10^4 t e^{-5000t} + 20e^{-5000t} \text{ V}, \quad t \geq 0$$

P 9.31 [a] $v_a(0) = v_c(0) = 72 \text{ V}$

[b] $t > 0$:

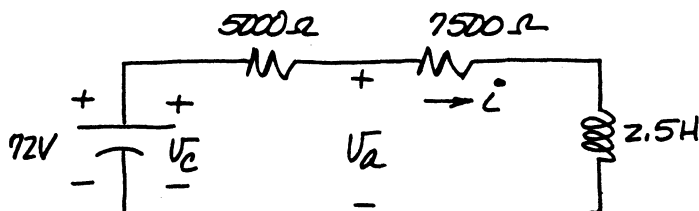

$$v_a = v_c - 5000i$$

$$\frac{dv_a}{dt} = \frac{dv_c}{dt} - 5000 \frac{di}{dt}$$

$$\frac{dv_c(0)}{dt} = 0 \quad \text{since } i(0) = 0; \quad \therefore \frac{dv_a(0)}{dt} = -5000 \frac{di(0)}{dt}$$

$$\frac{di(0)}{dt} = \frac{72}{2.5} = 28.80 \text{ A/s}; \quad \therefore \frac{dv_a(0)}{dt} = -144,000 \text{ V/s}$$

[c] $\alpha = \frac{R}{2L} = \frac{12,500}{5} = 2500 \text{ rad/s}; \quad \alpha^2 = 625 \times 10^4$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(0.1)(2.5)} = 4 \times 10^6 = 400 \times 10^4$$

$$\therefore \alpha^2 > \omega_o^2 \quad \text{overdamped}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -2500 + \sqrt{225 \times 10^4} = -2500 + 1500 = -1000 \text{ rad/s}$$

$$s_2 = -2500 - 1500 = -4000 \text{ rad/s}$$


$$v_a = A_1 e^{-1000t} + A_2 e^{-4000t}; \quad v_a(0) = A_1 + A_2 = 72$$

$$\frac{dv_a(0)}{dt} = -1000A_1 - 4000A_2 = -144,000$$

$$\therefore A_1 + 4A_2 = 144; \quad \therefore 3A_2 = 72, \quad A_2 = 24, \quad A_1 = 48$$

$$\therefore v_a = 48e^{-1000t} + 24e^{-4000t} \text{ V}, \quad t \geq 0$$


P 9.32 $t < 0$:

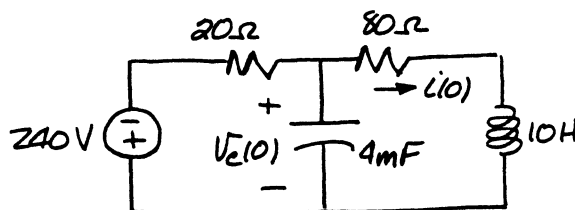

$$i(0) = -240/100 = -2.4 \text{ A}$$

$$v_C(0) = -240 - 20[i(0)] = -240 - 20(-2.4) = -240 + 48 = -192 \text{ V}$$

$t > 0$:

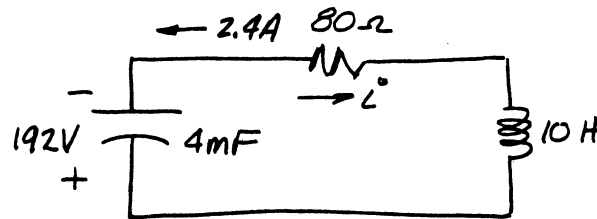

$$\alpha = \frac{R}{2L} = \frac{80}{20} = 4 \text{ rad/s}, \quad \alpha^2 = 16$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^3}{(10)(4)} = \frac{100}{4} = 25$$

$$\omega_o^2 > \alpha^2 \text{ underdamped}$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{25 - 16} = 3 \text{ rad/s}$$

$$\therefore i(t) = B_1 e^{-4t} \cos 3t + B_2 e^{-4t} \sin 3t$$

$$i(0) = B_1 = -2.4 \text{ A}$$

$$L \frac{di(0)}{dt} = -192 - 80[i(0)] = -192 - 80(-2.4) = -192 + 192 = 0$$


$$\frac{di(0)}{dt} = -4B_1 + 3B_2 = 0$$

$$\therefore B_2 = \frac{4}{3}B_1 = \frac{4}{3}(-2.4) = -3.2$$

$$\therefore i(t) = (-2.4 \cos 3t - 3.2 \sin 3t)e^{-4t}$$

$$i(t) = -(2.4 \cos 3t + 3.2 \sin 3t)e^{-4t} \text{ A}, \quad t \geq 0$$


P 9.33 $t < 0$:

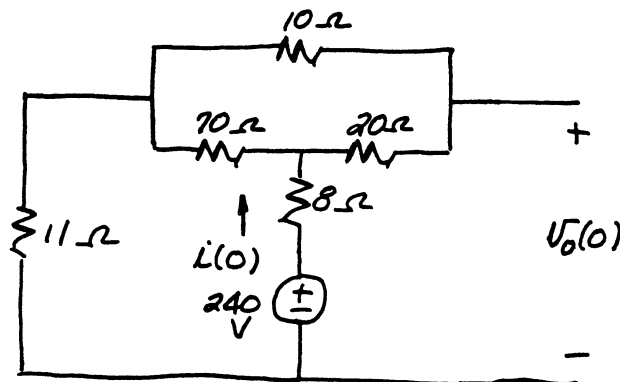

$$i(0) = \frac{240}{8 + 21 + 11} = \frac{240}{40} = 6 \text{ A}$$

$$v_o(0) = 240 - 6(8) - 20(6) \left(\frac{70}{100} \right) = 108 \text{ V}$$

$t > 0$:

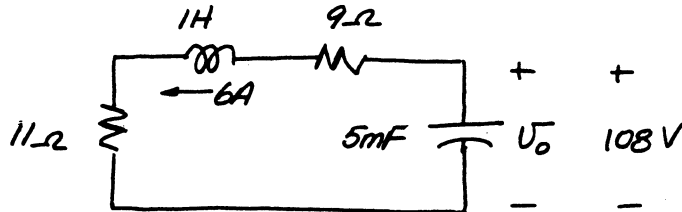

$$\alpha = \frac{R}{2L} = \frac{20}{2} = 10, \quad \alpha^2 = 100$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1000}{5} = 200$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}$$

$$v_o = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t; \quad \omega_d = \sqrt{200 - 100} = 10$$

$$v_o = B_1 e^{-10t} \cos 10t + B_2 e^{-10t} \sin 10t$$

$$v_o(0) = B_1 = 108 \text{ V}$$

$$C \frac{dv_o}{dt}(0) = -6, \quad \frac{dv_o}{dt} = \frac{-6}{5} \times 10^3 = -1200 \text{ V/s}$$

$$\frac{dv_o}{dt}(0) = -10B_1 + 10B_2 = -1200$$

$$10B_2 = -1200 + 10B_1 = -1200 + 1080$$

$$B_2 = -120/10 = -12 \text{ V}$$

$$\therefore v_o = 108e^{-10t} \cos 10t - 12e^{-10t} \sin 10t \text{ V}, \quad t \geq 0$$

P9.34 [a] $i_o(0) = \frac{80}{800} = 0.10 \text{ A}; \quad v_o(0) = 500(0.1) = 50 \text{ V}$

$$L \frac{di_o}{dt}(0) = 0; \quad \therefore \frac{di_o}{dt}(0) = 0$$

$$\alpha = \frac{R}{2L} = \frac{500}{5} \times 10^3 = 10^5; \quad \alpha^2 = 10^{10}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^9)}{(2.5)(40)} = 10^{10}$$

$$\therefore \omega_o^2 = \alpha^2 \quad \text{critically damped}$$

$$i_o(t) = D_1 t e^{-10^5 t} + D_2 e^{-10^5 t}$$

$$i_o(0) = D_2 = 0.10 \text{ A}$$

$$\frac{di_o}{dt}(0) = -\alpha D_2 + D_1 = 0; \quad D_1 = \alpha D_2 = 10^5(0.1) = 10^4$$

$$i_o(t) = 10^4 t e^{-10^5 t} + 0.1 e^{-10^5 t} \text{ A}, \quad t \geq 0$$

$$\begin{aligned}
 \text{[b]} \quad v_o(t) &= D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \\
 v_o(0) &= 50 = D_2 \\
 C \frac{dv_o}{dt}(0) &= -0.10; \quad \frac{dv_o}{dt} = -25 \times 10^5 \\
 \frac{dv_o}{dt}(0) &= -\alpha D_2 + D_1 = -25 \times 10^5; \quad D_1 = -25 \times 10^5 + 10^5(50) = 25 \times 10^5 \\
 \therefore v_o(t) &= 25 \times 10^5 t e^{-10^5 t} + 50 e^{-10^5 t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\text{P9.35} \quad \alpha = \frac{R}{2L} = \frac{250 \times 10^3}{(2)(62.5)} = 2000 \text{ rad/s}; \quad \alpha^2 = 4 \times 10^6$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^6)}{(62.5)(6.25)} = 2.56 \times 10^6$$

$$\alpha^2 > \omega_o^2 \text{ overdamped}$$

$$\therefore v_o(t) = V_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -2000 + 1200 = -800$$

$$s_2 = -2000 - 1200 = -3200$$

$$V_f = 60 \text{ V}$$

$$\therefore v_o(t) = 60 + A'_1 e^{-800t} + A'_2 e^{-3200t} \text{ V}$$

$$v_o(0) = 0 = 60 + A'_1 + A'_2$$

$$\frac{dv_o}{dt}(0) = 0 = -800A'_1 - 3200A'_2$$


$$\therefore -800A'_1 = 3200A'_2; \quad A'_1 = -4A'_2$$

$$\therefore 60 - 4A'_2 + A'_2 = 0; \quad A'_2 = 20 \text{ V}$$

$$\therefore A'_1 = -80 \text{ V}$$


$$\therefore v_o(t) = 60 - 80e^{-800t} + 20e^{-3200t} \text{ V}, \quad t \geq 0$$

P9.36 For $t < 0$:

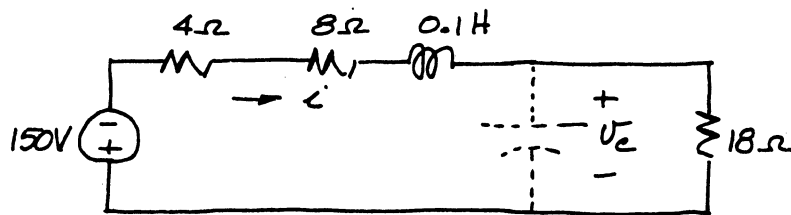

$$i = \frac{-150}{30} = -5 \text{ A}, \quad v_c(0) = 18i = -90 \text{ V}$$

$t > 0$:

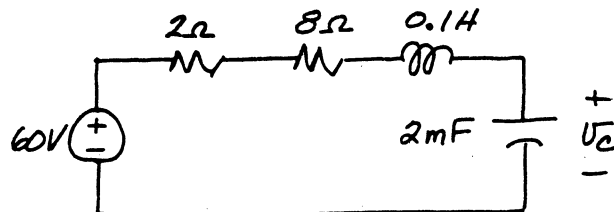

$$\alpha = \frac{R}{2L} = \frac{10}{0.2} = 50 \text{ rad/s}; \quad \alpha^2 = 2500$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^3}{(0.1)(2)} = 5000$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}; \quad \omega_d = 50 \text{ rad/s}$$

$$\therefore v_C = 60 + B_1 e^{-50t} \cos 50t + B_2 e^{-50t} \sin 50t$$

$$v_C(0) = -90 = 60 + B_1; \quad B_1 = -150 \text{ V}$$

$$C \frac{dv_C}{dt} = -5, \quad \frac{dv_C}{dt} = \frac{-5}{2} \times 10^3 = -2500$$

$$\frac{dv_C}{dt}(0) = -\alpha B_1 + \omega_d B_2 = -2500$$

$$-50B_1 + 50B_2 = -2500$$

$$-B_1 + B_2 = -50; \quad \therefore B_2 = -50 + B_1 = -50 - 150 = -200 \text{ V}$$

$$\therefore v_C = 60 - 150e^{-50t} \cos 50t - 200e^{-50t} \sin 50t \text{ V}, \quad t \geq 0$$

P9.37 $\alpha = \frac{10}{0.4} = 25 \text{ rad/s}, \quad \alpha^2 = 625$

$$\omega_o^2 = \frac{1000}{(0.2)(8)} = 625$$

$$\alpha^2 = \omega_o^2 \quad \text{critical damping}$$


$$v_C = 400 + D'_1 t e^{-25t} + D'_2 e^{-25t}$$

$$v_C(0) = 100 = 400 + D'_2, \quad D'_2 = -300$$

$$\frac{dv_C}{dt}(0) = 0 = -25D'_2 + D'_1; \quad \therefore D'_1 = 25D'_2 = 25(-300) = -7500$$


$$\therefore v_C(t) = 400 - 7500te^{-25t} - 300e^{-25t} \text{ V}, \quad t \geq 0$$

P9.38 [a] $t < 0$:

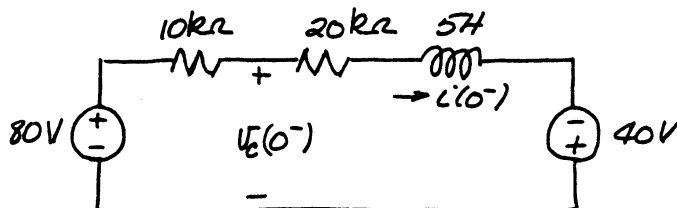

$$i(0^-) = \frac{120}{30} = 4 \text{ mA}; \quad v_C(0^-) = 80 - 10(4) = 40 \text{ V}$$

$$t = 0^+:$$

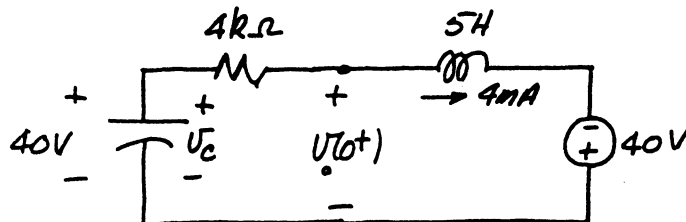

$$v_o(0^+) = 40 - 4(4) = 40 - 16 = 24 \text{ V}$$

$$[b] \quad v_o = v_C - 4000i$$

$$\frac{dv_o}{dt} = \frac{dv_C}{dt} - 4000 \frac{di}{dt}$$

$$\frac{dv_o}{dt}(0^+) = \frac{dv_C}{dt}(0^+) - 4000 \frac{di}{dt}(0^+)$$

$$\frac{dv_C}{dt}(0^+) = \frac{-4 \times 10^{-3}}{(125/64) \times 10^{-6}} = \frac{-256,000}{125} = -2048 \text{ V/s}$$

$$\frac{di(0^+)}{dt} = \frac{64}{5} = 12.8 \text{ A/s}$$

$$\frac{dv_o(0^+)}{dt} = -2048 - 4000(12.8) = -53,248 \text{ V/s}$$

$$[c] \quad \alpha = \frac{R}{2L} = \frac{4000}{10} = 400, \quad \alpha^2 = 16 \times 10^4$$

$$\omega_o^2 = \frac{64 \times 10^6}{(5)(125)} = 10.24 \times 10^4$$

$$\alpha^2 > \omega_o^2 \quad \text{overdamped}$$

$$s_1 = -400 + \sqrt{(16 - 10.24)10^4} = -400 + 240 = -160 \text{ rad/s}$$

$$s_2 = -640 \text{ rad/s}$$

$$v_o = -40 + A'_1 e^{-160t} + A'_2 e^{-640t}$$

$$v_o(0^+) = 24 = -40 + A'_1 + A'_2; \quad \therefore A'_1 + A'_2 = 64$$


$$\frac{dv_o}{dt}(0^+) = -160A'_1 - 640A'_2 = -53,248$$

$$\therefore A'_1 + 4A'_2 = 332.80$$


$$\therefore 3A'_2 = 268.80; \quad A'_2 = 89.60 \text{ V}; \quad \therefore A'_1 = -25.60 \text{ V}$$

$$\therefore v_o(t) = -40 - 25.60e^{-160t} + 89.60e^{-640t} \text{ V}, \quad t \geq 0^+$$

P9.39 For $t < 0$:

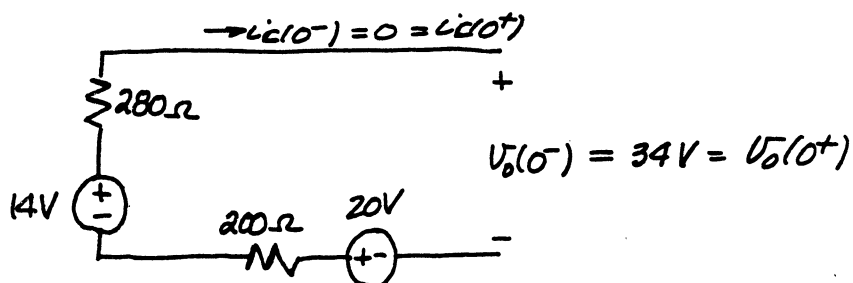

For $t > 0$:

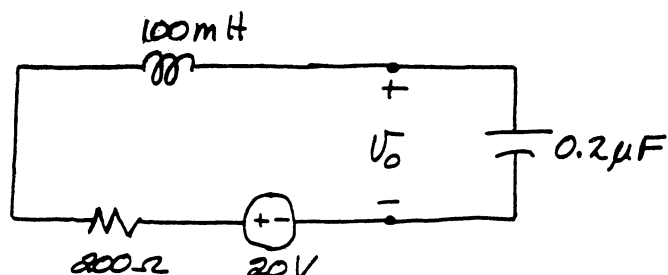

$$\alpha = \frac{R}{2L} = \frac{200}{0.2} = 1000, \quad \alpha^2 = 10^6$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^6)}{100(0.2)} = 50 \times 10^6$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}$$

$$s_{1,2} = -1000 \pm j7000 \text{ rad/s}$$

$$v_o = v_F + B'_1 e^{-1000t} \cos 7000t + B'_2 e^{-1000t} \sin 7000t, \quad v_F = 20 \text{ V}$$

$$v_o(0) = 20 + B'_1 = 34; \quad B'_1 = 34 - 20 = 14 \text{ V}$$


$$\frac{dv}{dt} = e^{-1000t} [-7000B'_1 \sin 7000t + 7000B'_2 \cos 7000t]$$

$$+ [B'_1 \cos 7000t + B'_2 \sin 7000t](-1000e^{-1000t})$$

$$\frac{dv}{dt}(0^+) = 7000B'_2 - 1000B'_1$$


$$\frac{dv}{dt}(0^+) = 0 \quad \text{since } i_C(0^+) = 0; \quad \therefore B'_2 = \frac{1}{7}B'_1 = \frac{1}{7}(14) = 2 \text{ V}$$

$$\therefore v_o = 20 + 14e^{-1000t} \cos 7000t + 2e^{-1000t} \sin 7000t \text{ V}, \quad t \geq 0$$

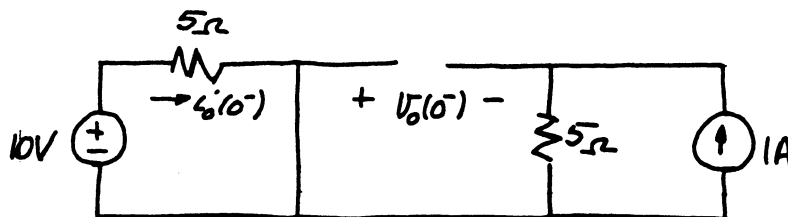P9.40 [a] $t < 0$:

$$i_o(0^-) = 10/5 = 2 \text{ A} = i_o(0^+)$$

$$v_o(0^-) = -5(1) = -5 \text{ V} = v_o(0^+)$$

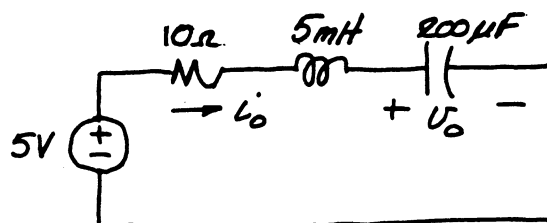
 $t > 0^+$:

$$\alpha = \frac{R}{2L} = \frac{10}{10} \times 1000 = 1000 \text{ rad/s}; \quad \omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^6)}{(5)(200)} = 10^6$$

$$\alpha^2 = \omega^2 \quad \therefore \text{critically damped}$$

$$\therefore i_o = i_F + D'_1 t e^{-1000t} + D'_2 e^{-1000t}; \quad i_F = 0$$

$$\therefore i_o = D'_1 t e^{-1000t} + D'_2 e^{-1000t}; \quad i_o(0^+) = D'_2 = 2$$

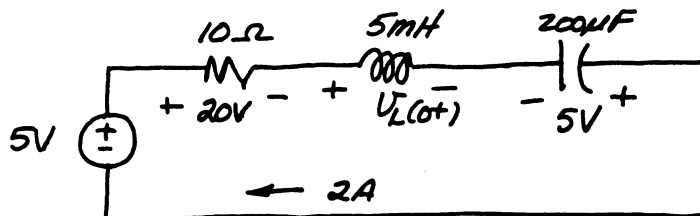At $t = 0^+$:

$$-5 + 20 + v_L(0^+) - 5 = 0, \quad v_L(0^+) = -10 \text{ V}$$

$$\therefore \frac{di}{dt}(0^+) = \frac{-10}{5} \times 10^3 = -2000 \text{ A/s}$$

$$\frac{di_o}{dt} = -1000e^{-1000t}(D'_1 t + D'_2) + e^{-1000t}D'_1$$

$$\frac{di_o}{dt}(0^+) = -1000D'_2 + D'_1 = -2000$$

$$-2000 + D'_1 = -2000; \quad D'_1 = 0$$

$$\therefore i_o(t) = 2e^{-1000t} \text{ A}, \quad t \geq 0$$

$$[b] \quad v_o = v_F + D'_3te^{-1000t} + D'_4e^{-1000t}$$

$$v_o(0^+) = v_F + D'_4 = -5$$

$$v_F = 5 \text{ V}; \quad \therefore D'_4 = -10 \text{ V}$$

$$v_o = 5 + D'_3te^{-1000t} - 10e^{-1000t}$$

$$\frac{dv_o}{dt} = -1000e^{-1000t}(D'_3t - 10) + D'_3e^{-1000t}$$

$$\frac{dv_o}{dt}(0^+) = 10,000 + D'_3$$

$$\frac{dv_o}{dt}(0^+) = \frac{2}{200} \times 10^6 = 10^4 = 10,000$$

$$\therefore D'_3 = 0$$

$$\therefore v_o = 5 - 10e^{-1000t} \text{ V}, \quad t \geq 0$$

P 9.41 [a] $v_c = V_f + [A'_1 \cos \omega_d t + A'_2 \sin \omega_d t] e^{-\alpha t}$

$$\frac{dv_c}{dt} = [(\omega_d A'_2 - \alpha A'_1) \cos \omega_d t - (\alpha A'_2 + \omega_d A'_1) \sin \omega_d t] e^{-\alpha t}$$

Since the initial stored energy is zero, $v_c(0^+) = 0$ and $\frac{dv_c(0^+)}{dt} = 0$

It follows that $A'_1 = -V_f$ and $A'_2 = \frac{\alpha A'_1}{\omega_d}$

When these values are substituted into the expression for $[dv_c/dt]$, we get

$$\frac{dv_c}{dt} = \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) V_f e^{-\alpha t} \sin \omega_d t$$

But $V_f = V$ and $\frac{\alpha^2}{\omega_d} + \omega_d = \frac{\alpha^2 + \omega_d^2}{\omega_d} = \frac{\omega_o^2}{\omega_d}$

Therefore $\frac{dv_c}{dt} = \left(\frac{\omega_o^2}{\omega_d} \right) V e^{-\alpha t} \sin \omega_d t$

[b] $\frac{dv_c}{dt} = 0$ when $\sin \omega_d t = 0$, or $\omega_d t = n\pi$ where $n = 1, 2, 3, \dots$

Therefore $t = \frac{n\pi}{\omega_d}$

[c] When $t_n = \frac{n\pi}{\omega_d}$, $\cos \omega_d t_n = \cos n\pi = (-1)^n$ and $\sin \omega_d t = \sin n\pi = 0$

Therefore $v_c(t_n) = V[1 - (-1)^n e^{-\alpha n\pi/\omega_d}]$

[d] It follows from [c] that

$$v_c(t_1) = V + Ve^{-(\alpha\pi/\omega_d)} \quad \text{and} \quad v_c(t_3) = V + Ve^{-(3\alpha\pi/\omega_d)}$$

$$\text{Therefore } \frac{v_c(t_1) - V}{v_c(t_3) - V} = \frac{e^{-(\alpha\pi/\omega_d)}}{e^{-(3\alpha\pi/\omega_d)}} = e^{(2\alpha\pi/\omega_d)}$$

$$\text{But } \frac{2\pi}{\omega_d} = t_3 - t_1 = T_d, \quad \text{thus } \alpha = \frac{1}{T_d} \ln \frac{[v_c(t_1) - V]}{[v_c(t_3) - V]}$$

$$\mathbf{P9.42} \quad \frac{1}{T_d} \ln \left\{ \frac{v_c(t_1) - V}{v_c(t_3) - V} \right\}; \quad T_d = t_3 - t_1 = \frac{3\pi}{7} - \frac{\pi}{7} = \frac{2\pi}{7} \text{ ms}$$

$$\alpha = \frac{7000}{2\pi} \ln \left[\frac{63.84}{26.02} \right] = 999.91; \quad \omega_d = \frac{2\pi}{T_d} = 7000 \text{ rad/s}$$

$$\omega_o^2 = \omega_d^2 + \alpha^2 = 49 \times 10^6 + 0.9998 \times 10^6 = 49.9998 \times 10^6 \approx 50$$

$$L = \frac{1}{(49.9998)(0.1)} = 0.20 \text{ H}; \quad R = 2\alpha L = (0.4)(999.91) = 399.96 \Omega$$

P9.43 [a] Let i be the current in the direction of the voltage drop $v_o(t)$. Then by hypothesis

$$i = i_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$i_f = i(\infty) = 0, \quad i(0) = \frac{V_g}{R} = B'_1$$

$$\text{Therefore } i = B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$L \frac{di(0)}{dt} = 0, \quad \text{therefore } \frac{di(0)}{dt} = 0$$

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

$$\text{Therefore } \omega_d B'_2 - \alpha B'_1 = 0; \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha}{\omega_d} \frac{V_g}{R}$$

Therefore

$$\begin{aligned} v_L &= L \frac{di}{dt} = - \left\{ L \left(\frac{\alpha^2 V_g}{\omega_d R} + \frac{\omega_d V_g}{R} \right) \sin \omega_d t \right\} e^{-\alpha t} \\ &= - \left\{ \frac{L V_g}{R} \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) \sin \omega_d t \right\} e^{-\alpha t} = - \frac{V_g L}{R} \left(\frac{\alpha^2 + \omega_d^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\ v_L &= - \frac{V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t \end{aligned}$$

$$[b] \quad \frac{dv_L}{dt} = - \frac{V_g}{\omega_d RC} \{ \omega_d \cos \omega_d t - \alpha \sin \omega_d t \} e^{-\alpha t}$$

$$\frac{dv_L}{dt} = 0 \quad \text{when} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}$$

$$\text{Therefore } \omega_d t = \tan^{-1}(\omega_d/\alpha) \quad (\text{smallest } t)$$

$$t = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

$$\mathbf{P9.44} \quad [\mathbf{a}] \quad \alpha = \frac{R}{2L} = \frac{600}{40} \times 10^3 = 15,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^6)}{(20)(0.08)} = 0.625 \times 10^9 = 625 \times 10^6$$

$$\omega_d = \sqrt{625 \times 10^6 - 225 \times 10^6} = 20,000 \text{ rad/s}$$

$$\frac{-V_g}{\omega_d RC} = \frac{+480 \times 10^6}{(2 \times 10^4)(600)(0.08)} = 500 \text{ V}$$

$$v_o = 500e^{-15,000t} \sin 20,000t \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad t_{\max} = \frac{1}{\omega_d} \tan^{-1} \frac{\omega_d}{\alpha} = 50 \tan^{-1} \left(\frac{4}{3} \right) \mu\text{s} \cong 46.36 \mu\text{s}$$

$$[\mathbf{c}] \quad v_o(\max) = 500e^{-0.015(46.36)} \sin(0.02)(46.36) \cong 199.54 \text{ V}$$

$$[\mathbf{d}] \quad R = 60 \Omega, \quad \alpha = 1500 \text{ rad/s}$$

$$\omega_d = \sqrt{(625 - 2.25)10^6} = 24,954.96 \text{ rad/s}$$

$$\frac{-V_g}{\omega_d RC} = \frac{+480}{(24,954.96)(60)(0.08 \times 10^{-6})} = 4007.22 \text{ V}$$

$$v_o = 4007.22e^{-1500t} \sin 24,954.96t \text{ V}, \quad t \geq 0^+$$

$$t_{\max} = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) = 40.07 \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) \mu\text{s} \cong 60.54 \mu\text{s}$$

$$v_o(\max) = 4007.22e^{-0.0015(60.54)} \sin[0.02495496(60.54)] \cong 3652.77 \text{ V}$$

$$\mathbf{P9.45} \quad [\mathbf{a}] \quad \frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1 R_2 C_2} v_g$$

$$\frac{1}{R_1 C_1 R_2 C_2} = \frac{10^{-6}}{(100)(400)(0.5)(0.2) \times 10^{-6} \times 10^{-6}} = 250$$

$$\therefore \frac{d^2 v_o}{dt^2} = 250 v_g$$

$$0 \leq t \leq 0.5^-:$$

$$v_g = 80 \text{ mV}$$

$$\therefore \frac{d^2 v_o}{dt^2} = 20, \quad \text{let } g(t) = \frac{dv_o}{dt}, \quad \text{then } \frac{dg}{dt} = 20 \quad \text{or } dg = 20 dt$$

$$\therefore \int_{g(0)}^{g(t)} dx = 20 \int_0^t dy; \quad g(t) - g(0) = 20t, \quad g(0) = \frac{dv_o}{dt}(0) = 0$$

$$\therefore g(t) = \frac{dv_o}{dt} = 20t$$

$$\therefore dv_o = 20t dt$$

$$\therefore \int_{v_o(0)}^{v_o(t)} dx = 20 \int_0^t x dx; \quad v_o(t) - v_o(0) = 10t^2, \quad v_o(0) = 0$$

$$\therefore v_o(t) = 10t^2 \text{ V}, \quad 0 \leq t \leq 0.5^-$$

$$\frac{dv_{o1}}{dt} = -\frac{1}{R_1 C_1} v_g = -20 v_g = -1.6$$

$$\therefore dv_{o1} = -1.6 dt$$

$$\int_{v_{o1}(0)}^{v_{o1}(t)} dx = -1.6 \int_0^t dy; \quad v_{o1}(t) - v_{o1}(0) = -1.6t, \quad v_{o1}(0) = 0$$

$$v_{o1}(t) = -1.6t \text{ V}, \quad 0 \leq t \leq 0.5^-$$

$$0.5^+ \leq t \leq t_{\text{sat}}:$$

$$\frac{d^2 v_o}{dt^2} = -10, \quad \text{let } g(t) = \frac{dv_o}{dt}$$

$$\frac{dg(t)}{dt} = -10$$

$$dg(t) = -10 dt$$

$$\int_{g(0.5^+)}^{g(t)} dx = -10 \int_{0.5}^t dy$$

$$g(t) - g(0.5^+) = -10(t - 0.5) = -10t + 5, \quad g(0.5^+) = \frac{dv_o(0.5^+)}{dt}$$

$$C \frac{dv_o}{dt}(0.5^+) = \frac{0 - v_{o1}(0.5^+)}{400 \times 10^3}$$

$$v_{o1}(0.5^+) = v_o(0.5^-) = -1.6(0.5) = -0.80 \text{ V}$$

$$\therefore C \frac{dv_{o1}(0.5^+)}{dt} = \frac{0.80}{0.4 \times 10^{-6}} = 2 \mu\text{A}$$

$$\frac{dv_{o1}}{dt}(0.5^+) = \frac{2 \times 10^{-6}}{0.2 \times 10^{-6}} = 10 \text{ V/s}$$

$$\therefore g(t) = -10t + 5 + 10 = -10t + 15 = \frac{dv_o}{dt}$$

$$\therefore dv_o = -10t dt + 15 dt$$

$$\int_{v_o(0.5^+)}^{v_o(t)} dx = \int_{0.5^+}^t -10y dy + \int_{0.5^+}^t 15 dy$$

$$v_o(t) - v_o(0.5^+) = -5y^2 \Big|_{0.5}^t + 15y \Big|_{0.5}^t$$

$$v_o(t) = v_o(0.5^+) - 5t^2 + 1.25 + 15t - 7.5$$

$$v_o(0.5^+) = v_o(0.5^-) = 2.5 \text{ V}$$

$$\therefore v_o(t) = -5t^2 + 15t - 3.75 \text{ V}, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

$$\frac{dv_{o1}}{dt} = -20(-40 \times 10^{-3}) = 0.8, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

$$dv_{o1} = 0.8 dt$$

$$\int_{v_{o1}(0.5^+)}^{v_{o1}(t)} dx = 0.8 \int_{0.5^+}^t dy$$

$$v_{o1}(t) - v_{o1}(0.5^+) = 0.8t - 0.4; \quad v_{o1}(0.5^+) = v_{o1}(0.5^-) = -0.8 \text{ V}$$

$$\therefore v_{o1}(t) = 0.8t - 1.2 \text{ V}, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

Summary

$$0 \leq t \leq 0.5^- \text{ s}: \quad v_{o1} = -1.6t \text{ V}, \quad v_o = 10t^2 \text{ V}$$

$$0.5^+ \text{ s} \leq t \leq t_{\text{sat}}: \quad v_{o1} = 0.8t - 1.2 \text{ V}, \quad v_o = -5t^2 + 15t - 3.75 \text{ V}$$

$$\begin{aligned}
 [b] \quad & -12.5 = -5t_{\text{sat}}^2 + 15t_{\text{sat}} - 3.75 \\
 & \therefore 5t_{\text{sat}}^2 - 15t_{\text{sat}} - 8.75 = 0 \\
 & t_{\text{sat}}^2 - 3t_{\text{sat}} - 1.75 = 0 \\
 & t_{\text{sat}} = 1.5 \pm \sqrt{2.25 + 1.75} = 1.5 \pm 2 \\
 & \therefore t_{\text{sat}} = 3.5 \text{ sec} \\
 & v_{o1}(t_{\text{sat}}) = 0.8(3.5) - 1.2 = 1.6 \text{ V}
 \end{aligned}$$

P9.46 $\tau_1 = (10^6)(0.5 \times 10^{-6}) = 0.50 \text{ s}$

$$\frac{1}{\tau_1} = 2; \quad \tau_2 = (5 \times 10^6)(0.2 \times 10^{-6}) = 1 \text{ s}; \quad \therefore \frac{1}{\tau_2} = 1$$

$$\therefore \frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2 = 20$$

$$s^2 + 3s + 2 = 0$$

$$(s+1)(s+2) = 0; \quad s_1 = -1, \quad s_2 = -2$$

$$v_o = V_f + A'_1 e^{-t} + A'_2 e^{-2t}; \quad V_f = \frac{20}{2} = 10 \text{ V}$$

$$v_o = 10 + A'_1 e^{-t} + A'_2 e^{-2t}$$

$$v_o(0) = 0 = 10 + A'_1 + A'_2; \quad \frac{dv_o}{dt}(0) = 0 = -A'_1 - 2A'_2$$

$$\therefore A'_1 = -2A'_2, \quad A'_2 = 10 \text{ V}, \quad A'_1 = -20 \text{ V}$$


$$v_o(t) = 10 - 20e^{-t} + 10e^{-2t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = -1.6; \quad \therefore v_{o1} = -0.8 + 0.8e^{-2t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$

$$v_o(0.5) = 10 - 20e^{-0.5} + 10e^{-1} = 1.55 \text{ V}$$

$$v_{o1}(0.5) = -0.8 + 0.8e^{-1} = -0.51 \text{ V}$$

At $t = 0.5 \text{ s}$

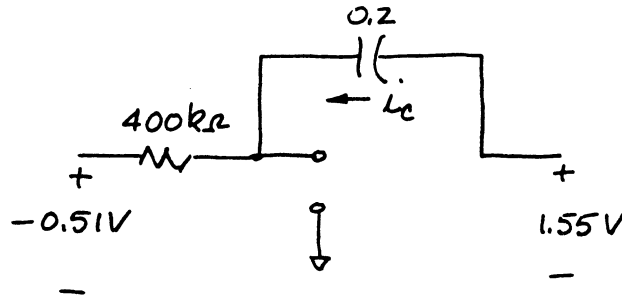

$$i_C = \frac{0 + 0.51}{0.400 \times 10^6} = 1.26 \mu\text{A}; \quad C \frac{dv_o}{dt} = 1.26 \mu\text{A}; \quad \frac{dv_o}{dt} = \frac{1.26}{0.2} = 6.32 \text{ V/s}$$

$$0.5 \text{ s} \leq t \leq \infty$$

$$\frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2 = -10$$

$$v_o(\infty) = -5$$

$$\therefore v_o = -5 + A'_1 e^{-(t-0.5)} + A'_2 e^{-2(t-0.5)}$$

$$1.55 = -5 + A'_1 + A'_2$$

$$\frac{dv_o}{dt}(0.5) = 6.32 = -A'_1 - 2A'_2$$


$$\therefore A'_1 + A'_2 = 6.55; \quad -A'_1 - 2A'_2 = 6.32$$

$$-A'_2 = 12.87; \quad A'_2 = -12.87; \quad A'_1 = 6.55 - A'_2 = 19.42$$

$$\therefore v_o = -5 + 19.42e^{-(t-0.5)} - 12.87e^{-2(t-0.5)} \text{ V}, \quad 0.5 \leq t \leq \infty$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = 0.8$$

$$\therefore v_{o1} = 0.4 + (-0.51 - 0.40)e^{-2(t-0.5)} = 0.4 - 0.91e^{-2(t-0.5)} \text{ V}, \quad 0.5 \leq t \leq \infty$$

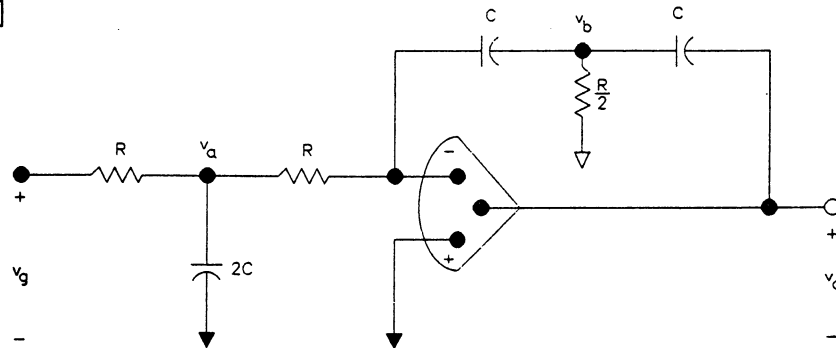P 9.47 [a]

$$2C \frac{dv_a}{dt} + \frac{v_a - v_g}{R} + \frac{v_a}{R} = 0$$

$$(1) \text{ Therefore } \frac{dv_a}{dt} + \frac{v_a}{RC} = \frac{v_g}{2RC}; \quad \frac{0 - v_a}{R} + C \frac{d(0 - v_b)}{dt} = 0$$

$$(2) \text{ Therefore } \frac{dv_b}{dt} + \frac{v_a}{RC} = 0, \quad v_a = -RC \frac{dv_b}{dt}$$

$$\frac{2v_b}{R} + C \frac{dv_b}{dt} + C \frac{d(v_b - v_o)}{dt} = 0$$

$$(3) \text{ Therefore } \frac{dv_b}{dt} + \frac{v_b}{RC} = \frac{1}{2} \frac{dv_o}{dt}$$

$$\text{From (2) we have } \frac{dv_a}{dt} = -RC \frac{d^2 v_b}{dt^2} \text{ and } v_a = -RC \frac{dv_b}{dt}$$

When these are substituted into (1) we get

$$(4) \quad -RC \frac{d^2 v_b}{dt^2} - \frac{dv_b}{dt} = \frac{v_g}{2RC}$$

Now differentiate (3) to get

$$(5) \quad \frac{d^2 v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = \frac{1}{2} \frac{d^2 v_o}{dt^2}$$

But from (4) we have

$$(6) \frac{d^2 v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = -\frac{v_g}{2R^2C^2}$$

Now substitute (6) into (5)

$$\frac{d^2 v_o}{dt^2} = -\frac{v_g}{R^2C^2}$$

$$[b] \quad \text{When } R_1C_1 = R_2C_2 = RC : \quad \frac{d^2 v_o}{dt^2} = \frac{v_g}{R^2C^2}$$

The two equations are the same except for a reversal in algebraic sign.

[c] Two integrations of the input signal with one operational amplifier.

P 9.48 [a] $f(t)$ = inertial force + frictional force + spring force
 $= M[d^2x/dt^2] + D[dx/dt] + Kx$

$$[b] \quad \frac{d^2x}{dt^2} = \frac{f}{M} - \left(\frac{D}{M}\right) \left(\frac{dx}{dt}\right) - \left(\frac{K}{M}\right) x$$

Given $v_A = \frac{d^2x}{dt^2}$, then

$$v_B = -\frac{1}{R_1C_1} \int_0^t \left(\frac{d^2x}{dy^2}\right) dy = -\frac{1}{R_1C_1} \frac{dx}{dt}$$

$$v_C = -\frac{1}{R_2C_2} \int_0^t v_B dy = \frac{1}{R_1R_2C_1C_2} x$$

$$v_D = -\frac{R_3}{R_4} \cdot v_B = \frac{R_3}{R_4R_1C_1} \frac{dx}{dt}$$

$$v_E = \left[\frac{R_5 + R_6}{R_6}\right] v_C = \left[\frac{R_5 + R_6}{R_6}\right] \cdot \frac{1}{R_1R_2C_1C_2} \cdot x$$

$$v_F = \left[\frac{-R_8}{R_7}\right] f(t), \quad v_A = -(v_D + v_E + v_F)$$

$$\text{Therefore } \frac{d^2x}{dt^2} = \left[\frac{R_8}{R_7}\right] f(t) - \left[\frac{R_3}{R_4R_1C_1}\right] \frac{dx}{dt} - \left[\frac{R_5 + R_6}{R_6R_1R_2C_1C_2}\right] x$$

$$\text{Therefore } M = \frac{R_7}{R_8}, \quad D = \frac{R_3R_7}{R_8R_4R_1C_1} \quad \text{and} \quad K = \frac{R_7(R_5 + R_6)}{R_8R_6R_1R_2C_1C_2}$$

Box Number	Function
1	inverting and scaling
2	inverting and summing
3	integrating and scaling
4	integrating and scaling
5	inverting and scaling
6	noninverting and scaling

P9.49 From the form of the solution we have

$$v(0) = A_1 + A_2$$

$$\frac{dv(0^+)}{dt} = -\alpha(A_1 + A_2) + j\omega_d(A_1 - A_2)$$

We know both $v(0)$ and $dv(0^+)/dt$ will be real numbers. To facilitate the algebra we let these numbers be K_1 and K_2 , respectively. Then our two simultaneous equations are

$$K_1 = A_1 + A_2$$

$$K_2 = (-\alpha + j\omega_d)A_1 + (-\alpha - j\omega_d)A_2$$

The characteristic determinate is $\Delta = \begin{vmatrix} 1 & 1 \\ (-\alpha + j\omega_d) & (-\alpha - j\omega_d) \end{vmatrix} = -j2\omega_d$

The numerator determinates are $N_1 = \begin{vmatrix} K_1 & 1 \\ K_2 & (-\alpha - j\omega_d) \end{vmatrix} = -(\alpha + j\omega_d)K_1 - K_2$

and $N_2 = \begin{vmatrix} 1 & K_1 \\ (-\alpha + j\omega_d) & K_2 \end{vmatrix} = K_2 + (\alpha - j\omega_d)K_1$

It follows that $A_1 = \frac{N_1}{\Delta} = \frac{\omega_d K_1 - j(\alpha K_1 + K_2)}{2\omega_d}$

and $A_2 = \frac{N_2}{\Delta} = \frac{\omega_d K_1 + j(\alpha K_1 + K_2)}{2\omega_d}$

We see from these expressions that $A_1 = A_2^*$

P9.50 By definition $B_1 = A_1 + A_2$

From the solution to Problem 9.49 we have $A_1 + A_2 = \frac{2\omega_d K_1}{2\omega_d} = K_1$

But K_1 is $v(0)$, therefore $B_1 = v(0)$, which is identical to Eq. (9.27).

By definition $B_2 = j(A_1 - A_2)$

From Problem 9.49 we have $B_2 = j(A_1 - A_2) = \frac{j[-2j(\alpha K_1 + K_2)]}{2\omega_d} = \frac{\alpha K_1 + K_2}{\omega_d}$

It follows that $K_2 = -\alpha K_1 + \omega_d B_2$, but $K_2 = \frac{dv(0^+)}{dt}$ and $K_1 = B_1$

Thus we have $\frac{dv}{dt}(0^+) = -\alpha B_1 + \omega_d B_2$, which is identical to Eq. (9.28).

Sinusoidal Steady-State Analysis

Drill Exercises

- DE 10.1** [a] $\omega = 2\pi f = 2513.27 \text{ rad/s}, \quad f = 400 \text{ Hz}$
 [b] $T = 1/f = 2.5 \text{ ms}$
 [c] $V_m = 40 \text{ V}$
 [d] $v(0) = 40(0.8) = 32 \text{ V}$
 [e] $\phi = 36.87^\circ$
 [f] $2513.27t = 53.13/57.3 = 0.9273 \text{ rad}, \quad t = 368.96 \mu\text{s}$
 [g] $(dv/dt) = (-40)2513.27 \sin(2513.27t + 36.87^\circ)$
 $(dv/dt) = 0$ when $2513.27t + 36.87^\circ = 180^\circ$ or $2513.27t = 2.498 \text{ rad}$
 Therefore $t = 993.96 \mu\text{s}$

DE 10.2
$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

Therefore $V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$

- DE 10.3** [a] The numerical values of the terms in Eq. 10.8 are
 $V_m = 100, \quad R/L = 533.33, \quad \omega L = 30$

$$\sqrt{R^2 + \omega^2 L^2} = 50$$

$$\phi = 60^\circ, \quad \theta = \tan^{-1} 30/40, \quad \theta = 36.87^\circ$$

$$i = [-1.84e^{-533.33t} + 2 \cos(400t + 23.13^\circ)] \text{ A}, \quad t \geq 0^+$$

[b] Transient component = $-1.84e^{-533.33t}$

Steady-state component = $2 \cos(400t + 23.13^\circ)$

[c] By direct substitution into the expression in [a], $i(1.875 \text{ ms}) = 133.61 \text{ mA}$

[d] 2 A, 400 rad/s, 23.13°

[e] The current lags the voltage by 36.87°.

DE 10.4 [a] $V = 170/\underline{-40^\circ}$

[b] $I = 10/\underline{-70^\circ}$

[c] $I = 5/\underline{36.87^\circ} + 10/\underline{-53.13^\circ} = 4 + j3 + 6 - j8 = 10 - j5 = 11.18/\underline{-26.6^\circ}$

[d] $V = 300/\underline{45^\circ} - 100/\underline{-60^\circ} = 212.13 + j212.13 - (50 - j86.60)$
 $= 162.13 + j298.73 = 339.90/\underline{61.51^\circ} \text{ mV}$

DE 10.5 [a] $v = 86.3 \cos(\omega t + 26^\circ) \text{ V}$

[b] $I = 10/\underline{30^\circ} + 25/\underline{60^\circ} = 8.66 + j5.00 + 12.50 + j21.65$
 $= 21.16 + j26.65 = 34.03/\underline{51.55^\circ}$

Therefore $i = 34.03 \cos(\omega t + 51.55^\circ) \text{ mA}$

[c] $V = 60 + j30 + 100/\underline{-28^\circ} = 60 + j30 + 88.29 - j46.95$
 $= 148.29 - j16.95 = 149.26/\underline{-6.52^\circ}$
 $v = 149.26 \cos(\omega t - 6.52^\circ) \text{ V}$

DE 10.6 [a] $\omega L = (4 \times 10^4)(75 \times 10^{-3}) = 3000 \Omega$

[b] $Z_L = j3000 \Omega$

[c] $V_L = IZ_L = (4/\underline{-38^\circ})(3000/\underline{90^\circ}) \times 10^{-3} = 12/\underline{52^\circ} \text{ V}$

[d] $v_L = 12 \cos(40,000t + 52^\circ) \text{ V}$

DE 10.7 [a] $X_C = \frac{-1}{\omega C} = -\frac{10^6}{10^5(0.2)} = -50 \Omega$

[b] $Z_C = jX_C = -j50 \Omega$

[c] $I = \frac{40/\underline{-50^\circ}}{50/\underline{-90^\circ}} = 0.8/\underline{40^\circ} \text{ A}$

[d] $i = 0.8 \cos(100,000t + 40^\circ) \text{ A}$


DE 10.8 $I_1 = 100/\underline{25^\circ} = 90.63 + j42.26$

$I_2 = 100/\underline{145^\circ} = -81.92 + j57.36$

$I_3 = 100/\underline{-95^\circ} = -8.71 - j99.62$

$I_4 = -(I_1 + I_2 + I_3) = (0 + j0) \text{ A}, \quad \text{therefore } i_4 = 0 \text{ A}$

DE 10.9 [a]

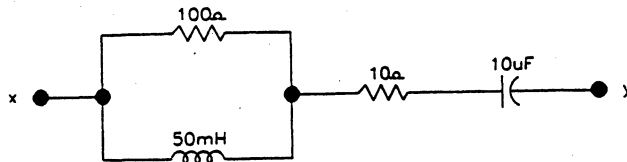

$\omega = 1000 \text{ rad/s}$

$\omega L = 50 \Omega, \quad \frac{-1}{\omega C} = -100 \Omega$

$Z_{xy} = \frac{100(j50)}{(100 + j50)} + 10 - j100 = 20 + j40 + 10 - j100 = (30 - j60) \Omega$

[b] $\omega L = 200 \Omega, \quad \frac{-1}{\omega C} = -25 \Omega$

$Z_{xy} = 10 - j25 + \left[\frac{(100)(j200)}{100 + j200} \right] = 10 - j25 + 80 + j40 = (90 + j15) \Omega$

[c] $Z_{xy} = \left[\frac{100(j\omega L)}{100 + j\omega L} \right] + \left(10 - \frac{j10^5}{\omega} \right) = \frac{100\omega^2 L^2}{10^4 + \omega^2 L^2} + \frac{j10^4 \omega L}{10^4 + \omega^2 L^2} + 10 - \frac{j10^5}{\omega}$

The impedance will be purely resistive when the j terms cancel, i.e.,

$$\frac{10^4 \omega L}{10^4 + \omega^2 L^2} = \frac{10^5}{\omega}$$

Solving for ω yields $\omega = 2000 \text{ rad/s}$.

[d] $Z_{xy} = \frac{100\omega^2 L^2}{10^4 + \omega^2 L^2} + 10 = 50 + 10 = 60 \Omega$

DE 10.10 $V = 300/\underline{0^\circ}, \quad I_s = \frac{300/\underline{0^\circ}}{60} = 5/\underline{0^\circ} \text{ A}$

$I_L = \frac{5(100)}{100 + j100} = 2.5 - j2.5 = 3.54/\underline{-45^\circ} \text{ A}$

$i_L = 3.54 \cos(2000t - 45^\circ) \text{ A}, \quad I_m = 3.54 \text{ A}$

DE 10.11 [a] $Y = \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4}$

$= 0.12 - j0.16 + 0.04 + j0.03 + j0.25 = 0.16 + j0.12$

$= 0.2/\underline{36.87^\circ} \text{ S} = 200/\underline{36.87^\circ} \text{ mS}$

[b] $G = 0.16 \text{ S} = 160 \text{ mS}$


$$[c] \quad B = 0.12 \text{ V} = 120 \text{ mV}$$

$$[d] \quad I = 8 \angle 0^\circ \text{ A}, \quad V = \frac{I}{Y} = \frac{8}{0.2 \angle 36.87^\circ} = 40 \angle -36.87^\circ \text{ V}$$

$$I_C = \frac{V}{Z_C} = \frac{40 \angle -36.87^\circ}{4 \angle -90^\circ} = 10 \angle 53.13^\circ \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

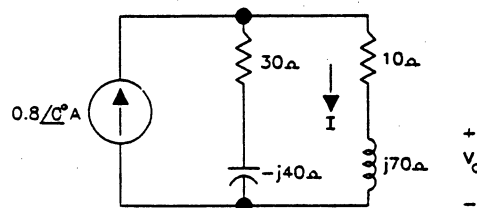
DE 10.12 Construct the phasor domain equivalent circuit:



$$I = \frac{0.8(30 - j40)}{40 + j40 + j70} = -j0.8 \text{ A}$$

$$V_o = j70I = 56 \angle 0^\circ, \quad v_o = 56 \cos 4000t \text{ V}$$

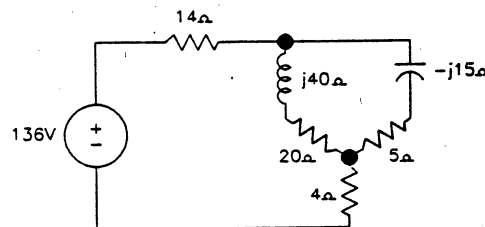DE 10.13 After replacing the delta made up of the 50-Ω, 40-Ω, and 10-Ω resistors with its equivalent wye, the circuit becomes



The circuit is further simplified by combining the parallel branches,
 $(20 + j40) \parallel (5 - j15) = (12 - j16) \Omega$

$$\text{Therefore } I = \frac{136 \angle 0^\circ}{14 + 12 - j16 + 4} = 4 \angle 28.07^\circ \text{ A}$$


DE 10.14 Use the lower node as the reference node. Let V_1 = node voltage across the 40-Ω resistor and V_{Th} = node voltage across the capacitor.

Writing the node voltage equations gives us

$$\frac{V_1}{40} - 5 + \frac{V_1 - 10I_x}{j50} = 0 \quad \text{and} \quad \frac{V_{Th}}{-j5} + \frac{V_{Th} - 10I_x}{5} = 0$$

We also have $I_x = \frac{V_1 - 10I_x}{j50}$

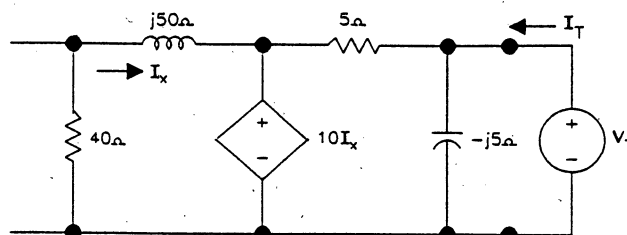Solving these equations for V_{Th} gives $V_{Th} = 20\angle -90^\circ V$. To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus




It follows from the circuit that $10I_x = -(40 + j50)I_x$

Therefore $I_x = 0$ and $I_T = \frac{V_{Th}}{-j5} + \frac{V_T}{5}$

$Z_{Th} = \frac{V_{Th}}{I_T}$, therefore $Z_{Th} = (2.5 - j2.5)\Omega$

DE 10.15 $V_{ab} = V_{Th} = j2I_\beta + 4I_\beta = 2(2 + j1)I_\beta$

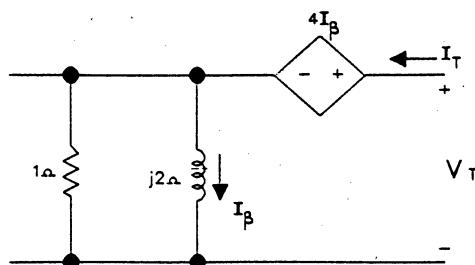$I_\beta = \frac{5(1)}{1 + j2} = (1 - j2)A$, therefore $V_{Th} = 8 - j6 = 10\angle -36.87^\circ V$



$V_T = 4I_\beta + j2I_\beta = 2(2 + j1)I_\beta$, $I_\beta = \frac{1}{1 + j2}I_T = \frac{1}{5}(1 - j2)I_T$


$Z_{Th} = \frac{V_T}{I_T} = \frac{2}{5}(4 - j3) = 1.6 - j1.2\Omega$

DE 10.16 The phasor domain circuit is as shown in the following diagram. The node voltage equation is

$$-10 + \frac{V}{5} + \frac{9V}{-j20} + \frac{V}{j5} + \frac{V - 100\angle -90^\circ}{20} = 0$$

Therefore $V = 10 - j30 = 31.62\angle -71.57^\circ$

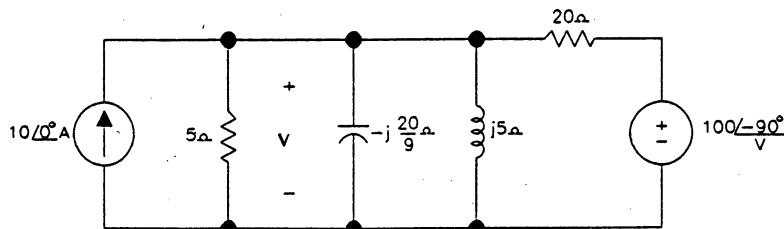Therefore $v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$



DE 10.17 Let I_a , I_b , and I_c be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives $33.8 = (1 + j2)I_a + (3 - j5)(I_a - I_b)$ and $0 = (3 - j5)(I_b - I_a) + 2(I_b - I_c)$. But $V_x = -j5(I_a - I_b)$, therefore $I_c = -0.75[-j5(I_a - I_b)]$. Solving for $I = I_a = 29 + j2 = 29.07\angle 3.95^\circ \text{ A}$.

DE 10.18 [a] $I = \frac{240}{24} + \frac{240}{j32} = (10 - j7.5) \text{ A}$

$$V_s = 240\angle 0^\circ + (0.1 + j0.8)(10 - j7.5) = 247 + j7.25 = 247.11\angle 1.68^\circ \text{ V}$$

[b] Use the capacitor to eliminate the j component of I , therefore

$$I_c = j7.5 \text{ A}, \quad Z_c = \frac{240}{j7.5} = -j32 \Omega$$

$$V_s = 240 + (0.1 + j0.8)10 = 241 + j8 = 241.13\angle 1.90^\circ \text{ V}$$

[c] Let I_c denote the magnitude of the current in the capacitor branch. Then

$$I = (10 - j7.5 + jI_c) = 10 + j(I_c - 7.5) \text{ A}$$

$$\begin{aligned} V_s &= 240\angle \alpha = 240 + (0.1 + j0.8)[10 + j(I_c - 7.5)] \\ &= (247 - 0.8I_c) + j(7.25 + 0.1I_c) \end{aligned}$$

It follows that $240 \cos \alpha = (247 - 0.8I_c)$ and $240 \sin \alpha = (7.25 + 0.1I_c)$

Now square each term and then add to generate the quadratic equation $I_c^2 - 605.77I_c + 5325.48 = 0$, $I_c = 302.88 \pm 293.96$, therefore $I_c = 8.92 \text{ A}$ (smallest value) and $Z_c = 240/j8.92$ or $-j26.90 \Omega$.

Problems

P10.1 [a] 100 V; [b] $f = 400\pi/2\pi = 200$ Hz; [c] $\omega = 400\pi = 1256.64$ rad/s

[d] $\theta = \pi/3$ or 1.05 radians; [e] $\theta = 60^\circ$; [f] $T = 1/f = 5$ ms

[g] $400\pi t + \frac{\pi}{3} = 2\pi$

$$\therefore 400\pi t = \frac{6\pi}{3} - \frac{\pi}{3} = \frac{5\pi}{3}; \quad t = \frac{5}{1200} = \frac{5}{1.2} \text{ ms} = \frac{25}{6} \text{ ms}; \quad t = 4\frac{1}{6} \text{ ms}$$

[h] $v(t) = 100 \cos \left[400\pi \left(t + \frac{5}{12} \times 10^{-3} \right) + \frac{\pi}{3} \right] = 100 \cos \left(400\pi t + \frac{\pi}{6} + \frac{\pi}{3} \right)$
 $= 100 \cos \left(400\pi t + \frac{\pi}{2} \right)$ or

$$v(t) = -100 \sin(400\pi t) \text{ V}$$

[i] $400\pi(t - t_o) + \frac{\pi}{3} = 400\pi t$

$$\therefore -400\pi t_o + \frac{\pi}{3} = 0; \quad 400\pi t_o = \frac{\pi}{3}$$


$$t_o = \frac{\pi}{1200\pi} = \frac{1}{1200} = \frac{1}{1.2} \text{ ms}; \quad t_o = \frac{10}{12} \text{ ms} = \frac{5}{6} \text{ ms}$$

[j] $400\pi(t + t_o) + \frac{\pi}{3} = 400\pi t + \frac{3\pi}{2}$

$$\therefore 400\pi t_o = -\frac{\pi}{3} + \frac{3\pi}{2} = \frac{-2\pi}{6} + \frac{9\pi}{6} = \frac{7\pi}{6}$$

$$t_o = \frac{7\pi}{2400\pi} = \frac{7}{2400} = \frac{7}{2.4} \text{ ms}; \quad t_o = \frac{70}{24} \text{ ms} = \frac{35}{12} \text{ ms}$$


P10.2

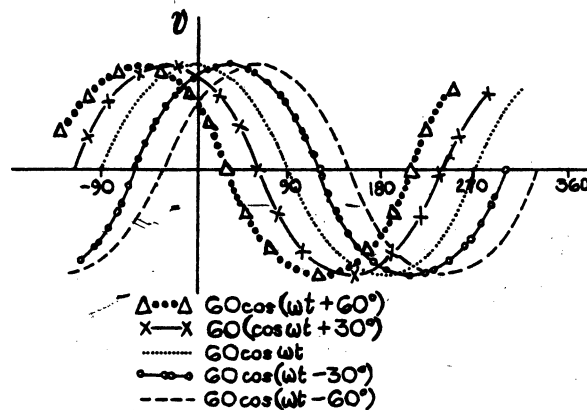

[a] Left as ϕ becomes more positive

[b] Right

P10.3 [a]

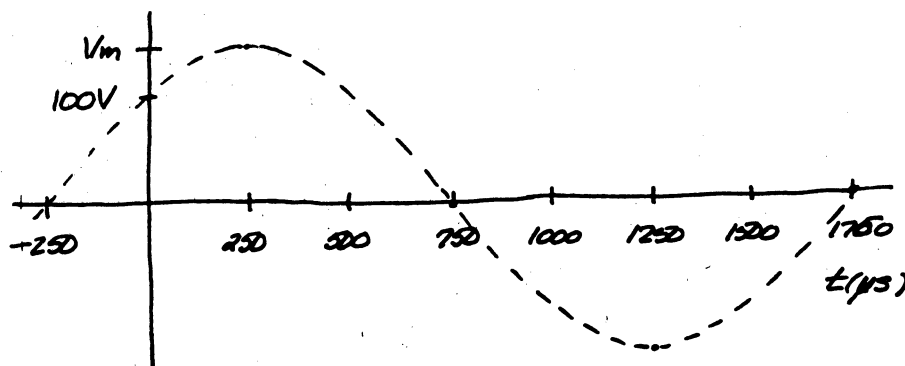

$$T = 1750 + 250 = 2000 \mu\text{s}; \quad f = \frac{1}{T} = \frac{10^6}{2000} = 500 \text{ Hz}$$

$$[b] \quad \omega = 2\pi f = 1000\pi \text{ rad/s}; \quad 250 \mu\text{s} \Rightarrow \pi/4 \text{ radians}$$

$$\therefore v = V_m \sin(1000\pi t + \pi/4)$$

$$\therefore 100 = V_m \sin \pi/4, \quad V_m = 100\sqrt{2}$$

$$\therefore v = 100\sqrt{2} \sin(1000\pi t + \pi/4) = 100\sqrt{2} \cos(1000\pi t - \pi/4)$$

$$\text{P10.4 [a]} \quad i = 10 \cos(\omega t + \theta); \quad \frac{di}{dt} = -10\omega \sin(\omega t + \theta)$$

$$i(15 \mu\text{s}) = 0 = 10 \cos(15 \times 10^{-6} \omega + \theta)$$

$$\therefore 15 \times 10^{-6} \omega + \theta = \pm \pi/2$$

$$-10\omega \sin(\pm \pi/2) = 2 \times 10^5 \pi$$

Since $\omega > 0$, minus $\pi/2$ must be used.

$$\therefore 10\omega = 2 \times 10^5 \pi; \quad \omega = 2 \times 10^4 \pi = 20,000\pi \text{ rad/s}$$

$$[b] \quad 15 \times 10^{-6} (20,000\pi) + \theta = -\frac{\pi}{2}$$

$$\theta = -\frac{\pi}{2} - 0.3\pi = -0.8\pi = \frac{-8\pi}{10} = -\frac{4\pi}{5} \text{ radians or } -144^\circ$$

$$i = 10 \cos(2 \times 10^4 \pi t - 144^\circ) \text{ A}$$

$$\text{P10.5 [a]} \quad \text{From Eq. 10.8 we have}$$

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$\text{But } \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to $V_m \cos(\omega t + \phi)$

$$\text{At } t = 0, \text{ Eq. 10.8 reduces to } i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 - \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

$$[b] \quad i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$\text{Therefore } L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta) \quad \text{and}$$

$$R i_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$L \frac{di_{ss}}{dt} + R i_{ss} = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right] = V_m \cos(\omega t + \phi)$$

$$\begin{aligned} \text{P10.6 [a]} \quad Y &= 100/30^\circ + 50/-45^\circ = 86.60 + j50 + 35.36 - j35.36 \\ &= 121.96 + j14.64 = 122.83/6.85^\circ \\ \therefore y &= 122.83 \cos(500t + 6.85^\circ) \end{aligned}$$

$$\begin{aligned} [b] \quad Y &= 100/-50^\circ - 50/200^\circ = 64.28 - j76.60 - (-46.98 - j17.10) \\ &= 111.26 - j59.50 = 126.18/-28.14^\circ \\ \therefore y &= 126.18 \cos(377t - 28.14^\circ) \end{aligned}$$

$$\begin{aligned} [c] \quad Y &= 40/60^\circ + 80/45^\circ - 100/270^\circ \\ &= 20 + j34.64 + 56.57 + j56.57 - (0 - j100) \\ &= 76.57 + j191.21 = 205.97/68.18^\circ \\ \therefore y &= 205.97 \cos(\omega t + 68.18^\circ) \end{aligned}$$

$$\begin{aligned} [d] \quad Y &= 100/0^\circ + 100/120^\circ + 100/-120^\circ \\ &= 100 + j0 + (-50 + j86.60) + (-50 - j86.60) \\ &= 100 - 100 + j86.60 - j86.60 = 0 \\ \therefore y &= 0 \end{aligned}$$

$$\begin{aligned} \text{P10.7} \quad u &= \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt \\ &= V_m^2 \int_{t_0}^{t_0+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt \\ &= \frac{V_m^2}{2} \left\{ \int_{t_0}^{t_0+T} dt + \int_{t_0}^{t_0+T} \cos(2\omega t + 2\phi) dt \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_0}^{t_0+T} \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_0 + 4\pi + 2\phi) - \sin(2\omega t_0 + 2\phi)] \right\} \\ &= V_m^2 \left(\frac{T}{2} \right) + \frac{1}{2\omega}(0) = V_m^2 \left(\frac{T}{2} \right) \end{aligned}$$

P10.8 $V_m = \sqrt{2}V_{\text{rms}} = \sqrt{2}(120) = 169.71 \text{ V}$

P10.9 [a] 1000 Hz; [b] 0°

[c] $I = \frac{V}{j\omega L} = \frac{200/0^\circ}{\omega L/90^\circ} = \frac{200}{\omega L} \angle -90^\circ; \quad \therefore \theta_i = -90^\circ$

[d] $\frac{200}{\omega L} = 25, \quad \omega L = 8 \Omega$

[e] $\omega = 2\pi f = 2000\pi \text{ rad/s}; \quad \therefore L = \frac{8}{2000\pi} = \frac{4}{\pi} \text{ mH} \cong 1.27 \text{ mH}$

[f] $Z_L = j\omega L = j8 \Omega$

P10.10 [a] $\omega = 2\pi(50 \times 10^3) = 100\pi \text{ krad/s}$

[b] $I = j\omega C V = j\omega C \times 10 \times 10^{-3} \angle 0^\circ = 1000\pi C \angle 90^\circ; \quad \therefore \theta_i = 90^\circ$

[c] $1000\pi C = 628.32 \times 10^{-6}$

$\therefore C = \frac{628.32 \times 10^{-6}}{1000\pi} = 0.2 \times 10^{-6}$

$\therefore -\frac{1}{\omega C} = \frac{10^6}{(100\pi \times 10^3)(0.2)} = \frac{-10}{0.2\pi} = -\frac{50}{\pi} = -15.92 \Omega$


[d] $C = 0.2 \mu\text{F}$

[e] $Z_C = \frac{1}{j\omega C} = -j\frac{1}{\omega C} = -j15.92 \Omega$

P10.11 [a] $j\omega L = j(5000)(8 \times 10^{-3}) = j40 \Omega$

$\frac{1}{j\omega C} = \frac{10^6}{j(5000)(2.5)} = -j\frac{1000}{12.5} = -j80 \Omega$


$V = 240 \angle -40^\circ \text{ V}$

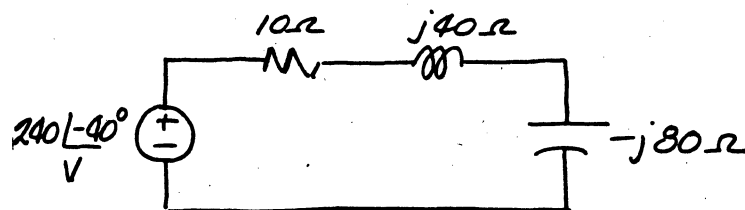

[b] $I = \frac{240 \angle -40^\circ}{10 + j40 - j80} = \frac{24 \angle -40^\circ}{1 - j4}; \quad I = 5.82 \angle 35.96^\circ \text{ A}$

[c] $i = 5.82 \cos(5000t + 35.96^\circ) \text{ A}$

P10.12 [a]

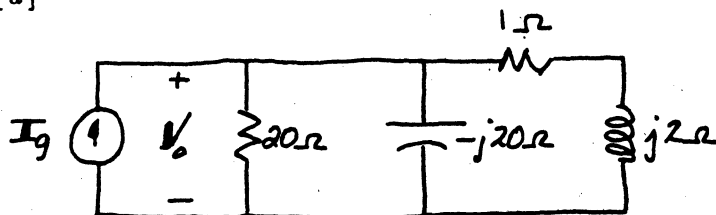

$$\frac{1}{j\omega C} = \frac{10^6}{j50,000} = -j20 \Omega$$

$$j\omega L = j(50,000)(40 \times 10^{-6}) = j2 \Omega$$

$$\begin{aligned} \text{[b]} \quad Y &= \frac{1}{20} + \frac{1}{-j20} + \frac{1}{1+j2} = 0.05 + j0.05 + \frac{1-j2}{5} \\ &= 0.25 + j0.05 - j0.40 = 0.25 - j0.35 = 0.43 \angle -54.46^\circ \text{ S} \end{aligned}$$

$$Z = \frac{1}{Y} = 2.32 \angle 54.46^\circ \Omega$$

$$V_o = ZI_g; \quad I_g = 20 \angle -20^\circ \text{ A}; \quad V_o = 46.50 \angle 34.46^\circ \text{ V}$$


$$\text{[c]} \quad v_o(t) = 46.50 \cos(50,000t + 34.46^\circ) \text{ V}$$

P10.13 Construct the phasor-domain circuit

$$j\omega L = j50(240 \times 10^{-3}) = j12 \Omega$$

$$\frac{1}{j\omega C} = \frac{10^3}{j50(2.5)} = -j8 \Omega$$
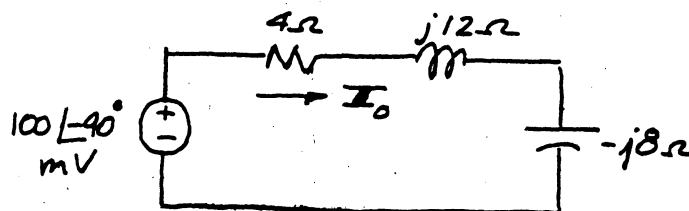
$$V_s = 100 \angle -90^\circ \text{ mV}$$




$$I_o = \frac{100 \angle -90^\circ \times 10^{-3}}{4 + j12 - j8} = \frac{25 \angle -90^\circ}{1 + j1} \text{ mA} = 17.68 \angle -135^\circ \text{ mA}$$

$$i_o(t) = 17.68 \cos(50t - 135^\circ) \text{ mA}$$

P10.14 Construct the phasor-domain circuit
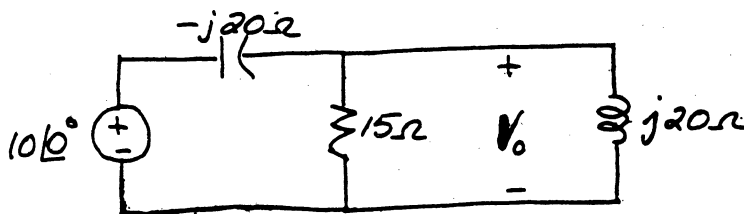
$$\frac{1}{j\omega C} = \frac{10^6}{(j100)(500)} = -j20 \Omega; \quad j\omega L = j20 \Omega; \quad V_g = 10 \angle 0^\circ \text{ V}$$



$$\text{Let } Z_1 = -j20\Omega, \quad Z_2 = \frac{(15)(j20)}{15 + j20} = \frac{j60}{3 + j4} = 12\angle 36.87^\circ$$

$$V_o = \frac{10\angle 0^\circ (Z_2)}{(Z_1 + Z_2)} = \frac{120\angle 36.87^\circ}{9.6 - j12.80} = 7.5\angle 90^\circ \text{ V}$$

$$v_o = 7.5 \cos(100t + 90^\circ) \text{ V}$$

P10.15 Let $Z_1 = 4 - j8\Omega$, $Z_2 = 2 + j10\Omega$

$$\text{Then } Z_1 // Z_2 = \frac{(4 - j8)(2 + j10)}{6 + j2} = \frac{88 + j24}{(6 + j2)} = \frac{(88 + j24)(6 - j2)}{40} = 14.4 - j0.8\Omega$$

$$Z_3 = 20\Omega, \quad Z_4 = -j10\Omega$$

$$Z_3 // Z_4 = \frac{-j200}{20 - j10} = \frac{-j20}{2 - j1} = \frac{-j20(2 + j1)}{5} = 4 - j8\Omega$$

$$Z_{ab} = 21.6 + j38.8 + 14.4 - j0.8 + 4 - j8 = 40 + j30\Omega = 50\angle 36.87^\circ\Omega$$

P10.16 $Y_1 = \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = \frac{6 + j2}{40} + \frac{4 - j12}{160} + \frac{32}{160} - j\frac{16}{160}$

$$= \frac{24 + j8 + 4 - j12 + 32 - j16}{160} = \frac{60 - j20}{160} = \frac{3 - j1}{8}$$


$$Z_1 = \frac{1}{Y_1} = \frac{8}{3 - j1} = 2.4 + j0.8$$

$$Z_{ab} = 13.6 - j12.8 + 2.4 + j0.8 = 16 - j12 = 20\angle -36.87^\circ$$

$$Y_{ab} = \frac{1}{Z_{ab}} = 50\angle 36.87^\circ \text{ mS} = 40 + j30 \text{ mS}$$

P10.17 $\frac{1}{j\omega C} = \frac{10^6}{j2 \times 10^4(2.5)} = \frac{100}{j5} = -j20\Omega$
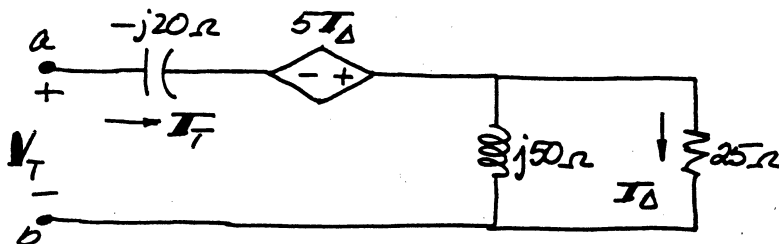
$$j\omega L = j2 \times 10^4(2.5) \times 10^{-3} = j50\Omega$$



$$\begin{aligned}
 V_T &= -j20I_T - 5 \frac{(j50)I_T}{25 + j50} + I_T \frac{(25)(j50)}{(25 + j50)} \\
 \frac{V_T}{I_T} &= -j20 - \frac{j250}{25 + j50} + j \frac{1250}{25 + j50} = -j20 + j \frac{1000}{25 + j50} = -j20 + j \frac{40}{1 + j2} \\
 Z_{ab} &= -j20 + j8 + 16 = 16 - j12 \Omega
 \end{aligned}$$

P10.18 [a]
$$\begin{aligned}
 Z_{ab} &= j\omega 4 + \frac{5000[(4 \times 10^6)/j\omega]}{5000 + [(4 \times 10^6)/j\omega]} = j\omega 4 + \frac{2 \times 10^{10}}{5000(j\omega) + 4 \times 10^6} \\
 &= j\omega 4 + \frac{2 \times 10^7}{j\omega 5 + 4000} = j\omega 4 + \frac{(4000 - j\omega 5)(2 \times 10^7)}{16 \times 10^6 + 25\omega^2} \\
 \therefore 4\omega &= \frac{10^8\omega}{25\omega^2 + 16 \times 10^6} \\
 \therefore 25\omega^2 + 16 \times 10^6 &= 25 \times 10^6 \\
 25\omega^2 &= 9 \times 10^6; \quad 5\omega = 3000; \quad \omega = 600 \text{ rad/s}
 \end{aligned}$$

[b]
$$\begin{aligned}
 Z_{ab} &= j2400 + \frac{5000[(4 \times 10^6)/j600]}{5000 + [(4 \times 10^6)/j600]} = j2400 + \frac{2 \times 10^{10}}{4 \times 10^6 + j3 \times 10^6} \\
 &= j2400 + \frac{20,000}{4 + j3} = j2400 + \frac{20,000(4 - j3)}{25} \\
 &= j2400 + 3200 - j2400 \\
 Z_{ab} &= 3200 \Omega
 \end{aligned}$$

P10.19 [a]
$$\begin{aligned}
 \frac{1}{j\omega C} &= \frac{10^6}{j(500)(2.5)} = -j800 \Omega \\
 \therefore Z &= 400 - j800 + \frac{2000(j\omega L)}{2000 + j\omega L} = 400 - j800 + \frac{j2000L}{4 + jL} \\
 &= 400 - j800 + \frac{j2000L(4 - jL)}{16 + L^2} = 400 - j800 + \frac{2000L^2}{16 + L^2} + j \frac{8000L}{16 + L^2} \\
 \therefore \frac{8000L}{16 + L^2} &= 800; \quad 10L = 16 + L^2 \\
 \therefore L^2 - 10L + 16 &= 0; \quad L = 5 \pm \sqrt{25 - 16} = 5 \pm 3 \\
 L_1 &= 2 \text{ H}; \quad L_2 = 8 \text{ H}
 \end{aligned}$$

[b] When $L_1 = 2 \text{ H}$

$$\begin{aligned}
 Z &= 400 + \frac{2000(4)}{(16 + 4)} = 400 + 400 = 800 \Omega \\
 I_g &= \frac{200 \angle 0^\circ}{800 \angle 0^\circ} = 0.25 \angle 0^\circ \text{ A} \\
 i_g &= 0.25 \cos 500t \text{ A}
 \end{aligned}$$

When $L_2 = 8 \text{ H}$

$$Z = 400 + \frac{2000(64)}{(16 + 64)} = 2000 \Omega$$

$$I_g = \frac{200/0^\circ}{2000/0^\circ} = 0.1/0^\circ \text{ A}$$

$$i_g = 0.10 \cos 500t \text{ A}$$

$$\begin{aligned} \text{P10.20 [a]} \quad Z &= j1000(5) + \frac{12,500(1/j1000C)}{12,500 + (1/j1000C)} \\ &= j5000 + \frac{12,500}{1 + j12.5 \times 10^6 C} \\ &= j5000 + \frac{12,500(1 - j12.5 \times 10^6 C)}{1 + 156.25 \times 10^{12} C^2} \\ &= \frac{12,500}{1 + 156.25 \times 10^{12} C^2} + j5000 - \frac{j156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2} \end{aligned}$$

i_g will be in phase with v_g when the j terms cancel, therefore

$$5000 = \frac{156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2}$$

$$1 + 156.25 \times 10^{12} C^2 = 31,250 \times 10^3 C$$

$$C^2 - 2 \times 10^{-7} C + 6400 \times 10^{-18} = 0$$

$$C = 10^{-7} \pm \sqrt{10^{-14} - 0.64 \times 10^{-14}} = 10^{-7} \pm \sqrt{0.36 \times 10^{-14}}$$

$$= 10^{-7} \pm 0.6 \times 10^{-7} = (0.10 \pm 0.06) \times 10^{-6}$$

$$C = 0.16 \mu\text{F} \text{ or } C = 0.04 \mu\text{F}$$

[b] When $C = 0.16 \mu\text{F}$

$$Z = \frac{12,500}{1 + 15625 \times 10^{10} (0.16 \times 10^{-6})^2} + j0 = \frac{12,500}{1 + 4} = 2500 + j0 \Omega$$

$$I_g = \frac{250/0^\circ}{2500/0^\circ} = 0.10/0^\circ \text{ A} = 100/0^\circ \text{ mA}$$

$$i_g = 100 \cos 1000t \text{ mA}$$

When $C = 0.04 \mu\text{F}$

$$Z = \frac{12,500}{1 + 15625 \times 10^{10} (0.04 \times 10^{-6})^2} + j0 = \frac{12,500}{1 + 0.25} = 10,000 + j0 \Omega$$

$$I_g = \frac{250/0^\circ}{10,000/0^\circ} = 25 \times 10^{-3}/0^\circ \text{ A} = 25/0^\circ \text{ mA}$$

$$i_g = 25 \cos 1000t \text{ mA}$$

$$\text{P10.21 [a]} \quad \text{Let } Y_1 = \frac{11}{2500} \times 10^{-3} = 4.4 \times 10^{-6} \text{ S}$$

$$\begin{aligned} \text{Let } Y_2 &= \frac{1}{14,000 + j\omega 5} + j\omega 2 \times 10^{-9} = \frac{14,000 - j5\omega}{196 \times 10^6 + 25\omega^2} + j2\omega \times 10^{-9} \\ &= \frac{14,000}{196 \times 10^6 + 25\omega^2} + j2\omega \times 10^{-9} - \frac{j5\omega}{196 \times 10^6 + 25\omega^2} \end{aligned}$$

v_o will be in phase with i_g when Y_2 is pure conductance. Therefore we find ω such that

$$2\omega \times 10^{-9} = \frac{5\omega}{196 \times 10^6 + 25\omega^2}$$

$$\therefore 196 \times 10^6 + 25\omega^2 = 2.5 \times 10^9 = 2500 \times 10^6$$

$$\therefore 25\omega^2 = 2304 \times 10^6$$

$$\omega^2 = 92.16 \times 10^6; \quad \omega = 9.6 \times 10^3 = 9600 \text{ rad/s}$$

$$[b] \quad Y_2(9600) = \frac{14,000}{196 \times 10^6 + 25(92.16 \times 10^6)} = \frac{14,000}{2500} \times 10^{-6} = 5.6 \times 10^{-6} \text{ S}$$

$$\therefore Y = Y_1 + Y_2 = (4.4 + 5.6) \times 10^{-6} = 10^{-5} \text{ S}$$

$$Z = \frac{1}{Y} = 10^5 \Omega$$

$$V_o = I_g Z = (0.25 \times 10^{-3} \angle 0^\circ) 10^5 \angle 0^\circ = 25 \angle 0^\circ \text{ V}$$

$$v_o = 25 \cos 9600t \text{ V}$$

P10.22 [a] Let $Y = j\omega 10 \times 10^{-9} + \frac{1}{8000 + j\omega(1)} = j\omega 10^{-8} + \frac{8000 - j\omega}{64 \times 10^6 + \omega^2}$

$$= \frac{8000}{64 \times 10^6 + \omega^2} + j10^{-8}\omega - \frac{j\omega}{64 \times 10^6 + \omega^2}$$

i_o will be in phase with v_g when Y is pure conductance, therefore

$$\omega 10^{-8} = \frac{\omega}{\omega^2 + 64 \times 10^6}$$

$$\omega^2 + 64 \times 10^6 = 10^8 = 100 \times 10^6$$

$$\omega^2 = 36 \times 10^6; \quad \omega = 6 \times 10^3 = 6000 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \frac{3000}{\pi} = 954.93 \text{ Hz}$$

$$[b] \quad Z(6000) = \frac{1}{Y(6000)}$$

$$Y(6000) = \frac{8000}{64 \times 10^6 + 36 \times 10^6} = \frac{8000}{10^8}$$

$$Z(6000) = \frac{10^8}{8000} = 12,500 \Omega$$

$$\therefore Z_g = 3500 + 12,500 = 16,000 \Omega$$

$$I_o = \frac{V_g}{Z_g} = \frac{80 \angle 0^\circ}{16,000 \angle 0^\circ} = 5 \times 10^{-3} = 5 \text{ mA}$$

$$i_o = 5 \cos 6000t \text{ mA}$$


P10.23 $V_g = 500 \angle 30^\circ \text{ V}; \quad I_o = 0.10 \angle 83.1301^\circ$

$$Z = \frac{V_g}{I_o} = 5000 \angle -53.13^\circ = 3000 - j4000 \Omega$$

$$\therefore j\omega 1 + \frac{10^9}{j\omega(31.25)} = -j4000$$

$$\begin{aligned}
 \therefore j\omega + \frac{32 \times 10^6}{j\omega} &= -j4000 \\
 \omega^2 - 32 \times 10^6 &= -4000\omega \\
 \omega^2 + 4000\omega - 32 \times 10^6 &= 0 \\
 \omega &= -2000 \pm \sqrt{36 \times 10^6} = -2000 \pm 6000, \quad \omega > 0 \\
 \therefore \omega &= 4000 \text{ rad/s}
 \end{aligned}$$

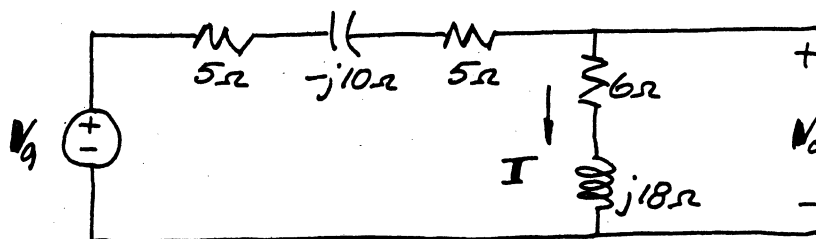P 10.24 $\frac{1}{j\omega C} = -j\frac{100}{8} = -j12.5 \Omega$
 $j\omega L = j8(2.25) = j18 \Omega$
 $Z_1 = 25 \Omega // -j12.5 \Omega = \frac{(25)(-j12.5)}{25 - j12.5} = \frac{-j25}{2 - j1} = -j5(2 + j1) = 5 - j10 \Omega$
 $I_g = 10 \angle 0^\circ \text{ A}; \quad V_g = 50 - j100 \text{ V}$



$$\begin{aligned}
 I &= \frac{50 - j100}{16 + j8} = \frac{6.25 - j12.5}{2 + j1} = \frac{1}{5}(6.25 - j12.5)(2 - j1) = (1.25 - j2.5)(2 - j1) \\
 &= 2.5 - j1.25 - j5.0 - 2.5 = -j6.25 = 6.25 \angle -90^\circ \text{ A} \\
 V_o &= (6 + j18)(6.25 \angle -90^\circ) = 118.59 \angle -18.43^\circ \text{ V} \\
 v_o &= 118.59 \cos(8t - 18.43^\circ) \text{ V}
 \end{aligned}$$

P 10.25 $Z_1 = 30 + j0.25 \times 10^{-3}(40,000) = 30 + j10 \Omega$

$$Z_2 = 20 - j\frac{10^6}{(40,000)(2.5)} = 20 - j10 \Omega$$

$$I_g = 20 \angle -73.74^\circ \text{ A}$$

Let I_C represent the current down through the capacitive branch. Then

$$I_C = \frac{Z_1}{Z_1 + Z_2} I_g = \frac{30 + j10}{50} (20 \angle -73.74^\circ) = 12.65 \angle -55.31^\circ \text{ A}$$

$$V_o = 20I_C = 252.98 \angle -55.31^\circ \text{ V}$$

$$v_o = 252.98 \cos(40,000t - 55.31^\circ) \text{ V}$$

P 10.26 [a] $V_g = 240 \angle 120^\circ \text{ V}; \quad I_g = 12 \angle 84^\circ \text{ A}; \quad Z = \frac{V_g}{I_g} = \frac{240 \angle 120^\circ}{12 \angle 84^\circ} = 20 \angle 36^\circ$

$$[b] \quad \omega = 2\pi f = 2000\pi; \quad f = 1000 \text{ Hz}; \quad T = \frac{1}{1000} = 1 \text{ ms}$$

$36^\circ \equiv 1/10$ of the period

$$\therefore \left(\frac{1}{10}\right)(10^{-3}) = 100 \times 10^{-6} = 100 \mu\text{s}$$

$\therefore$ Current is out of phase with the voltage by $100 \mu\text{s}$. Note i_g lags v_g .

$$\begin{aligned} \text{P10.27 [a]} \quad Z_1 &= R_1 - j\frac{1}{\omega C_1} \\ Z_2 &= \frac{R_2/j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \\ Z_1 &= Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and} \\ \frac{1}{\omega C_1} &= \frac{\omega R_2^2 C_2^2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2} \end{aligned}$$

$$\begin{aligned} [b] \quad R_1 &= \frac{1000}{1 + (4 \times 10^4)^2 (0.05 \times 10^{-6})^2 (1000)^2} \\ &= \frac{1000}{1 + (16 \times 10^8)(0.0025)(10^{-12} \times 10^6)} = \frac{1000}{1 + (16)(0.25)} = \frac{1000}{5} \\ R_1 &= 200 \Omega \\ C_1 &= \frac{5}{(16 \times 10^8)(10^6)(0.05 \times 10^{-6})} \\ C_1 &= 62.5 \times 10^{-9} = 62.5 \text{ nF} \end{aligned}$$

$$\begin{aligned} \text{P10.28 [a]} \quad Y_2 &= \frac{1}{R_2} + j\omega C_2 \\ Y_1 &= \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2} \\ \text{Therefore } Y_1 &= Y_2 \quad \text{when} \quad R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2} \end{aligned}$$

$$\begin{aligned} [b] \quad R_2 &= \frac{1 + (5 \times 10^4)^2 (10^6)(1600 \times 10^{-18})}{(5 \times 10^4)^2 (1000)(1600 \times 10^{-18})} \\ &= \frac{1 + (25 \times 10^8)(10^6)(16 \times 10^{-16})}{(25 \times 10^8)(10^3)(16 \times 10^{-16})} = \frac{1 + 400 \times 10^{-2}}{400 \times 10^{-5}} = \frac{5}{4} \times 10^3 \\ R_2 &= 1250 \Omega \\ C_2 &= \frac{1}{5} C_1 = 8 \text{ nF} \end{aligned}$$

$$\begin{aligned} \text{P10.29 [a]} \quad Z_1 &= R_1 + j\omega L_1 \\ Z_2 &= \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2} \\ Z_1 &= Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2} \end{aligned}$$

$$[b] \quad R_1 = \frac{(64 \times 10^6)(6.25)(10^4)}{10^8 + 64 \times 10^6(6.25)} = \frac{400 \times 10^{10}}{10^8 + 400 \times 10^6} = \frac{400 \times 10^2}{5}$$

$$R_1 = 8000 \Omega = 8 \text{ k}\Omega$$

$$L_1 = \frac{10^8(2.5)}{5 \times 10^8} = 0.5 \text{ H}$$

P10.30 [a] $Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

Therefore $Y_2 = Y_1$ when $R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1}$ and $L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$

[b] $R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} = \frac{25 \times 10^6 + 16 \times 10^6(0.25)^2}{5000}$

$$= \frac{25 \times 10^6 + 1 \times 10^6}{5000} = \frac{26}{5} \times 10^3$$

$$R_2 = 5200 \Omega$$

$$L_2 = \frac{26 \times 10^6}{(16 \times 10^6)(0.25)} = \frac{26}{4} = 6.5 \text{ H}$$

P10.31 [a] $V_1 = (20 + j60)I_a = 100 + j300 \text{ V}$

$$I_b = \frac{V_1}{12 - j3.5} = \frac{100 + j300}{12 - j3.5} = 14.40 + j20.80 = 25.30/55.30^\circ \text{ A}$$

$$I_c = I_a + I_b + 22.56/24.07^\circ = 5 + j0 + 14.40 + j20.8 + 20.6 + j9.2$$


$$= 40 + j30 \text{ A} = 50/36.87^\circ$$

$$V_g = 2I_c + V_1 = 80 + j60 + 100 + j300 = 180 + j360 = 402.49/63.43^\circ \text{ V}$$

[b] $i_b = 25.30 \cos(5000t + 55.30^\circ) \text{ A}$

$$i_c = 50 \cos(5000t + 36.87^\circ) \text{ A}$$

$$v_g = 402.49 \cos(5000t + 63.43^\circ) \text{ V}$$

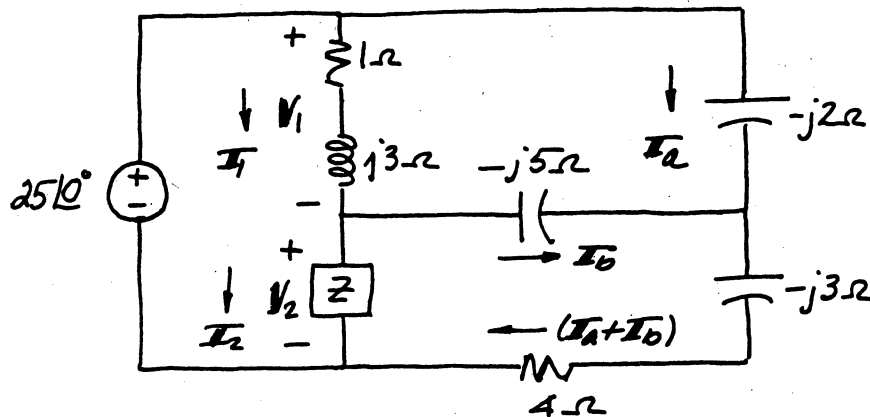P10.32

$$25\angle 0^\circ = (j5)(-j2) + (4 - j3)(\mathbf{I}_a + \mathbf{I}_b) = 10 + (4 - j3)\mathbf{I}_b + j20 + 15$$

$$\therefore \mathbf{I}_b = \frac{-j20}{4 - j3} = \frac{-j20(4 + j3)}{25} = 2.4 - j3.2 \text{ A}$$

$$\mathbf{V}_1 = -j2\mathbf{I}_a - (-j5)\mathbf{I}_b = 10 + j5(2.4 - j3.2) = 26 + j12 \text{ V}$$


$$\mathbf{I}_1 = \frac{26 + j12}{1 + j3} = \frac{(26 + j12)(1 - j3)}{10} = \frac{26 - j78 + j12 + 36}{10} = 6.2 - j6.6 \text{ A}$$

$$\mathbf{V}_2 = 25 - \mathbf{V}_1 = -1 - j12 \text{ V}$$

$$\mathbf{I}_2 = \mathbf{I}_1 - \mathbf{I}_b = 6.2 - j6.6 - 2.4 + j3.2 = 3.8 - j3.4$$

$$\mathbf{Z} = \frac{\mathbf{V}_2}{\mathbf{I}_2} = \frac{-1 - j12}{3.8 - j3.4} = \frac{12.04\angle -94.76^\circ}{5.10\angle -41.82^\circ} = 2.36\angle -52.94^\circ = (1.42 - j1.88) \Omega$$

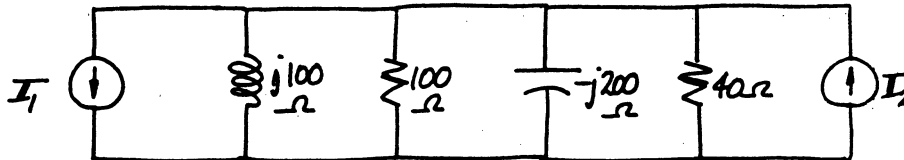P 10.33 $j\omega L = j5000(20 \times 10^{-3}) = j100 \Omega$; $\frac{1}{j\omega C} = \frac{10^6}{j5000} = -j200 \Omega$




$$\mathbf{I}_1 = \frac{400\angle 36.87^\circ}{j100} = 4\angle -53.13^\circ = 2.4 - j3.2 \text{ A}$$

$$\mathbf{I}_2 = \frac{128\angle -90^\circ}{40} = 3.2\angle -90^\circ = -j3.2 \text{ A}$$

$$\mathbf{Y} = \frac{1}{j100} + \frac{1}{100} + \frac{1}{-j200} + \frac{1}{40} = \frac{-j2 + 2 + j + 5}{200} = \frac{7 - j1}{200}$$
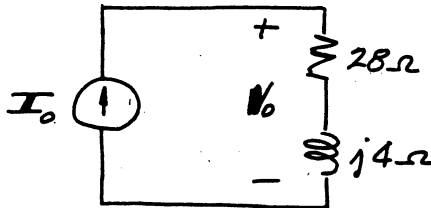
$$\mathbf{Z} = \frac{200}{7 - j1} = \frac{200}{50}(7 + j1) = 28 + j4 \Omega$$



$$\mathbf{I}_o = \mathbf{I}_2 - \mathbf{I}_1 = -j3.2 - 2.4 + j3.2 = -2.4 = 2.4\angle 180^\circ$$


$$\mathbf{V}_o = (28 + j4)\mathbf{I}_o = (28.28\angle 8.13^\circ)(2.4\angle 180^\circ) = 67.88\angle 188.13^\circ$$

$$v_o = 67.88 \cos(5000t + 188.13^\circ) \text{ V} \quad \text{or} \quad v_o = 67.88 \sin(5000t - 81.87^\circ) \text{ V}$$

P10.34 Construct a phasor-domain equivalent circuit.

$$\frac{1}{j\omega C} = \frac{1000}{j200(12.5)} = -j0.4\Omega; \quad j\omega L = j200(2 \times 10^{-3}) = j0.4\Omega; \quad \mathbf{I}_s = 3\angle 0^\circ \text{ mA}$$

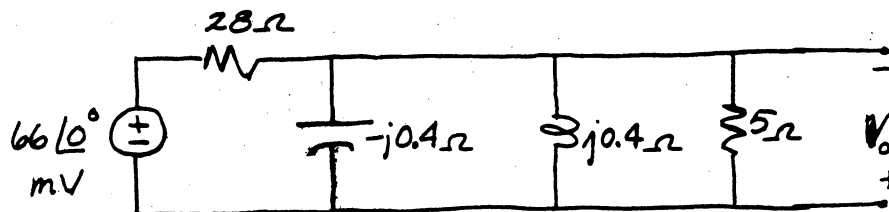
Make a source transformation where $\mathbf{V}_s = 22(3\angle 0^\circ) = 66\angle 0^\circ \text{ mV}$



Compute the admittance of the parallel branches:

$$Y_P = \frac{1}{-j0.4} + \frac{1}{j0.4} + \frac{1}{5} = 0.2\text{S}; \quad \therefore Z_P = \frac{1}{Y_P} = 5\Omega$$

Therefore the circuit simplifies to

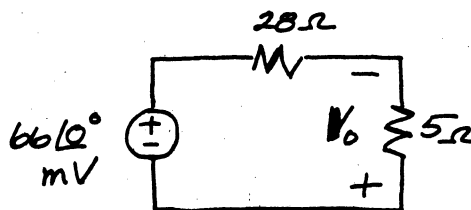


$$\therefore \mathbf{V}_o = \frac{-66}{33}(5) = -10 \text{ mV} = 10\angle 180^\circ \text{ mV}$$

$$\therefore v_o(t) = 10 \cos(200t + 180^\circ) \text{ mV}$$

P10.35 $j\omega L = j[40,000(0.5) \times 10^{-3}] = j20\Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j40,000(5)} = -j5\Omega$
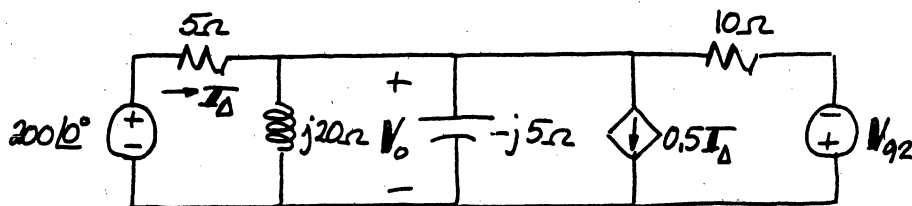
$$\mathbf{V}_{g1} = 200\angle 0^\circ \text{ V}; \quad \mathbf{V}_{g2} = 100\angle 36.87^\circ \text{ V}$$



$$\frac{V_o - 200/0^\circ}{5} + \frac{V_o}{j20} + \frac{V_o}{-j5} + 0.5 \left(\frac{200/0^\circ - V_o}{5} \right) + \frac{V_o + 100/36.87^\circ}{10} = 0$$

$$V_o \left[\frac{1}{5} - \frac{j}{20} + \frac{j}{5} - 0.1 + 0.1 \right] = 40 - 20 - 10/36.87^\circ$$

$$V_o \left[\frac{4 - j1 + 4}{20} \right] = 20 - (8 + j6)$$

$$V_o(4 + j3) = 20[12 - j6] = 120(2 - j1)$$


$$V_o = \frac{120(2 - j1)(4 - j3)}{25} = 4.8(8 - j6 - j4 - 3)$$

$$= 4.8(5 - j10) = 24(1 - j2) = 53.67 \angle -63.43^\circ \text{ V}$$

$$\therefore v_o(t) = 53.67 \cos(40,000t - 63.43^\circ) \text{ V}$$

P10.36 $j\omega L = j50,000 \times 160 \times 10^{-6} = j8 \Omega$; $\frac{1}{j\omega C} = \frac{10^6}{j50,000 \times 4} = -j5 \Omega$

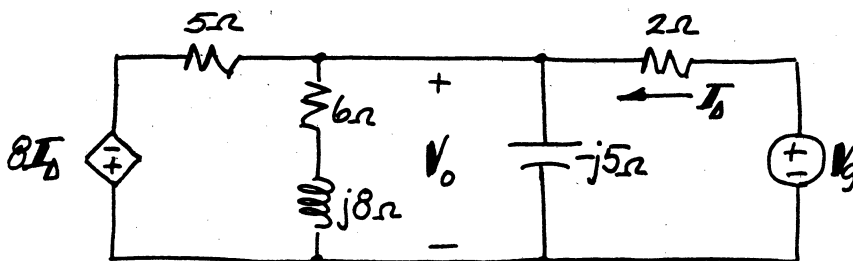$V_g = 160/0^\circ \text{ mV}$; $I_\Delta = \frac{V_g - V_o}{2} = 0.5V_g - 0.5V_o$



$$\frac{V_o + 8I_\Delta}{5} + \frac{V_o}{6 + j8} + \frac{V_o}{-j5} + \frac{V_o - V_g}{2} = 0$$

$$V_o \left[\frac{1}{5} + \frac{6 - j8}{100} + \frac{j}{5} + \frac{1}{2} \right] + 1.6(0.5V_g - 0.5V_o) = \frac{V_g}{2}$$

$$V_o[20 + 6 - j8 + j20 + 50] + 80V_g - 80V_o = 50V_g$$

$$V_o[76 + j12 - 80] = (50 - 80)V_g$$

$$V_o(-4 + j12) = -30V_g$$

$$V_o = \left(\frac{30}{4 - j12} \right) V_g = \frac{7.5}{1 - j3} V_g = 0.75(1 + j3)V_g$$

$$= 120(1 + j3) = 379.47 \angle 71.57^\circ \text{ mV}$$

$$\therefore v_o = 379.47 \cos(50,000t + 71.57^\circ) \text{ mV}$$

P10.37 $\frac{V_o}{-j8} + \frac{V_o - 2.4I_\Delta}{j4} + \frac{V_o}{5} = 10\sqrt{2} \angle +45^\circ$

$$j5V_o - j10(V_o - 2.4I_\Delta) + 8V_o = 400\sqrt{2} \angle +45^\circ$$

$$V_o[j5 - j10 + 8] + j24 \frac{V_o}{-j8} = 400\sqrt{2}/+45^\circ$$


$$V_o(8 - j5 - 3) = 400\sqrt{2}/+45^\circ$$

$$V_o(5 - j5) = 400\sqrt{2}/+45^\circ$$

$$V_o = \frac{400\sqrt{2}/+45^\circ}{5\sqrt{2}/-45^\circ} = 80/90^\circ \text{ V}$$

$$V_o = 0 + j80 \text{ V}$$

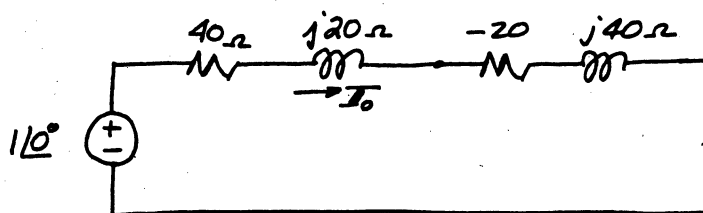P10.38 $V_o = -16I_o \frac{(50)(-j25)}{50 - j25} = (-160 + j320)I_o; \quad \frac{V_o}{8} = (-20 + j40)I_o$



$$I_o = \frac{1/0^\circ}{20 + j60} = \frac{0.05/0^\circ}{1 + j3}$$

$$I_o = 0.005(1 - j3) = 15.81/-71.57^\circ \text{ mA}$$


$$V_o = (-160 + j320)I_o = 5.66/45^\circ \text{ V}$$

P10.39 $V_g = 10/-90^\circ = -j10 \text{ V}; \quad I_g = 4/0^\circ \text{ A}$

$$\frac{1}{j\omega C_1} = \frac{10^6}{j10^4(2)} = -j50 \Omega$$

$$j\omega L = j10^4(0.6 \times 10^{-3}) = j6 \Omega$$
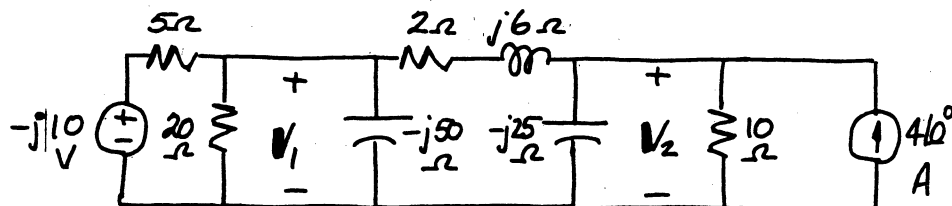
$$\frac{1}{j\omega C_2} = \frac{10^6}{j10^4(4)} = -j25 \Omega$$



$$\frac{V_1 + j10}{5} + \frac{V_1}{20} + \frac{V_1}{-j50} + \frac{V_1 - V_2}{2 + j6} = 0$$

$$V_1 \left[\frac{1}{5} + \frac{1}{20} + \frac{1}{50} + \frac{2 - j6}{40} \right] - \frac{V_2(2 - j6)}{40} = -j2$$

$$V_1[20 + 5 + j2 + 5 - j15] - V_2(5 - j15) = -j200$$

$$\boxed{V_1(30 - j13) - V_2(5 - j15) = -j200}$$

$$\frac{V_2 - V_1}{2 + j6} + \frac{V_2}{-j25} + \frac{V_2}{10} = 4\angle 0^\circ$$

$$-V_1 \left(\frac{1 - j3}{20} \right) + V_2 \left[\frac{1 - j3}{20} + \frac{1}{25} + \frac{1}{10} \right] = 4\angle 0^\circ$$

$$-V_1(5 - j15) + V_2[5 - j15 + j4 + 10] = 400$$

$$\boxed{-V_1(5 - j15) + V_2[15 - j11] = 400}$$

$$\Delta = \begin{vmatrix} 30 - j13 & -(5 - j15) \\ -(5 - j15) & 15 - j11 \end{vmatrix} = 450 - j330 - j195 - 143 - (25 - j75 - j75 - 225)$$

$$= 650 - 143 - j525 + j150 = 507 - j375 = 630.61\angle -36.49^\circ$$

$$N_1 = \begin{vmatrix} -j200 & -(5 - j15) \\ 400 & 15 - j11 \end{vmatrix} = -j3000 - 2200 + 2000 - j6000$$

$$= -200 - j9000 = 9002.22\angle -91.27^\circ$$

$$N_2 = \begin{vmatrix} 30 - j13 & -j200 \\ -(5 - j15) & 400 \end{vmatrix} = 12,000 - j5200 - j200(5 - j15)$$

$$= 12,000 - j5200 - j1000 - 3000 = 9000 - j6200 = 10,928.86\angle -34.56^\circ$$

$$V_1 = \frac{N_1}{\Delta} = \frac{9002.22\angle -91.27^\circ}{630.61\angle -36.49^\circ} = 14.28\angle -54.78^\circ \text{ V}$$

$$V_2 = \frac{N_2}{\Delta} = \frac{10,928.86\angle -34.56^\circ}{630.61\angle -36.49^\circ} = 17.33\angle 1.93^\circ \text{ V}$$

$$\therefore v_1 = 14.28 \cos(10^4 t - 54.78^\circ) \text{ V}; \quad v_2 = 17.33 \cos(10^4 t + 1.93^\circ) \text{ V}$$

P10.40 Let I_2 be the current in the $35 + j20 \Omega$ branch.

$$400\angle 0^\circ = (5 - j10)I_1 + (35 + j20)I_2$$

$$I_1 - I_2 = 0.1V_\Delta = 0.1(j20I_2)$$

$$I_1 - I_2 = j2I_2$$

$$I_1 = (1 + j2)I_2, \quad I_2 = \frac{I_1}{(1 + j2)} = \frac{(1 - j2)}{5}I_1$$


$$\therefore 400\angle 0^\circ = (5 - j10)I_1 + (7 + j4)(1 - j2)I_1$$

$$= [5 - j10 + 7 - j14 + j4 + 8]I_1 = (20 - j20)I_1$$

$$I_1 = \frac{400}{20 - j20} = \frac{20}{1 - j1} = 10(1 + j1)$$

$$I_1 = 10 + j10 = 14.14\angle 45^\circ \text{ A}$$

P10.41

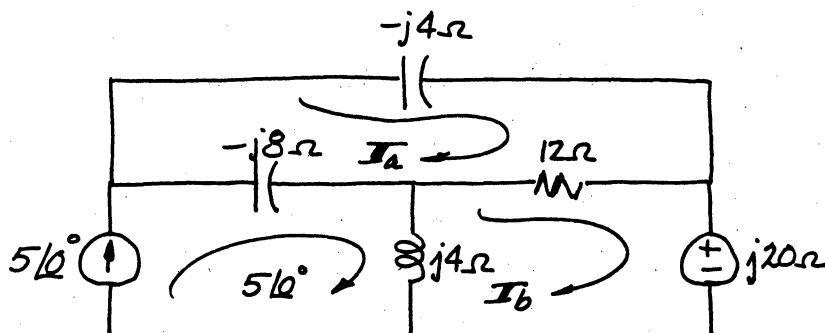

$$-j4I_a + 12(I_a - I_b) - j8(I_a - 5) = 0;$$

$$I_a(12 - j12) - 12I_b = -j40$$

$$j4(I_b - 5) + 12(I_b - I_a) + j20 = 0;$$

$$-12I_a + (12 + j4)I_b = 0$$

$$\Delta = \begin{vmatrix} 12 - j12 & -12 \\ -12 & 12 + j4 \end{vmatrix} = 144 + j48 - j144 + 48 - 144 = 48 - j96 = 48(1 - j2)$$

$$N_b = \begin{vmatrix} 12 - j12 & -j40 \\ -12 & 0 \end{vmatrix} = -j480$$

$$I_b = \frac{N_b}{\Delta} = \frac{-j480}{48(1 - j2)} = \frac{-j10(1 + j2)}{5} = -j2(1 + j2) = 4 - j2 \text{ A}$$

$$I_g = 4 - j2 = 4.47 \angle -26.57^\circ \text{ A}$$

P10.42 I_1 and I_2 are clockwise mesh currents.

$$240 \angle 0^\circ = (3 + j4)I_1 - (1 - j5)I_2$$

$$-120 \angle -90^\circ = -(1 - j5)I_1 + (3.92 + j1.44)I_2$$

$$\begin{aligned} \Delta &= \begin{vmatrix} 3 + j4 & -(1 - j5) \\ -(1 - j5) & 3.92 + j1.44 \end{vmatrix} \\ &= 11.76 + j4.32 + j15.68 - 5.76 - (+1 - j5 - j5 - 25) \\ &= 6 + j20 + 24 + j10 = 30 + j30 \end{aligned}$$

$$N_1 = \begin{vmatrix} 240 & -(1 - j5) \\ j120 & 3.92 + j1.44 \end{vmatrix} = 1540.8 + j465.60$$

$$N_2 = \begin{vmatrix} 3 + j4 & 240 \\ -(1 - j5) & j120 \end{vmatrix} = -240 - j840$$

$$I_1 = \frac{N_1}{\Delta} = \frac{1540.8 + j465.60}{30 + j30} = 33.44 - j17.92$$


$$I_2 = \frac{N_2}{\Delta} = \frac{-240 - j840}{30 + j30} = -18 - j10$$

$$I_a = I_1 = 33.44 - j17.92 = 37.94 \angle -28.19^\circ \text{ A}$$

$$I_b = I_2 = -18 - j10 = 20.59 \angle -150.95^\circ \text{ A}$$

$$I_c = I_1 - I_2 = 51.44 - j7.92 = 52.05 \angle -8.75^\circ \text{ A}$$

P10.43

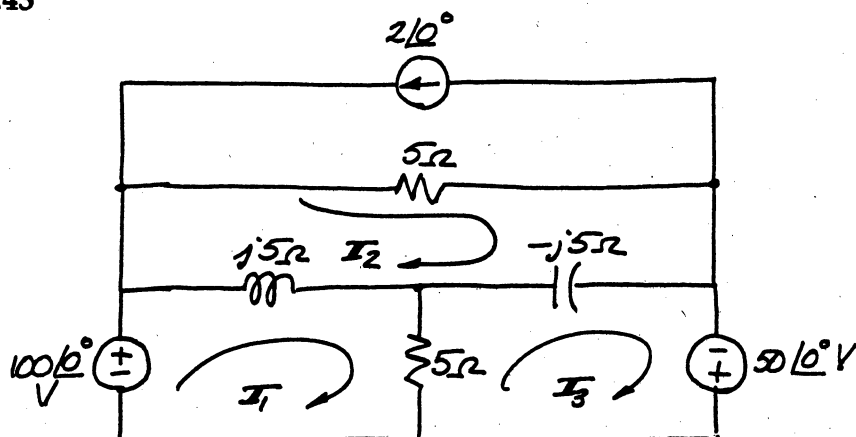

$$100\angle 0^\circ = (5 + j5)I_1 - j5I_2 - 5I_3$$

$$-10\angle 0^\circ = -j5I_1 + 5I_2 + j5I_3$$

$$50\angle 0^\circ = -5I_1 + j5I_2 + (5 - j5)I_3$$

$$20 = (1 + j1)I_1 - jI_2 - I_3$$

$$-2 = -jI_1 + I_2 + jI_3$$

$$10 = -I_1 + jI_2 + (1 - j1)I_3$$

$$\Delta = \begin{vmatrix} 1 + j1 & -j & -1 \\ -j & 1 & j \\ -1 & j & 1 - j1 \end{vmatrix}$$

$$= (1 + j1)(1 - j1 + 1) + j(-j - 1 + j) - 1(1 + 1)$$

$$= (1 + j1)(2 - j) - j - 2 = 2 - j1 + j2 + 1 - j - 2 = 1$$

$$N_1 = \begin{vmatrix} 20 & -j & -1 \\ -2 & 1 & j \\ 10 & j & (1 - j1) \end{vmatrix}$$

$$= 20(1 - j1 + 1) + 2(-j - 1 + j) + 10(1 + 1)$$

$$= 20(2 - j) + 2(-1) + 20 = 58 - j20$$

$$\therefore I_1 = 58 - j20 \text{ A}$$

$$N_2 = \begin{vmatrix} (1 + j1) & 20 & -1 \\ -j & -2 & j \\ -1 & 10 & (1 - j1) \end{vmatrix}$$

$$= (1 + j1)(-2 + j2 - 10j) + j(20 - j20 + 10) - 1(20j - 2)$$

$$= (1 + j1)(-2 - j8) + j(30 - j20) - j20 + 2 = 28 + j0$$

$$\therefore I_2 = 28 + j0 \text{ A}$$


$$N_3 = \begin{vmatrix} (1 + j1) & -j & 20 \\ -j & 1 & -2 \\ -1 & j & 10 \end{vmatrix}$$

$$= 20(1 + 1) + 2(j - 1 - j) + 10(1 + j + 1)$$

$$= 40 - 2 + 20 + j10 = 58 + j10$$

$$\begin{aligned}
 \therefore \mathbf{I}_3 &= 58 + j10 \text{ A} \\
 \mathbf{I}_a &= 2 + \mathbf{I}_2 = 30 + j0 \text{ A} \\
 \mathbf{I}_b &= \mathbf{I}_1 - \mathbf{I}_2 = 58 - j20 - 28 = 30 - j20 \text{ A} \\
 \mathbf{I}_c &= \mathbf{I}_3 - \mathbf{I}_2 = 58 + j10 - 28 = 30 + j10 \text{ A} \\
 \mathbf{I}_d &= \mathbf{I}_1 - \mathbf{I}_3 = 58 - j20 - 58 - j10 = -j30 \text{ A}
 \end{aligned}$$

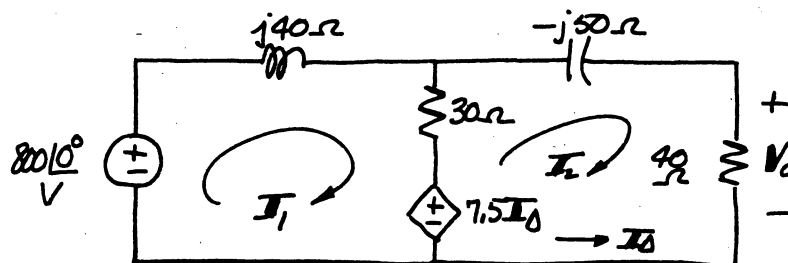P10.44 $\mathbf{V}_g = 800\angle 0^\circ \text{ V}; \quad j\omega L = j40 \Omega; \quad \frac{1}{j\omega C} = -j50 \Omega$



$$800\angle 0^\circ = (30 + j40)\mathbf{I}_1 - 30\mathbf{I}_2 + 7.5(-\mathbf{I}_2);$$

$$800\angle 0^\circ = (30 + j40)\mathbf{I}_1 - 37.5\mathbf{I}_2$$

$$0 = -7.5(-\mathbf{I}_2) + 30(\mathbf{I}_2 - \mathbf{I}_1) + (40 - j50)\mathbf{I}_2;$$

$$0 = -30\mathbf{I}_1 + (77.5 - j50)\mathbf{I}_2$$

$$\begin{aligned}
 \Delta &= \begin{vmatrix} (30 + j40) & -37.5 \\ -30 & (77.5 - j50) \end{vmatrix} = 2325 - j1500 + j3100 + 2000 - 1125 \\
 &= 3200 + j1600 = 1600(2 + j1)
 \end{aligned}$$


$$N_2 = \begin{vmatrix} (30 + j40) & 800\angle 0^\circ \\ -30 & 0 \end{vmatrix} = 24,000\angle 0^\circ$$

$$\mathbf{I}_2 = \frac{N_2}{\Delta} = \frac{24,000}{1600(2 + j1)} = \frac{15}{5}(2 - j1) = 6 - j3 \text{ A}$$

$$\mathbf{V}_o = 40\mathbf{I}_2 = 240 - j120 \text{ V} = 268.33\angle -26.57^\circ \text{ V}$$

$$v_o = 268.33 \cos(8000t - 26.57^\circ) \text{ V}$$

P10.45 [c]

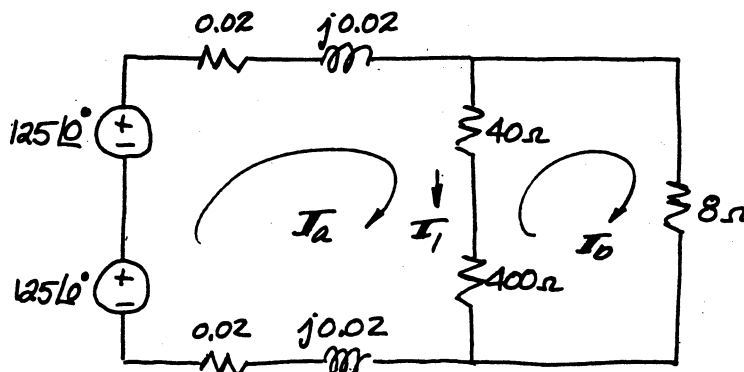

$$250 = (440.04 + j0.04)I_a - 440I_b$$

$$0 = -440I_a + 448I_b$$

$$\Delta = \begin{vmatrix} (440.04 + j0.04) & -440 \\ -440 & 448 \end{vmatrix} = 197,137.92 + j17.92 - 193,600 \\ = 3537.92 + j17.92 = 3537.97 \angle 0.29^\circ$$

$$N_a = \begin{vmatrix} 250 & -440 \\ 0 & 448 \end{vmatrix} = 112,000 + j0$$

$$I_a = \frac{N_a}{\Delta} = 31.66 \angle -0.29^\circ = 31.66 - j0.16$$

$$N_b = \begin{vmatrix} (440.04 + j0.04) & 250 \\ -440 & 0 \end{vmatrix} = 110,000 \angle 0^\circ$$


$$I_b = \frac{N_b}{\Delta} = 31.09 \angle -0.29^\circ = 31.09 - j0.16$$

$$I_1 = I_a - I_b = 0.57 - j0.00286$$

$$V_1 = 40I_1 = 22.61 - j0.11 = 22.61 \angle -0.29^\circ \text{ V}$$

$$V_2 = 400I_1 = 226.12 - j1.15 = 226.12 \angle -0.29^\circ \text{ V}$$

[d]

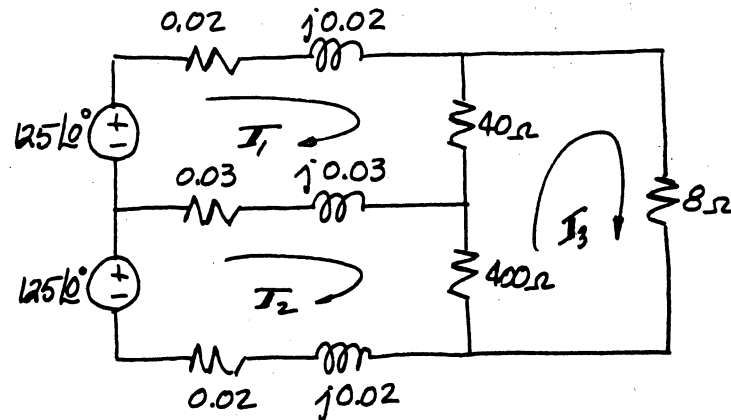

$$125 = (40.05 + j0.05)I_1 - (0.03 + j0.03)I_2 - 40I_3$$

$$125 = -(0.03 + j0.03)I_1 + (400.05 + j0.05)I_2 - 400I_3$$

$$0 = -40I_1 - 400I_2 + 448I_3$$

$$\Delta = \begin{vmatrix} (40.05 + j0.05) & -(0.03 + j0.03) & -40 \\ -(0.03 + j0.03) & (400.05 + j0.05) & -400 \\ -40 & -400 & 448 \end{vmatrix} \\ = 128,816 + j817.4336 = 128,818.59 \angle 0.36^\circ$$

$$N_1 = \begin{vmatrix} 125 & -(0.03 + j0.03) & -40 \\ 125 & (400.05 + j0.05) & -400 \\ 0 & -400 & 448 \end{vmatrix} \\ = 4,404,480 + j4480 = 4,404,482.28 \angle 0.06^\circ$$

$$I_1 = \frac{N_1}{\Delta} = 34.19 / -0.31^\circ = 34.19 - j0.18 \text{ A}$$

$$N_2 = \begin{vmatrix} (40.05 + j0.05) & 125 & -40 \\ -(0.03 + j0.03) & 125 & -400 \\ -40 & 0 & 448 \end{vmatrix}$$

$$= 4,044,480 + j4480 = 4,044,482.48 / 0.06^\circ$$

$$I_2 = \frac{N_2}{\Delta} = 31.40 / -0.30^\circ = 31.40 - j0.16 \text{ A}$$

$$N_3 = \begin{vmatrix} (40.05 + j0.05) & -(0.03 + j0.03) & 125 \\ -(0.03 + j0.03) & (400.05 + j0.05) & 125 \\ -40 & -400 & 0 \end{vmatrix}$$

$$= 4,004,400 + j4400 = 4,004,402.42 / 0.06^\circ$$

$$I_3 = \frac{N_3}{\Delta} = 31.09 / -0.30^\circ = 31.09 - j0.16 \text{ A}$$


$$V_1 = 40(I_1 - I_3) = 124.23 / -0.35^\circ \text{ V}$$

$$V_2 = 400(I_2 - I_3) = 124.45 / -0.25^\circ \text{ V}$$

[e] Because an open neutral can result in severely unbalanced voltages across the 125-V loads.

P10.46 $V_a = 240 / -90^\circ = -j240 \text{ V}; \quad V_b = 120 / 0^\circ \text{ V}$
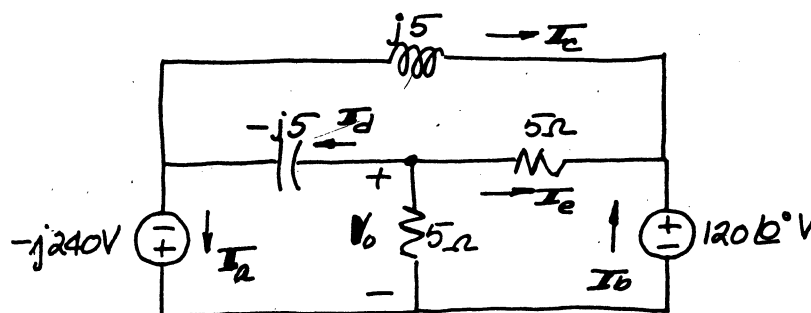
$$j\omega L = j10^5(50 \times 10^{-6}) = j5 \Omega; \quad \frac{1}{j\omega C} = -j \left(\frac{10^6}{2 \times 10^5} \right) = -j5 \Omega$$



$$\frac{V_o}{5} + \frac{V_o - j240}{-j5} + \frac{V_o - 120}{5} = 0$$

$$V_o + (V_o - j240)j + V_o - 120 = 0$$

$$(2 + jV_o) = -120; \quad V_o = -48 + j24 \text{ V}$$

$$I_c = \frac{j240 - 120}{j5} = 48 + j24 \text{ A}$$

$$I_d = \frac{-48 + j24 - j240}{-j5} = 43.2 - j9.6 \text{ A}$$

$$\mathbf{I}_a = \mathbf{I}_d - \mathbf{I}_c = -4.8 - j33.6 \text{ A}$$

$$\mathbf{I}_e = \frac{-48 + j24 - 120}{5} = -33.6 + j4.8$$

$$\mathbf{I}_b = -\mathbf{I}_e - \mathbf{I}_c = 33.6 - j4.8 - 48 - j24 = -14.40 - j28.80 \text{ A}$$

$$\therefore \mathbf{I}_a = 33.94 \angle -98.13^\circ \text{ A}$$

$$\mathbf{I}_b = 32.20 \angle -116.57^\circ \text{ A}$$

$$\mathbf{I}_c = 48 + j24 = 53.67 \angle 26.57^\circ \text{ A}$$


$$\therefore i_a = 33.94 \cos(10^5 t - 98.13^\circ) \text{ A}$$

$$i_b = 32.20 \cos(10^5 t - 116.57^\circ) \text{ A}$$

$$i_c = 53.67 \cos(10^5 t + 26.57^\circ) \text{ A}$$

P10.47 [a] $\mathbf{I}_g = 5 \angle 0^\circ \text{ A}; \quad \frac{1}{j\omega C} = -j10 \Omega; \quad j\omega L = j20 \Omega$
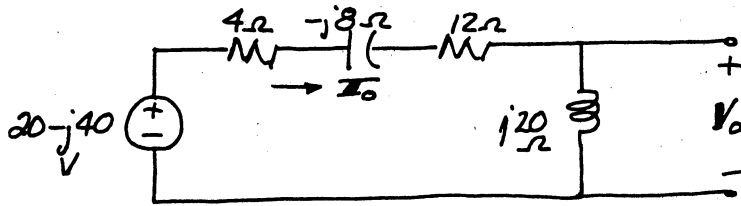
$$20 \Omega // -j10 \Omega = \frac{20(-j10)}{20 - j10} = \frac{-j20}{2 - j1} = -j4(2 + j1) = 4 - j8 \Omega$$



$$\mathbf{I}_o = \frac{20 - j40}{16 + j12} = \frac{5 - j10}{4 + j3} = \frac{5(1 - j2)(4 - j3)}{25} = 0.2(4 - j3 - j8 - 6)$$

$$= 0.2(-2 - j11)$$

$$\mathbf{V}_o = j20\mathbf{I}_o = j20(0.2)(-2 - j11) = 44 - j8 = 44.72 \angle -10.30^\circ \text{ V}$$

$$v_o = 44.72 \cos(800,000t - 10.30^\circ) \text{ V}$$

[b] $T = \frac{1}{f} = \frac{\pi}{0.8 \times 10^6} = 7.854 \times 10^{-6} = 7854 \text{ ns}$

$$\frac{10.3}{360}(7854) = 224.7 \text{ ns}$$

P10.48 $\mathbf{V}_a$ is the voltage across $j5 \Omega$ impedance.

$$\frac{\mathbf{V}_a}{j5} + \frac{\mathbf{V}_a - 100 + j50}{20} + \frac{\mathbf{V}_a - 140 - j30}{12 + j16} = 0$$

$$-j4\mathbf{V}_a + \mathbf{V}_a - 100 + j50 + \frac{5\mathbf{V}_a - 700 - j150}{3 + j4} = 0$$

$$\mathbf{V}_a \left(1 - j4 + \frac{5}{3 + j4} \right) = 100 - j50 + \frac{700 + j150}{3 + j4}$$

$$\mathbf{V}_a(1.6 - j4.8) = 208 - j144$$

$$V_a = 40 + j30 \text{ V}$$

$$\frac{V_b}{-j10} + \frac{V_b - V_a}{12 + j16} - I_g + \frac{V_b - V_g}{Z} = 0$$

$$\frac{140 + j30}{-j10} + \frac{140 + j30 - 40 - j30}{12 + j16} - 30 - j20 + \frac{40 + j80}{Z} = 0$$


$$j(14 + j3) + \frac{100(12 - j16)}{400} - 30 - j20 + \frac{40 + j80}{Z} = 0$$

$$j14 - j4 - 30 - j20 + \frac{40 + j80}{Z} - 30 - j10 + \frac{40 + 80}{Z} = 0$$

$$Z = \frac{40 + j80}{30 + j10} = \frac{4 + j8}{3 + j1} = \frac{(4 + j8)(3 - j1)}{10} = \frac{12 - j4 + j24 + 8}{10} = 2 + j2 \Omega$$


$$\begin{aligned} \text{P10.49 } V_{Th} = V_{ab} &= \frac{240/0^\circ(36)}{36 + j60 - j48} = \frac{240/0^\circ(36)}{36 + j12} = \frac{720/0^\circ}{3 + j1} \\ &= 72(3 - j1) = 216 - j72 \text{ V} \end{aligned}$$
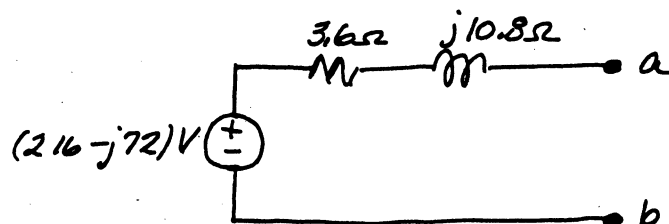
$$Z_{Th} = \frac{(36)(j12)}{36 + j12} = \frac{j36}{3 + j1} = j3.6(3 - j1) = 3.6 + j10.8 \Omega$$



Thevenin Equivalent

P10.50

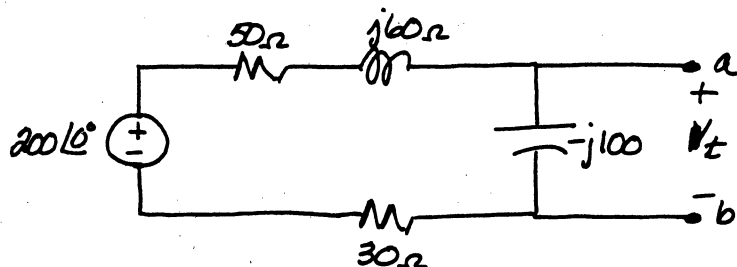


$$V_{Th} = \left(\frac{200}{80 - j40} \right) (-j100) = \frac{5}{2 - j1} (-j100) = -j100(2 + j1) = 100 - j200 \text{ V}$$

$$Z_{Th} = \frac{(-j100)(80 + j60)}{(80 - j40)} = 100 - j50 \Omega$$


$$I_N = \frac{V_{Th}}{Z_{Th}} = \frac{100 - j200}{100 - j50} = \frac{2 - j4}{2 - j1} = 1.6 - j1.2 \text{ A}$$

$$Z_N = Z_{Th} = 100 - j50 \Omega$$

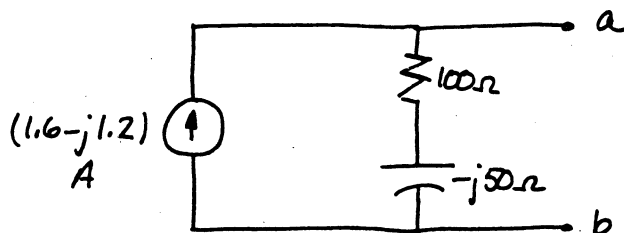

Norton Equivalent


Alternate solution:

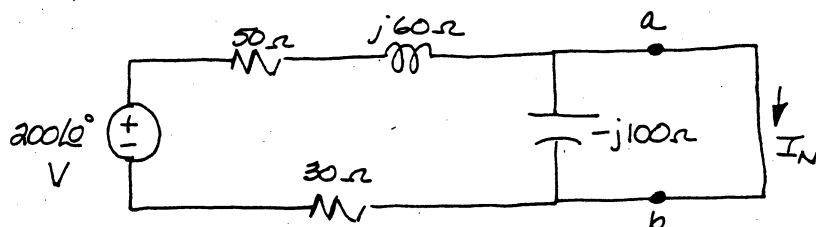

$$I_N = \frac{200}{80 + j60} = 2 \angle -36.87^\circ = 1.6 - j1.2 \text{ A}$$

$$Z_N = Z_{Th} = 100 - j50 \Omega$$

P 10.51

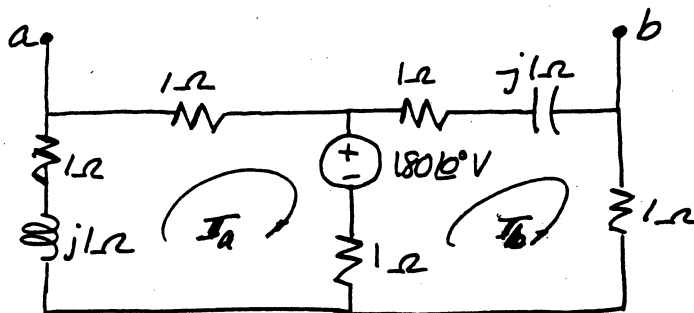

$$(3 + j1)I_a - I_b = -180$$

$$-I_a + (3 - j1)I_b = 180$$

$$\Delta = \begin{vmatrix} (3 + j1) & -1 \\ -1 & (3 - j1) \end{vmatrix} = 9$$

$$N_b = \begin{vmatrix} (3 + j1) & -180 \\ -1 & 180 \end{vmatrix} = 180(3 + j1 - 1) = 180(2 + j1)$$


$$N_a = \begin{vmatrix} -180 & -1 \\ 180 & (3 - j1) \end{vmatrix} = -180(3 - j1) + 180 = -180(2 - j1)$$

$$I_a = \frac{N_a}{\Delta} = -20(2 - j1) = -40 + j20 \text{ A}$$

$$I_b = \frac{N_b}{\Delta} = 20(2 + j1) = 40 + j20 \text{ A}$$

$$\begin{aligned} V_{ab} = V_{Th} &= I_a \cdot 1 + I_b(1 - j1) = -40 + j20 + (1 - j1)(40 + j20) \\ &= -40 + j20 + 40 + j20 - j40 + 20 \end{aligned}$$


$$V_{Th} = 20 \angle 0^\circ \text{ V}$$

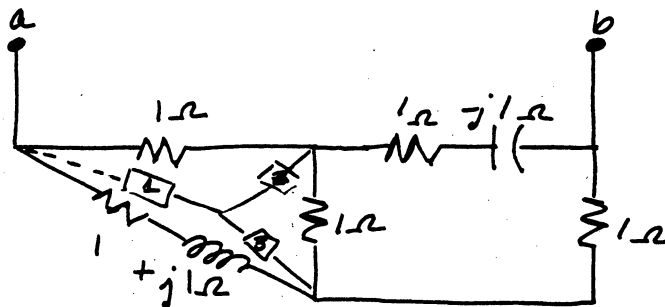


$$\begin{aligned} Z_1 &= \frac{(1)(1 + j1)}{(3 + j1)} = \frac{1}{10}(1 + j1)(3 - j1) = \frac{1}{10}(3 - j1 + j3 + 1) \\ &= \frac{1}{10}(4 + j2) = 0.4 + j0.2 \Omega \end{aligned}$$

$$Z_2 = \frac{(1)(1)}{3 + j1} = \frac{1}{10}(3 - j1) = 0.3 - j0.1$$

$$Z_3 = Z_1 = 0.4 + j0.2 \Omega$$

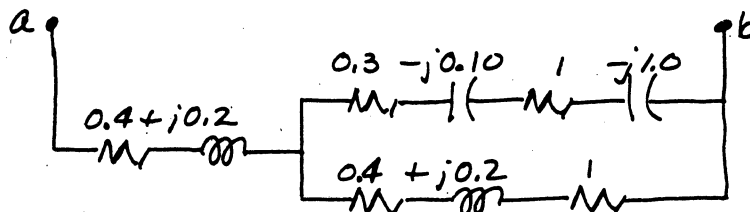
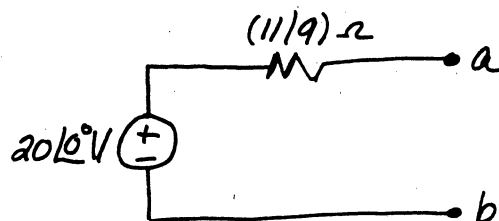
$$\begin{aligned} Z_{ab} = Z_{Th} &= 0.4 + j0.2 + \frac{(1.3 - j1.1)(1.4 + j0.2)}{(2.7 - j0.9)} \\ &= \frac{3.6 + j1.8 + (1.82 + j0.26 - j1.54 + 0.22)(3 + j1)}{9} \\ &= \frac{3.6 + j1.8 + (2.04 - j1.28)(3 + j1)}{9} \\ &= \frac{3.6 + j1.8 + 6.12 + j2.04 - j3.84 + 1.28}{9} \\ &= \frac{11 + j3.84 - j3.84}{9} = \frac{11}{9} \Omega \end{aligned}$$



Thevenin equivalent

P 10.52 $-0.03V_o + \frac{V_1 - 250}{20 + j10} + \frac{V_1}{50 - j100} = 0$

$$V_o = \frac{V_1}{50 - j100}(-j100) = \frac{-j2V_1}{1 - j2} = \frac{(4 - j2)}{5}V_1$$

$$-0.03\left(\frac{4 - j2}{5}\right)V_1 + \frac{V_1}{20 + j10} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$= \left[\frac{-0.06(2 - j1)}{5} + \frac{20 - j10}{500} + \frac{50 + j100}{12,500} \right] V_1 = \frac{250(20 - j10)}{500}$$

$$[-150(2 - j1) + 25(20 - j10) + 50 + j100]V_1 = (10 - j5)(12,500)$$


$$[250 + j0]V_1 = 12,500(10 - j5)$$

$$V_1 = \frac{(12,500)(10 - j5)}{250 + j0}$$

$$V_1 = 500 - j250 \text{ V}$$

$$V_o = \left(\frac{4 - j2}{5}\right)(500 - j250) = (4 - j2)(100 - j50) = 400 - j200 - j200 - 100$$
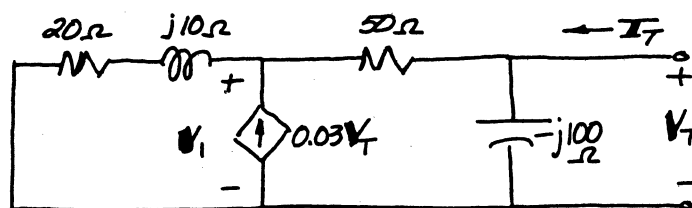
$$= 300 - j400 \text{ V} = 500\angle -53.13^\circ \text{ V}$$



$$I_T = \frac{V_T}{-j100} + \frac{V_T - V_1}{50}$$

$$-0.03V_T + \frac{V_1}{20 + j10} + \frac{V_1 - V_T}{50} = 0$$

$$-0.03V_T + \frac{V_1(20 - j10)}{500} + \frac{V_1 - V_T}{50} = 0$$

$$-15V_T + (20 - j10)V_1 + 10V_1 - 10V_T = 0$$

$$(30 - j10)V_1 = 25V_T$$


$$V_1 = \frac{25V_T}{30 - j10}$$

$$\therefore I_T = \frac{j}{100} V_T + \frac{1}{50} V_T - \frac{1}{50} \frac{25V_T}{(30 - j10)}$$

$$\frac{I_T}{V_T} = \frac{j}{100} + \frac{1}{50} - \frac{1}{2} \frac{(30 + j10)}{1000} = \frac{j}{100} + \frac{1}{50} - \frac{(3 + j1)}{200}$$

$$= \frac{2j + 4 - 3 - j1}{200} = \frac{1 + j1}{200}$$
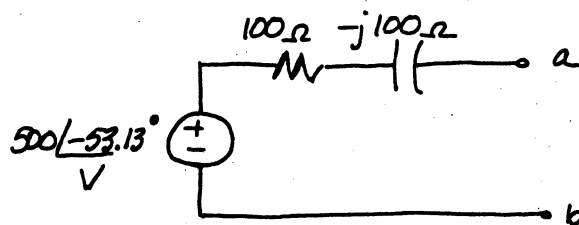
$$Z_{Th} = \frac{V_T}{I_T} = \frac{200}{1 + j1} = 100(1 - j1) = 100 - j100 \Omega$$



Thevenin equivalent

Alternate solution:

$$\text{Find } I_{sc}: I_{sc} = \frac{250}{70 + j10} = \frac{250}{5000}(70 - j10) = 3.5 - j0.5$$

$$Z_{Th} = \frac{300 - j400}{3.5 - j0.5} = \frac{600 - j800}{7 - j1} = \frac{(600 - j800)(7 + j1)}{50} = (12 - j16)(7 + j1)$$

$$= 84 + 16 - j112 + j12 = 100 - j100 \Omega$$


P10.53 $\frac{V_2}{10} + 88I_\phi + \frac{V_2 - (V_2/5)}{-j50} = 0$

$$\frac{V_2}{10} + j\frac{0.8V_2}{50} + 88 \left[\frac{5 - 0.2V_2}{200} \right] = 0$$

$$20V_2 + j3.2V_2 + 440 - 17.6V_2 = 0$$

$$(2.4 + j3.2)V_2 = -440$$
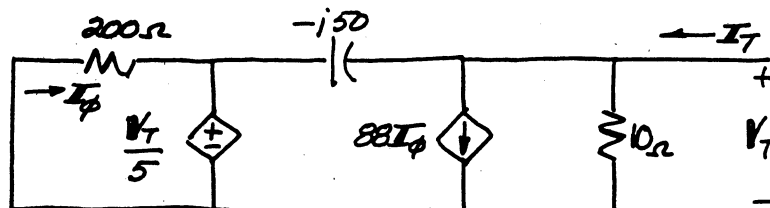
$$V_2 = V_{Th} = -110/-53.13^\circ = 110/126.87^\circ \text{ V}$$




$$I_T = \frac{V_T}{10} + 88 \left(\frac{-V_T}{1000} \right) + \frac{V_T - 0.2V_T}{-j50}$$

$$\frac{I_T}{V_T} = \frac{1}{10} - 0.088 + \frac{0.80}{-j50} = 0.1 - 0.088 + j0.016 = 0.012 + j0.016$$


$$Z_N = Z_{Th} = \frac{1}{0.012 + j0.016} = \frac{1000}{12 + j16} = 50 \angle -53.13^\circ \Omega$$
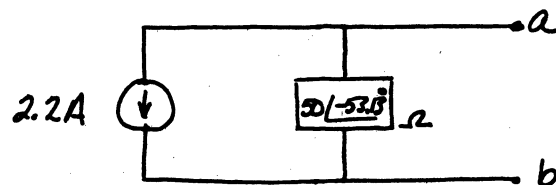
$$I_N = \frac{V_{Th}}{Z_N} = \frac{110 \angle 126.87^\circ}{50 \angle -53.13^\circ} = 2.2 \angle 180^\circ = -2.2 + j0 \text{ A}$$



NORTON EQUIVALENT

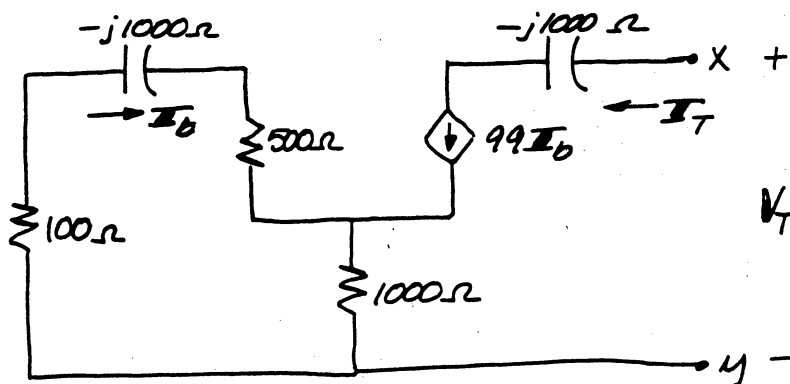P10.54 [a] $\frac{1}{j\omega C} = -j1000 \Omega$; $\omega = 1000 \text{ rad/s}$



First find Z_{xy} , then $Z_{ab} = 2000 \Omega // Z_{xy}$

Now observe $I_T = 99I_b$


But $I_b = -I_T \left(\frac{1000}{1600 - j1000} \right)$

$$\therefore I_T = \frac{-99I_T(1000)}{1600 - j1000}, \quad \therefore I_T = 0$$

$$\therefore Z_{xy} = \frac{V_T}{I_T} = \infty$$

$$\therefore Z_{ab} = 2000 \Omega = Z_{Th}$$

[b]

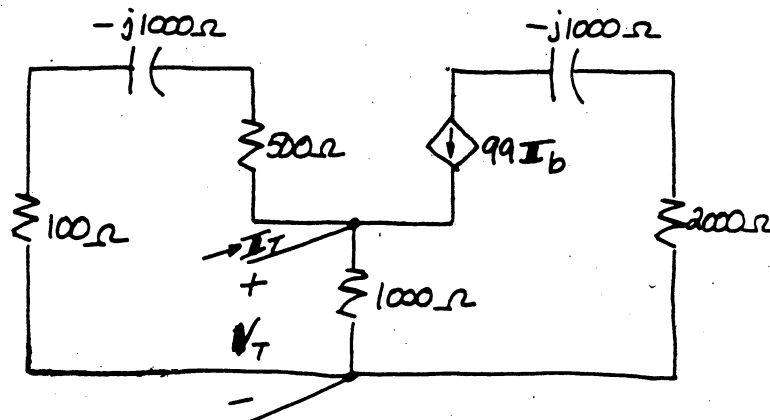

$$I_T = \frac{V_T}{1000} + \frac{V_T}{600 - j1000} - 99I_b$$


$$I_b = \frac{-V_T}{600 - j1000}$$

$$\therefore I_T = \frac{V_T}{1000} + \frac{V_T}{600 - j1000} + \frac{99V_T}{600 - j1000}$$

$$\frac{I_T}{V_T} = \frac{1}{1000} + \frac{100}{600 - j1000} = \frac{1}{1000} + \frac{1}{6 - j10} = \frac{1006 - j10}{1000(6 - j10)}$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{1000(6 - j10)}{(1006 - j10)} = 11.59 \angle -58.57^\circ \Omega$$

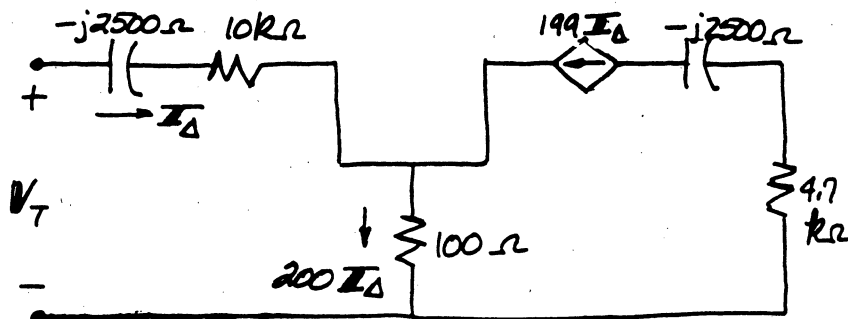P 10.55 $\omega = 400 \text{ rad/s}; \quad \frac{1}{j\omega C} = -j2500 \Omega$




$$I_T = I_\Delta$$

$$V_T = -j2500I_T + 10,000I_T + 100(200I_T)$$

$$\frac{V_T}{I_T} = 30,000 - j2500 = 30,103.99 \angle -4.76^\circ \Omega$$


$$Z_{Th} = Z_{ab} = 30,103.99 \angle -4.76^\circ \Omega$$

P10.56

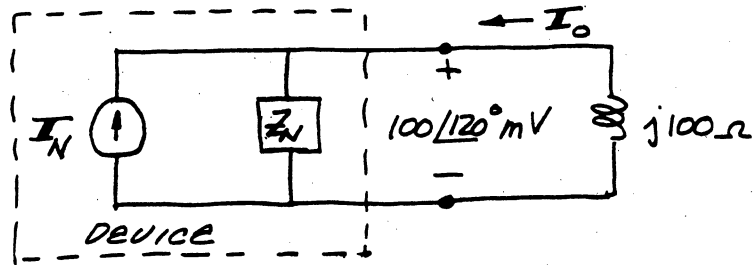

$$I_N = \frac{100/120^\circ \times 10^{-3}}{Z_N} + \frac{100/120^\circ \times 10^{-3}}{j100}$$
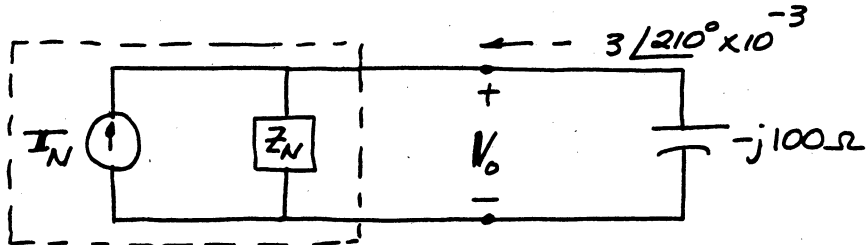
$$I_N = \frac{0.1/120^\circ}{Z_N} + 10^{-3}/30^\circ$$



$$V_o = -(-j100)(-3/210^\circ \times 10^{-3}) = -j300/210^\circ \times 10^{-3} = 0.3/120^\circ \text{ V}$$


$$I_N = \frac{0.3/120^\circ}{Z_N} - (-3 \times 10^{-3}/210^\circ) = \frac{0.3/120^\circ}{Z_N} + 3 \times 10^{-3}/210^\circ$$

$$\therefore \frac{0.1/120^\circ}{Z_N} + 10^{-3}/30^\circ = \frac{0.3/120^\circ}{Z_N} + 3 \times 10^{-3}/210^\circ$$

$$\therefore \frac{0.2/120^\circ}{Z_N} = 10^{-3}/30^\circ - 3 \times 10^{-3}/210^\circ = 4 \times 10^{-3}/30^\circ$$

$$\therefore Z_N = 50/90^\circ \Omega; \quad I_N = 3/30^\circ \text{ mA}$$

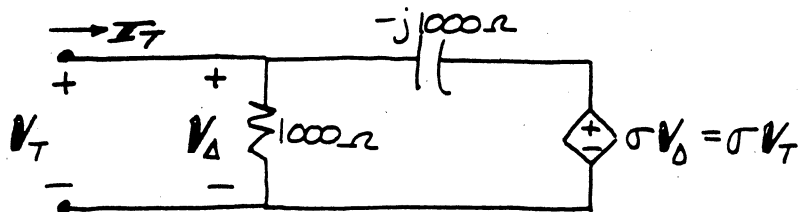P10.57 [a] $\frac{1}{j\omega C} = \frac{10^6}{j10(100)} = -j1000 \Omega$



$$\mathbf{I}_T = \frac{\mathbf{V}_T}{1000} + \frac{\mathbf{V}_T - \sigma \mathbf{V}_T}{-j1000}$$

$$\frac{\mathbf{I}_T}{\mathbf{V}_T} = \frac{1}{1000} + \frac{j(1-\sigma)}{1000} = \frac{1+j(1-\sigma)}{1000}$$

$$Z_{Th} = Z_{ab} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = \frac{1000}{1+j(1-\sigma)}$$

Z_{Th} is resistive when $\sigma = 1$.

$$[b] \quad Z_{Th} = \frac{1000}{1+j0} = 1000 \Omega$$

$$[c] \quad 500 - j500 = \frac{1000}{1+j(1-\sigma)} = \frac{1000[1-j(1-\sigma)]}{1+(1-\sigma)^2}$$

$$\therefore 500 = \frac{1000}{1+(1-\sigma)^2}$$

$$500 = \frac{1000(1-\sigma)}{1+(1-\sigma)^2}$$

$$\therefore 1+(1-\sigma)^2 = 2$$

$$(1-\sigma)^2 = 1$$

$$(1-\sigma) = \pm 1, \quad \sigma = 1 \mp 1$$

$\sigma = 0, \quad \sigma = 2$ makes the real part equal to 500

The imaginary part will equal 500 when

$$1+(1-\sigma)^2 = 2(1-\sigma) \quad \text{or} \quad (1-\sigma)^2 - 2(1-\sigma) + 1 = 0$$

$$\text{Let } x = (1-\sigma)$$

$$x^2 - 2x + 1 = 0$$

$$(x-1)^2 = 0; \quad x = 1$$

$$\therefore 1-\sigma = 1; \quad \sigma = 0$$

$$\therefore \text{If } \sigma = 0, \quad Z_{Th} = 500 - j500 \Omega$$

Yes, $\sigma = 0$


$$[d] \quad Z_{Th} = \frac{1000}{1+j(1-\sigma)} = \frac{1000}{1+(1-\sigma)^2} - j \frac{1000(1-\sigma)}{1+(1-\sigma)^2}$$

$\therefore Z_{Th}$ will be inductive whenever $\sigma > 1$. For example, if $\sigma = 2$.

$$Z_{Th} = \frac{1000}{(1+1)} - j \frac{1000(-1)}{(1+1)} = 500 + j500 \Omega$$

P10.58 Since the current sources are operating at different frequencies, we must use superposition to find the steady-state expression for v_o .

When $\omega = 25 \text{ rad/s}$ we have

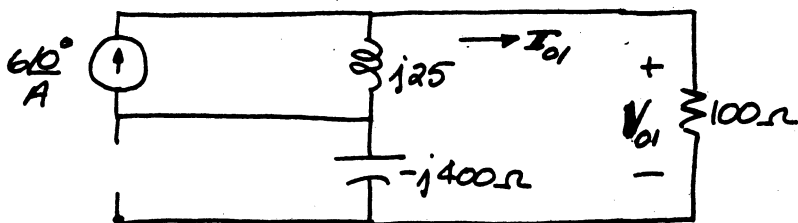


$$I_{o1} = \frac{6(j25)}{100 - j375} = \frac{j6}{4 - j15}$$

$$V_{o1} = 100I_{o1} = \frac{j600}{4 - j15} = 38.65 \angle 165.07^\circ \text{ V}$$

$$\therefore v_{o1} = 38.65 \cos(25t + 165.07^\circ) \text{ V}$$

When $\omega = 50 \text{ rad/s}$

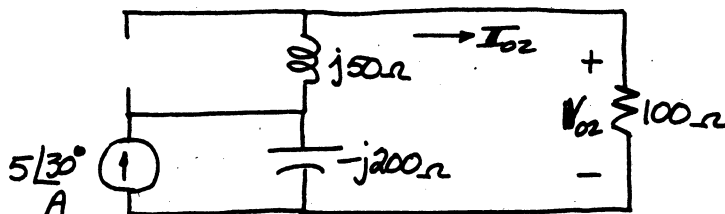

$$I_{o2} = \frac{5/30^\circ(-j200)}{(100 - j150)} = 5.54 \angle -3.69^\circ$$

$$V_{o2} = 100I_{o2} = 554.70 \angle -3.69^\circ \text{ V}$$

$$v_{o2} = 554.70 \cos(50t - 3.69^\circ) \text{ V}$$


$$v_o = v_{o1} + v_{o2} = 38.65 \cos(25t + 165.07^\circ) + 554.70 \cos(50t - 3.69^\circ) \text{ V}$$

P 10.59 [a] $I_L = \frac{240/0^\circ}{8} + \frac{240/0^\circ}{j6} = 30 - j40 \text{ A}$


$$V_L = (0.1 + j0.8)(30 - j40) = 3 - j4 + j24 + 32 = 35 + j20 \text{ V}$$

$$V_s = 240/0^\circ + V_L = 275 + j20 = 275.73 \angle 4.16^\circ \text{ V}$$


[b]

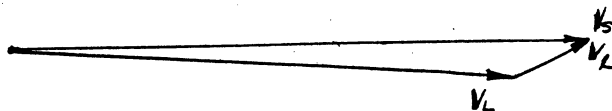
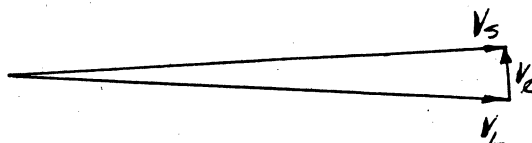
$$\begin{aligned}
 [c] \quad \mathbf{I}_t &= 30 - j40 + \frac{240/0^\circ}{-j5} = 30 - j40 + j48 \\
 \mathbf{V}_t &= (0.1 + j0.8)(30 + j8) = 3 + j0.8 + j24 - 6.4 = -3.4 + j24.80 \text{ V} \\
 \mathbf{V}_s &= 240/0^\circ - 3.4 + j24.8 = 236.60 + j24.8 = 237.90/5.98^\circ
 \end{aligned}$$




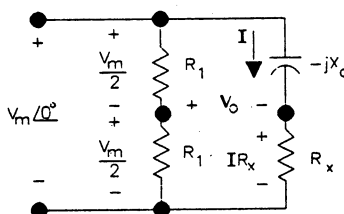P10.60 The phasor domain equivalent circuit is



$$V_o = \frac{V_m}{2} - IR_x; \quad \mathbf{I} = \frac{V_m}{R_x - jX_c}$$

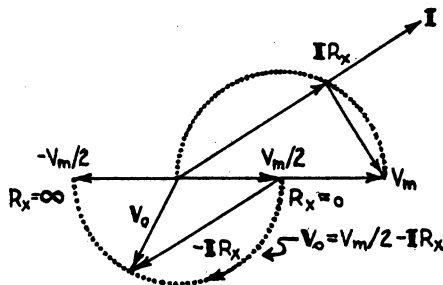As R_x varies from 0 to ∞ , the amplitude of v_o remains constant and its phase angle increases from 0° to -180° .



P10.61 [a] $\mathbf{V}_g = 2/0^\circ \text{ V}; \quad \mathbf{V}_2 = 0.8\mathbf{V}_g = 1.6/0^\circ \text{ V}; \quad \mathbf{V}_1 = \mathbf{V}_2 = 1.6/0^\circ$

$$\frac{1.6/0^\circ}{10^4} + \frac{1.6 - \mathbf{V}_o}{Z} = 0$$

$$1.6 \left[\frac{1}{10^4} + \frac{1}{Z} \right] = \frac{\mathbf{V}_o}{Z}$$

$$\therefore \mathbf{V}_o = 1.6 \left(1 + \frac{Z}{10^4} \right)$$

$$\frac{1}{j\omega C} = \frac{10^{12}}{j10^5(200)} = \frac{10^5}{j2} = -j50,000 \Omega$$

$$Z = \frac{(-j50,000)(50,000)}{50,000 - j50,000} = \frac{-j50,000}{1 - j1}$$

$$Z = -j25,000(1 + j1) = 25,000 - j25,000 \Omega$$

$$\mathbf{V}_o = 1.6(1 + 2.5 - j2.5) = 1.6(3.5 - j2.5) = 6.88 \angle -35.54^\circ \text{ V}$$

$$v_o = 6.88 \cos(10^5 t - 35.54^\circ) \text{ V}$$

$$[b] \quad \mathbf{V}_o = 0.8 \mathbf{V}_m(3.5 - j2.5) = \mathbf{V}_m(2.8 - j2.0) = 3.44 \mathbf{V}_m \angle -35.54^\circ$$

$$\therefore 3.44 \mathbf{V}_m = 15; \quad \mathbf{V}_m = 4.36 \text{ V}$$

$$\text{P10.62} \quad \frac{10^{12}}{j2 \times 10^6(100)} = \frac{10^4}{j2} = -j5 \text{ k}\Omega$$

$$\frac{10^{12}}{j2 \times 10^6(10)} = -j50 \text{ k}\Omega; \quad \mathbf{V}_g = 2 \angle 0^\circ \text{ V}$$

$$\therefore \frac{\mathbf{V}_a}{-j5} + \frac{\mathbf{V}_a - \mathbf{V}_g}{5} + \frac{\mathbf{V}_a - \mathbf{V}_o}{100} + \frac{\mathbf{V}_a - 0}{20} = 0$$

$$j20\mathbf{V}_a + 20\mathbf{V}_a - 20\mathbf{V}_g + \mathbf{V}_a - \mathbf{V}_o + 5\mathbf{V}_a = 0$$

$$(26 + j20)\mathbf{V}_a - \mathbf{V}_o = 20(2 \angle 0^\circ) = 40 \angle 0^\circ$$

$$\frac{0 - \mathbf{V}_a}{20} + \frac{0 - \mathbf{V}_o}{-j50} = 0$$

$$-\frac{\mathbf{V}_a}{20} + \frac{\mathbf{V}_o}{j50} = 0; \quad \mathbf{V}_a = \frac{20}{j50} \mathbf{V}_o = -j\frac{2}{5} \mathbf{V}_o$$

$$\therefore (26 + j20) \left(-j\frac{2}{5} \mathbf{V}_o \right) - \mathbf{V}_o = 40 \angle 0^\circ$$

$$(7 - j10.40)\mathbf{V}_o = 40 \angle 0^\circ$$

$$\mathbf{V}_o = 3.19 \angle -56.06^\circ \text{ V}$$

$$v_o = 3.19 \cos(2 \times 10^6 t - 56.06^\circ) \text{ V}$$

$$\text{P10.63} [a] \quad \frac{10^6}{j10^5(0.5)} = -j20 \Omega$$

$$\mathbf{V}_2 = \frac{6 \angle 0^\circ}{5 + (1/j\omega C_o)} \left(\frac{1}{j\omega C_o} \right) = \frac{6}{1 + j5\omega C_o} = \mathbf{V}_1$$

$$\frac{\mathbf{V}_1}{20} + \frac{\mathbf{V}_1 - \mathbf{V}_o}{-j20} = 0; \quad \mathbf{V}_1(1 + j) = j\mathbf{V}_o$$

$$\mathbf{V}_o = (1 - j1)\mathbf{V}_1 = (1 - j1) \left(\frac{6}{1 + j5\omega C_o} \right)$$

$$|\mathbf{V}_o| = 6$$

$$\therefore 6 = \frac{6\sqrt{2}}{\sqrt{1 + 25\omega^2 C_o^2}}$$

$$\therefore \sqrt{1 + 25\omega^2 C_o^2} = \sqrt{2}; \quad 25\omega^2 C_o^2 = 1$$

$$C_o = \frac{1}{5\omega} = \frac{1}{5 \times 10^5} = 2 \times 10^{-6} = 2 \mu\text{F}$$

$$[b] \quad V_o = \frac{(1-j1)6}{(1+j1)} = \frac{(\sqrt{2}/-45^\circ)6}{(\sqrt{2}/45^\circ)} = 6/-90^\circ \text{ V}$$

$$v_o = 6 \cos(10^5 t - 90^\circ) \text{ V} = -6 \sin 10^5 t \text{ V}$$

P10.64 $V_g = 4/0^\circ \text{ V}; \quad \frac{1}{j\omega C} = -j \frac{10^6}{(200)(0.25)} = -j20 \text{ k}\Omega$

$V_a \equiv$ voltage across the capacitor, positive at the upper terminal, then

$$\frac{V_a}{-j20} + \frac{V_a}{20} + \frac{V_a - 4/0^\circ}{20} = 0$$

$$V_a(2 + j1) = 4/0^\circ$$

$$\frac{0 - V_a}{20} + \frac{0 - V_o}{100} = 0; \quad \therefore V_a = -0.2V_o$$

$$-0.2V_o(2 + j1) = 4$$

$$V_o = \frac{-20}{2 + j1} = -4(2 - j1) = -8 + j4$$

$$V_o = 8.94/153.43^\circ \text{ V}$$

$$v_o = 8.94 \cos(200t + 153.43^\circ) \text{ V}$$

P10.65 [a] V_a is as defined in the solution of Problem 10.64.

$$\frac{V_a - 4}{20,000} + j200C V_a + \frac{V_a}{20,000} = 0$$

$$V_a - 4 + j4 \times 10^6 C V_a + V_a = 0$$

$$V_a(2 + j4 \times 10^6 C) = 4$$

$$V_a = -\frac{V_o}{5}$$


$$\therefore (2 + j4 \times 10^6 C)V_o = -20; \quad V_o = \frac{20/180^\circ}{2 + j4 \times 10^6 C}$$

$$\therefore 4 \times 10^6 C = 2, \quad C = \frac{1}{2} \mu\text{F}$$

$$[b] \quad V_o = \frac{20/180^\circ}{2 + j2} = \frac{10/180^\circ}{2} (1 - j1) = 5\sqrt{2}/135^\circ \text{ V} = 7.07/135^\circ \text{ V}$$

$$v_o = 7.07 \cos(200t + 135^\circ) \text{ V}$$

P10.66 [a]

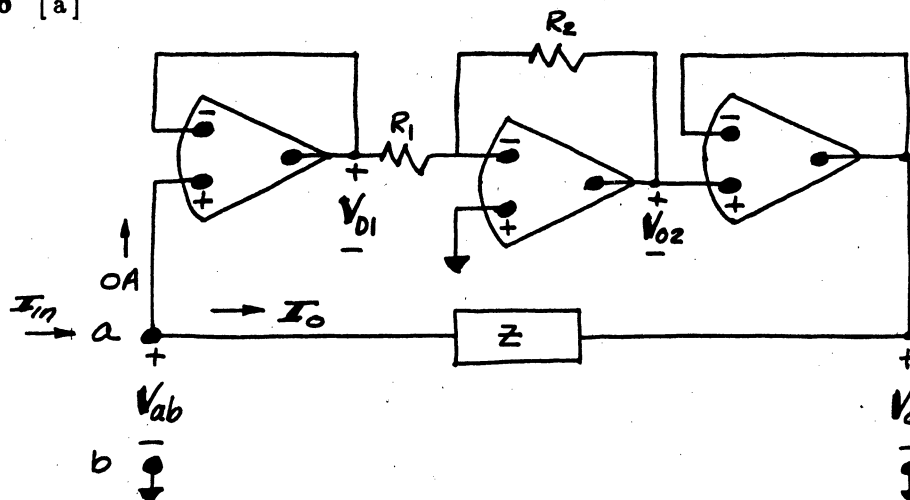

Because the op-amps are ideal $I_{in} = I_o$, thus

$$Z_{ab} = \frac{V_{ab}}{I_{in}} = \frac{V_{ab}}{I_o}; \quad I_o = \frac{V_{ab} - V_o}{Z}$$

$$V_{o1} = V_{ab}; \quad V_{o2} = -\left(\frac{R_2}{R_1}\right) V_{o1} = -K V_{o1} = -K V_{ab}$$

$$V_o = V_{o2} = -K V_{ab}$$

$$\therefore I_o = \frac{V_{ab} - (-K V_{ab})}{Z} = \frac{(1 + K) V_{ab}}{Z}$$

$$\therefore Z_{ab} = \frac{V_{ab}}{(1 + K) V_{ab}} Z = \frac{Z}{(1 + K)}$$

$$[b] \quad Z = \frac{1}{j\omega C}; \quad Z_{ab} = \frac{1}{j\omega C(1 + K)}; \quad \therefore C_{ab} = C(1 + K)$$

$$P10.67 [a] \quad I_1 = \frac{120}{24} + \frac{240}{8.4 + j6} = 23.29 - j13.71 = 27.02 \angle -30.5^\circ \text{ A}$$

$$I_2 = \frac{120}{12} - \frac{120}{24} = 5 \angle 0^\circ \text{ A}$$

$$I_3 = \frac{120}{12} + \frac{240}{8.4 + j6} = 28.29 - j13.71 = 31.44 \angle -25.87^\circ \text{ A}$$

$$I_4 = \frac{120}{24} = 5 \angle 0^\circ \text{ A}; \quad I_5 = \frac{120}{12} = 10 \angle 0^\circ \text{ A}$$

$$I_6 = \frac{240}{8.4 + j6.3} = 18.29 - j13.71 = 22.86 \angle -36.87^\circ \text{ A}$$

$$[b] \quad \begin{array}{lll} I_1 = 0 & I_3 = 15 \text{ A} & I_5 = 10 \text{ A} \\ I_2 = 10 + 5 = 15 \text{ A} & I_4 = -5 \text{ A} & I_6 = 5 \text{ A} \end{array}$$

[c] The clock and television set were fed from the uninterrupted side of the circuit, that is, the $12\text{-}\Omega$ load includes the clock and the TV set.

- [d] No, the motor current drops to 5 A, well below its normal running value of 22.86 A.
- [e] After fuse A opens, the current in fuse B is only 15 A.