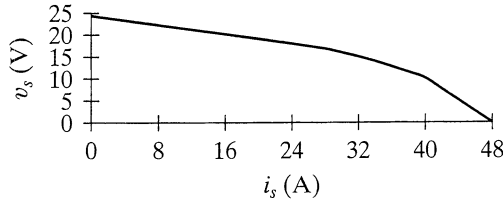


Chapter 1

- 1.1 3.93 MB
- 1.3 3.5 s
- 1.6 $362 \mu\text{m}^2$
- 1.9 $4 \sin 5000t \text{ mC}$
- 1.12 a) 300 W, A to B
b) 500 W, B to A
c) 200 W, B to A
d) 400 W, A to B
- 1.17 a) 42.21 mW
b) $12.14 \mu\text{J}$
c) $140.625 \mu\text{J}$
- 1.24 a) 8.45 s
b) -15.40 W (15.40 W delivered)
c) 31.55 s
d) 15.40 W (15.40 W extracted)
e) $w(0) = 0 \text{ J}$; $w(10) = 112.5 \text{ J}$; $w(20) = 200 \text{ J}$;
 $w(30) = 112.5 \text{ J}$; $w(40) = 0 \text{ J}$
- 1.26 1740 W


Chapter 2

- 2.2 $8 \text{ k}\Omega$
- 2.4 20Ω

- 2.14 a) 0.4 A
b) 1.6 A
c) 120 V
d) $P_{40\Omega} = 160 \text{ W}$; $P_{300\Omega} = 48 \text{ W}$; $P_{75\Omega} = 192 \text{ W}$
e) 400 W
- 2.16 a) $i_g = 6 \text{ A}$; $i_o = 2 \text{ A}$
b) 240 V
c) $P_{\text{dev}} = P_{\text{abs}} = 1440 \text{ W}$
- 2.21 a) -30 V source; 20Ω resistor
b) 10 W
- 2.23 a) 
b) 24 V source; 0.25Ω resistor
c) 19.2 A
d) 96 A
e) 48 A
f) A linear model cannot predict the nonlinear behavior of the voltage source.
- 2.26 a) $P_{4\Omega} = 900 \text{ W}$; $P_{20\Omega} = 1620 \text{ W}$; $P_{5\Omega} = 180 \text{ W}$;
 $P_{22.5\Omega} = 360 \text{ W}$; $P_{15\Omega} = 1500 \text{ W}$
b) 4560 W
c) $P_{\text{supp}} = 4560 \text{ W} = P_{\text{dis}}$
- 2.29 a) 5.55 V
b) $P_{\text{supp}} = 44.82 \text{ mW} = P_{\text{dis}}$

- 2.34 $i = 385 \text{ mA}$, so a warning sign should be posted and precautions taken.

2.35

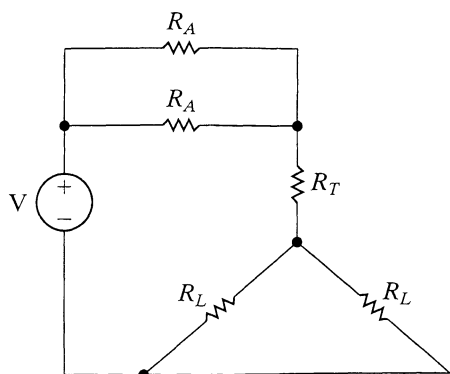


- 2.36 a) $P_{\text{arm}} = 59.17 \text{ W}$; $P_{\text{leg}} = 29.59 \text{ W}$;
 $P_{\text{trunk}} = 7.40 \text{ W}$
 b) $t_{\text{arm}} = 1414.23 \text{ s}$; $t_{\text{leg}} = 7071.13 \text{ s}$;
 $t_{\text{trunk}} = 70,677.37 \text{ s}$
 c) All values are much greater than a few minutes.

- 2.37 a) 40 V
 b) No, $12 \text{ V}/800 \Omega = 15 \text{ mA}$ will only cause a shock.


2.38 3000 V

Chapter 3


- 3.1 a) 6Ω and 12Ω ; 9Ω and 7Ω

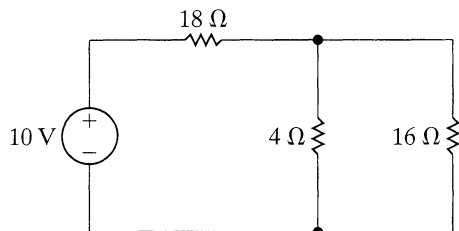

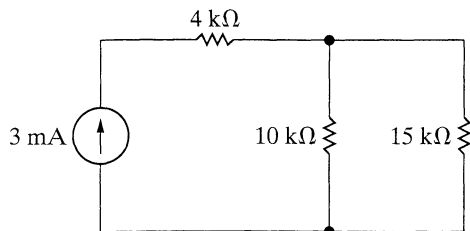
- b) $3 \text{ k}\Omega$, $5 \text{ k}\Omega$, and $7 \text{ k}\Omega$




- c) 300Ω , 400Ω , and 500Ω

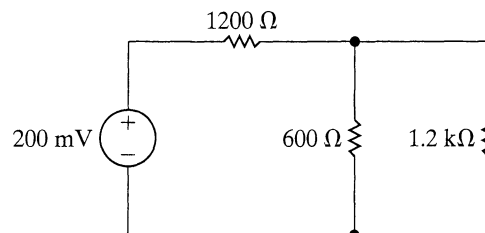


- 3.2 a) 10Ω and 40Ω ; 100Ω and 25Ω

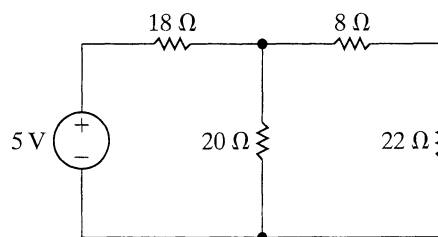

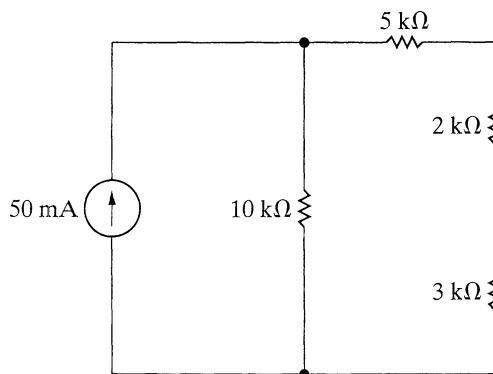- b) $9 \text{ k}\Omega$, $18 \text{ k}\Omega$, and $6 \text{ k}\Omega$



- c) 600Ω , 200Ω , and 300Ω

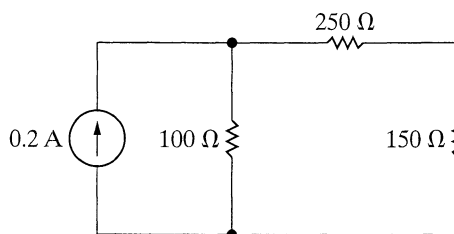

- 3.5 a) $21.2\ \Omega$
b) $10\ \text{k}\Omega$
c) $1600\ \Omega$
- 3.6 a) $30\ \Omega$
b) $5\ \text{k}\Omega$
c) $80\ \Omega$
- 3.13 a) $10\ \text{V}$
b) $P_{R_1} = 800\ \text{mW}$; $P_{R_2} = 200\ \text{mW}$
c) $R_1 = 1600\ \Omega$; $R_2 = 400\ \Omega$ (minimum values)
- 3.14 $26.67\ \Omega$
- 3.21 $R_1 = 800\ \Omega$; $R_2 = 1.6\ \text{k}\Omega$; $R_3 = 16\ \text{k}\Omega$;
 $R_4 = 16\ \text{k}\Omega$
- 3.22 a) $15\ \text{V}$, positive at the top
b) $20\ \text{mA}$, right to left
c) $1.5\ \text{mA}$, top to bottom
d) $18\ \text{V}$, positive at the top
- 3.23 a) $30\ \text{mV}$, positive on the left
b) $4.5\ \text{V}$, positive at the top
c) $0.4\ \text{A}$, bottom to top
- 3.31 a) $i_m = \frac{(10/99)}{10 + (10/99)} i_{\text{meas}} = \frac{1}{100} i_{\text{meas}}$
b) $\frac{1}{100,000}$
c) Yes
- 3.34 a) $49,980\ \Omega$
b) $4980\ \Omega$
c) $230\ \Omega$
d) $5\ \Omega$
- 3.49 a) $2000\ \Omega$
b) $8.4\ \text{mA}$
c) $800\ \Omega$; $28.8\ \text{mW}$
d) $500\ \Omega$; $2.88\ \text{mW}$
- 3.53 $v_1 = 23.2\ \text{V}$; $v_2 = 21.0\ \text{V}$
- 3.54 a) Equivalent wye is $5\ \Omega$, $20\ \Omega$, $4\ \Omega$; $R_{ab} = 33\ \Omega$.
b) Equivalent delta is $100\ \Omega$, $80\ \Omega$, $20\ \Omega$;
 $R_{ab} = 33\ \Omega$.
c) Convert R_4 – R_5 – R_6 delta to wye; convert
 R_3 – R_4 – R_6 wye to delta.
- 3.55 $90\ \Omega$
- 3.71 $R_1 = 1.0372\ \Omega$, $R_2 = 1.1435\ \Omega$, $R_3 = 1.2\ \Omega$,
 $R_4 = 1.1435\ \Omega$, $R_5 = 1.0372\ \Omega$, $R_a = 0.0259\ \Omega$,
 $R_b = 0.0068\ \Omega$, $R_c = 0.0068\ \Omega$, $R_d = 0.0259\ \Omega$
- 3.72 $P_{\text{diss}} = 624\ \text{W} = P_{\text{del}}$
- 3.73 a) $R_1 = 0.4269\ \Omega$, $R_2 = 0.4617\ \Omega$, $R_3 = 0.48\ \Omega$,
 $R_4 = 0.4617\ \Omega$, $R_5 = 0.4269\ \Omega$,
 $R_a = 0.0085\ \Omega$, $R_b = 0.0022\ \Omega$,
 $R_c = 0.0022\ \Omega$, $R_d = 0.0085\ \Omega$
b) $i_1 = 26.51\ \text{A}$, $i_1^2 R_1 = 300\ \text{W}$ or $200\ \text{W/m}$;
 $i_2 = 25.49\ \text{A}$, $i_2^2 R_2 = 300\ \text{W}$ or $200\ \text{W/m}$;
 $i_b = 52\ \text{A}$, $i_b^2 R_b = 6\ \text{W}$ or $200\ \text{W/m}$;
 $P_{\text{del}} = 1548\ \text{W} = P_{\text{diss}}$

Chapter 4

- 4.1 a) 11
b) 9
c) 9
d) 7
e) 6
f) 4
g) 6
- 4.2 a) 2
b) 5
c) 7
d) 1; 4; 7

- 4.3 a) 7
b) 3
c) 4
d) top mesh; leftmost mesh
- 4.4 a) 5
b) 3
c) $-i_g + i_{R_1} + i_{R_2} = 0$; $-i_{R_1} + i_{R_4} + i_{R_3} = 0$;
 $i_{R_5} - i_{R_2} - i_{R_3} = 0$
d) 2
e) $R_1 i_{R_1} + R_3 i_{R_3} - R_2 i_{R_2} = 0$;
 $R_3 i_{R_3} + R_5 i_{R_5} - R_4 i_{R_4} = 0$
- 4.6 -5 V
- 4.9 $v_1 = 120 \text{ V}$, $v_2 = 96 \text{ V}$
- 4.10 a) $i_a = 8 \text{ A}$, $i_b = 2 \text{ A}$, $i_c = 6 \text{ A}$, $i_d = 2 \text{ A}$,
 $i_e = 4 \text{ A}$
b) 360 W
- 4.19 750 W delivered
- 4.20 a) $P_{25\text{A}} = -8800 \text{ W}$; $P_{\text{dev}} = 8800 \text{ W}$
b) $P_{84i_\Delta} = 628.32 \text{ W}$, $P_{40\Omega} = 3097.6 \text{ W}$,
 $P_{160\Omega} = 774.4 \text{ W}$, $P_{10\Omega} = 1960 \text{ W}$,
 $P_{20\Omega} = 2247.2 \text{ W}$, $P_{8\Omega} = 92.48 \text{ W}$,
 $P_{\text{diss}} = 8800 \text{ W}$
- 4.21 10 V
- 4.26 $v_1 = -37.5 \text{ V}$, $P_{25\text{V}} = 31.25 \text{ W}$ delivered
- 4.27 25 V
- 4.31 a) $i_a = 5.6 \text{ A}$, $i_b = 3.2 \text{ A}$, $i_c = -2.4 \text{ A}$
b) $i_a = -8.8 \text{ A}$, $i_b = -1.6 \text{ A}$, $i_c = 7.2 \text{ A}$
- 4.32 a) $P_{230\text{V}} = -1012 \text{ W}$, $P_{460\text{V}} = -16,928 \text{ W}$,
 $P_{\text{dev}} = 17,940 \text{ W}$
b) $P_{\text{abs}} = 17,940 \text{ W}$
- 4.33 259.2 W
- 4.34 2016 W delivered
- 4.37 a) -312 W delivered (312 W absorbed)
b) $21,000 \text{ W}$
c) $P_{\text{dev}} = 21,000 \text{ W} = P_{\text{diss}}$
- 4.38 a) 2 mA
b) 304 mW delivered
c) 0.9 mW delivered
- 4.43 740 W
- 4.46 a) $i_a = -4.2 \text{ A}$, $i_b = 7.4 \text{ A}$, $i_c = 4.68 \text{ A}$,
 $i_d = 11.6 \text{ A}$, $i_e = 2.72 \text{ A}$
b) $P_{\text{dev}} = 1329.632 \text{ W} = P_{\text{abs}}$
- 4.52 a) Three unknown node voltages, but only two unknown mesh currents, so choose mesh current method.
b) 3.6 W
c) No, since it is straightforward to calculate the voltage drop across the current source from mesh currents.
d) 52.8 W delivered
- 4.54 a) Node-voltage method because constraint equations are easier to formulate.
b) 480 mW absorbed
- 4.55 a) -1 mA
b) -1 mA

- 4.58 a) -0.85 A
b) -0.85 A
- 4.59 $V_{\text{Th}} = 60\text{ V}$, $R_{\text{Th}} = 10\ \Omega$
- 4.62 $I_{\text{N}} = 1\text{ mA}$, top to bottom; $R_{\text{N}} = 3.75\text{ k}\Omega$
- 4.63 a) 51.3 V
b) -5%
- 4.65 $v_{\text{Th}} = 160\text{ V}$, negative at the top; $R_{\text{Th}} = 56.4\text{ k}\Omega$
- 4.72 $1.43\ \mu\text{A}$
- 4.75 $2.5\ \Omega$ and $22.5\ \Omega$
- 4.76 a) $6\ \Omega$
b) 24 W
- 4.87 a) 50 V
b) 250 W
- 4.88 30 V
- 4.101 $v_1 = 39.583\text{ V}$, $v_2 = 102.5\text{ V}$
- 4.102 $v_1 = 37.5\text{ V}$, $v_2 = 105\text{ V}$
- 4.103 $v_1 = 52.083\text{ V}$, $v_2 = 117.5\text{ V}$

Chapter 5


- 5.1 a)
-
- b) Input resistance is infinite, so $i_n = 0\text{ A}$
- c) Gain in the linear region is infinite, so $v_p - v_n = 0$
- d) -10 V
- 5.2 a) -15 V (saturated)
b) -10 V
c) -4 V
d) 7 V
e) $-1.08\text{ V} \leq v_a \leq 4.92\text{ V}$

- 5.3 -1 mA
- 5.6 a) Use a single $20\text{ k}\Omega$ resistor in the forward path and 6 series-connected $20\text{ k}\Omega$ resistors in the feedback path, OR, use 6 parallel-connected $20\text{ k}\Omega$ resistors in the forward path and a single $20\text{ k}\Omega$ resistor in the feedback path.
b) $\pm 18\text{ V}$
- 5.7 a) Non-inverting amplifier
b) 9 V
- 5.16 a) Inverting summing amplifier
b) -4 V
c) $-2.5\text{ V} \leq v_b \leq -1.3\text{ V}$
- 5.17 a) 14 V
b) $3.818\text{ V} \leq v_a \leq 9.273\text{ V}$
- 5.19 $R_a = 24\text{ k}\Omega$, $R_b = 12\text{ k}\Omega$, $R_c = 8\text{ k}\Omega$, $R_d = 6\text{ k}\Omega$
- 5.22 a) Non-inverting amplifier
b) $2v_s$
c) $-6\text{ V} \leq v_s \leq 4\text{ V}$
- 5.23 a) 10.54 V
b) $-4.554\text{ V} \leq v_g \leq 4.554\text{ V}$
c) $181.76\text{ k}\Omega$
- 5.29 $20\text{ k}\Omega$
- 5.30 a) 4.2 V
b) $-771\text{ mV} \leq v_c \leq 1371\text{ mV}$
- 5.31 a) -1.53 V
b) $33.5\text{ k}\Omega$
c) $80\text{ k}\Omega$
- 5.37 a) 24.98
b) -0.04
c) 624.5
- 5.38 $19.93\text{ k}\Omega \leq R_x \leq 20.07\text{ k}\Omega$
- 5.39 a) -19.9915 V
b) $403.2\ \mu\text{V}$
c) $5002.02\ \Omega$
d) $-20; 0\text{ V}; 5000\ \Omega$
- 5.48 a) $2\text{ k}\Omega$
b) $12\text{ m}\Omega$


Chapter 6

6.1 a) $i = 0 \quad t < 0$
 $i = 50t \text{ A} \quad 0 \leq t \leq 5 \text{ ms}$
 $i = 0.5 - 50t \text{ A} \quad 5 \text{ ms} \leq t \leq 10 \text{ ms}$
 $i = 0 \quad 10 \text{ ms} \leq t \leq \infty$

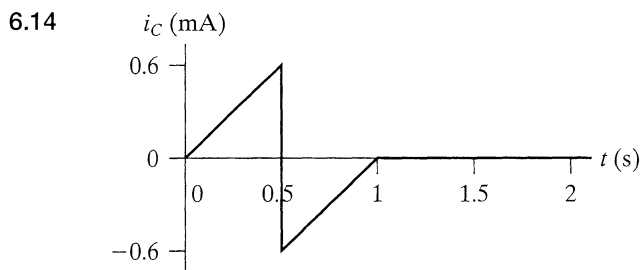b) $v = 0 \quad t < 0$
 $v = 1 \text{ V} \quad 0 \leq t \leq 5 \text{ ms}$
 $v = -1 \text{ V} \quad 5 \text{ ms} \leq t \leq 10 \text{ ms}$
 $v = 0 \quad 10 \text{ ms} \leq t \leq \infty$
 $p = 0 \quad t < 0$
 $p = 50t \text{ W} \quad 0 \leq t \leq 5 \text{ ms}$
 $p = 50t - 0.5 \text{ W} \quad 5 \text{ ms} \leq t \leq 10 \text{ ms}$
 $p = 0 \quad 10 \text{ ms} \leq t \leq \infty$
 $w = 0 \quad t < 0$
 $w = 25t^2 \text{ J} \quad 0 \leq t \leq 5 \text{ ms}$
 $w = 25t^2 - 0.5t + 0.0025 \text{ J} \quad 5 \text{ ms} \leq t \leq 10 \text{ ms}$
 $w = 0 \quad 10 \text{ ms} \leq t \leq \infty$



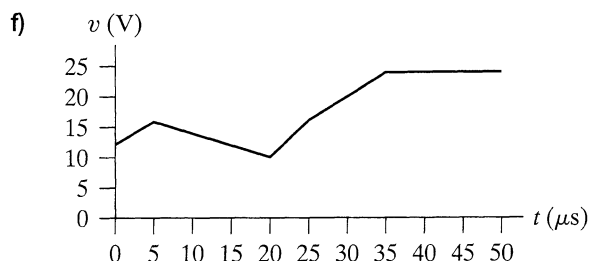6.15 a) $8 \times 10^5 t + 12 \text{ V}$
b) $-4 \times 10^5 t + 18 \text{ V}$
c) $12 \times 10^5 t - 14 \text{ V}$
d) $8 \times 10^5 t - 4 \text{ V}$
e) 24 V



6.21 15 H
6.22 a) $6e^{-t} \text{ A}$
b) $4e^{-t} - 2 \text{ A}$
c) $2e^{-t} + 2 \text{ A}$
d) 36 J
e) 54 J
f) 18 J
g) $54 \text{ J} - 36 \text{ J} = 18 \text{ J}$ (checks)
6.26 $2 \mu\text{F}$ with 25 V positive at the top
6.27 a) $10e^{-t} \text{ V}$
b) $6.67e^{-t} - 2.67 \text{ V}$
c) $3.33e^{-t} + 2.67 \text{ V}$
d) $100 \mu\text{J}$
e) $132 \mu\text{J}$
f) $32 \mu\text{J}$
g) $100 \mu\text{J} + 32 \mu\text{J} = 132 \mu\text{J}$ (checks)

6.34 a) $16 \frac{di_2}{dt} + 32i_2 = 2 \frac{di_g}{dt}$
b) $-16e^{-t} + 32e^{-2t} + 32e^{-t} - 32e^{-2t} = 16e^{-t}$
c) $34e^{-t} - 4e^{-2t} \text{ V}, \quad t \geq 0$
d) 30 V; yes

6.38 a) 50 mH; 2.4
b) $0.2 \times 10^{-6} \text{ Wb/A}$
6.39 0.8 nWb/A; 1.2 nWb/A
6.47 a) 2721.6 mJ
b) 2721.6 mJ
c) 518.4 mJ
d) 518.4 mJ

- 6.48 a) -4.5 A
b) no

6.49 $v = \frac{1}{3}v_s(t) + v(0)$

- 6.51 The finger causes no change in the output voltage.

Chapter 7

- 7.1 a) $i_1(0^-) = 5 \text{ mA}$, $i_2(0^-) = 15 \text{ mA}$
b) $i_1(0^+) = 5 \text{ mA}$, $i_2(0^+) = -5 \text{ mA}$
c) $5e^{-20,000t} \text{ mA}$
d) $-5e^{-20,000t} \text{ mA}$
e) The current in a resistor can change instantaneously.
- 7.2 a) 4 A
b) 80 ms
c) $i = 4e^{-12.5t} \text{ A}$, $t \geq 0$; $v_1 = -180e^{-12.5t} \text{ V}$, $t \geq 0^+$; $v_2 = -200e^{-12.5t} \text{ V}$, $t \geq 0^+$
d) 56.89%
- 7.3 a) 0
b) 160 mA
c) 65 mA
d) 160 mA
e) 225 mA
f) 0
g) $160e^{-200t} \text{ mA}$, $t \geq 0$
h) 0
i) -3.2 V
j) 0
k) $-3.2e^{-200t} \text{ V}$, $t \geq 0^+$
l) $225 - 160e^{-200t} \text{ mA}$, $t \geq 0^+$
- 7.21 a) $i = 1.6e^{-50t} \text{ mA}$, $t \geq 0^+$, $v_1 = 32e^{-50t} + 8 \text{ V}$, $t \geq 0$, $v_2 = -8e^{-50t} + 8 \text{ V}$, $t \geq 0$
b) $800 \mu\text{J}$
c) $w_{\text{trapped}} = 160 \mu\text{J}$, $w_{\text{diss}} = 640 \mu\text{J}$
- 7.22 a) $9.9e^{-1000t} \text{ mA}$
b) 42.14%

7.33 a) $i_L(t) = -2 - 3e^{-5000t} \text{ A}$, $t \geq 0$;
 $v_o(t) = 48 - 48e^{-5000t} \text{ V}$, $t \geq 0$

b) $v_L(0^+) = 60 \text{ V}$, $v_o(0^+) = 0 \text{ V}$

7.34 a) $5 + 15e^{-1000t} \text{ A}$, $t \geq 0$

b) $50 - 450e^{-1000t} \text{ V}$, $t \geq 0^+$

7.35 $i_o(t) = 2.5 + 7.5e^{-1250t} \text{ A}$, $t \geq 0$;
 $v(t) = -150e^{-1250t} \text{ V}$, $t \geq 0$

7.47 $-60 + 90e^{-2000t} \text{ V}$, $t \geq 0$

7.48 a) $60 - 60e^{-100t} \text{ V}$, $t \geq 0$

b) $1 - 0.6e^{-100t} \text{ mA}$, $t \geq 0^+$

c) $1 + 2.4e^{-100t} \text{ mA}$, $t \geq 0^+$

d) $4 - 2.4e^{-100t} \text{ mA}$, $t \geq 0^+$

e) 3.4 mA

7.61 a) 50 V

b) -24 V

c) $0.1 \mu\text{s}$

d) -18.5 A

e) $-24 + 74e^{-10^7t} \text{ V}$, $t \geq 0$

f) $-18.5e^{-10^7t} \text{ A}$, $t \geq 0^+$

7.62 a) 90 V

b) -60 V

c) $1000 \mu\text{s}$

d) $916.3 \mu\text{s}$

7.63 a) -13 mA

b) -12 mA

c) $80 \mu\text{s}$

d) $-12 - e^{-12,500t} \text{ mA}$, $t \geq 0$

7.64 a) $6 - 6e^{-10t} \text{ A}$, $t \geq 0$

b) $100e^{-10t} \text{ V}$, $t \geq 0$

c) $7 - 7e^{-10t} \text{ A}$, $t \geq 0$

d) $-1 + e^{-10t} \text{ A}$, $t \geq 0$

e) Yes, check initial conditions and final values.

- 7.66 a) $4 - 4e^{-20t}$ A, $t \geq 0$
 b) $80e^{-20t}$ V, $t \geq 0^+$
 c) $2.4 - 2.4e^{-20t}$ A, $t \geq 0$
 d) $1.6 - 1.6e^{-20t}$ A, $t \geq 0$
 e) Yes, check initial conditions and final values.
- 7.69 $-100 + 130e^{-200t}$ V, $t \geq 0$
- 7.70 a) 7.5 A
 b) 6.14 A
 c) 226.48 mA
 d) -220.73 V
 e) -110.4 V
- 7.84 a) 2.25
 b) $272.1 \mu\text{s}$
- 7.85 83.09 ms
- 7.89 80 ms
- 7.90 $v_o = 8 - 1600t$ V, $0 \leq t \leq t_{\text{sat}}$;
 $v_2 = 11e^{-200t} - 15$ V, $0 \leq t \leq t_{\text{sat}}$;
 $v_f = 23 - 1600t - 11e^{-200t}$ V, $0 \leq t \leq t_{\text{sat}}$
- 7.103 a) $1.091 \text{ M}\Omega$
 b) 0.29 s
- 7.104 a) 8.55 flashes/min
 b) 559.3 k Ω
- 7.105 a) 24.3 flashes/min
 b) 99.06 mA
 c) \$43.39 per year
- Chapter 8**
- 8.1 a) -100 rad/s, -400 rad/s
 b) overdamped
 c) 1562.5Ω
 d) $-160 + j120$ rad/s, $-160 - j120$ rad/s
 e) 1250Ω
- 8.2 a) $R = 8 \text{ k}\Omega$, $L = 40 \text{ H}$, $\alpha = 625$ rad/s,
 $\omega_0 = 500$ rad/s
 b) $i_R(t) = 4e^{-1000t} - e^{-250t}$ mA, $t \geq 0^+$;
 $i_C(t) = 0.2e^{-250t} - 3.2e^{-1000t}$ mA, $t \geq 0^+$;
 $i_L(t) = 0.8e^{-250t} - 0.8e^{-1000t}$ mA, $t \geq 0^+$
- 8.7 a) 40 mH
 b) 625Ω
 c) 100 V
 d) 40 mA
 e) $e^{-20,000t}(40 \cos 15,000t + 220 \sin 15,000t)$ mA,
 $t \geq 0$
- 8.8 a) $\alpha = 500$ rad/s, $\omega_0 = 400$ rad/s,
 $L = 1.5625 \text{ H}$, $C = 4 \mu\text{F}$, $A_1 = -31$ mA,
 $A_2 = 76$ mA
 b) $38.75e^{-200t} - 23.75e^{-800t}$ V, $t \geq 0$
 c) $155e^{-200t} - 95e^{-800t}$ mA, $t \geq 0^+$
 d) $-124e^{-200t} + 19e^{-800t}$ mA, $t \geq 0$
- 8.9 a) $R = 1 \text{ k}\Omega$, $C = 1 \mu\text{F}$, $D_1 = 6000$ V/s,
 $D_2 = 8$ V
 b) $(-3000t + 2)e^{-500t}$ mA, $t \geq 0^+$
- 8.16 $5e^{-2000t} + 10e^{-8000t}$ V, $t \geq 0$
- 8.17 $15e^{-2000t} \cos 3122.5t + 4.8e^{-2000t} \sin 3122.5t$ V,
 $t \geq 0$
- 8.18 $15e^{-4000t}$ V, $t \geq 0$
- 8.24 $60 - 120e^{-5000t} + 15e^{-20,000t}$ mA, $t \geq 0$
- 8.25 $60 - 105e^{-8000t} \cos 6000t - 90e^{-8000t} \sin 6000t$ mA,
 $t \geq 0$
- 8.26 $60 - 750,000te^{-10,000t} - 105e^{-10,000t}$ mA, $t \geq 0$
- 8.40 $-2.4e^{-4t} \cos 3t - 3.2e^{-4t} \sin 3t$ A, $t \geq 0^+$
- 8.42 a) $10,000te^{-10^5t} + 0.1e^{-10^5t}$ A, $t \geq 0$
 b) $25 \times 10^5te^{-10^5t} + 50e^{-10^5t}$ V, $t \geq 0$
- 8.46 a) 24 V
 b) $-53,248$ V/s
 c) $-40 - 25.6e^{-160t} + 89.6e^{-640t}$ V, $t \geq 0^+$
- 8.51 a) $v_o = 10t^2$ V, $0 \leq t \leq 0.5^-$ s;
 $v_o = -5t^2 + 15t - 3.75$ V, $0.5^+ \text{ s} \leq t \leq t_{\text{sat}}$;
 $v_{o1} = -1.6t$ V, $0 \leq t \leq 0.5^-$ s;
 $v_{o1} = 0.8t - 1.2$ V, $0.5^+ \text{ s} \leq t \leq t_{\text{sat}}$
 b) 3.5 s

8.52 $v_o = 10 - 20e^{-t} + 10e^{-2t}$ V, $0 \leq t \leq 0.5$ s;
 $v_o = -5 + 19.42e^{-(t-0.5)} - 12.87e^{-2(t-0.5)}$ V,
 $0.5 \leq t \leq \infty$; $v_{o1} = -0.8 + 0.8e^{-2t}$ V,
 $0 \leq t \leq 0.5$ s; $v_{o1} = 0.4 - 0.91e^{-2(t-0.5)}$ V,
 $0.5 \leq t \leq \infty$

8.60 a) $55.23 \mu\text{s}$

b) 262.42 V

c) $t_{\max} = 53.63 \mu\text{s}$, $v(t_{\max}) = 262.15$ V

8.61 a) 40 mJ

b) $-27,808.04$ V

c) 568.15 V

Chapter 9

9.1 a) 600 Hz

b) 1.67 ms

c) 10 V

d) 6 V

e) -53.13° or -0.9273 rad

f) $662.64 \mu\text{s}$

g) $245.97 \mu\text{s}$

9.2 $\frac{V_m}{2}$

9.3 a) 40 V

b) 50 Hz

c) 314.159 rad/s

d) 1.05 rad

e) 60°

f) 20 ms

g) 6.67 ms

h) $40 \cos 100\pi t$ V

i) 8.33 ms

j) 16.67 ms

9.9 a) $-195.72e^{-1066.67t} + 200 \cos(800t - 11.87^\circ)$ mA

b) $-195.72e^{-1066.67t}$ mA,
 $200 \cos(800t - 11.87^\circ)$ mA

c) 28.39 mA

d) 0.2 A, 800 rad/s, -11.87°

e) 36.87°

9.12 a) 1000 Hz

b) 0°

c) -90°

d) 8Ω

e) 1.27 mH

f) $j8 \Omega$

9.13 a) $314,159.27$ rad/s


b) 90°

c) -15.92Ω

d) $0.2 \mu\text{F}$

e) $-j15.92 \Omega$


9.14 a)

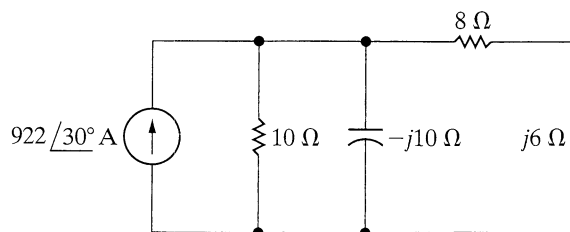

b) $5000.25 \angle 17.47^\circ$ V

c) $5000.25 \cos(2 \times 10^4 t + 17.47^\circ)$ V

9.15 a)

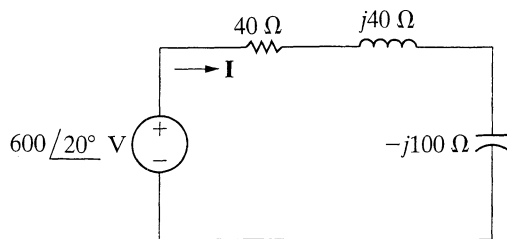

b) $8.32 \angle 76.31^\circ \text{ A}$

c) $8.32 \cos(8000t + 76.31^\circ) \text{ A}$

9.16 $17.68 \cos(50t - 135^\circ) \text{ mA}$

9.17 a) $200 \angle 36.87^\circ \text{ mS}$

b) 160 mS

c) 120 mS

d) 10 A

9.18 $42.43 \cos(2000t + 45^\circ) \text{ V}$

9.19 a) $50 \angle 45^\circ \Omega$

b) $50 \mu\text{s}$

9.20 $42.43 \cos(50,000t + 45^\circ) \text{ V}$

9.35 0.667Ω

9.39 $10 \cos 200t \text{ mV}$

9.42 $227.68 \angle -18.43^\circ \text{ V}$, positive at the top;
 $3.6 + j10.8 \Omega$

9.43 $2.2 \angle 0^\circ \text{ A}$, flowing top to bottom; $30 - j40 \Omega$

9.51 $188.43 \angle -42.88^\circ \text{ V}$

9.54 $36 \cos 2000t \text{ V}$

9.56 $j80 \text{ V} = 80 \angle 90^\circ \text{ V}$

9.59 $4 - j2 \text{ A} = 4.47 \angle -26.57^\circ \text{ A}$

9.66 a) $i_g = 5 \cos(5000t - 36.87^\circ) \text{ A}$,
 $i_L = \cos(5000t - 180^\circ) \text{ A}$

b) 0.5

c) $9.0 \text{ mJ}, 12 \text{ mJ}$


9.67 $850 + j850 \text{ V}$, positive at the top; $85 + j85 \Omega$

9.71 $512 \angle 60^\circ \text{ k}\Omega$

9.75 a) $247.11 \angle 1.68^\circ \text{ V}$

b) $-32 \Omega, 241.13 \angle 1.90^\circ \text{ V}$

c) -26.90Ω

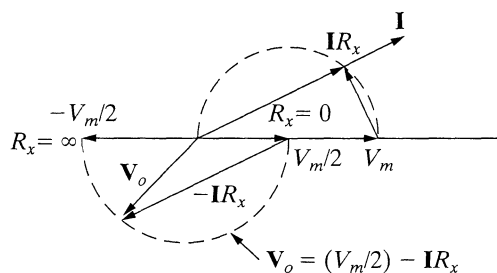9.76 As R_x varies from 0 to ∞ , the amplitude of v_o remains constant and its phase angle changes from 0 to -180° .

9.85 a) $\mathbf{I}_1 = 24 \angle 0^\circ \text{ A}$, $\mathbf{I}_2 = 2.04 \angle 0^\circ \text{ A}$,
 $\mathbf{I}_3 = 21.96 \angle 0^\circ \text{ A}$, $\mathbf{I}_4 = 19.40 \angle 0^\circ \text{ A}$,
 $\mathbf{I}_5 = 4.6 \angle 0^\circ \text{ A}$, $\mathbf{I}_6 = 2.55 \angle 0^\circ \text{ A}$

b) $0.42 \angle 0^\circ \text{ A}$

9.86 a) 0 A

b) 0.436 A

c) When the two loads are equal, more current is drawn from the primary.

Chapter 10

10.1 a) $P = 409.58 \text{ W (abs)}$;
 $Q = 286.79 \text{ VAR (abs)}$

b) $P = 103.53 \text{ W (abs)}$;
 $Q = -386.37 \text{ VAR (del)}$

c) $P = -1000 \text{ W (del)}$;
 $Q = -1732.05 \text{ VAR (del)}$

d) $P = -250 \text{ W (del)}$;
 $Q = 433.01 \text{ VAR (abs)}$

- 13.49 a) $\frac{200}{s+200}$ pole at -200 rad/s
 b) $\frac{s}{s+200}$ zero at 0, pole at -200 rad/s
 c) $\frac{s}{s+8000}$ zero at 0, pole at -8000 rad/s
 d) $\frac{8000}{s+8000}$ pole at -8000 rad/s
 e) $\frac{100}{s+500}$ pole at -500 rad/s

13.57 $1 - e^{-t}$ V, $0 \leq t \leq 1$; $(e-1)e^{-t}$ V, $1 \leq t \leq \infty$

13.58 e^{-t} V, $0 \leq t \leq 1$; $(1-e)e^{-t}$ V, $1 \leq t \leq \infty$

13.76 $16.97 \cos(3t + 8.13^\circ)$ V

13.77 a) $\frac{-10^4 s}{(s+400)(s+1000)}$
 b) $13.13 \cos(400t - 156.8^\circ)$ V

- 13.83 a) 80 V
 b) 20 V
 c) 0 V
 d) $32\delta(t)$ μ A
 e) 16 V
 f) 4 V
 g) 20 V


- 13.84 a) 0.8 A
 b) 0.6 A
 c) 0.2 A
 d) -0.6 A
 e) $0.6e^{-2 \times 10^6 t} u(t)$ A
 f) $-0.6e^{-2 \times 10^6 t} u(t)$ A
 g) $-1.6 \times 10^{-3} \delta(t) - 7200e^{-2 \times 10^6 t} u(t)$ V

- 13.89 a) $i_2(0^-) = i_2(0^+) = 0$ A;
 $i_L(0^-) = i_L(0^+) = 35.36$ A
 b) $V_0 =$

$$\frac{1440\pi(122.92\sqrt{2}s - 3000\pi\sqrt{2})}{(s+1475\pi)(s^2+14,400\pi^2)} + \frac{300\sqrt{2}}{s+1475\pi};$$
 $v_0(t) =$
 $252.89e^{-1475\pi t} + 172.62 \cos(120\pi t + 6.85^\circ)$ V;
 $v_0(0^+) = 424.26$ V


c) $V_0 = 122.06 \angle 6.85^\circ$ V (rms)

d)

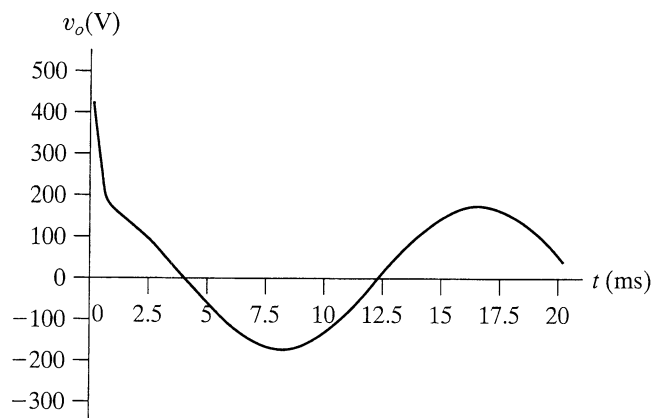

13.90 a) $-20.58e^{-1475\pi t} + 172.62 \cos(120\pi t - 83.15^\circ)$ V

b)

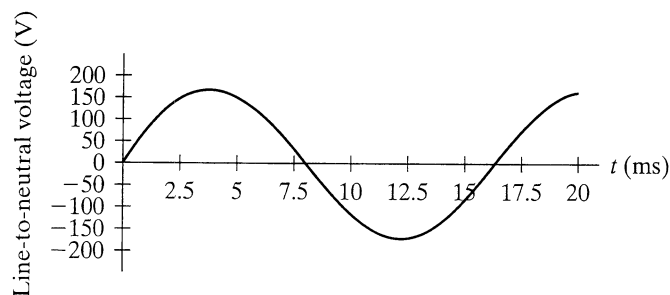

c) Voltage spikes in Problem 13.89 but not here

Chapter 14

14.1 a) 2021.27 Hz

b) $H(j\omega_c) = 0.71 \angle -45^\circ$;
 $H(j0.2\omega_c) = 0.98 \angle -11.31^\circ$;
 $H(j5\omega_c) = 0.2 \angle -78.69^\circ$

c) $v_o(\omega_c) = 7.07 \cos(12,700t - 45^\circ)$ V;
 $v_o(0.2\omega_c) = 9.81 \cos(2540t - 11.31^\circ)$ V;
 $v_o(5\omega_c) = 1.96 \cos(63,500t - 78.69^\circ)$ V

- 14.2 a) 31.42Ω
b) 895.77 Hz

- 14.9 a) $5.31 \text{ k}\Omega$
b) 333.86 Hz

- 14.10 a) 125Ω
b) $3 \text{ k}\Omega$

- 14.15 a) 100 krad/s
b) 15.92 kHz
c) 8
d) 93.95 krad/s
e) 14.96 kHz
f) 106.45 krad/s
g) 16.94 kHz
h) 12.5 krad/s or 1.99 kHz

- 14.16 a) $R = 5 \text{ k}\Omega$, $L = 50 \text{ mH}$
b) $f_{c1} = 2.88 \text{ kHz}$, $f_{c2} = 3.52 \text{ kHz}$
c) 636.62 Hz

- 14.24 a) 1 Mrad/s
b) 159.15 kHz
c) 15
d) 967.22 krad/s
e) 153.94 kHz
f) 1.03 Mrad/s
g) 164.55 kHz
h) 10.61 kHz


- 14.25 a) $R = 397.89 \Omega$, $L = 3.17 \text{ mH}$
b) $f_{c1} = 3.62 \text{ kHz}$, $f_{c2} = 4.42 \text{ kHz}$
c) 800 Hz

- 14.31 a) $L = 0.39 \text{ H}$, $C = 0.1 \mu\text{F}$
b) $0.948|V_{\text{peak}}|$
c) $0.344|V_{\text{peak}}|$


- 14.32 $L = 0.225 \text{ H}$, $C = 0.057 \mu\text{F}$, $0.344|V_{\text{peak}}|$

Chapter 15

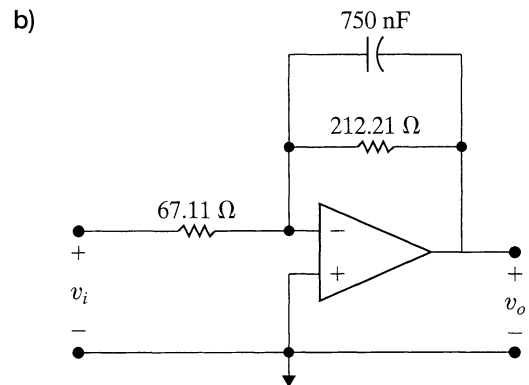- 15.4 a) $R_1 = 67.11 \Omega$, $R_2 = 212.21 \Omega$




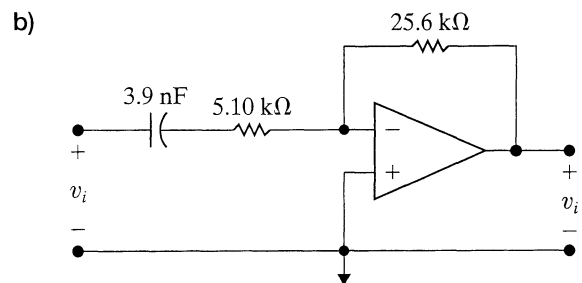- 15.5 a) $R_1 = 5.10 \text{ k}\Omega$, $R_2 = 25.6 \text{ k}\Omega$



- 15.9 a) $R = 0.05 \Omega$, $L = 1 \text{ H}$, $C = 1 \text{ F}$

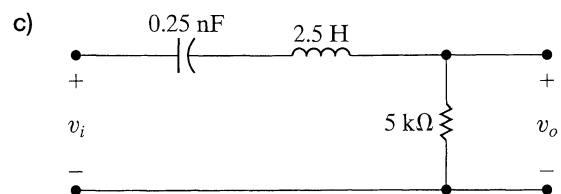
- b) $R = 5 \text{ k}\Omega$, $L = 2.5 \text{ H}$, $C = 0.25 \text{ nF}$



15.10 a) $1/Q$

b) $\frac{s/Q}{s^2 + s/Q + 1}$

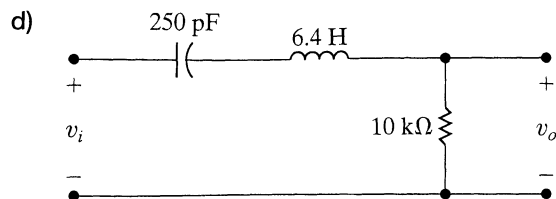c) $R = 10 \text{ k}\Omega$, $L = 6.4 \text{ H}$, $C = 250 \text{ pF}$



e) $\frac{1562.5s}{s^2 + 1562.5s + 625 \times 10^6}$


15.25 $f_{c1} = 38.52 \text{ Hz}$, $f_{c2} = 1038.52 \text{ Hz}$, $R_L = 30.65 \Omega$,
 $R_H = 826.43 \Omega$

15.26 $R_L = 21.18 \text{ k}\Omega$, $R_H = 1.18 \text{ k}\Omega$, $\frac{R_f}{R_i} = 6$


15.28 a) 3

b) -32.65 dB

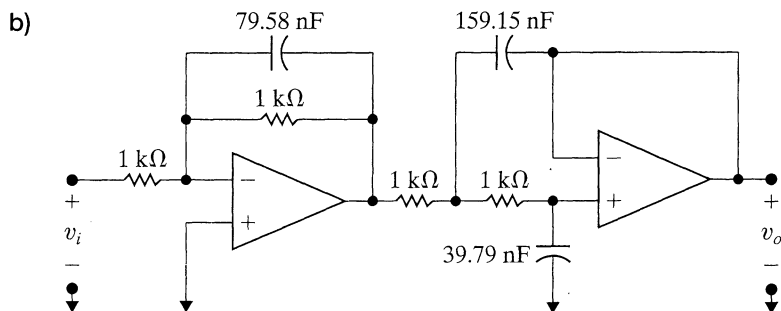
15.31 a) First-order circuit: $R = 1 \text{ k}\Omega$, $C = 79.58 \text{ nF}$
Second-order circuit: $R = 1 \text{ k}\Omega$,
 $C_1 = 159.15 \text{ nF}$, $C_2 = 39.79 \text{ nF}$



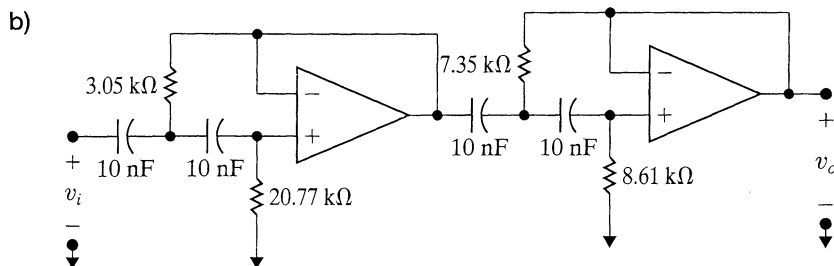15.32 a) First section: $R_1 = 3.05 \text{ k}\Omega$, $R_2 = 20.77 \text{ k}\Omega$
Second section: $R_1 = 7.35 \text{ k}\Omega$, $R_2 = 8.61 \text{ k}\Omega$



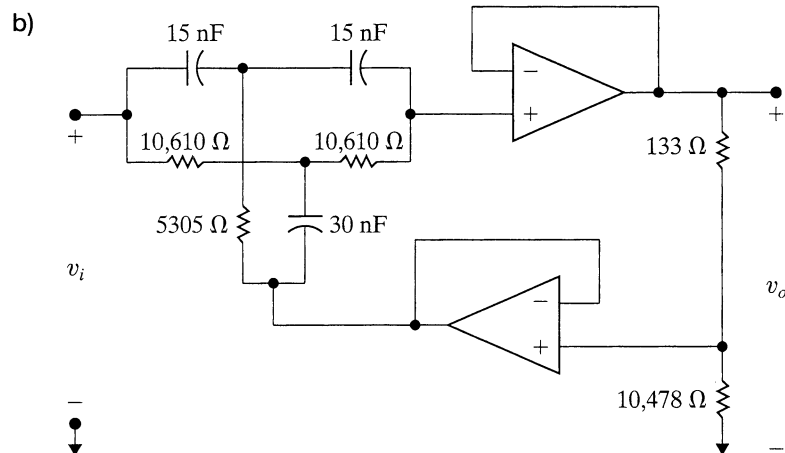- 15.53 a) $R = 10,610 \Omega$; $\sigma R = 10,478 \Omega$;
 $(1 - \sigma)R = 133 \Omega$



c)
$$\frac{s^2 + 4 \times 10^6 \pi^2}{s^2 + 100\pi s + 4 \times 10^6 \pi^2}$$

- 15.54 $C = 39.79 \text{ nF}$, $|H(j\omega)|_{\max} = 20.01 \text{ dB}$,
 $|H(j/R_2 C_1)| = 17.04 \text{ dB}$

- 15.55 Choose $R_1 = 100 \text{ k}\Omega$, then $R_2 = 400 \text{ k}\Omega$,
 $C_1 = 7.96 \text{ nF}$.

Chapter 16

- 16.1 a) $\omega_{oa} = 31,415.93 \text{ rad/s}$, $\omega_{ob} = 3978.87 \text{ rad/s}$

b) $f_{oa} = 5 \text{ kHz}$, $f_{ob} = 25 \text{ kHz}$

c) $a_{va} = 0$, $a_{vb} = 25 \text{ V}$

d) $a_{va} = 0$; $a_{ka} = 0$ for k even;

$$a_{ka} = \frac{-80}{\pi k} \sin \frac{\pi k}{2} \text{ for } k \text{ odd};$$

$$b_{ka} = 0 \text{ for } k \text{ even}; b_{ka} = \frac{240}{\pi k} \text{ for } k \text{ odd};$$

$$a_{ab} = 25; a_{kb} = \frac{200}{\pi k} \sin \frac{\pi k}{4} \text{ for all } k;$$

$$b_{kb} = 0 \text{ for all } k$$

e)
$$v_a(t) = \frac{80}{\pi} \sum_{n=1,3,5,\dots}^{\infty} -\frac{1}{n} \sin \frac{\pi n}{2} \cos n\omega_o t + \frac{3}{n} \sin n\omega_o t \text{ V};$$

$$v_b(t) = 25 + \frac{200}{\pi} \sum_{n=1}^{\infty} \frac{1}{n} \sin \frac{n\pi}{4} \cos n\omega_o t \text{ V}$$