

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

1. (10 points) Using superposition




a. find the contribution to v from the 4A current source

$V_{4A} = \underline{10.43}$ volts


b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.23}$ volts



8
10

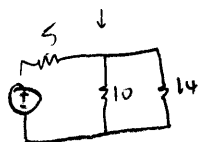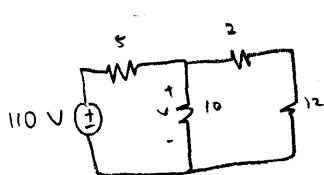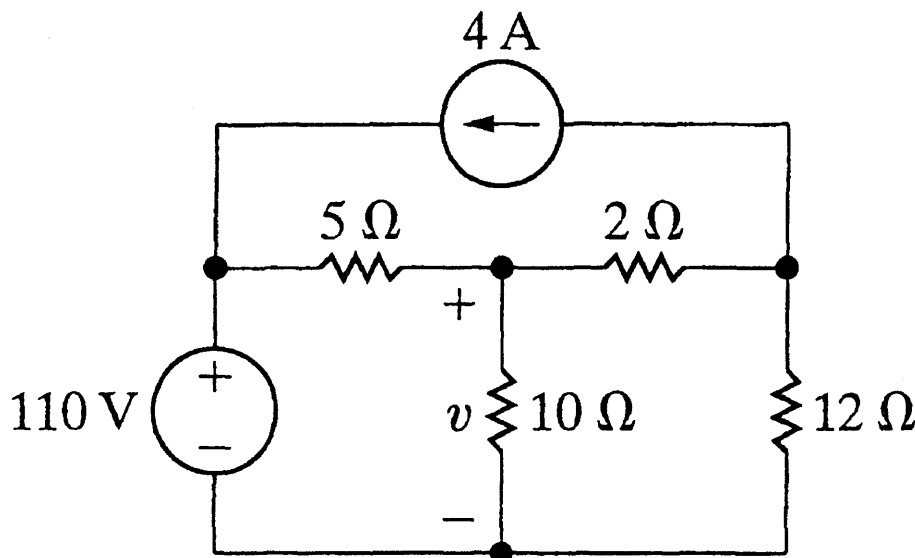
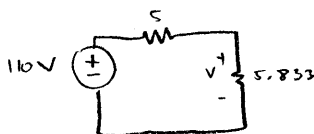
$$R_{eq} = \frac{14(10)}{14+10} = 5.833 \Omega$$


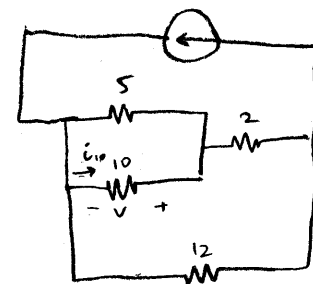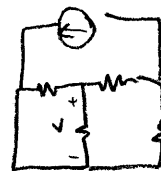
$$V = \frac{5.833}{5+5.833} (110V) = 59.23 V$$



$$i_{10} = \frac{1/10}{1/10 + 1/5 + 1/12} (4A) = 1.043 A$$

$$V = i_{10} R = (1.043 A)(10 \Omega) = 10.43 V$$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

mesh 1 $i_1 = 5 \text{ mA}$ ✓

mesh 2 $-(40 \text{ V}) + (i_2 - i_1)(2000 \Omega) + (i_2 - i_3)4000 \Omega = 0$
 $-40 + (i_2 - (5 \times 10^{-3}))(2000) + (i_2 - i_3)4000 = 0$
 $6000i_2 - 4000i_3 = 50$ ✓

mesh 3 $+(i_3 - i_2)(4000 \Omega) + i_3(8000 \Omega) - 20 = 0$
 $4000i_3 + 4000i_2 = 20$

use passive sign convention.



(c) Solve your equations for v_x and i_x .

$v_x = \underline{36 \text{ V}}$
 $i_x = \underline{0.002 \text{ A}}$

$6000i_2 - 4000i_3 = 50$ ①

$4000i_2 + 4000i_3 = 20$ ②


① + ② $10000i_2 = 70$

$i_2 = 7 \text{ mA}$

$6000(0.007) - 4000i_3 = 50$

$i_3 = -2 \text{ mA}$

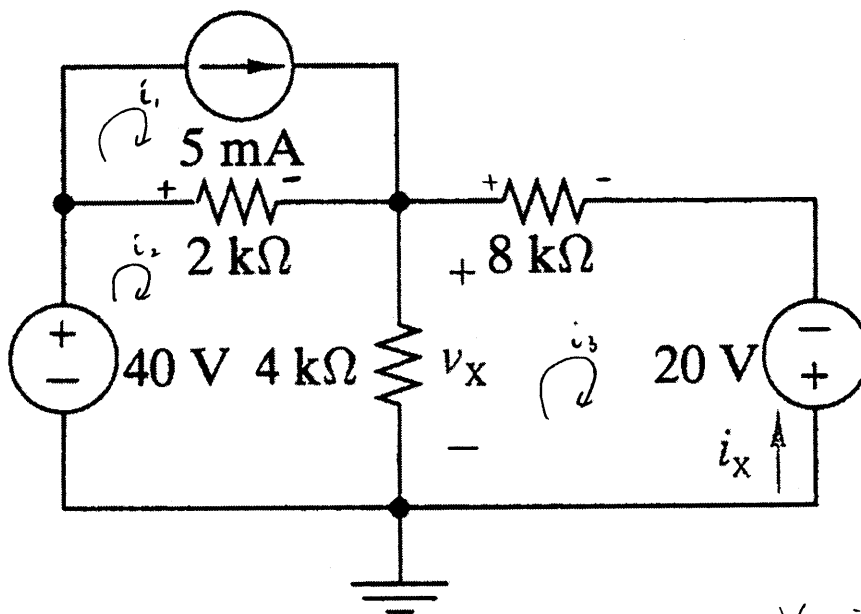$i_x = -i_3$
 $= -(-0.002 \text{ A})$
 $= 0.002 \text{ A}$



$v_x = (i_2 - i_3)(4000 \Omega)$
 $= [7 \text{ mA} - (-2 \text{ mA})](4000 \Omega)$
 $= 36 \text{ V}$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

1. (10 points) Using superposition


a. find the contribution to v from the 4A current source

$V_{4A} = \underline{4.53}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{37.93}$ volts


6

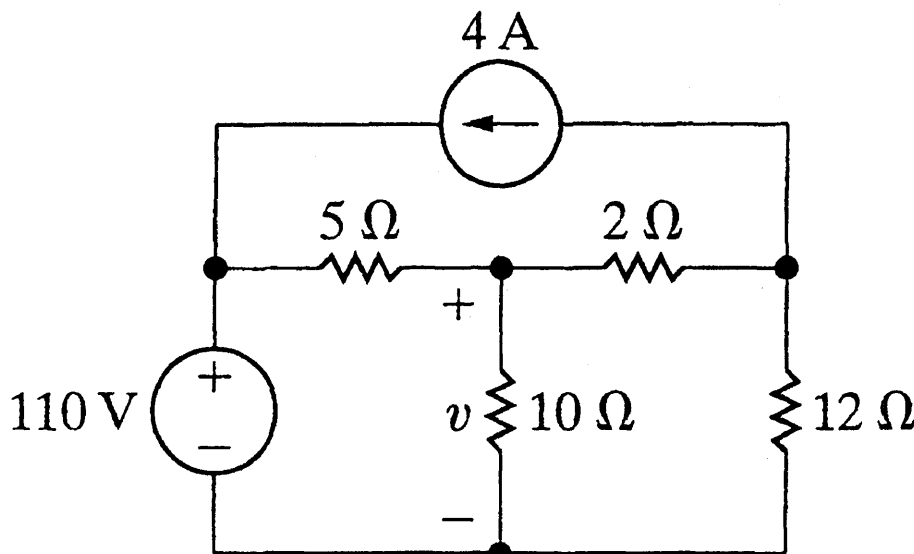

$V_{110V} = \text{OFF}$


$I_S = \text{OFF}$
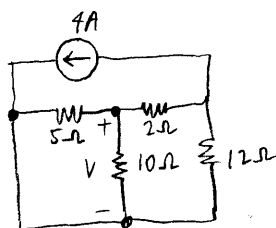
$$V_{110V} = \frac{10\Omega}{(5+2+12+10)\Omega} V_S$$




$$\bar{I} = \frac{110V}{5\Omega} = 22A$$
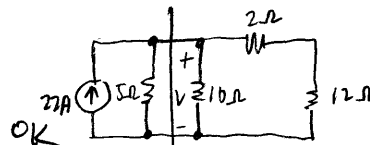
$$V_{110V} = \frac{10\Omega(110V)}{5\Omega + 2\Omega + 12\Omega + 10\Omega}$$




$$V_S = 110V = \underline{37.93V}$$

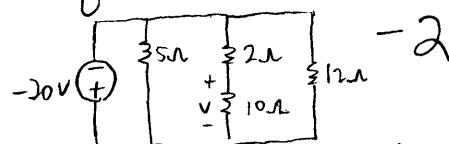You cannot do this type of source transform on this circuit



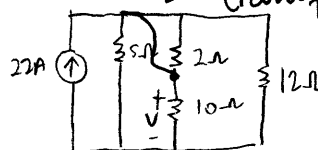You cannot transform the circuit and reconnect the 5Ω to a different location



$$\bar{I}_{4A} = \frac{\frac{1}{10}}{\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{1}{12}} (4A)$$

$$V_{4A} = (10\Omega)(0.4528A) = 4.528V$$

$$\bar{I}_{4A} = 0.4528A$$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

These equations don't make any sense. mesh current means KVL what is $\frac{i}{R}$?

$$\bar{i}_1: \bar{i}_1 + \frac{\bar{i}_1 - \bar{i}_3}{2k\Omega} + \frac{\bar{i}_1 - \bar{i}_2}{4k\Omega} = 0 \rightarrow 8\bar{i}_1 + 4\bar{i}_1 - 4\bar{i}_3 + 2\bar{i}_1 - 2\bar{i}_2 = 0$$

$$\bar{i}_3: 5mA - \frac{\bar{i}_3 - \bar{i}_1}{2k\Omega} = 0 \rightarrow 10 - \bar{i}_3 - \bar{i}_1 = 0$$

$$\bar{i}_2: -\frac{\bar{i}_2 - \bar{i}_1}{4k\Omega} - \bar{i}_x = 0$$

$$- \bar{i}_2 + \bar{i}_1 - 4000\bar{i}_x = 0$$

$$\bar{i}_1 = 4000\bar{i}_x + \bar{i}_2$$

$$14\bar{i}_1 - 2\bar{i}_2 - 4\bar{i}_3 = 0$$

$$7\bar{i}_1 - \bar{i}_2 - 2\bar{i}_3 = 0$$

$$\bar{i}_3 = 10 - \bar{i}_1$$

$$\bar{i}_2 = 7\bar{i}_1 - 2\bar{i}_3$$

$$\frac{1}{10}$$

(c) Solve your equations for v_x and i_x .


$$v_x = \underline{8.57V}$$

$$i_x = \underline{2.14A}$$

$$\bar{i}_1 = 4000\bar{i}_x + 7\bar{i}_1 - 2\bar{i}_3$$


$$\bar{i}_1 = 4000\bar{i}_x + 7\bar{i}_1 - 20 + 2\bar{i}_1$$

$$-8\bar{i}_1 = 4000\bar{i}_x - 20$$


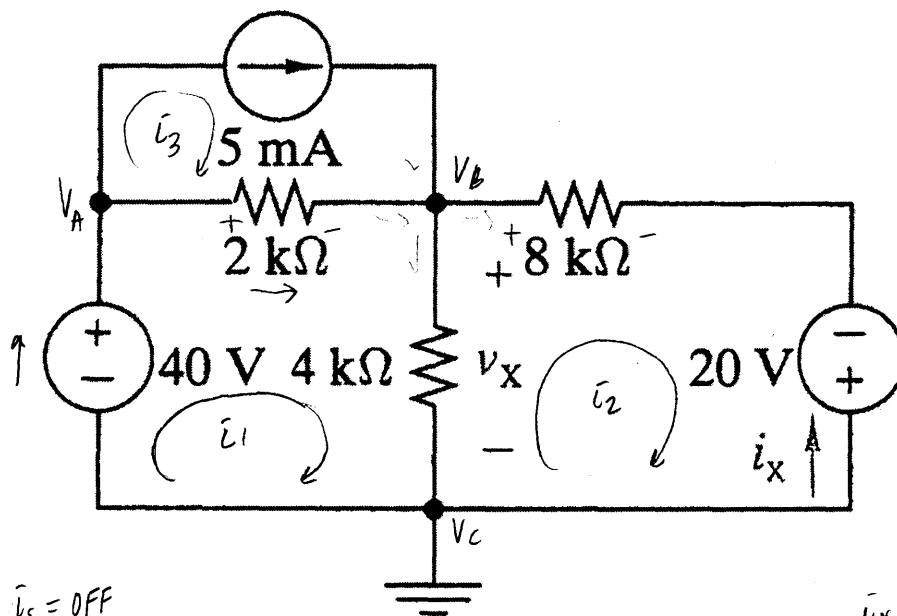


$\bar{i}_5 = OFF$
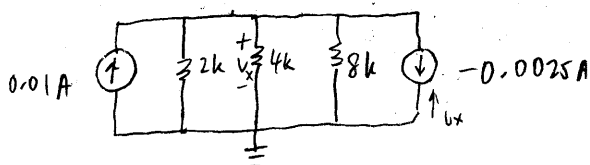
$$\bar{i}_x = \frac{v_x}{4k\Omega} = \frac{8.571V}{4k\Omega} =$$


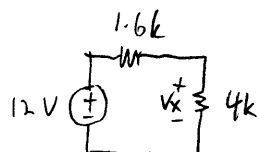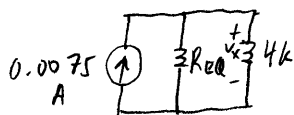
$$R_{eq} = \frac{8k(2k)}{8k + 2k} = 1600\Omega$$



$$V_{12V} = v_x = \frac{4k(12V)}{1.6k + 4k} = 8.571V$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

1. (10 points) Using superposition


a. find the contribution to v from the 4A current source

$V_{4A} = \underline{-9.23V}$ volts
sign


b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{-41.25V}$ volts

9.5
10.

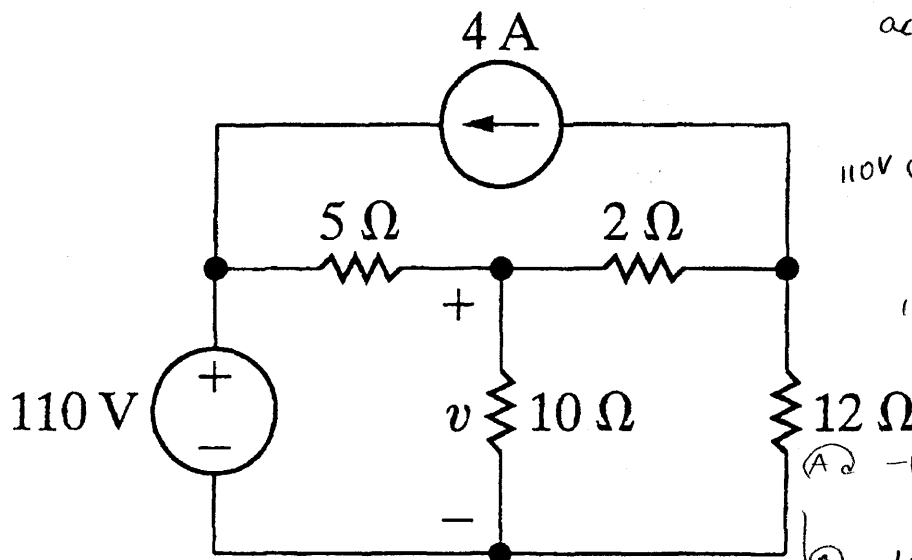

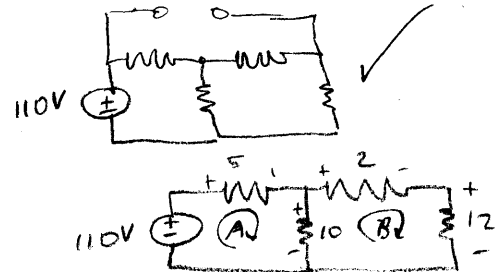(b) turn off current source → acts as open



① $-110 + 5i_A + 10i_A - 10i_B = 0$

② $+10i_B + 10i_A + 2i_B + 12i_B = 0$

sign errors $4i_B + 10i_A = 0$

$2i_B + 5i_A = 0$

$i_B = -\frac{5i_A}{2}$

$15i_A - 10i_B = 110$

$15i_A - 10(-\frac{5}{2}i_A) = 110$

$15i_A + 25i_A = 110$


$40i_A = 110$

$i_A = 2.75A$

$i_B = -6.875A$

$v = 10i_A - 10i_B = -41.25V$

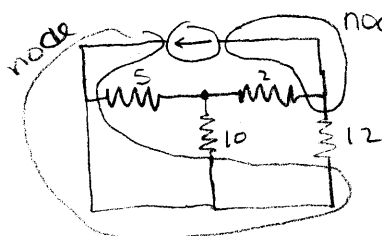(a) turn off voltage source → acts as short



current through 1

$i = \frac{R_2}{R_1 + R_2} i_s$
 $= \frac{12\Omega}{5\Omega + 12\Omega} (4A)$

$= 2.77A$

current through $R_{5,10}$ & R_2 same



$V_{5,10} = iR_{5,10}$
 $= 2.77(\frac{1}{5} + \frac{1}{10})$

$V_{5,10} = 9.23V$

v through $5 \parallel 10 \Omega$ is same

can all be made R_{eq}

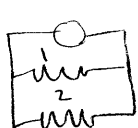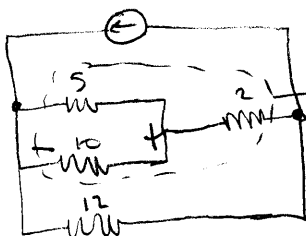$R_{eq} = \frac{1}{\frac{1}{5} + \frac{1}{10}} + 2 = 5.3\Omega$



current divider

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ^{theoretically w/supermesh}
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

For redrawn circuit

KVL 1) $-40V - 10V + 2i_1 + 4i_1 - 4i_2 = 0$
 $6i_1 - 4i_2 = 50V$

... used wrong method...
 didn't write current eqns...

2) $+4i_2 + 4i_1 + 8i_2 - 20V = 0$

$4i_1 + 4i_2 = 20V$

$i_1 + i_2 = 5$

$i_1 = (5 - i_2)$ ^{plug in}

$6(5 - i_2) - 4i_2 = 50$

$30 - 6i_2 - 4i_2 = 50$

$-10i_2 = 20$

$i_2 = -2mA$

$i_x = -i_2 = 2mA$


$i_1 = 7mA$

supermesh


$V_x = 4i_1 - 4i_2$

$= 4(7) - 4(-2)$


$V_x = 36V$

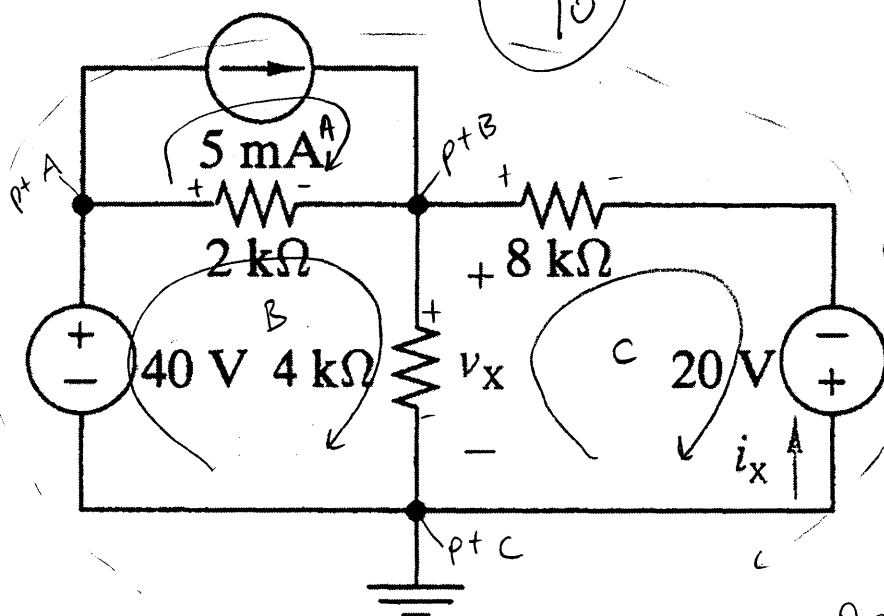

Mesh A

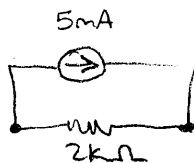


⇒

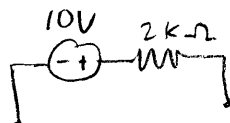

$V = iR$
 $= 5mA(2k\Omega)$
 $= 10V$

Redrawn circuit:

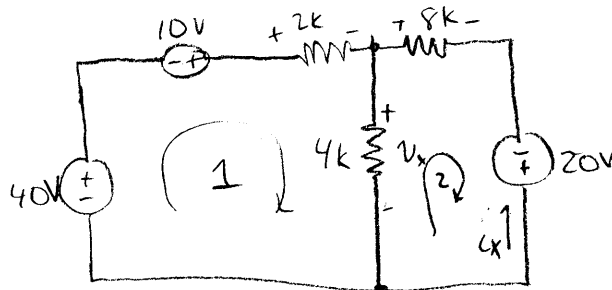

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS




1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{\underline{\frac{40}{3}}}$ volts

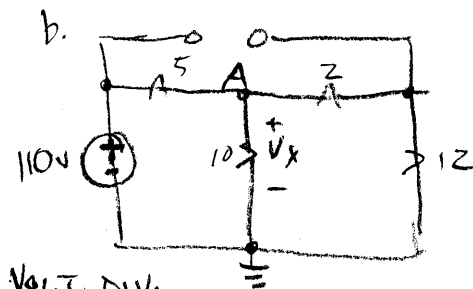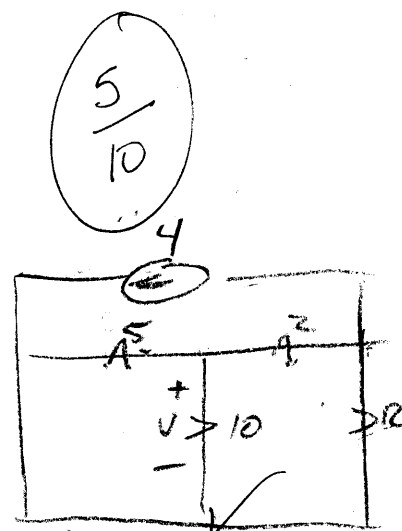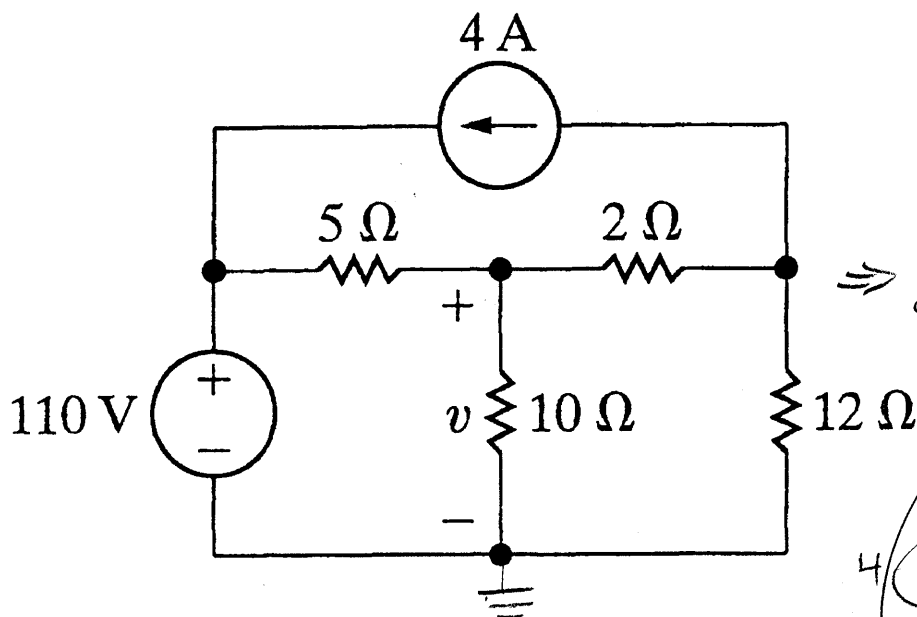b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{\underline{\frac{220}{3}}}$ volts




VOLT. DIV.

ⓐ A

~~$$V_A = 0 \Rightarrow V_x = \frac{V_S \cdot 10}{15} = \frac{V_S \cdot \frac{2}{3}}{3} = \frac{220}{3}$$~~

NOT in parallel with 4A source

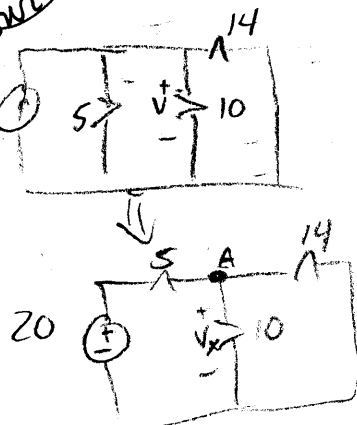

$$V_A = V_x = \frac{4 \cdot 10}{\frac{15}{3}} = \frac{40}{3}$$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 2X
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form. *You did node voltage, not mesh current.*

(a) $i_1 + i_3 = -50$

(b) $i_x + i_2 + i_3 = 0$

$V_A - 0 = V_x$

$\frac{50 - V_A}{2k} + \frac{V_A - 0}{4k} = 0$

$\frac{50 - V_x}{2k} + \frac{V_x}{4k} = 0$

$\frac{50}{2k} - \frac{V_x}{2k} + \frac{V_x}{4k} = 0$
 $+\frac{V_x}{4k} = +\frac{50}{2k}$

(c) Solve your equations for V_x and i_x .

$V_x = \frac{100}{3} \text{ V}$
 $i_x = 15 \text{ mA}$

$V_x = V_s \cdot \frac{4k}{6k} = \frac{100}{3}$

$i_x + i_2 + i_3 = 0$

$i_x = 0 - i_2 - i_3$

$= 0 + \frac{100 - V_x}{8k} - \frac{V_x}{4k}$



$i_x = \frac{20}{8k} + \frac{V_x}{8k} - \frac{V_x}{4k}$

$= \frac{5}{2k} + \frac{100}{24k} - \frac{100}{12k}$

$= \frac{66}{24k} + \frac{100}{24k} - \frac{200}{24k}$

$= \frac{366}{24k} = \frac{30}{2k} = \frac{15}{1000} \text{ A}$

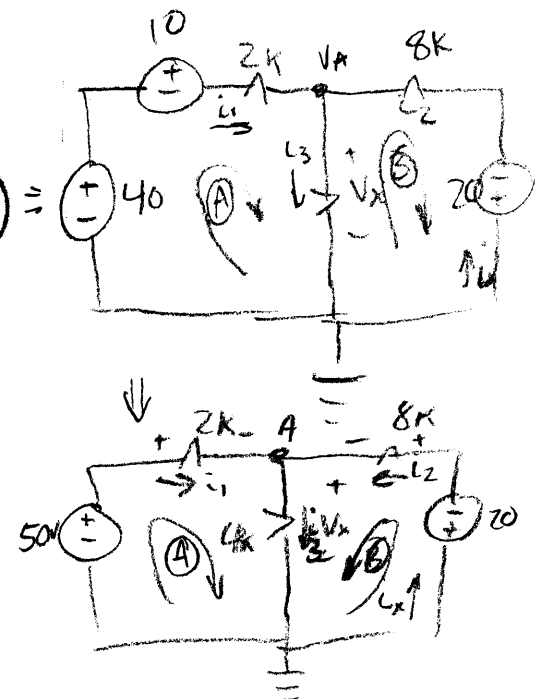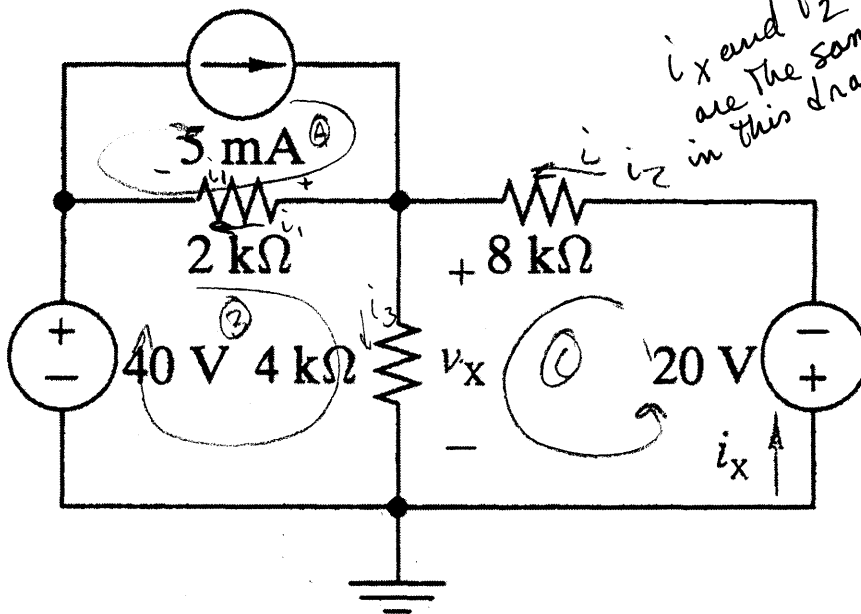i_x and i_2 are the same in this drawing.



Name: Daniel Donato Section: ME CWRU e-mail: dpd11

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS




1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{\frac{40}{3}}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.23}$ volts

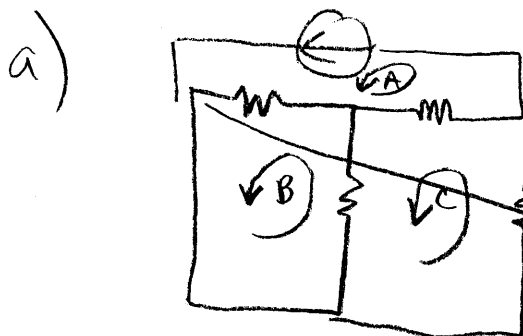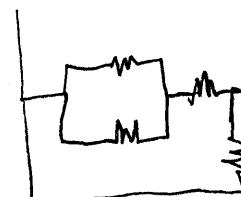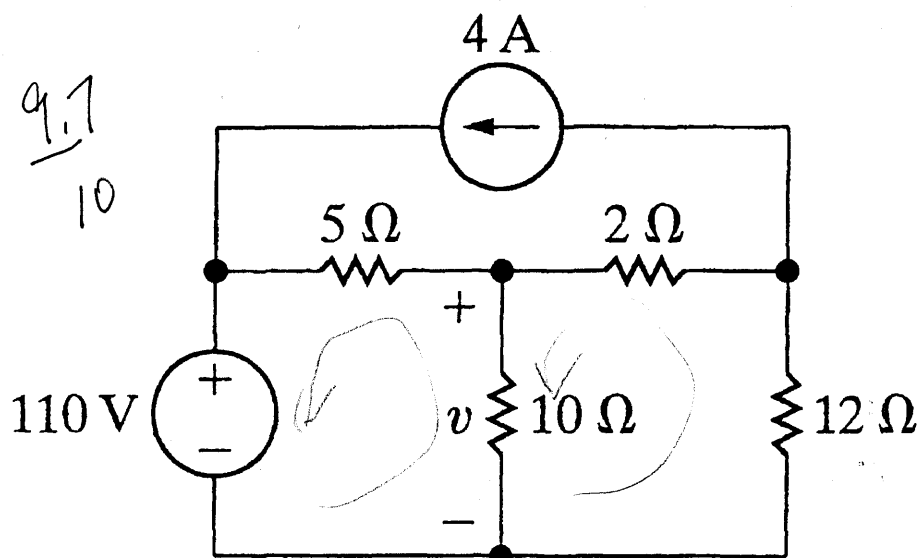

$I_A = 4A$

$24I_C = 8 - 10I_B$

C: $12I_C + 2I_C - 2(4) + 10I_C - 10I_B = 0$

B: $10I_B - 10I_C + 5I_B - 20 = 0$

$I_B = \frac{10I_C + 20}{15}$

$V = 10 \left(\frac{16}{23} - 1.7971 \right) =$

$= 16 \angle 11.01^\circ$

$24I_C = 8 - \frac{10(10I_C + 20)}{15} \quad \frac{100I_C}{15} + \frac{200}{15}$

$\frac{460}{15} I_C = 8 + \frac{200}{15} \quad I_C = \frac{16}{23} A$

$I_B = 1.7971 A$

Name: Daniel Donato Section: ME CWRU e-mail: dpd11

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

A: $20 + 8i_a + 4(i_a - i_b) = 0$ ✓
 B: $40 + 4(i_b - i_a) + 2(i_b - i_c) = 0$ ✓
 $i_c = 5 \text{ mA}$ ✓

A: $20 + 12i_a - 4i_b = 0$

B: $40 + 6i_b - 4i_a - 2i_c = 0$

$i_c = 5 \text{ mA}$ ✓


equations correct.
 sign error
 signs not in agreement.

- (c) Solve your equations for v_x and i_x .

$v_x = \underline{54.286 \text{ V}}$
 $i_x = \underline{\frac{36}{7} \text{ mA}}$




i_x

$\frac{9}{10}$

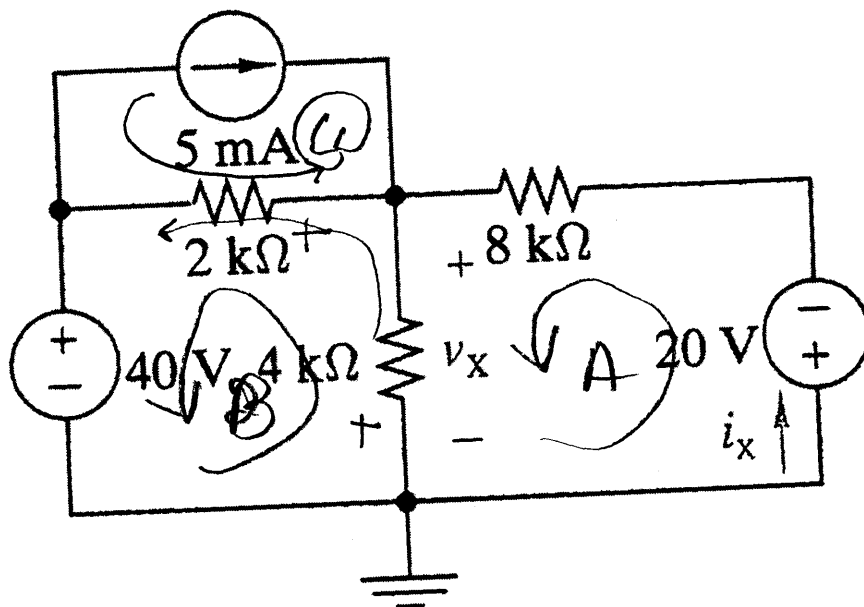

Donato

b)

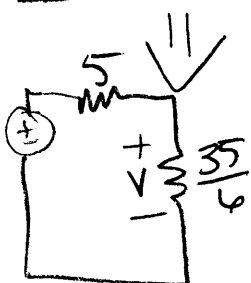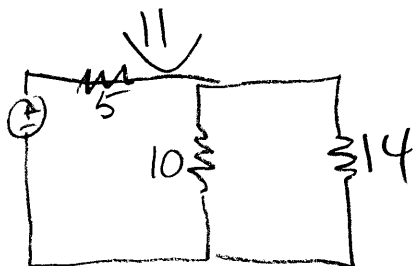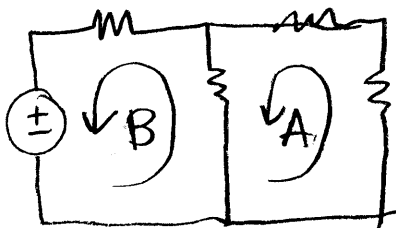

$$B: 10(I_A - I_B) + 5(I_B) + 110 = 0$$

$$A: 10(I_B - I_A) + 2(I_A) + 12(I_A) = 0$$

$$A: 10I_B + 4I_A = 0$$

$$I_A = -\frac{5}{2}I_B$$

$$B: 10I_A - 5I_B + 110 = 0$$

$$-25I_B - 5I_B = -110$$

$$I_B = \frac{-110}{-30} = \frac{11}{3}A$$

$$I_A = -\frac{5}{2}\left(\frac{11}{3}\right) = -\frac{55}{6}A$$



$$\frac{1}{10} + \frac{1}{14} = \frac{24}{140} \quad \frac{140}{24} = \frac{35}{6}$$

$$V = (I_B - I_A)10 = \left(\frac{55}{6} - \frac{11}{3}\right)10 = 55V$$


$$\textcircled{2} V = \left(\frac{\frac{35}{6}}{5 + \frac{35}{6}}\right)110 = 59.23V$$

Danie!
Donato

a)

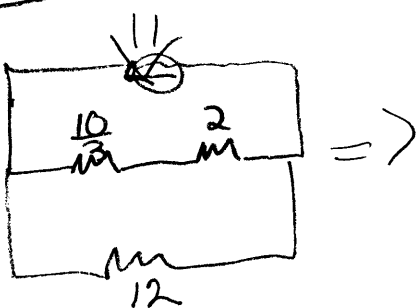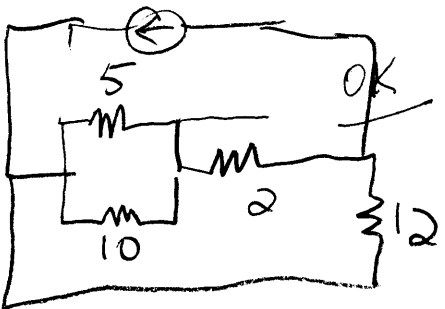
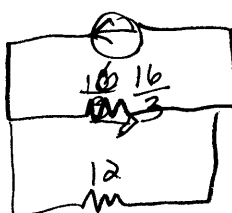
$$\frac{1}{5} + \frac{1}{10} = \frac{3}{10} = \frac{10}{3}$$



$$I_A = 4\left(\frac{12}{\frac{10}{3} + 12}\right) = \frac{36}{64} = \frac{9}{16}A = \frac{9}{4}A$$

Small math error near this point

$$V = \frac{4}{3}(10)(4) = \frac{40}{3}V$$

-0.3

$$20 + 12i_a - 4i_b$$

$$i_b = 5 + 3i_a$$

$$40 + 6(5 + 3i_a) - 4i_a - 10 = 0$$

$$40 + 30 + 18i_a - 4i_a - 10 = 0$$

$$60 = -14i_a \quad i_a = \frac{30}{7} \text{ mA} = i_x$$

$$i_b = 5 + \frac{90}{7} = \frac{125}{7} \text{ mA}$$

$$V_x = 4(i_b - i_a)$$

$$V_x = \frac{4(95)}{7} = 54.286 \text{ V}$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source


$V_{4A} = \underline{33.3}$ volts

b. find the contribution to v from the 110V voltage source


$V_{110V} = \underline{73.3V}$ volts

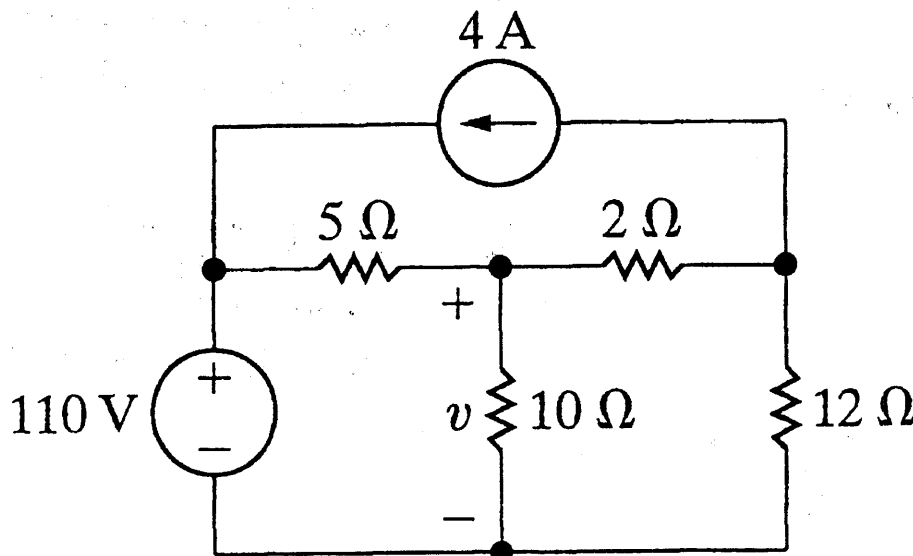

$\frac{5}{10}$

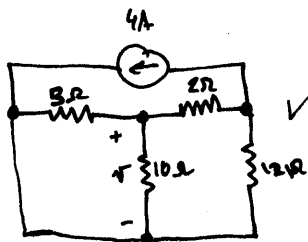

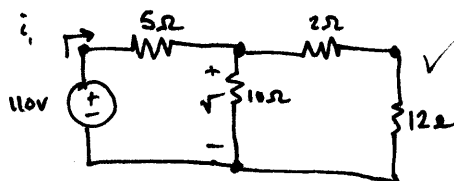$V_{4A} = i_{EQ} \cdot 10\Omega$, $i_{EQ} = \left(\frac{10}{10+2} \right) 4A \rightarrow i_{EQ} = 3.33A$
 $V_{4A} = 3.33A \cdot 10\Omega = 33.3V$



$i_1 = \frac{V}{R_{EQ}}$, $R_{EQ} = 5\Omega + \left(\frac{1}{\frac{1}{10\Omega} + \frac{1}{14\Omega}} \right) = 10.83\Omega$
 $i_1 = 10.15A$
 $V_{110V} = \left(\frac{10\Omega}{10+5\Omega} \right) 110V = 73.3V$

-3

2. (10 points)

- (a) How many meshes are there in the circuit given below. 2 X
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

~~$B: -4i_1 + 2i_2 - 10V + 40V = 0$~~ if you use i_x as your reference i_B are signs are wrong
 $A: -20V + 8i_x + 4i_x = 0$
 ~~$B: 40V + 10V + 2.5A + 4k5mA = 0$~~
 ~~$B: -40V + 10V + V_x = 0$~~
 ~~$V_x = 30V$~~

~~$V_x = 4i_x = 30V \Rightarrow 7.5mA = i_x$~~


$+4i_1 + 2i_2 = 30V$
 $+12i_x = 20V$
 $\Rightarrow i_x = +1.67mA$

- (c) Solve your equations for v_x and i_x .


$v_x = \underline{30V} \quad 10.16V$
 $i_x = \underline{7.5mA} \quad +1.67mA$

$\frac{0}{10}$

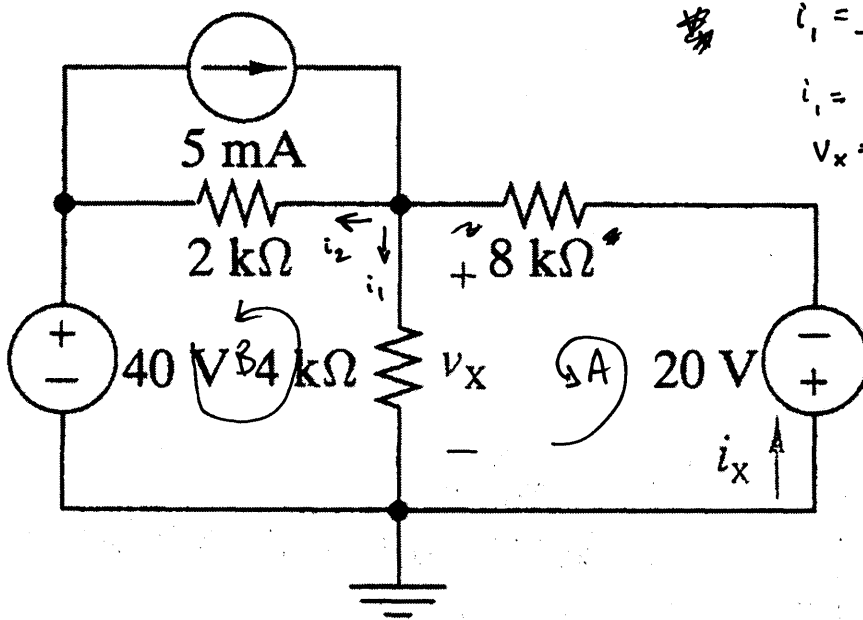~~$i_1 = \frac{4i_x}{6} + \left(\frac{4}{4}\right) 5mA$
 $i_1 = 2.54mA$
 $V_x = 4i_1 = 4 \cdot 2.54mA = 10.16V$~~



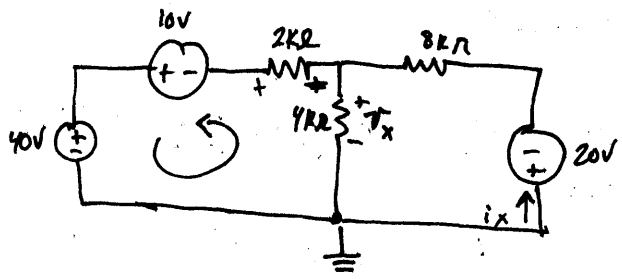$i_1 = \frac{4i_x}{6} + \left(\frac{4}{4}\right) 5mA$
 $i_1 = 2.54mA$
 $V_x = 4i_1 = 4 \cdot 2.54mA = 10.16V$



CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS

1. (10 points) Using superposition

a. find the contribution to v from the 4A current source


$V_{4A} = \underline{-120/13} \text{ V}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{770/13} \text{ V}$ volts

$$V = V_{110V} + V_{4A} = \frac{770}{13} - \frac{120}{13} = \frac{650}{13} = 50$$

$V = 50V$

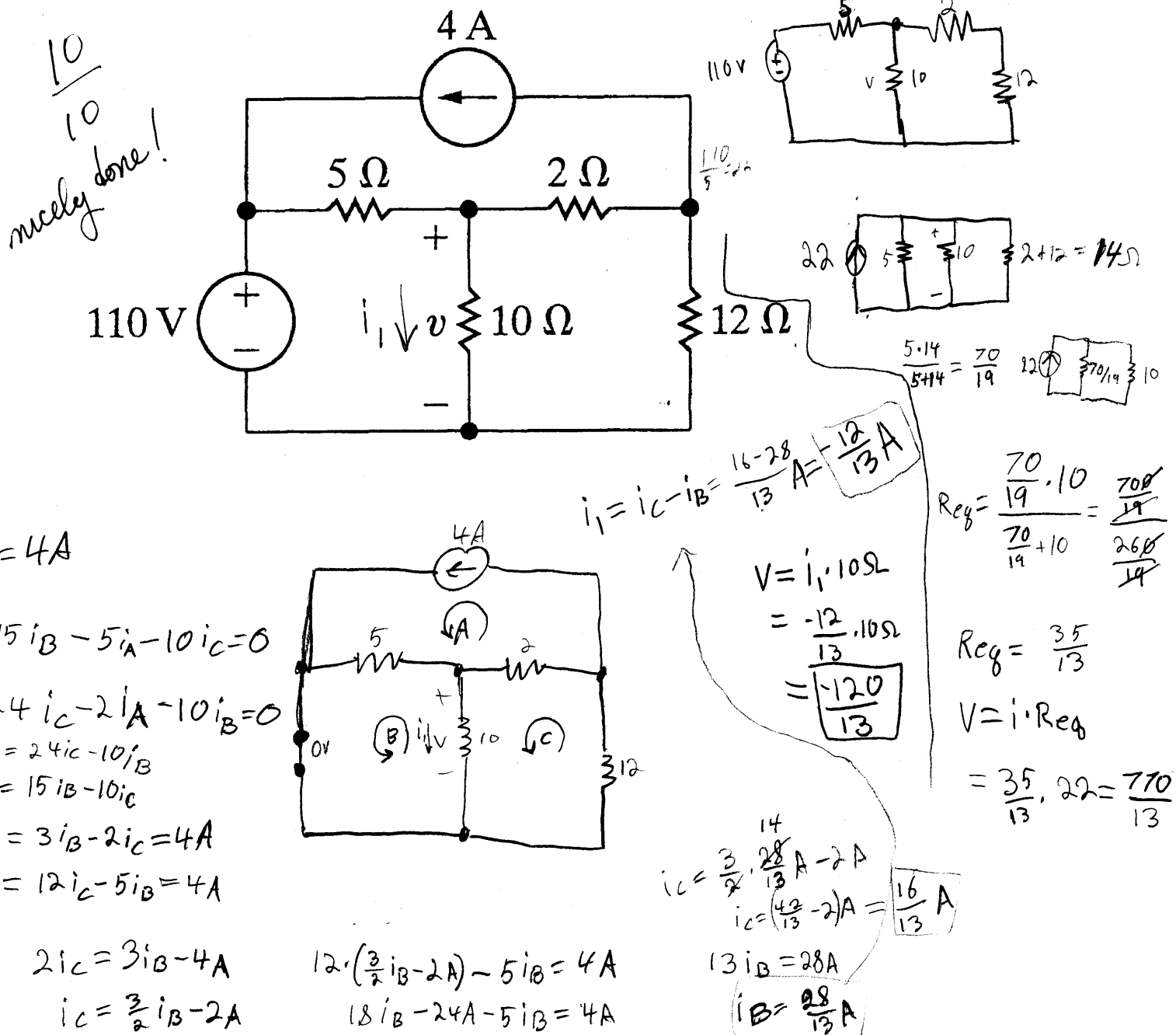

$K = k\Omega$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 meshes: A, B, C 3 supermeshes: AB, BC, ABC 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

A

$i_A = 5\text{mA}$ ✓

B

$-2ki_A + 6ki_B - 4ki_C = 40V$ ✓

C

$0i_A - 4ki_B + 12ki_C = 20V$ ✓

$k\Omega \cdot \begin{bmatrix} 1 & 0 & 0 \\ -2 & 6 & -4 \\ 0 & -4 & 12 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 5\text{A} \\ 40V \\ 20V \end{bmatrix}$

equations OK.

$12k i_C = 4k i_B + 20V$

$i_C = \frac{1}{3} i_B + \frac{5}{3} \text{mA}$

math error somewhere

(c) Solve your equations for v_x and i_x .

$v_x = \frac{20}{3} V$
 $i_x = -\frac{10}{3} \text{mA}$

(c): $-2k \cdot 5\text{mA} + 6k i_B - 4k(\frac{1}{3} i_B + \frac{5}{3} \text{mA}) = 20V$


$-10V + 6k i_B - \frac{4}{3}k i_B + \frac{20}{3}V = 20V$
 $\frac{18}{3} - \frac{4}{3} = \frac{14}{3}$

$\frac{14}{3}k i_B = (20 + 10 - \frac{20}{3})V$

$\frac{14}{3}k i_B = \frac{70}{3}V$

$i_B = \frac{70}{14k}V$

$i_B = 5\text{mA}$

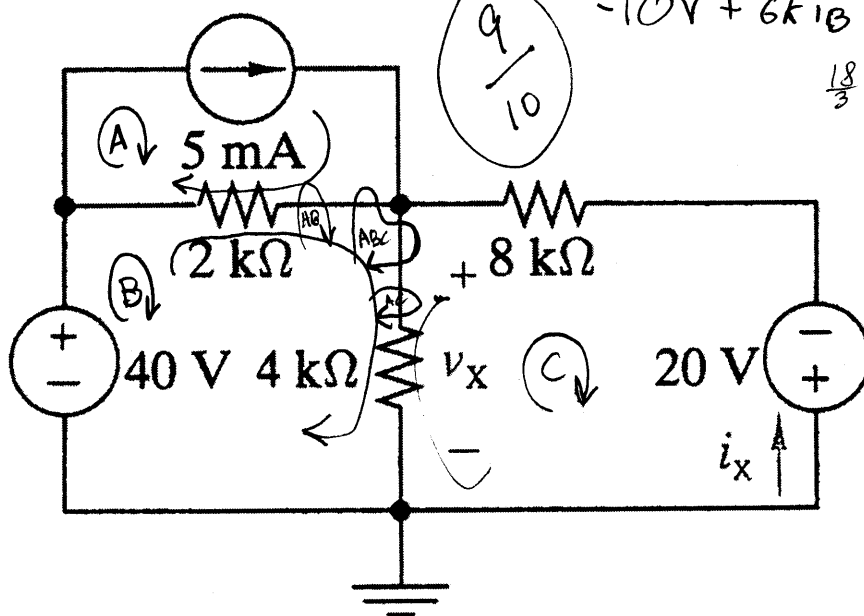

$V_x = (i_B - i_C) 4k\Omega$
 $(5\text{mA} - \frac{10}{3}\text{mA}) 4k\Omega$
 $\frac{5}{3}\text{mA} \cdot 4k\Omega$

$V_x = \frac{20}{3} V$

$-4k \cdot 5\text{mA} + 12ki_C = 20V$
 $-20 + 12ki_C = 20V$

$i_C = \frac{40}{12} \text{mA}$

$i_C = \frac{10}{3} \text{mA}$

$i_C = -i_x$

$i_x = -\frac{10}{3} \text{mA}$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$v_{4A} = \underline{1.537}$ volts


b. find the contribution to v from the 110V voltage source

$v_{110V} = \underline{59.2}$ volts




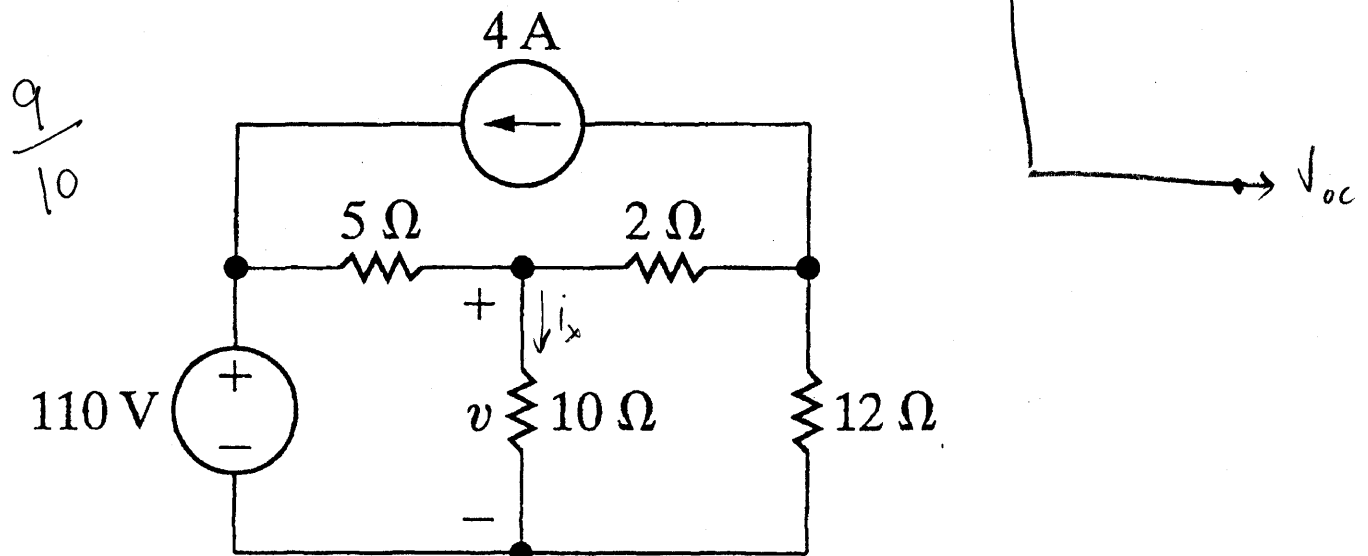


(b)

(a)

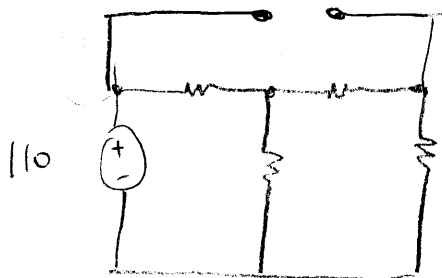
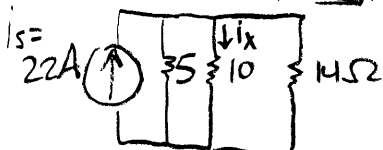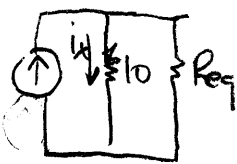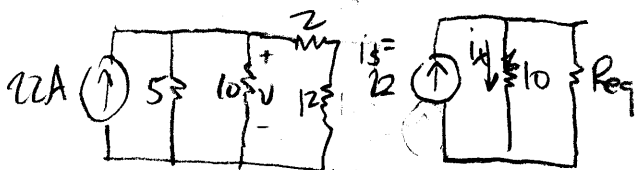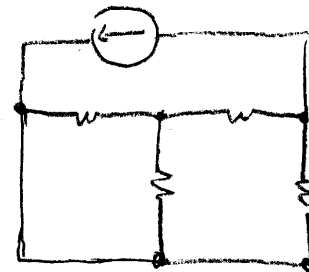
$$R_{eq} = \frac{5 \cdot 12}{5 + 12} = 3.68$$



$$i_x = \frac{22A(3.68\Omega)}{3.68 + 10} = 5.92A$$

$$v_{110V} = 10\Omega(5.92A) = \boxed{59.2V}$$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

(A) $5\text{mA} = i_A$ ✓

(B) $-40\text{V} + 2\text{k}\Omega(i_B - i_A) + 4\text{k}\Omega(i_B - i_C) = 0$ ✓


(C) $4\text{k}\Omega(i_C - i_B) + 8\text{k}\Omega i_C - 20\text{V} = 0$ ✓

(c) Solve your equations for v_x and i_x .

$v_x = \underline{25.71\text{V}}$
 $i_x = \underline{-5.71\text{mA}}$

$\frac{10}{10}$

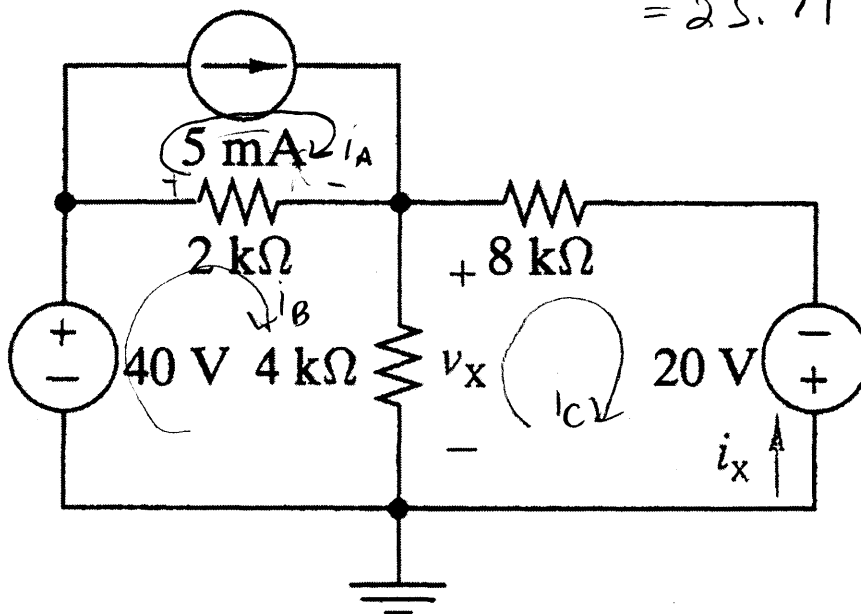$v_x = 4\text{k}(i_B - i_C)$
 $= 25.71\text{V}$





$0.005 = i_A$ ✓

$6000i_B - 2000i_A - 4000i_C = 40\text{V}$

$12000i_C - 4000i_B = 20\text{V}$



$$\begin{bmatrix} 6000 & -4000 \\ -4000 & 12000 \end{bmatrix} = \begin{bmatrix} 50\text{V} \\ 20 \end{bmatrix} \begin{bmatrix} i_B \\ i_C \end{bmatrix} = \begin{matrix} 0.0121 = 12.1\text{mA} \\ 0.0057 = 5.71\text{mA} \end{matrix}$$

(a)

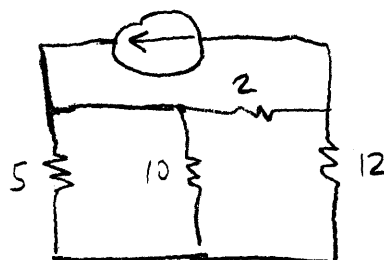
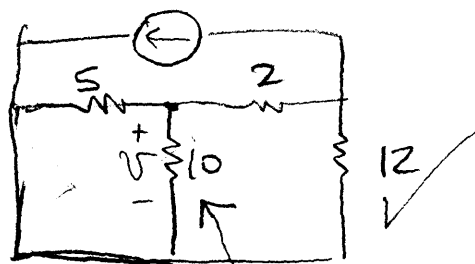


Liz Hahn
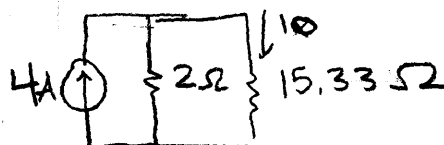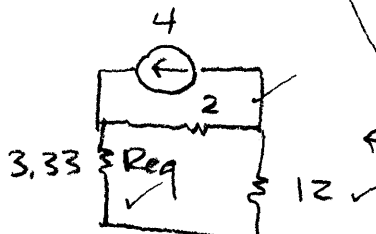
$$R_{eq1} = \frac{5 \cdot 10}{15} = 3.33 \Omega$$


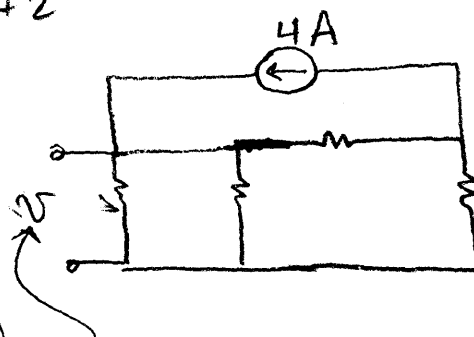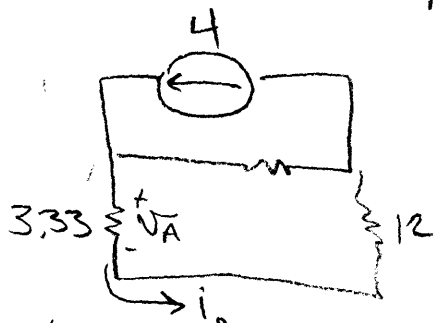
$$i_o = \frac{4A(2\Omega)}{15.33 + 2} = 0.4615 A$$



$$V_A = (0.4615 A)(3.33 \Omega) = 1.537 V = V_{4V}$$

this is not the current
labeled i_o above

-1

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{6\frac{2}{3}}$ volts

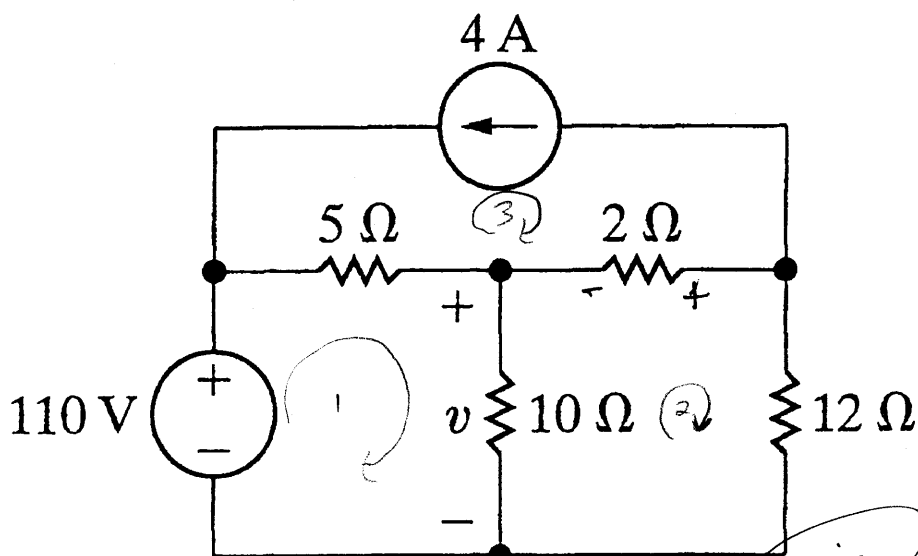b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{73\frac{1}{3}}$ volts



$\frac{8.5}{10.}$

B

KVL $\rightarrow$ Loop rule $110V - i_1 5\Omega - i_1 10\Omega = 0$
Assume current source is broken

$110V = i_1(5+10\Omega)$
 $7\frac{1}{3} = i_1$

Voltage = $iR = (7\frac{1}{3}A)(10\Omega) = \underline{73\frac{1}{3}V}$

A

Use mesh currents This is a very difficult way to solve problem.

mesh 1: $-5\Omega i_3 - (10\Omega i_2 + (15\Omega) i_1) = 0$ OK

mesh 2: $24\Omega i_2 - (10\Omega i_1 - 2\Omega) i_3 = 0$ OK

mesh 3: $i_3 = -4A$ OK.

Plug into matrix

Find

$i_1 - i_2 = i_{total} = (6.7A)(10\Omega) = \underline{6.7V}$

This does not agree with your other answers

$2.4(24\Omega)(\frac{20V+15\Omega i_1}{10\Omega}) - 10\Omega i_1 - 2\Omega(-4A) = 0$

$48V + 36\Omega i_1 - 10\Omega i_1 + 8V = 0$

$56V + 26\Omega i_1 = 0$

$i_1 = \frac{-56V}{26\Omega} = -2.14A$

seems correct to here.

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

I hope part A isn't a trick question. I realize that the current in mesh 1 is 5mA. Yes

$$i_1 = 5\text{mA} \quad \checkmark$$

$$i_2(6\text{k}\Omega) - (2\text{k}\Omega)(i_1) - 4\text{k}\Omega i_3 = +40\text{V}$$

$$i_3(12\text{k}\Omega) - (4\text{k}\Omega)i_2 = +20\text{V}$$

$$\frac{9}{10}$$


- (c) Solve your equations for v_x and i_x .

$$v_x = \underline{108.6\text{V}}$$

$$i_x = \underline{-19.28\text{mA}}$$

$$i_x = -i_3$$

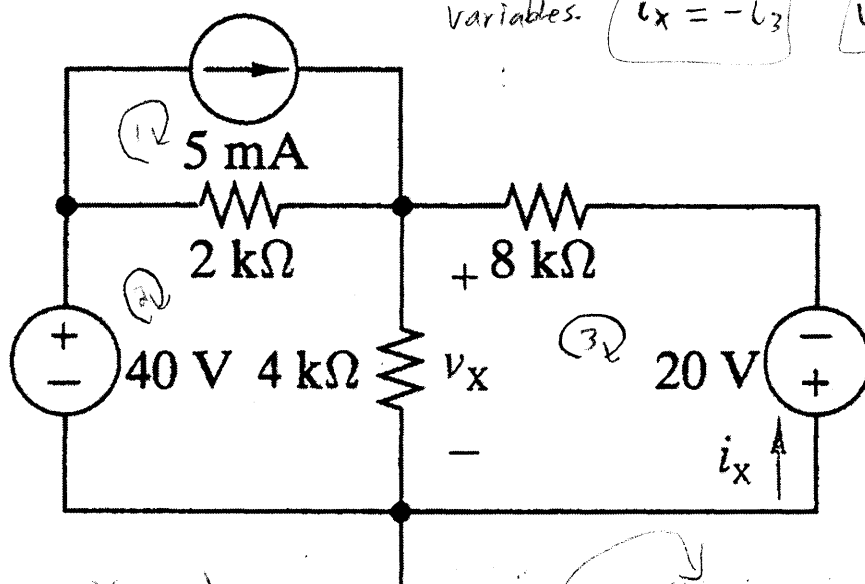Either use a matrix, or solve for variables. $i_x = -i_3$ $v_x = (i_2 - i_3)(4\text{k}\Omega)$



$$i_2(6\text{k}\Omega) - (2\text{k}\Omega)(5\text{mA}) - 4\text{k}\Omega i_3 = +40\text{V}$$

$$i_2(6\text{k}\Omega) - 10\text{V} + 40\text{V} = (4\text{k}\Omega)i_3$$

$$\frac{(6000\Omega)i_2 + 30\text{V}}{4000\Omega} = i_3$$

$$i_3(12\text{k}\Omega) - (4\text{k}\Omega)i_2 = -20\text{V}$$

$$3(12000\Omega)\left(\frac{6000\Omega i_2 + 30\text{V}}{4000\Omega}\right) - i_2(4000\Omega) + 20\text{V} = 0$$

$$i_2(18\text{k}\Omega) + 90\text{V} - i_2(4\text{k}\Omega) + 20\text{V} = 0$$

$$i_2(14\text{k}\Omega) + 110\text{V} = 0$$

$$i_2 = -7.86\text{mA}$$

$$(6000)(-0.007857\text{A}) + 30\text{V} = i_3 = \frac{77.14\text{V}}{4000\Omega} = 19.28\text{mA}$$

$$i_3 = 19.28\text{mA}$$

$$i_x = -i_3$$

$$v_x = ((-7.86\text{mA}) - (19.28\text{mA}))(4000\Omega) = 108.57\text{V}$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{4.67 \text{ V}}$ volts

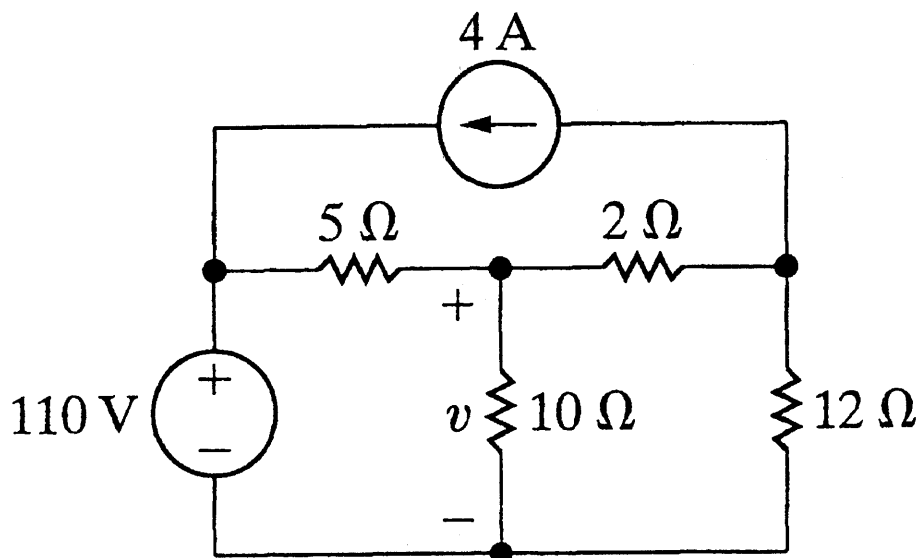
b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{58.92 \text{ V}}$ volts



$\frac{6}{10}$

a.) turn off Voltage Source

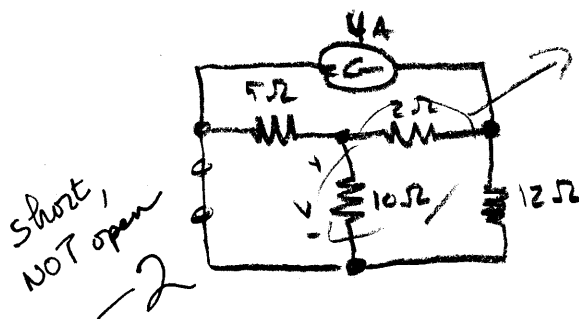


$R_{eq} = \frac{(2)(10)}{12} = \frac{20}{12}$

$R_{eq} = \frac{20}{12} + 5\Omega + 12\Omega = 18.67\Omega$

$V = IR \quad \frac{18.67}{4} = 4.67 \text{ V}$

b.) Turn off current source

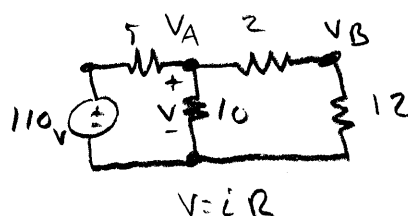

$R_{eq} = \frac{(2)(10)}{12} = \frac{20}{12}$

I have no idea what you are doing here. 2 and 10 are not in parallel.
-2.

$R_{eq} = 18.67\Omega$

$V = IR \quad I = \frac{110}{18.67} = 5.9 \text{ A}$

$V = (5.9 \text{ A})(10\Omega) = 58.92 \text{ V}$

Name: Mark KrajcarckSection: WACWRU e-mail: Mgk5

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 meshes ✓ 1 Super Mesh
- (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

① $(5 \text{ mA})\left(\frac{2 \cdot 4}{6}\right) - (20 \text{ mA})(2 \text{ k}\Omega)$ what is this?

② $\frac{40 \text{ V}}{2 \text{ k}\Omega} - \frac{10 \text{ V}}{2 \text{ k}\Omega} + \frac{V_x}{4 \text{ k}\Omega} + \frac{i_x(8 \text{ k}\Omega)}{4 \text{ k}\Omega} = 0$

$\frac{V_x}{4 \text{ k}\Omega} + \frac{i_x(8 \text{ k}\Omega)}{4 \text{ k}\Omega} = 15 \text{ mA} \Rightarrow \frac{V_x + i_x(8 \text{ k}\Omega)}{4 \text{ k}\Omega} = 15 \text{ mA}$

③ $\frac{-20 \text{ V}}{8 \text{ k}\Omega} + \frac{V_x}{4 \text{ k}\Omega} - \frac{20 \text{ V}}{12 \text{ k}\Omega} = 0 \Rightarrow \frac{V_x}{4 \text{ k}\Omega} = \frac{20 \text{ V}}{8 \text{ k}\Omega} + \frac{20 \text{ V}}{12 \text{ k}\Omega}$

(c) Solve your equations for v_x and i_x .


$v_x = \underline{16.67 \text{ V}}$

$i_x = \underline{4.67 \text{ mA}}$

$V_x = i_x R$

$V_x = 16.67 \text{ V}$

$i_x = \frac{16.67}{4 \text{ k}\Omega}$

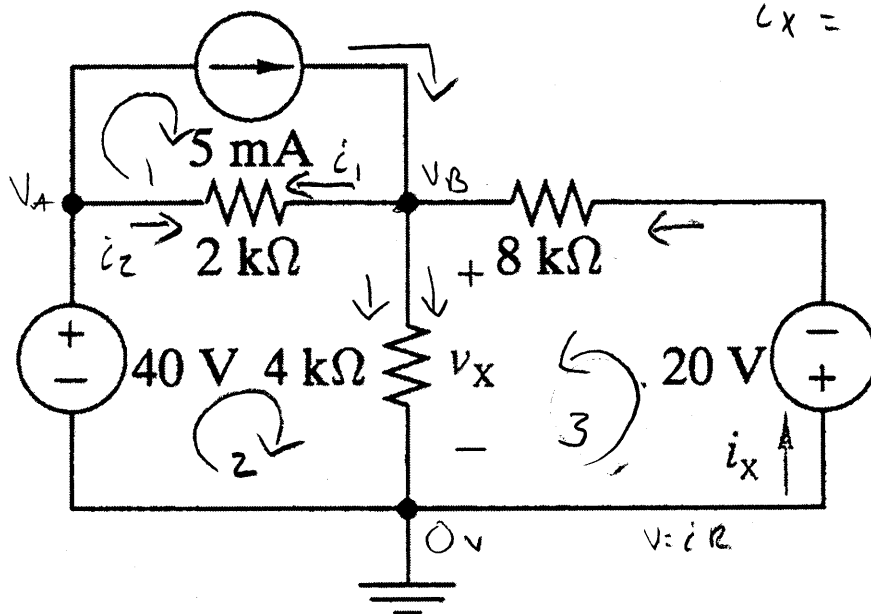

$i_x = \frac{20 \text{ V}}{4 \text{ k} + 8 \text{ k}} = \frac{20 \text{ V}}{12 \text{ k}\Omega}$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{24.51}$ volts


b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.22}$ volts

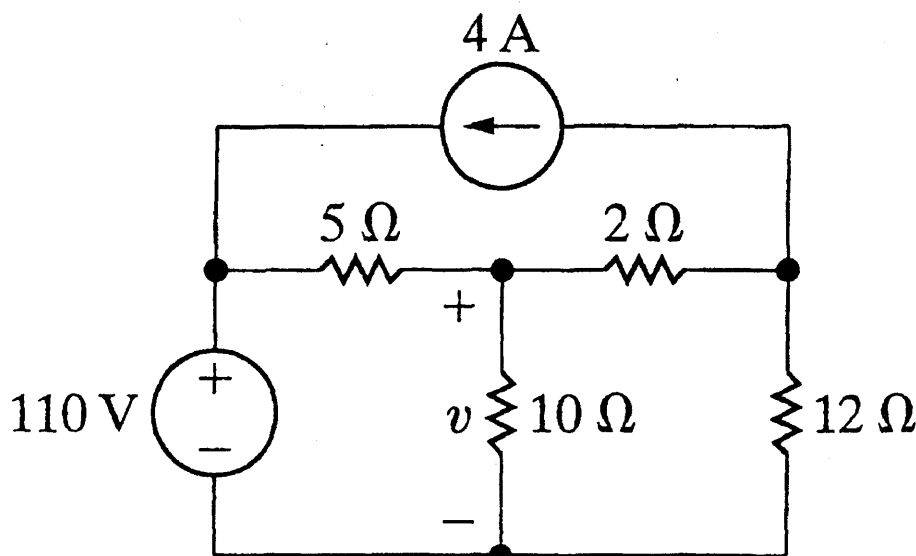


$\frac{7}{10}$


Turn off the current source:

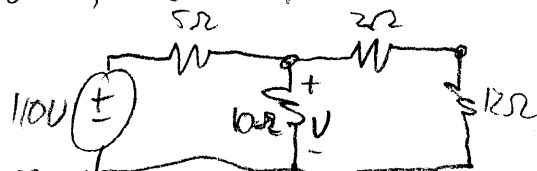

Combine resistances:

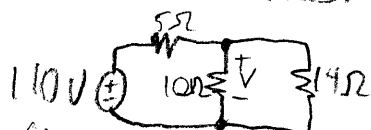


Combine resistances:

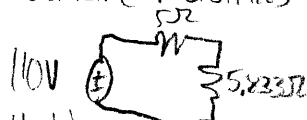

Voltage across the 5.833Ω resistor is 59.22V. It's the same as the voltage across the 10Ω resistor

Turn off the voltage source:

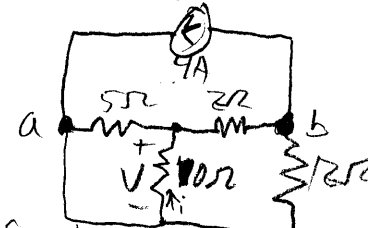

Current has a path of 7Ω, a path of 12Ω, and a path of 12Ω from a to b. Use this as a current divider. The current is $4A \times \left(\frac{7\Omega}{31\Omega}\right) = 24.51A$. Use $V=IR$ to find $V_{4A} = 24.51V$

— 3

Name: Charles Kanel Section: WA

CWRU e-mail: CPK4

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

Mesh 1: $i_1 + i_2 - 5 \text{ mA} = 0$


Mesh 2: $i_2 + i_1 - (40 \text{ V} / 6 \text{ k}\Omega) - i_x = 0$

Mesh 3: $i_x - i_2 + (20 \text{ V} / 12 \text{ k}\Omega) = 0$

~~Meshe~~ equations are written in terms of currents not voltages.

- (c) Solve your equations for v_x and i_x .
 $v_x =$ 31.415 V
 $i_x =$ -1.4285 A

1
10

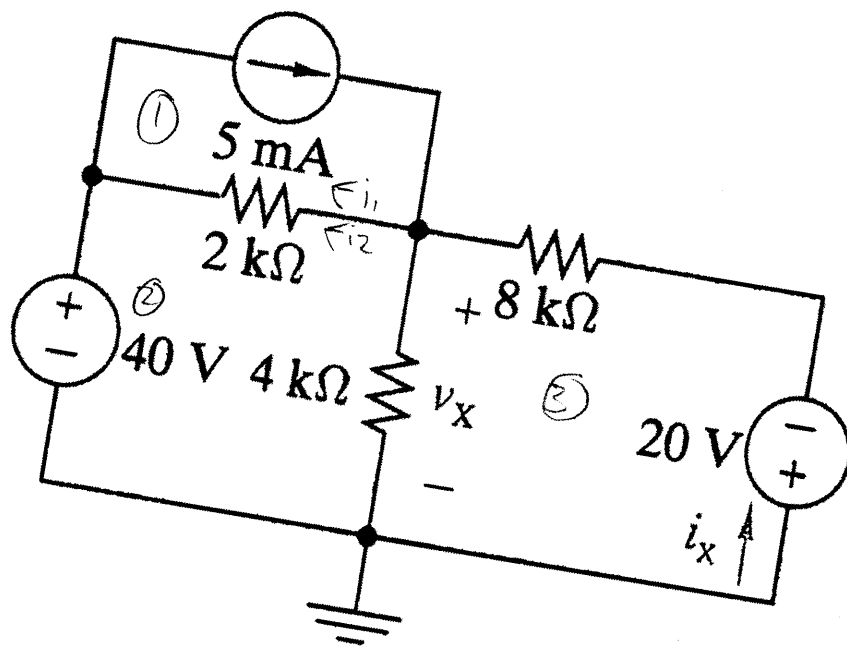

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} =$ 0.45 V volts




b. find the contribution to v from the 110V voltage source

$V_{110V} =$ 72.6 V volts

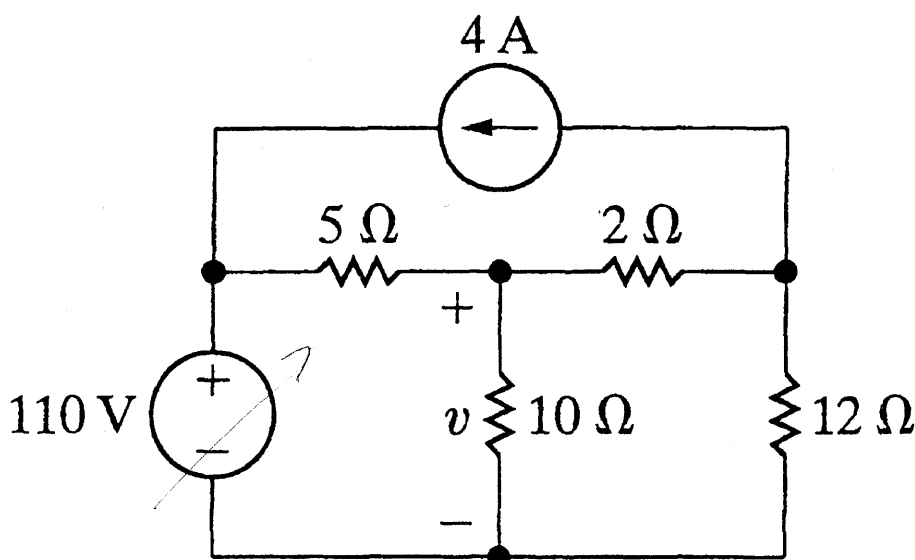

$\frac{5.5}{10}$

$V = 112$

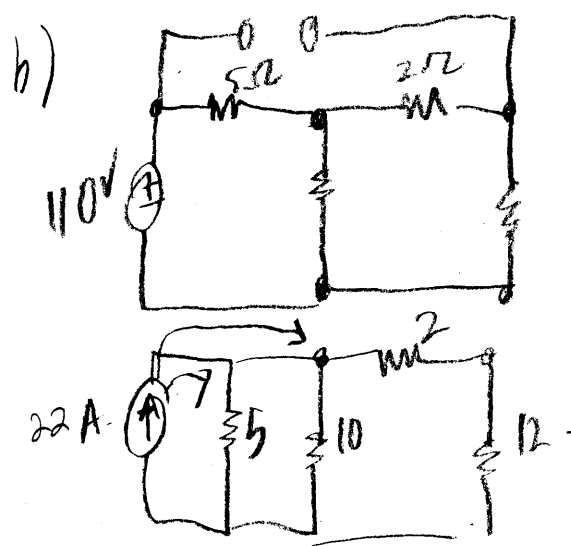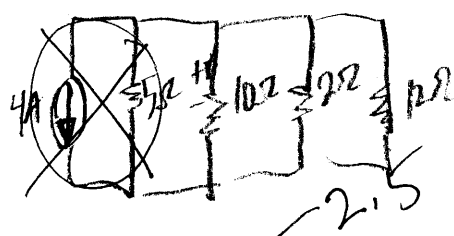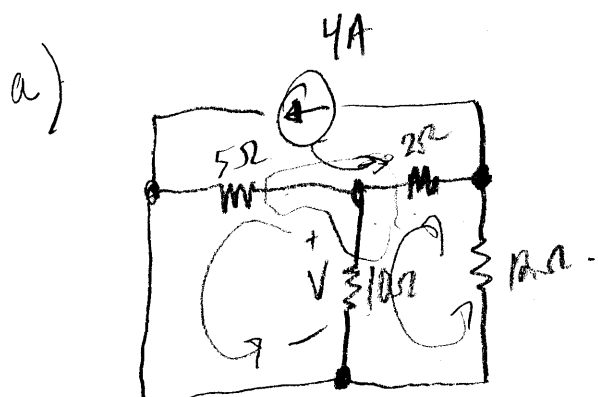

Name: Max Kotlarczyk Section: MA CWRU e-mail: mak46

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

MESH (A): $2k i_A - 2k i_B = 0$ X You ignored the $5mA$ source in loop i_B NOT i_x

MESH (B): $+40V + 4k i_B - 4k i_x + 2k i_A = 0$

$-2k i_A + 4k i_B - 2k i_x = -40$

MESH (C): $+20V + 8k i_x + v_x - 4k i_B = 0$ ✓

$8k i_x + v_x - 4k i_B = -20V$


(c) Solve your equations for v_x and i_x .

$v_x = \underline{200V}$
 $i_x = \underline{25mA}$

$(2k)(5mA) = 10V$

$10V - 2k i_B = 0 \quad i_A = i_B$

$i_B = 5mA$

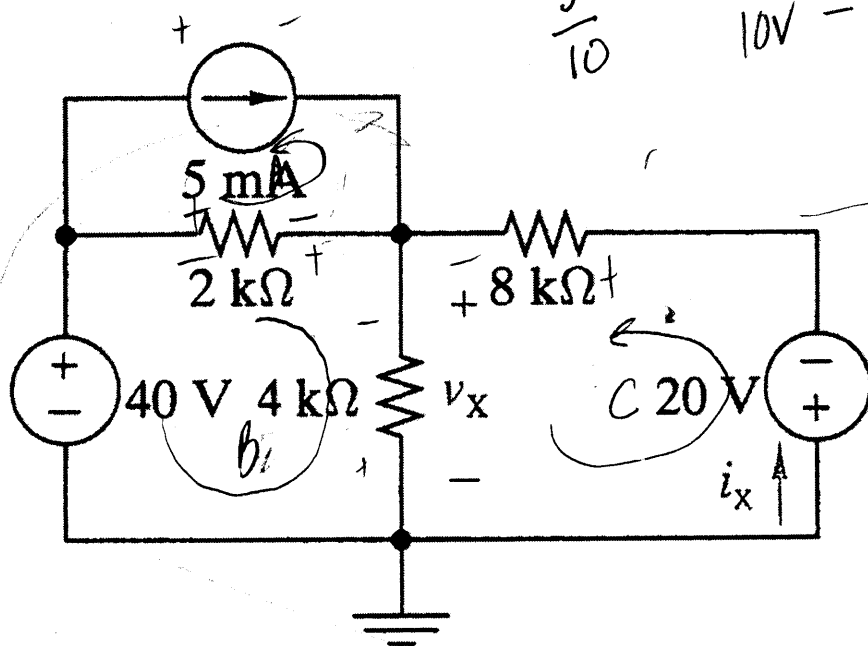

$-10 + 40 - 2k i_x = -40$

$-2k i_x = -50$

$i_x = 25mA$


$8k \cdot (25mA) + v_x - 20 = -20$

$v_x = 200V$

1a)

Current divider

Max
Kotludye

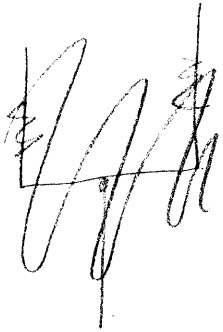



$$i_s = \left(\frac{\frac{1}{10}}{\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{1}{12}} \right) (4A) =$$

$$V = IR = (10 \Omega) (0.113 A) = 0.45V$$

1b) cont

$$\frac{50}{15} = 3.3$$

Max K.

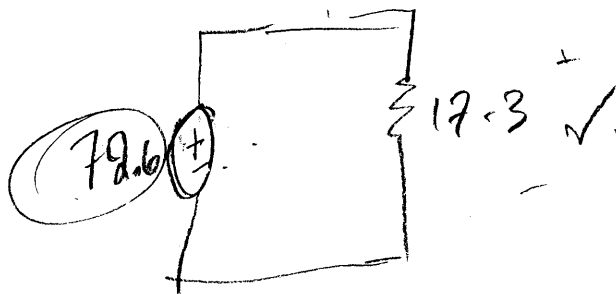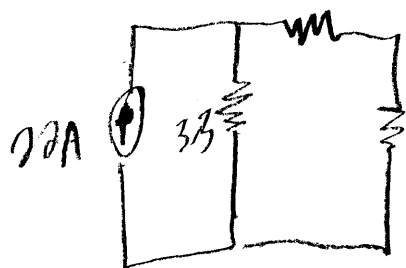

$V =$
Not sure what you
transformed here,
-2

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{7.09}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.22}$ volts

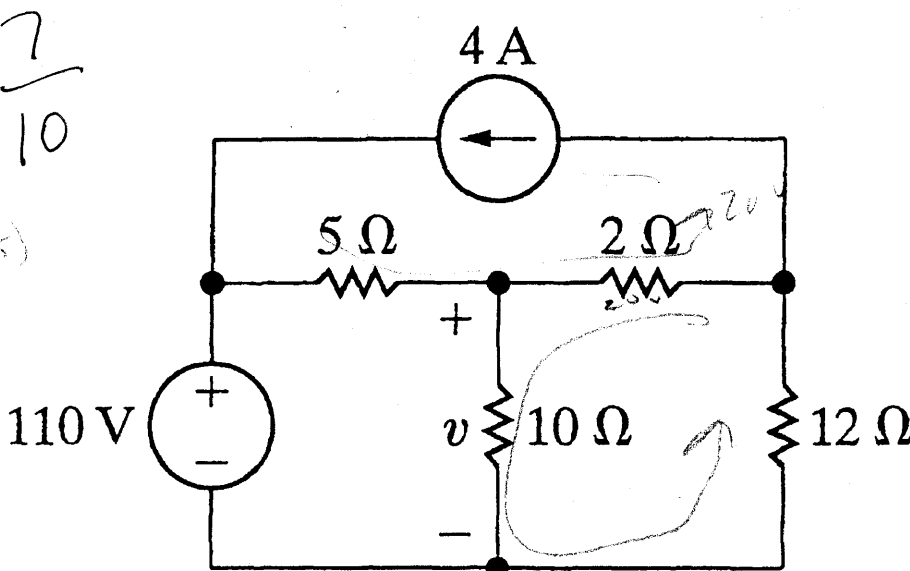

$V = IR$
 $4A(5)$
 $\frac{7}{10}$

$V = iR$

$V = iR$

$-20 + i(R+R) = 0$

$-20 + V - iR = 0$

12

$+20 = i(10+12)$


$20 = i(22)$

$i = 0.90909$


$V = iR$

$R = 10$

$V = 0.90909(10)$

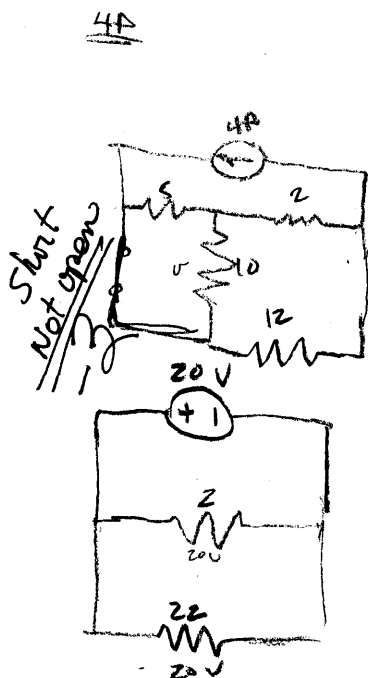

$\frac{10}{22}$

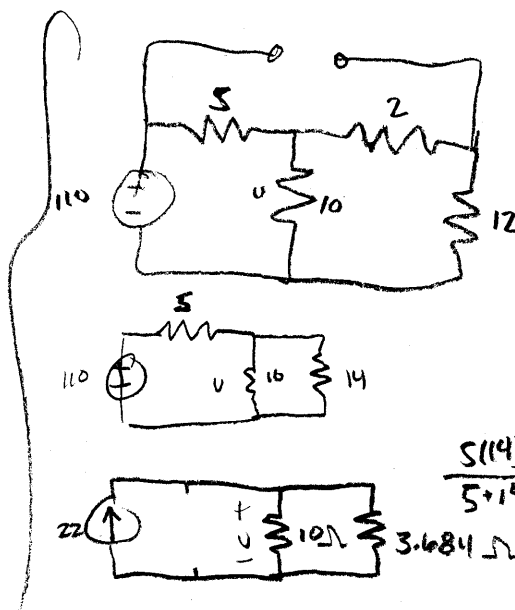

$i_5 = \frac{\frac{10}{10}}{\frac{1}{10} + \frac{1}{3.684}} (22) =$

5.922

$\frac{5(14)}{5+14} = 3.684$

$V = iR = 5.922(10)$

$V = 59.22$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

MESH I: $-i_1 + 5 \text{ mA} = 0$
 MESH II: $i_5 + i_1 + i_2 + i_3 = 0$
 MESH III: $-i_2 - i_4 - i_x = 0$

~~No~~


mesh current means you sum up the voltage using KVL.

$i_1 = 5 \text{ mA}$
 $i_x = i_4 - i_2$

$i_4 + 0.005 + i_1 = i_2$
 $i_3 = i_1 + 0.005$
 $i_2 = i_3 + i_x$

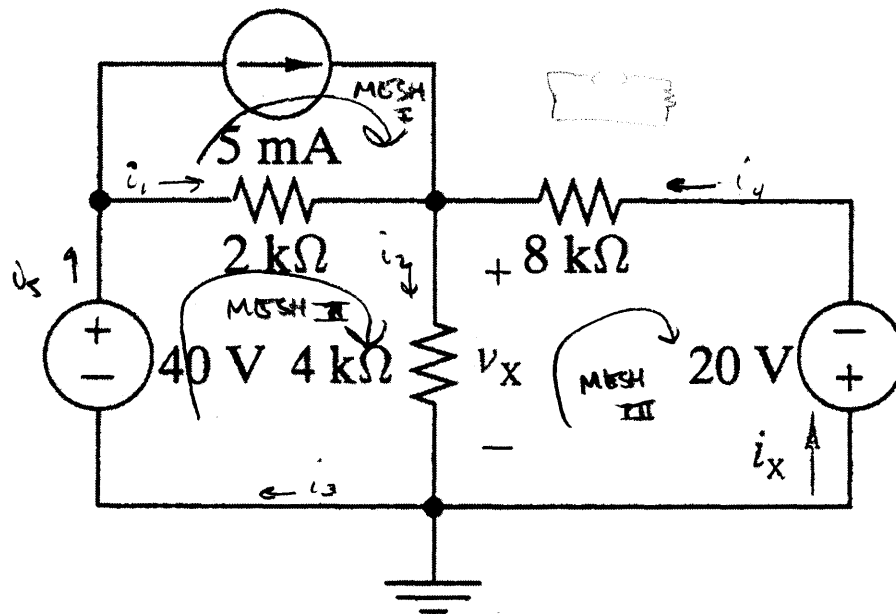(c) Solve your equations for v_x and i_x .

$v_x = \underline{\quad \quad \quad} \text{ V}$
 $i_x = \underline{\quad \quad \quad} \text{ mA}$



$$V = IR$$

$$v_x + 20 - 8000 i_4 = 0$$

$$-40 + 2000 i_1 + v_x = 0$$

$$v_x = i_2 4000$$

$$-40 + 2000 i_1 + 8000 i_4 - 20 \text{ V} = 0$$

$$40 - 2000(0.03 - 4 i_4) = v_x$$

$$60 = 2000 i_1 + 8000 i_4$$

$$0.03 = i_1 + 4 i_4$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source



$V_{4A} = \underline{20V}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{128.33V}$ volts

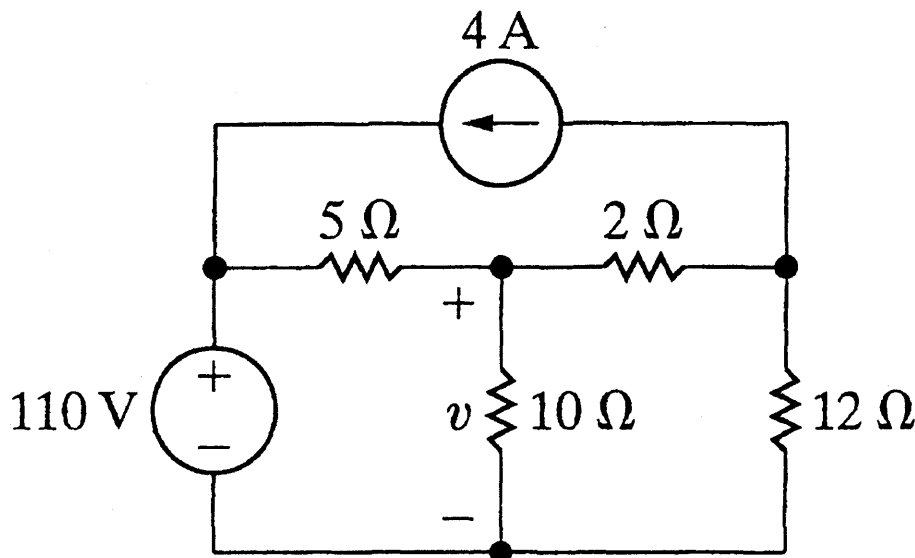

~~3~~ $\frac{3}{10}$

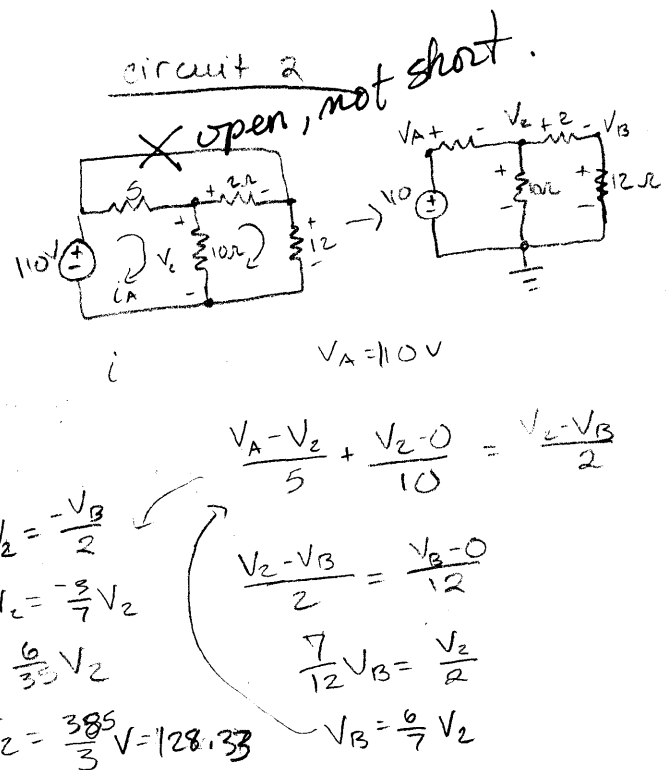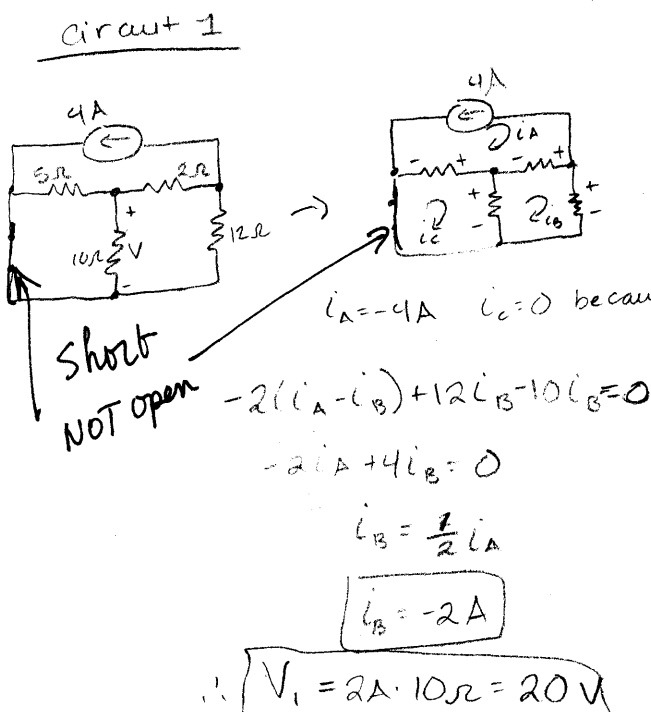

Name: Amy Orsborn Section: _____ CWRU e-mail: _____

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

$$i_A = 5 \text{ mA} \quad i_x = -i_c$$

$$8i_c - 20\text{V} - 4(i_B - i_c) = 0 \quad 4(i_B - i_c) - 40\text{V} - 2(i_A - i_B) = 0 \quad \text{OK}$$

(c) Solve your equations for v_x and i_x .

$$v_x = \underline{25.712 \text{ V}} \\ i_x = \underline{-5.714 \text{ mA}}$$

$$\frac{9.7}{10}$$

$$12i_c - 4i_B = 20$$

$$i_B = 3i_c - 5 \text{ mA}$$

$$6i_B - 4i_c - 2\text{k}\Omega(5\text{mA}) = 40$$


$$6i_B - 4i_c = 50$$

$$6(3i_c - 5) - 4i_c = 50$$

$$14\text{k}\Omega i_c = 80 \text{ V}$$

$$i_c = 5.714 \text{ mA}$$

$$\therefore i_B = 12.142 \text{ mA}$$

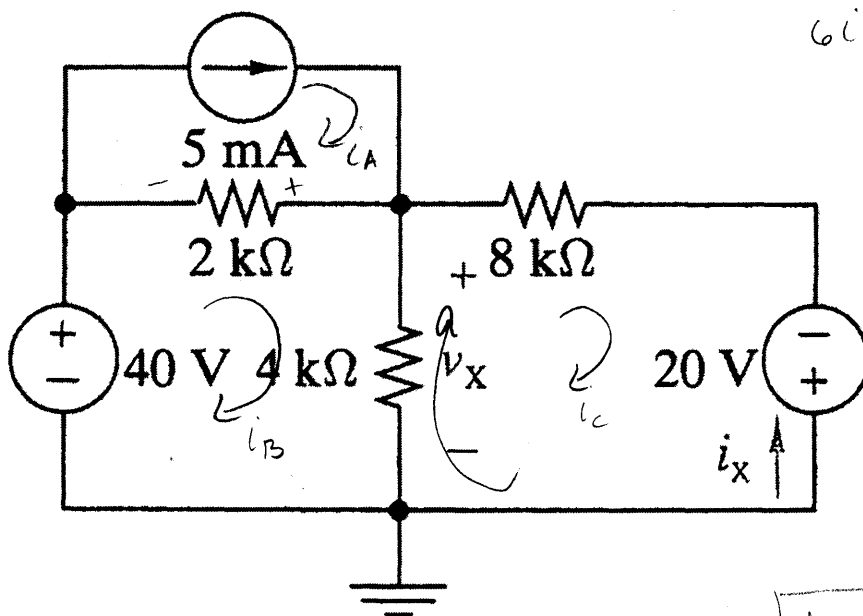

$$V_x = (i_B - i_c) 4\text{k}\Omega$$

$$= (12.142 - 5.714) \text{ mA} \cdot 4\text{k}\Omega$$

$$= 25.712 \text{ V}$$

$$i_x = -i_c = -5.714 \text{ mA}$$

Small
math error
somewhere.

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{20V}$ volts

b. find the contribution to v from the 110V voltage source


$V_{110V} = \underline{73.33}$ volts

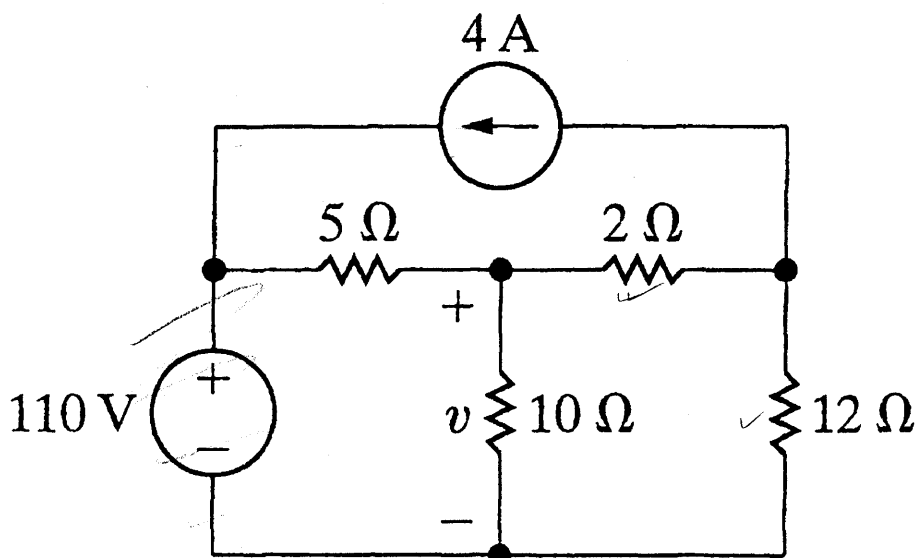

V_{4A}


$\frac{4.5}{10}$

For 4A

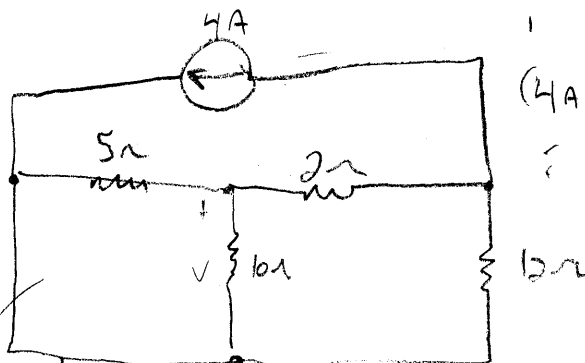


$(4A \cdot 5\Omega) = 20V$

For 110V

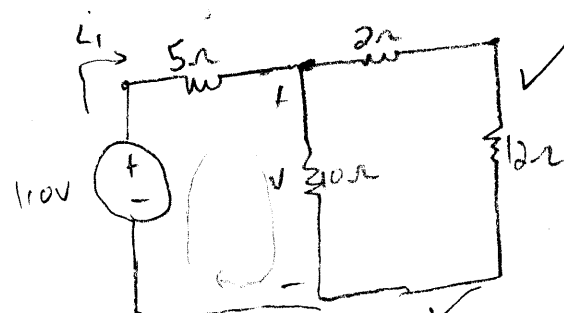

$110V + i_1(5\Omega) + v = 0$
 $i_1 = \frac{110}{5} = 22A$
 $\Rightarrow 110V + 22(5\Omega) = 220V$
how did you get 20V? - 2.5

Can't transform with 5Ω

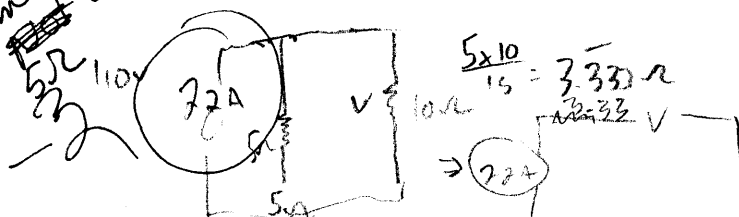

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

MESH 1

$V_1 = 5 \text{ mA} \times 2 \text{ k}\Omega = 10 \text{ V}$ what's V_1 ? ~~10V~~

MESH 2

$40 \text{ V} + 2 \text{ k}\Omega (5 \text{ mA}) = 4 \text{ k}\Omega (V_x)$

MESH 3

$-20 \text{ V} + 8 \text{ k}\Omega (i_x) = V_x$ OK Not standard form.

(c) Solve your equations for v_x and i_x .


$v_x = 12.5 \text{ V}$
 $i_x = 4.065 \text{ mA}$

FOR $v_x = 40 \text{ V} + 10 \text{ V} = 4 \text{ k}\Omega (v_x)$
 $\Rightarrow v_x = 12.5 \text{ V}$

FOR $i_x \Rightarrow -20 \text{ V} + 8 \text{ k}\Omega (i_x) = 12.5 \text{ V}$

$\Rightarrow 8 \text{ k}\Omega (i_x) = 32.5 \text{ V}$

$\Rightarrow i_x = 4.065 \text{ mA}$

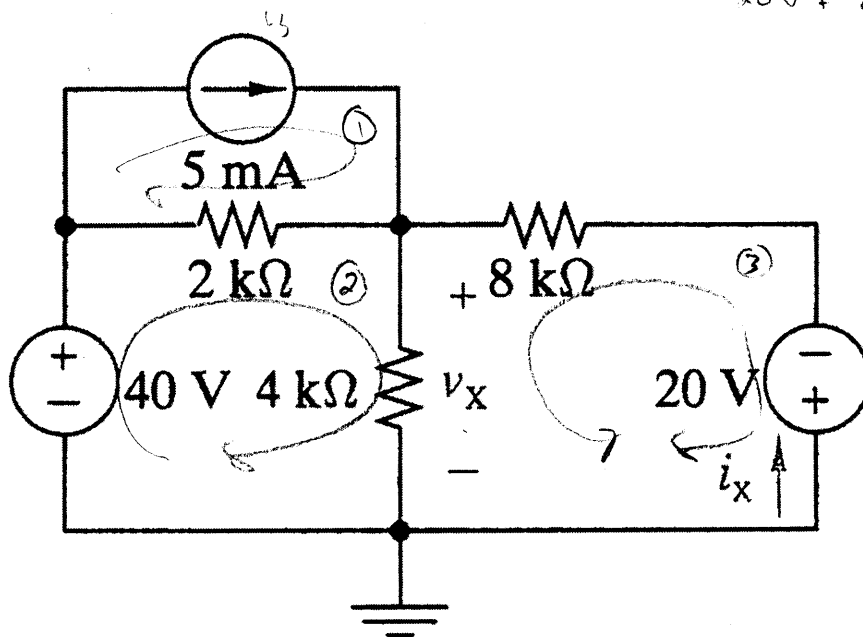

Name: Kate MooreSection: TACWRU e-mail: KXM99**CASE WESTERN RESERVE UNIVERSITY**

Case School of Engineering

Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)**MAKE-UP QUIZ 1****3/1/05****PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS**


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source


$$V_{4A} = \underline{-24} \text{ volts}$$

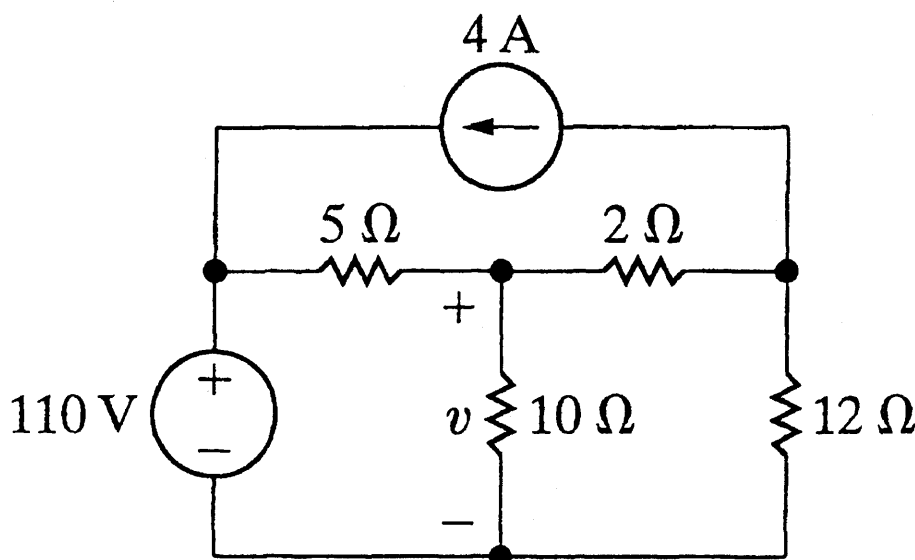b. find the contribution to v from the 110V voltage source

$$V_{110V} = \underline{59.23} \text{ volts}$$



$$\frac{9.8}{10}$$

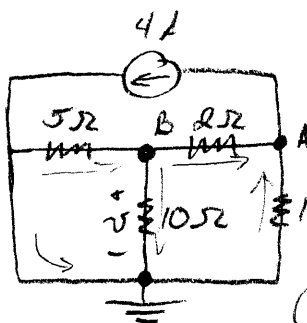

$$\frac{A}{2.5\Omega} + \frac{A-0}{12.5\Omega} = 4A \checkmark$$

$$\frac{B}{2\Omega} - \frac{A}{2\Omega} + \frac{A}{12\Omega} = 4A$$

$$-\frac{5}{12\Omega} A + \frac{B}{2\Omega} = 4A_{mp}$$

 $\frac{6}{5}$

$$\frac{B}{0.5\Omega} - \frac{B-0}{10\Omega} - \frac{B-A}{2\Omega} = 0$$

$$\frac{2B}{10.5\Omega} - \frac{1B}{10\Omega} - \frac{5B}{10.25\Omega} + \frac{A}{2\Omega} = 0$$

$$\frac{1}{2.5\Omega} A - \frac{8}{5\Omega} B = 0$$

$$-\frac{1}{2.5\Omega} A + \frac{3}{5} B = 4.8A_{mp}$$

$$-\frac{1}{5\Omega} B = 4.8A_{mp}$$

$$B = 5 \quad / \quad B = -24V = 25$$

math error
-0.2

$$2c) \quad -i_A(6k\Omega) + i_B(18k\Omega) - i_C(12k\Omega) = -120V \quad / \quad i_A = 5mA$$

$$i_B(18k\Omega) - i_C(12k\Omega) = -90V$$

$$-i_B(4k\Omega) + i_C(12k\Omega) = -20V$$

$$i_B(14k\Omega) = -110V$$

$$i_B = 7.86mA$$

$$-(7.86mA)(4k\Omega) + i_C(12k\Omega) = -20V$$

$$i_C = .95mA$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source




$V_{4A} = \underline{8.21}$ volts

b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.23}$ volts

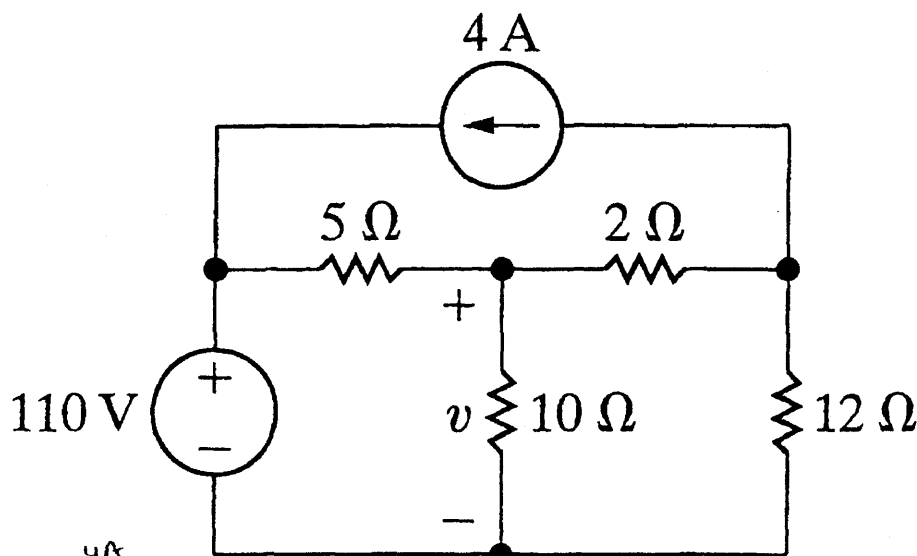




$\frac{9}{10}$

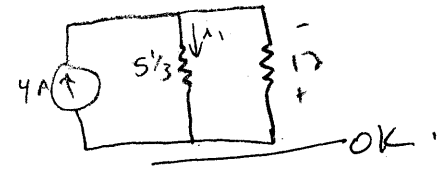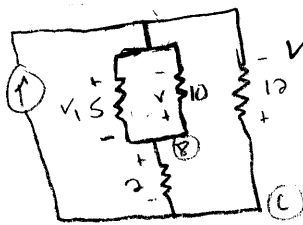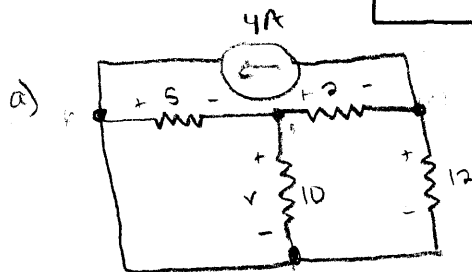

$$I_1 = \frac{5\frac{1}{3}}{5\frac{1}{3} + 12} 4 = 1.23 \text{ A}$$

$$I_2 = \frac{10}{5 + 10} 1.23 = 0.821 \text{ A}$$

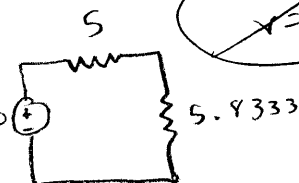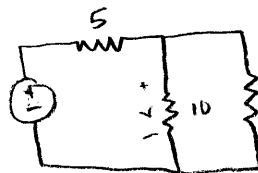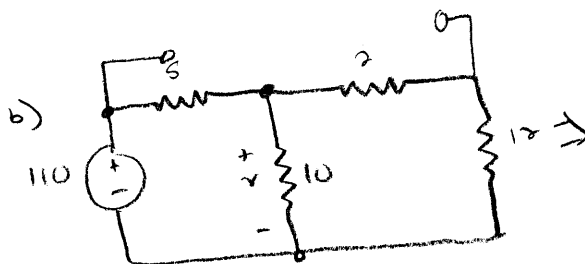$V = I_2 R = 0.821(10)$
 $V = 8.21 \text{ V}$



$$V = \frac{5.8333}{5.8333 + 5} 110 = 59.23 \text{ V}$$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

(A) $i_A = 5 \text{ mA}$ ✓

(B) $-40 + 2k(i_B - i_A) + 4k(i_B - i_C) = 0$

$-2000i_A + 6000i_B - 4000i_C = 40$ ✓

(C) $4k(i_C - i_B) + 8k i_C - 20 = 0$

$-4000i_B + 12000i_C = 20$ ✓

$\frac{7}{10}$

(c) Solve your equations for v_x and i_x .

$v_x = 8.58 \text{ V}$

$i_x = 1.43 \text{ mA}$

$v_x = 4k(i_C - i_B)$

$i_x = i_C$

$-10 + 6000(3i_C - 0.005) - 4000i_C = 40$
 $14000i_C = 20$


$i_B = 3i_C - 0.005$

$i_C = 1.43 \text{ mA}$

$i_B = -0.714 \text{ mA}$

$v_x = 4000(1.43 \text{ mA} - (-0.714 \text{ mA}))$

$v_x = 8.58$

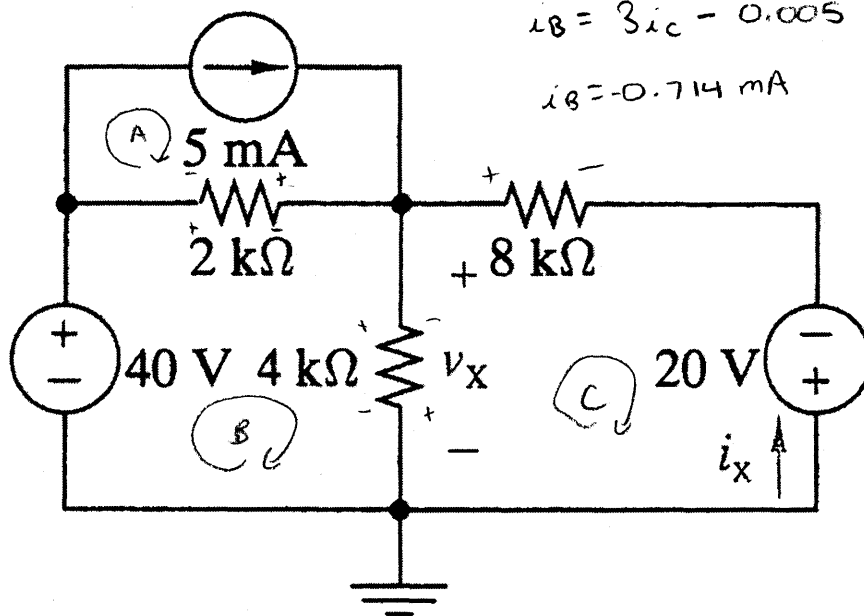

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{20}$ volts

b. find the contribution to v from the 110V voltage source



$V_{110V} = \underline{14V}$ volts

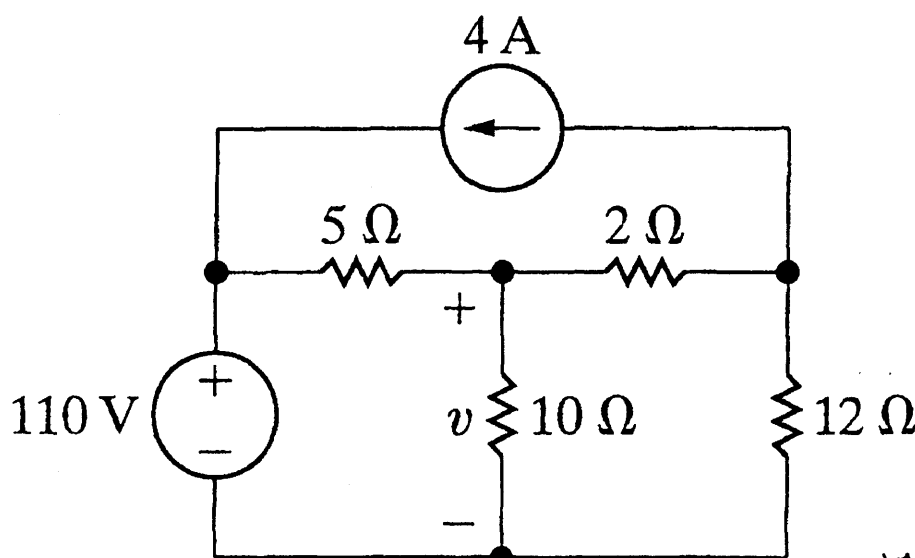

$\frac{6}{10}$




you can't get rid of the 5Ω resistor - 3

a)

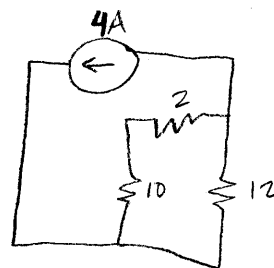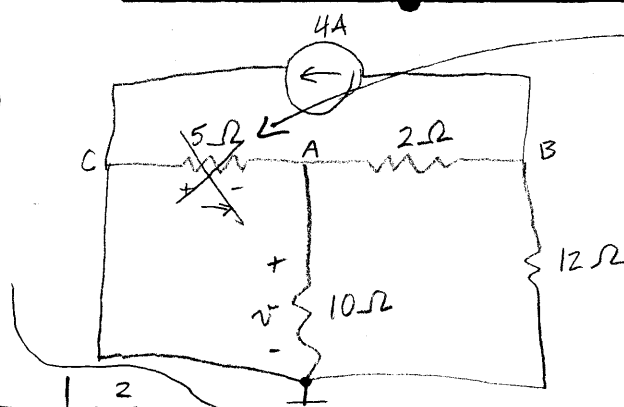

$\frac{10}{10+2} (24) = 20V$

b)

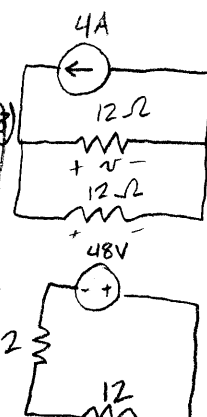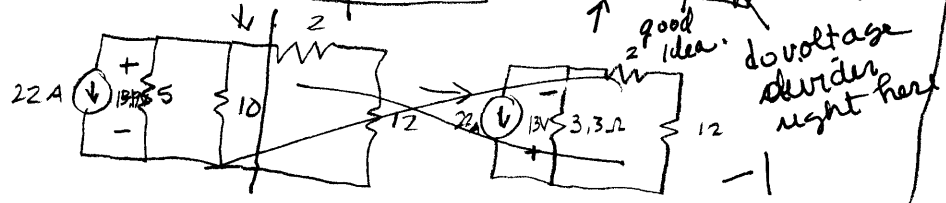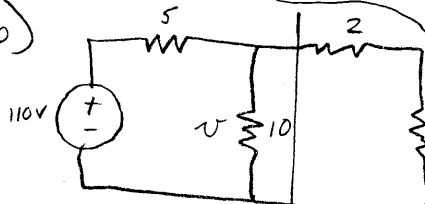

$\frac{12}{12+12} (48) = 24V$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 2X
- (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

~~$$-i_A(4k) + i_x(4k) - i_A(2k) = 30$$~~

~~$$i_x(8k) + i_x(4k) - i_A(4k) = -20$$~~

0
10

(c) Solve your equations for v_x and i_x .

$$v_x = \underline{25V}$$

$$i_x = \underline{4.29mA}$$

$$-6k i_A + 4k i_x = 30$$

$$-4k i_A + 12k i_x = -20$$

$$24k i_A - 16k i_x = -120$$

$$-24k i_A + 72k i_x = -120$$

$$56k i_x = -240$$

$$i_x = 4.29mA$$




$$-6k i_A + 4k(4.29mA) = 30$$

$$i_A = -2.14mA$$

$$v_x = (i_x - i_A) R$$

$$= (4.29 + 2.14) 4$$

$$= 25V$$

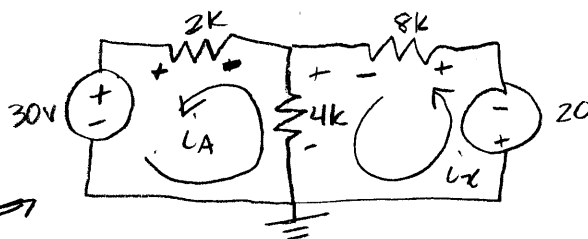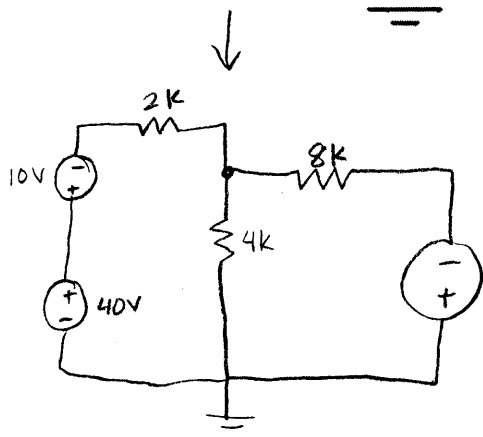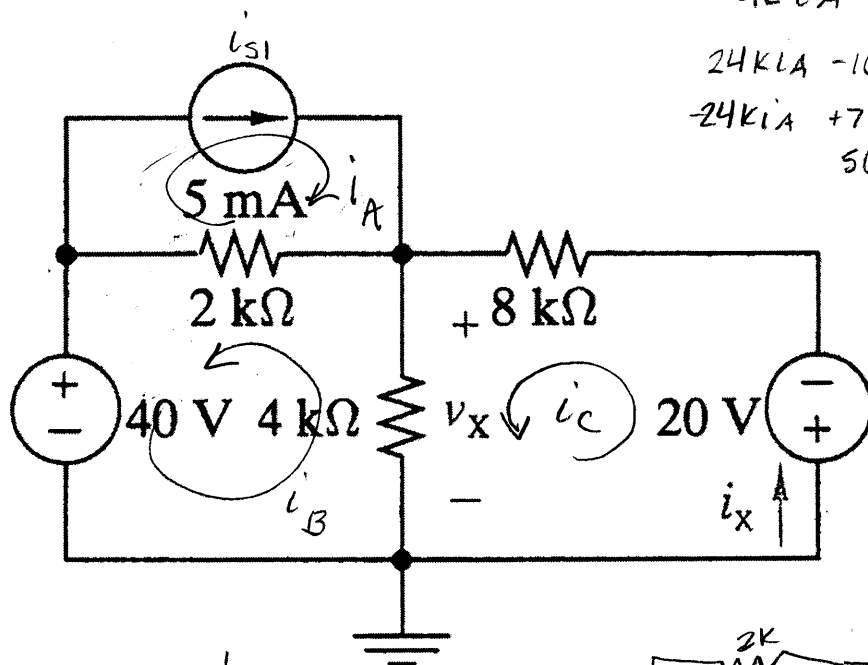

CASE WESTERN RESERVE UNIVERSITY

Case School of Engineering

Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS




1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$$V_{4A} = 7V \text{ volts}$$

b. find the contribution to v from the 110V voltage source

$$V_{110V} = 96.25V \text{ volts}$$

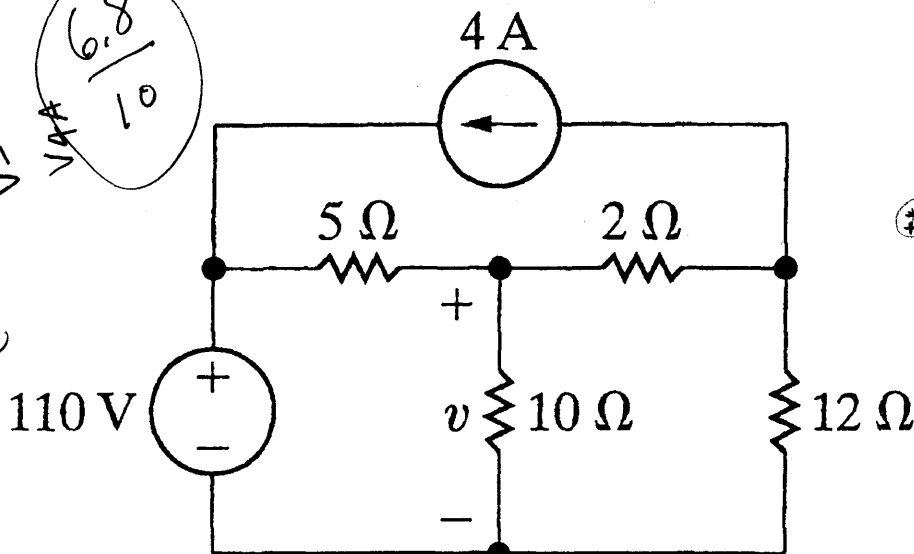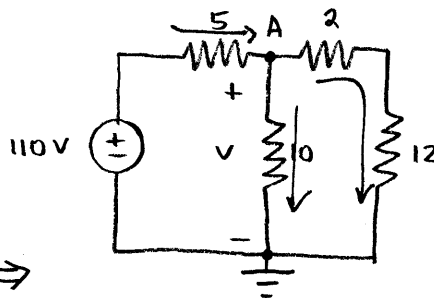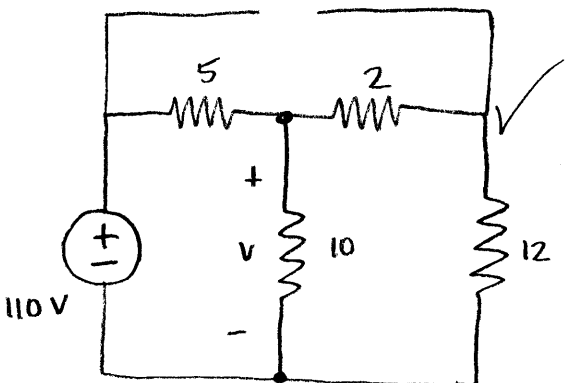 V_{110V} 

KCL A

$$\frac{110 - V_A}{5\Omega} - \frac{V_A}{10\Omega} - \frac{0 - V_A}{12\Omega} = 0$$

-0.2
sign backwards

$$22 - \frac{32}{140}V = 0$$

$$\left(\frac{140}{32}\right) \frac{32}{140}V = 22 \left(\frac{140}{32}\right)$$

$$V = 96.25V$$

$$\rightarrow V_{110V}$$

$$-\frac{1}{5}V - \frac{1}{10}V + \frac{1}{14}V \rightarrow -\frac{28}{140} - \frac{14}{140} + \frac{10}{140}$$


$$\frac{110 - V}{5} - \frac{V}{10} + \frac{V}{14} = 0$$

$$\frac{110}{5} - \frac{28V}{140} - \frac{14V}{140} + \frac{V}{140} = 0$$



$$V = 96.25V$$

$$\rightarrow V_{110V}$$

3/1/05

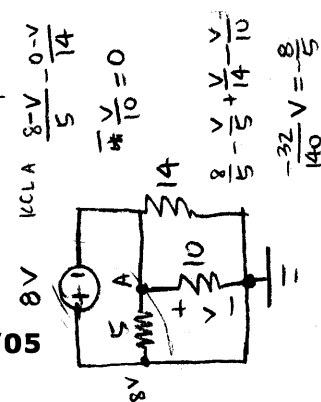

$$V = iR$$

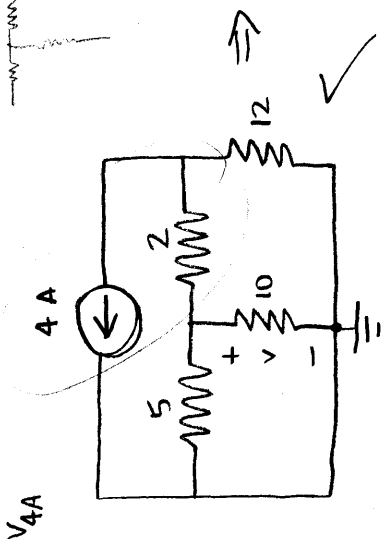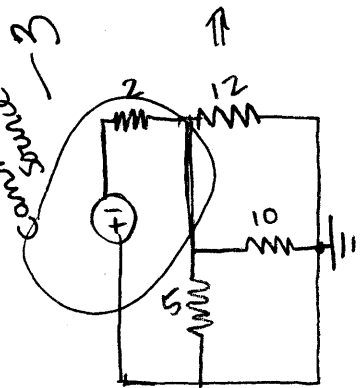

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 meshes ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

A $-40 + 2000(i_A - i_B) + 4000(i_A - i_C) = 0$

$$2000i_A - 2000i_B - 4000i_A + 4000i_C = 40$$

$$-2000i_A - 2000i_B + 4000i_C = 40$$

B $2000(i_B - i_A) = 0$

$$-2000i_A + 2000i_B = 0$$

C $-4000(i_C - i_A) + 8000i_C - 20 = 0 \rightarrow -4000i_C + 4000i_A + 8000i_C = 20$

$$4000i_A + 4000i_C = 20$$

(c) Solve your equations for v_x and i_x .

$$v_x = \underline{-20 \text{ V}}$$

$$i_x = \underline{0}$$

$$i_A = \frac{20 - 4000i_C}{4000}$$


$$i_A = 0.005 - i_C \rightarrow i_C = 0.005 - i_A$$

$$i_A = i_B = 0.005 \text{ A}$$

$$i_C = 0.005 - 0.005 = 0$$

$$i_C = 0 \therefore i_x = 0 \text{ V}$$

$$i_x = -i_C$$

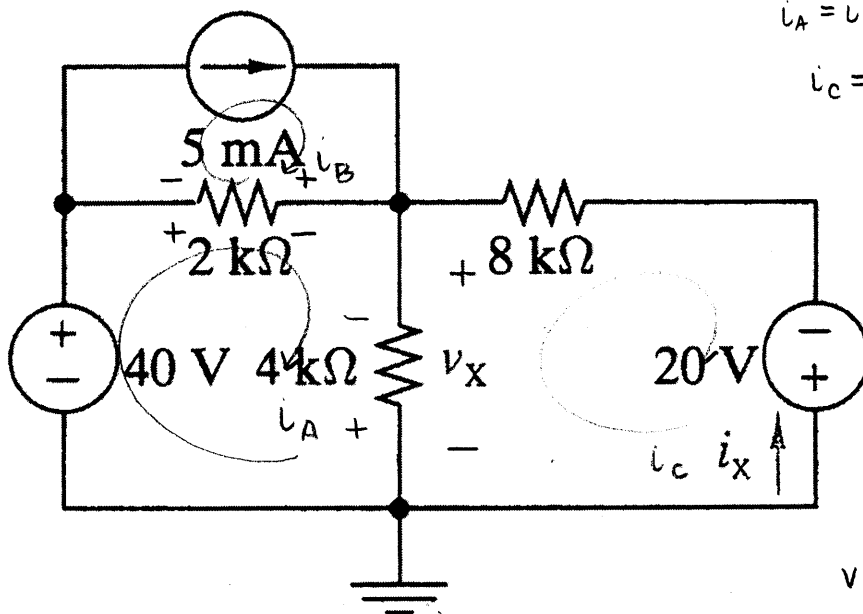

$$v = iR$$

$$v_x = (4000 \Omega)(-i_C - i_A)$$

$$v_x = (4000 \Omega)(0 - 0.005 \text{ A})$$

$$v_x = -20 \text{ V}$$

A $-40 \text{ V} + 2000(i_A - i_B) - 4000(i_A - i_C) = 0$

B $2000(i_B - i_A) = 0$

C $-4000(i_C - i_A) + 8000i_C - 20 = 0$

5/10

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS



1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$v_{4A} = \underline{10V}$ volts

b. find the contribution to v from the 110V voltage source

$v_{110V} = \underline{59.2V}$ volts

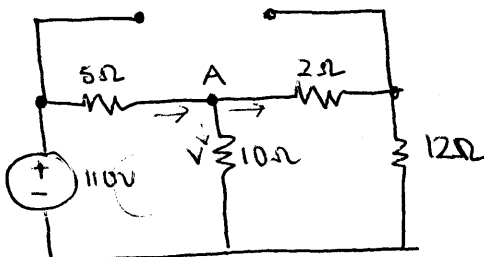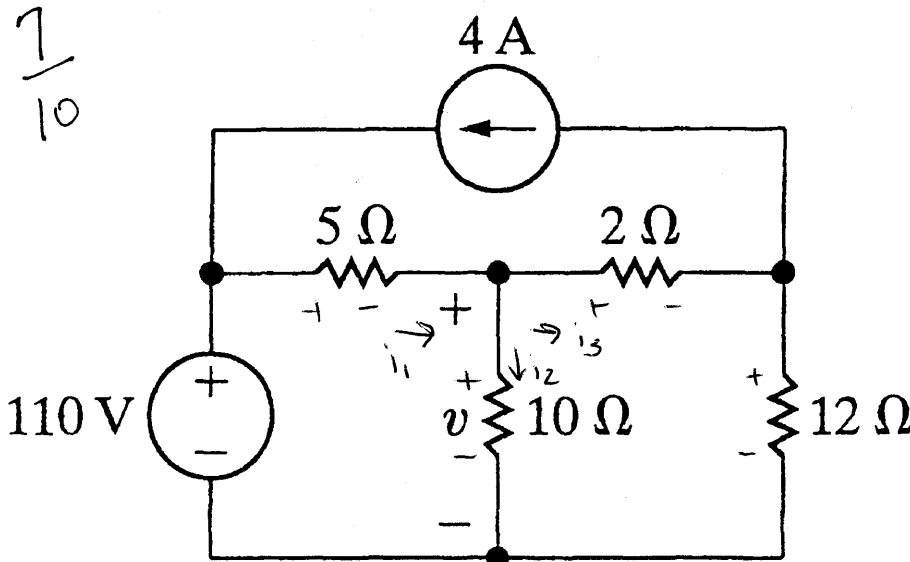

$$5\Omega i_1 + 10\Omega i_2 = 110V$$

$$2\Omega i_3 + 12\Omega i_3 = 10\Omega i_2$$

$$i_1 = i_2 + i_3$$

$$5\Omega (i_2 + i_3) + 10\Omega i_2 = 110V$$

$$15\Omega i_2 + 5\Omega i_3 = 110V$$

$$14\Omega i_3 = 10\Omega i_2$$


$$i_3 = \frac{10\Omega}{14\Omega} i_2$$

$$15\Omega i_2 + 5\left(\frac{10\Omega}{14\Omega}\right) i_2 = 110V$$

$$i_2 = 5.92A$$

$$10\Omega i_2 = v_{110V}$$

$$v_{110V} = 59.2V$$

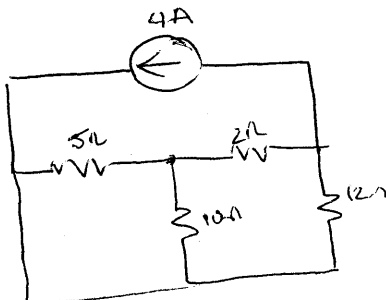

2. (10 points)

- (a) How many meshes are there in the circuit given below. 2
- (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

~~5mA~~ ~~2kΩ~~ ~~40V + (2kΩ)(5mA)~~

~~1: $40V + (2kΩ)(i_1 - i_3)$~~

~~(scrap sheet)~~

~~1: $-40V - 10V + 2kΩ i_1 + 4kΩ(i_1 - i_2) = 0$~~

~~2: $-20V - 4kΩ(i_2 - i_1) + 8kΩ(i_2) = 0$~~


~~$2ki_1 + V_x = 50V$~~

~~$V_x + 8kΩ i_x = 20V$~~

- (c) Solve your equations for v_x and i_x .



$v_x = \underline{40V}$

$i_x = \underline{2.5mA}$





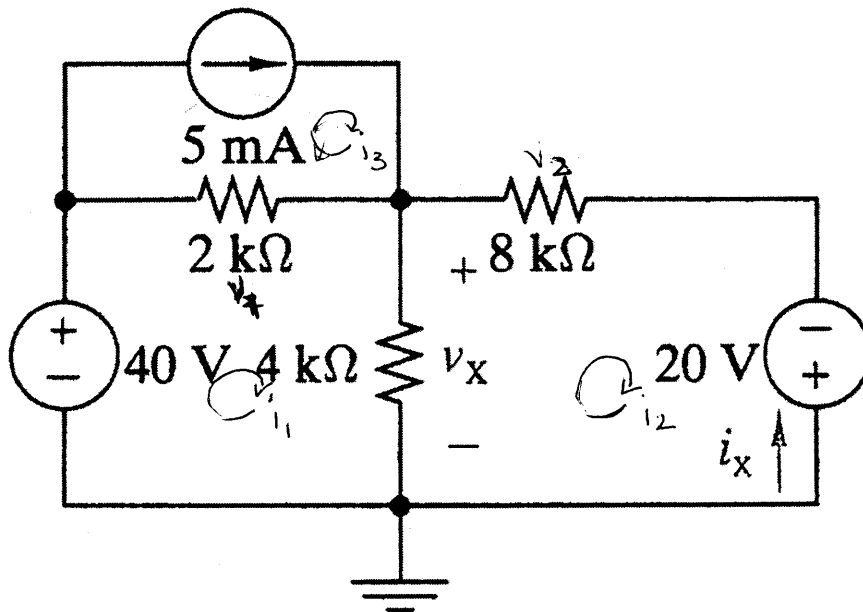


$i_2 = -i_x$ ✓

$4kΩ(i_1 - i_2) = v_x$ ✓

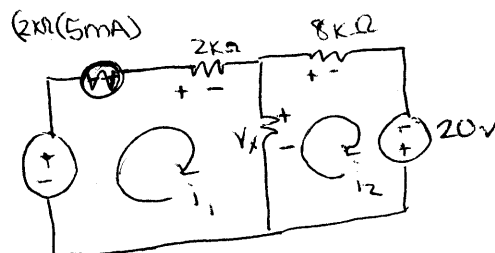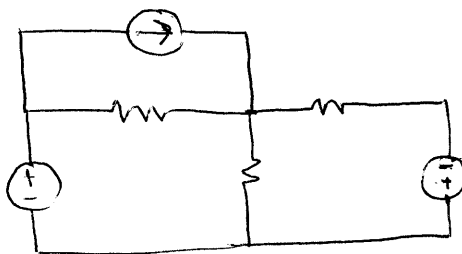

1.)

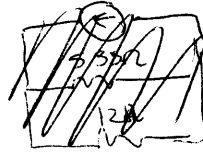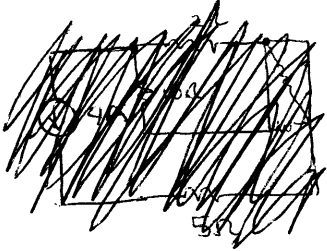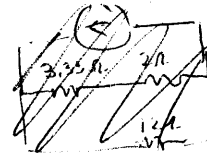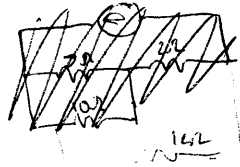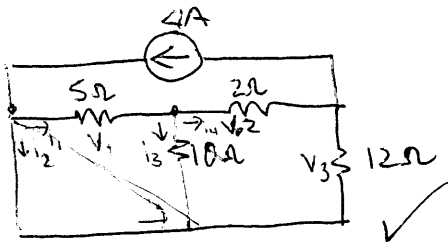

~~4A~~

$$V_1 = V$$

$$i_2 = i_4 + i_3$$

$$i_1 = i_4 + i_3$$

$$i_1 = i_2$$

$$i_1 + i_2 = 4A \quad i_1 = 2A$$

$$V_1 = (2A)(5\Omega)$$

$$V_{4A} = 10V$$

Not clear what you did to get V_{4A} .

- 3.

Jennifer Rischer
TA
jmr44

$$2.) -40V + 2k\Omega(i_1 - i_2) + 2k\Omega(i_1 - i_2) = 0 \checkmark$$
$$-2k\Omega(i_3 - i_1) = 0 \quad i_3 = 5mA$$
$$i_1 = 5mA$$

$$-20V + 4k\Omega(i_2 - i_1) + 8k\Omega(i_2) = 0 \checkmark$$

$$40V = 2k\Omega i_1 - 2k\Omega i_3 + V_x$$

$$V_x + 8k\Omega i_2 = 20V$$

$$i_3 = 5mA \checkmark$$

$$-2k\Omega(i_3 - i_1) = 0 \quad i_2 = -i_x$$
$$i_1 = 5mA$$

$$\frac{6.5}{10}$$

$$a) \quad 40V = 2k\Omega(5mA) - 2k\Omega(5mA) + V_x$$

$$V_x = 40V$$

$$V_x + 8k\Omega(-i_x) = 20V$$

$$V_x - 8i_x = 20V$$

$$V_x - 8i_x = 20V$$

$$20V = 8i_x \quad i_x = 2.5mA$$

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

MAKE-UP QUIZ 1

3/1/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE. BE SURE TO STATE ANY ASSUMPTIONS


1. (10 points) Using superposition

a. find the contribution to v from the 4A current source

$V_{4A} = \underline{10.4348}$ volts


b. find the contribution to v from the 110V voltage source

$V_{110V} = \underline{59.2308}$ volts


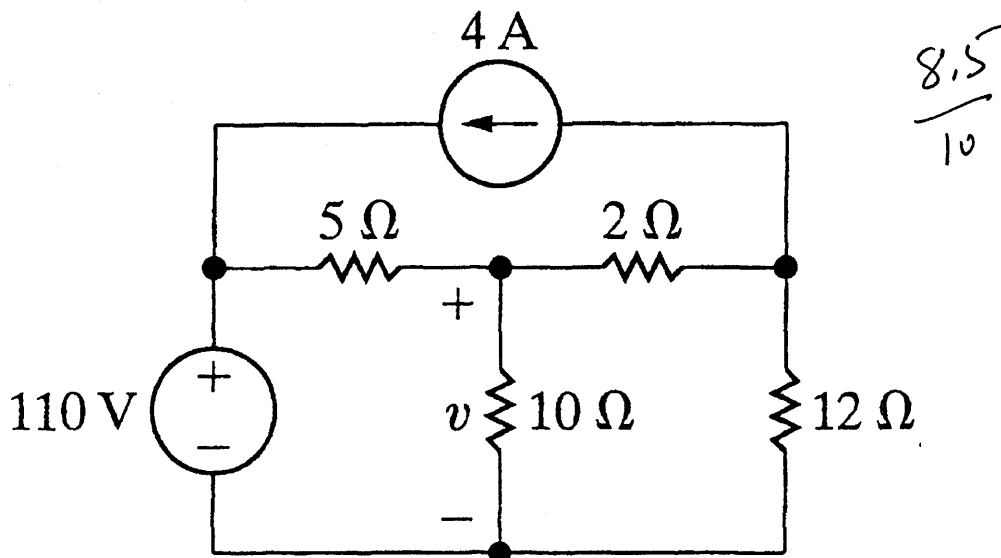


$\frac{8.5}{10}$

a)

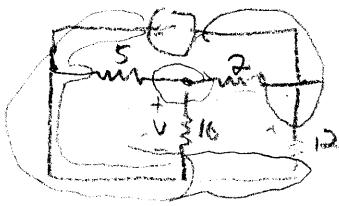

b)

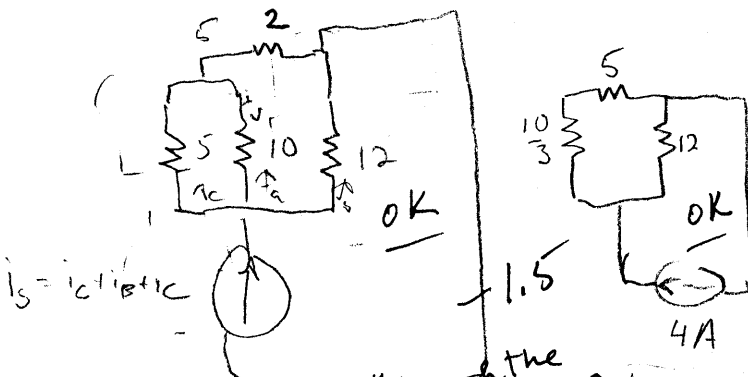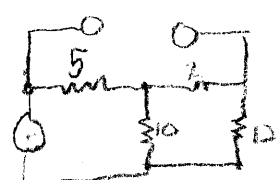

$i_o = \frac{1}{\frac{1}{5} + \frac{1}{10} + \frac{1}{14}} = 2.2$
 $i_o = 77/13$

You want the current through the 10Ω resistor = $\frac{1}{\frac{1}{5} + \frac{1}{10} + \frac{1}{14}} \cdot 4A = 10 \cdot \frac{24}{23}A$
 $V = i_o R \rightarrow V = \frac{24}{23} \cdot 10 = 10.4348V$
 $V_{10} = \frac{77}{13} \cdot 10\Omega$
 $V_1 = 59.2308V$

2. (10 points)

- (a) How many meshes are there in the circuit given below. 3 ✓
 (b) Write a complete set of mesh current equations for this circuit below. Put your equations into standard form.

$$I_C = 5 \text{ mA} \quad \checkmark$$

$$\text{Mesh C: } 2 \text{ k}\Omega (I_C - I_B) = 5 \text{ mA}$$

$$\text{Mesh B: } 2 \text{ k}\Omega (I_B - I_C) + 4 \text{ k}\Omega (I_B - I_A) - 40 = 0 \quad \checkmark$$

$$\text{Mesh A: } 4 \text{ k}\Omega (I_A - I_B) + 8 \text{ k}\Omega I_A - 20 = 0 \quad \checkmark$$

$$I_A = 15.714 \text{ mA}$$

$$I_B = 12.14 \text{ mA}$$

$$I_C = 5 \text{ mA}$$

$$\frac{7}{10}$$

- (c) Solve your equations for v_x and i_x .

$$v_x = \underline{25.716 \text{ V}}$$

$$i_x = \underline{-5.714 \text{ mA}}$$

$$v_x = (I_B - I_A) \cdot 4 \Omega$$

$$i_x = -I_A$$

$$v_x = (12.14 - 15.714) \cdot 4000$$

$$v_x = 25.716 \text{ V}$$

