
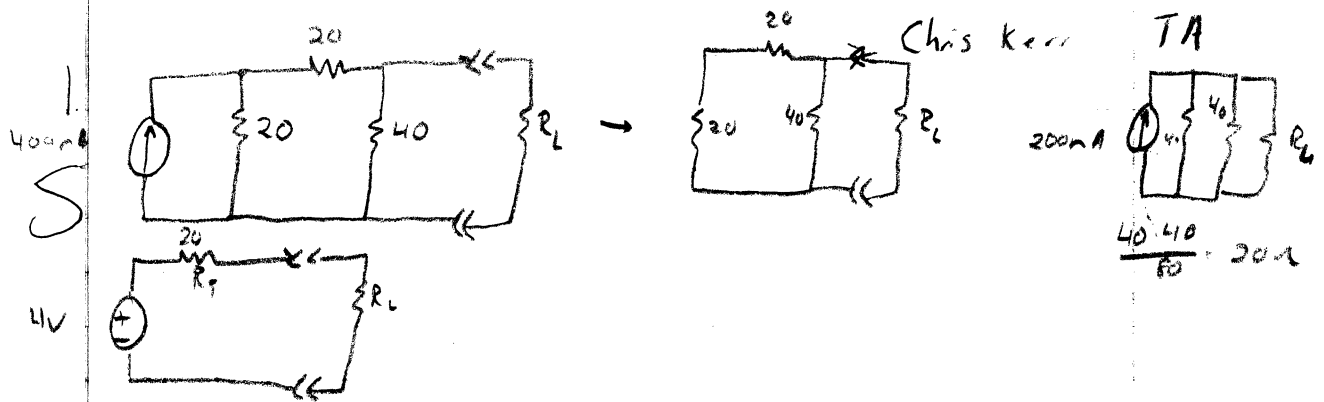


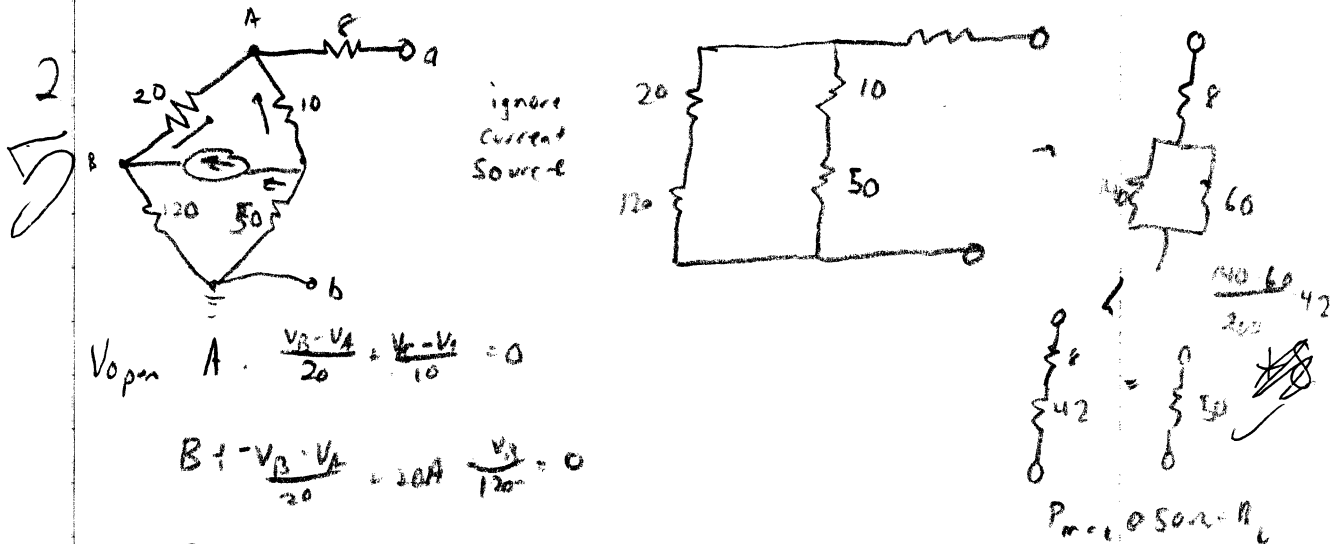

A. $R_T = R_L = 20\Omega$ $P_{max} = \frac{i_N^2 R_T}{4} = \frac{12^2 \cdot 20}{4} = 0.2W$

B. $R_L \rightarrow \infty$ $V_{max} = V_T = 4V$


C. $R_L = 0$ $i_{max} = \frac{V_T}{R_T} = \frac{4}{20} = 200mA$




$I_{sc} A. \frac{V_A - V_B}{20} = \frac{V_C - V_B}{10} - \frac{V_C}{8} = 0$

$V_A = 16/5$

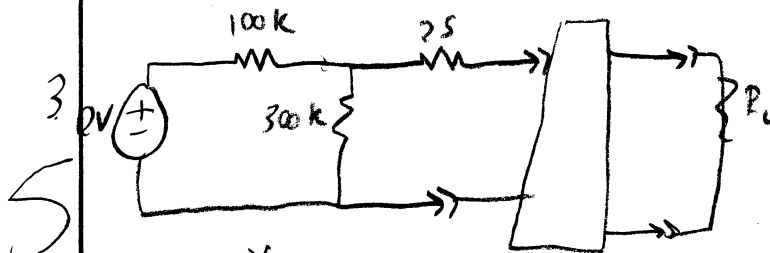$I_{sc} = \frac{V_A}{8} = \frac{16/5}{8} = .4A$ $P_{max} = \left(\frac{I_{sc}}{2}\right) \left(\frac{V_B}{2}\right) \left(\frac{1}{2}\right) \left(\frac{20}{2}\right) = 2W$


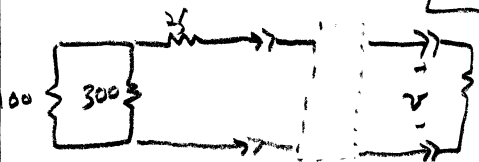
$$P_{max} = \left(\frac{V_{oc}}{2}\right) \left(\frac{I_{sc}}{2}\right) = 0.001 W$$




$$\frac{100 \cdot 360}{400} = 75 k\Omega$$

$$P_{max} = \frac{V_r^2}{4R} = \frac{9^2}{4(100)} \leq 0.001 W$$

$$2.025 \times 10^{-4} W \leq 0.001 W$$

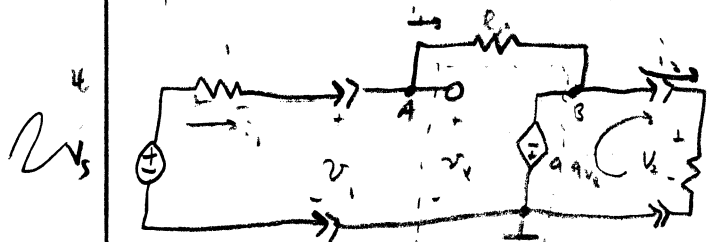- power is below indicated power resistor of value 0 will work.



$$i_1 = i_F \quad i_1 = \frac{V_5 - V_1}{1 k\Omega} = \frac{V_2 - V_1}{R_F} = F$$

$$V_B = V_2 \quad KVL @ 99V, +V_2 = 0$$

$$V_1 = -\frac{V_2}{99}$$

$$V_5 = 10mV$$

$$R_F = 10k\Omega$$

$$\frac{10mV + V_2/99}{1k\Omega} = \frac{-V_2/99 - V_2}{10k\Omega} \quad i_2 = V_2/1k$$

$$A \quad 10mV + V_2/99 = \frac{1}{10} \left(\frac{-10mV - V_2}{99} \right) = -10V/99$$

$$10mV = -110V_2/99$$

$$99V = -110V_2$$

$$\boxed{-9\mu V = V_2}$$


$$i_1 = \frac{10mV - 9\mu V/99}{1k\Omega} \approx 0.01mA$$

$$i_2 = \frac{-9\mu V}{1k\Omega} = -0.009mA$$

$$\boxed{i_2/i_1 = -0.9} \quad X$$

$$B. R_{in} = \frac{V_1}{i_1} = \frac{-V_2/99}{0.01mA} = \frac{9\mu V}{99} = 90\Omega \quad X$$

5

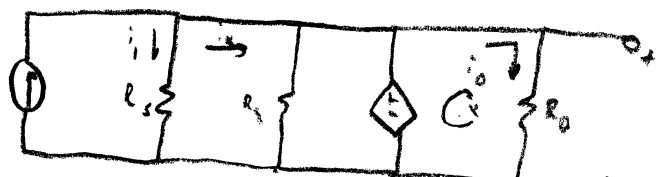


$$\begin{aligned} KVL: -v_s + i_o R_o &= 0 \\ i_s &= i_x + i_o \\ i_s &= v_s / R_s + i_o \end{aligned}$$

Gain i_o / i_s $i_o = \frac{R_s}{R_o} i_s$

$$\frac{i_o}{i_s} = \frac{R_s}{R_o} \frac{v_s / R_s + i_o}{i_s}$$

6

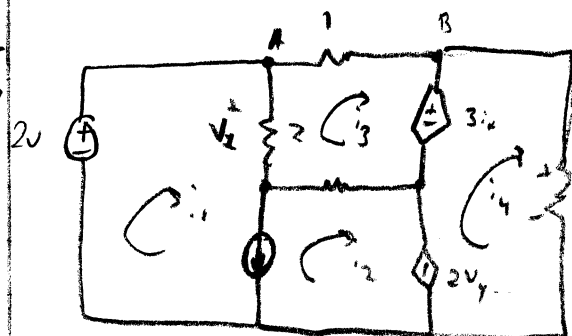

$$\begin{aligned} i_1 - i_2 &= 9A \quad V_y = i_1 - i_3 \\ 4 - i_2 &= 2V_y = 4(i_1 - i_3) \\ -4i_1 - i_2 + 4i_3 &= -4 \\ \text{Loop 4: } -x + i_3 + 2V_y &= 2 \\ i_y &= -i_e \end{aligned}$$

$$\begin{aligned} 2V_y - V_c &= -2(i_1 - i_3) + i_3 + 3i_x + 1(i_3 - i_1) = 0 \\ -2i_1 + 2i_3 + i_3 - 2 + 3i_x &= 0 \\ -2i_1 - i_2 + 4i_3 + 3i_x &= 0 \rightarrow 2i_1 - i_2 - 3i_4 = 0 \end{aligned}$$

$$\begin{aligned} 2i_1 - i_2 + 4i_3 - 3i_4 &= 0 \\ i_1 - i_2 &= 9 \\ -4i_1 - i_2 + 4i_3 + i_x &= 0 \\ i_3 + 2i_4 &= 2V \end{aligned}$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ -4 & -1 & 4 & 1 \\ 0 & 0 & 1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 9 \\ 0 \\ 2 \end{bmatrix}$$


$$\begin{aligned} i_1 &= 2 \\ i_2 &= -7 \\ i_3 &= 0 \\ i_4 &= 1 \end{aligned}$$

Node Voltage $V_B = 2V$
 $V_A = -2V = V_{s1}$
 $V_A - V_B = V_y$

$$V_B - 2V_B + 3V_A - \frac{1}{2}V_D = 0$$

$$\frac{1}{2}V_A - \frac{3}{2}V_B - V_C = 9$$

$$V_C - \frac{1}{2}V_D = 0$$

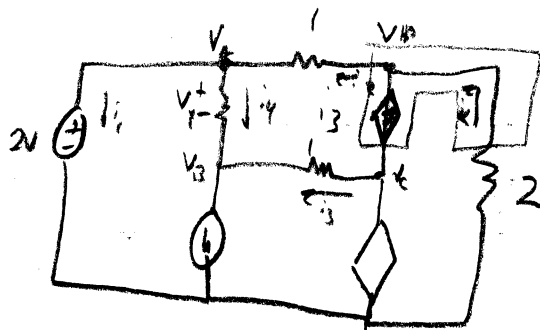

A. $-1(V_B - V_C) + 2(V_A - V_B) - \frac{1}{2}V_D = 1(V_A - V_B)$

B. $\frac{1}{2}(V_A - V_B) = 9 + 1(V_B - V_C)$

C. $V_D = V_C + 3V$

$i_x = V_D/2$ $V_D = V_C + \frac{3}{2}V_B$

$$V_B - V_C + 2V_A - 2V_B - \frac{1}{2}V_D + V_A - V_B = 0$$

$$2V_A + V_A - V_B - 2V_B + V - \frac{3}{2}V_B = 0$$

A. $3V_A - 3V_B + V_C - \frac{3}{2}V_D = 0$

$$-V_B - \frac{1}{2}V_D = -6$$

$$-3\frac{1}{2}V_B = V_C = 9$$

$$V_C - \frac{1}{2}V_D = 0$$

$$V_C = 20 \quad V_B = -2V$$

$$V_B = 40V \quad V_C = 34$$

$$i_x = -20A \quad V_D = 68$$

B. $\frac{1}{2}V_A - \frac{1}{2}V_B - V_B + V_C = 9$

$\frac{1}{2}V_A - \frac{3}{2}V_B + V_C = 9$

C. $V_D - \frac{3}{2}V_D - V_C = 0$

$-\frac{1}{2}V_D - V_C = 0$

A. $-6 = 3V_B - V_C + \frac{3}{2}V_D$

B. $-8 = \frac{3}{2}V_B - V_C$

C. $0 = -\frac{1}{2}V_D - V_C$

$i_x = 1A$




$$\begin{bmatrix} 3 & -1 & 1.5 \\ 3/2 & -1 & 0 \\ 0 & -1 & -1.5 \end{bmatrix} \begin{bmatrix} V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} -6 \\ -8 \\ 0 \end{bmatrix}$$

$$V_B = 8.66V$$


$$V_C = 5V$$

$$V_D = -10V$$

(2)

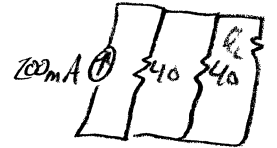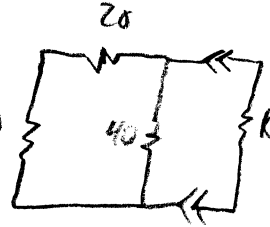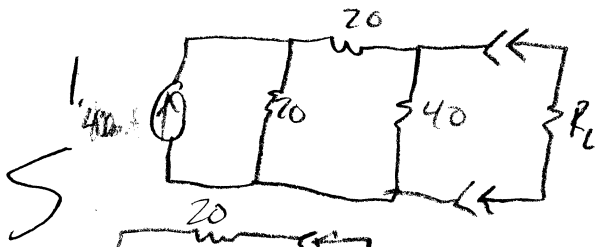

$$\frac{40 \cdot 40}{80} = 20 \Omega$$

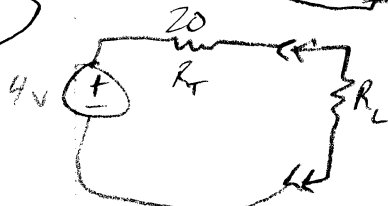


A) $R_T = R_L = 20 \Omega$

$$P_{max} = \frac{I_N^2 R_T}{4} = \frac{(0.2)^2 20}{4} = 0.2 W$$




B) $R_L \rightarrow \infty \quad V_{max} = V_T = 4V$

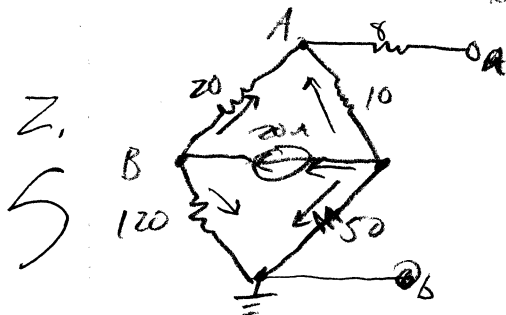
C) $R_L = 0 \quad I_{max} = \frac{V_T}{R_T} = \frac{4}{20} = 200mA$



ignore
current
source

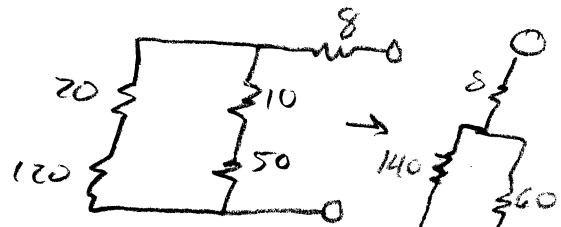

$$\frac{140 \cdot 60}{200} = 42$$

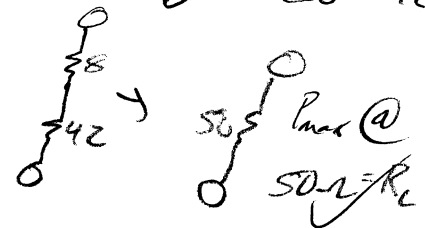

Node A: $\frac{V_B - V_A}{20} + \frac{V_C - V_A}{10} = 0$

Node B: $-\frac{V_B - V_A}{20} + 20A - \frac{V_B}{120} = 0$

Node C: $-\frac{V_C - V_A}{10} - \frac{V_C}{50} - 20A = 0$

Mathematica

$$V_A = 20V - V_C$$


$$V_B = 360V$$

$$V_C = -150V$$



(I_{sc}) Node A: $\frac{V_B - V_A}{20} + \frac{V_C - V_A}{10} - \frac{V_A}{5} = 0$
 $V_A = \frac{16}{5} V$

$$I_{sc} = \frac{V_A}{5} = \frac{16}{5} = 3.2A$$

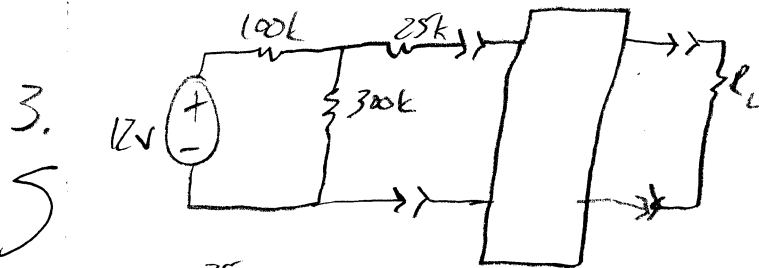
$$P_{max} = \left(\frac{I_{sc}}{2}\right) \left(\frac{V_{oc}}{2}\right) = \left(\frac{3.2}{2}\right) \left(\frac{20}{2}\right) = 2W$$


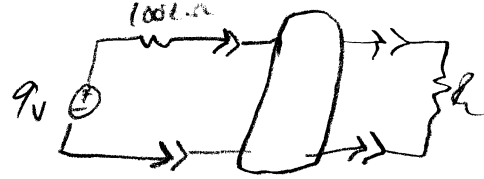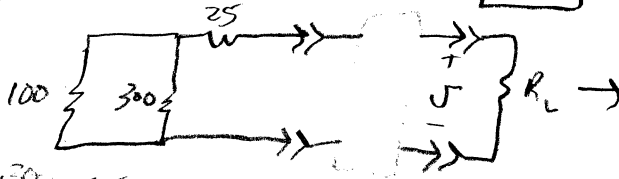
$$P_{max} = \left(\frac{V_{oc}}{2}\right) \left(\frac{I_{sc}}{2}\right) < .001W$$



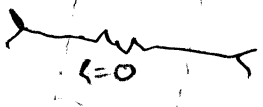
$$\frac{100 \cdot 300}{400} = 75k\Omega$$



$$P_{max} = \frac{V_T^2}{4R_T} = \frac{9^2}{4(100k)} \leq .001W$$

$$2.025 \times 10^{-4} W \leq 1 \times 10^{-3} W$$

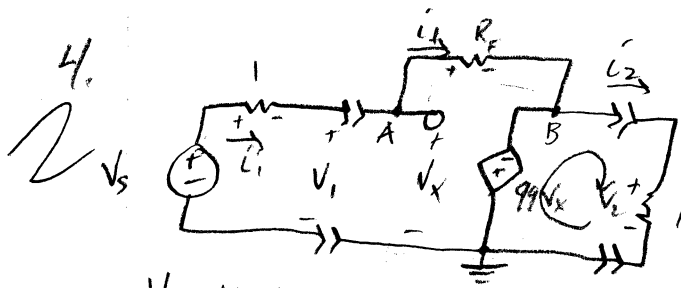Max power is below specified power so resistor with resistance of 0 works.



$$I_1 = I_F \quad I_1 = \frac{V - V_x}{1k\Omega} = \frac{V_x - V_S}{R_F} = I_F$$

$$V_B = V_x \quad KVL \text{ on } 99k\Omega: 99V_x + V_2 = 0$$

$$V_x = \frac{-V_2}{99}$$

$$V_S = 10mV$$

$$R_F = 10k\Omega$$

$$\frac{10mV + \frac{V_2}{99}}{1k\Omega} = \frac{-\frac{V_2}{99} - V_2}{10k\Omega}$$

$$I_2 = \frac{V_2}{1k}$$

A) $10mV + \frac{V_2}{99} = \frac{1}{10} \left(\frac{-100V_2}{99} \right) = \frac{-10V_2}{99}$

$$10mV = \frac{-110V_2}{99}$$

$$.99V = -110V_2$$


$$\boxed{-9mV = V_2}$$

$$I_1 = \frac{10mV - \frac{-9mV}{99}}{1k\Omega} \approx 0.01mA$$

$$I_2 = \frac{-9mV}{1k\Omega} = -0.009mA$$

$$\boxed{I_2/I_1 = -0.9} \quad X$$

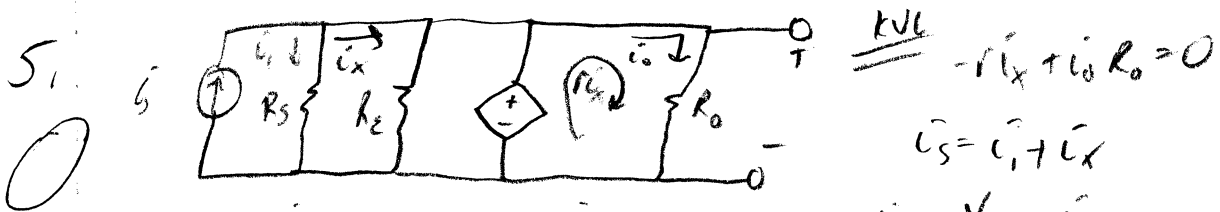B) $R_{in} = \frac{V_1}{I_1} = \frac{-V_2}{.01mA} = \frac{9mV}{.01mA} \approx \boxed{9.09k\Omega} \quad X$




$$g_{adn} = \frac{i_o}{i_s}$$

$$i_o = \frac{V_o}{R_o}$$

$$i_s = \frac{V_o}{R_s} + i_x$$
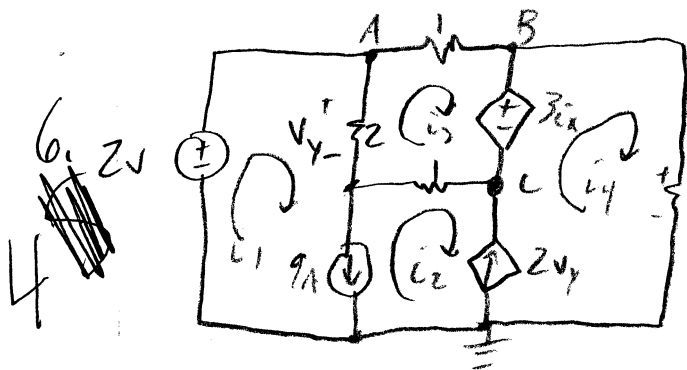
$$\frac{i_o}{i_s} = \frac{\frac{V_o}{R_o}}{\frac{V_o}{R_s} + i_x}$$



$$i_1 - i_2 = 9A$$

$$V_y = i_1 - i_3$$

$$i_4 - i_2 - 2V_y = 4(i_1 - i_3)^2$$

$$-4i_1 - i_2 + 4i_3 + i_4 = 0$$

$$\text{Loop A: } -1 + i_3 + 2i_4 = 2$$

$$i_x = -i_x$$

$$2V_y = V_c$$

$$-2(i_1 - i_3) + 1i_3 + 3i_x + 1(i_3 - i_2) = 0$$

$$-2i_1 + 2i_3 + 2i_3 - i_2 + 3i_x = 0$$

$$-2i_1 - i_2 + 4i_3 + 3i_x = 0 \rightarrow 2i_1 - i_2 - 3i_4 = 0$$

$$\begin{cases} 2i_1 - i_2 + 4i_3 - 3i_4 = 0 \\ i_1 - i_2 = 9 \\ -4i_1 - i_2 + 4i_3 + i_4 = 0 \\ i_3 + 2i_4 = 2V \end{cases}$$

$$\begin{bmatrix} 1 & -1 & 0 & 0 \\ -4 & -1 & 4 & 1 \\ 0 & 0 & 1 & 2 \\ -2 & -1 & 4 & -3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 9 \\ 0 \\ 2 \end{bmatrix}$$

$$i_1 = 2$$

$$i_2 = -7$$

$$i_3 = 0$$

$$i_4 = 1$$

Node Voltage $V_B = 2i_x$

$$V_A = -2V = V_B$$

$$V_A - V_B = V_Y$$

$$V_B - 2V_B + 3V_A - \frac{1}{2}V_D = 0$$

$$\frac{1}{2}V_A - \frac{3}{2}V_B - V_C = 9$$

$$V_C - \frac{1}{2}V_D = 0$$

$$-V_D - \frac{1}{2}V_D = -6$$

$$-\frac{3}{2}V_B - V_C = 8$$

$$V_C - 1.5V_D = 0$$

$$V_C = 20V \quad V_B = -28$$

$$V_A = -40V \quad V_C = 34$$

$$i_x = -20A \quad V_D = 68$$

$$\textcircled{B} \quad \frac{1}{2}V_A - \frac{1}{2}V_B - V_B + V_C = 9$$

$$\left[\frac{1}{2}V_A - \frac{3}{2}V_B + V_C = 9 \right]$$

$$\textcircled{A} \quad -6 = 3V_B - V_C + \frac{3}{2}V_D$$

$$\textcircled{A} \quad -8 = \frac{3}{2}V_B - V_C$$


$$\textcircled{C} \quad 0 = -\frac{1}{2}V_D - V_C$$

$$i_x = 7A$$

$$V_B = 8.667 \checkmark$$

$$V_C = 5V$$

$$V_D = -10V$$

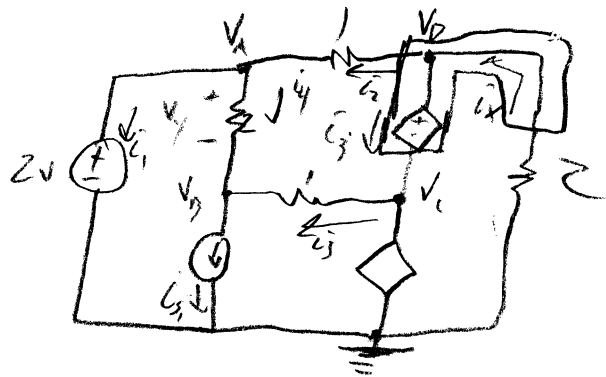

$$\textcircled{A} \quad -1(V_B - V_C) + 2(V_A - V_B) - \frac{1}{2}V_D + 1(V_A - V_B) = 0$$

$$\textcircled{B} \quad \frac{1}{2}(V_A - V_B) = 9 + 1(V_B - V_C)$$

$$\textcircled{C} \quad V_D = V_C + 3i_x$$

$$i_x = \frac{V_A}{2}$$

$$V_D = V_C + \frac{3}{2}V_A$$

$$V_B - V_C + 2V_A - 2V_B - \frac{1}{2}V_D + V_A - V_B = 0$$

$$2V_A + V_A - V_B - 2V_B + V - \frac{3}{2}V_D$$

$$\textcircled{A} \quad 3V_A - 3V_B + V_C - \frac{3}{2}V_D = 0$$

$$\textcircled{C} \quad V_D - \frac{3}{2}V_D - V_C = 0$$

$$\left[-\frac{1}{2}V_D - V_C = 0 \right]$$


$$\begin{bmatrix} 3 & -1 & 1.5 \\ \frac{3}{2} & -1 & 0 \\ 0 & -1 & -5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_D \end{bmatrix} = \begin{bmatrix} 6 \\ -8 \\ 0 \end{bmatrix}$$

$\frac{27}{30}$ Very Good


Engr 210

Danielle Henkel
2-23-05 WA


#1

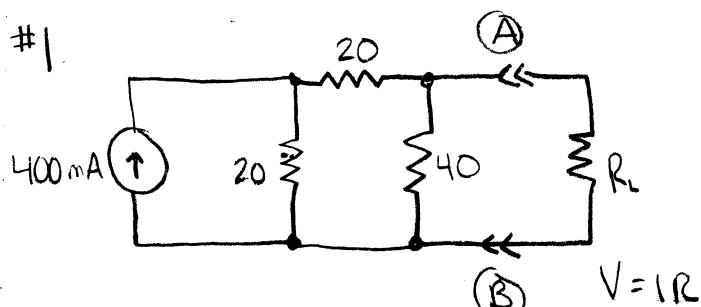

+5

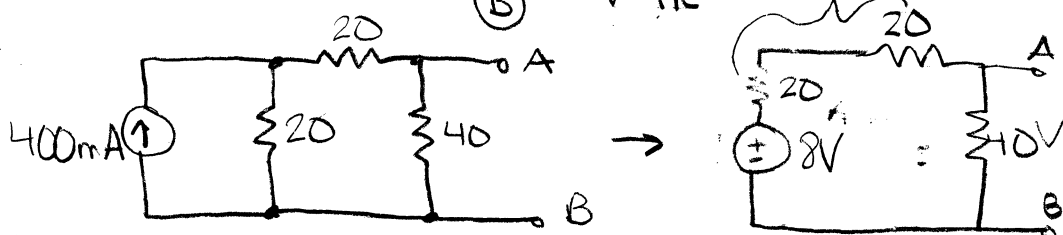



$I = V/R$

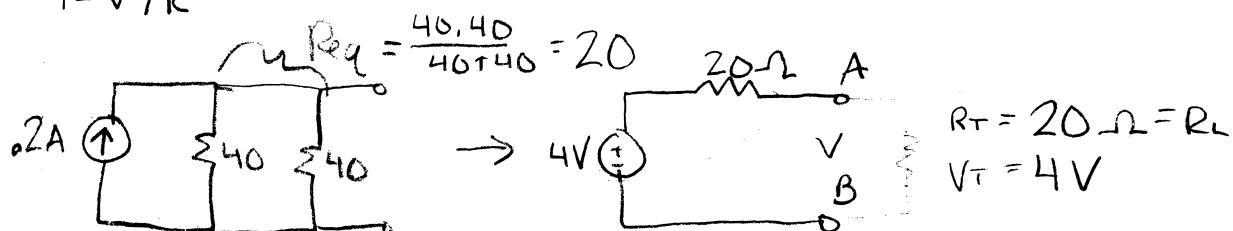


a) $P_{max} = \frac{V_T^2}{4R_T} = \frac{4^2}{4(20)} = .2 W$

b) V_{max} when $R_L = \infty$ so $V_{max} = V_{oc} = V_T = 4V$

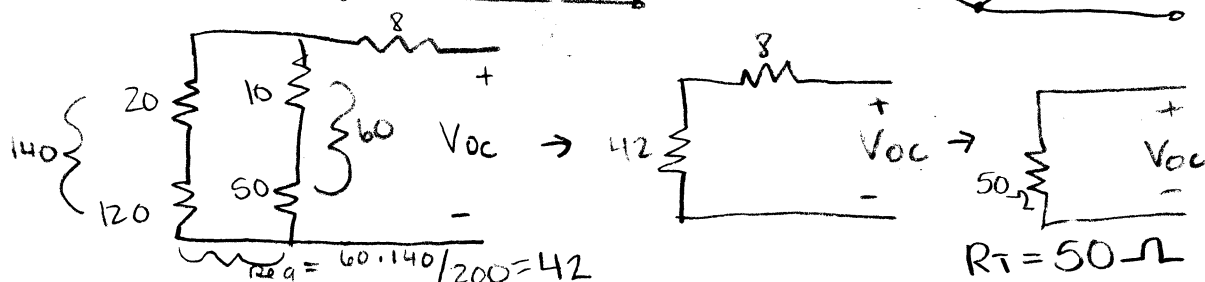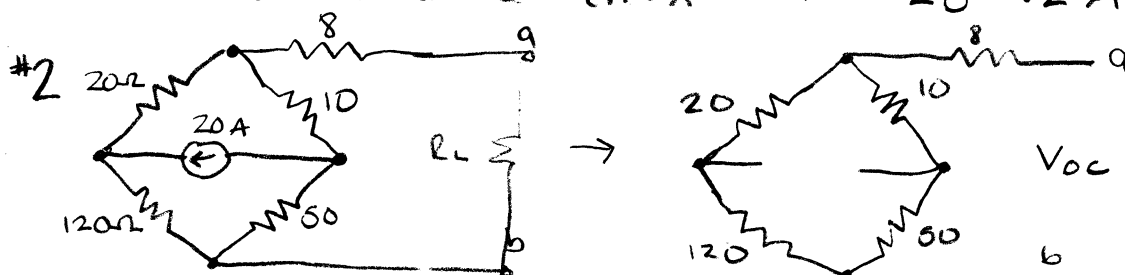c) i_{max} when $R_L = 0$ $i_{max} = \frac{V_T}{R_T} = \frac{4}{20} = .2 A$



44

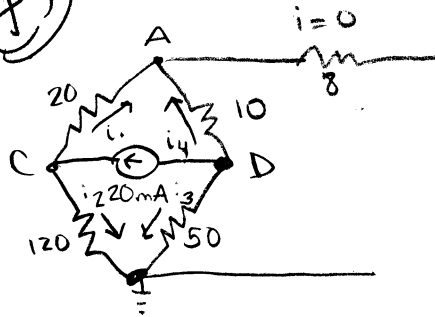

KCL:

$$A: i_1 + i_4 = 0$$

$$C: -i_1 - i_2 + i_3 = 0$$

$$D: -i_4 + i_3 - i_5 = 0$$

$$A: \frac{V_C - V_A}{20} + \frac{V_D - V_A}{10} = 0$$

$$\frac{V_C - V_A}{20} = -\frac{V_D - V_A}{10}$$

$$C: -\frac{(V_C - V_A)}{20} - \frac{V_C}{120} + 20\text{mA} = 0$$

$$V_C - V_A = -2V_D - 2V_A$$

$$V_C + V_A = V_D$$

$$D: -\frac{(V_D - V_A)}{10} - \frac{V_D}{50} - 20\text{mA} = 0$$

$$-20\text{mA} = \frac{V_D - V_A}{10} + \frac{V_D}{50}$$

$$-20\text{mA} = \frac{V_D}{10} - \frac{V_A}{10} + \frac{V_D}{50}$$

$$\frac{V_A}{10} - 20 = \frac{V_D}{10} + \frac{V_D}{50}$$

$$\frac{V_A}{10} - 20 = V_D \left(\frac{1}{10} + \frac{1}{50} \right)$$

$$\frac{V_A}{10} - 20 = .12 V_D$$

$$.1 V_A - 20 = V_D$$

$$\frac{5}{6} V_A - \frac{500}{3} = V_D = V_C + V_A$$

$$-\frac{1}{6} V_A - \frac{500}{3} = V_C$$

$$-\frac{V_A}{6} = V_C + \frac{500}{3}$$

$$-V_A = 6V_C + 1000$$

$$V_A = -6V_C - 1000$$

$$V_A = -6(.2V_D + 480) - 1000$$

$$V_A = -1.2V_D - 2880 - 1000$$

$$V_A = -1.2V_D - 3880$$

$$V_D = (-1.2V_D - 3880) + (.2V_D + 480)$$

$$V_D = -V_D - 3400$$


$$2V_D = -3400$$

$$V_D = -170V = V_{OC} = V_T \text{ OK}$$

$$P_{max} = \frac{V_T^2}{4R_T} = \frac{(-170)^2}{4(50)} = 44.5W$$


$$R_L = R_T = 50\Omega$$

15


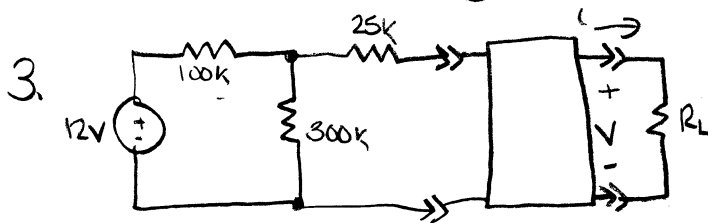


$$P < 1 \text{ mW}$$

$$I = \frac{V}{R}$$

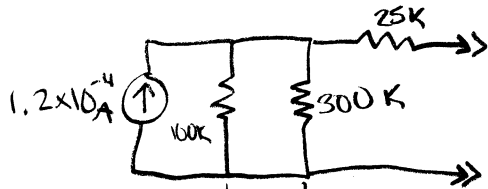
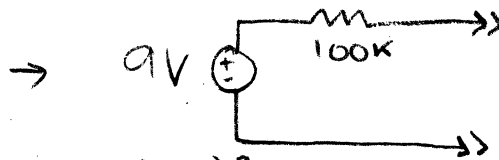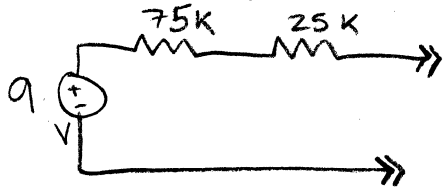
$$R_{eq} = \frac{100k \cdot 300k}{100k + 300k} = \frac{30000k}{400k} = 75k$$





$$R_T = 100k$$

$$V_T = 9V$$

$$\frac{V_T^2}{4R_T} = P_{max}$$

$$\frac{(9V)^2}{4(100k)} = 2.025 \times 10^{-4} W$$

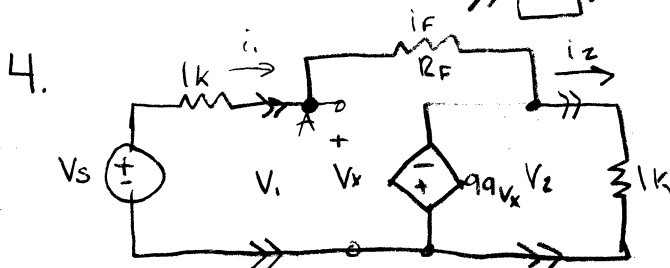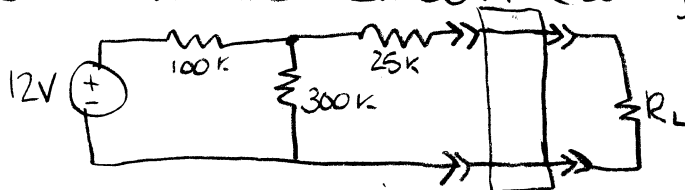$P_{max} = 2.025 \times 10^{-4} W$ is always less than 1mW
so interface circuit can just be two wires



$$i_1 = i_F$$

KVL right side:

$$99V_x + V_2 = 0$$

$$V_x = -\frac{V_2}{99}$$

a) $V_s = 10mV$ $R_F = 10k\Omega$

15

$$\frac{V_S - V_X}{1K} = \frac{V_X - V_Z}{R_F}$$

$$99V_X + V_Z = 0$$

$$V_X = -V_Z/99$$

$$\frac{V_S + (V_Z/99)}{1K} = \frac{-V_Z/99 - V_Z}{R_F}$$

$$V_S + \frac{V_Z}{99} = 1000 \left(\frac{-V_Z/99 - V_Z}{R_F} \right)$$

$$10\text{mV} + \frac{V_Z}{99} = \cancel{1000} \left(\frac{-V_Z/99 - V_Z}{10K} \right)$$

$$10\text{mV} + \frac{V_Z}{99} = \frac{-V_Z/99 - V_Z}{10}$$

$$100\text{mV} + \frac{10V_Z}{99} = \frac{-V_Z}{99} - V_Z$$

$$= -V_Z \left(\frac{1}{99} + 1 \right)$$

$$100\text{mV} + \frac{10V_Z}{99} = -V_Z (1.01)$$

$$100\text{mV} = -1.01V_Z - \frac{10V_Z}{99}$$

$$100\text{mV} = \left(-1.01 - \frac{10}{99} \right) V_Z$$

$$100\text{mV} = (-10/9) V_Z$$

$$\boxed{-0.09 = V_Z}$$


$$i_2 = \frac{V_Z}{1000\Omega} = \frac{-0.09}{1000\Omega} = -9 \times 10^{-5} \text{A}$$

$$i_1 = \frac{V_S - V_X}{1000\Omega} = \frac{10\text{mV} - 9.09 \times 10^{-4} \text{V}}{1000} = 9.091 \times 10^{-6}$$

$$\frac{i_2}{i_1} = \frac{-9 \times 10^{-5} \text{A}}{9.091 \times 10^{-6}} = \boxed{-9.899}$$

$$4b) R_{in} = \frac{V_1}{i_1} \quad V_1 = V_x = 9.09 \times 10^{-4} V$$
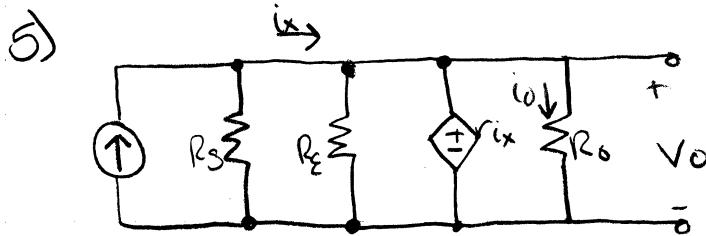
$$= \frac{9.09 \times 10^{-4} V}{9.091 \times 10^{-6} A} = \boxed{99.98952 \Omega}$$



$$i_{gain} = \frac{i_o}{i_s}$$

(X5)

$$\begin{aligned} i_s &= i_1 + i_x \\ i_1 &= V_o / R_s \end{aligned} \quad \left\} \quad i_s = V_o / R_s + i_x$$


$$\begin{aligned} V_o &= i_o R_o \\ -i_x + V_o &= 0 \\ -i_x + i_o R_o &= 0 \\ i_o R_o &= i_x \\ i_x &= \frac{i_o R_o}{r} \end{aligned}$$

$$i_s = \frac{V_o}{R_s} + \frac{i_o R_o}{r}$$

$$i_s = \frac{i_o R_o}{R_s} + \frac{i_o R_o}{r}$$

$$i_s = i_o \left(\frac{R_o}{R_s} + \frac{R_o}{r} \right) = \frac{R_o r}{R_s r} + \frac{R_o R_s}{R_s r}$$
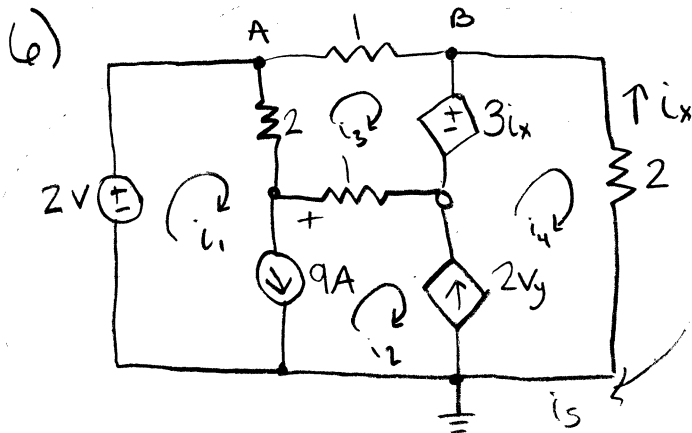
$$\boxed{i_o = i_s \left(\frac{R_s \cdot r}{R_o (r + R_s)} \right)}$$



(+3)

$$\begin{aligned} a) \quad i_1 - i_2 &= 9A \quad (1) \\ i_4 - i_2 &= 2V_4 \quad (2) \end{aligned}$$

$$i_x = -i_4$$

$$V_c + 3i_x = 2i_4 \quad V_c = 2i_4 - 3i_x$$

KVL:

$$(i_3 - i_1)2 + i_3 \cdot 1 + 3i_x + (i_3 - i_2)1 = 0 \quad (3)$$

$$-2 + i_3(1-2) + i_4(2) = 0 \quad (4)$$

$$2i_3 - 2i_1 + i_3 + 3i_x + i_3 - i_2 = 0$$

$$4i_3 - 2i_1 + 3i_x - i_2 = 0$$

$$4i_3 + 3i_x - 2i_1 - i_2 = 0$$

$$4i_3 + 3i_4 - 2i_1 - i_2 = 0$$

$$V_4 = (i_1 - i_3)R$$

$$i_4 - i_2 = 2(i_1 - i_3)2$$

$$i_4 - i_2 = 4i_1 - 4i_3$$

$$i_3 + 2i_4 = 2V \quad i_3 = 2V - 2i_4$$

$$i_1 = i_2 + 9A$$

$$i_4 + 4i_3 = 4i_1 + i_2$$

$$4i_3 = 3i_4 + 2i_1 + i_2$$

$$i_4 + 3i_4 + 2i_1 + i_2 = 4i_1 + i_2$$

$$4i_4 = 2i_1$$

$$2i_4 = i_1$$

$$4i_3 = 3i_4 + 4i_4 + i_2$$

$$4i_3 = 7i_4 + i_2$$

$$4(2V - 2i_4) = 7i_4 + i_2$$

$$8V - 8i_4 = 7i_4 + i_2$$

$$8V = 15i_4 + i_2$$

$$i_3 + 2i_4 = 2$$

$$i_1 - i_2 = 9$$

$$4i_1 + i_2 - 4i_3 - i_4 = 0$$

$$2i_1 + i_2 - 4i_3 + 3i_4 = 0$$

$$i_1 = 2A$$

$$i_2 = -7$$

$$i_3 = 0$$

$$i_4 = 1$$

$$\begin{bmatrix} 0 & 0 & 1 & 2 \\ 1 & -1 & 0 & 0 \\ 4 & 1 & -4 & -1 \\ 2 & 1 & -4 & 3 \end{bmatrix}$$

A

$$\begin{bmatrix} 2 \\ 9 \\ 0 \\ 0 \end{bmatrix}$$

B

$$A^{-1}B = \text{Ans}$$

$$i_x = -1A$$


$$V_c = 2(1) - 3(-1)$$

$$V_c = 2 + 3 = 5V$$

b) $V_A = 2V$

$V_B = V_C + 3i_x$

$3i_x = V_B - V_C$

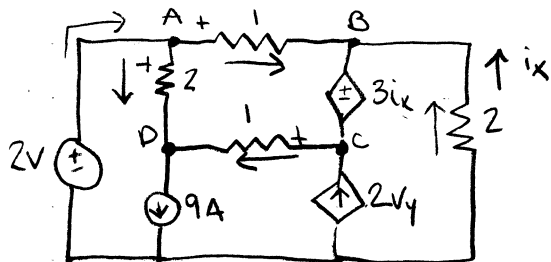

A: $(2 - V_A) - \frac{(V_A - V_D)}{2} - \frac{V_A - V_B}{1} = 0$

B: $3i_x + \frac{(V_A - V_B)}{1} + i_x = V_B - V_C + \frac{(V_A - V_B)}{1} + \frac{V_B - V_C}{3}$

C: $-3i_x - \frac{(V_C - V_D)}{1} + 2V_y = 0 = -(V_B - V_C) - \frac{(V_C - V_D)}{1} + \frac{2(V_A - V_B)}{2}$

D: $-9 + \frac{V_C - V_D}{1} + \frac{V_A - V_D}{2} = 0$

A: $2 - V_A - \frac{V_A}{2} + \frac{V_D}{2} - V_A + V_B = 0 \quad \frac{5}{2}V_A - V_B - \frac{V_D}{2} = 2$

B: $V_B - V_C + V_A - V_B + \frac{V_B}{3} - \frac{V_C}{3} = 0 \quad V_A + \frac{V_B}{3} - \frac{4}{3}V_C = 0$

C: $-V_B + V_C - V_C + V_D + V_A - V_D = 0 \quad V_A - V_B + V_D = 0$

D: $-9 + V_C - V_D + \frac{V_A}{2} - \frac{V_D}{2} = 0 \quad \frac{V_A}{2} + V_C - \frac{3}{2}V_D = 9$

$$\begin{bmatrix} 5/2 & -1 & 0 & -1/2 \\ 1 & 1/3 & -4/3 & 0 \\ 1 & -1 & 0 & 1 \\ 1/2 & 0 & 1 & -3/2 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \\ 9 \end{bmatrix} = \begin{bmatrix} 29/3 \\ 57/3 \\ 36/3 \\ 28 \end{bmatrix} \begin{matrix} V_A \\ V_B \\ V_C \\ V_D \end{matrix}$$

You said
 $V_A = 2V$
above.
✓

$V_C = V_A - V_B + V_D = 0$
 $= 29/3 - 57/3 + 28$
 $V_C = 0$


$3i_x = V_B - V_C$
 $57/3 - 36/3$
 $i_x = 7$

Very Nice!

27/30





Barbie Baran
2-23-05
Circuits WA

Circuits HW #6

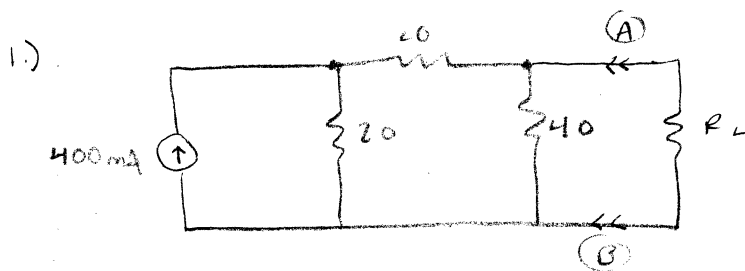

15

simplify $\Rightarrow$

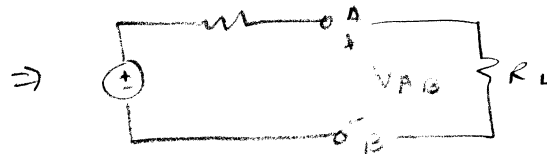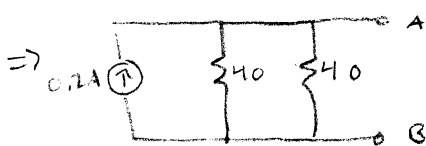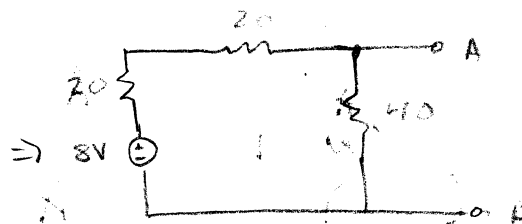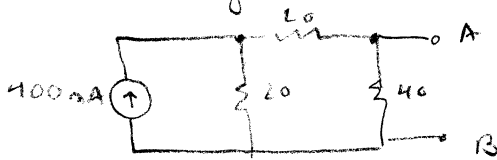

$$R_T = 20 \Omega = R_L$$


$$V_T = 4.0V$$

a.) $P_{max} = \frac{V_T^2}{4R_T} = \frac{(4.0)^2}{4(20)} = \boxed{0.2W}$


b.) $V_{max} = \dots R_L = \infty \therefore V_{max} = V_{\infty} = \boxed{V_T = 4V}$

c.) $I_{max} = R_L = 0 ; I_{max} = V_T/R_T = 4/20 = \boxed{0.2A}$

2.)

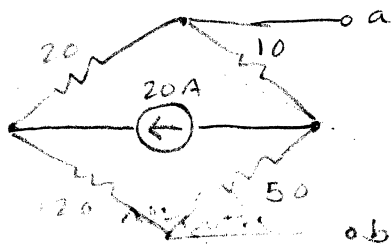


open circuit $\Rightarrow$

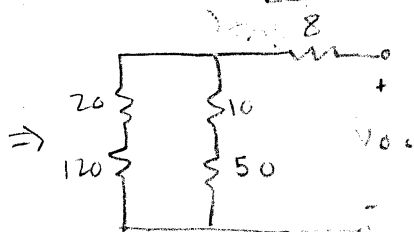

$$\therefore \boxed{R_T = 50 \Omega} = \boxed{R_L}$$

4

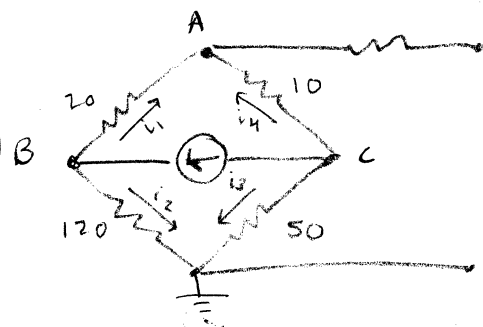

$$A: i_1 + i_4 = 0$$

$$B: -i_1 - i_2 + i_3 = 0$$

$$C: -i_4 - i_3 - i_5 = 0$$

$$A: \frac{V_B - V_A}{20} + \frac{V_C - V_A}{10} = 0$$

$$\frac{V_B - V_A}{20} = -\frac{V_C - V_A}{10}$$

$$B: -\frac{(V_B - V_A)}{20} - \frac{V_B}{120} + 20 \text{ mA} = 0$$

$$V_B - V_A = -2V_C - 2V_A$$

$$V_B + V_A = V_C$$

$$C: -\frac{(V_C - V_A)}{10} - \frac{V_C}{50} - 20 \text{ mA} = 0$$

$$-20 \text{ mA} = \frac{V_C - V_A}{10} + \frac{V_C}{50} \quad ; \quad -20 \text{ mA} = \frac{V_C - V_A}{10} + \frac{V_C}{50}$$

$$\frac{V_A}{10} - 20 = V_C \left(\frac{1}{10} + \frac{1}{50} \right) \quad ; \quad V_C = \frac{0.1V_A - 20}{0.12}$$

$$\frac{V_C + V_B}{120} - \frac{V_B}{20} + 20 = 0 \quad ; \quad \frac{V_B + V_C}{120} + 20 = \frac{V_B}{20} \quad ; \quad \frac{V_C + V_B}{120} + 20 = \frac{V_B}{20}$$

$$\frac{V_C}{120} + 20 = V_B \left(\frac{1}{20} - \frac{1}{120} \right) \quad ; \quad \frac{V_C}{120} + 20 = \frac{V_B}{24} \quad ; \quad V_B = 0.2V_C + 480$$

$$\frac{5}{6}V_A - \frac{500}{3} = V_C = V_B + V_A \quad ; \quad -\frac{V_A}{6} = V_B + \frac{500}{3} \quad ; \quad V_A = -6V_B - 1000$$


$$V_A = -1.2V_C - 2880 - 1000 = -1.2V_C - 3880$$

$$V_C = (-1.2V_C - 3880) + (0.2V_C + 480) \Rightarrow \boxed{V_C = -170 \text{ V} = V_{OC} = V_T}$$

$$P_{\max} = \frac{V_T^2}{4(R_T)} = \frac{(-170)^2}{(4)(50)} = \boxed{144.5 \text{ W} = P_{\max}}$$




OK given
error

3

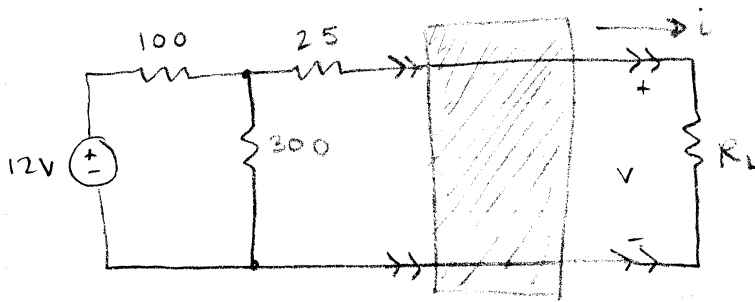

$$P \leq 1 \text{ mW}$$

(+5)

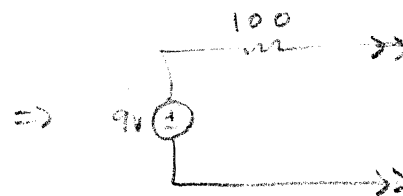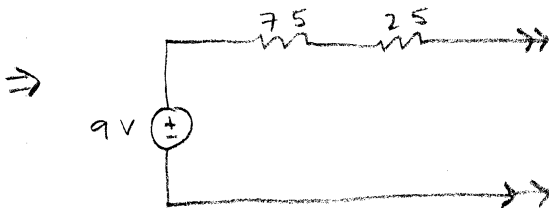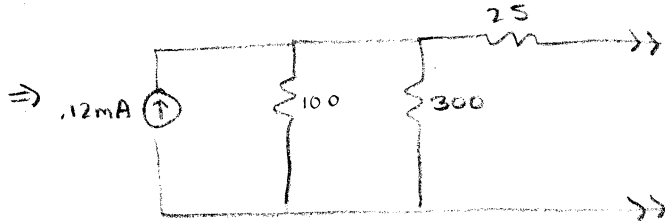


$$\therefore R_T = 100 \text{ k}, V_T = 9 \text{ V}$$

$$P_{\max} = \frac{V_T^2}{4R_T} = \frac{(9)^2}{4(100)} = 2.025 \times 10^{-4} \text{ W}$$

$\therefore$ interface circuit can be wires

H.

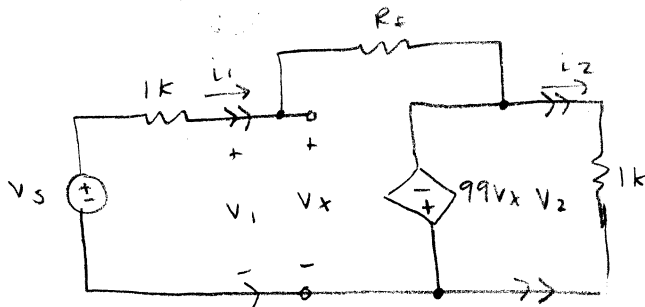

$$i_1 = i_2$$

(+5)

$$\text{KVL right} = 99V_x + V_2 = 0; V_x = -V_2/99$$

$$a.) V_S = 10 \text{ mV}, R_F = 10 \text{ k}\Omega$$

$$\frac{V_S - V_x}{1 \text{ k}} = \frac{V_x - V_2}{R_F}; V_S + \left(\frac{V_2}{99}\right) = \frac{-\frac{V_2}{99} - V_2}{R_F}$$

$$V_S + \frac{V_2}{99} = 1000 \left(\frac{-\frac{V_2}{99} - V_2}{R_F} \right); 10 \text{ mV} + \frac{V_2}{99} = 1000 \left(\frac{-\frac{V_2}{99} - V_2}{1000} \right)$$

$$10 \text{ mV} + \frac{V_2}{99} = \frac{-\frac{V_2}{99} - V_2}{10} ; 100 \text{ mV} + \frac{10V_2}{99} = \frac{-V_2}{99} - V_2 = -V_2 \left(\frac{1}{99} + 1 \right)$$

$$100 \text{ mV} + \frac{10V_2}{99} = -V_2 (1.01) ; 100 \text{ mV} = -1.01V_2 - 10V_2/99$$

$$\Rightarrow 100 \text{ mV} = (-1.01 - 10/99)V_2 ; 100 \text{ mV} = (-10/9)V_2 ; \boxed{V_2 = -0.09}$$


$$\boxed{i_2 = V_2/1000 = -0.09/1000 = -9.0 \times 10^{-5} \text{ A}}$$

$$\boxed{i_1 = \frac{V_S - V_x}{1000} = \frac{10 \text{ mV} - 9.09 \times 10^{-4} \text{ V}}{1000} = 9.091 \times 10^{-6} \text{ A}}$$

$$\therefore \text{Gain} = i_2/i_1 = \frac{-9.0 \times 10^{-5} \text{ A}}{9.091 \times 10^{-6} \text{ A}} = \boxed{-9.899}$$

$$b.) R_{IN} = V_1/i_1$$
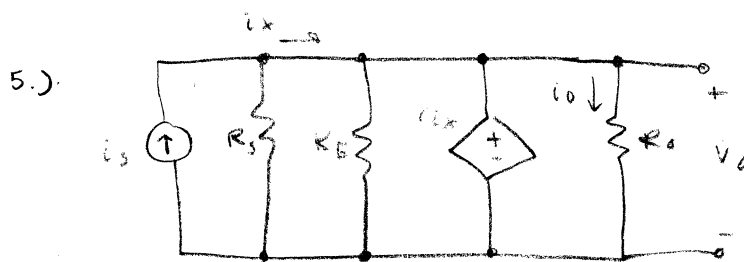
$$\left. \begin{array}{l} V_1 = V_x = 9.09 \times 10^{-4} \text{ V} \\ i_1 = 9.091 \times 10^{-6} \text{ A} \end{array} \right\} R_{IN} = \frac{9.09 \times 10^{-4} \text{ V}}{9.091 \times 10^{-6}} = \boxed{99.99 \Omega}$$



$$\text{GAIN} = \frac{i_o}{i_s}$$

15


$$\left. \begin{array}{l} i_o = i_1 + i_x \\ i_1 = \frac{V_o}{R_s} \end{array} \right\} i_s = \frac{V_o}{R_s} + i_x$$

$$V_o = i_o R_o ; -r i_x + V_o = 0 ; -r i_x + i_o R_o = 0 ; i_o R_o = r i_x ; i_x = \frac{i_o R_o}{r}$$

$$i_s = \frac{V_o}{R_s} + \frac{i_o R_o}{r} \Rightarrow \frac{i_o R_o}{R_s} + \frac{i_o R_o}{r}$$

$$i_s = i_o \left(\frac{R_o}{R_s} + \frac{R_o}{r} \right) = \frac{R_o r}{R_s r} + \frac{R_o R_s}{R_s r} ;$$
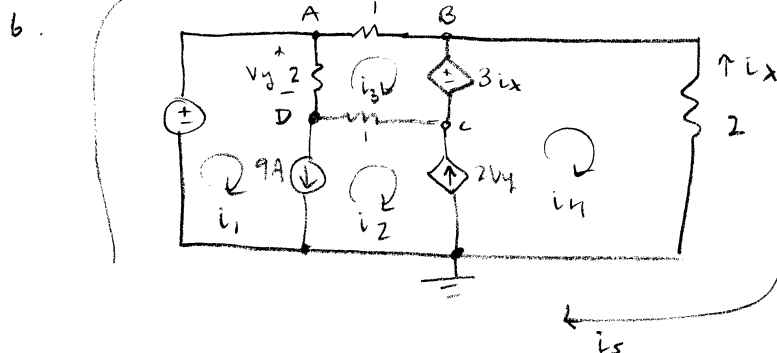
$$\boxed{i_o = i_s \left[\frac{R_s \cdot r}{R_o (r + R_s)} \right]}$$



43

a.) $i_1 - i_2 = 9A$

$i_x = -i_4$

$i_4 - i_2 = 2V_y$

$V_C + 3i_x = 2i_4$

$V_C = 2i_4 - 3i_x$

$2(i_3 - i_1) + i_3 + 3i_x + (i_3 - i_2) = 0$

$-2 + i_3(1-2) + 4(2-2) = 0$

$2i_3 - 2i_1 + i_3 + 3i_x + i_3 - i_2 = 0 ; 4i_3 - 2i_1 + 3i_x - i_2 = 0$

$4i_3 + 3i_x - 2i_1 - i_2 = 0$

$V_y = (i_1 - i_3)R ; i_4 - i_2 = 2(i_1 - i_3)2 ; i_4 - i_2 = 4i_1 - 4i_3$

$i_3 + 2i_4 = 2V ; i_3 = 2V - 2i_4 ; i_1 = i_2 + 9A ; i_4 + 4i_3 = 4i_1 + i_2$

$i_4 + 3i_4 + 2i_1 + i_2 = 4i_1 + i_2 \Rightarrow 4i_4 = 2i_1 ; 2i_4 = i_1$

$4i_3 = 3i_4 + 4i_4 + i_2 ; 4i_3 = 7i_4 + i_2 ; 4(2V - 2i_4) = 7i_4 + i_2$

$\Rightarrow 8V - 8i_4 = 7i_4 + i_2 ; 8V = 15i_4 + i_2$

1. $i_1 - i_2 = 9 ; i_3 + 2i_4 = 2 ; 4i_1 + i_2 - 4i_3 - i_4 = 0 ;$

$2i_1 + i_2 - 4i_3 + 3i_4 = 0$

using solver in calculator $\Rightarrow$

$i_1 = 2$

$i_2 = -7$

$i_3 = 0$

$i_4 = 1$

$i_x = -1A$

$V_C = (2)(10) - 3(-1) = 5V$

Good

b.) $V_A = 2V$

$V_D = V_C + 3i_x ; 3i_x = V_B - V_C$

A: $(2 - V_A) - \frac{(V_A - V_D)}{2} - (V_A - V_B) = 0$

B: $3i_x + (V_A - V_B) + i_x = 0 ; V_B - V_C + (V_A - V_B) + \frac{(V_B - V_C)}{2}$

C: $-3i_x - (V_C - V_B) + 2V_y = 0 = -(V_B - V_C) - (V_C - V_D) + \frac{3(V_A - V_D)}{2}$

D: $-9 + (V_C - V_D) + \frac{V_A - V_D}{2} = 0$

simplified equations.

$$2.5V_A - V_B - 0.5V_D = 2$$

$$V_A - 1.3V_B - 1.3V_C = 0$$

$$V_A - V_B + V_D = 0$$

$$0.5V_A + V_C - 1.5V_D = 9$$

use solver in calculator

$$V_A = 29\frac{1}{3} \text{ V}$$

$$V_B = 57\frac{1}{3} \text{ V}$$

$$V_C = 36\frac{2}{3} \text{ V}$$

$$V_D = 28 \text{ V}$$

$$V_C = V_A - V_B + V_D = 0$$


$$= 29\frac{1}{3} - 57\frac{1}{3} + 28 = 0 = V_C$$

$$3V_A = V_D - V_C = 57\frac{1}{3} - 36\frac{2}{3} = 21 = 3 \times 7$$





Answers will match
part a)

$$V_A = 2 \text{ V}$$

Joseph Barone
Homework #6

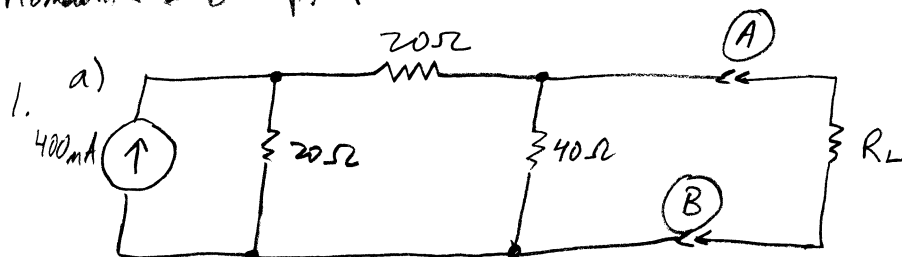

$\frac{26}{30}$ Good Job!

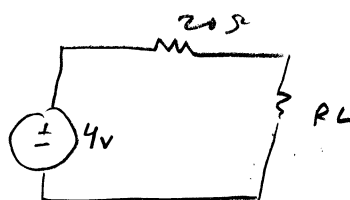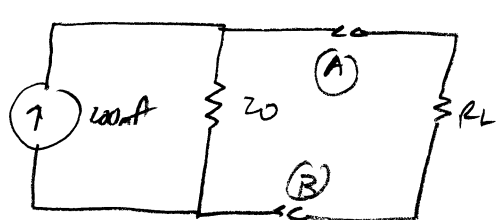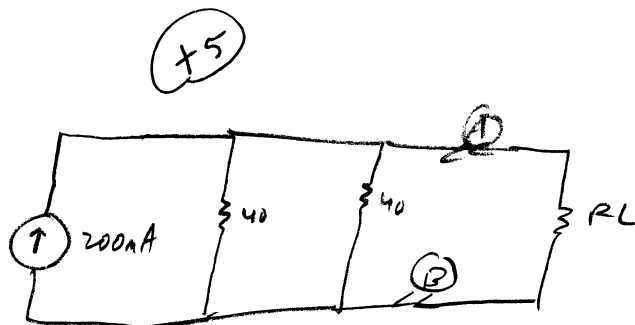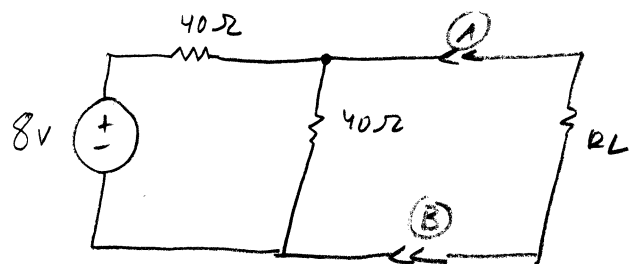

$R_L = 20\Omega$

$\left(\frac{20}{40}\right)4 = 2V$

$V_{RL} = 2V$

$\left(\frac{20}{40}\right)200 = 100mA$

$i = 0.1A$

$v = \left(\frac{20}{20}\right)4 = 2V$

$R_L = 20\Omega$

$i_{max} = \frac{4V}{20\Omega} = 0.2A = 200mA = i_N$

$P_{max} = \frac{v_T i_N}{4} = 0.2 \text{ Watts}$

b)

$v = \left(\frac{40}{40+40}\right)8 = 4V$


$4V = \left(\frac{R_L}{20+R_L}\right)4V \quad R_L \Rightarrow \infty$

c)

$i_{max} = \frac{4V}{20\Omega} = 0.2A$

$R_L \rightarrow 0$

2)

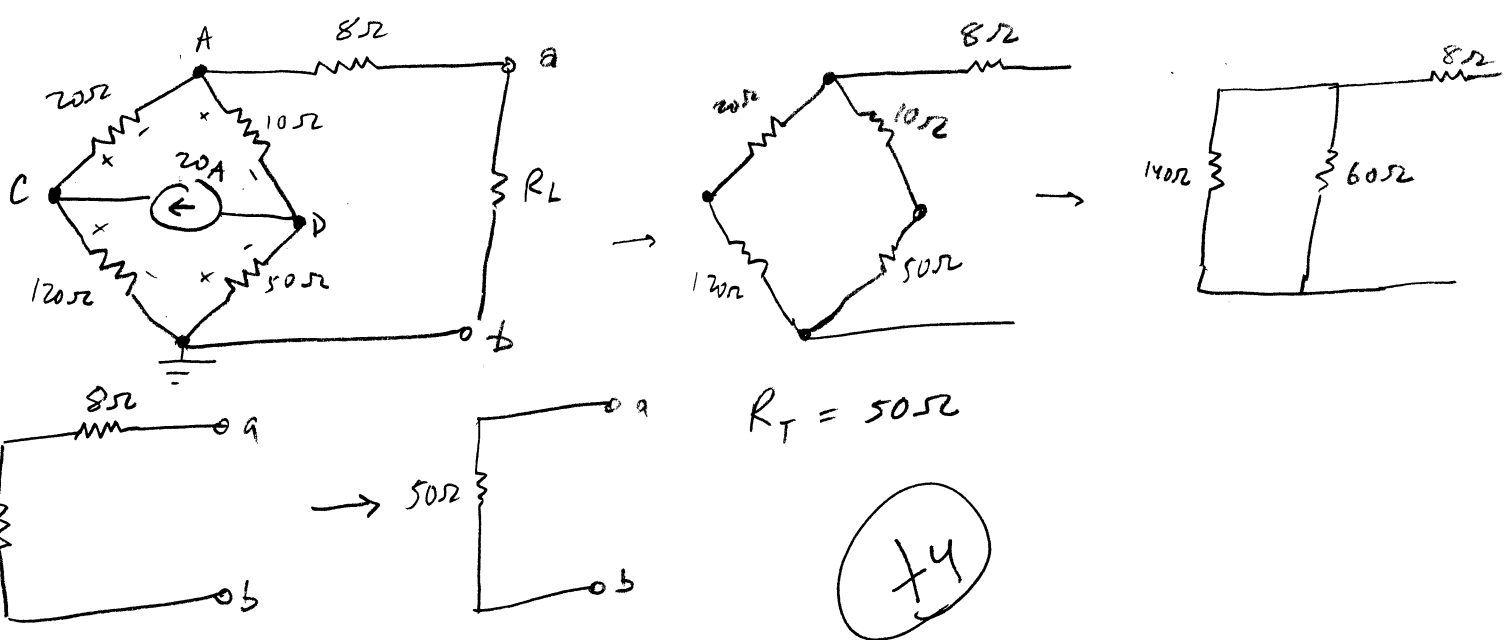

$$\text{KCL A: } \frac{V_C - V_A}{20\Omega} - \left(\frac{V_A - V_D}{10\Omega} \right) = 0$$

$$\frac{V_C}{20\Omega} - V_A \left(\frac{1}{20} + \frac{1}{10} \right) + \frac{V_D}{10\Omega}$$

$$\text{KCL C: } -\frac{V_C}{120} - \left(\frac{V_C - V_A}{20} \right) + 20A = 0 \quad = -\frac{V_C}{120} - \frac{V_A}{20} + \frac{V_C}{20} = V_C \left(\frac{1}{20} - \frac{1}{120} \right) - \frac{V_A}{20}$$

$$\text{KCL D: } -\left(\frac{V_A - V_D}{10} \right) + \frac{V_D}{50} - 20A = 0 \quad \frac{V_A}{10} + V_D \left(\frac{1}{50} - \frac{1}{10} \right) = 20$$

$$\text{A: } \frac{V_C}{20\Omega} + \frac{V_D}{10\Omega} = V_A \left(\frac{3}{20}\Omega \right) \quad \text{C: } V_C \left(\frac{1}{24} \right) - V_A \left(\frac{1}{20} \right) = -20$$

$$\text{D: } \frac{V_A}{10} - V_D \left(-\frac{2}{25} \right) = 20$$

$$V_A = 14.10 \quad V_C = 1200 \quad V_D = 1000$$

$$V_A = 14.10V$$


$$V = IR$$

$$\frac{V}{R} = \frac{14}{50} = 0.28A$$

$$P = Vi = 14 \times 0.28 = 3.92W$$

OK given error

3)

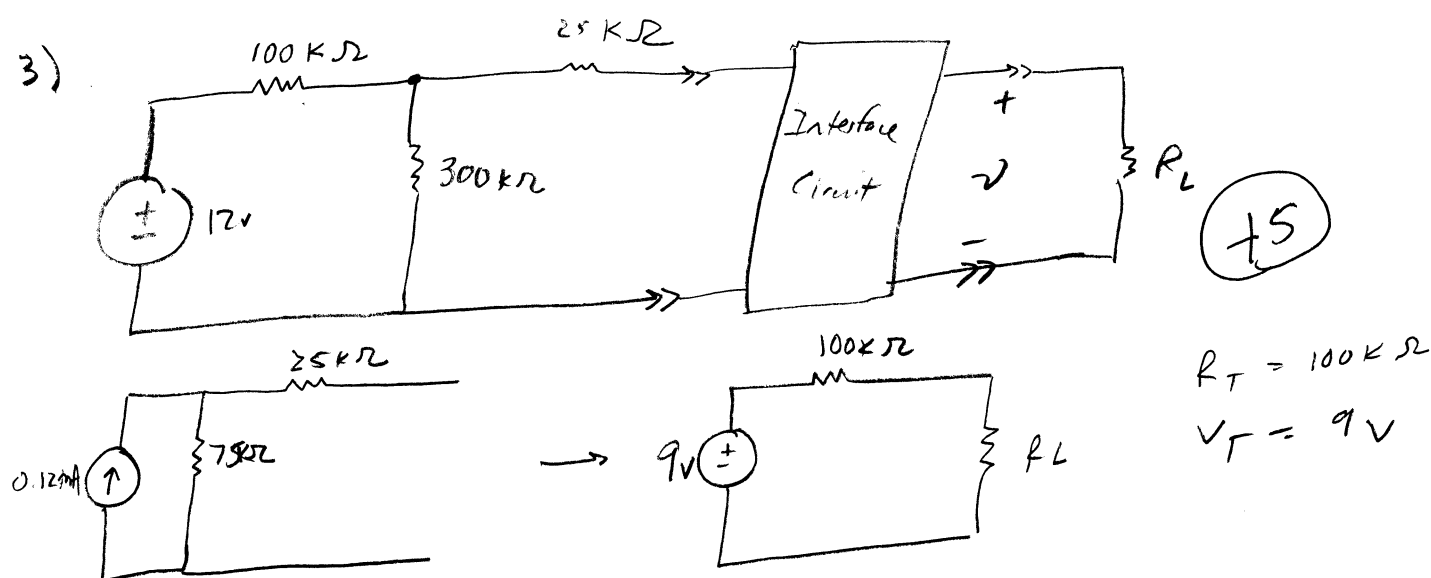


$$R_T = 100\text{ k}\Omega$$

$$V_T = 9\text{ V}$$

$$P_{\max} = \frac{(9)^2}{4(100000)} = 0.2025\text{ mW}$$

→ This does not exceed 1 mW, therefore the interface circuit could be anything.

4) a)

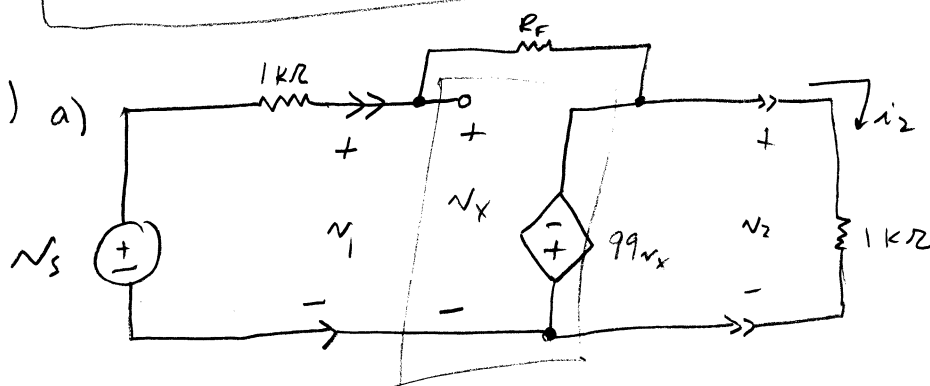

$$V_S = 10\text{ mV}$$

$$R_F = 10\text{ k}\Omega$$

$$\frac{V_S - V_x}{1\text{ k}} = \frac{V_x - V_2}{R_F}$$

$$99V_x + V_2 = 0$$

$$V_x = -\frac{V_2}{99}$$

$$i_2 = \frac{V_2}{1\text{ k}\Omega}$$

$$= \frac{-9 \times 10^{-2}\text{ V}}{1\text{ k}\Omega} = -9 \times 10^{-5}$$

$$V_S - V_x = 1\text{ k} \left(\frac{V_x - V_2}{R_F} \right)$$

$$V_x = V_S - 1\text{ k} \left(\frac{V_x - V_2}{R_F} \right)$$

$$V_x = V_S - \left(\frac{1000V_x - 1000V_2}{10\text{ k}\Omega} \right)$$

$$i_1 = \frac{V_S - V_x}{1000}$$

$$= \frac{10\text{ mV} - 9.09 \times 10^{-4}\text{ V}}{1000}$$

$$= 9.091 \times 10^{-6}$$

$$V_x = \frac{10\text{ k}\Omega \cdot V_S}{10\text{ k}\Omega + 1 \times 10^5} = \frac{10\text{ k}\Omega \cdot 10\text{ mV}}{10\text{ k}\Omega + 1 \times 10^5} = 9.09 \times 10^{-4}\text{ V}$$

$$V_2 = -9 \times 10^{-2}\text{ V}$$


$$\frac{i_2}{i_1} = -9.8999$$

④ b) $R_{in} = \frac{V_1}{i_1}$

$V_1 = V_X = 9.09 \times 10^{-4} \text{ V}$

$i_1 = 9.091 \times 10^{-6} \text{ A}$

$R_{in} = 99.98752$

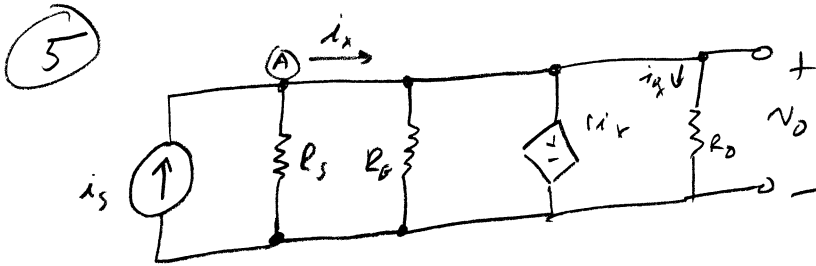

① $i_s - i_x - \frac{V_o}{R_s} = 0$

$V_o = r i_x = R_o i_o$

$i_x = \frac{R_o i_o}{r}$


$i_s = i_x + \frac{V_o}{R_s}$

$i_s = \frac{R_o i_o}{r} + \frac{V_o}{R_s}$

$i_o = \frac{\left(i_s - \frac{V_o}{R_s}\right) r}{R_o i_o} = \frac{r i_s - \frac{r V_o}{R_s}}{R_o i_o}$

$\frac{i_o}{i_s} = \frac{r R_s}{r R_o + R_s R_o}$

⑤

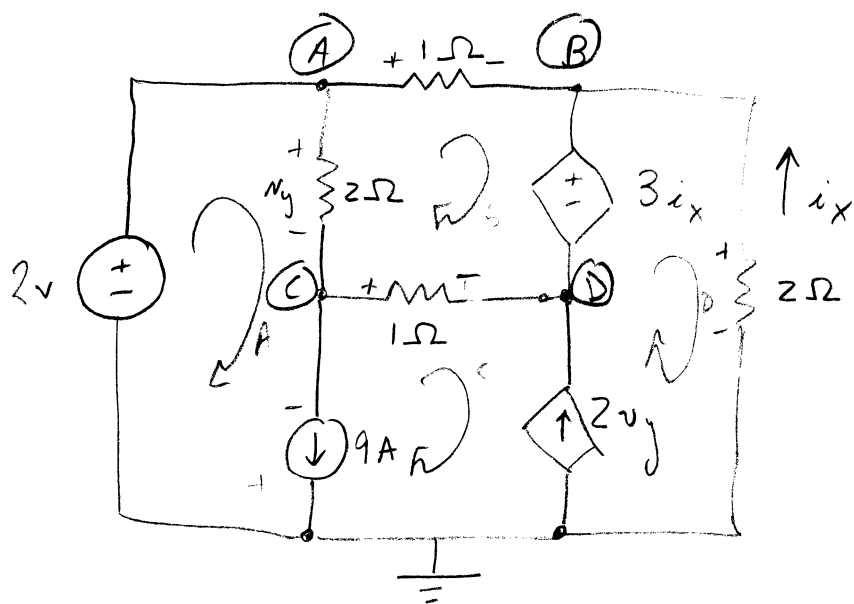

(+2)

$V_A = 2V$ set by source

(KCL) (A) $-\left(\frac{V_A - V_C}{2\Omega}\right) - \left(\frac{V_A - V_B}{1\Omega}\right) = 0$

$$-\frac{V_A}{2} - \frac{V_C}{2} - V_A + V_B = 0$$

(B) $\left(\frac{V_A - V_B}{1\Omega}\right) + i_x = 0$

$$V_A - V_B + i_x = 0$$

(C) $\left(\frac{V_A - V_C}{2\Omega}\right) + \left(\frac{V_C - V_D}{1\Omega}\right) = 9$

$$\frac{V_A}{2} - \frac{V_C}{2} + V_C - V_D = 9$$

(D) $2v_y - \left(\frac{V_C - V_D}{1\Omega}\right) = 0$

$$2v_y - V_C + V_D = 0$$

$$-V_A \left(\frac{3}{2}\right) - V_C \left(\frac{1}{2}\right) + V_B = 0$$

$$2v_y = 2(V_A - V_C)$$

$$V_A \left(\frac{1}{2}\right) + V_C \left(\frac{1}{2}\right) - V_D = 9$$

$$i_x = \frac{V_B}{2}$$

$$2V_A - 2V_C - V_C + V_D = 0$$

$$2V_A - 3V_C + V_D = 0$$

$$V_A - V_B + \frac{V_B}{2} = V_A - \frac{V_B}{2} = 0$$


$$V_A = -3V$$

$$V_B = -6V$$

$$V_C = -3V$$

$$V_D = -12V$$



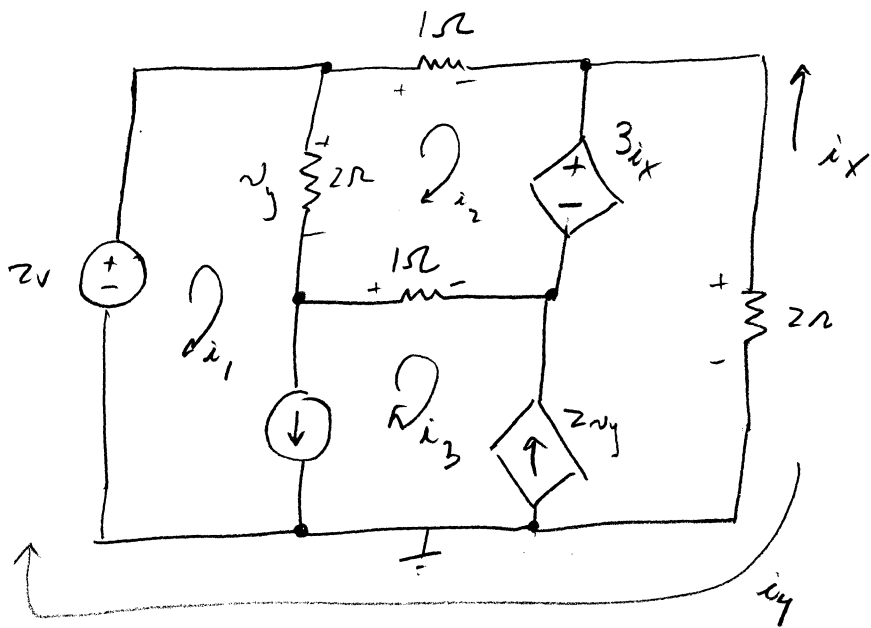

$$\textcircled{i_1} \quad \underbrace{-2V}_{\text{voltage}} + \underbrace{(i_1 - i_2)}_{\text{current}} = 0 \quad 2 = i_1 - i_2$$

$$\textcircled{i_2} \quad \frac{-(i_1 - i_2)}{2} + (i_2 + i_4) - (i_3 - i_2) + 3i_x$$

$$\textcircled{i_3} \quad (i_3 - i_2) = 0 \quad i_3 = i_2$$

$$\textcircled{i_4} \quad -2V + (i_2 + i_4) + \frac{i_4}{2} = 0$$



$$2 = i_2 + \frac{3}{2} i_4$$

$$\frac{-i_1}{2} + i_2 \left(\frac{5}{2} \right) + i_4 - i_3 + 3i_x$$

$$i_x = i_2$$

$$-\frac{i_1}{2} + \frac{7}{2} i_2 + i_4 - i_3 = 0$$
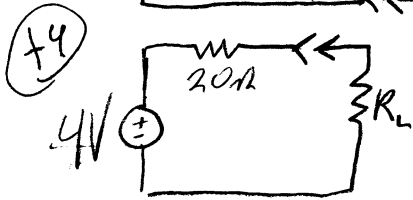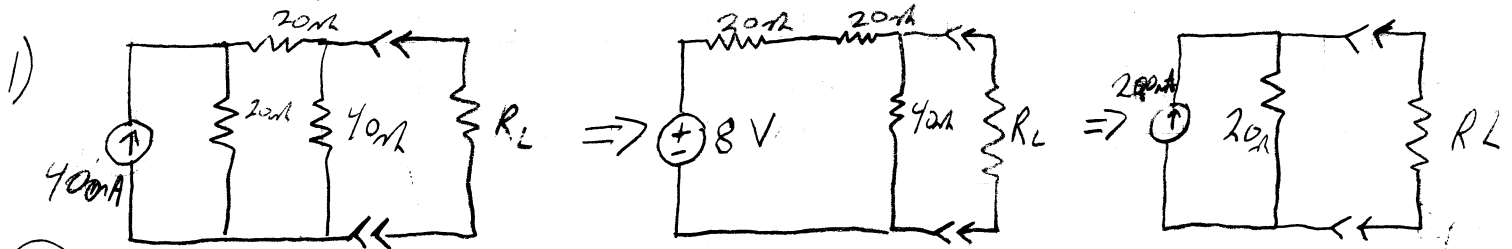
$$i_1 = 1.75 \quad i_2 = -0.25 \quad i_3 = -0.25 \quad i_4 = 1.5$$





a) $R_L = R_T = 20\Omega$

$P = \frac{V^2}{4R_T} = \frac{(4)^2}{4(20)} = 0.2 \text{ W}$

b) $V_{max} = V_T = V_{oc} = 4 \text{ V}$ $R_L = \infty$

c) $I_{max} = \frac{V_T}{R_T} = 0.2 \text{ A}$ $R_L = 0$

— What is R_L in these cases?

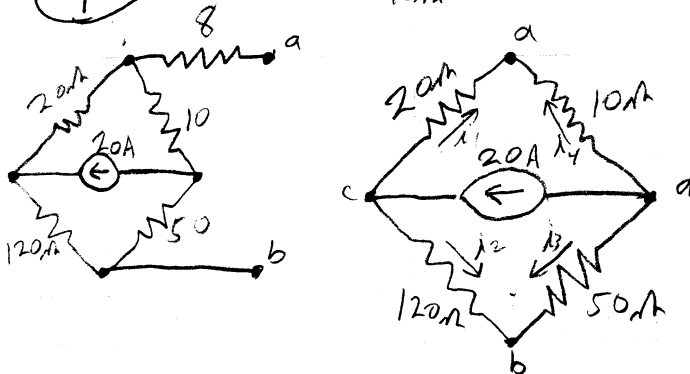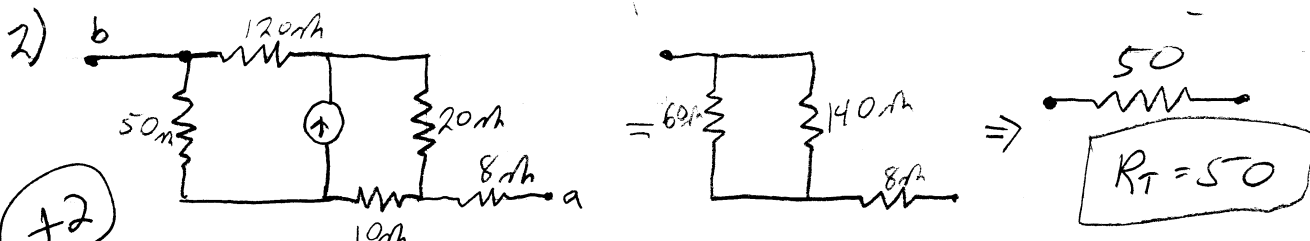

KCL:

A: $G_1(V_C - V_A) - G_4(V_A - V_D) = 0$

C: $-G_2(V_C) - G_1(V_A - V_C) + 20 = 0$

D: $-G_4(V_A - V_D) + G_3 V_C - 20 = 0$

must have opposite signs

$i_1 = G_1(V_A - V_C)$ $i_2 = G_2(V_A - V_D)$ $i_3 = G_3 V_C$ $i_4 = G_4 V_D$ $i_5 = i_{s1}$

A: $(G_1 + G_2)V_A - G_1 V_C - G_2 V_D = 0$

C: $-G_1 V_A + (G_1 + G_2)V_C = 20$

D: $-G_2 V_A + (G_2 + G_4)V_D = -20$

$-G_1 V_A + (G_1 + G_2)V_C = G_2 V_A - (G_2 + G_4)V_D$


$-G_1 V_A + (G_1 + G_3)V_C = G_2 V_A - (G_2 + G_4)V_D$

$G_1 V_A + G_2 V_A = (G_1 + G_3)V_C + (G_2 + G_4)V_D$

$V_A = \frac{(G_1 + G_3)V_C + (G_2 + G_4)V_D}{(G_1 + G_2)}$

$R_T = ?$ $P_{max} = ?$

— 2

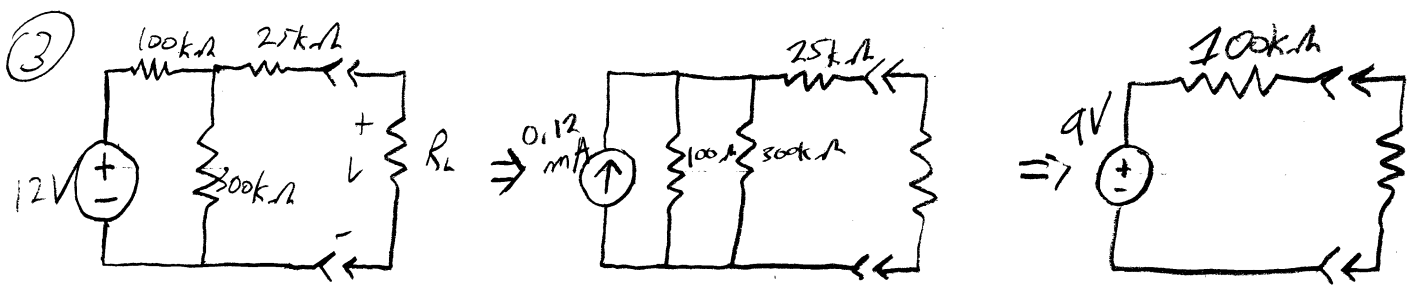

⑤ $P_{\max} = \frac{V^2}{4R} = \frac{9^2}{4(100 \times 10^3)} = \boxed{2.025 \times 10^{-4} \text{ W}}$

Since this value is less than 1mW you do not need any resistors you can just use 2 wire.

④ $i_1 = i_f \quad V_x = -V_2/99$

$i_1 = \frac{V_1 - V_x}{1k} = \frac{V_x - V_2}{R_F}$

⑤

$10 + \frac{V_2}{99} = \frac{-\frac{V_2}{99} - V_2}{10} \Rightarrow 10mV + \frac{V_2}{99} = \frac{(-\frac{V_2}{99})}{10} - \frac{V_2}{99}$

$\Rightarrow 10mV + \frac{V_2}{99} = -\frac{V_2}{990} - \frac{V_2}{10} \Rightarrow 10mV = \frac{-10V_2}{990} - \frac{V_2}{990} - \frac{99V_2}{990}$

$10mV = -\frac{100V_2}{990} \quad V_2 = \frac{-10mV(990)}{110} = \boxed{-0.09V = V_2}$

$i_2 = \frac{V_2}{1k\Omega} = \frac{-0.09}{1k\Omega} = -9 \times 10^{-5}$

$V_x = V_2/0.99 = 9.09 \times 10^{-4}$

$\frac{i_2}{i_1} = \frac{-9 \times 10^{-5}}{9.091 \times 10^{-6}} = -9.8999$

$i_1 = \frac{V_1 - V_x}{1k} = \frac{10mV - 9.09 \times 10^{-4}}{1k\Omega} = 9.091 \times 10^{-6}$

$R_{in} = \frac{V_1}{i_1}$

$i_1 = 9.091 \times 10^{-6}$

$V_1 = V_x = 9.09 \times 10^{-4}$

$\frac{9.09 \times 10^{-4}}{9.091 \times 10^{-6}} \approx 100\Omega = R_{in}$

#2

$$G_1 V_C + G_2 V_D = (G_1 + G_3) V_C + (G_2 + G_4) V_D$$

$$-G_3 V_C = (G_2 + G_4) V_D - G_2 V_D$$

$$V_C = -\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3}$$

~~$$(G_1 + G_2) \left(\frac{(G_1 + G_3) V_C + (G_2 + G_4) V_D}{(G_1 + G_2)} \right) - G_1 \left(\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3} \right) - G_2 V_D = 0$$~~

~~$$(G_1 + G_3) \left(-\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3} \right) + (G_2 + G_4) V_D - G_1 \left(\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3} \right) - G_2 V_D = 0$$~~


~~$$(G_2 + G_4) V_D = (G_1 + G_3) \left(\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3} \right) + G_1 \left(\frac{(G_2 + G_4) V_D - G_2 V_D}{G_3} \right) + G_2 V_D$$~~

~~$$V_D = -0.2$$~~

~~$$V_C = 1/6$$~~

~~$$V_A = 1.03$$~~

5

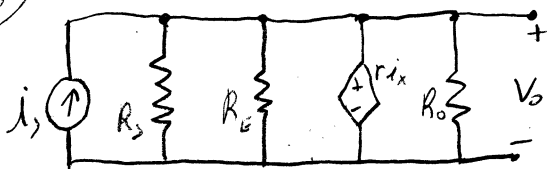

$$i_s = i_{R_s} + i_x \quad i_{R_s} = V_o / R_s$$

$$i_s = V_o / R_s + i_x \quad V_o = i_x R_o$$

$$r_{ix} = V_o \quad V_{ix} = i_o R_o$$

$$i_x = i_o R_o / r_{ix}$$

$$\frac{i_o}{i_s} = \frac{(V_o / R_o)}{(V_o / R_s) + (V_o / r_{ix})}$$

~~1/4~~

1/4

-d

Answer should
only have R_s

$$\textcircled{6} \text{ a) } i_1 - i_2 = 9 \quad i_4 - i_2 = 2V_y \quad -2 + i_3(7) + i_4(2) = 0$$

$$(i_3 - i_1)(2) + (1)(i_3) + 3i_x + (1)(i_3 - i_2) = 0$$

$$-2i_2 - 2i_1 + i_3 + 3i_x + i_3 - i_2 = 0$$

$$3i_x = 2i_1 + i_2$$

$$3i_x = 2i_2 + 18 + i_2 = 3i_2 + 18$$

(+1)

What are i_1 , i_2 etc. I need a picture.



-1

1

Node Voltage -2

Answers -1

$\frac{21}{30}$

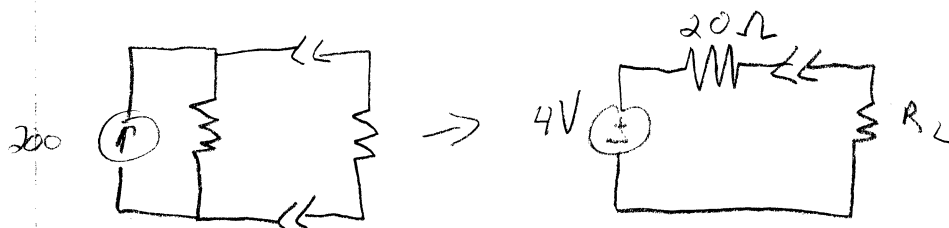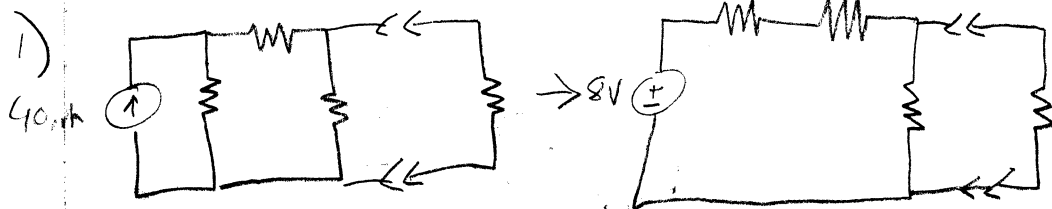


+4

a) $R_L = R_T = 20 \Omega$ $P = \frac{V^2}{R} \rightarrow \frac{4^2}{4(20)} = 0.2 W$

b) $V_{max} = V_T = V_{oc} = 4 V$

c) $i_{max} = \frac{V_T}{R_T} = \frac{4}{20} = 0.2 A$

What are R_L in these instances?

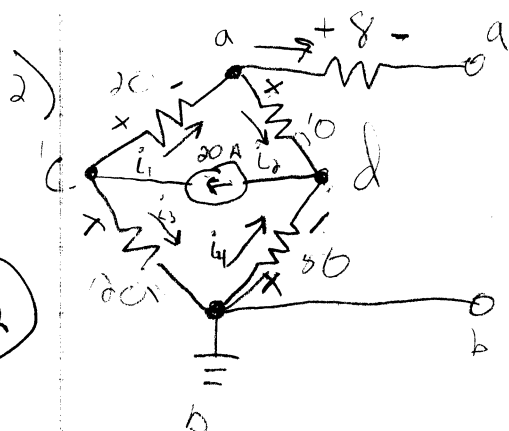

$8 + (20 + 10) // (10 + 50) = 50 \Omega = R_T$

+2

a $\rightarrow i_1 - i_2 = 0 \rightarrow i_1 = i_2$

c $\rightarrow 20A - i_3 - i_1 = 0 \rightarrow 20 = i_1 + i_3$

b $\rightarrow i_3 - i_4 = 0 \rightarrow i_3 = i_4$

d $\rightarrow -20A + i_4 + i_2 = 0 \rightarrow 20 = i_4 + i_2$

$$\check{i}_1 = \check{i}_2 \rightarrow$$

$$\check{i}_1 + \check{i}_3 = 20 \rightarrow$$




$$\check{i}_3 = \check{i}_4 \rightarrow$$

$$\check{i}_2 + \check{i}_4 = 20 \rightarrow$$

$$P_{\max} = ? \quad -2$$

3)


15

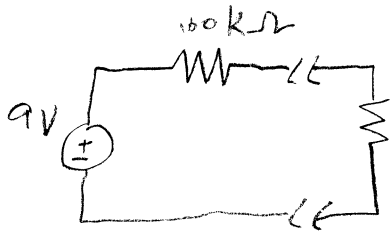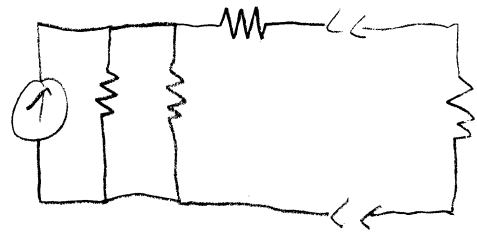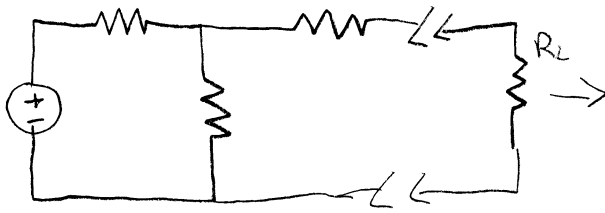

Try with just wires first $\rightarrow$

$$P_{\max} = \frac{V^2}{4R} = \frac{9^2}{4(100 \times 10^3)} = 2.025 \times 10^{-4} \text{ W}$$

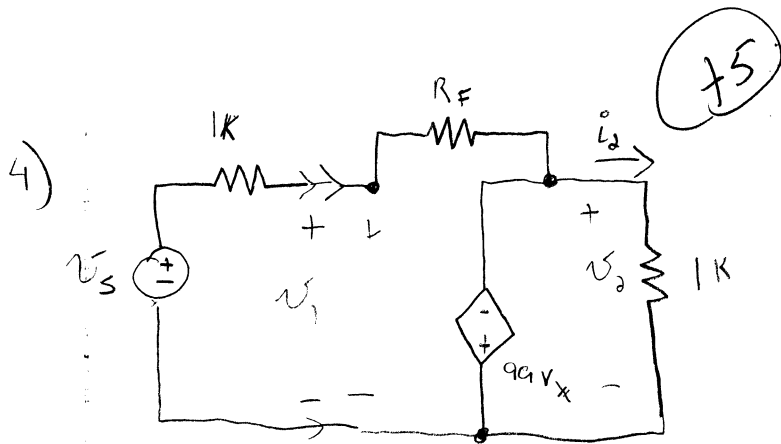The power from the source is less than 1mW, so you don't need any type of additional resistors



$$v_s = 10 \text{ mV}$$

$$R_F = 10 \text{ k}\Omega$$

$$\text{Find } v_2 + i_2 / i_1$$

$$R_{in} = v_1 / i_1$$

$$i_1 = i_x \rightarrow \frac{v_s - v_x}{1 \text{ k}} = \frac{v_x - v_2}{R_F} \rightarrow 99 v_x + v_2$$

$$v_x = -\frac{v_2}{99}$$

$$\frac{10 \text{ mV} + \frac{v_2}{99}}{10} = \frac{-\frac{v_2}{99} - v_2}{10}$$

$$10 \text{ mV} + \frac{v_2}{99} = \left(-\frac{v_2}{99} \right) - \frac{v_2}{10} \rightarrow 10 \text{ mV} + \frac{v_2}{99} = -\frac{v_2}{990} - \frac{v_2}{10}$$

$$10 \text{ mV} = -\frac{v_2}{99} - \frac{v_2}{990} - \frac{v_2}{10}$$

$$10 \text{ mV} = -\frac{10 v_2}{990} - \frac{v_2}{990} - \frac{99 v_2}{990}$$

$$10 \text{ mV} = -\frac{110 v_2}{990}$$

$$v_2 = \frac{-10 \text{ mV} (990)}{110} = -0.09 \text{ V}$$

$$i_2 = \frac{v_2}{1 \text{ k}\Omega} = \frac{-0.09}{1 \text{ k}\Omega} = -9 \times 10^{-5}$$

$$\frac{i_2}{i_1} = \frac{-9 \times 10^{-5}}{9.091 \times 10^{-6}} = -9.8999$$

$$v_x = \frac{v_2}{-0.09} = 9.09 \times 10^{-4}$$


$$i_1 = \frac{v_s - v_x}{1 \text{ k}} = \frac{10 \text{ mV} - 9.09 \times 10^{-4}}{1 \text{ k}} = 9.091 \times 10^{-6}$$

$$R_{in} = \frac{v_1}{i_1} \quad v_1 = v_x = 9.09 \times 10^{-4}$$

$$i_1 = 9.091 \times 10^{-6}$$

$$\frac{9.09 \times 10^{-4}}{9.091 \times 10^{-6}} \approx 100 \Omega$$

5)

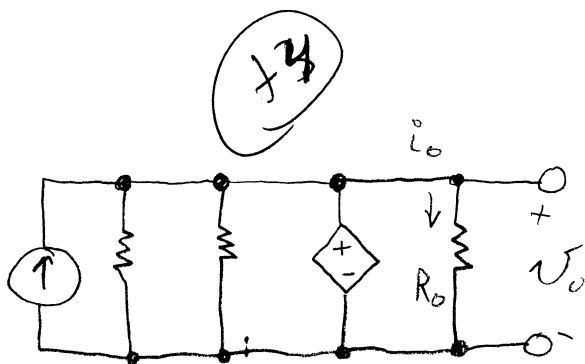

$$i_o/i_s$$

$$i_s = i_1 + i_x \quad i_s = \frac{V_o}{R_s} + i_x \quad V_o = i_o R_o \quad i_o = V_o/R_o$$

$$i_1 = \frac{V_o}{R_s}$$

$$\frac{i_o}{i_s} = \frac{(V_o/R_o)}{(\frac{V_o}{R_s}) + (\frac{V_o}{r})}$$


$$r i_x = V_o \quad V i_x = i_o R_o$$

$$i_x = \frac{i_o R_o}{r}$$

$$V_o = r i_x$$

Answer should only have R's

6)

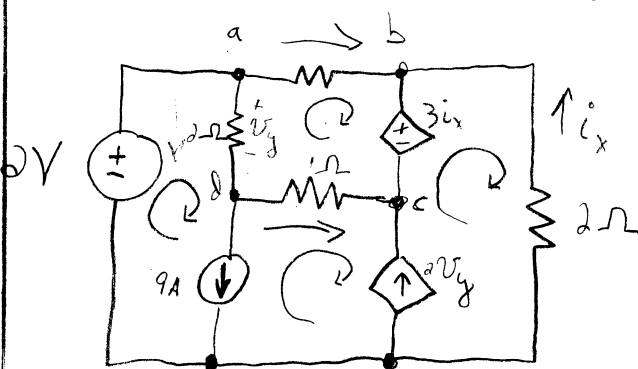

What is i_1, i_2 etc.?

$$i_1 - i_2 = 9$$

$$i_4 - i_2 = 2V_y$$

$$-i_3 + 2i_4 = 2$$

$$2i_1 - 2i_3 - 3i_4 + i_2$$

Nodal Voltage -2

Answers -1