
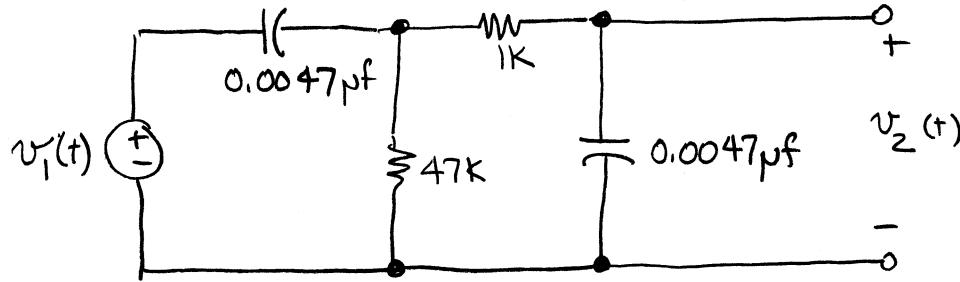


1-

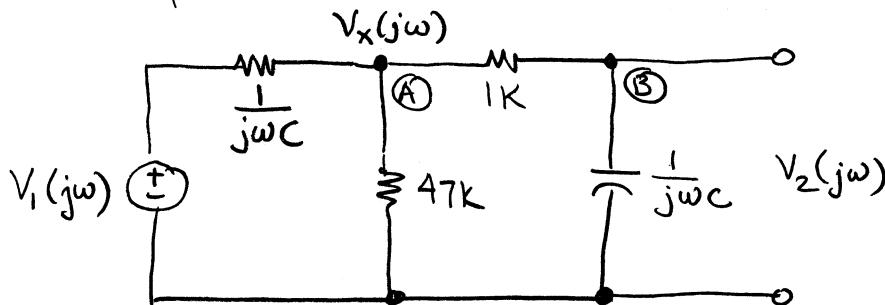Analysis of directly coupled high-pass / low-pass filter cascade.



Convert to phasors.



Do KCL at nodes A and B. Assume the voltage at node A is  $V_x(j\omega)$ .

$$\frac{V_1 - V_x}{\frac{1}{j\omega C}} - \frac{V_x - 0}{47k} - \frac{V_x - V_2}{1k} = 0 \quad (1)$$

$$\frac{V_x - V_2}{1k} - \frac{V_2 - 0}{\frac{1}{j\omega C}} = 0$$

$$\frac{V_x - V_2}{1k} - j\omega C V_2 = 0$$

$$V_x = 1k \left( \frac{1}{1k} + j\omega C \right) V_2 = (1 + j\omega 47k) C \quad (2)$$

Expanding (1) gives

$$j\omega C V_1 - j\omega C V_x - \frac{1}{47k} V_x - \frac{V_x}{1k} + \frac{V_2}{1k} = 0$$

Multiply through by  $1k$

$$j\omega(1k)C V_1 - j\omega(1k)C V_X - \frac{1}{47} V_X - V_X + V_2 = 0$$

Collect terms

$$j\omega(1k)C V_1 - V_X \left[ j\omega(1k)C + \frac{1}{47} + 1 \right] + V_2 = 0$$

↑  
substituting from (2)

$$j\omega(1k)C V_1 - [1 + j\omega(1k)C] \left[ 1 + \frac{1}{47} + j\omega(1k)C \right] V_2 + V_2 = 0$$

Rearranging

$$T(j\omega) = \frac{V_2}{V_1} = \frac{j\omega(1k)C}{\left[ 1 + j\omega(1k)C \right] \left[ 1 + \frac{1}{47} + j\omega(1k)C \right] + 1}$$

To plot this I will make two approximations

$$(1) \quad 1 + \frac{1}{47} \approx 1$$


(2) I can neglect the  $+1$  term in the denominator.  
As we will see this will only change the shape a little  
for  $\omega \rightarrow 0$

$$T(j\omega) \cong \frac{j\omega(1k)C}{[1 + j\omega(1k)C][1 + j\omega(1k)C]}$$

Taking logs

$$\begin{aligned} 20 \log_{10} |T(j\omega)| &\cong 20 \log_{10} |\omega(1k)C| - 20 \log_{10} |1 + j\omega(1k)C| \\ &\quad - 20 \log_{10} |1 + j\omega(1k)C| \end{aligned}$$

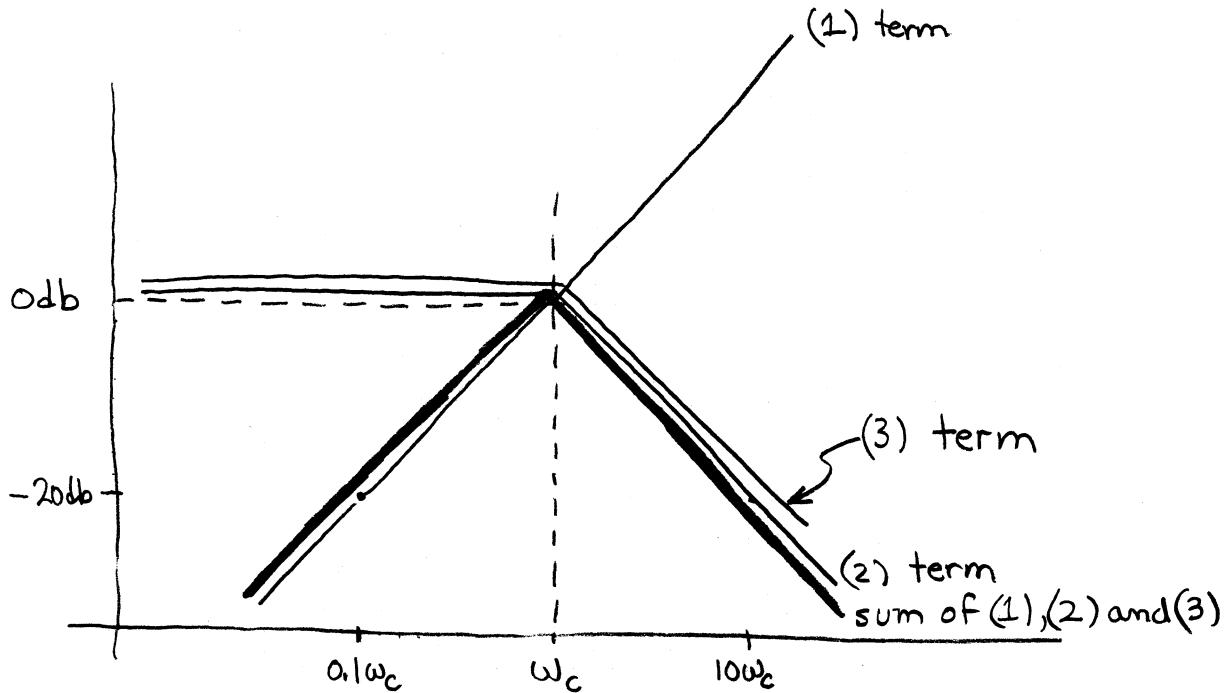Note: I could have combined the last two terms but do not since they are easier to plot this way.



(1) Start with the  $-20 \log_{10} |\omega(1k)c|$  term

This term is 0db when  $\omega(1k)c = 1$

$$\text{or } \omega_c = \frac{1}{(1000)(0.0047 \times 10^{-6})} = 2.13 \times 10^5 \frac{\text{rad}}{\text{sec}}$$

[in terms of laboratory  $f_c \approx \frac{\omega}{2\pi} = 33862 \text{ Hz}$

(2) Plot the second term  $-20 \log_{10} |1 + j\omega(1k)c|$

Substituting  $C = 0.0047 \mu\text{F}$

$$-20 \log_{10} |1 + j\omega(4.7 \times 10^{-6})|$$

This term has  $\omega_c = \frac{1}{4.7 \times 10^{-6}} = 2.13 \times 10^5 \frac{\text{rad}}{\text{sec}}$

It is for  $\omega \ll \omega_c \quad -20 \log_{10}(1) \rightarrow 0$

$$\omega \gg \omega_c \quad -20 \log_{10} |\omega(4.7 \times 10^5)|$$

So it does nothing (0db) for  $\omega < \omega_c$  and decreases at  $-20 \text{ dB/decade}$  for  $\omega > \omega_c$ .

This cancels out the (1) term for  $\omega > \omega_c$

(3) The third term repeats the second term

(4) Adding together gives a band-pass characteristic centered at  $\omega = 2.13 \times 10^5 \text{ rad/sec}$