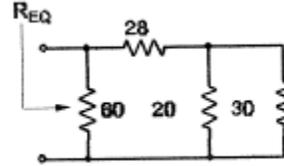


Homework Solutions 3

(2-28) Find the equivalent resistance R_{eq} in Figure P2-28

$$2-28 \quad R_{EQ} := \frac{1}{\frac{1}{60} + \frac{1}{28 + \frac{1}{\frac{1}{20} + \frac{1}{30}}}}$$

$$R_{EQ} = 24$$



Start with the 20Ω resistor is in parallel with 30Ω resistor, now add the 28Ω resistor. That equivalent resistance calculation is in parallel with a 60Ω resistor.

Req = 24Ω.

(2-34) A 5-mA practical current source is parallel with a 2-kΩ resistor. The voltage across the resistor is observed to be 5V. Find the source resistance of the practical current source.

$$2-34 \quad R := 2000 \quad V_R := 5 \quad i_R := \frac{V_R}{R}$$


$$i_R = 2.5 \times 10^{-3} \quad i_S := 5 \cdot 10^{-3}$$

$$i_{R_s} := i_S - i_R \quad i_{R_s} = 2.5 \times 10^{-3}$$

$$R_S := \frac{V_R}{i_{R_s}} \quad R_S = 2 \times 10^3$$

Simply consider a 2-kΩ resistor to be in parallel with a 5mA current then, find the current through the resistor. Now to find the source resistance current subtract the current through the 2-kΩ resistor from the 5mA current source. Since the voltage through the resistor is 2V divide this with the sources resistance current to obtain the source resistance.

(2-44) Find I_y in figure P2-43

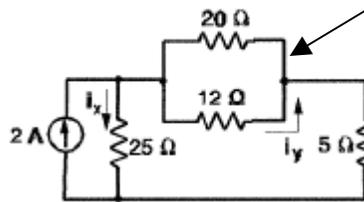

Start reducing the circuit by considering 20Ω resistor is in parallel with the 12Ω resistor.

After the 20Ω||12Ω reduction add the 5Ω to obtain the equivalent resistance ($R_{eq} = 5\Omega + (20\Omega||12\Omega)$)

In this problem the way to approach this problem is To consider that the current is being divide into two ways with a equivalent resistance and 25Ω resistor. This allows the problem to become much easier. Then after finding the values work backwards in the circuit.

$$20\Omega||12\Omega = (20 \times 12) / (20 + 12) = 7.5\Omega$$

Then, $R_{eq} = 7.5\Omega + 5\Omega = 12.5\Omega$


Find current through the R_{eq} by current division = $[25\Omega / (25\Omega + 12.5\Omega)] \times 2A$

If the current through R_{eq} is 1.333A, then consider the current through the R_{eq} which is divided between a 12Ω and 20Ω resistor.

Therefore using current division again,

$$I_y = [20\Omega / (20\Omega + 12\Omega)] \times (1.333A) = \underline{0.8333A}$$

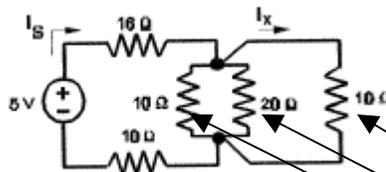(2-52) Use the circuit reduction to find I_s and I_x in the circuit shown in Figure P2-51



The voltage across of these three resistors in parallel is the same. Find $R_{eq} 20\parallel 10\parallel 10$ to solve.


2-52 The total resistance seen by the 5-V source is $R_T := 16 + \frac{1}{\frac{1}{20} + \frac{2}{10}} + 10$

$$R_T = 30 \text{ hence } i_s := \frac{5}{R_T} \quad i_s = 0.167$$

$$i_x := \frac{\frac{1}{10}}{\frac{2}{10} + \frac{1}{20}} i_s \quad i_x = 0.067$$

After considering the 3 resistors in parallel to be an equivalent resistance, find the voltage drops across the remaining resistor that are in series. After finding the voltage drop across the R_{eq} simply use Ohm's law to find current $I_x = \underline{0.067}$.

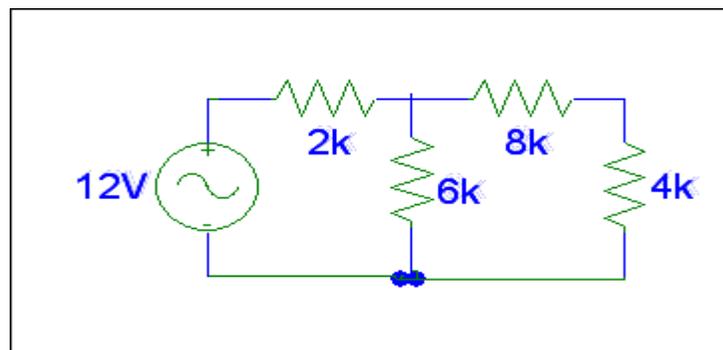(2-54) Use the circuit reduction to find V_x and I_x in the circuit shown in Figure P2-45



First reduce circuit to find the voltage at the node after the 2k Ω resistor. First add together 8 k Ω and 4 k Ω resistors because they are in series which is 12 k Ω . Now consider the 6 k Ω resistor to be in parallel with the 12 k Ω resistor:

$$12 \text{ k}\Omega \parallel 6 \text{ k}\Omega = (6 \times 12) / (6 + 12) = 4 \text{ k}\Omega$$

Now using voltage division find voltage drop across the 4 k Ω resistor.

$$\text{Therefore, } [4\text{k}\Omega / (4\text{k}\Omega + 2\text{k}\Omega)] \times 12\text{V} = 8\text{V}$$

Now use voltage division again to find voltage across the 4 k Ω resistor,

$$\text{Thus, } V_x = [(4 \text{ k}\Omega / (4 \text{ k}\Omega + 8 \text{ k}\Omega))] \times 8\text{V} = \underline{\underline{2.667 \text{ V}}}$$

Hence, the voltage drop across the 2 k Ω resistor is 2.667 V