

CASE WESTERN RESERVE UNIVERSITY
Case School of Engineering
Department of Electrical Engineering and Computer Science

ENGR 210. Introduction to Circuits and Instruments (4)

Homework Set No. 10

References: [T&R4] sections 6-1 to 6-4.

Issued 3/23/05

Due 3/30/05

Waveform partial descriptors

- 1) Measurements of a periodic sinusoidal waveform.**


A periodic waveform can be expressed as $V(t)=100-200\cos\pi t-75\sin 4000\pi t+35\cos 8000\pi t$ millivolts

- (a) What is the period of the waveform?
- (b) What is the average value of the waveform?
- (c) What is the amplitude of the fundamental component?
- (d) What is the highest frequency in the waveform?

Capacitor and inductor responses

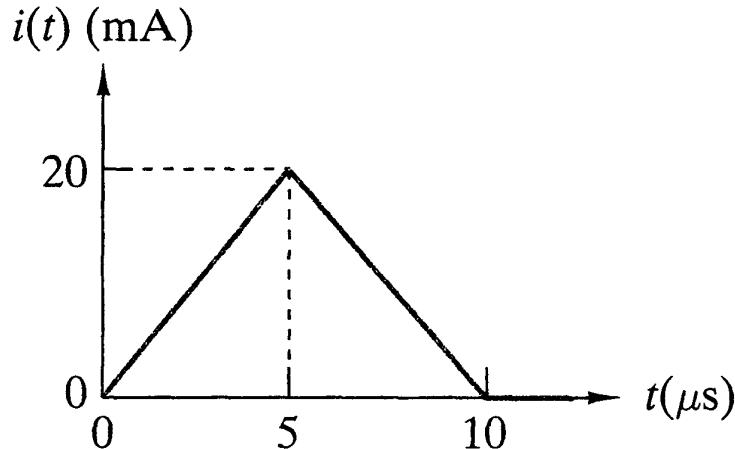
- 2) (5 pts) Problem 6-12, p. 272. Inductive power and energy.**

The current through a 25-mH inductor is shown in the figure below. Prepare sketches of $v_L(t)$, $p_L(t)$, and $w_L(t)$. Is the inductor absorbing power, delivering power, or both?



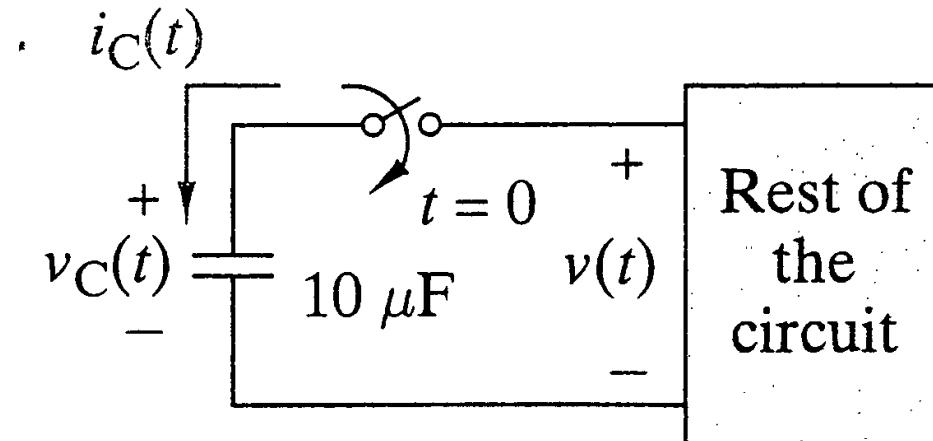3) (5 pts) Problem 6-14, p. 273. Capacitive power and energy.

The capacitor in the figure below carries an initial voltage $v_C(0)=25$ volts. At $t=0$, the switch is closed, and thereafter the voltage across the capacitor is $v_C(t)=50-25e^{-500t}$ volts. Derive expressions for $i_c(t)$ and $p_c(t)$. Is the capacitor absorbing power, delivering power, or both?




Dynamic OP AMP circuits

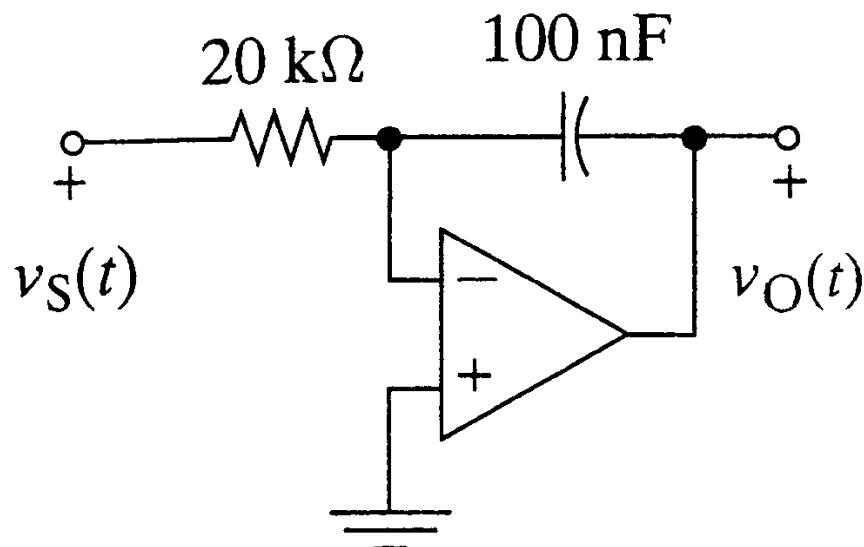4) (5 pts) Problem 6-26, p. 273-274. Integrator.


At $t=0$ the voltage across the capacitor in the figure below is zero. The OP AMP saturates at ± 15 volts.

For $v_s(t)=5[\sin \omega t]u(t)$ volts, derive an expression for the output voltage for the OP AMP in its linear range. What is the minimum value of ω for linear operation?



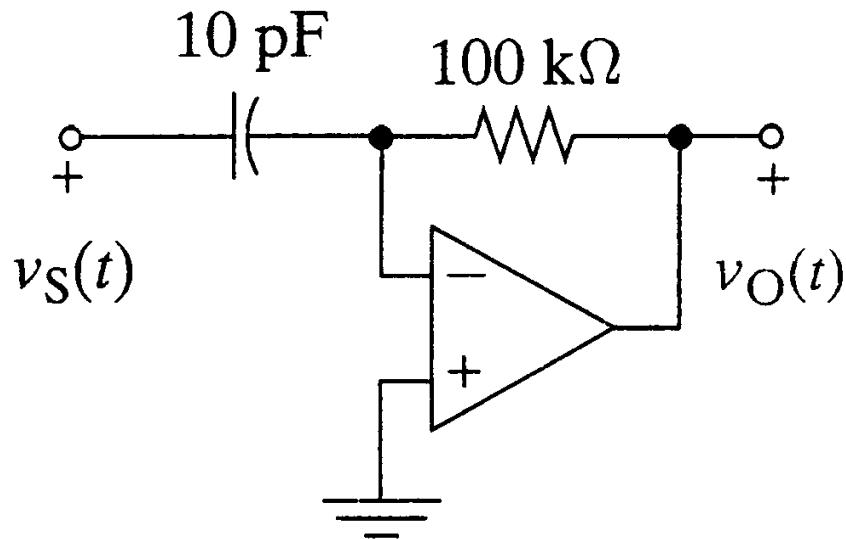5) (5 pts) Problem 6-29, p. 273-274. Integrator.


The input to the circuit shown below is $v_s(t)=5[e^{-\alpha t}]u(t)$ volts. Derive an expression for the output voltage for the OP AMP in its linear range. If the OP AMP saturates at ± 15 volts, what is the maximum value of α for linear operation?




Equivalent inductance and capacitance

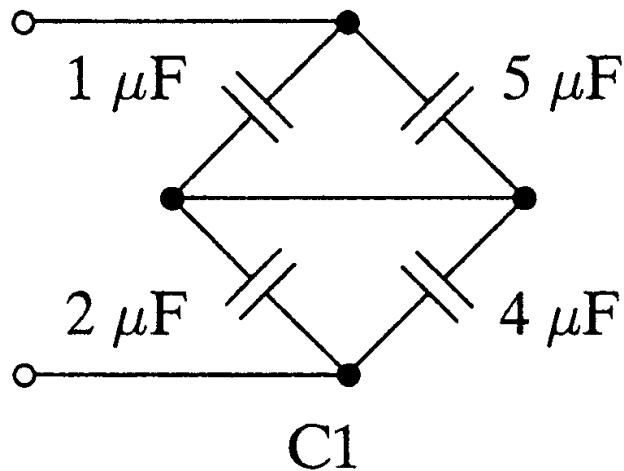6) (5 pts) Problem 6-36, p. 274. Equivalent reactance.

Find a single equivalent capacitance for circuit C1 and a single equivalent inductance for circuit C2.



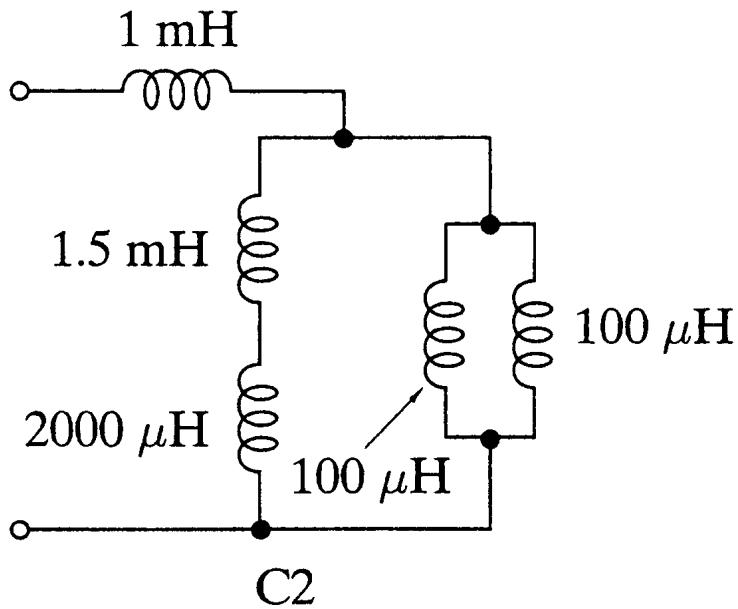

NOTE: Please put your section code AND your CWRU e-mail next to your name at the top of the page. Section codes are

- MA (Monday Afternoon)
- ME (Monday Evening)
- TA (Tuesday Afternoon)
- TE (Tuesday Evening)
- WA (Wednesday Afternoon)
- WE (Wednesday Evening)

Homework is due at the beginning of class on the assigned day.