

CASE WESTERN RESERVE UNIVERSITY
 Case School of Engineering
 Department of Electrical Engineering and Computer Science
ENGR 210. Introduction to Circuits and Instruments (4)

Homework Set No. 6

References: [T&R4] sections 3-5, 3-6, 4-1, 4-2


Issued 2/16/05

Due 2/23/05


MAXIMUM SIGNAL TRANSFER

1) (5 pts)

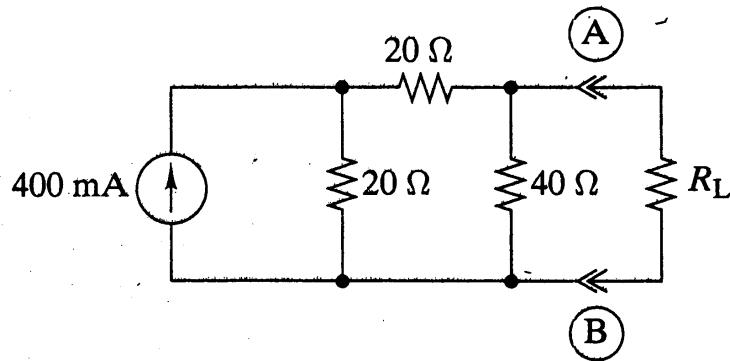- (a) The value of R_L is adjusted such that R_L dissipates the maximum power. What is the value of R_L at which this occurs? What is the maximum power dissipated by R_L ?
- (b) The value of R_L is adjusted such that the voltage between A and B is a maximum. What is the value of R_L at which this occurs? What is the maximum voltage between A and B?
- (c) The value of R_L is adjusted such that the current through R_L is a maximum. What is the value of R_L at which this occurs? What is the maximum current through R_L ?




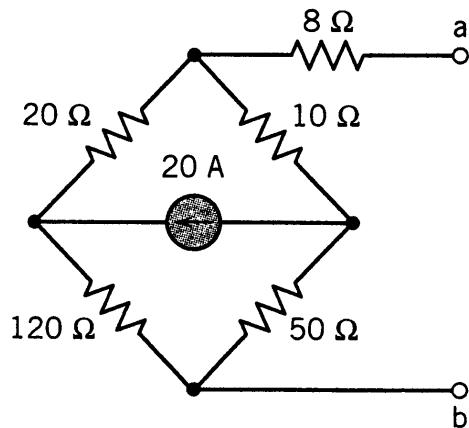- 2) (5 pts)** What is the maximum power that can be delivered to a resistor R_L connected between a and b in the circuit below? What is the value of R_L at which this occurs?



INTERFACE DESIGN

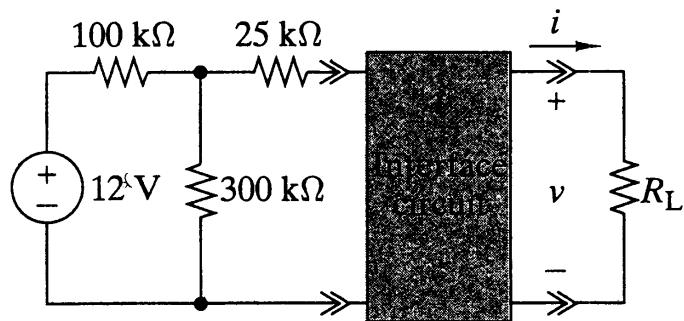
- 3) (5 pts) The black box in the circuit below represents an interface circuit which you will design. Possible interface circuits are listed in Figure 3-52 of our textbook. Select a circuit from Figure 3-52 and specify the component values such that the power delivered to the load never exceeds 1 milliwatt.




LINEAR DEPENDENT SOURCES

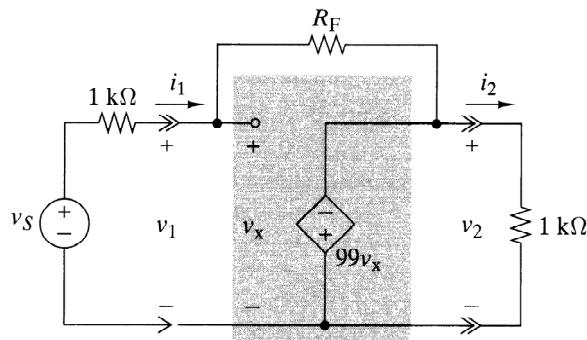- 4) (5 pts) The circuit shown below is an ideal voltage amplifier.

- Find the output voltage v_2 and the current gain i_2/i_1 when $v_s=10\text{mV}$ and $R_F=10\text{k}\Omega$.
- Find the input resistance $R_{IN}=v_1/i_1$.



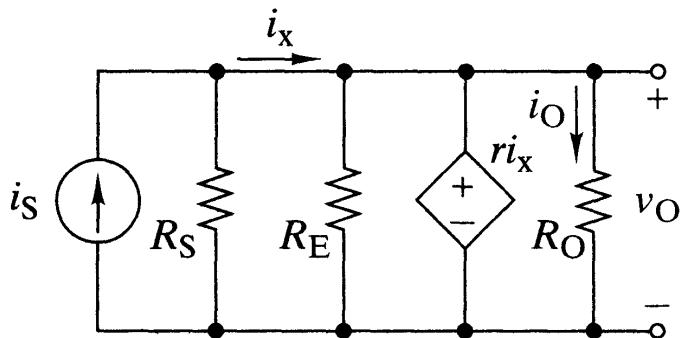- 5) (5 pts) Find an expression for the current gain i_o/i_s in the circuit below.



COMPARISON OF ANALYSIS METHODS

- 6) (5 pts)** Determine the node voltage v_c and the current i_x in the circuit shown below using
(a) mesh analysis and
(b) node analysis.

