

**CASE WESTERN RESERVE UNIVERSITY**  
 Case School of Engineering  
 Department of Electrical Engineering and Computer Science

**ENGR 210. Introduction to Circuits and Instruments (4)**

**Homework Set No. 8**

References: [T&R4] sections 4-4, 4-5, 4-7


Issued 3/2/05

Due 3/16/05

**MULTIPLE OP-AMP CIRCUITS**

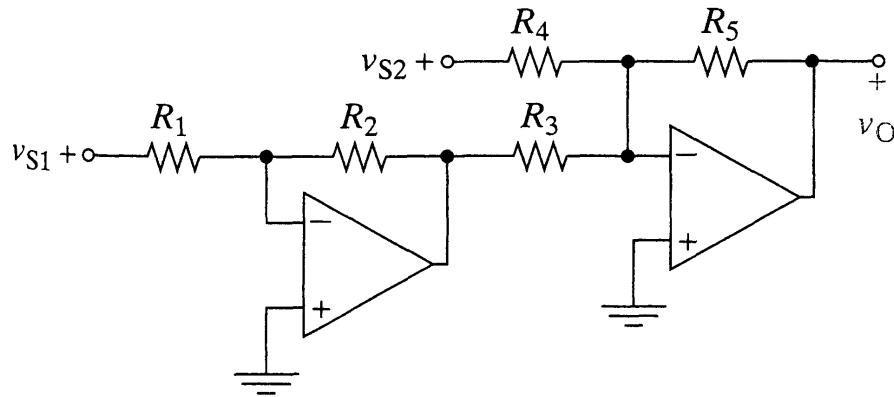
- 1) (5 pts) . Cascaded Amplifier**

Find  $v_o$  in terms of  $v_{s1}$  and  $v_{s2}$  for the circuit below.



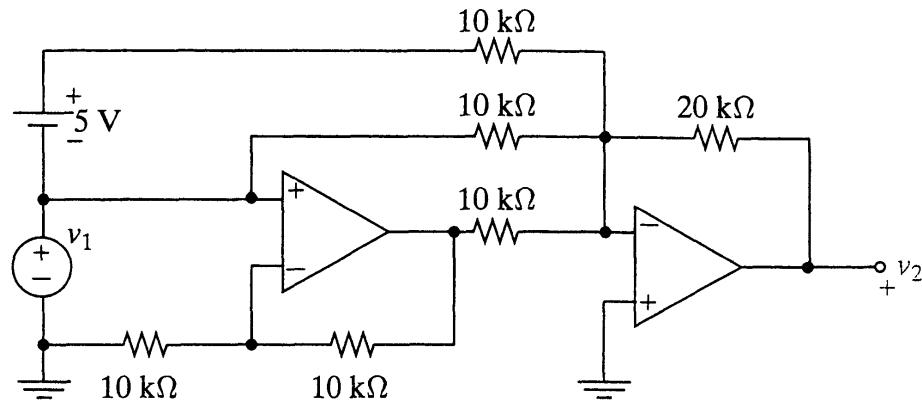- 2) (5 pts) Summing amplifier.**

Find the output  $v_2$  in terms of the input  $v_1$ .



**3) (5 pts) Subtractor circuits.**

The input/output relationships for CIRCUIT 1 and CIRCUIT 2 are of the form  $v_o = K_2 v_2 + K_1 v_1$ .


(a) For CIRCUIT 1 and CIRCUIT 2 determine  $K_1$  and  $K_2$  in terms of circuit parameters.

(b) In CIRCUIT 1 with  $R_1 = R_2 = 1\text{k}\Omega$  and  $R_3 = R_5 = 10\text{k}\Omega$ , select the values  $R_4$  and  $R_6$  that produce  $v_o = 5(v_2 - v_1)$ .


(c) In CIRCUIT 2 with  $R_1 = R_2 = 1\text{k}\Omega$  and  $R_3 = R_5 = 10\text{k}\Omega$ , select the values  $R_4$  and  $R_6$  that produce  $v_o = 5(v_2 - v_1)$ .

(d) Evaluate the two designs by comparing the number of devices each circuit requires and the input resistance seen by the signal courses  $v_1$  and  $v_2$ .

CIRCUIT 1:

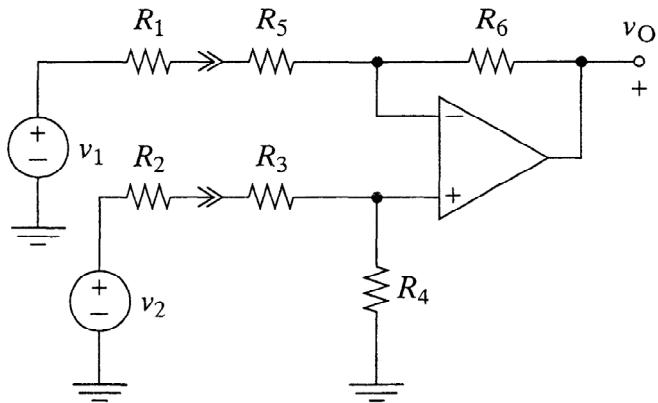

CIRCUIT 2:

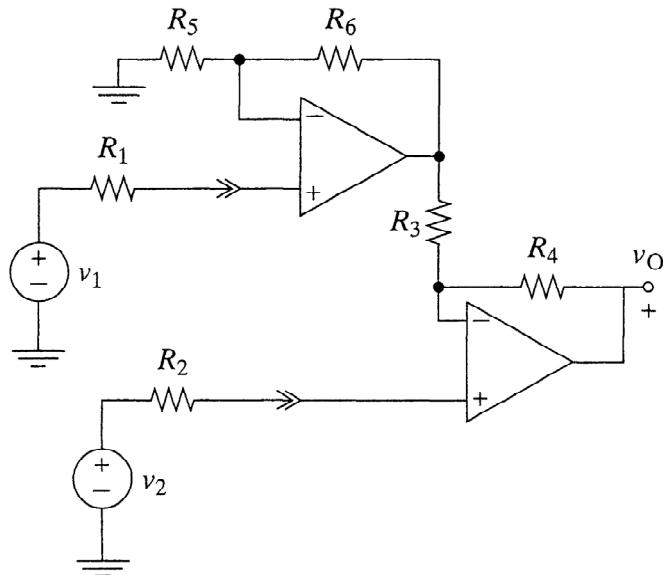


### OP-AMP COMPARATOR

- 4) (5 pts) Use power supply for reference.

The circuit shown below has  $V_{OH}=15$  volts and  $V_{OL}=0$  volts.

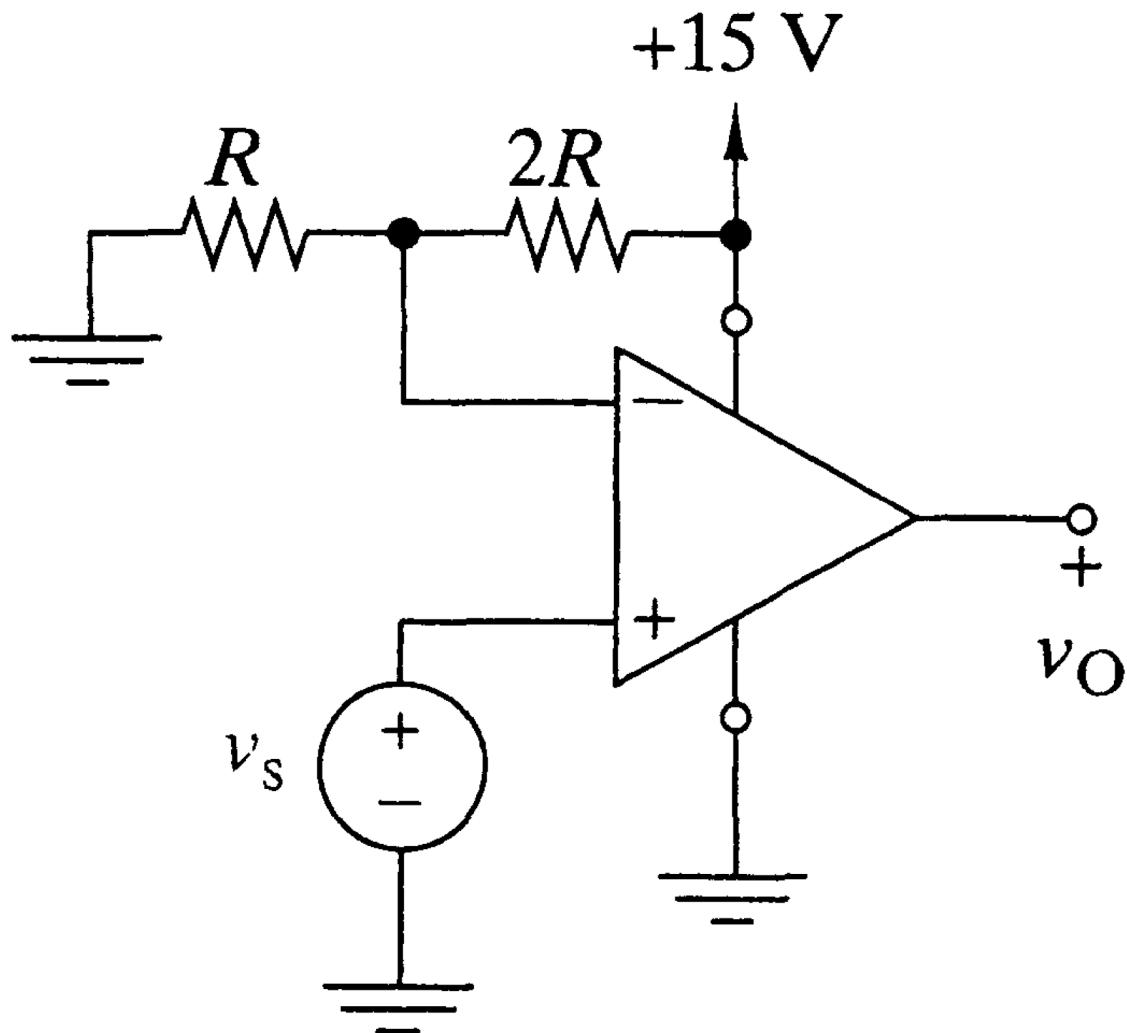- (a) Determine the input voltage range for which  $v_o=V_{OH}$  and  $v_o=V_{OL}$ .
- (b) Sketch the circuit transfer characteristics for  $v_s$  over the range -15 to +15 volts.




- 5) (5 pts) Use the battery as your voltage reference.

The circuit shown below has  $V_{OH}=10$  volts and  $V_{OL}=0$  volts.

- (c) Determine the input voltage range for which  $v_o = V_{OH}$  and  $v_o = V_{OL}$ .

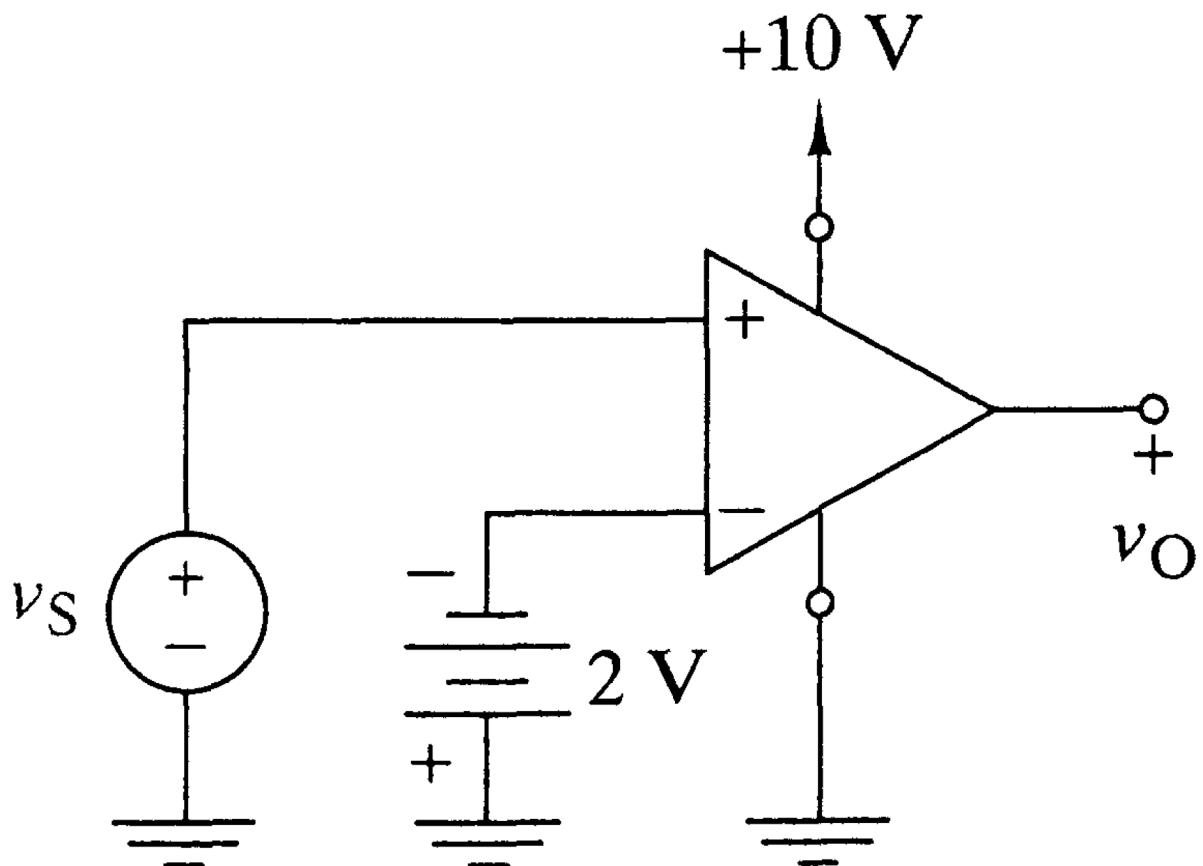(d) Sketch the circuit transfer characteristics for  $v_s$  over the range -15 to +15 volts.



**NOTE: Please put your section code AND your CWRU e-mail next to your name at the top of the page.** Section codes are

**MA (Monday Afternoon)**

### **ME (Monday Evening)**

TA (Tuesday Afternoon)

TE (Tuesday Evening)

WA (Wednesday Afternoon)

WE (Wednesday Evening)