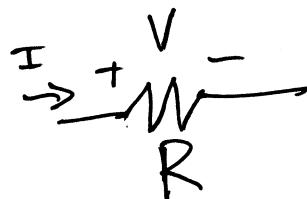




law of Bel
power $P = IV$



unit: Watts




$$V = IR$$

~~for
B - mo~~

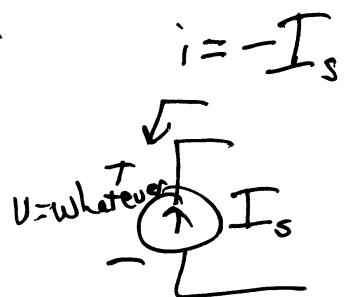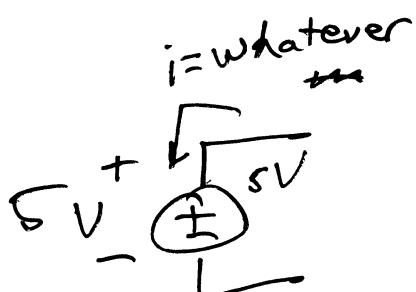


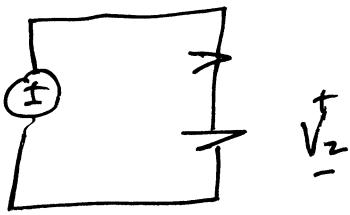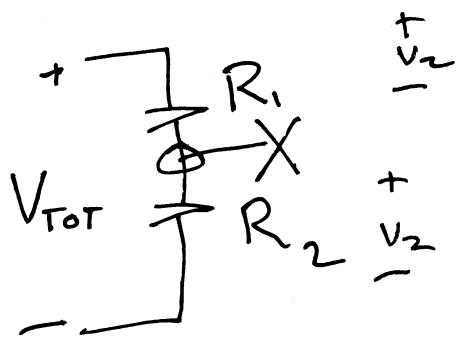
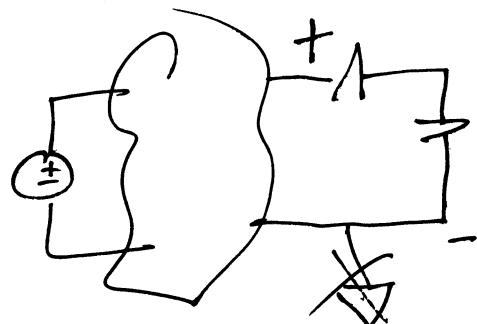
$$V_2 = V_{TOT} \cdot \frac{R_2}{R_1 + R_2}$$




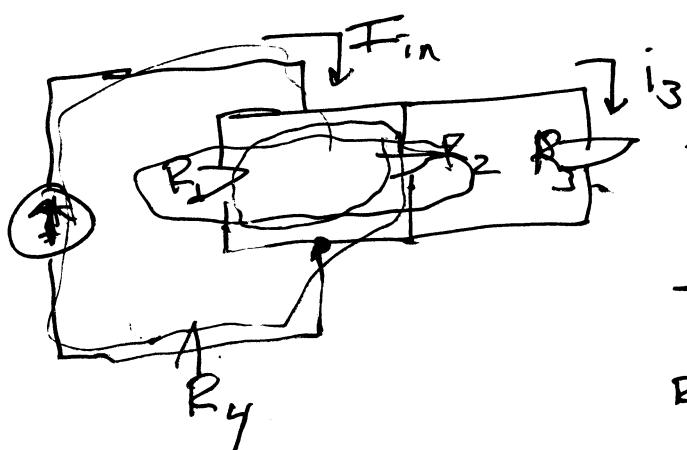
$$V_3 = V_{TOT} \cdot \frac{R_3}{\sum R_i}$$



$$i_3 = I_{IN} \cdot \frac{\frac{1}{R_3}}{\sum \frac{1}{R_i}}$$

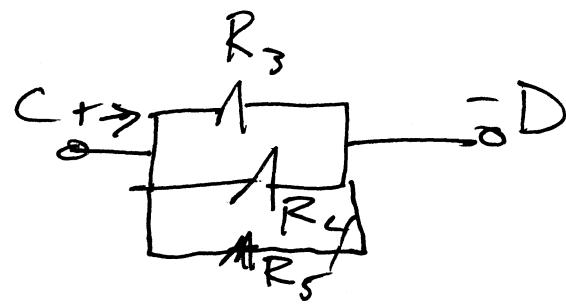
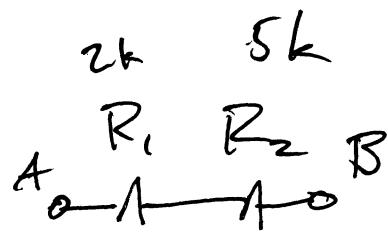
$$i_2 = i_{in} \cdot \frac{R_1}{R_1 + R_2}$$



$$R_1 + R_2 = 7k$$


$$\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

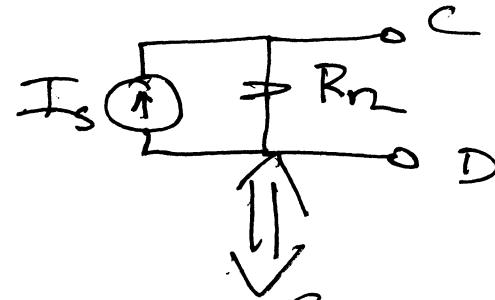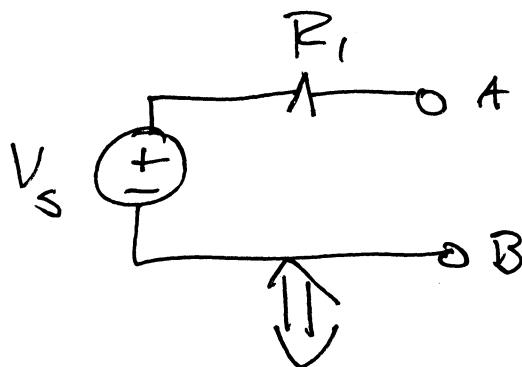
$$\frac{R_3}{R_3 + R_4} \Rightarrow \frac{A}{R_3 R_4 / (R_3 + R_4)}$$



$$I = \frac{V_s}{R_1}$$

$$V = I_s R_2$$

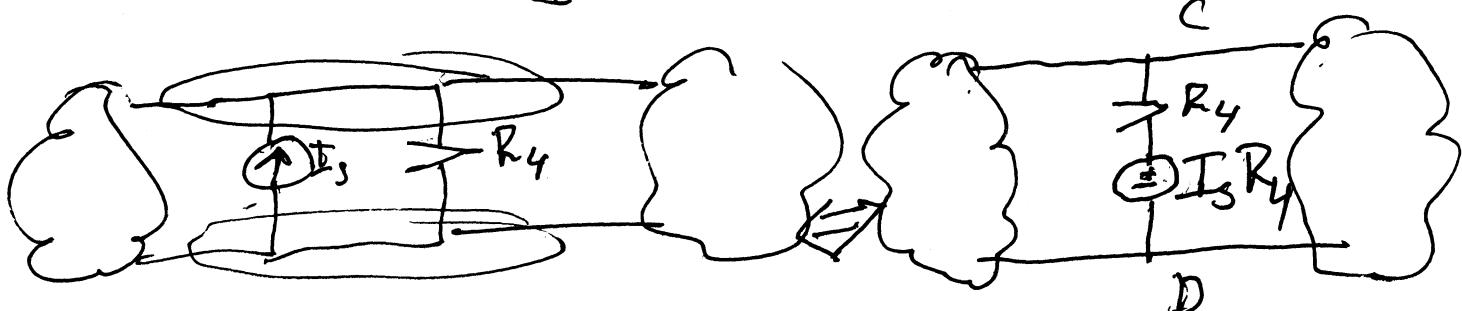

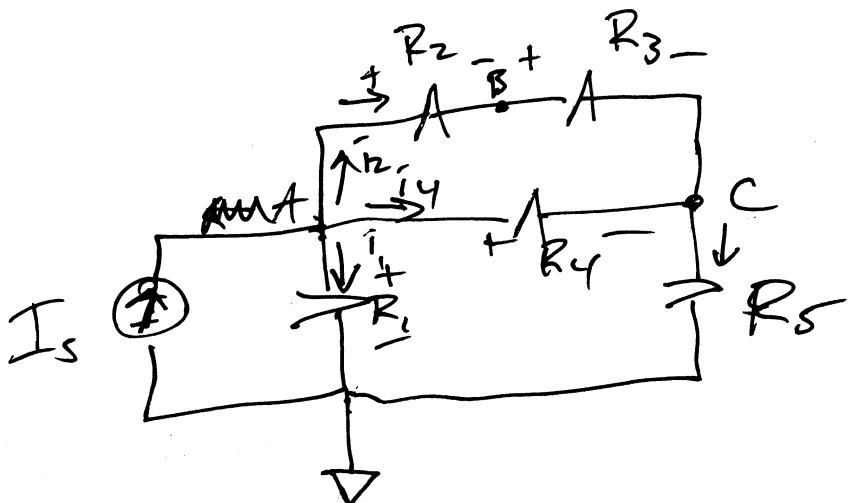


$$A: \quad i_1 + i_2 + i_4 = I_s$$

$$\frac{V_A - 0}{R_1} + \frac{V_A - V_B}{R_2} + \frac{V_A - V_C}{R_4} = I_s$$



(A) $\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}\right)V_A - \frac{1}{R_2}V_B - \frac{1}{R_4}V_C = I_s$


$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}\right)V_A$$

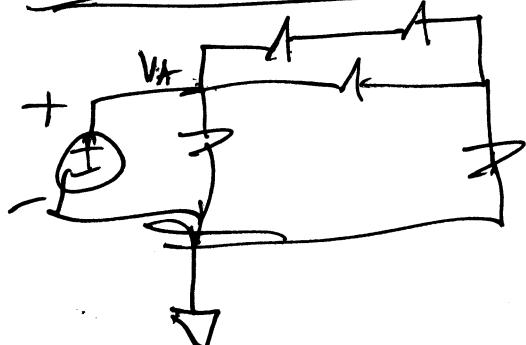(C) $-\frac{1}{R_4} \cdot V_A - \frac{1}{R_3} \cdot V_B + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)V_C = \cancel{I_s}$




$$(V_A - 0) = V_S$$

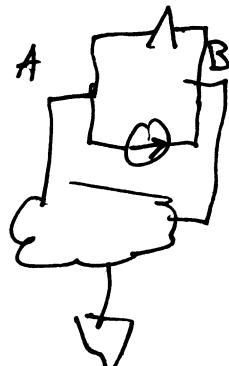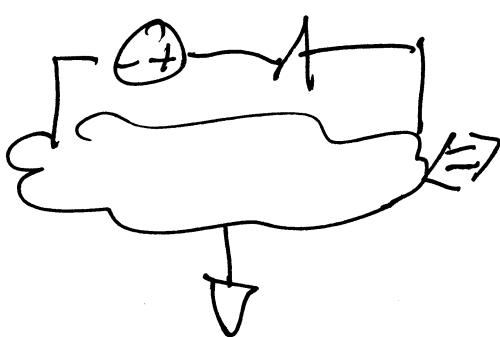

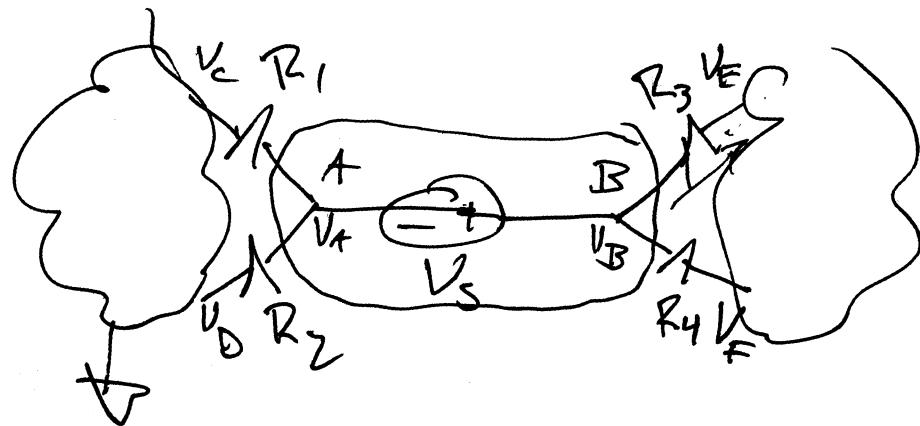


$$\begin{aligned}
 SN: & \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A + \left(\frac{1}{R_3} + \frac{1}{R_4} \right) V_B \\
 & - \frac{1}{R_1} V_C - \frac{1}{R_2} V_D - \frac{1}{R_3} \cdot V_E - \frac{1}{R_4} \cdot V_F = 0
 \end{aligned}$$

$$V_s = V_B - V_A$$

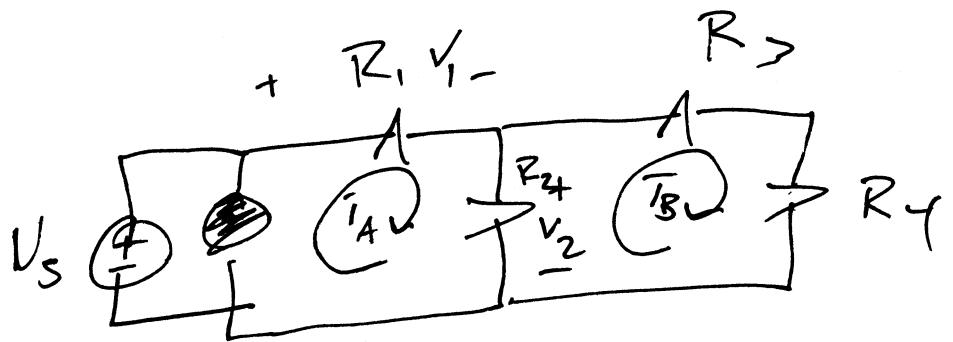



$$-V_s + V_1 + V_2 = 0$$
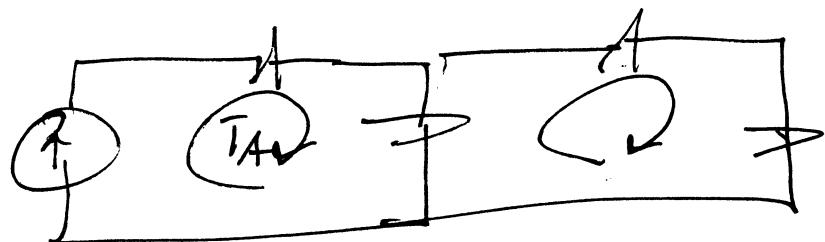
$$-V_s + \bar{I}_A R_1 + (I_A - \bar{I}_B) R_2 = 0$$





$$\bar{I}_A = I_s$$

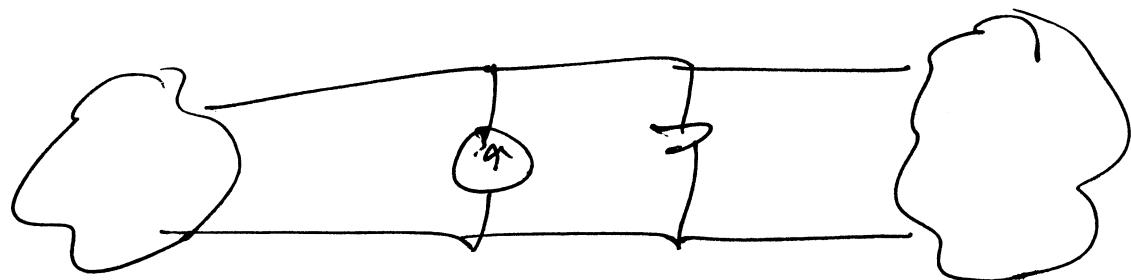

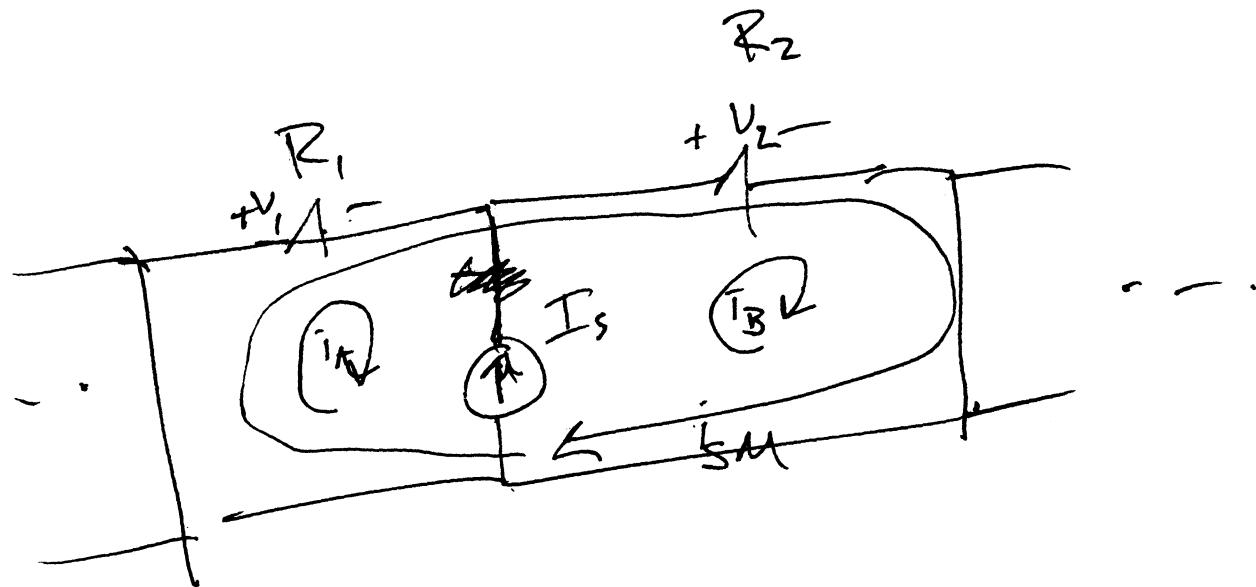

$$\begin{cases} V_1 + V_2 = 0 \\ i_A R_1 + i_B R_2 = 0 \end{cases}$$

$$I_S = i_B - i_A$$

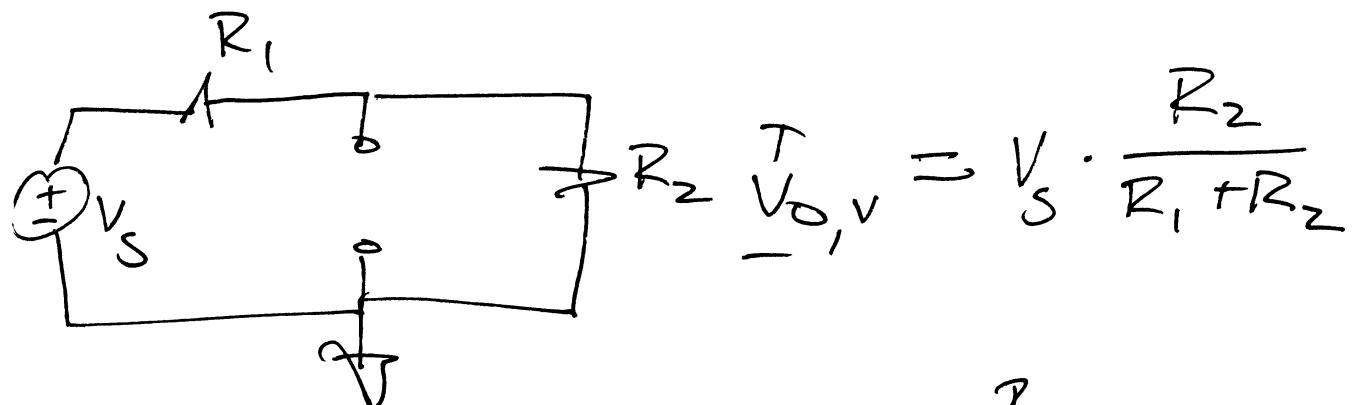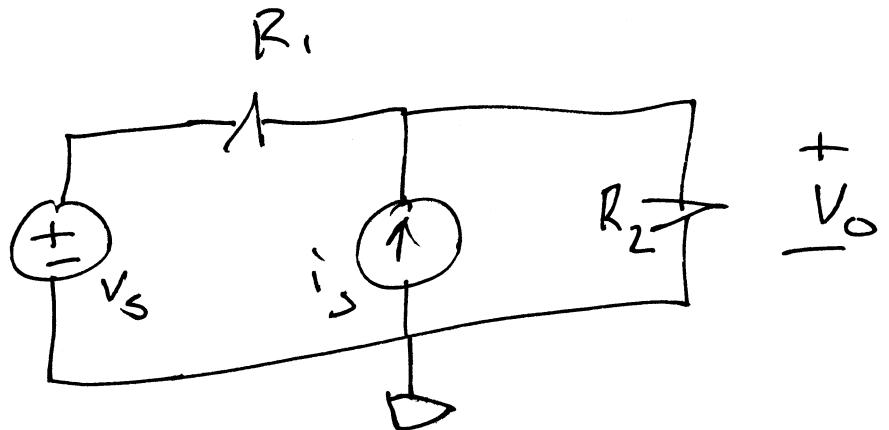

Circuit diagram showing a voltage source V_s connected in series with resistor R_1 . The output current $I_{o,I}$ is measured through resistor R_2 .

$$I_{o,I} = I_s \cdot \frac{R_1}{R_1 + R_2}$$

$$= i_s \frac{R_1 R_2}{R_1 + R_2}$$


$$I_2 = i_s \cdot \frac{R_1}{R_1 + R_2}$$

$$V_o = V_s \frac{R_2}{R_1 + R_2} + i_s \frac{R_1 R_2}{R_1 + R_2}$$

inductors/capacitors $i_c = C \frac{dV_c}{dt}$


$$V_L = L \frac{di_L}{dt}$$

Exercise 6.1

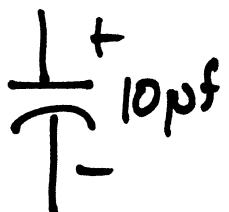

Given

$$V_c = 25 [\sin 2000t] u(t)$$

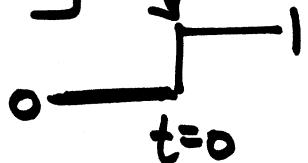

$$i_c = C \frac{dV_c}{dt}$$

$$= (10 \times 10^{-6}) \cancel{25} 2000 \cos 2000t \quad t \geq 0$$

$$= 0.5 \cos 2000t \quad t \geq 0$$


$$= 0.5 [\cos 2000t] u(t)$$

$$V_c(0) = -5 \text{ volts}$$

$\begin{array}{c} i_c \\ \downarrow \\ \text{---} \\ \text{---} \end{array}$

100 pF
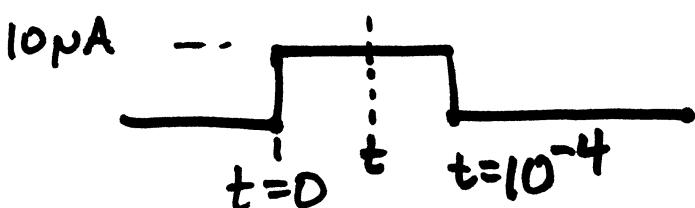
$$\text{Given } i_c = 10 [u(t) - u(t-10^{-4})] \mu A$$



$$100 \times 10^{-12}$$

find V_c use $i_c = C \frac{dV_c}{dt}$

$$\int_0^t \frac{1}{C} i_c dt = \int_0^t dV_c \quad \text{for } t < 10^{-4}$$

$$\frac{1}{C} \int_0^t \frac{10 \times 10^{-6}}{100 \times 10^{-12}} dt + t \Big|_0^t$$

$$= V_c(t) - V_c(0)$$

$$= V_c(t) - (-5)$$

$$\frac{10 \times 10^{-6}}{100 \times 10^{-12}} [t-0] = V_c(t) + 5$$

$$10000t = V_c(t) + 5$$

$$V_c(t) = 10000t - 5 \leftarrow$$

$$i_c = C \frac{dV_c}{dt}$$

for $t > 10^{-4}$

$$\int_{10^{-4}}^t \frac{1}{C} i_c dt = \int_{10^{-4}}^t dV_c$$

start at $t=10^{-4}$

$$\frac{1}{C} \int_{10^{-4}}^t 0 \cdot dt = V_c(t) - V_c(10^{-4})$$


$$0 = V_c(t) - V_c(t=10^{-4})$$

$$V_c(t) = V_c(t=10^{-4})$$

What $V_c(t=10^{-4})$ use first formula

$$V_c(t=10^{-4}) = 10000(10^{-4}) - 5$$

$$= 10 - 5 = +5 \text{ volts.}$$

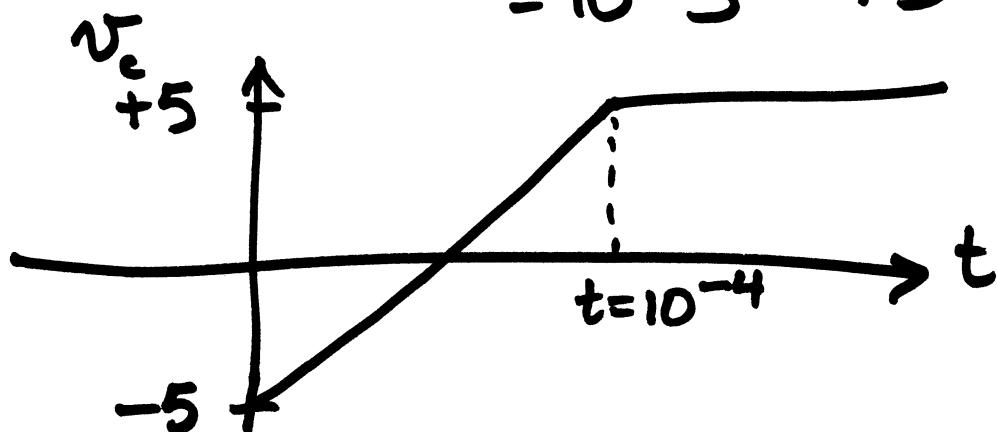

Exercise 6-2

$$v_c = 5e^{-4000t} \text{ V.}$$

capacitor
200pf


$$i_c = C \frac{d v_c}{dt} \quad \text{find } i_c$$

$$= (200 \times 10^{-12}) \left[5(-4000)e^{-4000t} \right] \text{ P}$$

$$i_c = -4e^{-4000t} \mu\text{A}$$

$\frac{4 \times 10^{-6}}{-4000t}$
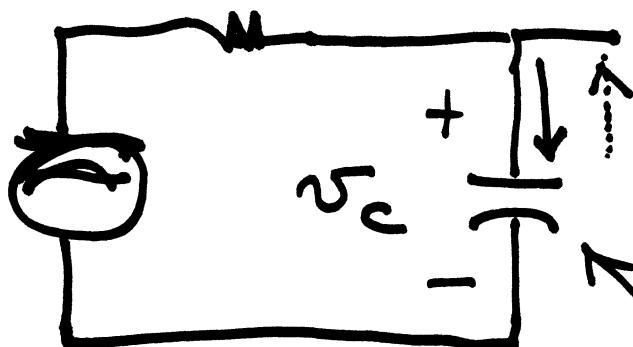
$$\begin{aligned} P &= v_i i = (5e^{-4000t}) (-4e^{-4000t}) \\ &= -20e^{-8000t} < 0 \end{aligned}$$



$$P > 0$$


i_c leaving capacitor
supplying power
to the circuit

Phasors

8-3)

$$\cos \omega t$$

$$10 \cos 4000t \text{ V.}$$

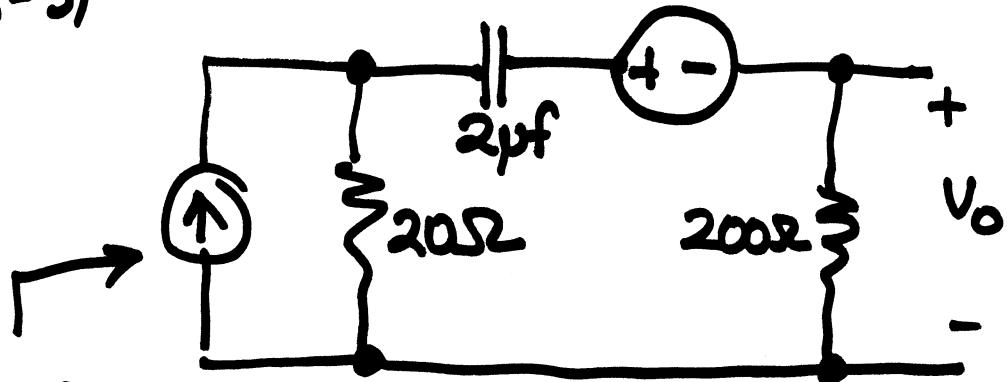

~~sin 2000~~

$3 \sin 4000t \text{ A}$

① what frequency is this operating at.

$$4000 \leftarrow \omega \text{ radian/sec.}$$

$$\omega = 2\pi f \quad \frac{\omega}{2\pi} \leftarrow f \text{ cycles/sec}$$

$$\frac{4000}{2\pi} = 637 \text{ Hz cycles/sec.}$$

② transform to phasor (= sinusoidal steady state)

$$200\Omega \rightarrow 200\Omega \quad \frac{1}{j} = -j$$


$$20\Omega \rightarrow 20\Omega$$

$$2\mu\text{F} \rightarrow \frac{1}{j\omega C} = \frac{1}{j(4000)(2 \times 10^{-6})} = -j125$$


$$10 \cos 4000t \rightarrow 10 \angle 0^\circ = 10 \quad \begin{matrix} \text{mag} \\ \text{real} \\ 10 \end{matrix}$$

$$\sin 4000t \rightarrow 1 \angle 0^\circ$$
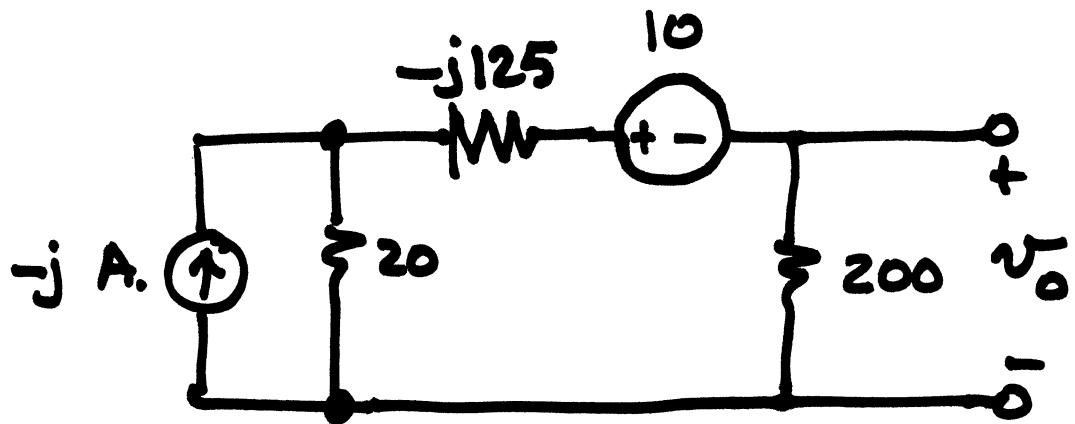
$$\cos(4000t - 90^\circ) \rightarrow 1 \angle -90^\circ = -j \quad \begin{matrix} \text{real} \\ -90^\circ \end{matrix}$$



Source transform:

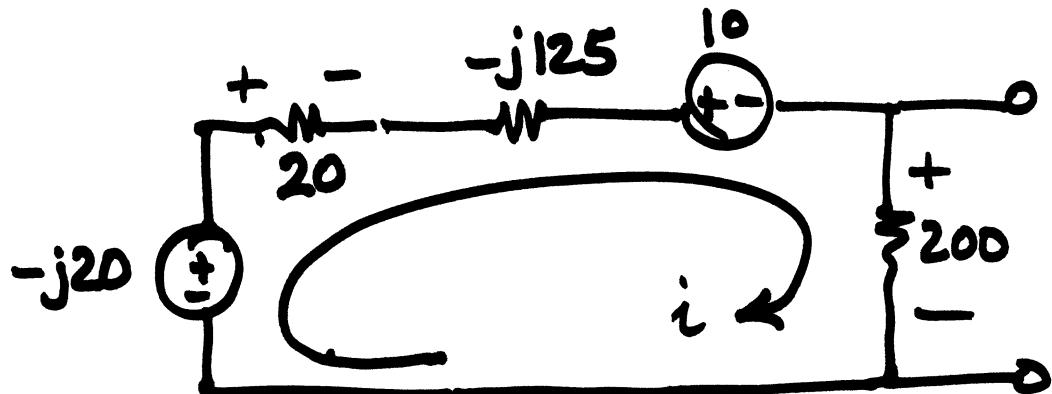

$$V = I Z = (-j) 20 = -j 20$$

$$\text{using KVL} \quad -(-j 20) + 20i + (-j 125)i + 10 + 200i = 0$$

$$+ \underline{j 20} + \underline{20i} - \underline{j 125i} + \underline{10} + \underline{200i} = 0$$

$$220i - j 125i = -10 - j 20$$



$$i = \frac{-10 - j 20}{220 - j 125} = .004686 - j .08825$$

$$V_o = i 200 = () (200 + j 0) = \underline{0.937 - j 17.65}$$

$$V_o = 17.67 \angle -87^\circ$$


$$V_o(t) = 17.67 \cos(4000t - 87^\circ)$$

superposition

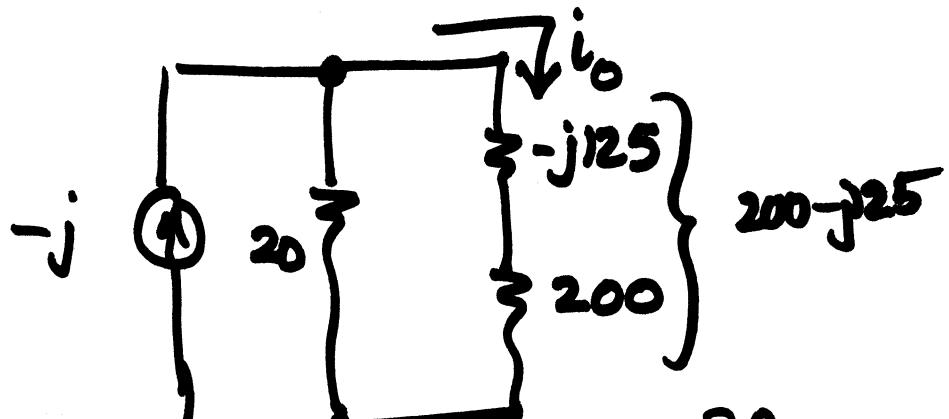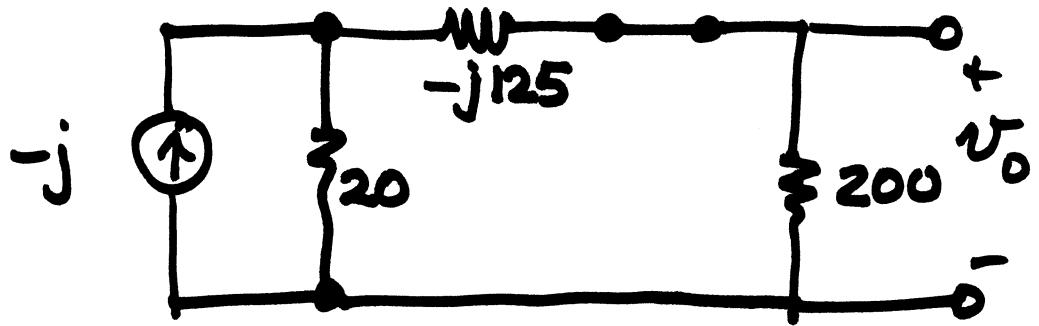

current divider $i_o = \frac{20}{20+200-j125} (-j)$

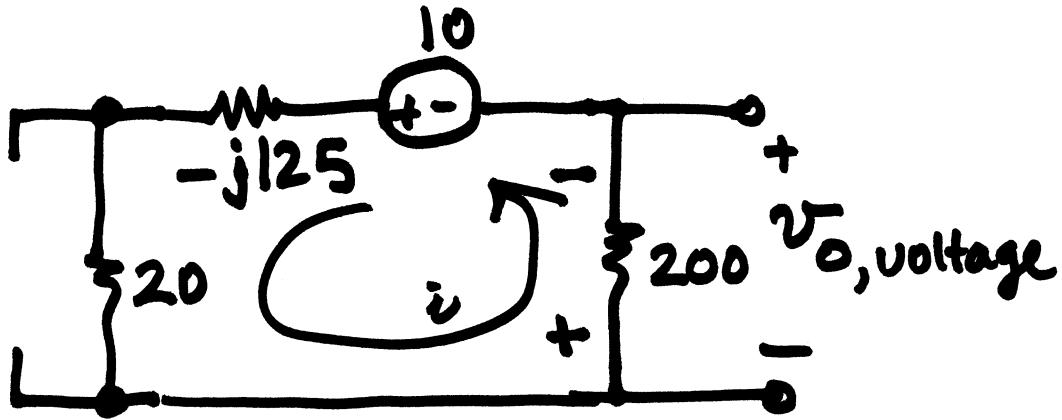
$v_o = 200 [i_o] = 200 \left[\frac{-j20}{220-j125} \right]$



voltage divider

$$V_o = - \frac{200}{-j125 + 20 + 200} \cdot 10$$

$$= \frac{-2000}{220-j125}$$

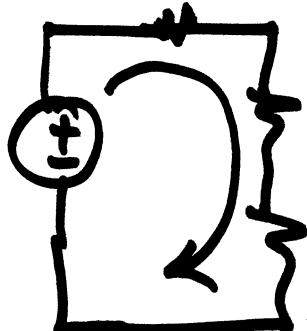

$$V_o = V_{o, \text{voltage}} + V_{o, \text{current}}$$

$$= \frac{-2000}{220-j125} + \frac{-j4000}{220-j125}$$


$$= \frac{-2000-j4000}{220-j125} = \checkmark$$


Phasor Domain

$$\vec{V}(j)$$

Time Domain

$$t$$

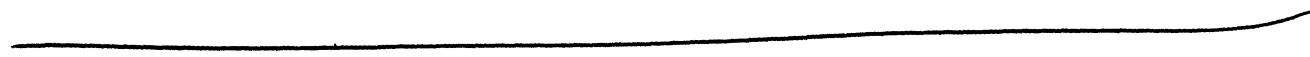

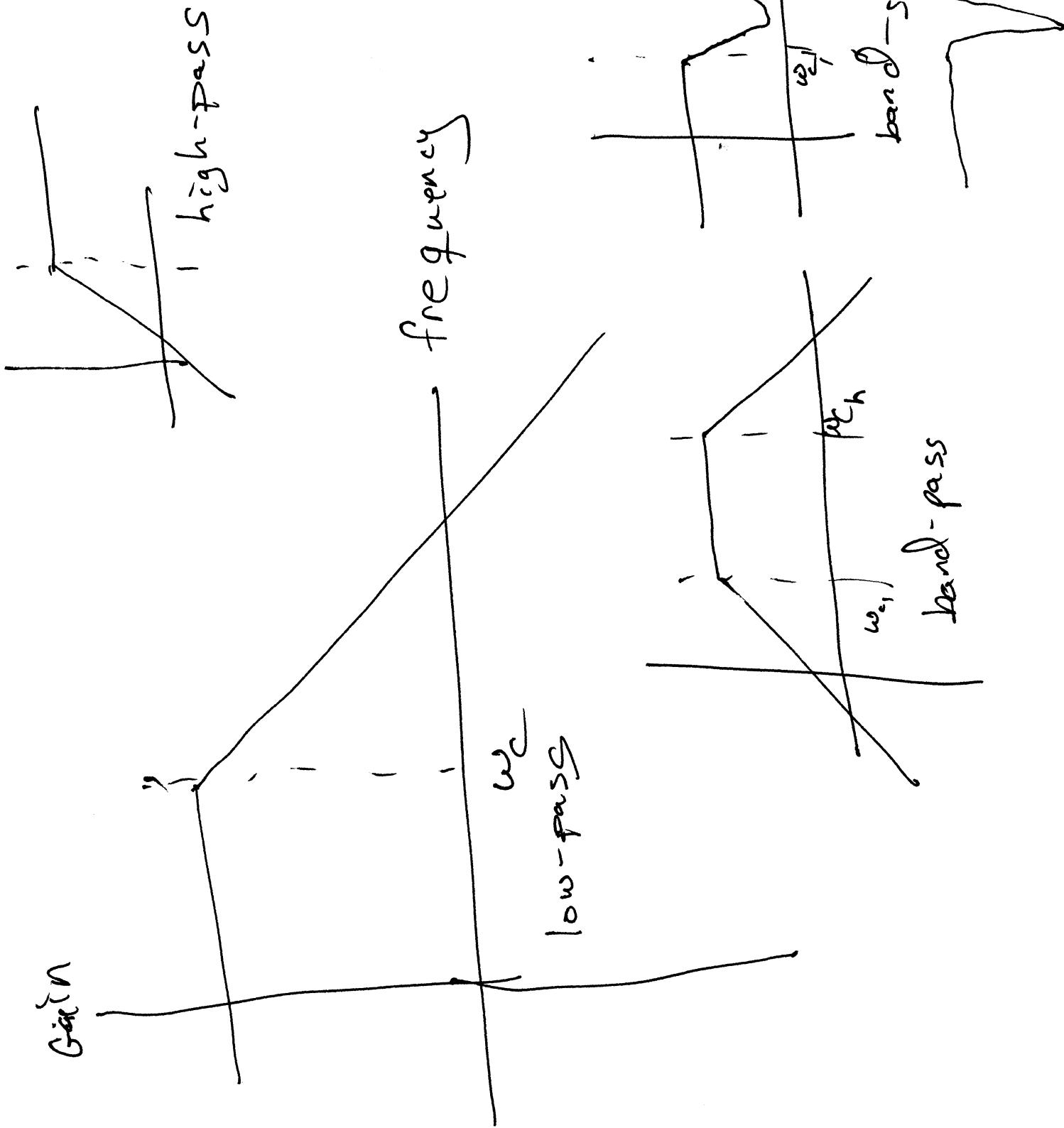


$$T_V = \frac{V_o}{V_i} = \frac{2000}{10 + j \frac{\omega}{200}} \quad \text{3 denominators}$$

$$= \frac{200}{1 + j \frac{\omega}{200}} \quad \text{low pass}$$

$$\frac{1}{1 + j \frac{\omega}{200}} = \frac{1200; \omega}{1 + j \frac{\omega}{2000}} \quad \text{high pass}$$


$$\text{in } Q_B = 20 \log_{10} (T_V)$$

$$1 T_V | Q_B = 46 \quad 20 \text{dB/decade}$$

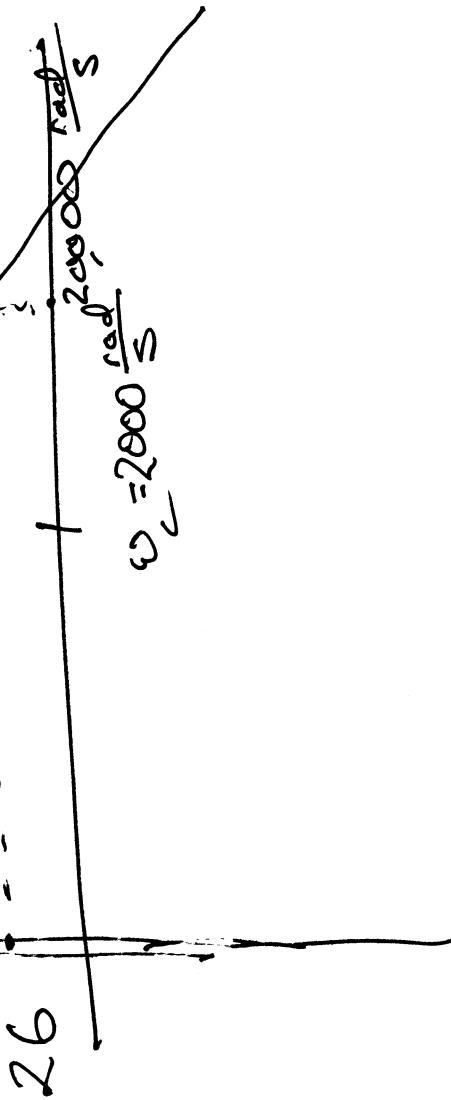


$$\frac{200 \int \omega}{1 + j \frac{\omega}{2000}} \quad |H_V(\omega \rightarrow \infty)| = \frac{200 \text{ rad/s}}{\frac{j\omega}{2000}}$$

$$= 400,000$$

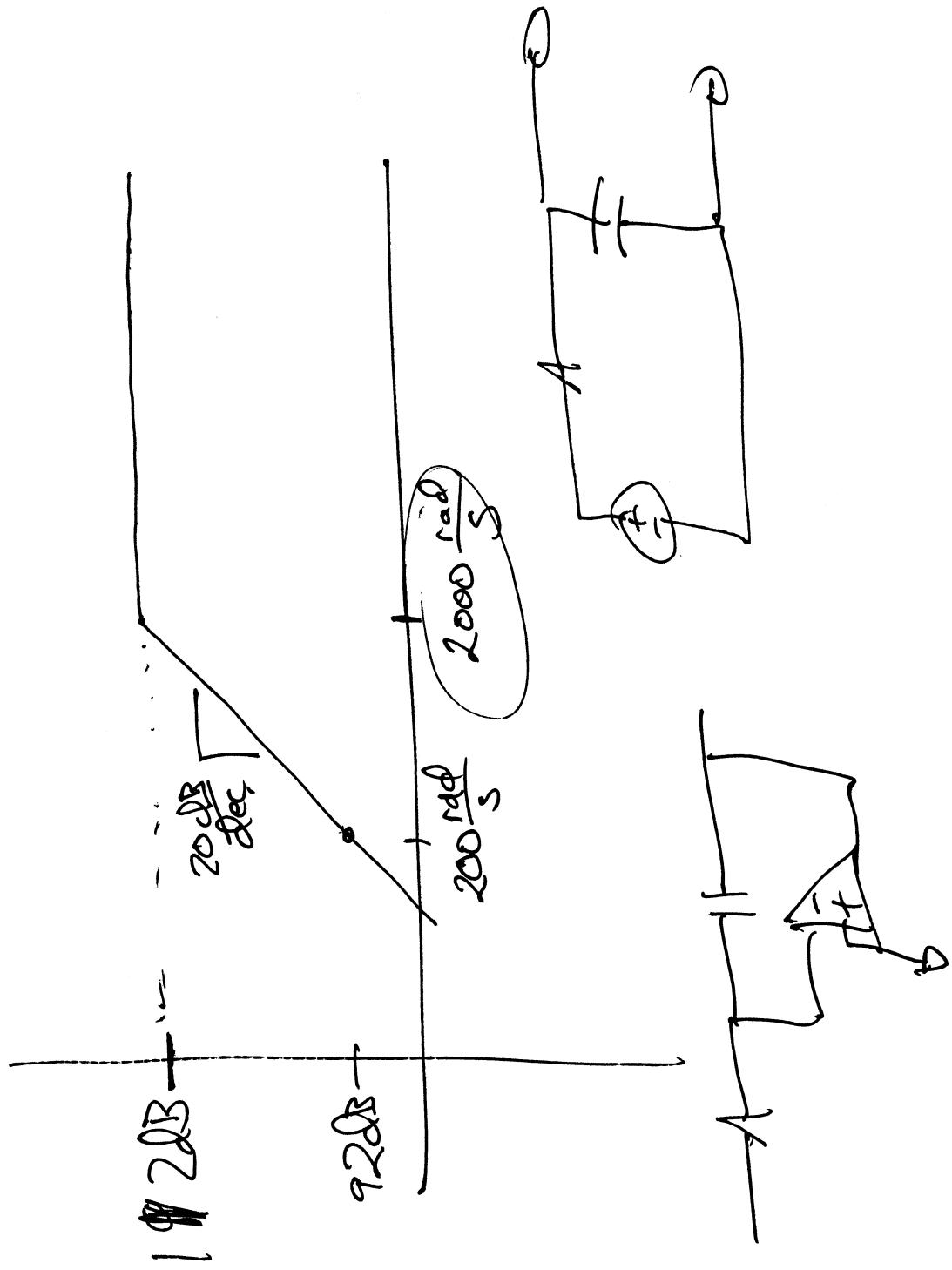


$$HW(B-4)$$

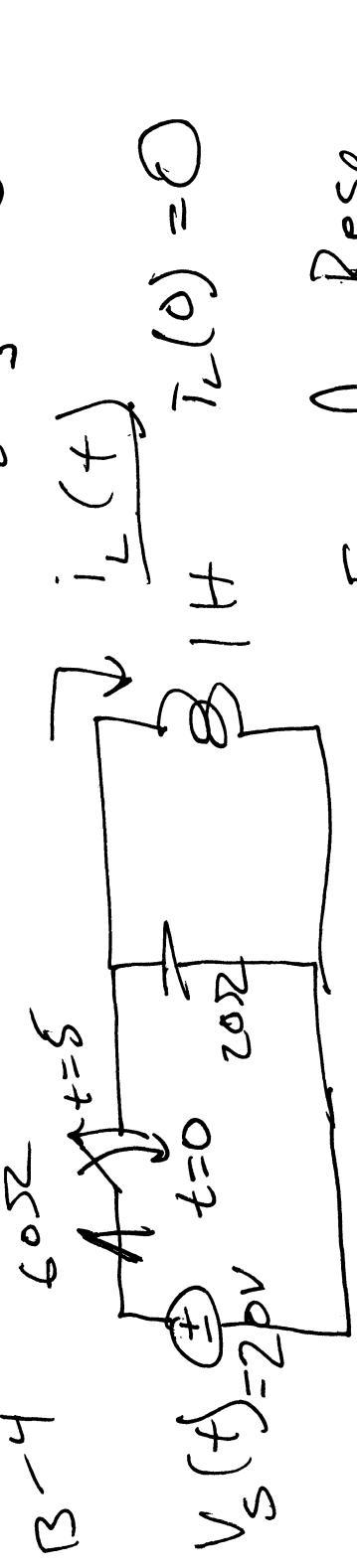

Natural Resp.

$$t > 0$$

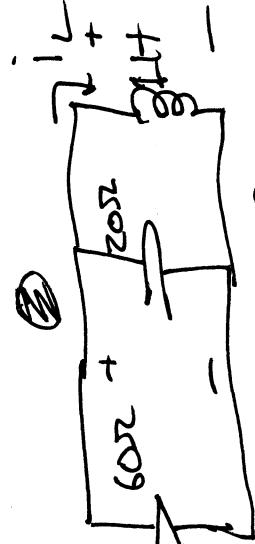

~~i_{natural}~~ \rightarrow i_{natural}-thse





$$i_L = \frac{Kc}{s+R}$$

$$i_L = Kc e^{st} + \frac{i_L}{s+R} = 0$$

$$\frac{di_L}{dt} = K_c e^{st} L \frac{di_L}{dt} + i_L s + R K c e^{st} = 0$$

$$L K_c e^{st} (L s + R) = 0$$

Forced Resp.

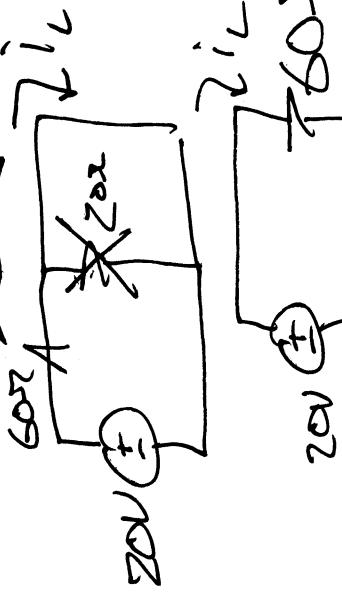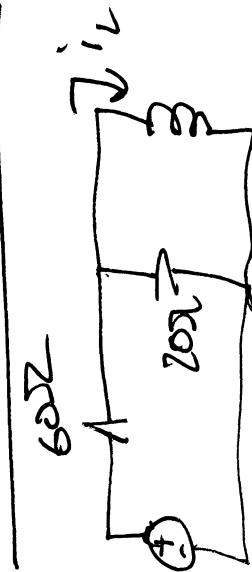

$$i_{L,\text{forced}} = \frac{20\sin t}{6\Omega + 2\Omega} = \frac{1}{3} A$$

$$i_L = \frac{1}{3} A + \frac{1}{3} e^{-\frac{2}{3}t} + \frac{1}{3} A + \frac{1}{3} e^{-\frac{2}{3}t}$$

$$s = -\frac{R}{L}$$


$$K_c = \frac{1}{3} A + \frac{1}{3} e^{-\frac{2}{3}t}$$

$$t \neq 0 \Rightarrow i_L = 0$$

$$0 \leq t < 20ms \Rightarrow i_L = \frac{1}{3}A - \frac{1}{3}Ae^{-15t} \quad 60\Omega$$

$$t \geq 20ms \Rightarrow i_L = 0.129e^{-20t} \quad 20V$$

i_L

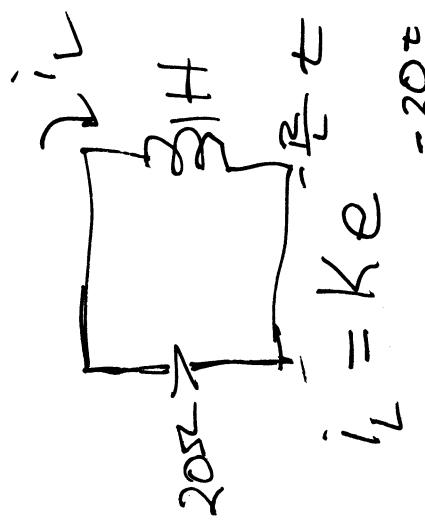

$$i_L = K e^{-20t}$$

$$i_L(20ms) = K e^{-0.4} = K e^{-0.4}$$

$$0.086 = K e^{-0.4}$$

$$\frac{0.086}{K} = e^{-0.4}$$

$$\frac{0.086}{K} = e^{-0.4}$$



$$K = \frac{0.086}{e^{-0.4}} = 0.129$$

i_L

$t \geq 20ms$



$i_L = K e^{-0.4}$

Hw 13-5

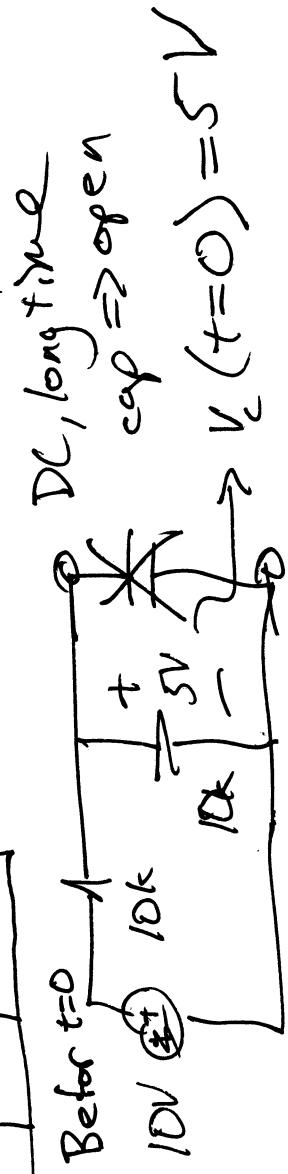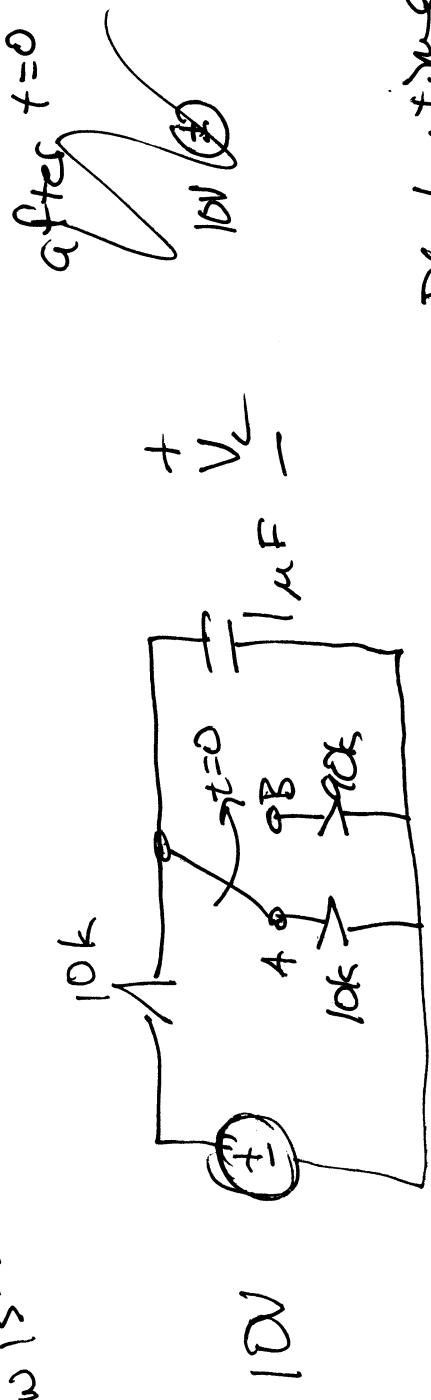

$$\begin{aligned}
 V_c &= 10V \cdot \frac{90\%}{10k + 90k} \\
 FV &= 9V \\
 V_c &= [9V - 9V] e^{-t/\tau_c} + 9V \\
 &= [9V - 9V] e^{-t/9ms} + 9V \\
 \tau_c &: \text{Capacitor time constant} \\
 T_{c, \text{cap}} &: R C = 9ms \\
 T_{c, \text{ind}} &: L/R
 \end{aligned}$$

equiv. ckt's.

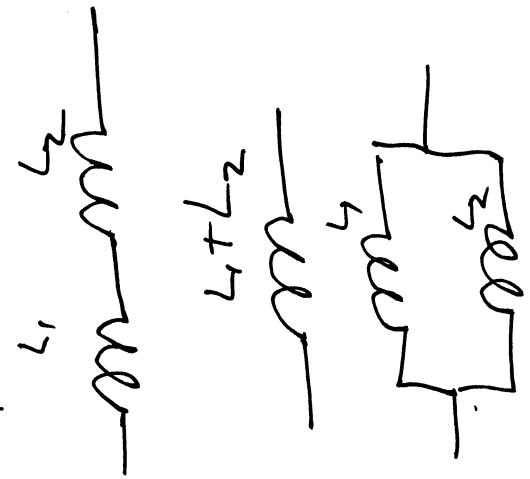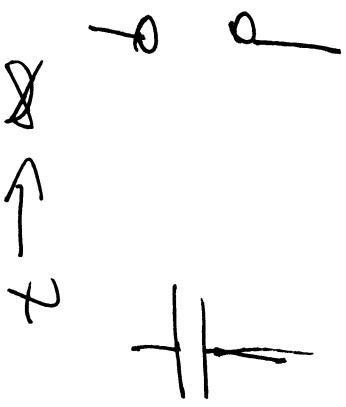

$$C_1 \parallel C_2 = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$$

$$C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$$