

Two Techniques - used by CAD programs

Multi Sim 7

Electronics Workbench


node voltage (KCL based)

mesh current (KVL based)

node voltage technique

- ① Assign voltages to every node
One of these is a reference node
→ ground reference, zero volts
- ② write KCL equations for every node
- ③ write all currents in terms of
node voltages
- ④ substitute currents into node KCL
equations, put into standard form
and solve

Example 3-1 . Wheatstone bridge

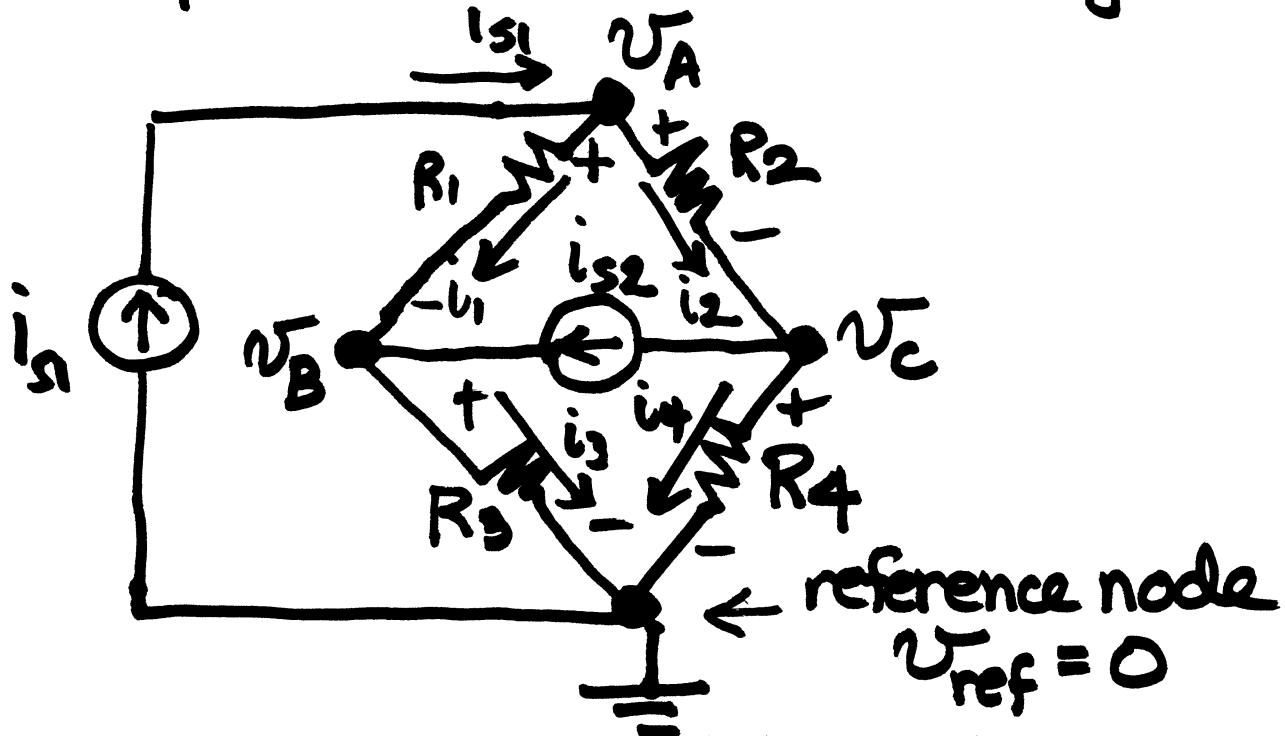

Designed to measure very small changes in R or i .

- Strain gages
- variety of sensors

- ① label voltages at node
- ② write KCL equations at each node.

$$\text{KCL } \sum i = 0 @ A \quad +i_{S1} - i_1 - i_2 = 0$$

$$\text{KCL } \sum i = 0 @ B \quad +i_1 + i_{S2} - i_3 = 0$$

$$\text{KCL } \sum i = 0 @ C \quad +i_2 - i_{S2} - i_4 = 0$$

think 3 equations in 3 unknowns.

③ write currents in terms of node voltages

$$i_1 = \frac{V_A - V_B}{R_1}$$

$$i_2 = \frac{V_A - V_C}{R_2}$$

$$i_3 = \frac{V_B - 0}{R_3}$$

$$i_4 = \frac{V_C - 0}{R_4}$$

$$i_{S1} - i_1 - i_2 = 0$$

i_{S1}

$$i_{S1} - \frac{V_A - V_B}{R_1} - \frac{V_A - V_C}{R_2} = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_A - \frac{1}{R_1} V_B - \frac{1}{R_2} V_C = i_{S1} \quad ①$$

use conductance $G = \frac{1}{R}$

$$(G_1 + G_2) V_A - G_1 V_B - G_2 V_C = i_{S1}$$

$$+ i_1 + i_{S2} - i_3 = 0$$

$$\frac{V_A - V_B}{R_1} + i_{S2} - \frac{V_B}{R_3} = 0$$

$$\frac{1}{R_1} V_A - \left(\frac{1}{R_1} + \frac{1}{R_3}\right) V_B = -i_{S2} \quad ②$$

$$G_1 V_A - (G_1 + G_3) V_B = -i_{S2}$$

$$i_2 - i_{S2} - i_4 = 0$$

$$\frac{V_A - V_C}{R_2} - i_{S2} - \frac{V_C}{R_4} = 0$$

$$\frac{1}{R_2} V_A - \left(\frac{1}{R_2} + \frac{1}{R_4}\right) V_C = +i_{S2} \quad ③$$

$$G_2 V_A - (G_2 + G_4) V_C = +i_{S2}$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_A - \frac{1}{R_1}V_B - \frac{1}{R_2}V_C = i_{S1}$$


$$\frac{1}{R_1}V_A - \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_B = -i_{S2}$$

$$\frac{1}{R_2}V_A - \left(\frac{1}{R_2} + \frac{1}{R_4}\right)V_C = +i_{S2}$$


$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_1} & -\frac{1}{R_2} \\ \frac{1}{R_1} & -\left(\frac{1}{R_1} + \frac{1}{R_3}\right) & 0 \\ 0 & 0 & -\left(\frac{1}{R_2} + \frac{1}{R_4}\right) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_{S1} \\ -i_{S2} \\ +i_{S2} \end{bmatrix}$$

Problems voltage sources are bad!



I.

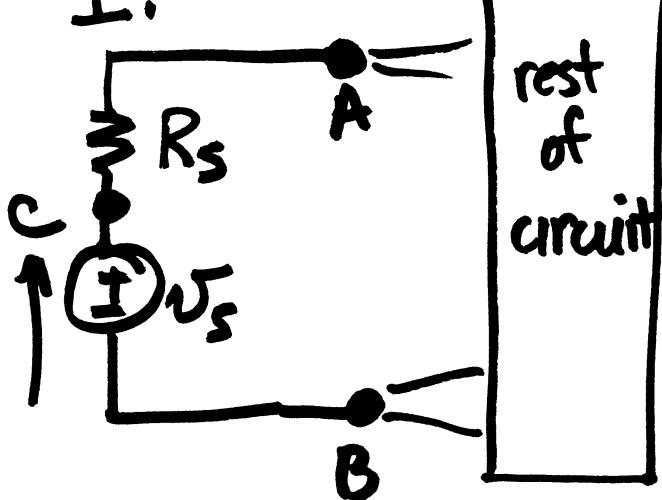

$$i_s = \frac{v_s}{R_s}$$

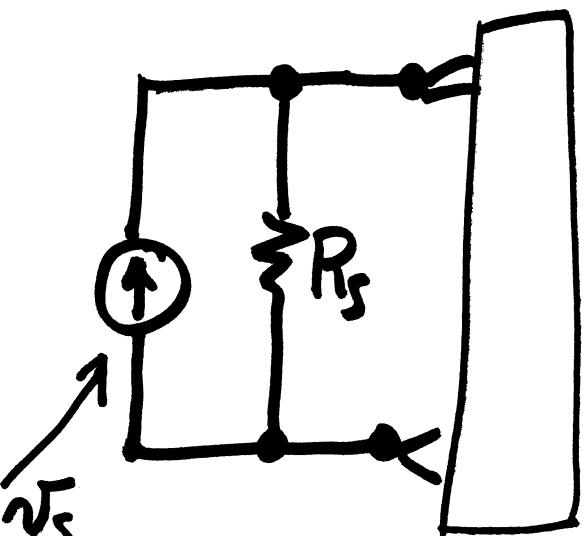


II.

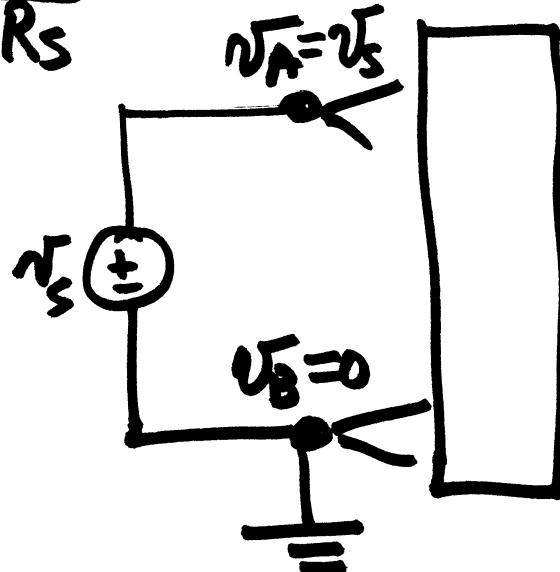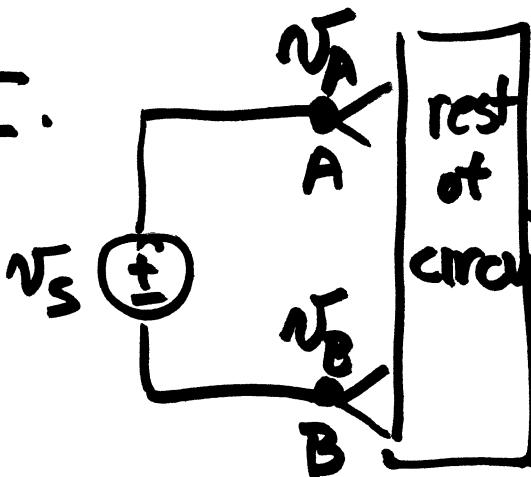

$$v_A - v_B = v_s$$

III.

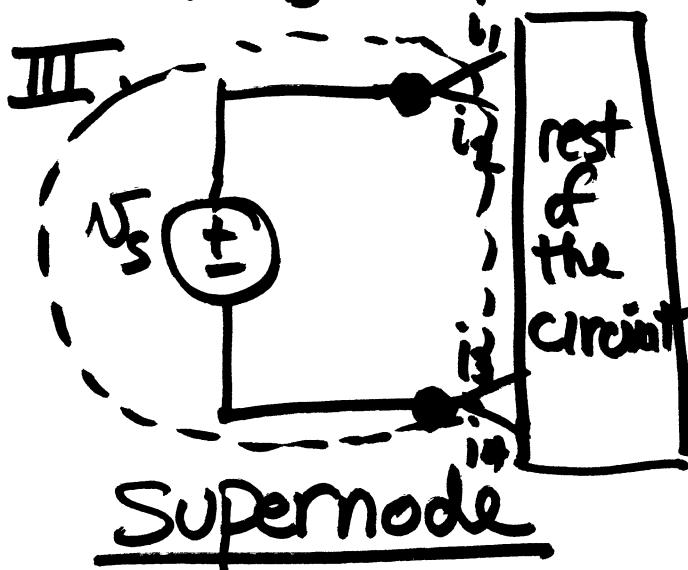

Supernode

$$\text{KCL: } -i_1 - i_2 + i_3 + i_4 = 0$$