

Linearity

input
output

input
 x



output
 y

linear $\rightarrow y = kx$


↑
gain

superposition $\rightarrow y_1 = kx_1$,
 $y_2 = kx_2$

$$(y_1 + y_2) = k(x_1 + x_2)$$

find the contribution to the output
due to each source
and add up the individual outputs
to get the total output

Example

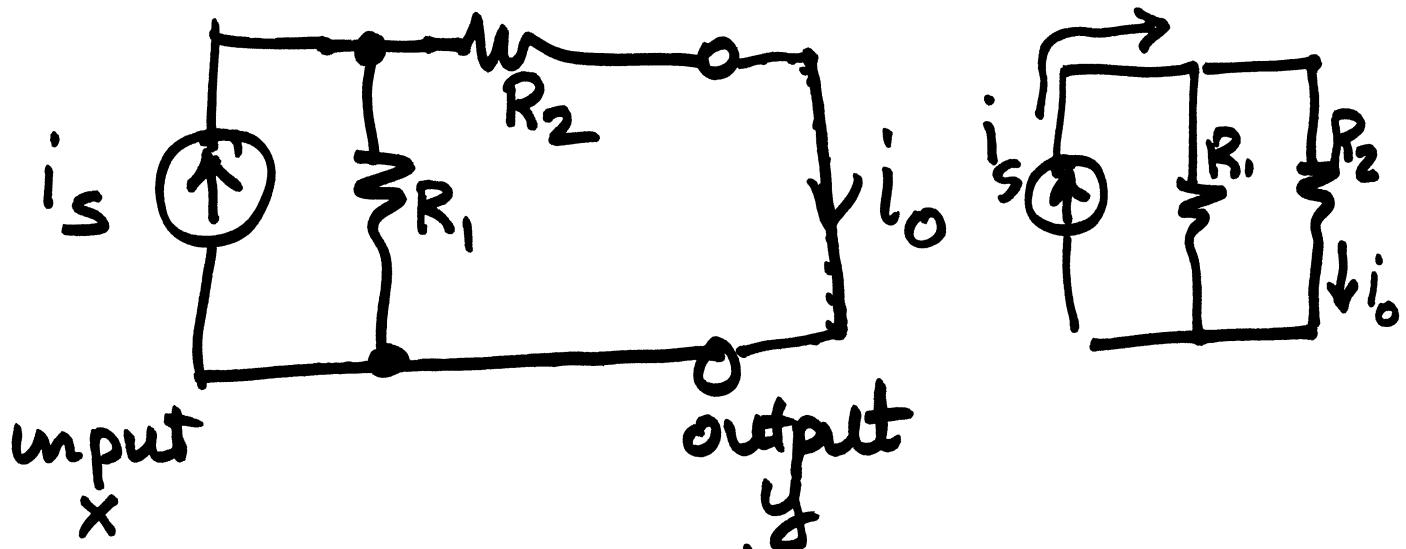


i_s — electrically — i_o

analyze using a current divider $i_o = \frac{R_1}{R_1 + R_2} i_s$

constant of proportionality

amplifier gain > 1
attenuator gain < 1


Example

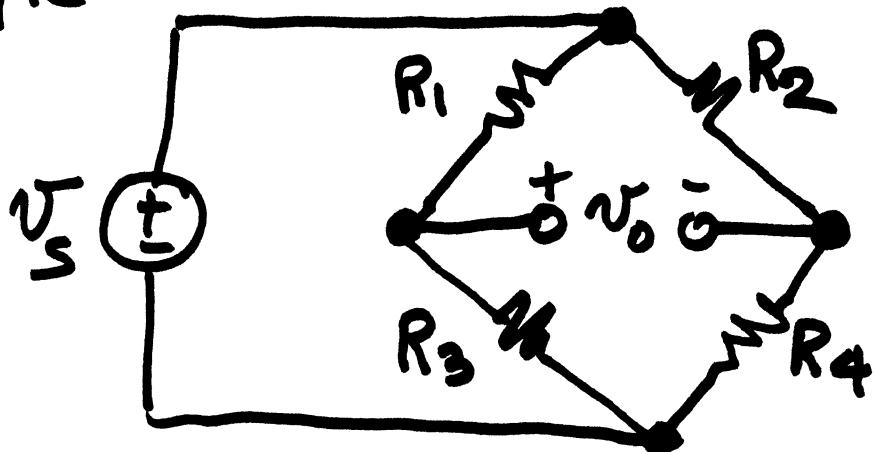

strain gage circuit

U_o - output

U_s - input

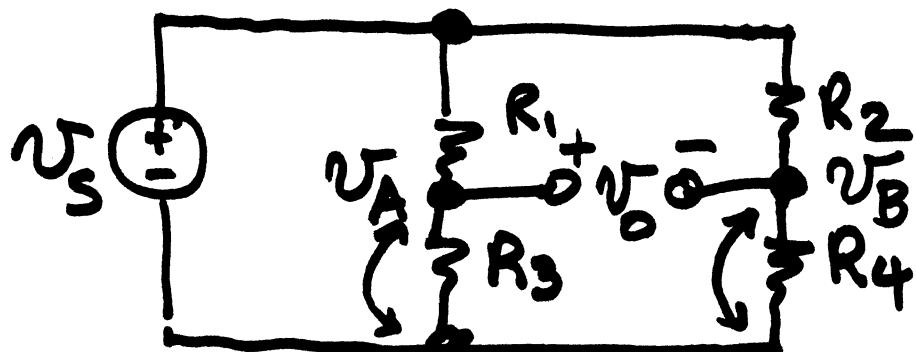


by voltage divider $V_A = \frac{R_3}{R_1 + R_3} U_s$

$$V_B = \frac{R_4}{R_2 + R_4} U_s$$

$$V_o = V_A - V_B = \frac{R_3}{R_1 + R_3} U_s - \frac{R_4}{R_2 + R_4} U_s$$

output $\underbrace{\left(\frac{R_3}{R_1 + R_3} - \frac{R_4}{R_2 + R_4} \right)}_{\text{gain}}$ $\underbrace{U_s}_{\text{input}}$
constant of proportionality

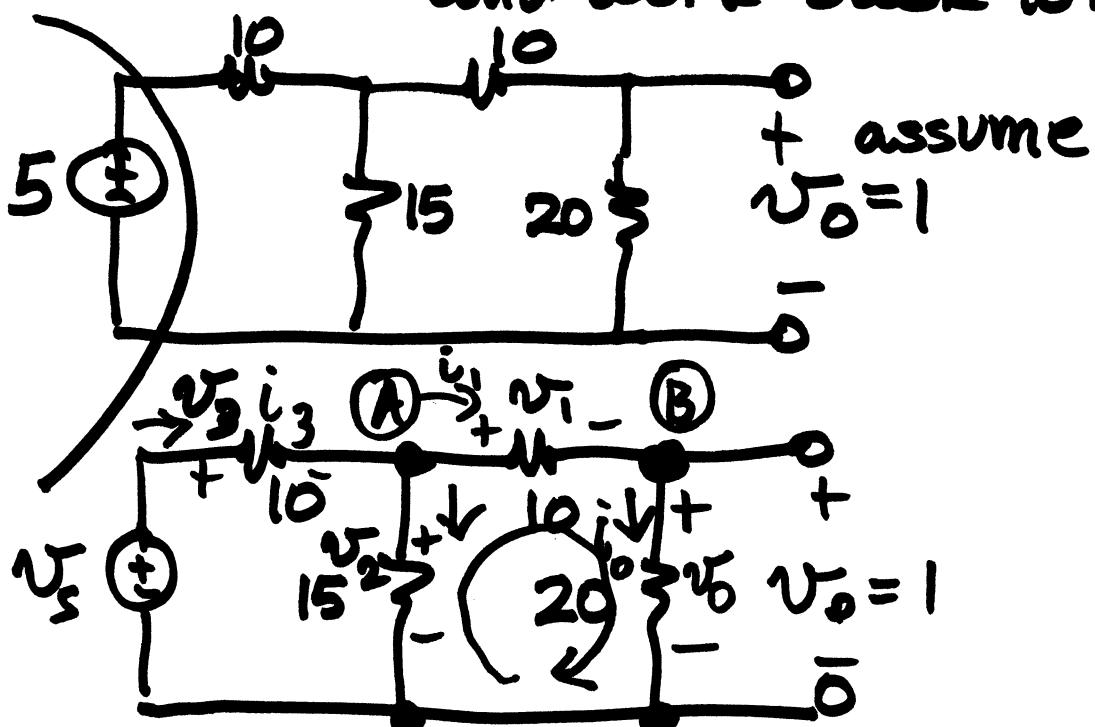Start at output let output = 1
and work back to input



$$i_0 = \frac{25}{20} = \frac{1}{20} = .05$$

$$\text{KCL @ B} \quad \sum_{i=0}^1 +i_1 - i_0 = 0$$

$i_1 = i_0 = .05 \text{ Amps.}$

$$V_1 = i_1 R_1 = (.05)(10) = 0.5 \text{ volts}$$

KVLQ

$$-\mathcal{V}_2 + \mathcal{V}_1 + \mathcal{V}_0 = 0$$

$$-25_2 + 0.5 + 1 = 0$$

$V_2 = 1.5$ volts

$$i_2 = \frac{V_2}{R_2} = \frac{1.5 \text{ Volts}}{15} = 0.1 \text{ A.}$$

KCL @ A $\sum_{\text{in}} i = 0 + i_3 - i_2 - i_1 = 0$
 $i_3 - 0.1 - 0.05 = 0$

$$i_3 = +0.15 \text{ Amps.}$$

$$V_3 = i_3 R_3 = (0.15)(10) = 1.5$$

loop $-V_S + V_3 + V_2 = 0$

$$-V_S + 1.5 + 1.5 = 0$$

$$V_S = 3$$

input
 $V_S = 3$


output
 $V_O = 1$

$$k = \frac{\text{output}}{\text{input}} = \frac{1}{3}$$

If the input is 5 Volts, then the output

$$V_O = k V_S = \frac{1}{3} \cdot 5 = \frac{5}{3} \text{ Volts.}$$

Superposition

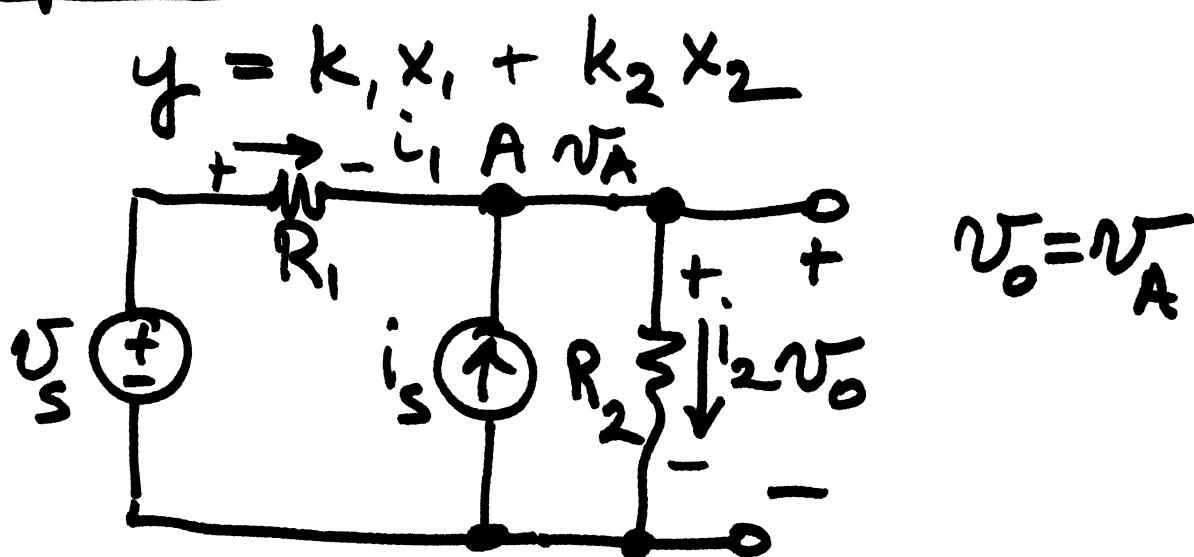

$$U_o = k_1 U_s + k_2 i_s$$

KCL @ node A $\sum_{\text{in}} i @ A = 0 \quad i_1 + i_s - i_2 = 0$

$$\left(\frac{U_s - U_A}{R_1} \right) + i_s - \left(\frac{U_A - 0}{R_2} \right) = 0$$

$$\frac{U_s}{R_1} - \frac{U_A}{R_1} + i_s - \frac{U_A}{R_2} = 0$$

$$\frac{-U_s}{R_1} + i_s = U_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = U_o \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= U_o \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$U_o = \frac{R_1 R_2}{R_1 + R_2} \frac{1}{R_1} U_s + \frac{R_1 R_2}{R_1 + R_2} i_s$$

output = k_1 input₁ + k_2 input₂




Superposition

→ turn off all sources but one and find the contribution from that source



repeat for all sources

turn off a source


voltage source

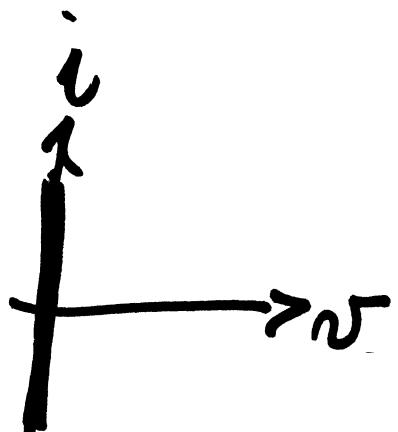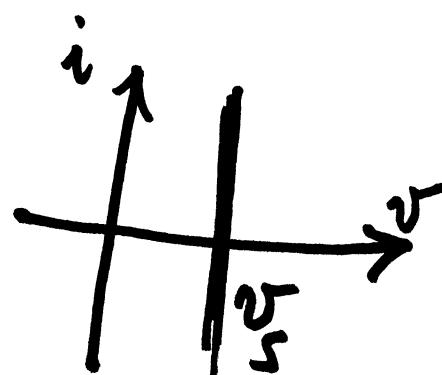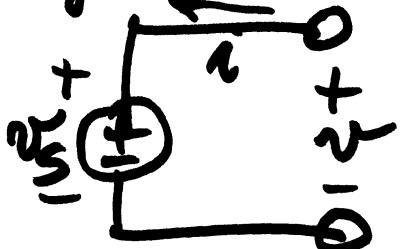

current source

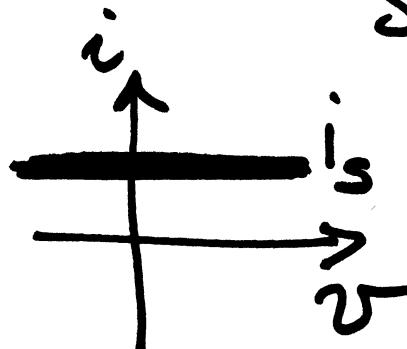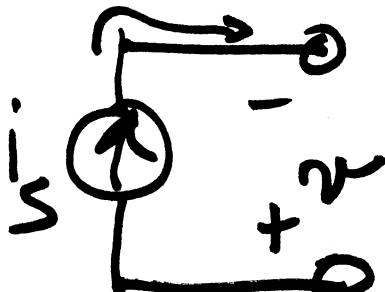

short

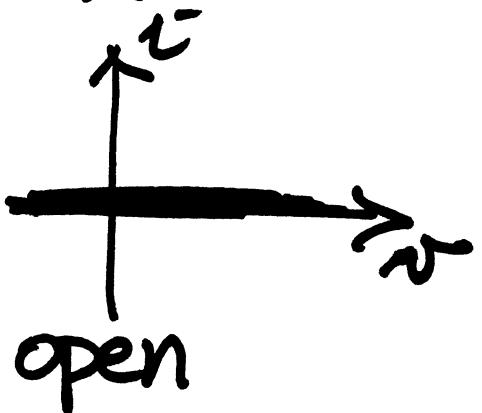

open