

Announcements

(Glennan 519)

- ① bjh7 Ben Hothem
mxc106 matt Cross
brian.inderhees
flm Glennan 518

② Passwords

User: engr210
password: kirchoff

③ problem 5, current hw


(a) 9.876543 mA

④ new hw policy


hw due at beginning of class

NO ~~LATE~~ HW ACCEPTED.

Thevenin Equivalent Circuit

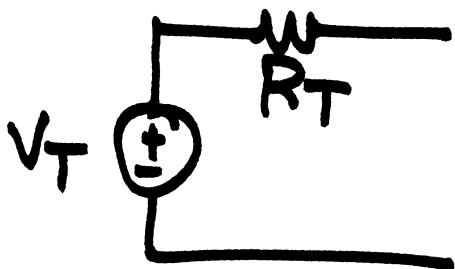


Norton Equivalent Circuit

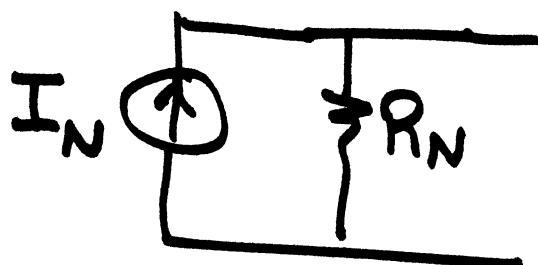


How to find equivalent circuits



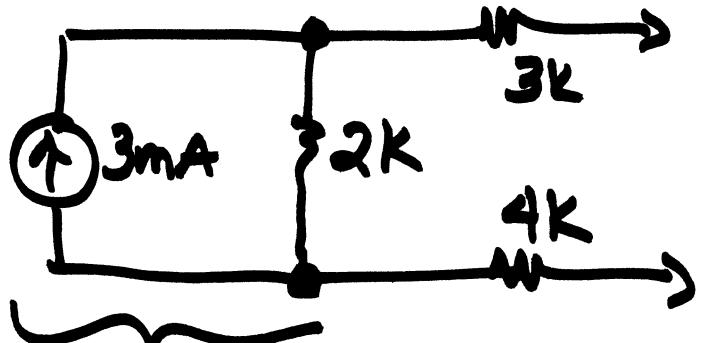
- ① transformation
- ② mathematically equivalent circuits
- ③ Thevenin's Theorem
- ④ open circuit voltage / short circuit current





source transform

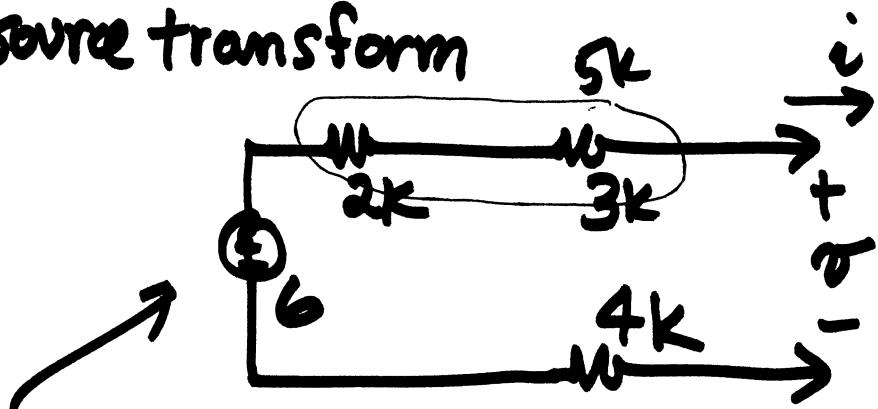

$$U = iR = \left(3 \text{mA}\right) \left(2 \text{k}\right) = 6 \text{volts}$$

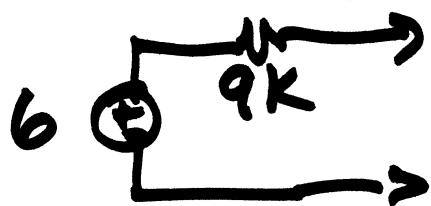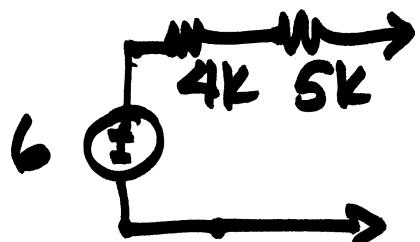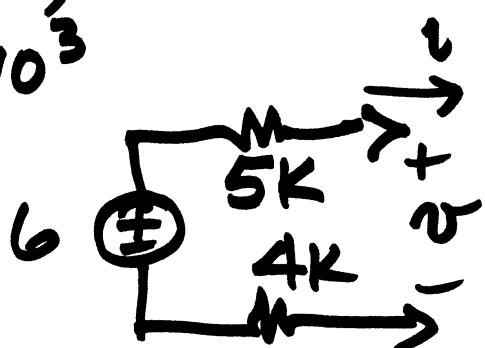

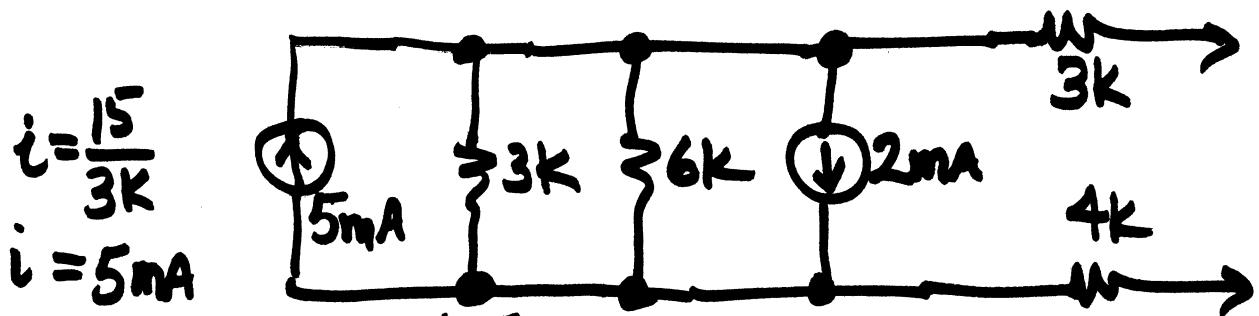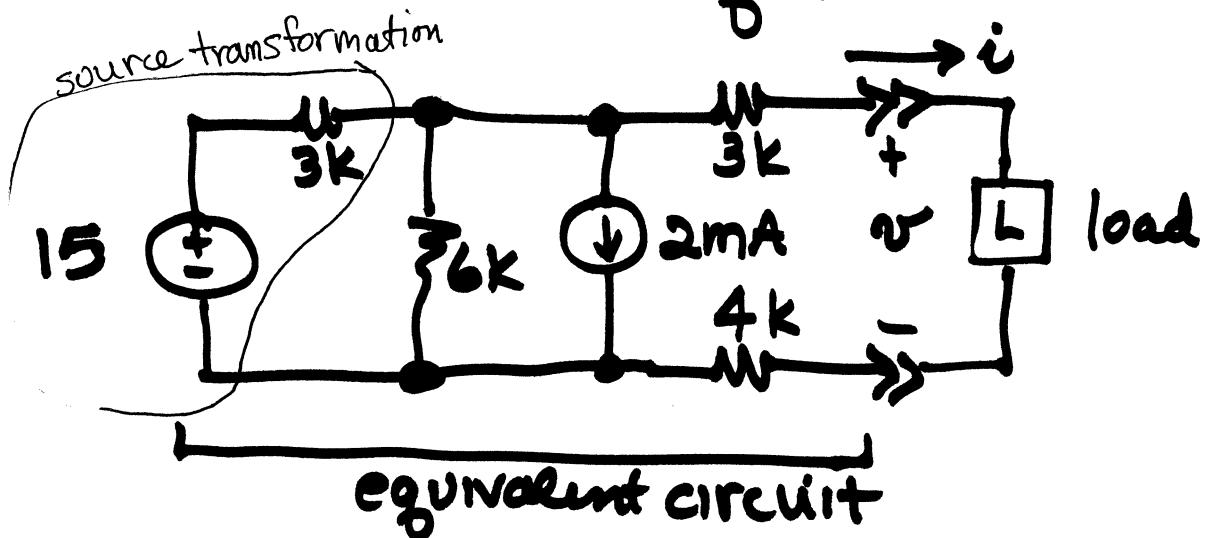
Example 3-13 (Source transformation) equivalent resistance




combine resistors

$$R_{EQ} = \frac{(3k)(6k)}{3k + 6k} = 2k$$

combine current source S

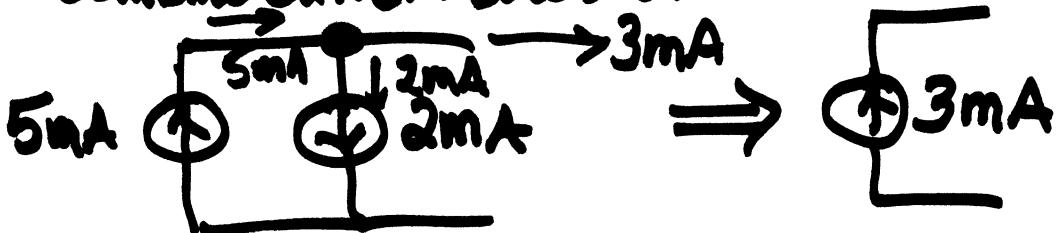

Example 3-14

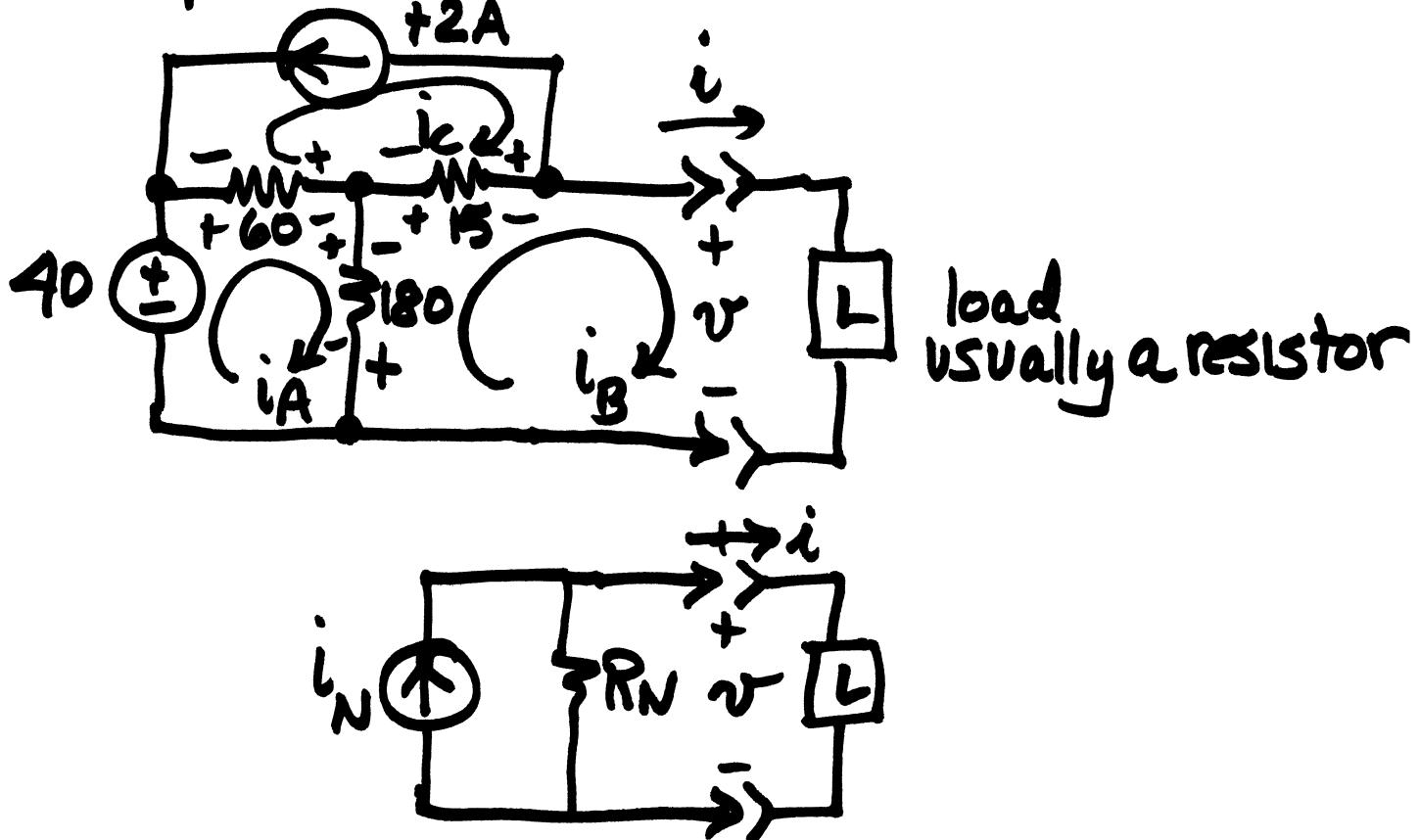

complicated (given circuit)

treat v and i at interface
basically as known

by inspection: $i_C = -2 \text{ amps}$


$$A: \text{ } -40 + 60i_A - 60i_C + 180i_A - 180i_B = 0$$

$$B: \text{ } +180i_B - 180i_A + 15i_B - 15i_C + v = 0$$

$$i_B = i$$

$$i = -1.5 - \frac{v}{60}$$

solving equations

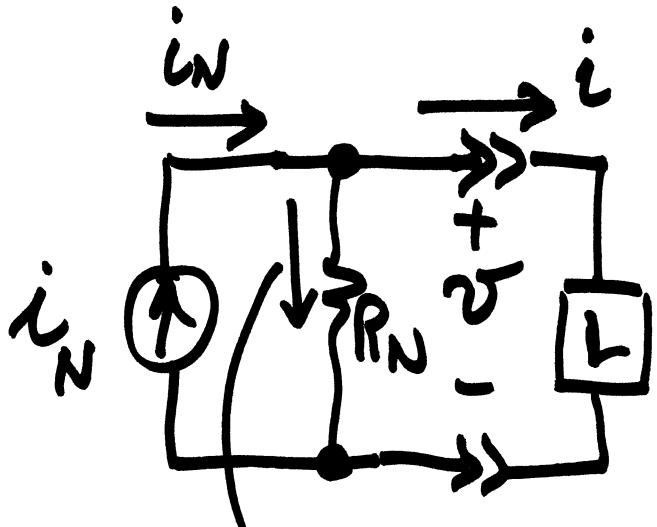

KCL: $i_{R_N} = \frac{v}{R_N}$

$$+i_N - \frac{v}{R_N} - i = 0$$


$$i = i_N - \frac{v}{R_N}$$

$$i = -1.5 - \frac{v}{60}$$


$$i_N = -1.5$$

$$R_N = 60$$

④

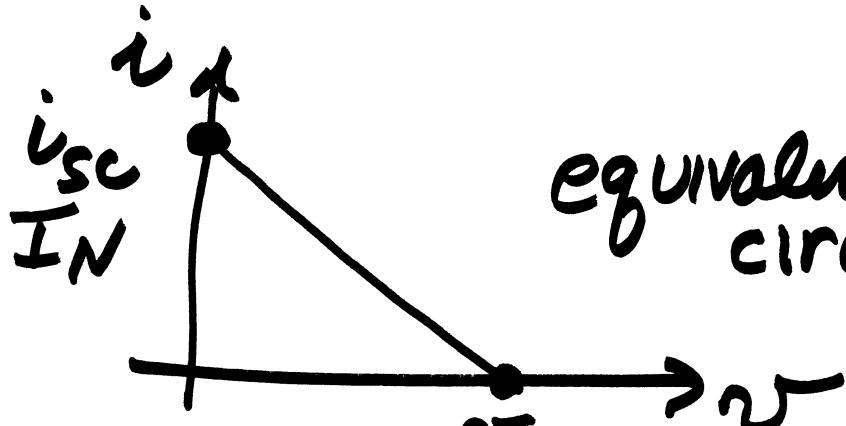

equivalent circuit

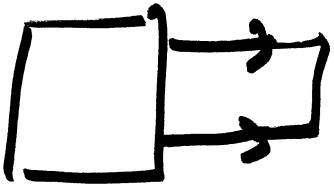


v_{oc}

E_U

open circuit voltage
 $i = 0$

Thevenin

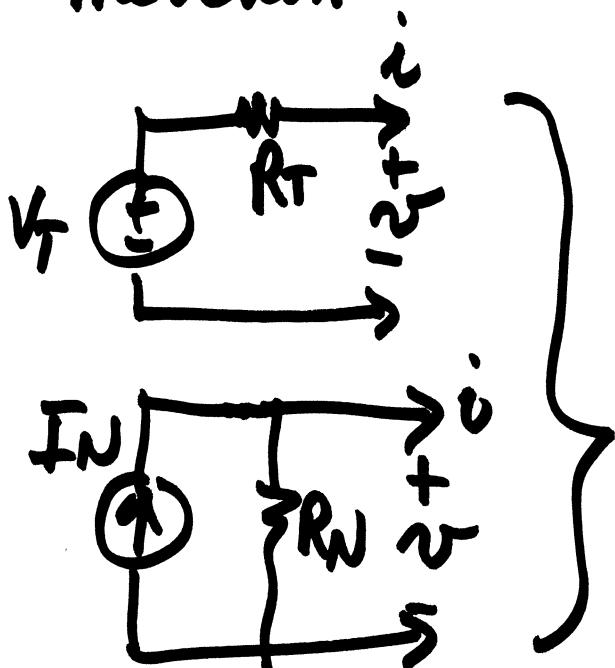


short circuit current
 $v=0$

$$R_T = R_N$$

$$V_T = I_N R_N$$

source transform

Thevenin's Theorem

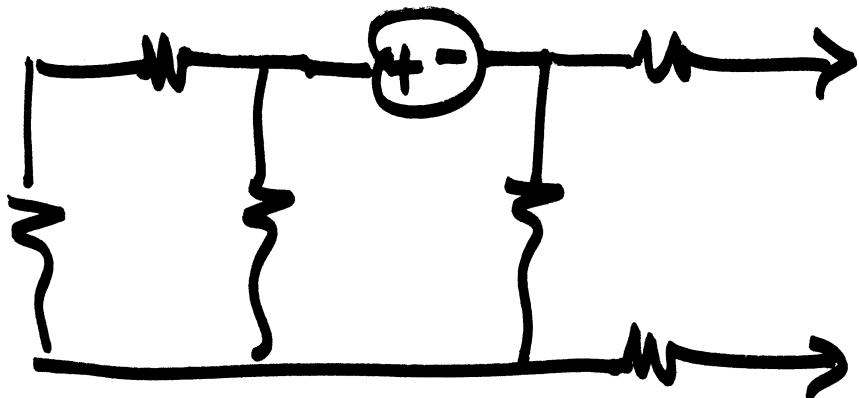

- ① measure
(calculate) $V_{OC} = V_T$

- ② turn all sources off
determine R_{EQ}

