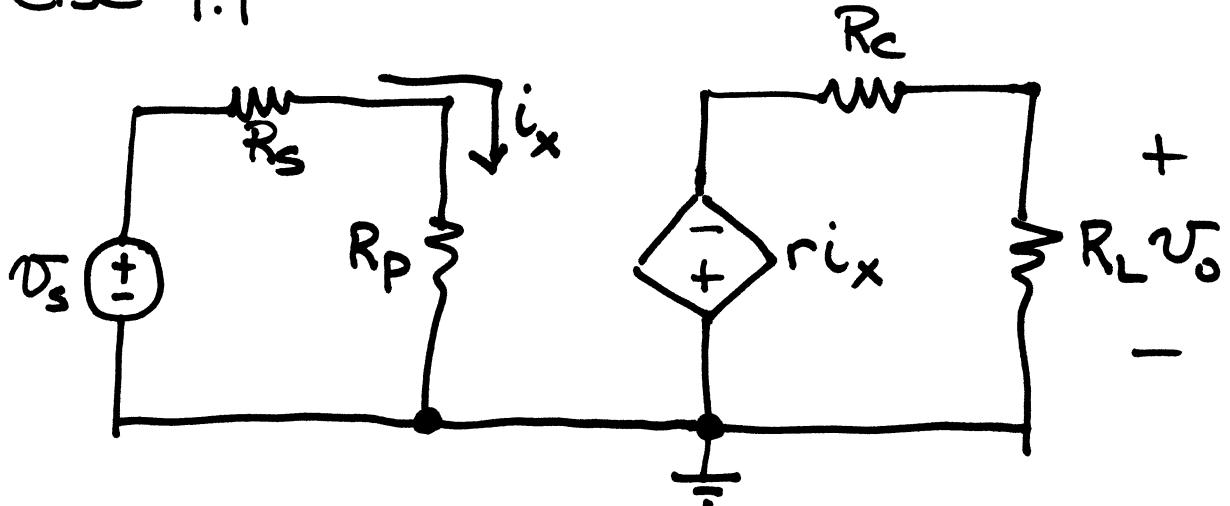


# Exercise 4.1



input circuit

$$i_x = \frac{V_s}{R_s + R_p}$$

constraint

output circuit do by voltage divider

$$V_o = \frac{R_L}{R_c + R_L} (-r i_x) = \frac{-r R_L}{R_c + R_L} \frac{V_s}{R_s + R_p}$$


$$V_o = -\frac{r R_L}{(R_c + R_L)(R_s + R_p)} V_s$$

OUTPUT

GAIN

INPUT

## Exercise 4-2

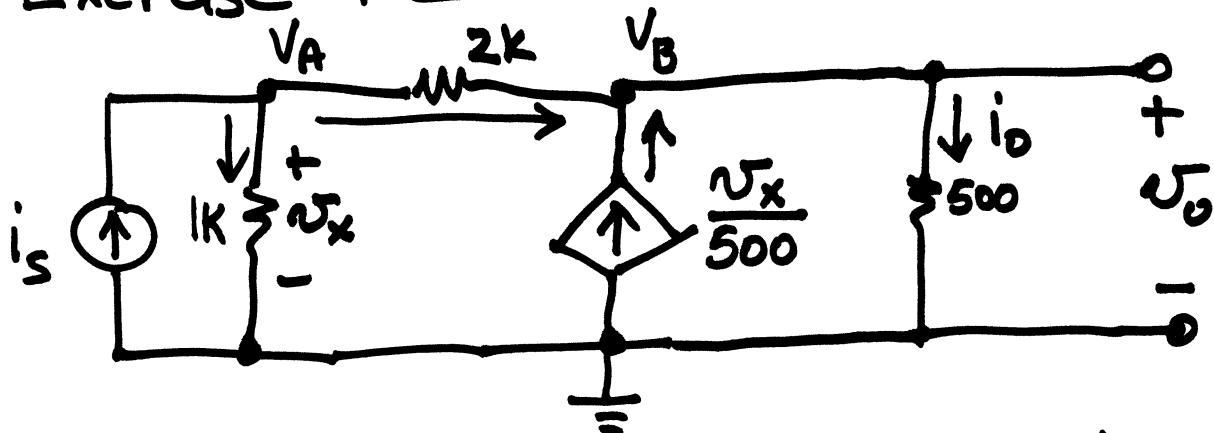

$$\text{KCL @ A} \quad \sum_{\text{in}} i = 0 \quad +i_s - \frac{v_A - 0}{1K} - \frac{v_A - v_B}{2K} = 0$$

$$\text{KCL @ B} \quad \sum_{\text{in}} i = 0 \quad +\frac{v_A - v_B}{2K} + \frac{v_x - v_A}{500} - \frac{v_B}{500} = 0$$

---

constraint  $v_x = v_A$

---

$$\left( \frac{1}{1K} + \frac{1}{2K} \right) v_A - \frac{1}{2K} v_B = i_s$$

$$\left( \frac{1}{2K} + \frac{1}{500} \right) v_A - \left( \frac{1}{2K} + \frac{1}{500} \right) v_B = 0$$

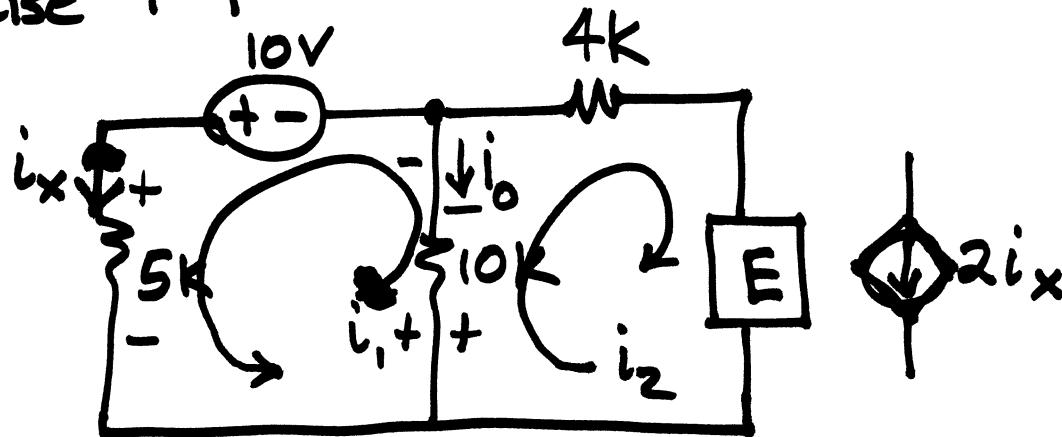

---

Find  $v_0$  &  $i_o$  in terms of  $i_s$

$$v_0 = v_B = 1000 i_s$$

$$i_o = \frac{v_B}{500} = \frac{1000 i_s}{500} = 2i_s$$

### Exercise 4-4



constraint  $i_1 = i_x$

$$i_2 = 2i_x$$


$$i_0 = -(i_1 + i_2)$$


---

$$\text{mesh 1} \quad -5000i_1 + 10 - 10000i_1 - 10000i_2 = 0$$

$\uparrow$   
 $2i_x$   
 $2(i_1)$

Exercise 4.6

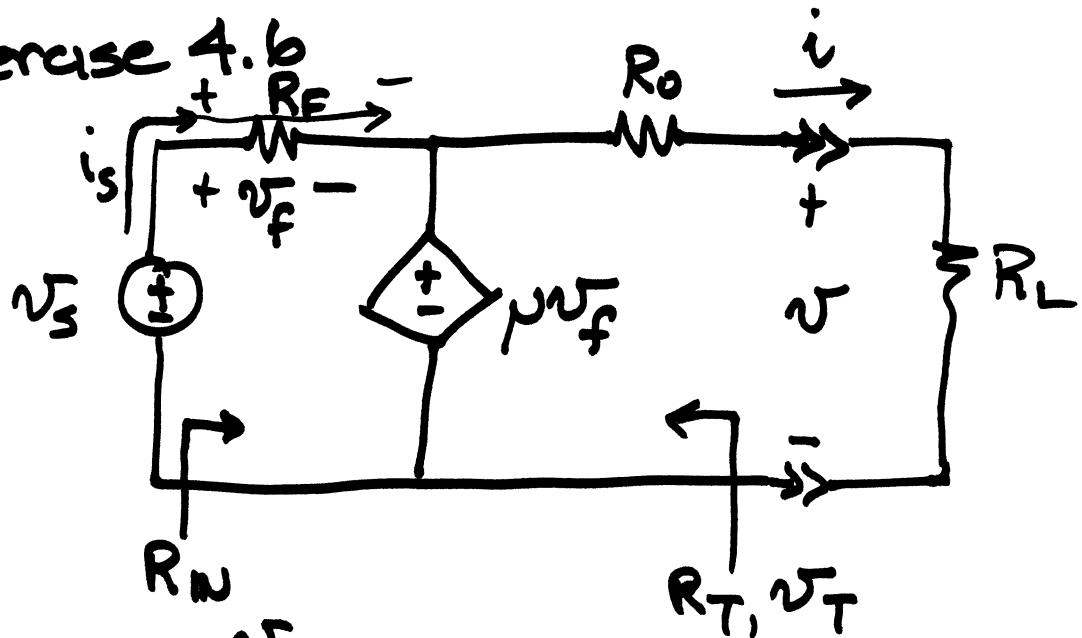

$$R_{IN} = \frac{v_s}{i_s}$$


$$i_s = \frac{v_s - \mu v_f}{R_F} = \frac{v_s - \mu(i_s R_F)}{R_F}$$

$$i_s R_F = v_s - \mu R_F i_s$$

$$i_s (1 + \mu) R_F = v_s$$

$$i_s = \frac{v_s}{(1 + \mu) R_F}$$
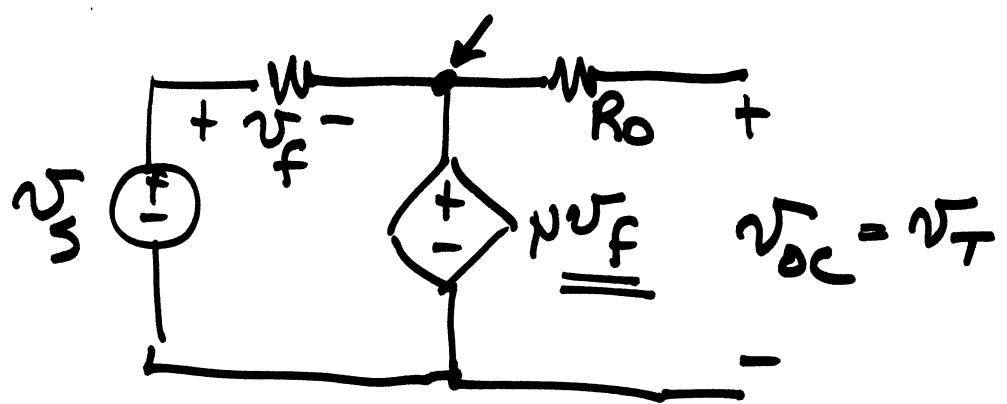
$$R_{IN} = \frac{v_s}{i_s} = \frac{v_s}{\frac{v_s}{(1 + \mu) R_F}} = (1 + \mu) R_F$$





$$\text{do KVL at input} \quad -V_s + V_f + N V_f = 0$$

$$-V_s + (1+N) V_f = 0$$

$$V_f = \frac{V_s}{1+N}$$


$$V_{oc} = N V_f = \frac{N}{1+N} V_s$$

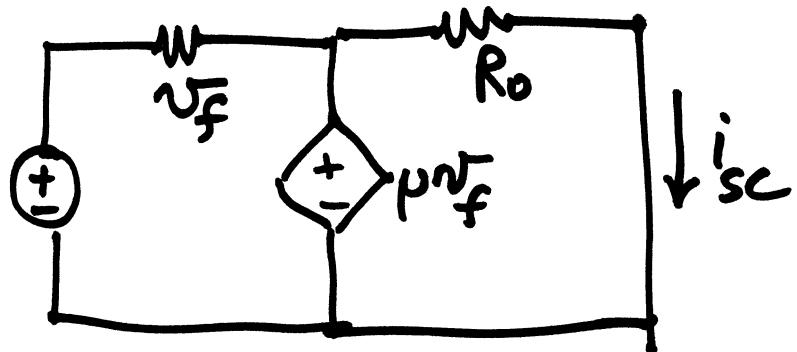

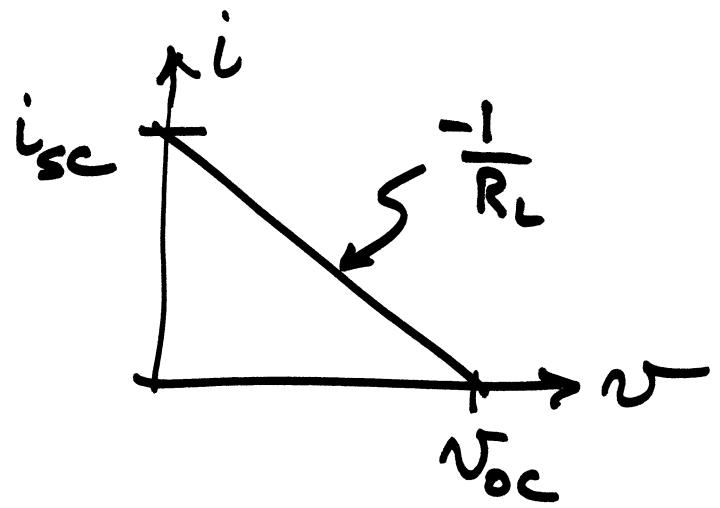
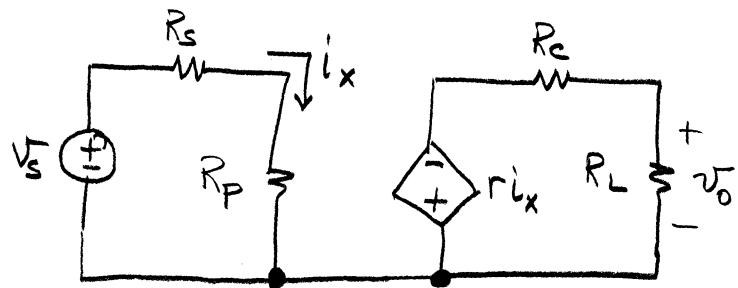
### Exercise 4.1

Find the output  $v_o$  in terms of the input  $v_s$  in the circuit below.



$$\text{For the input circuit} \quad i_x = \frac{v_s}{R_s + R_p}$$


For the output circuit use a voltage divider

$$v_o = \frac{R_L}{R_L + R_C} (-r i_x) = \left[ \frac{-r R_L}{(R_L + R_C)(R_s + R_p)} \right] v_s$$

### Exercise 4-2

(a) Formulate node-voltage equations for the circuit below.

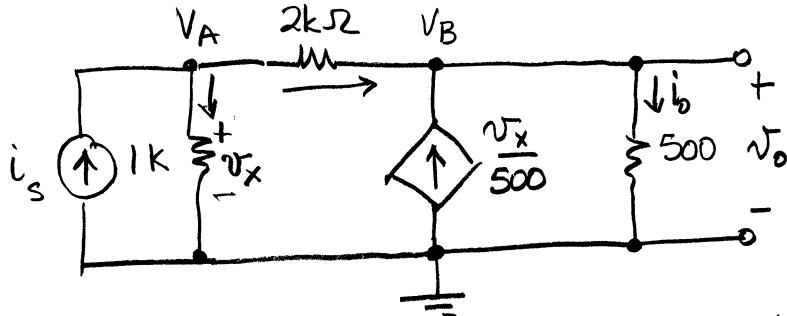(b) Solve the node-voltage equations for  $v_o$  and  $i_o$  in terms of  $i_s$ .



$$\text{KCL at } A: \sum_i = 0 \quad +i_s - \frac{V_A - 0}{1k} - \frac{V_A - V_B}{2k} = 0$$

$$\text{KCL at } B: \sum_i = 0 \quad +\frac{V_A - V_B}{2k} + \frac{v_x}{500} - \frac{V_B}{500} = 0$$

The constraint is  $v_x = V_A$ .

Substitute and solve

$$2000 \left( \frac{1}{1k} + \frac{1}{2k} \right) V_A - \frac{1}{2k} V_B = i_s$$

$$2000 \left( \frac{1}{2k} + \frac{1}{500} \right) V_A - \left( \frac{1}{2k} - \frac{1}{500} \right) V_B = 0$$

---


$$(2+1)V_A - V_B = 2000i_s$$

---


$$(1+4)V_A - (1-4)V_B = 0$$

---


$$3V_A - V_B = 2000i_s$$

---


$$5V_A - 5V_B = 0 \Rightarrow V_A = V_B$$

---


$$3V_B - V_B = 2000i_s$$

$$2V_B = 2000i_s$$

$$V_B = 1000i_s$$



By inspection

$$v_o = V_B = 1000i_s$$

$$i_o = \frac{V_B}{500} = \frac{1000i_s}{500} = 2i_s$$
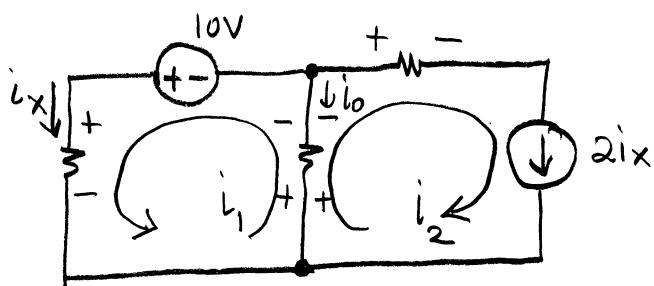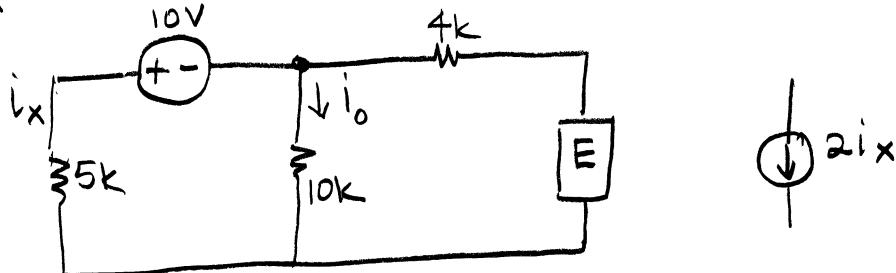
### Exercise 4-4

Use mesh analysis to find the current  $i_o$  in the circuit below when the element E is a dependent current source  $2i_x$  with the reference arrow directed down.



by inspection the constraints are

$$i_1 = i_x$$

$$i_o = -(i_1 + i_2)$$

$$-5000i_1 + 10 - 10000i_1 - 10000i_2 = 0$$

$$i_2 = 2i_x = 2i_1$$

$$-5000i_1 + 10 - 10000i_1 - 10000(2i_1) = 0$$

$$-5000i_1 + 10 - 10000i_1 - 20000i_1 = 0$$

$$35000i_1 = 10$$


$$i_1 = \frac{10}{35000} = 2.857 \times 10^{-4} \text{ A}$$

$$i_2 = 2i_1 = 2(2.857 \times 10^{-4}) = 5.714 \times 10^{-4} \text{ A}$$

$$i_o = -(i_1 + i_2) = -8.571 \times 10^{-4} \text{ mA}$$
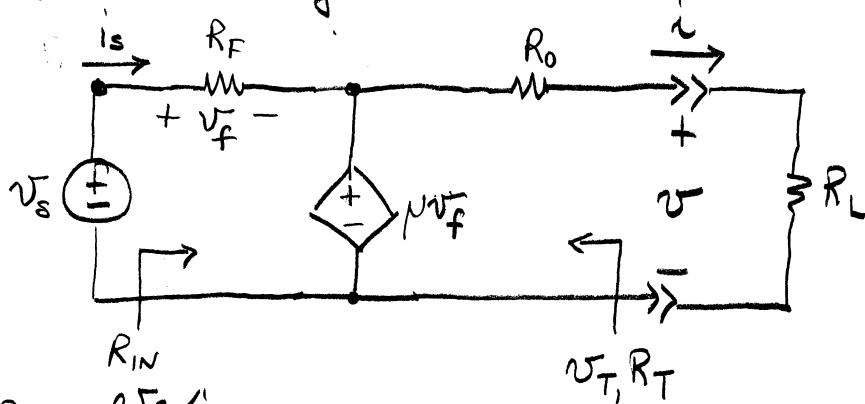
### Exercise 4.6

Find the input resistance and output Thvenin equivalent circuit of the circuit given below.



$$\text{Find } R_{IN} = \frac{V_s}{i_s}$$

$$i_s = \frac{V_s - \mu V_f}{R_F} \quad V_f = i_s R_F$$


$$i_s = \frac{V_s - \mu i_s R_F}{R_F}$$

$$i_s R_F = V_s - \mu i_s R_F$$

$$i_s (R_F + \mu R_F) = V_s \Rightarrow i_s = \frac{V_s}{R_F(1+\mu)}$$

$$R_{IN} = \frac{V_s}{i_s} = \frac{V_s}{\frac{V_s}{R_F(1+\mu)}} = R_F(1+\mu)$$

$$\text{Find } V_{OC}$$

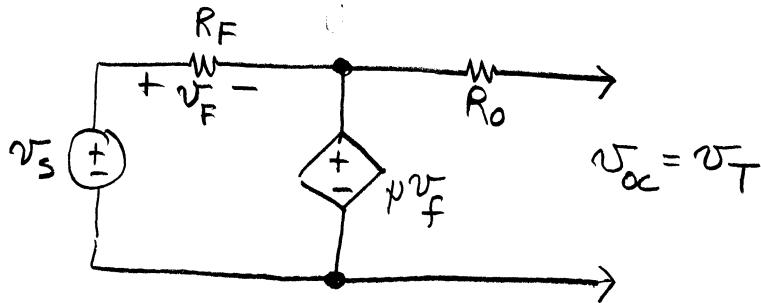


$$-V_s + V_F + \mu V_F = 0$$

$$-V_s + (1+\mu)V_F = 0$$

$$(1+\mu)V_F = V_s$$

$$V_F = \frac{V_s}{1+\mu} \Rightarrow V_T = \mu V_F = \frac{\mu}{1+\mu} V_s$$

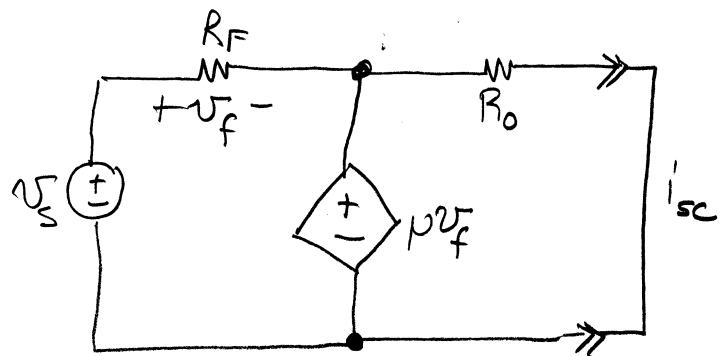To find  $R_T$  we must calculate  $i_{sc}$  as well.




$$-v_s + v_f + \mu v_f = 0$$

$$v_f = \frac{v_s}{1+\mu}$$

$$i_{sc} = \frac{\mu v_f}{R_o} = \frac{\mu \left( \frac{v_s}{1+\mu} \right)}{R_o} = \frac{\mu}{1+\mu} \frac{v_s}{R_o}$$

For a Thevenin circuit

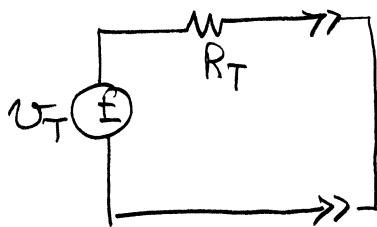


$$i_{sc} = \frac{v_T}{R_T} \text{ but } v_T = \frac{\mu}{1+\mu} v_s$$

$$\therefore i_{sc} = \frac{v_T}{R_o}$$

$$\Rightarrow R_T = R_o$$
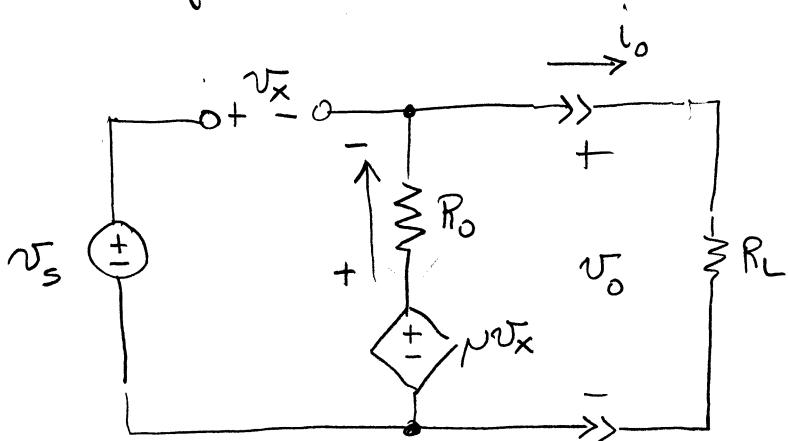
### Example 4-8

Find the Thevenin equivalent at the output interface of the circuit given below.



$$\text{Do KVL across input} \quad -v_s + v_x + v_o = 0 \Rightarrow v_x = v_s - v_o$$

$$\text{Do KCL at node } o_+ \sum_{\text{in}} i_o + \frac{\mu v_x - v_o}{R_o} - i_o = 0$$


$$\frac{\mu(v_s - v_o) - v_o}{R_o} = i_o$$

$$\mu v_s - \mu v_o - v_o = i_o R_o$$

$$\mu v_s - (\mu + 1) v_o = i_o R_o$$

$$(\mu + 1) v_o + i_o R_o = \mu v_s$$
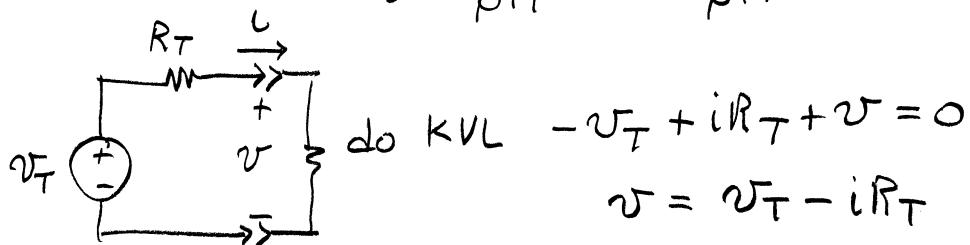
$$v_o = \frac{\mu}{\mu + 1} v_s - \frac{R_o}{\mu + 1} i_o$$



$$\Rightarrow v_T = \frac{\mu}{\mu + 1} v_s \quad R_T = \frac{R_o}{\mu + 1}$$