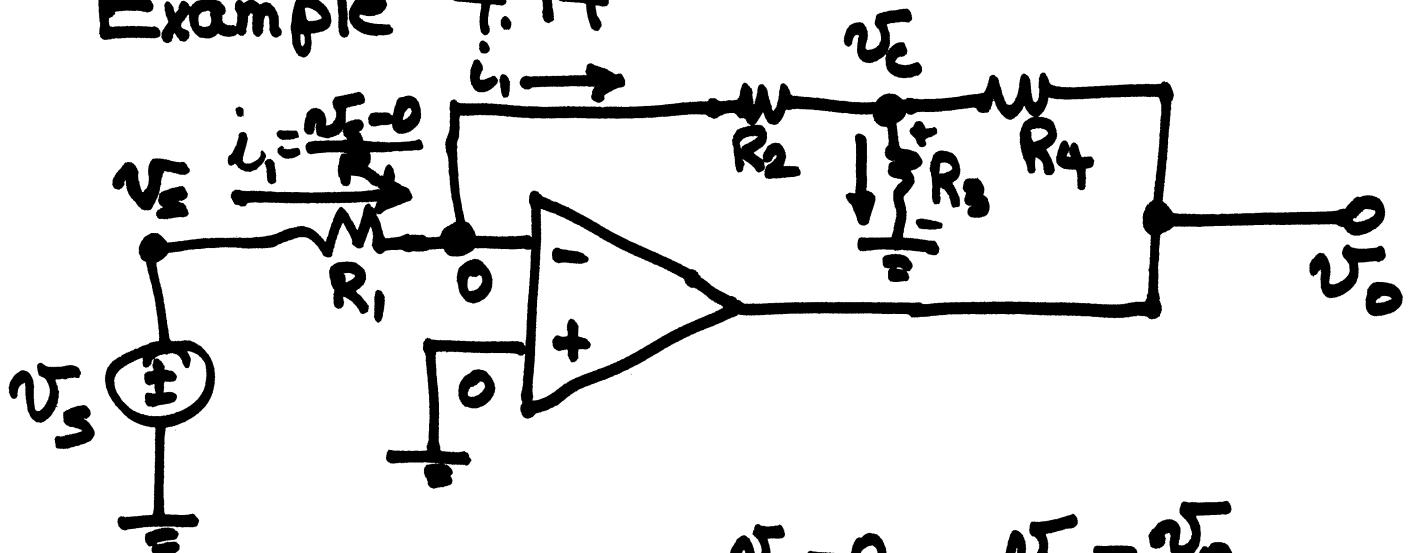


Example 4.14



$$@c \sum i = 0 \quad +i_1 - \frac{v_c - 0}{R_3} - \frac{v_c - v_o}{R_4} = 0$$

$$+in \quad \frac{v_s}{R_1} - \frac{v_c}{R_c} - \frac{v_c}{R_4} + \frac{v_o}{R_4} = 0 \quad (1)$$

$$+ \frac{v_s - 0}{R_1} - \frac{0 - v_c}{R_2} = 0 \quad (2)$$


$$\frac{v_s}{R_1} + \frac{v_c}{R_2} = 0 \quad \alpha \quad v_c = -\frac{v_s R_2}{R_1}$$

$$\frac{v_s}{R_1} - \left(\frac{1}{R_c} + \frac{1}{R_4} \right) \left(-\frac{v_s R_2}{R_1} \right) + \frac{v_o}{R_4} = 0$$

$$v_o = - \underbrace{\frac{R_c R_3 + R_2 R_4 + R_3 R_4}{R_1 R_3}}_{GAIN} v_s$$

GAIN

4.7 The Comparator

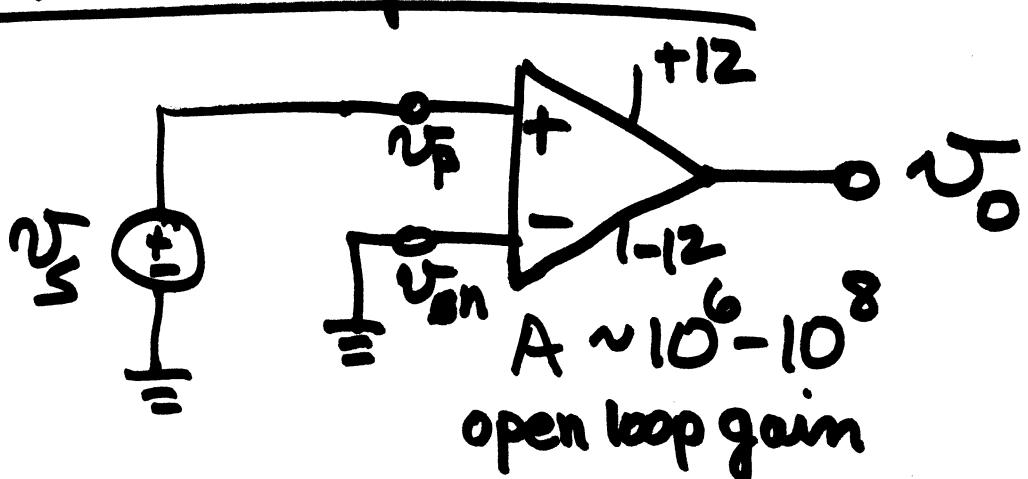



converting analog signals to digital
two values
ON/OFF

$$v_p > v_n$$


$v_o \rightarrow +$ saturation

$$v_p < v_n$$

$v_o \rightarrow -$ saturation

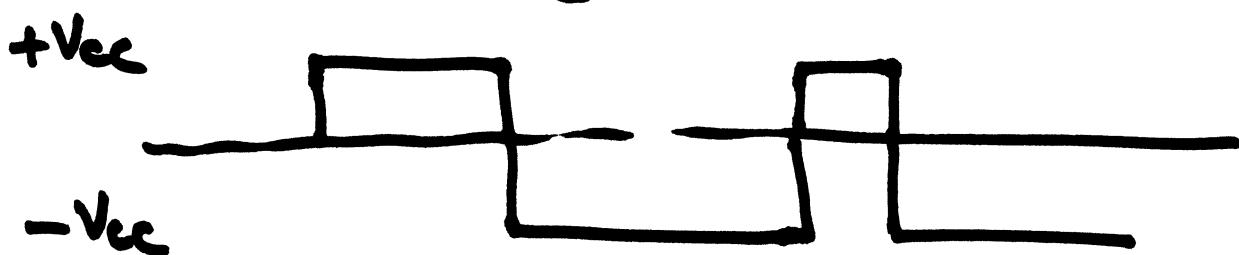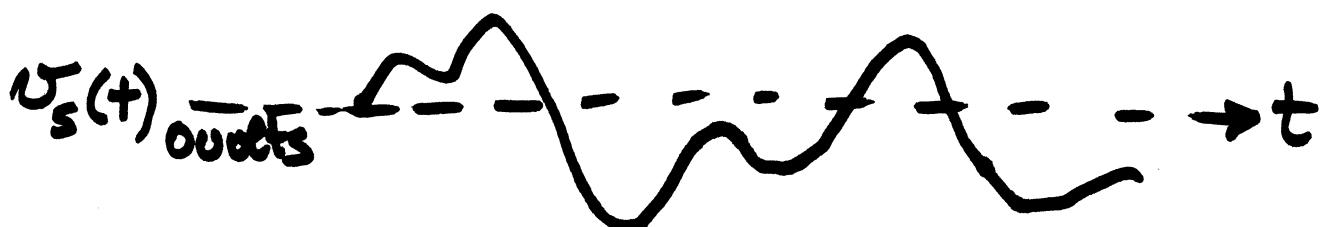

Example 4-24

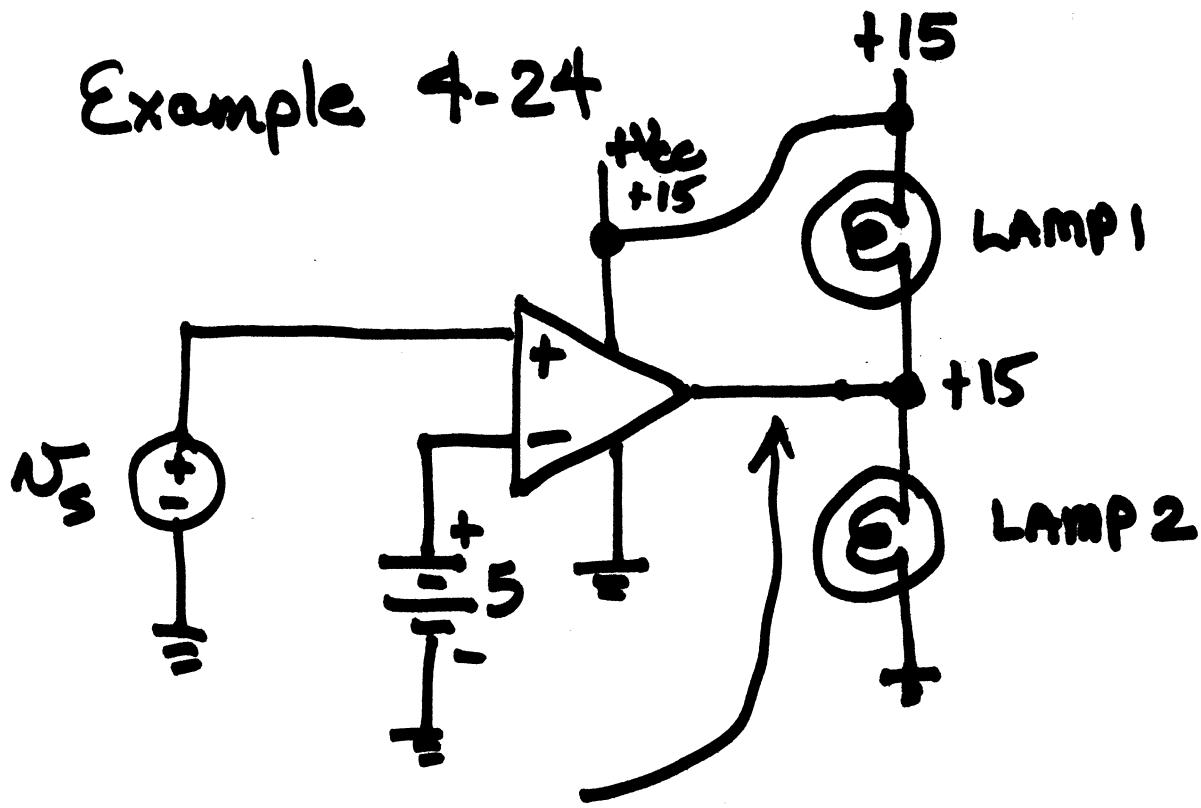

$$A(V_p - V_N) = \frac{+15}{-5} (V_p - 5)$$

If $V_s > 5 \rightarrow V_0 \rightarrow +15$ LAMP2 ON LAMP1 OFF

$V_s < 5 \rightarrow V_0 \rightarrow 0$ LAMP2 OFF LAMP1 ON