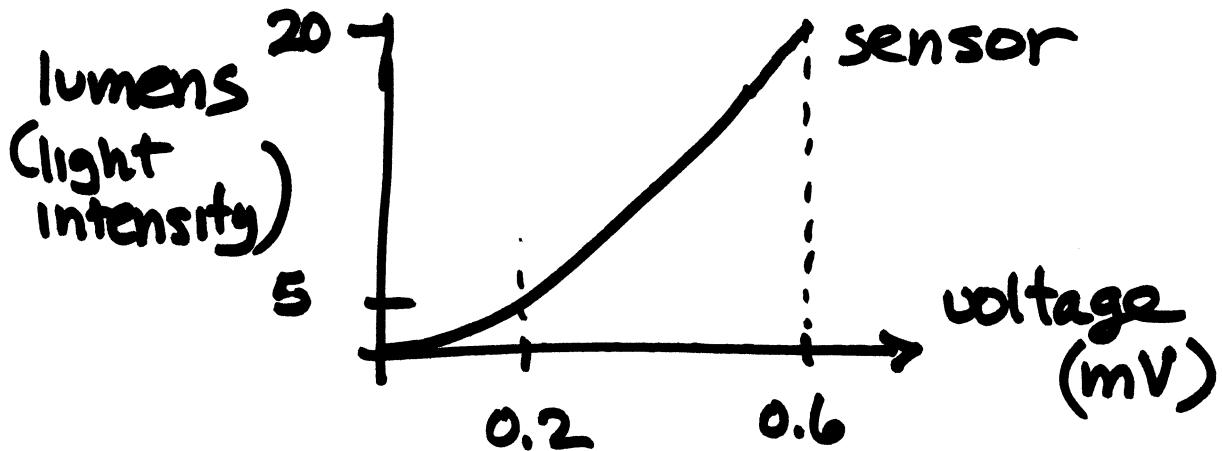


Design Problem



match the voltage range

0.2 - 0.6 mV

0-5

0.4 mV



$$K = \frac{\Delta V_{OUT}}{\Delta V_{IN}} = \frac{5 \text{ volts}}{0.4 \times 10^{-3} \text{ volts}}$$

$$K = 1250$$

0.2 - 0.6 mV

$\times 1250$

2.5 volt - 7.5 volts

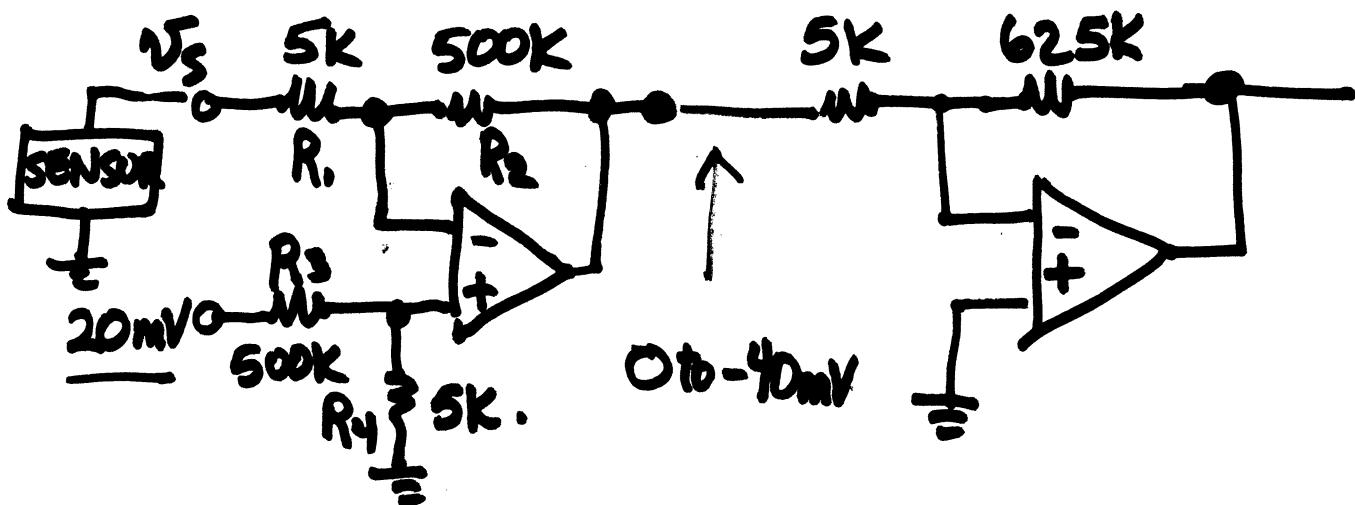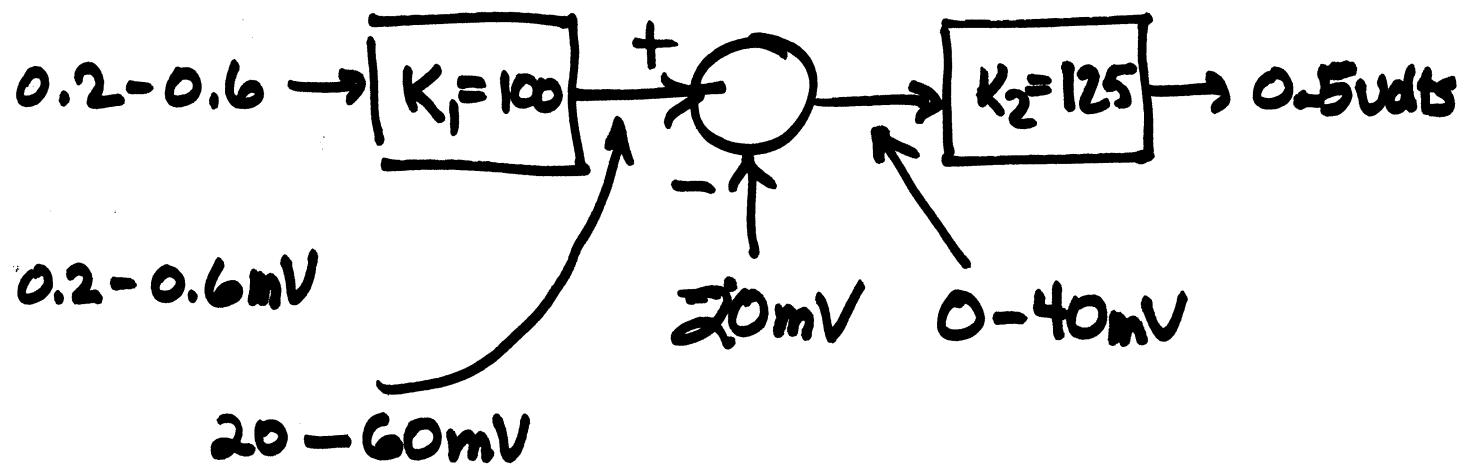


SUBTRACTOR

$$K_1 = -\frac{R_2}{R_1} = -\frac{500\text{k}}{5\text{k}} = -100$$

$$K_2 = \frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} = 1$$

INVERTING AMPLIFIER.
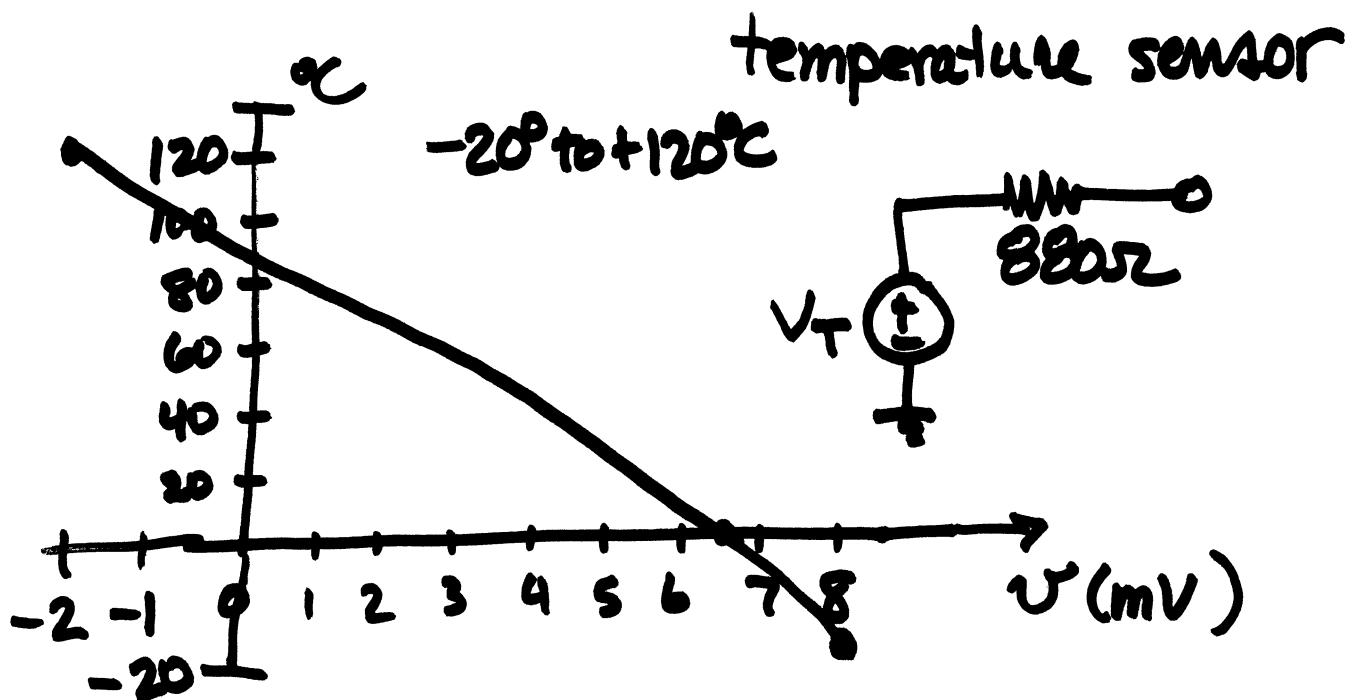
$$K = -\frac{R_2}{R_1} = -\frac{625\text{k}}{5\text{k}} = -125$$



input range $-2 \text{ to } +8 \text{ mV}$

output range $0 \text{ - } 1 \text{ volt}$

$$K_{\text{overall}} = \frac{\Delta V_{\text{out}}}{\Delta V_{\text{in}}} = \frac{1 \text{ volt}}{10 \text{ mV}} = 100$$

