

Sinusoidal waveforms:

period

linear frequency

T_0

$$f_0 = \frac{1}{T_0}$$

angular frequency $\omega_0 = 2\pi f_0$

Fourier coefficients

$$A \cos(\omega t + \phi) \rightarrow a \cos \omega t + b \sin \omega t$$

use Fourier coefficients to combine/add sinusoidal waveforms

$$v_1(t) = A_1 \cos(\underline{\omega t} + \phi_1) = a_1 \cos \omega t + b_1 \sin \omega t$$

$$v_2(t) = A_2 \cos(\underline{\omega t} + \phi_2) = a_2 \cos \omega t + b_2 \sin \omega t$$

same frequency

$$v_1(t) + v_2(t) = (a_1 + a_2) \cos \omega t + (b_1 + b_2) \sin \omega t$$

derivative: $\frac{d}{dt}(V_A \cos \omega t) = -\omega V_A \sin \omega t = \omega V_A \cos(\omega t + \frac{\pi}{2})$

integral: $\int V_A \cos \omega t dt = \frac{V_A \sin \omega t}{\omega} = \frac{V_A}{\omega} \cos(\omega t - \frac{\pi}{2})$


Fourier series

Example 5-15


$$v(t) = 5 - \frac{10}{\pi} \sin(2\pi 500t) - \frac{10}{2\pi} \sin(2\pi 1000t) - \frac{10}{3\pi} \sin(2\pi 1500t) + \dots$$

lowest frequency
is called the fundamental.

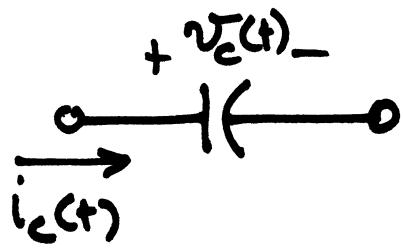Reactive component (capacitors, inductors)



$$i_c(t) = C \frac{dV_c(t)}{dt}$$

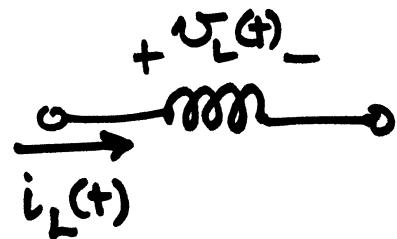

$$V_L(t) = L \frac{di_L(t)}{dt}$$

Example:

given i_c , find V_c

$$i_c(t) = C \frac{dV_c(t)}{dt}$$

$$\frac{1}{C} \int_{t_0}^t i_c(x) dx = \int_{t_0}^t dV_c(x)$$

$$\frac{1}{C} \int_{t_0}^t i_c(x) dx = V_c(t) - V_c(t_0)$$

usually (if you can) pick $t_0 = 0$

$$\text{power: } P_c(t) = i_c(t) V_c(t)$$

$P_c(t) > 0$ capacitor is absorbing power

$P_c(t) < 0$ capacitor is releasing stored power

$$P_c(t) = \frac{d}{dt} \left[\frac{1}{2} C V_c^2(t) \right]$$

$\curvearrowright W_c(t)$ energy in the capacitor

what is t_0 ?
what is $V_c(t_0)$?


↑
initial condition
often be zero

$$P_L(t) = \frac{d}{dt} \left[\frac{1}{2} L i_L^2(t) \right]$$

$i_L(t)$ energy
in the
inductor


Example 6-3

Given $v_c(t)$

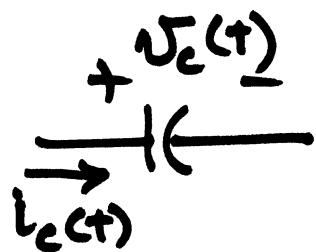

$$C = \frac{1}{2} \mu F$$

$$= \frac{1}{2} \times 10^{-6}$$

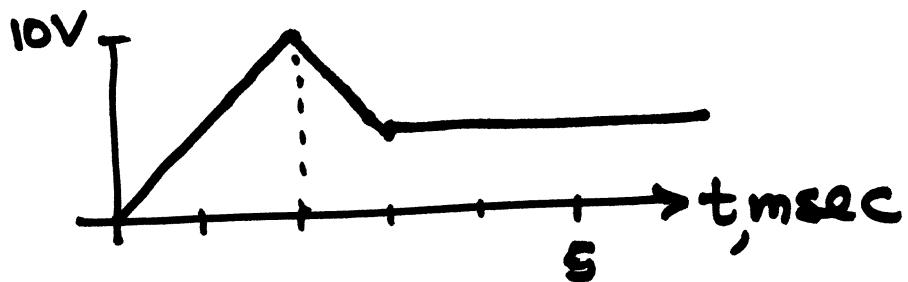



$$i_c(t) = C \frac{dv_c}{dt}$$

$$\left(\frac{1}{2} \times 10^{-6}\right) \left(\frac{10}{2 \times 10^{-3}}\right)$$

$$P = vi$$


$$= (10)(2.5 \text{ mA})$$

$$25 \text{ mW}$$

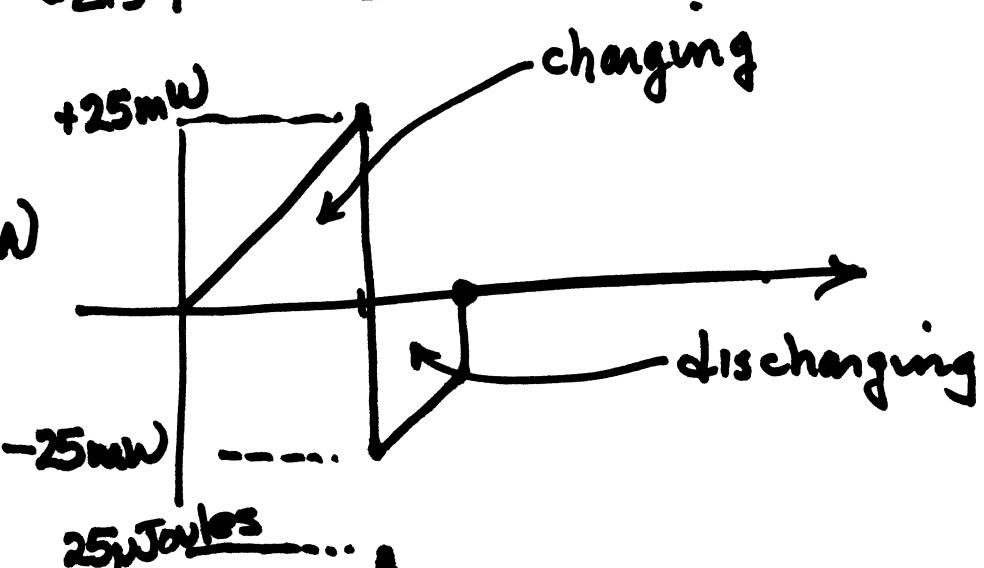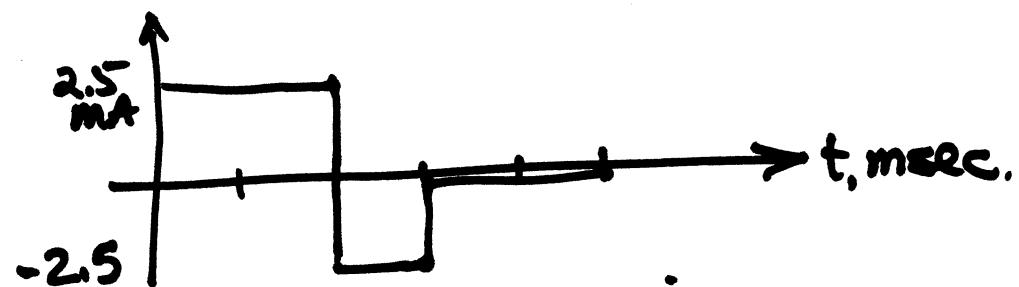


$$\omega_c = \frac{1}{2} C V^2$$
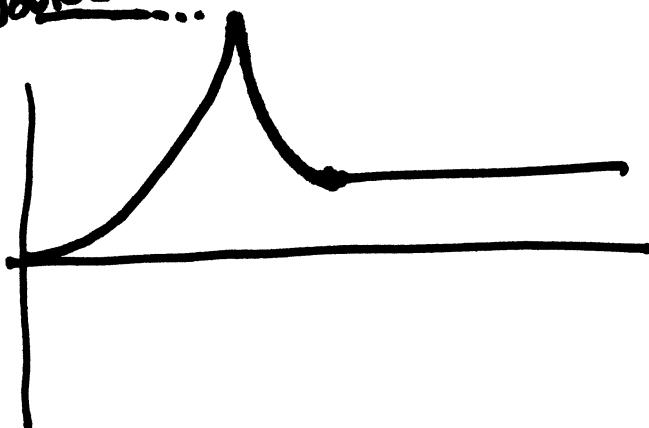
$$= \frac{1}{2} \left(\frac{1}{2} \times 10^{-6}\right) ()$$



OP AMP

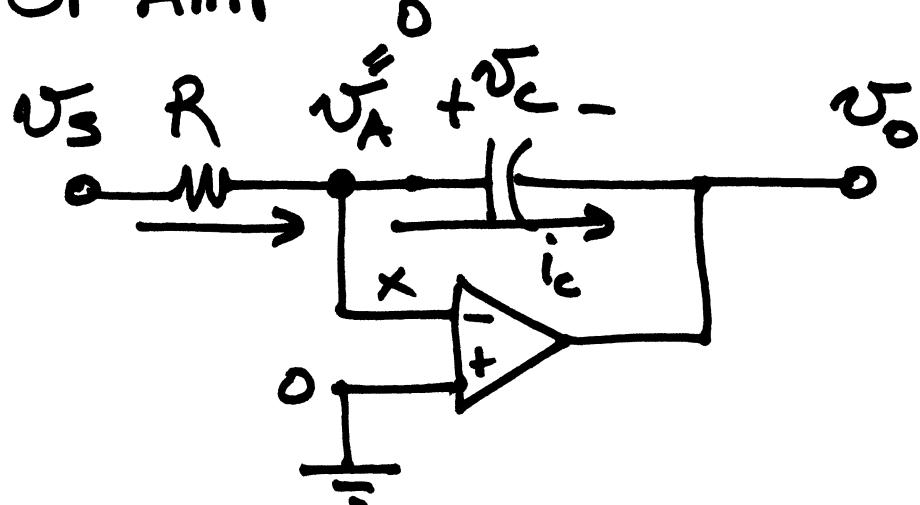

$$\frac{U_S - 0}{R} = i \quad i = C \frac{dU_C}{dt}$$

$$\frac{U_C}{R} = C \frac{d}{dt}(0 - U_O)$$

$$-\int_{t_0}^t \frac{U_C}{R} dt = -C \frac{dU_O}{dt}$$

$$-\frac{1}{RC} \int_{t_0}^t U_S dt = U_O(t) - U_O(t_0)$$