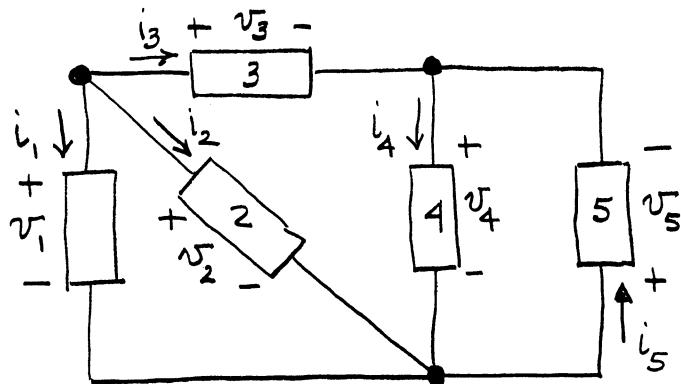


## Example 1-3



In this circuit the sign conventions are given on the drawing.  
If they are not given you should assign them!

The above labeling follows the passive sign convention.

The following circuit variables are measured.

Complete the missing variables. State whether the device is absorbing or supplying power.

	Device 1	Device 2	Device 3	Device 4	Device 5
v	+100 V		+25V	+75V	-75V
i		+5mA	+5mA		+5mA
P	-1W	+0.5W		0.75W	

$$\text{use } P = Vi$$

$$i_1 = \frac{P_1}{v_1} = \frac{-1}{100} = -0.01 \text{ Amp} \quad P_1 < 0 \Rightarrow \text{supplying power}$$

$$v_2 = \frac{P_2}{i_2} = \frac{0.5}{0.005} = 100V \quad P > 0 \Rightarrow \text{absorbing power}$$

$$P_3 = v_3 i_3 = (25)(0.005) = 0.125 \quad P > 0 \Rightarrow \text{absorbing power}$$

$$i_4 = \frac{P_4}{v_4} = \frac{0.75}{75} = 0.01 \quad P > 0 \Rightarrow \text{absorbing power}$$

$$P_5 = v_5 i_5 = (-75)(0.005) = -0.375 \quad P < 0 \Rightarrow \text{supplying power}$$

## Example 1.4

	Device 1	Device 2
v	+ 10 V	- 13.3 volts.
i	- 3 A	- 3 A
P	- 30 watt (supplying)	+ 40 W


passive sign convention

$$\varphi = vi$$

$$\varphi = (+10)(-3) = -30 \text{ watts.}$$

$$\begin{aligned}\varphi &= vi \\ +40 &= v(-3)\end{aligned}$$
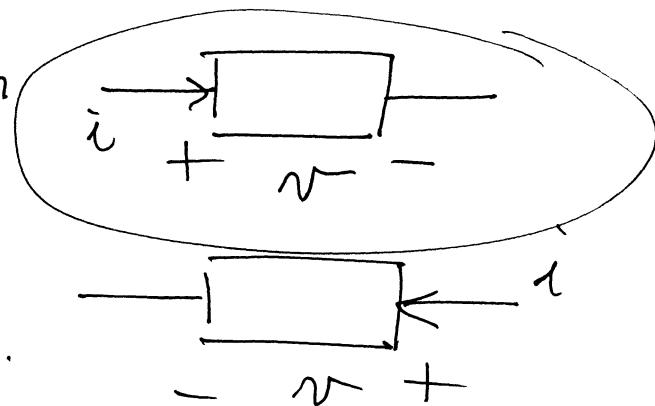
$$v = \frac{40}{-3} = -13.3 \text{ volts.}$$



### Example 1-4

The working variables of a set of two-terminal electrical devices are observed to be as follows:

	Device 1	Device 2	Device 3	Device 4	Device 5
$v$	+10V.	?	-15V.	+5	?
$i$	-3A.	-3A.	+10mA	?	-12mA
$P$		+40W.	?	+10mW	-120mW

Using the passive sign convention, find the magnitude and sign of the unknown variable and state whether the device is absorbing or delivering power.

Answer:

$$\text{Device 1: } P = vi = (+10)(-3) = -30 \text{ watts} \quad (\text{delivering power})$$


$$\text{Device 2: } P = vi = v(-3) = +40 \Rightarrow v = \frac{40}{-3} = -13.3 \text{ volts} \\ (\text{ } P > 0, \text{ absorbing power})$$

$$\text{Device 3: } P = vi = (-15)(10 \times 10^{-3}) = -150 \times 10^{-3} = -0.15 \text{ watts} < 0 \\ (\text{delivering power})$$

$$\text{Device 4: } P = vi = (5)i = 10 \text{ mW} \Rightarrow i = \frac{10 \text{ mW}}{5 \text{ V}} = \frac{10 \times 10^{-3}}{5} = 2 \times 10^{-3} = 2 \text{ mW} \\ (\text{absorbing power})$$

$$\text{Device 5: } P = vi = v(-12 \text{ mA}) = -120 \text{ mW} \\ \Rightarrow v = \frac{-120 \text{ mW}}{-12 \text{ mA}} = \frac{-120 \times 10^{-3}}{-12 \times 10^{-3}} = +10 \text{ V} \\ (\text{ } P < 0, \text{ delivering power})$$

GROUND — VOLTAGE REFERENCE

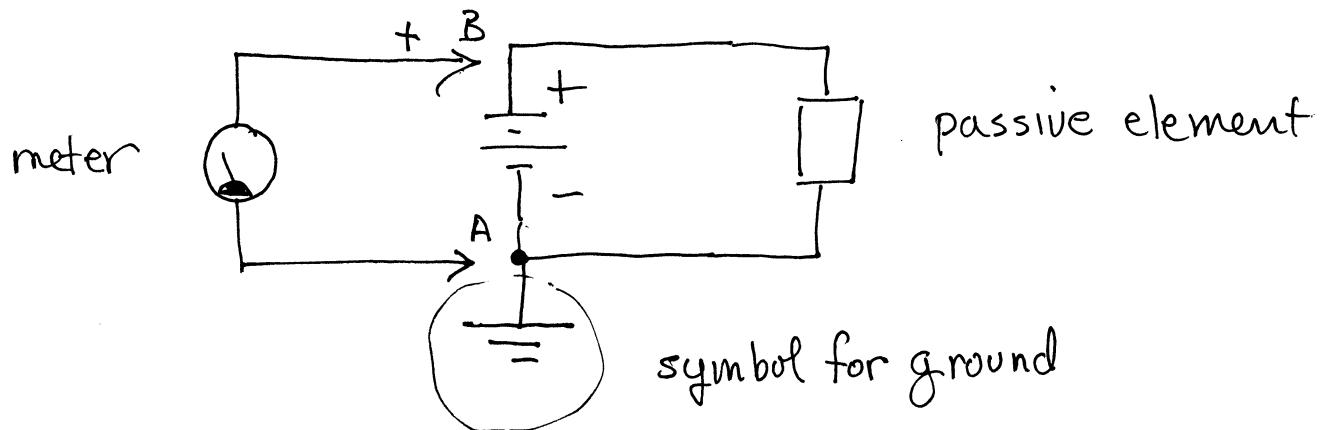

$V_{BA}$

voltage or current  
+ terminal  
+ point

- terminal reference.

$V_B$

no second subscript  
voltage wrt ground.

red - +  
black - -  
+ 7.5  
- 7.5

GROUND

A<sup>o</sup>      B<sup>o</sup>      C<sup>o</sup>

 symbol for electrical ground  
common voltage reference

The notation  $v_A(t)$ ,  $v_B(t)$ ,  $v_c(t)$  means the voltage at that node with respect to ground, assumed to be zero.

Voltage ALWAYS is measured between two points.

I might also be interested in the voltage

$v_{AB}(t)$  This is the voltage between two nodes. Polarity should be indicated on circuit diagram.



+  $v_{AB}$  -  
A<sup>o</sup>      o<sub>B</sub>



What is ground?

- The reference for all voltage measurements.

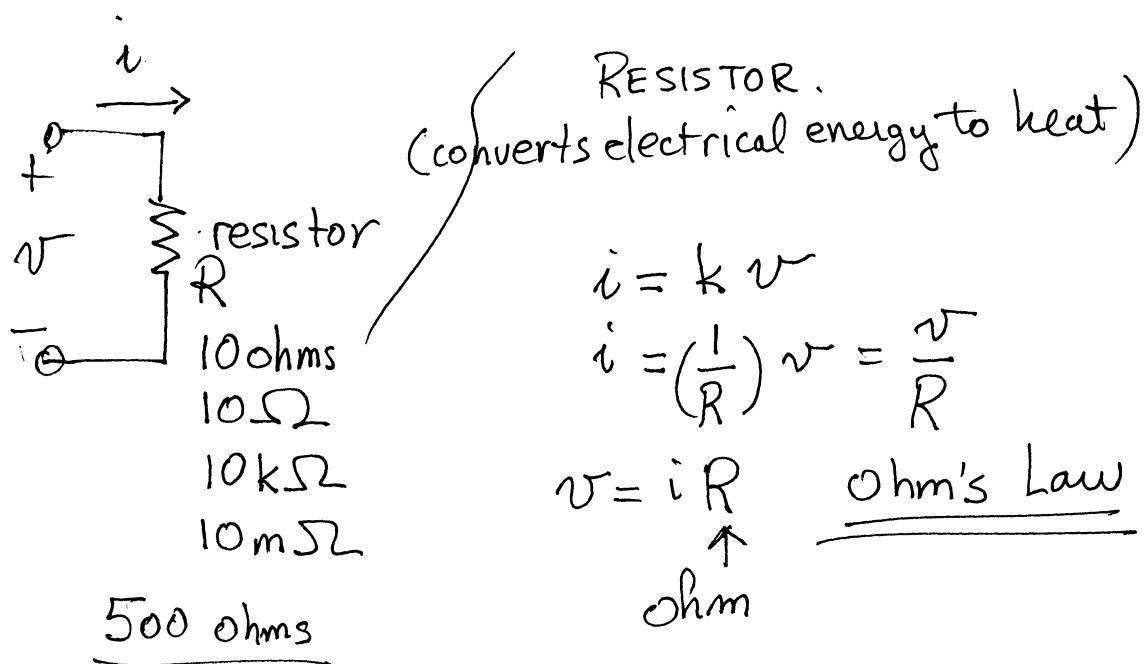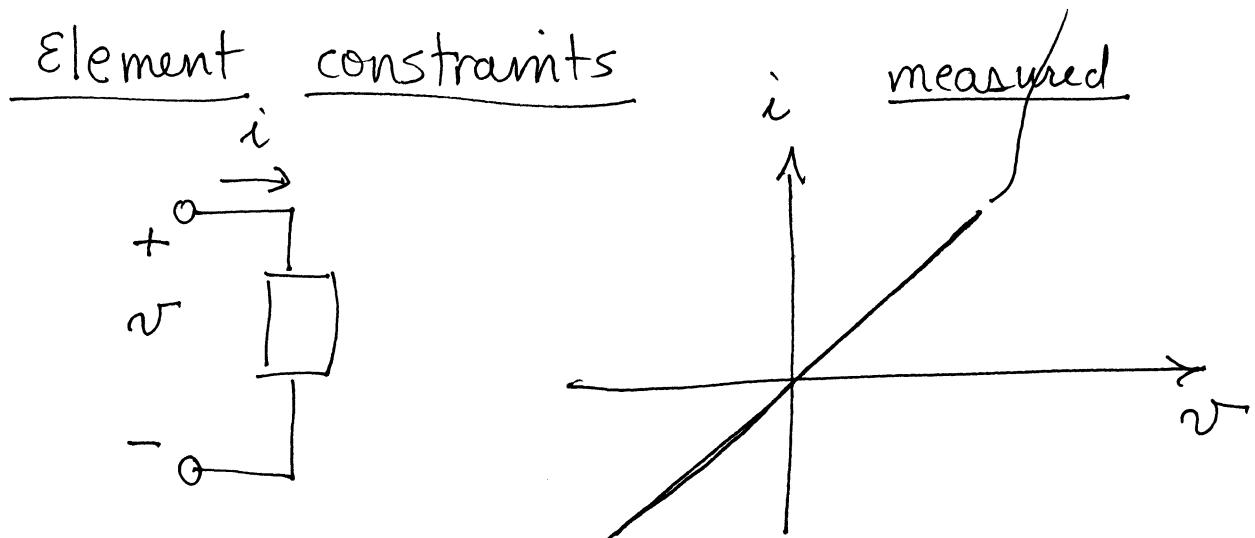one subscript-measurement wrt ground  
two subscripts-measurement between nodes specified



BRN	BRN	YEL	GOLD
1dig	2ndig	MULT	TOL
1	1	$10^4$	$\pm 5\%$