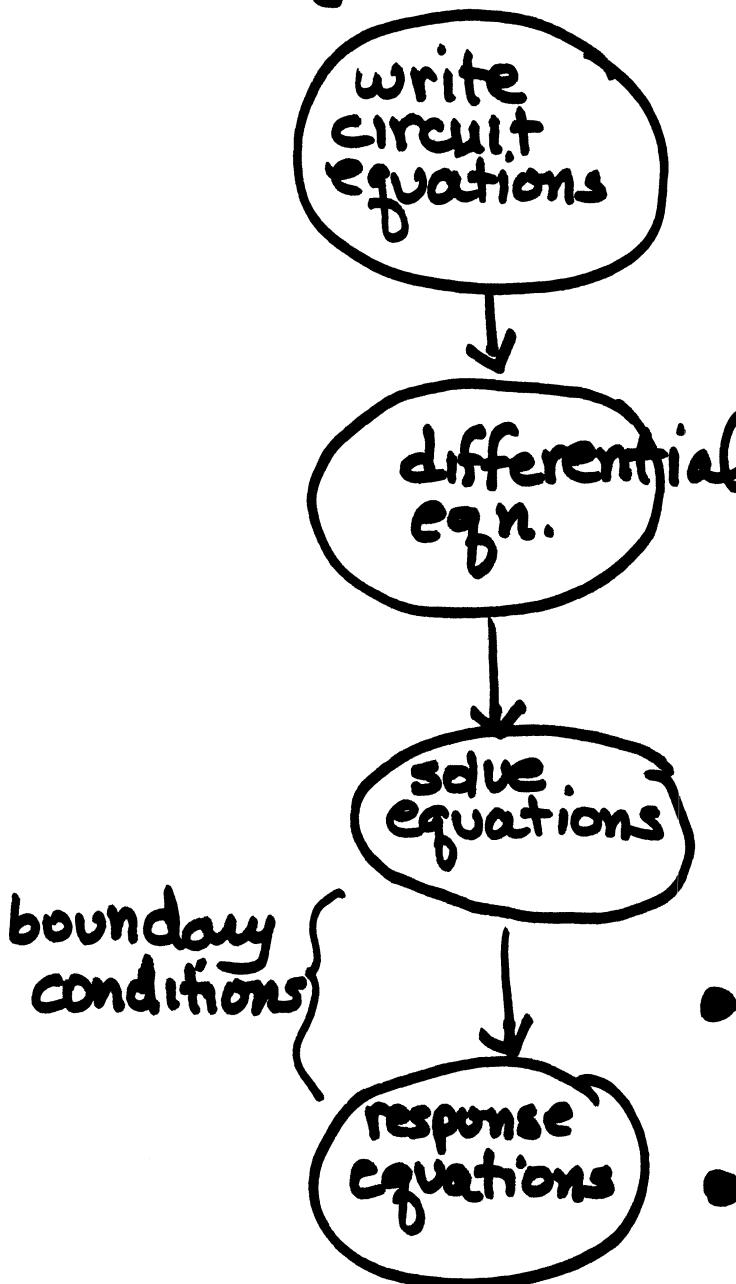


Circuits with one reactive element

Analyze such a circuit



$$i_C, V_C, i_L, V_L$$

put in component constraints



$$i_C = C \frac{dV_C}{dt}$$

$$V_L = L \frac{di_L}{dt}$$

use a few techniques
to solve equations

- method of undetermined coefficients

~~Laplace~~
~~Phasor~~

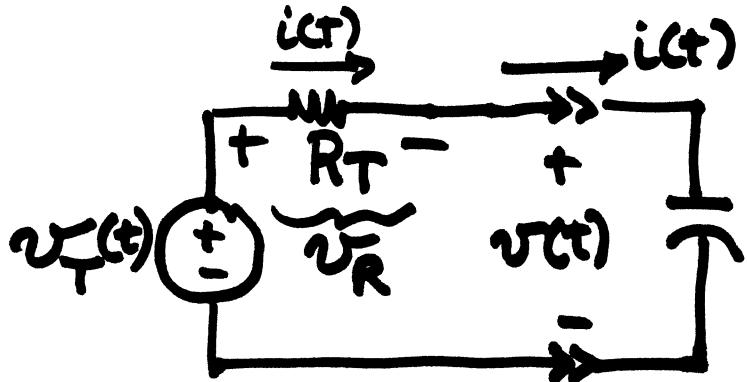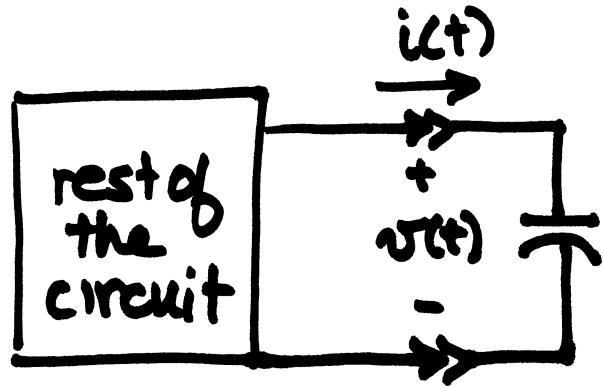

use KVL

$$-v_T(t) + i(t)R_T + v(t) = 0$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$-v_T(t) + R_T C \frac{dv(t)}{dt} + v(t) = 0$$

$$R_T C \frac{dv}{dt} + v = v_T$$

$v(t)$ is the response
function
state variable

$\underbrace{v_T}_{\text{input forcing function}}$
switch (step)
signal generator (sinusoid)

7.4 Forced sinusoidal response

$$R_T C \frac{d v}{dt} + v = V_T$$

$$R_T C \frac{d v_F(t)}{dt} + v_F(t) = V_A \cos \omega t$$

↑
forced response

(steady state response to signal generator)

method of undetermined coefficients

$$\text{Assume } v_F(t) = a \cos \omega t + b \sin \omega t$$

$$R_T C \frac{d}{dt} (a \cos \omega t + b \sin \omega t) + (a \cos \omega t + b \sin \omega t) = V_A \cos \omega t$$

$$R_T C (-a \omega \underline{\sin \omega t} + b \omega \cos \omega t) + (a \cos \omega t + b \underline{\sin \omega t}) = V_A \cos \omega t$$

Must always be true

$$-a \omega R_T C \underline{\sin \omega t} + b \underline{\sin \omega t} = 0$$

$$+ b \omega R_T C \cos \omega t + a \cos \omega t = V_A \cos \omega t$$

$$-a \omega R_T C + b = 0$$

$$+ b \omega R_T C + a = V_A$$

After some algebra

$$a = \frac{V_A}{1 + (\omega R_T C)^2}$$

$$b = \frac{\omega R_T C V_A}{1 + (\omega R_T C)^2}$$

$$v_F(t) = \frac{V_A}{1 + (\omega R_T C)^2} [\cos \omega t + \omega R_T C \sin \omega t]$$

$$v_F(t) = \frac{V_A}{\sqrt{1 + (\omega R_T C)^2}} \underline{\cos(\omega t + \theta)}$$
$$\theta = \tan^{-1}(-\omega R_T C)$$

Electrical engineers use a simple algebraic technique
→ phasors

better technique to manipulate

$$\underline{V(t)} = V_A \cos(\omega t + \phi)$$

Euler identity

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$j = \sqrt{-1}$$

Then use Euler identity to write cosines as exponentials

$$\operatorname{Re}\{1e^{j\theta}\} = 1 \cos\theta$$

$$\operatorname{Re}\{\underline{\cos\theta + j\sin\theta}\} = \cos\theta \leftarrow \text{use this}$$

$$\operatorname{Im}\{\underline{\cos\theta + j\sin\theta}\} = \sin\theta \quad \begin{matrix} \text{not too} \\ \text{useful} \end{matrix}$$

$$V_A \cos(\omega t + \phi) = \operatorname{Re}\{V_A e^{j(\omega t + \phi)}\}$$


$$= \operatorname{Re}\left\{\underline{V_A e^{j\phi}} e^{j\omega t}\right\}$$

$$\underline{V} = V_A e^{j\phi}$$


phasor

assume
and never
write it

V is a vector

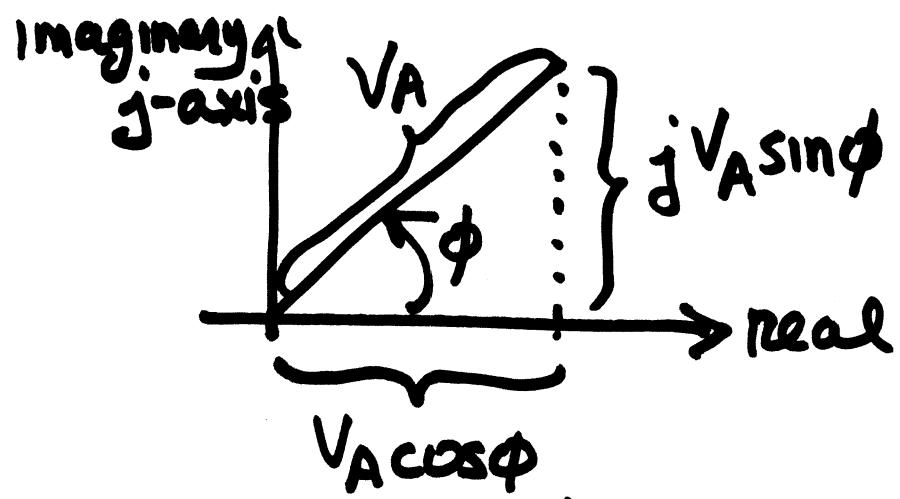

why do we ignore $e^{j\omega t}$

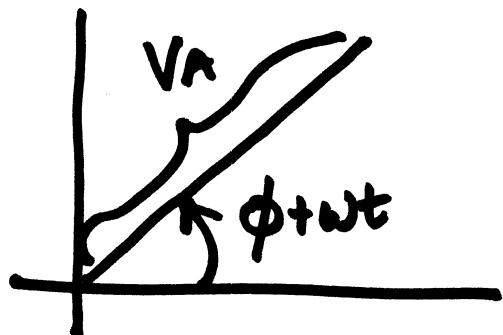

Example 8-1

$$v_1(t) = 10 \cos(\underline{1000t} - 45^\circ)$$

$$v_2(t) = 5 \cos(\underline{1000t} + 30^\circ)$$

$$v(t) = v_1(t) + v_2(t)$$


$-j45^\circ$

phasor for $v_1(t)$: $\underline{V_1} = 10 e^{\underline{-j30^\circ}}$

for $v_2(t)$: $\underline{V_2} = 5 e^{\underline{j30^\circ}}$

$$\underline{V_1} = 10(\cos 45^\circ - j \sin 45^\circ)$$

$$= 7.07 - j 7.07$$

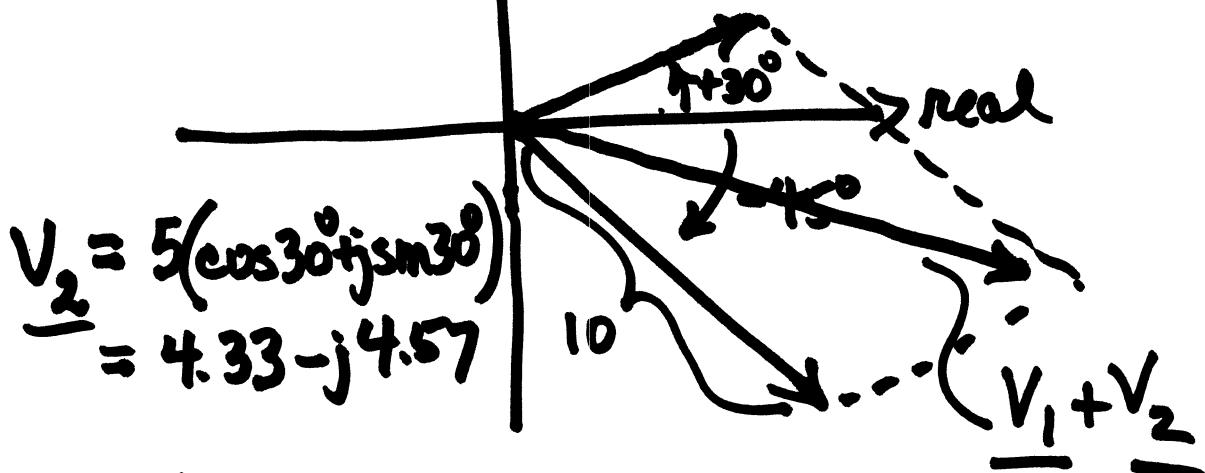

$$\underline{V_1} + \underline{V_2} = 11.4 - j 4.57$$