

phasors — vector notation for representing sinusoids

$$\underline{V}(t) = \underline{V}_1(t) + \underline{V}_2(t)$$


$$\underline{V}_1 = 10\cos(1000t - 45^\circ)$$

$$\underline{V}_2 = 5\cos(1000t + 30^\circ)$$

cosines $\bar{\omega}$

$$\underline{V}_1 = 10 \angle -45^\circ$$

$$\underline{V}_2 = 5 \angle +30^\circ$$

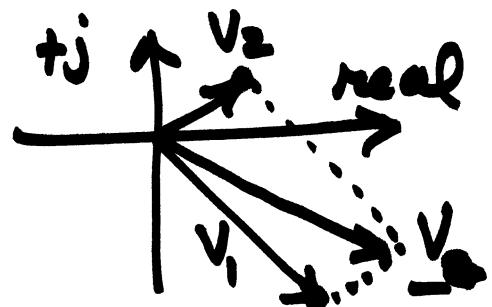

$$\begin{aligned} \underline{V} &= \underline{V}_1 + \underline{V}_2 = 10 \angle -45^\circ + 5 \angle +30^\circ \\ &= 10 \cos 45^\circ - j 10 \sin 45^\circ + 5 \cos 30^\circ + j 5 \sin 30^\circ \end{aligned}$$

$$\begin{aligned} \underline{V} &= (10 \cos 45^\circ + 5 \cos 30^\circ) + j (-10 \sin 45^\circ + 5 \sin 30^\circ) \\ &= 7.07 - j 7.07 + 4.33 + j 2.5 \end{aligned}$$

$$\underline{V} = 11.4 - j 4.57 = 12.28 \angle -21.8^\circ$$

$$V(t) = 12.28 \cos(1000t - 21.8^\circ)$$

Integration and differentiation

$$\frac{d}{dt} [15 \cos(200t - 30^\circ)]$$

$$\cdot \underline{15} \underline{-30^\circ} \\ ; \quad \underline{-j30^\circ} \quad \underline{j200t} \\ \underline{15e} - \underline{\frac{e}{}};$$

usually we don't
write this

$$\frac{d}{dt} \operatorname{Re} \{ 15e^{-j30^\circ} e^{j200t} \}$$

$$\operatorname{Re} \left\{ \frac{d}{dt} (15e^{-j30^\circ} e^{j200t}) \right\}$$

$$\operatorname{Re} \left\{ j200 \ 15e^{-j30^\circ} e^{j200t} \right\}$$

in general $j\omega$ Phasor
derivative

Integral $\frac{\text{Phasor}}{j\omega}$ } Integral

$$\frac{d}{dt} [15 \cos(200t - 30^\circ)]$$

$$\frac{d}{dt} [15 e^{-j30^\circ}]$$

$$\frac{d}{dt} [15 e^{-j30^\circ}]$$


$$j\omega 15 e^{-j30^\circ}$$

200

$$j(200)(15) e^{-j30^\circ}$$

$$e^{j90^\circ} 3000 e^{-j30^\circ}$$

$$3000 e^{+j60^\circ}$$

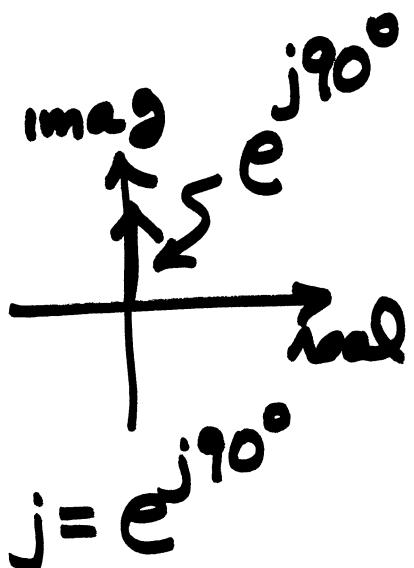

phasor derivative

$$3000 \cos(200t + 60^\circ)$$

Phasor circuit analysis

resistors

$$V_R = R i_R$$

$$\underline{V}_R = R \underline{I}_R$$

inductor

$$V_L = L \frac{di_L}{dt}$$

$$\underline{V}_L = L j\omega \underline{I}_L = \underline{\underline{j\omega L}} \underline{I}_L$$

↑
impedance
(generalized
resistance)

capacitor

$$i_c = C \frac{dV_c}{dt}$$

$$\underline{I}_c = C j\omega \underline{V}_c = j\omega C \underline{V}_c$$

$$\underline{V}_c = \frac{1}{j\omega C} \underline{I}_c$$

↑
impedance

do circuit analysis

convert

$$R \rightarrow R$$


$$L \rightarrow j\omega L$$

$$C \rightarrow \frac{1}{j\omega C}$$

} behave
algebraically
like
resistors

all sources
currents
voltages

Example 8-5

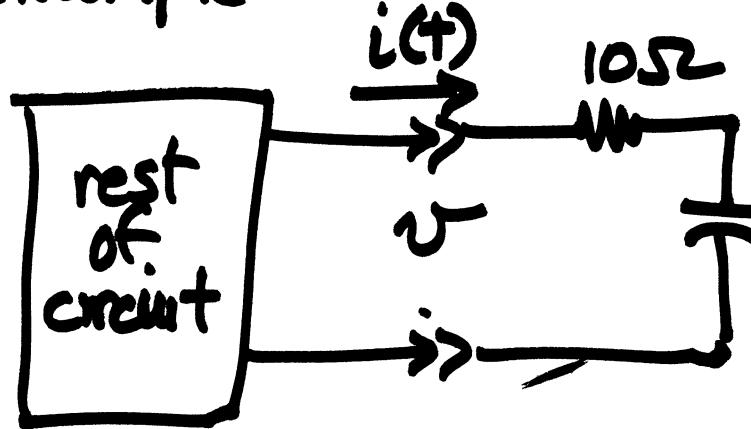

$$i(t) = 4 \cos 5000t$$

$$\underline{I} = 4 \angle 0^\circ$$

$$10 \mu F = 4 + j0$$

convert impedance

$$\underline{V_R} = iR \quad | \quad 4(10) = 40 = \underline{V_R}$$

real phasors

$$\underline{Z_C} = \frac{1}{j\omega C} = \frac{1}{j(5000)(10 \times 10^{-6})} = -j20$$

$$\underline{V_C} = \underline{I} \underline{Z_C} = (4)(-j20) = -j80$$

$$v(t) = \underline{V_R} + \underline{V_C}$$

$$\underline{V} = \underline{V_R} + \underline{V_C} = 40 - j80 = 89.44 \angle -64^\circ$$

$$v(t) = 89.44 \cos(5000t - 64^\circ)$$