

# Phasors (sinusoidal steady state)

- transform your circuit
  - R, L, C  $\rightarrow$  impedance
  - sources  $\rightarrow$  phasors
  - currents, voltages  $\rightarrow$  phasors
- solve circuit algebraically
  - Ohm's Law, KVL, KCL, superposition
- inverse transform your answer back to time domain

impedance       $R \rightarrow R$   
(use  $Z$  to indicate impedance)       $C \rightarrow \frac{1}{j\omega C}$   
 $Z_R, Z_C, Z_L$        $L \rightarrow j\omega L$


impedances behave just like resistances

impedances in series       $Z_{EQ} = Z_1 + Z_2 + \dots + Z_N$

impedances in parallel       $\frac{1}{Z_{EQ}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots$

### Example 8-6


operating in sinusoidal steady state

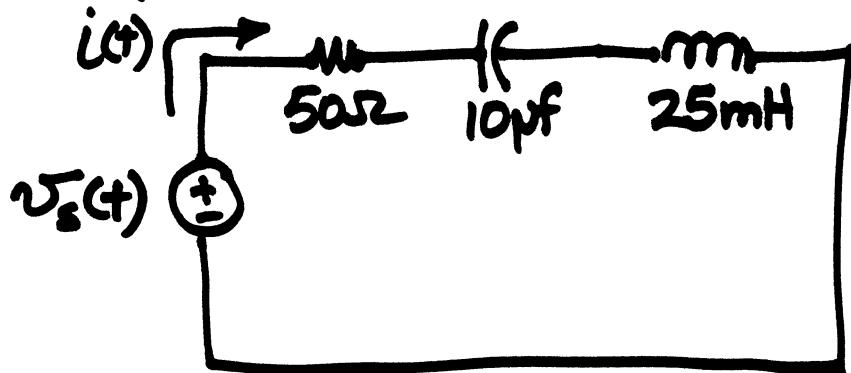


$$V_s(t) = 35\cos 1000t$$

$\therefore$  we can use phasors

↓ transform circuit

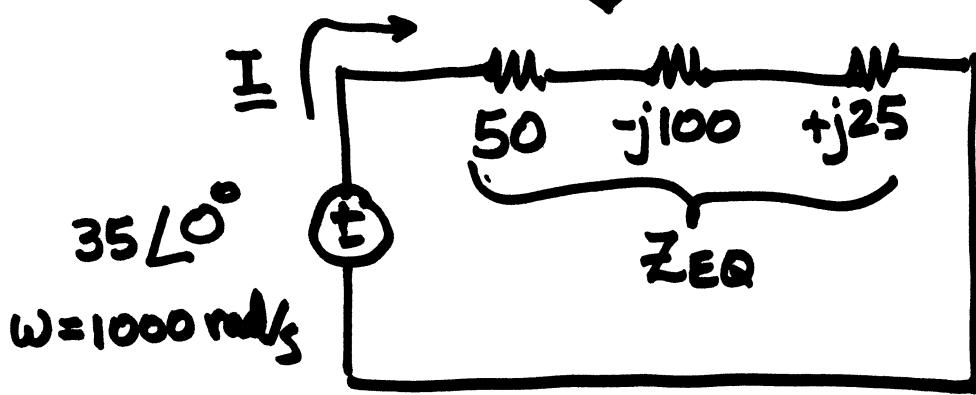
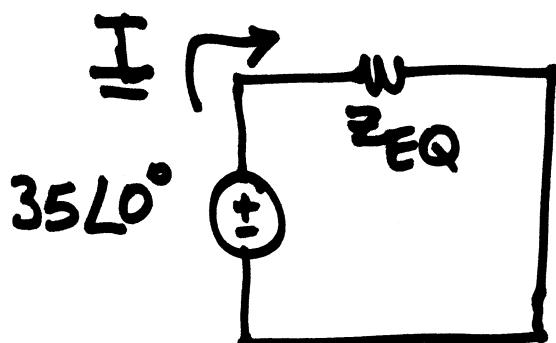
$$\text{series: } Z_{EQ} = 50 - j100 + j25 \\ = 50 - j75 \Omega$$



Ohm's Law

$$I = \frac{35 L 0^\circ}{Z_{EQ}} = \frac{35 + j0}{50 - j75} = 0.215 + j0.323$$

rect  $\rightarrow$  polar

$$I = 0.388 L + 56.3^\circ$$

$$i(t) = 0.388 \cos(1000t + 56.3^\circ)$$

$$Z_R = 50 \Omega$$

$$Z_{IL} = j\omega L$$

$$= j(1000)(25 \times 10^{-3})$$

$$Z_L = +j25 \Omega$$

$$Z_C = \frac{1}{j\omega C} = j \frac{1}{(1000)(10 \times 10^{-6})}$$


$$Z_C = \frac{100}{j} \cdot \frac{j}{j} = -j100$$

$$\frac{1}{j} \rightarrow -j$$


### Example 8-9

sinusoidal steady state

$$i_s(t) = 50 \cos 2000t \text{ mA}$$

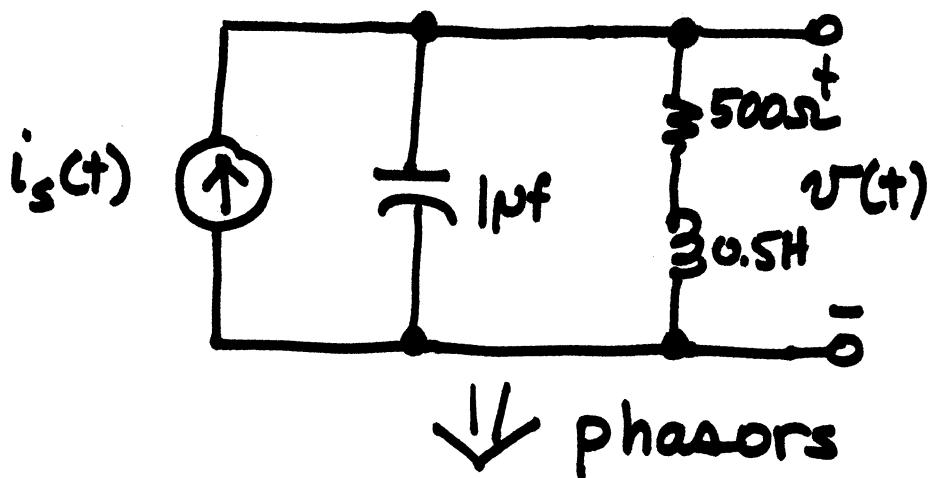


↓ phasors

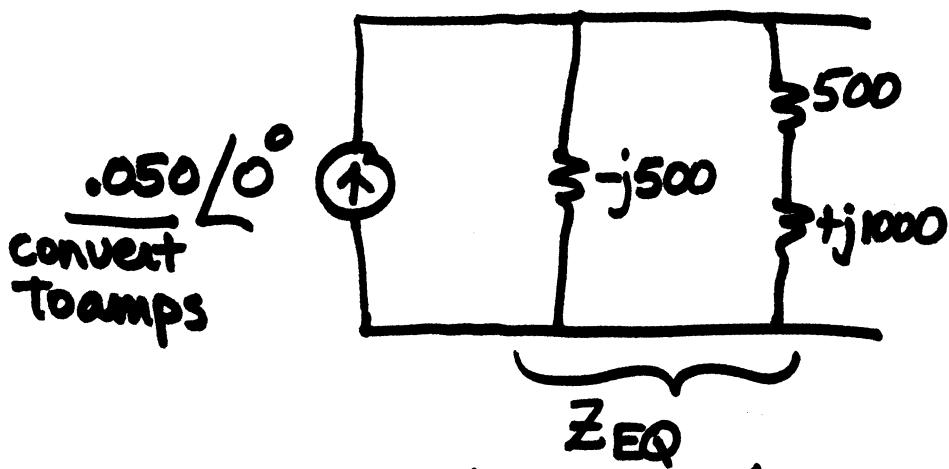

$$Z_{EQ} = (-j500) \parallel (500 + j1000) \quad \text{in series}$$

$$Z_{EQ} = \frac{(-j500)(500 + j1000)}{-j500 + 500 + j1000} = \frac{-j500(500 + j1000)}{500 + j500}$$

$$Z_{EQ} = 250 - j750 \Omega$$

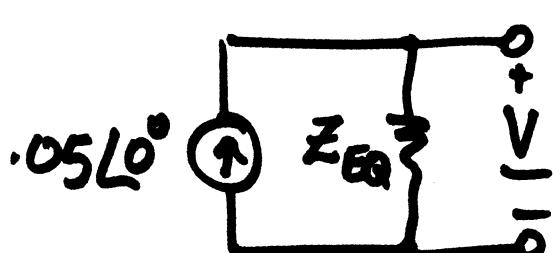

$$\begin{aligned} V &= I Z_{EQ} = (.05)(250 - j750) \\ V &= 12.5 - j37.5 \rightarrow 39.5 \angle -71.6^\circ \end{aligned}$$

Rectangular → polar

$$V(t) = 39.5 \cos(2000t - 71.6^\circ)$$

# Chapter 12 - Frequency Response

what happens when  $\omega$  changes

