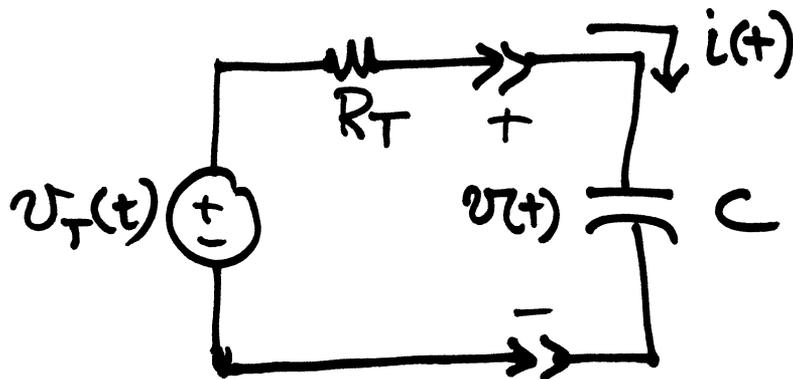


TRANSIENTS



$$-v_T + i R_T + v = 0$$

$$\uparrow i = C \frac{dv}{dt}$$

$$-v_T + R_T C \frac{dv}{dt} + v = 0$$


$$R_T C \frac{dv(t)}{dt} + v(t) = v_T(t)$$

$v(t)$ is the state variable

$A \cos(\omega t)$

sinusoidal steady state

stored energy $\frac{1}{2} C v^2(t)$

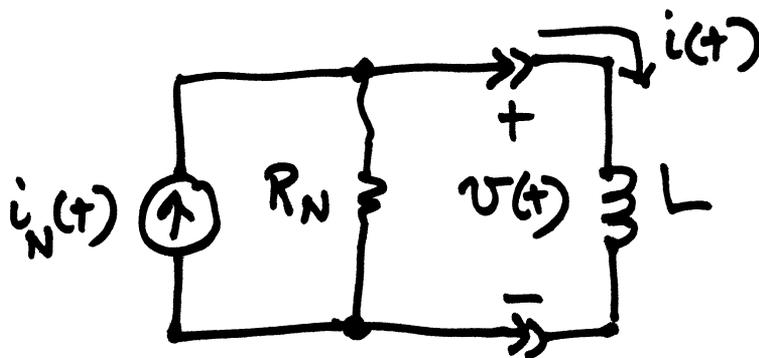

$$\frac{L}{R_N} \frac{di(t)}{dt} + i(t) = i_N(t)$$

$i(t)$ is the state variable

stored energy $\frac{1}{2} L i^2$

What does the solution depend on?

1. input $\begin{cases} \text{sinusoidal steadystate } A \cos \omega t \\ \text{transients } \begin{cases} \text{switch } u(t) \\ \text{nothing} \end{cases} \end{cases}$ 

2. circuit values R_T, C
 R_N, L

3. initial conditions (switched)

find the solution for zero input
capacitive circuit

$$R_T C \frac{dv(t)}{dt} + v(t) = \cancel{v_T(t)}^0$$

$$R_T C \frac{dv}{dt} + v = 0 \quad \text{Assume a solution}$$

$$k e^{st}$$

method of undetermined
coefficients

$$\frac{d}{dt}(Ke^{st}) = sKe^{st}$$

$$R_T C s Ke^{st} + Ke^{st} = 0$$

$$Ke^{st} (R_T C s + 1) = 0$$

require this
to be zero

$$R_T C s + 1 = 0$$

$$s = -\frac{1}{R_T C} \leftarrow \text{time constant}$$


$$v(t) = Ke^{st} = Ke^{-\frac{t}{R_T C}}$$

for an inductive circuit



$$i(t) = Ke^{-\frac{R_T}{L} t} = Ke^{-\frac{t}{L/R_T} \leftarrow \text{time constant}}$$

K (in both cases)
comes from initial conditions

Example 7-1

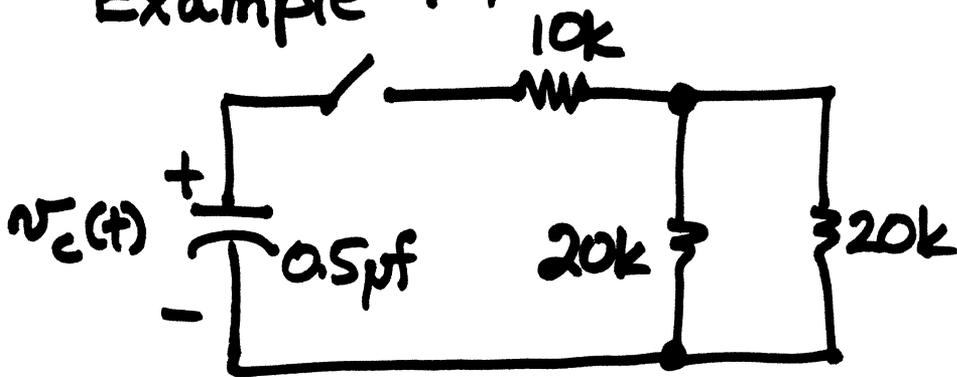

$v_c(t=0) = 30 \text{ volts}$

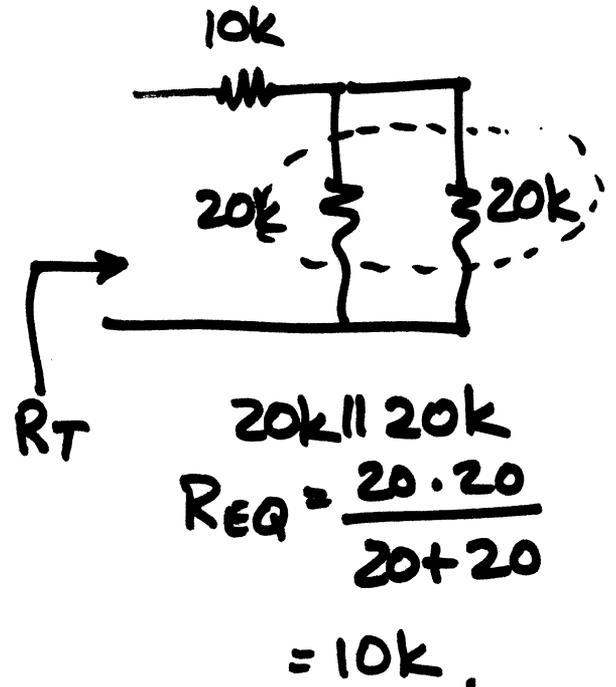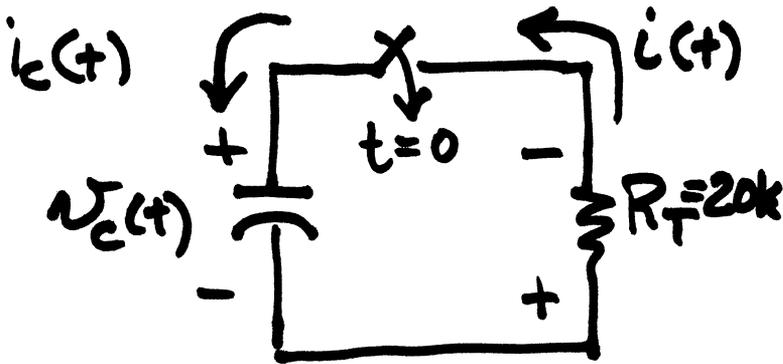

for $t \geq 0$



$$-v_c(t) - i(t) R_T = 0$$

$$i(t) = i_c(t) = C \frac{dv_c}{dt}$$

$$-v_c(t) - R_T C \frac{dv_c(t)}{dt} = 0$$

$$R_T C \frac{dv_c(t)}{dt} + v_c(t) = 0$$

Assume $v_c(t) = k e^{st}$

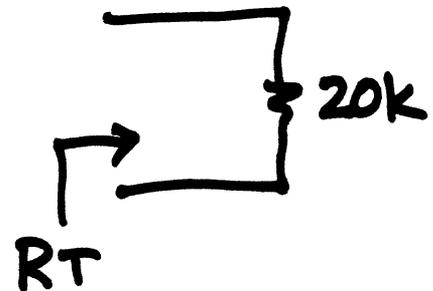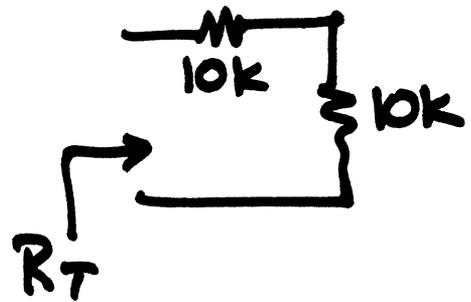

Substitute $v_c(t) = Ke^{st}$
into D.E.

$$R_T C s (Ke^{st}) + (Ke^{st}) = 0$$

$$Ke^{st} (R_T C s + 1) = 0$$

$$R_T C s + 1 = 0$$

$$s = -\frac{1}{R_T C} = -\frac{1}{(20 \times 10^3)(0.5 \times 10^{-6})}$$

$$= -100$$

$$v_c(t) = Ke^{-100t}$$


$$\text{time constant} \\ = \frac{1}{100} = 0.01 \text{ sec.}$$

$$v_c(t=0) = 30 \text{ volts.}$$

$$30 = Ke^{-0} = K$$

$$v_c(t) = 30e^{-100t} \quad t \geq 0$$

$$30e^{-100t} u(t)$$

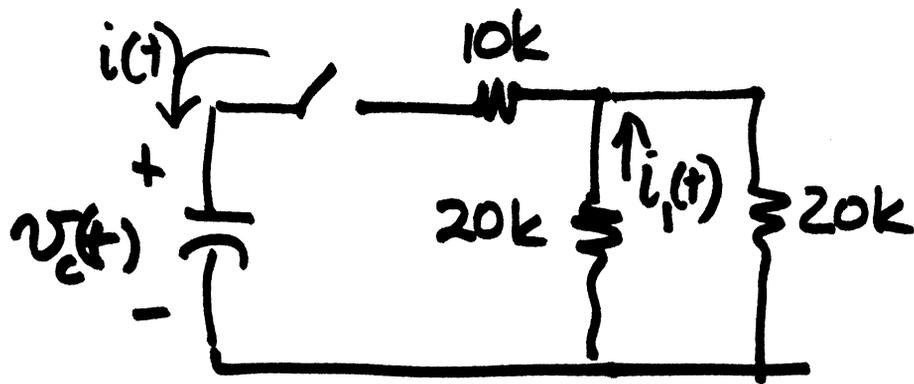

$$i(t) = i_c(t) = C \frac{dv_c}{dt}$$

$$= (0.5 \times 10^{-6}) \frac{d}{dt} (30e^{-100t})$$

$$i(t) = (0.5 \times 10^{-6})(30)(-100)e^{-100t}$$

=

$$i_1(t) = \frac{20k}{20k+20k} i(t)$$