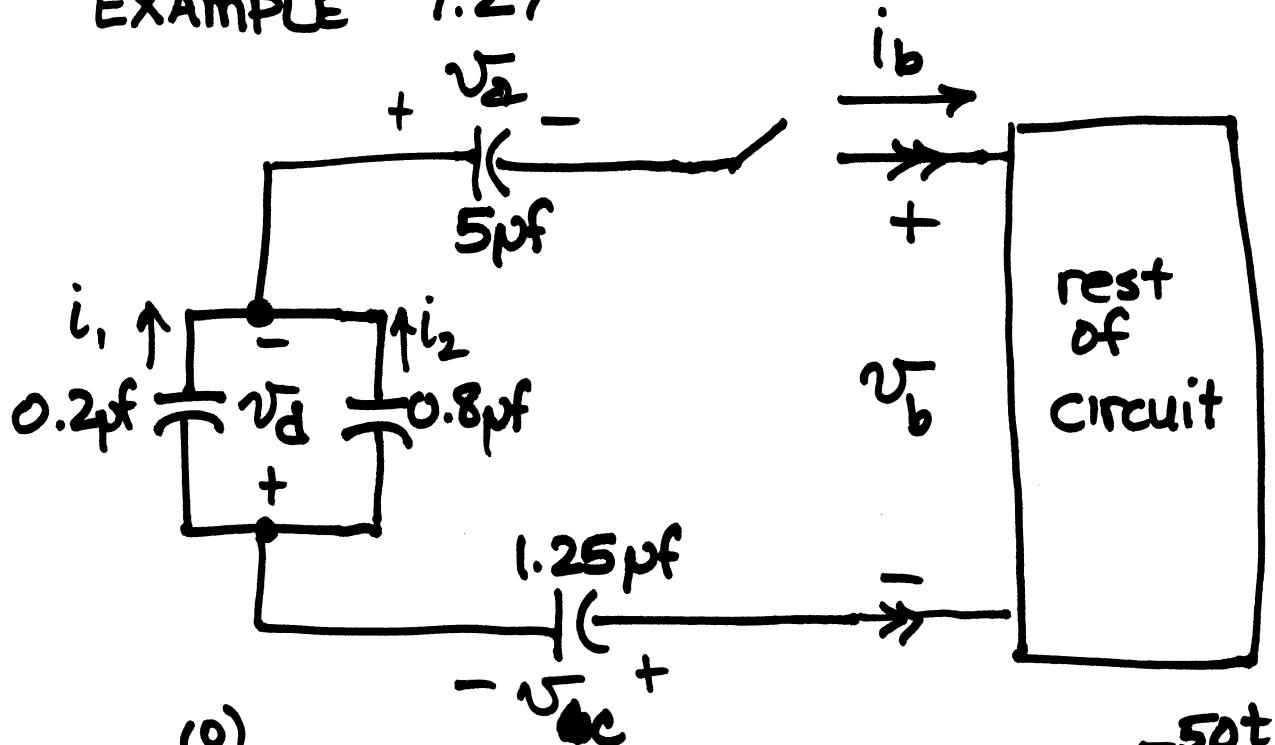


INITIAL CONDITIONS

EXAMPLE 7.27




measure $i_b(t) = -5e^{-50t}$ mA

$$0.2 \mu F \xrightarrow{250} 0.8 \mu F \Rightarrow 250 \parallel 1.0 \mu F$$

$$1 \mu F \parallel \frac{1}{5 \mu F} \parallel \frac{1}{1.25 \mu F} = \frac{1}{1} + \frac{1}{5} + \frac{1}{1.25}$$

$$C_{EQ} = 0.5 \mu F$$

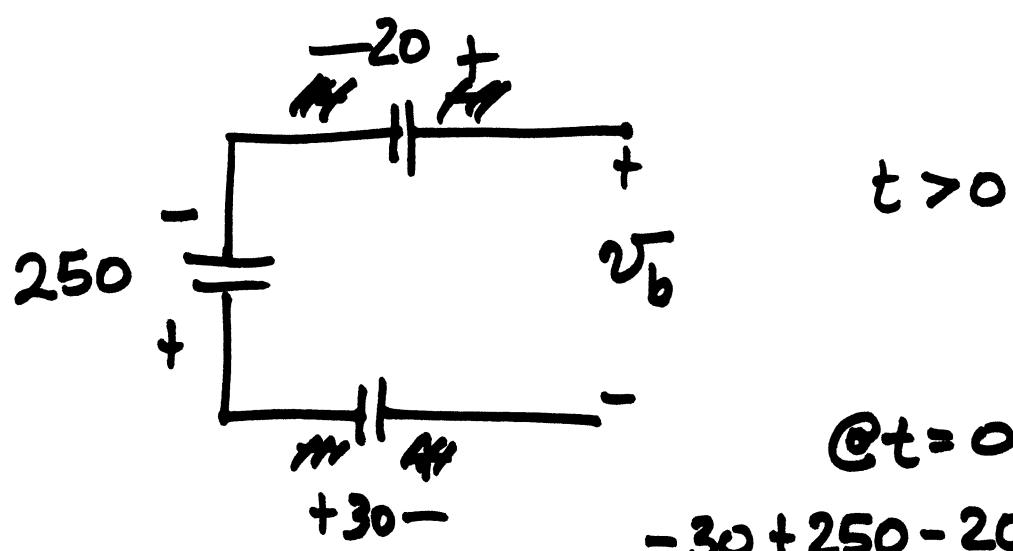


$\text{At } t = 0$

$$-30 + 250 - 20 + V_b = 0$$

$$200 + V_b = 0$$
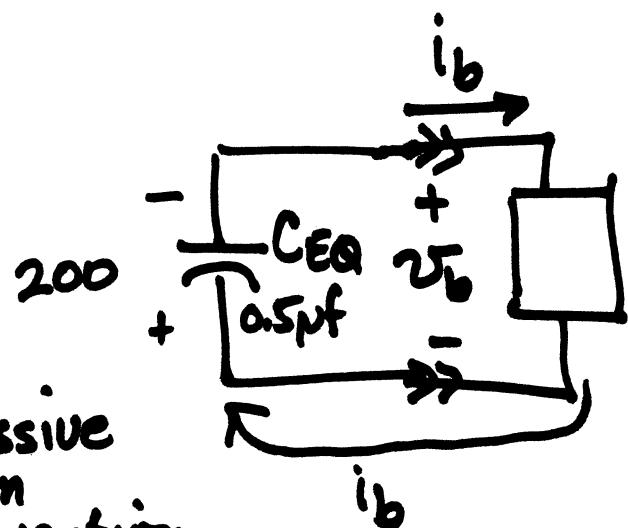
$$\underline{V_b(t=0) = -200 \text{ volts.}}$$



passive sign convention is OK.

$$i_b = C_{EQ} \frac{dV_b}{dt} = C \frac{d(-V_b)}{dt}$$

$$i_b = -C_{EQ} \frac{dV_b}{dt}$$

$$\int_0^t -\frac{1}{C_{EQ}} i_b dt = \int_0^t dV_b$$

$$-\frac{1}{C_{EQ}} \int_0^t (-5 \times 10^{-3} e^{-50x}) dx = V_b(t) - V_b(0)$$


$$\frac{5 \times 10^{-3}}{5 \times 10^{-6}} \frac{e^{-50x}}{-50} \Big|_0^t = V_b(t) - \underline{\underline{(-200)}}$$

$$v_b(t) + 200 = \frac{5 \times 10^{-3}}{\underline{.5 \times 10^{-6} (-50)}} [e^{-50t} - e^{\cancel{0^1}}]$$

$$v_b(t) + 200 = -200 e^{-50t} + \cancel{200}$$

$$v_b(t) = -200 e^{-50t} \text{ volts.}$$

Example 7.27

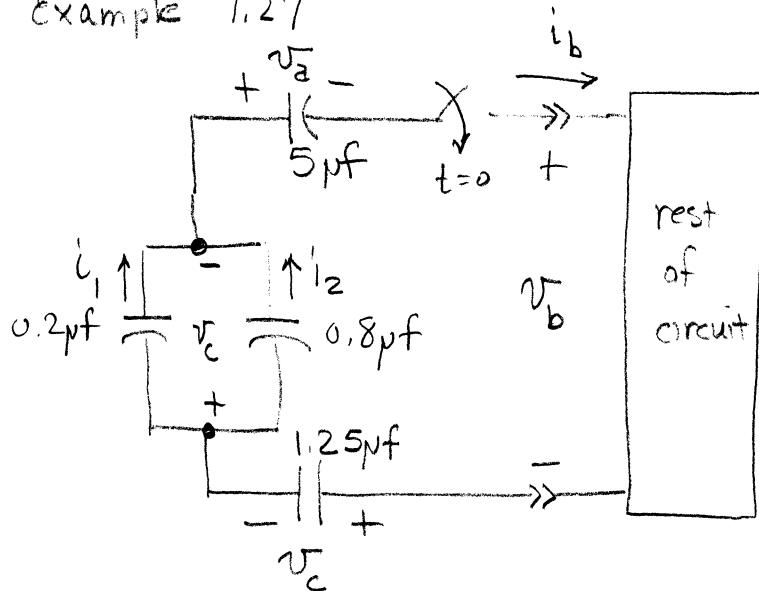

Given the initial conditions we determine that:
 $i_b(t) = -5e^{-50t} \text{ mA}$ for $t \geq 0$


Determine the equivalent circuit for the capacitances, the voltage v_b , and the power being delivered to the rest of the circuit.

$$v_a(0) = -20$$

$$v_c(0) = -30$$

$$v_a(0) = 250 \quad -50t$$


We measure $i_b = -5e^{-50t} \text{ mA}$

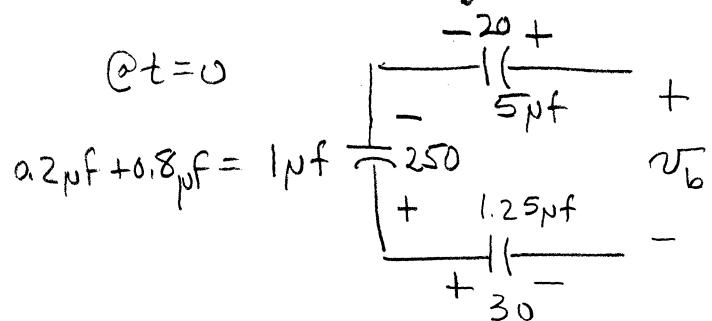

$$\text{at } t=0 \quad -30 + 250 - 20 + v_b(0) = 0$$

$$v_b(0) = -200 \text{ V}$$
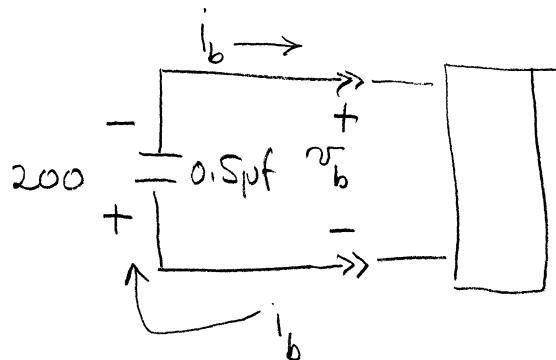
$$\frac{1}{C_{EQ}} = \frac{1}{1.25} + \frac{1}{1} + \frac{1}{5} = \frac{10}{5} \Rightarrow C_{EQ} = 0.5\text{ pF}$$



$$i_b = C_{EQ} \frac{d(-v_b)}{dt}$$

$$\int_0^t C_{EQ} i_b dt = \int_0^t dv_b$$


$$0.5 \times 10^{-6} \int_0^t -5 \times 10^{-3} e^{-50x} dx = -v_b(t) + v_b(0)$$

$$\frac{-5 \times 10^{-3}}{0.5 \times 10^{-6}} \int_0^t e^{-50x} dx = -v_b(t) + (-200) = v_b(t) - 200$$

$$-v_b(t) - 200 = -10^4 \left. \frac{e^{-50x}}{-50} \right|_0^t = \frac{-10^4}{-50} (e^{-50t} - 1) = 200 e^{-50t} - 200$$

$$v_b(t) = -200 e^{-50t}$$
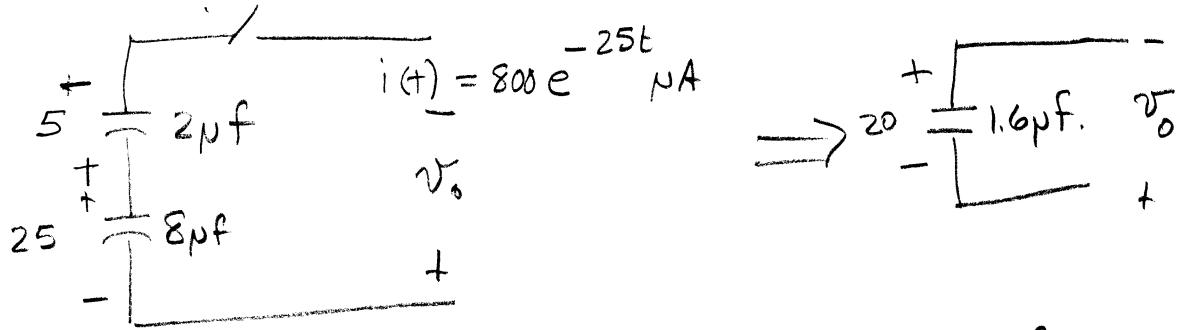
$$p = v_b(t) i_b(t) = (-5 e^{-50t} \times 10^{-3}) (-200 e^{-50t}) \\ = + e^{-100t} \text{ watts}$$



$$(a) \frac{1}{C_{EQ}} = \frac{1}{2} + \frac{1}{8} = \frac{4}{8} + \frac{1}{8} = \frac{5}{8} \quad C_{EQ} = \frac{8}{5} = 1.6 \mu F.$$

$$V_{EQ}(0) = 25 - 5 = 20$$

$$i = C \frac{dV_o}{dt}$$

$$-20 - V_o = 0$$

$$V_o = -20$$

$$\frac{1}{C} \int i(x) dx = dV_o$$

$$\frac{1}{C} \int_0^t i(x) dx = V_o(t) - V_o(0)$$


$$\frac{1}{1.6 \times 10^{-6}} \int_0^t 800 \times 10^{-6} e^{-25x} dx = V_o(t) - (-20)$$

$$\frac{800}{1.6} \left[\frac{e^{-25x}}{-25} \right]_0^t = V_o(t) + 20$$

$$\frac{500}{-25} (e^{-25t} - 1) = V_o(t) + 20$$

$$-20 e^{-25t} + 20 = V_o(t) + 20$$

$$V_o(t) = -20 e^{-25t}$$

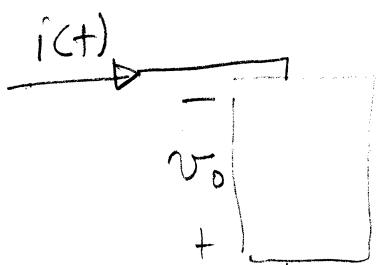

$$(b) V_1(t) = -16 e^{-25t} + 21$$

$$(c) V_2(t) = -4 e^{-25t} - 21$$

$$(d) P = -V_o i = 16 \times 10^{-3} e^{-50t} \text{ watts}$$



↑ passive sign convention

$$w = \int_0^\infty p(x)dx = 16 \times 10^3 \int_0^\infty e^{-50x} dx = 16 \times 10^3 \left[\frac{e^{-50x}}{-50} \right]_0^\infty = 320 \times 10^6 J.$$

$$(e) w(0) = \frac{1}{2} C v^2(0) + \frac{1}{2} C v^2(0) = 2525 J,$$

what is trapped energy?

Example 7-2

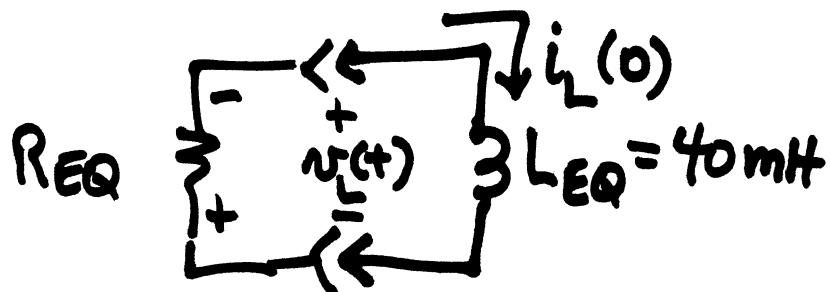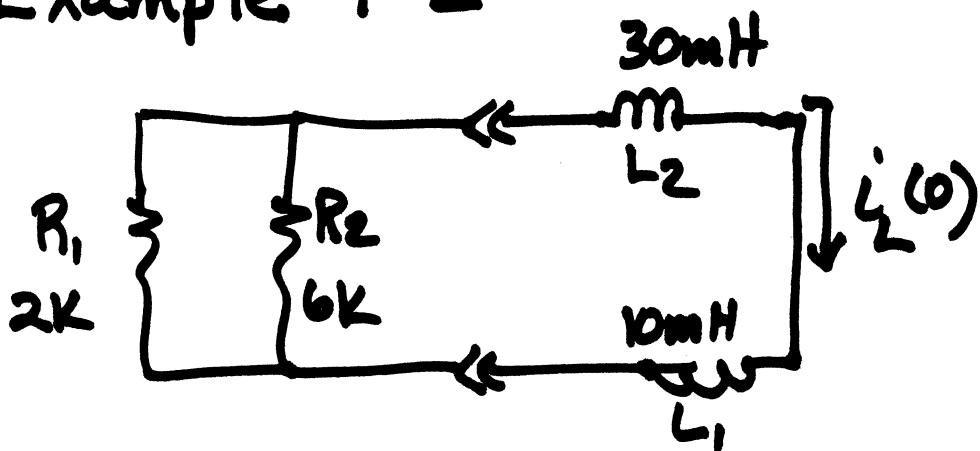

$$R_{EQ} = \frac{2 \cdot 6}{2+6} = \frac{3}{2} k \text{ or } 1500 \Omega$$

$$\frac{1}{R_{EQ}} = \frac{1}{2k} + \frac{1}{6k}$$

KVL gives

$$i_L R_{EQ} + v_L = 0$$

$$1500 i_L + L \frac{di_L}{dt} = 0$$

$$v_L = L \frac{di_L}{dt}$$

$$40 \times 10^{-3} \frac{di_L}{dt} + 1500 i_L = 0$$

let $i_L(t) = K e^{st}$

$$40 \times 10^{-3} s (K e^{st}) + 1500 K e^{st} = 0$$

$$40 \times 10^{-3} s + 1500 = 0$$

$$s = -37500$$

$$i_L(t) = K e^{-37500t} \quad t \geq 0$$

what is the time constant T_c ?

$$T_c = \frac{1}{37500} \quad -\frac{t}{26.7 \mu\text{sec}}$$


$$i_L(t) = K e^{-\frac{t}{26.7 \mu\text{sec}}}$$

To get K use $i_L(0) = 0.1$ Amps.


$$i_L(0) = K e^0 = 0.1 \text{ amps.}$$

$$K = 0.1$$
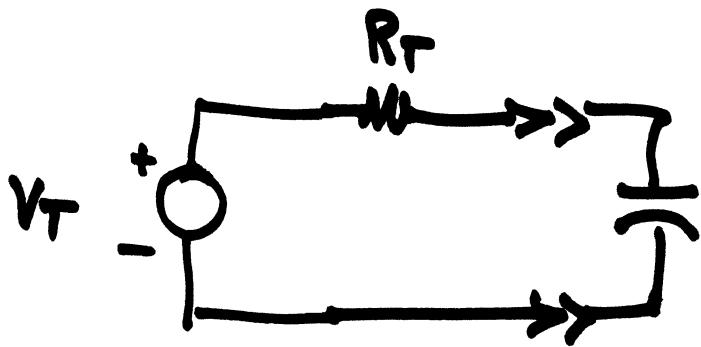
$$i_L(t) = 0.1 e^{-\frac{t}{26.7 \mu\text{sec}}} \quad t \geq 0$$



What do you do with an opamp circuit?

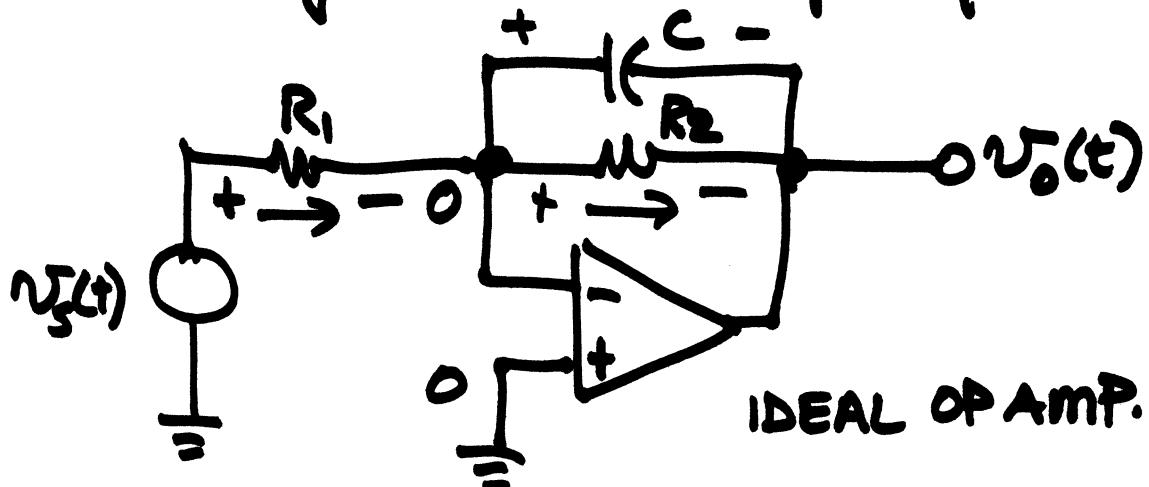

Don't Thevenize . $\sum_{+m} i = 0$

$$+\frac{v_s - 0}{R_1} - \frac{0 - v_o(t)}{R_2} - C \frac{d}{dt}(0 - v_o(t)) = 0$$

$$\underline{\frac{v_s}{R_1} + \frac{v_o}{R_2} + C \frac{d v_o}{dt}} = 0$$

$$R_2 C \frac{d v_o}{dt} + v_o = -\frac{R_2}{R_1} v_s$$

What is forced response?

$$V_T = A \sin(t)$$

$$R_C \frac{dv}{dt} + v = V_T(t) \quad A \quad t \geq 0$$


D.C. or steady state $\Rightarrow \frac{d}{dt} \rightarrow 0$

$$v = A$$


Total solution

$$v(t) = v_N(t) + v_F(t)$$

$$= Ke^{st} + A$$

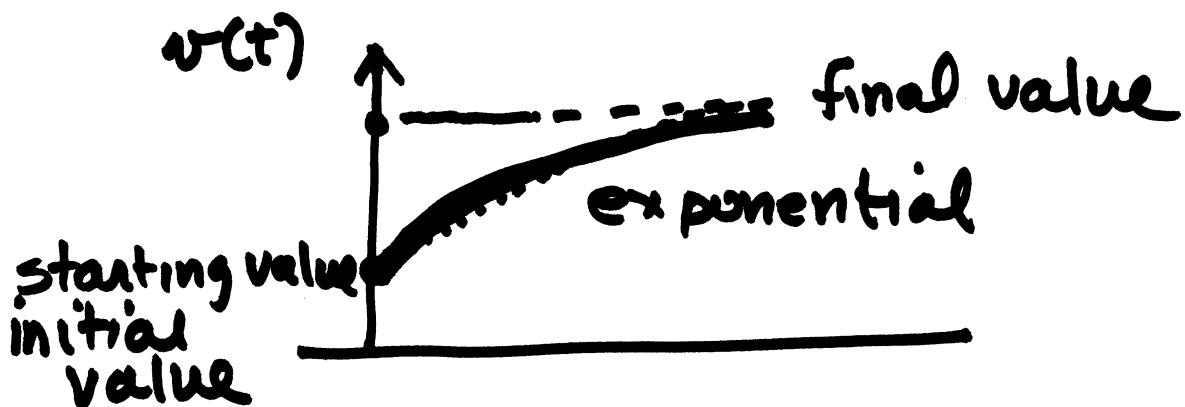

First order step response

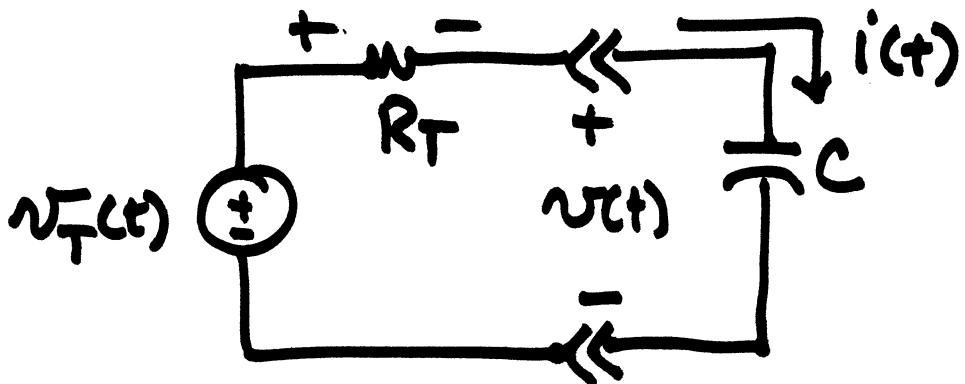

$$\text{KVL} \quad -\mathcal{U}_f(t) + i(t)R_T + \mathcal{U}(t) = 0$$

constraint for capacitor $i(t) = C \frac{d\mathcal{U}}{dt}$

$$-\mathcal{U}_f(t) + R_C C \frac{d\mathcal{U}}{dt} + \mathcal{U}(t) = 0$$

$$R_C C \frac{d\mathcal{U}}{dt} + \mathcal{U} = \mathcal{U}_f(t)$$

Two solutions

zero-input response

forced response

natural response

$$\mathcal{U}_N(t)$$

$$\mathcal{U}_F(t)$$

Superposition:

(DC or steady state)

$$\mathcal{U}(t) = \mathcal{U}_N(t) + \mathcal{U}_F(t)$$