

Two methods to solve transient problems:

1. writing a differential equation in the state variable


Capacitor — voltage

inductor — current

2. initial - final value theorem


for first order
(one reactive element)

Example 7-5

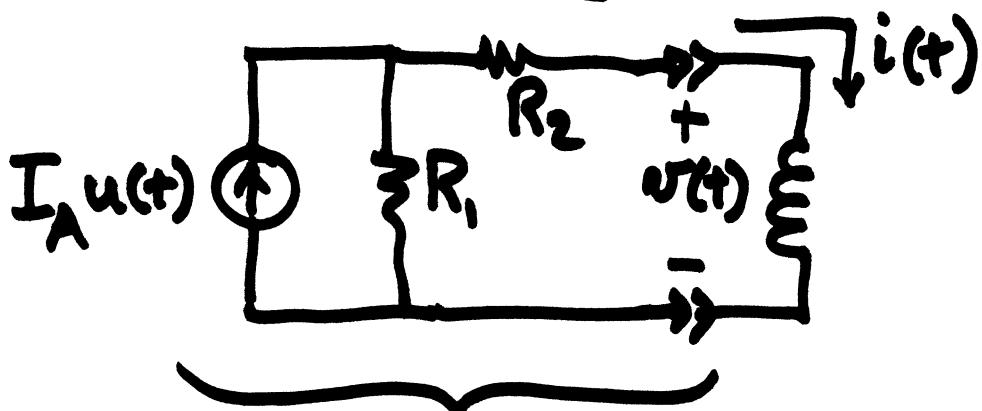

Nortonize



turn off
sources to
get R_N

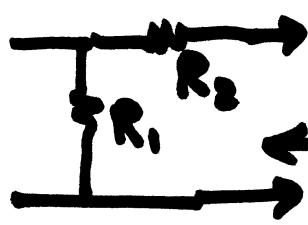


Step 1: simplify
source (left hand)
side

$$R_N = R_1 + R_2$$

short
circuit
 $t \geq 0$ I_A

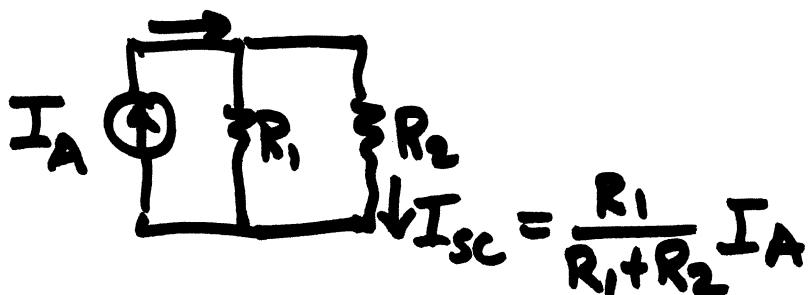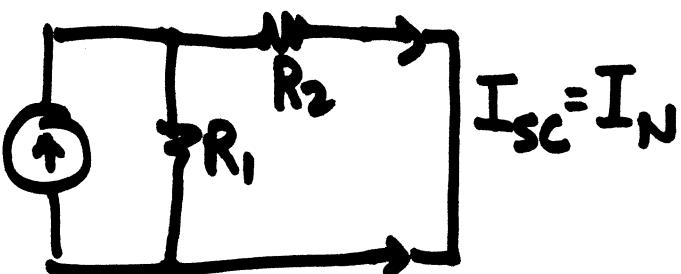

$$I_{sc} = \frac{R_1}{R_1 + R_2} I_A$$

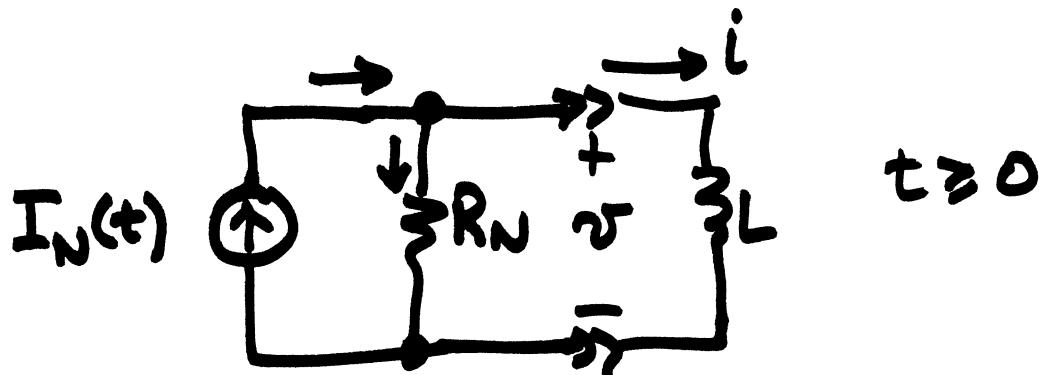

Step 2: find D.E. in the state variable

use KCL $\sum_{+in} i = 0$

$$+ I_N - \frac{v}{R_N} - i = 0$$

use constraint eqn.

$$v = L \frac{di}{dt}$$

$$I_N - \frac{L}{R_N} \frac{di}{dt} - i = 0$$

$$\frac{L}{R_N} \frac{di}{dt} + i = I_N$$

Step 3 solve the equation

$$i(t) = i_{\text{NATURAL}} + i_{\text{FORCED}} \\ \text{steady-state DC}$$

$$i_{\text{NATURAL}} \quad \frac{L}{R_N} \frac{di}{dt} + i = 0$$

$$i_N(t) = Ke^{-\frac{R_N}{L}t}$$

$$= Ke^{-\frac{t}{\tau_N}}$$

$$\text{let } i_N = Ke^{st}$$

$$\frac{L}{R_N} s Ke^{st} + Ke^{st} = 0$$

$$Ke^{st} \left(\frac{L}{R_N} s + 1 \right) = 0$$

require this to be zero

$$s = -\frac{R_N}{L}$$

$$i_{\text{Forced}} \quad \frac{d}{dt} \rightarrow 0 \quad \frac{L}{R_N dt} + i = I_N$$

$$\Rightarrow i_F = I_N$$

total solution

$$i(t) = i_N + i_F = Ke^{-\frac{t}{\tau_N}} + I_N$$

get K from initial condition

initial condition $i(0) = I_0$

$$i(0) = I_0 = Ke^0 + I_N = Ke^0 + \frac{R_1}{R_1 + R_2} I_A$$

$$\text{solve for } K = I_0 - \frac{R_1 I_A}{R_1 + R_2}$$

Example 7-6

State variable response of a first-order RC circuit is

$$V_c(t) = 20e^{-\frac{t}{200}} - 10 \quad t \geq 0$$

(a) What is the time constant?

$$e^{-\frac{t}{T_c}} \quad T_c = \frac{1}{200} = 5 \text{ msec.}$$

(b) What is the initial voltage across the capacitor?

$$V_c(0) = 20e^0 - 10 = 20 - 10 = +10 \text{ volts.}$$

(c) What is the amplitude of the forced response?

$$\lim_{t \rightarrow \infty} V_c(t) = -10$$

(d) At what time is $V_c(t) = 0$

$$0 = 20e^{-\frac{t}{200}} - 10$$

$$\ln \frac{10}{20} = -\frac{t}{200}$$

$$t = \frac{\ln(\frac{1}{2})}{-\frac{1}{200}} = 3.46 \text{ msec.}$$