

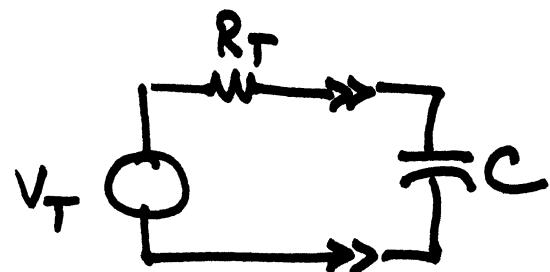


9.

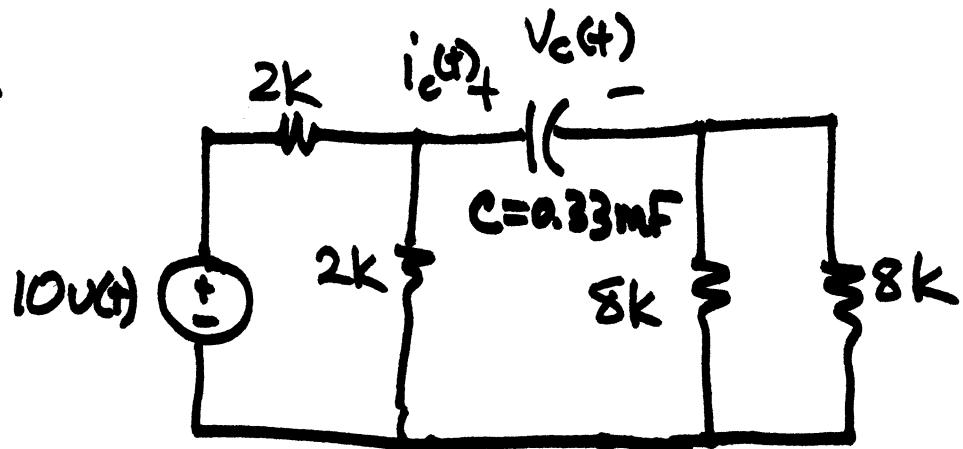


(a) What is state variable? $v_c(t)$



(b) Write the differential equation.

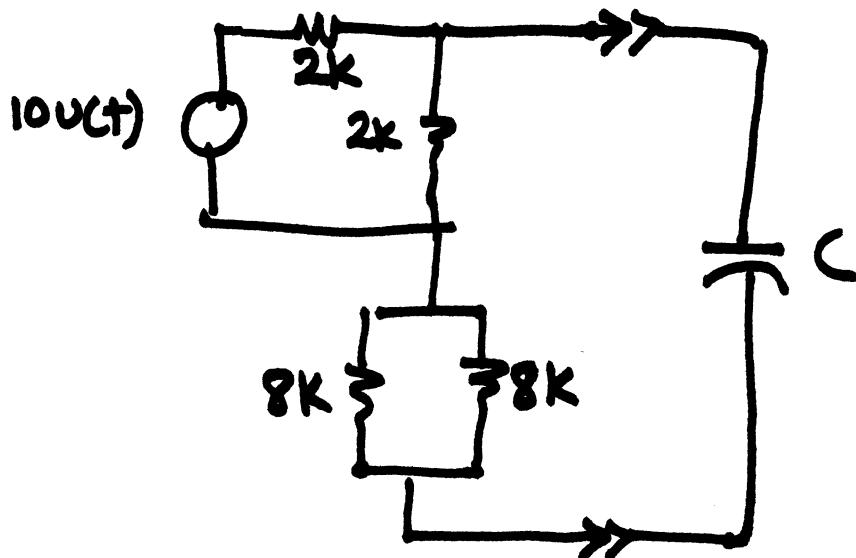

To find R_T turn off sources
 $t \geq 0$

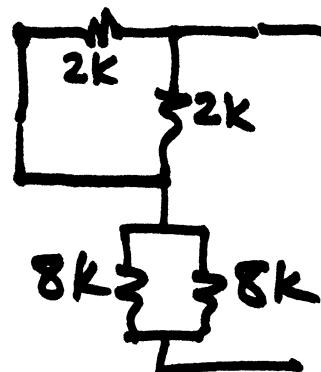

(2)

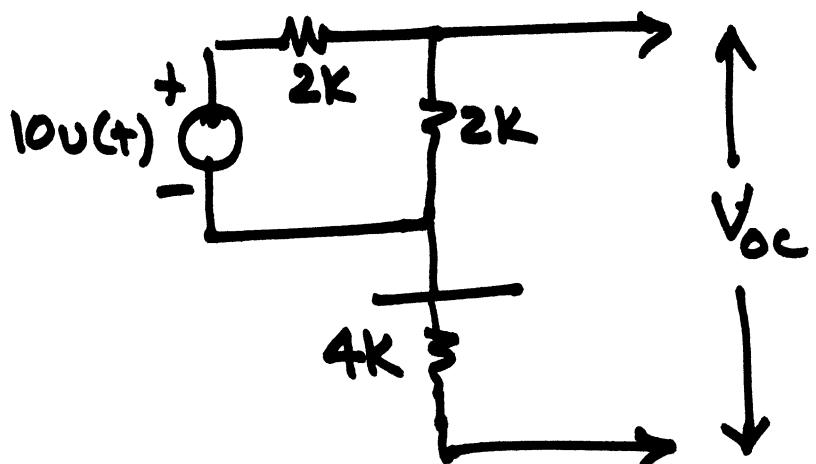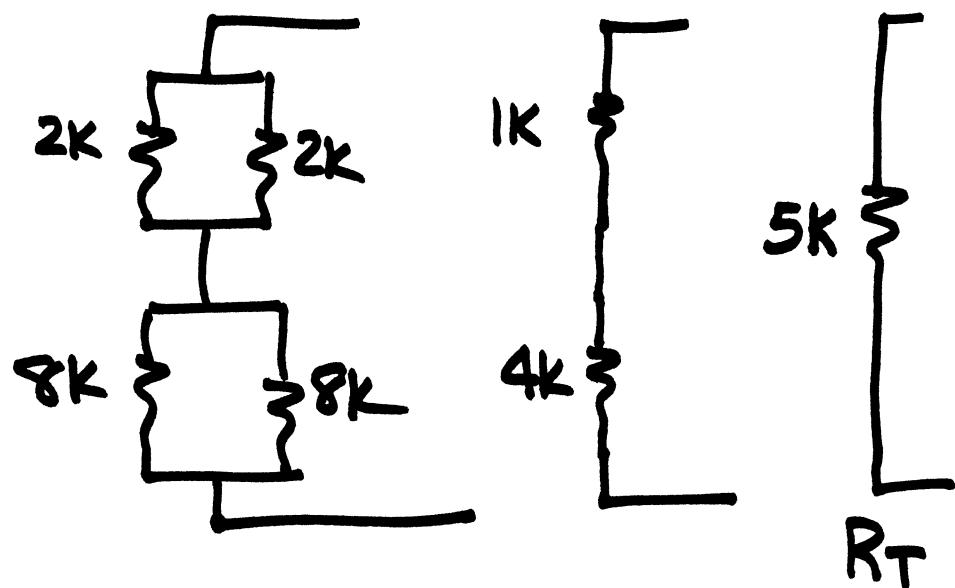


V_{oc} is the
voltage
across the
vertical 2k
resistor

voltage divider

$$t \geq 0$$
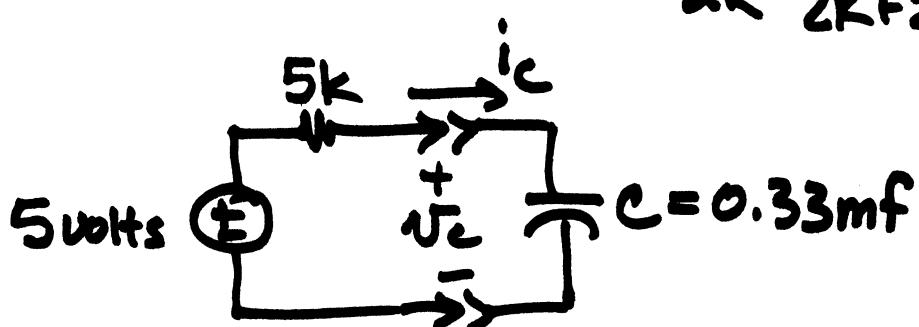
$$V_{2k} = \frac{2k}{2k+2k} 10 = 5 \text{ volts}$$



$$\text{KVL: } -5 + (5k) i_c + V_c = 0$$

$$\text{use } i_c = C \frac{dV_c}{dt}$$

$$-5 + (5k) C \frac{dV_c}{dt} + V_c = 0$$

$$(5k)c \frac{dV_c}{dt} + V_c = 5$$

(3)

^{DC}
forced
Steady-state $\frac{d}{dt} \neq 0$ $V_F(t) = 5$

natural. $(5k)c \frac{dV_c}{dt} + V_c = 0$

$$V_c(t) = ke^{st}$$

$$(5k)c s(ke^{st}) + (ke^{st}) = 0$$

$$(5k)c s + 1 = 0$$

$$s = -\frac{1}{(5k)c}$$


$$V_c(t) = V_F(t) + V_{NAT}(t)$$

$$V_c(t) = 5 + K e^{-\frac{t}{(5k)c}}$$

initial condition $V_c(t) = 0$

2.



/ 4

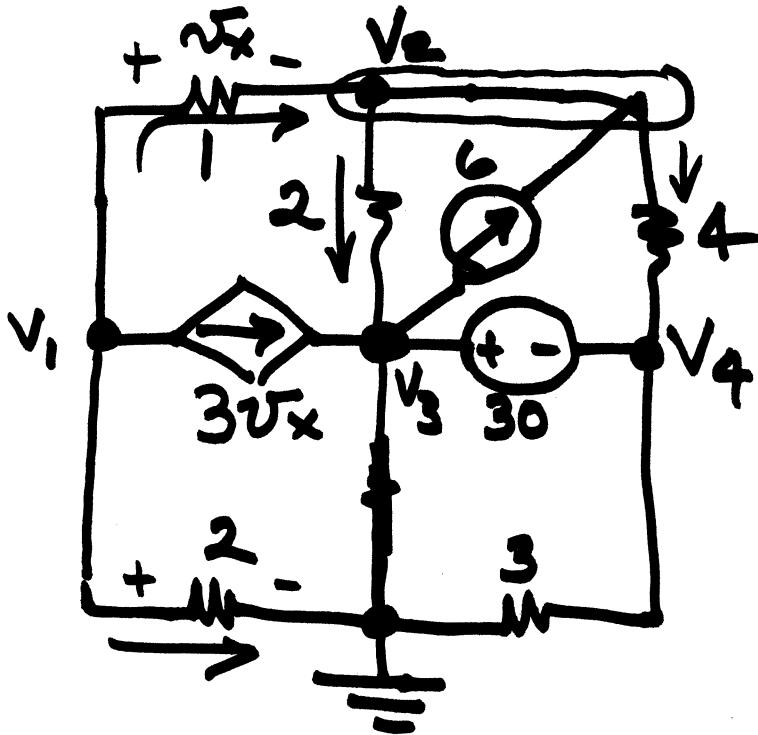

by inspection $V_3 = 0$

$$V_4 = V_3 - 30 = -30$$


node voltage technique (KCL)

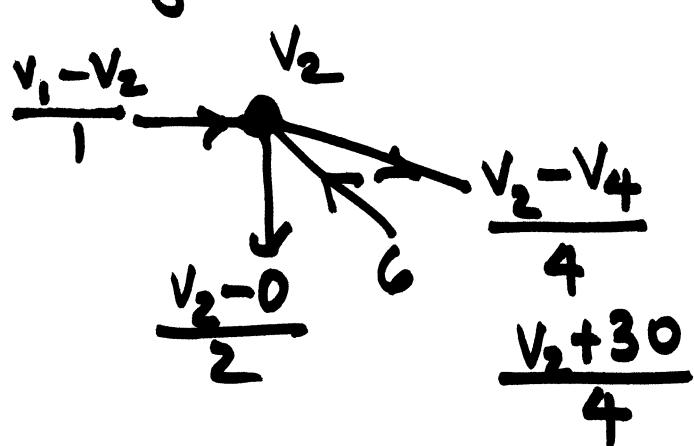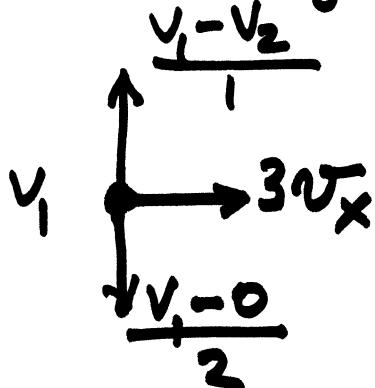

@1 $\frac{V_1 - V_2}{1} + 3V_x + \frac{V_1}{2} = 0$

@2 $\frac{V_1 - V_2}{1} + \frac{V_2}{2} - 6 + \frac{V_2 + 30}{4} = 0$ substitute
 $V_x = V_1 - V_2$

6.

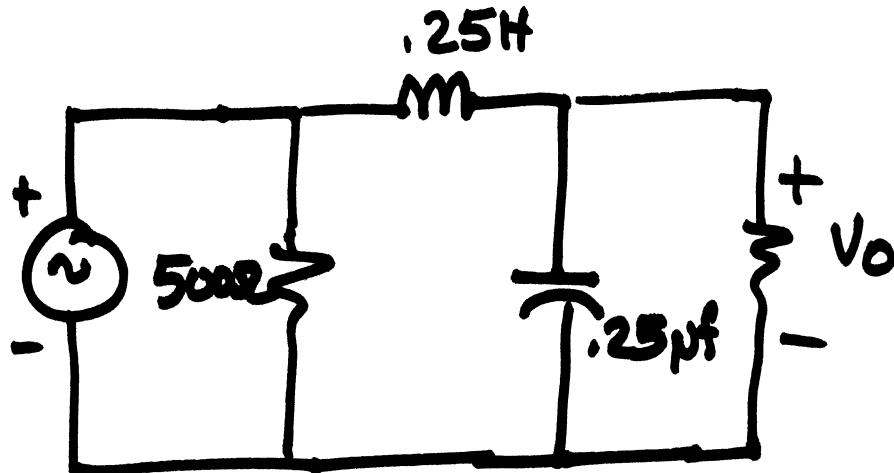

$$V_s = 1000 \cos(400t)$$

(a) What is the frequency in Hertz?

$$\omega = 400$$

$$\omega = 2\pi f$$

$$2\pi f = 400$$




$$f = \frac{400}{2\pi} = 63.6 \text{ Hz}$$

(b) What is the impedance of the C and L?

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j(400)(.25 \times 10^{-6})} = -j100$$

$$Z_L = j\omega L = j(400)(.25) = +j100$$

(c) for $R_L = 1000$ determine V_o

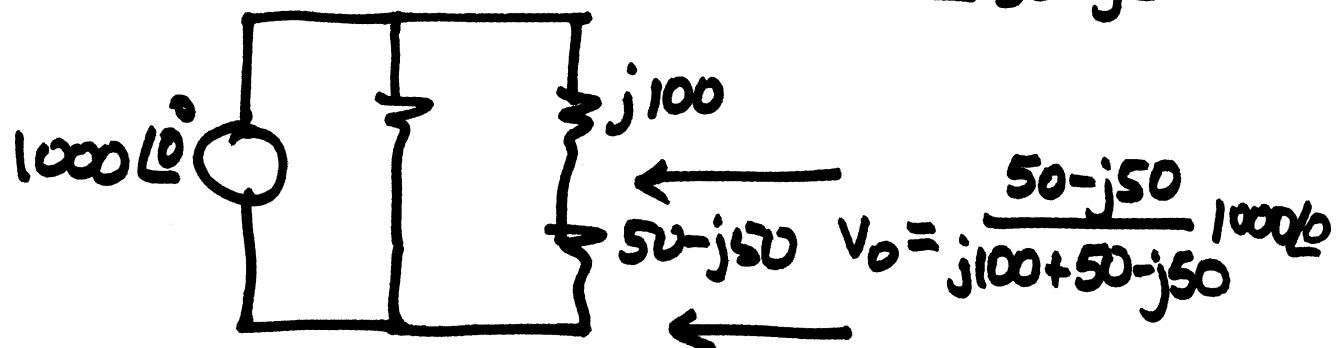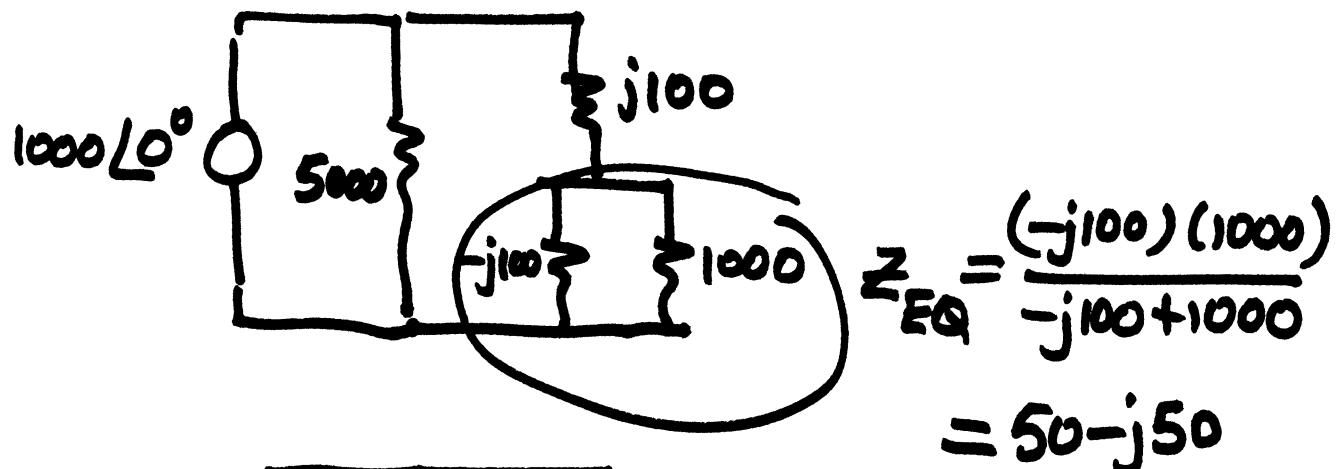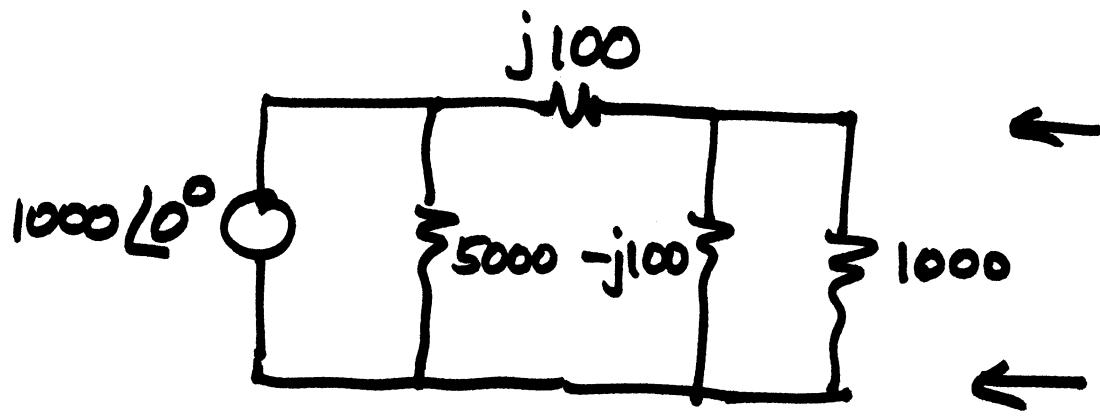

$$V_o = -j1000$$

$$= 1000 \angle -90^\circ$$

$$V_o = 1000 \cos(400t - 90^\circ)$$