

Department of Electrical Engineering and Computer Science  
**ENGR 210. Introduction to Circuits and Instruments (4)**

**Quiz No. 12****4/15/05**

**PUT ANSWERS IN THE SPACE PROVIDED AND, IF APPROPRIATE, SHOW YOUR WORK. BE SURE TO STATE ANY ASSUMPTIONS**

**Problem 1 Transfer functions (10 points)**

- (a) Determine the transfer function  $T_V(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$  of the following circuit. Be sure to put the denominator of your transfer function in standard form.

$$T_V(j\omega) = \underline{\hspace{10cm}}$$

- (b) What is the cutoff frequency  $\omega_c$  for this filter?  $\omega_c = \underline{\hspace{10cm}}$

- (c) What is  $T_V(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$  for  $\omega = 2\omega_c$ ?


$$T_V(j2\omega_c) = \underline{\hspace{10cm}}$$

- (d) If  $v_i(t) = 10 \cos(\omega t)$  write the steady state expression for  $v_o(t)$  when  $\omega = 2\omega_c$ .

$$v_o(t) = \underline{\hspace{10cm}}$$

- (e) What kind of filter is this? High-pass, low-pass, band-pass, band-reject, notch, something else?

Type = \_\_\_\_\_

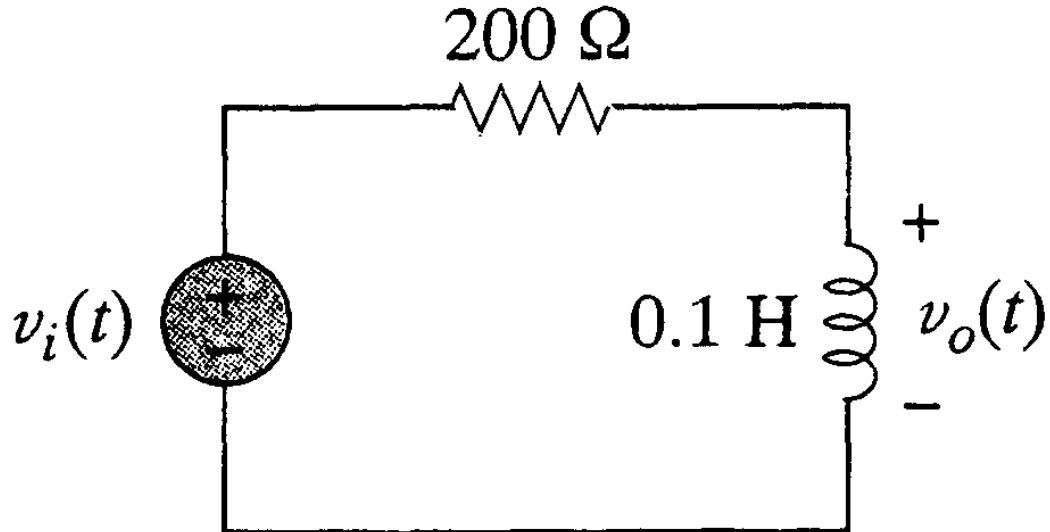

Name : \_\_\_\_\_ Section:\_\_\_\_\_ CWRU e-mail:\_\_\_\_\_

**Problem 2 Frequency dependent transfer functions (10 points)**


- (a) What is the cutoff frequency  $\omega_c$  for the filter described by

$$T_v(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{4}{2 + j\omega 10} \quad \omega_c = \text{_____}$$

- (b) Using the chart below plot the frequency dependence of this filter. Be sure to label your axes.

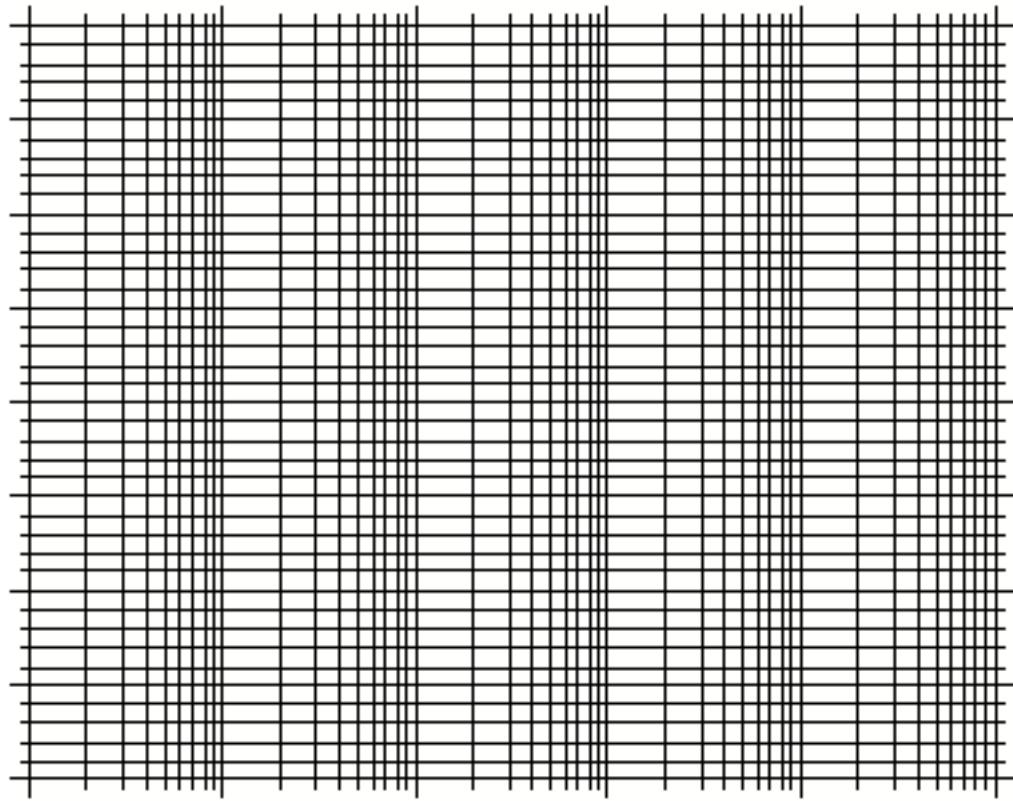- (c) What is the passband gain of this filter in decibels.

$$\text{Passband gain} = \text{_____ dB}$$



$\omega$