

2-12

$$i_1 = 20 \text{ mA}$$


$$i_3 = -30 \text{ mA}$$

$$\text{KCL at A: } \sum_{\text{in}} i = 0$$

$$-i_1 - i_2 - i_3 = 0$$

$$i_2 = -(i_1 + i_3)$$

$$i_2 = 10 \text{ mA}$$

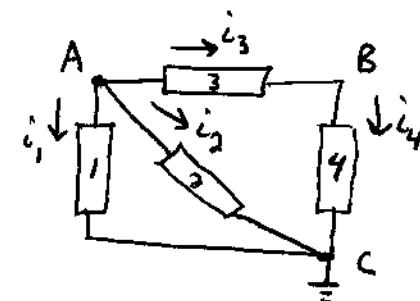

$$\text{KCL at B: } \sum_{\text{in}} i = 0 = i_3 - i_4 = 0$$

$$i_3 = i_4$$

$$i_4 = -30 \text{ mA}$$

$$\text{Check answer with KCL at C: } \sum_{\text{in}} i = 0 = i_1 + i_2 + i_3 = 20 \text{ mA} + 10 \text{ mA} - 30 \text{ mA} = 0$$

2-13

a) Nodes: A, B, C, D

Loops: (1,2,3), (2,4,5),
 (3,4,6), (1,5,6), (2,3,6,5)
 and others possible

b) series: [None] parallel [None]


$$\text{c) KCL at A: } -i_1 - i_3 - i_4 = 0$$

$$\text{at B: } -i_1 + i_3 - i_6 = 0$$

$$\text{at C: } i_1 + i_2 + i_5 = 0$$

$$\text{at D: } i_4 + i_6 - i_5 = 0$$
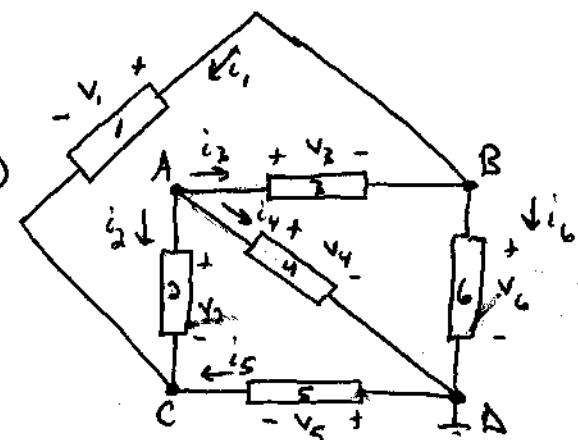
$$\text{d) } v_3 = -8 \text{ V} \quad v_4 = -8 \text{ V} \quad v_5 = 9 \text{ V}$$



$$\text{KVL loop (1,2,3): } -v_1 - v_3 + v_2 = 0$$

$$\text{loop (2,4,5): } -v_2 + v_4 + v_5 = 0$$

$$\text{loop (3,6,4)} \quad v_3 + v_6 - v_4 = 0$$


$$v_2 = +v_4 + v_5 = +8 + 9 = +17 \text{ V}$$

$$v_6 = v_4 - v_3 = -8 - (-8) = 0 \text{ V}$$

$$v_1 = -v_3 + v_2 = +8 + 17 = +25 \text{ V}$$

2-21

$$V_x = 5 i_x$$

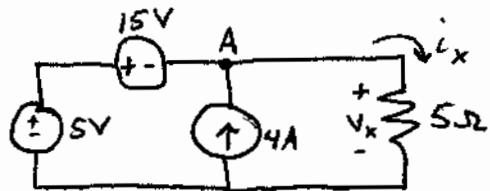KVL around outside: $-5 + 15 + V_x = 0$

$$V_x = -10V$$

~~check by KCL~~

$$i_x = -2A$$

2-22

KVL around bottom Left loop:

$$-5V + V_2 + 10V = 0$$

$$V_2 = -5V$$

KVL around bottom right loop

$$-10V + V_3 + 5V = 0$$


$$V_3 = 5V$$

KVL around outside loop

$$-5V + V_1 + 5V = 0$$

$$V_1 = 0V$$

$$\begin{aligned} i_1 &= \frac{V_1}{50} = 0A \\ i_2 &= \frac{V_2}{100} = -50mA \\ i_3 &= \frac{V_3}{100} = 50mA \end{aligned}$$

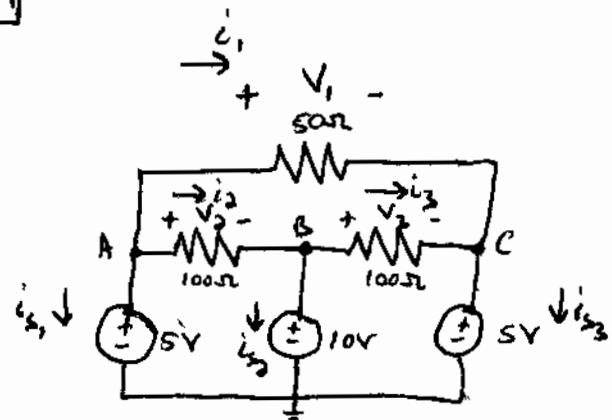KCL @ A $-i_1 - i_2 - i_{s1} = 0$

$$i_{s1} = -i_1 - i_2 = 50mA$$

KCL @ B $i_2 - i_{s2} - i_3 = 0$

$$i_{s2} = i_2 - i_3 = -100mA$$

KCL @ C $i_1 + i_3 - i_{s3} = 0$

$$i_{s3} = i_3 = 50mA$$

* Signs (+ or -) for V_2, V_3, i_2 and i_3 could be different if voltages and currents for resistors were defined differently.

2-24

a) KCL @ A:

$$i_1 - 10\text{mA} + 5\text{mA} - i_x = 0$$

$$i_x = i_1 - 5\text{mA}$$

$$V_1 = i_1 R_1$$

$$8\text{V} = i_1 (2\text{k}\Omega)$$

$$i_1 = 4\text{mA}$$

$$i_x = -1\text{mA}$$

$$V_x = i_x R_x = (-1\text{mA}) (10\text{k}\Omega)$$

$$V_x = -10\text{V}$$

b) $10\text{mA} - 5\text{mA} - i_1 + i_x = 0$ KCL using "rest of ckt" as a node

$$10\text{mA} - 5\text{mA} - 4\text{mA} - 1\text{mA} = 0 \quad \checkmark$$

