
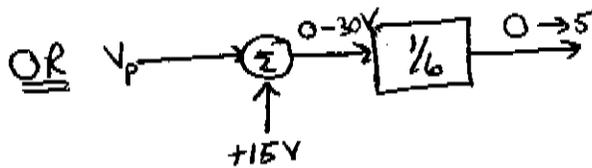
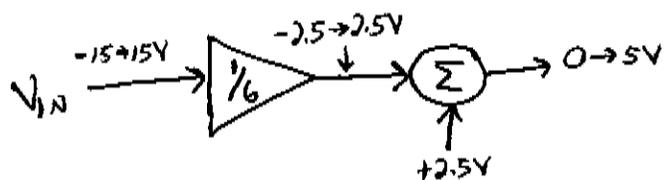


#1 Leg position sensor for Biosabat

$V_o$  needs to be  $0 \rightarrow 5V$


$V_{in} = V_p = (-15 \rightarrow 15)V$

We need to scale as well as shift.

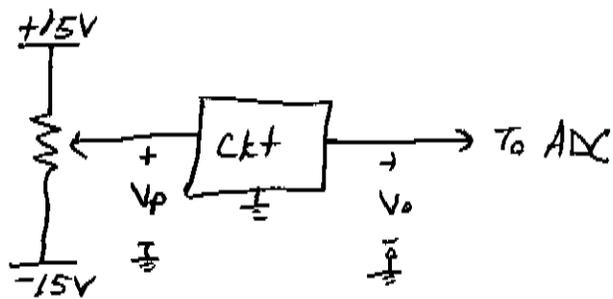

Either design (as well as others) will work.

Let's use a Subtractor circuit.

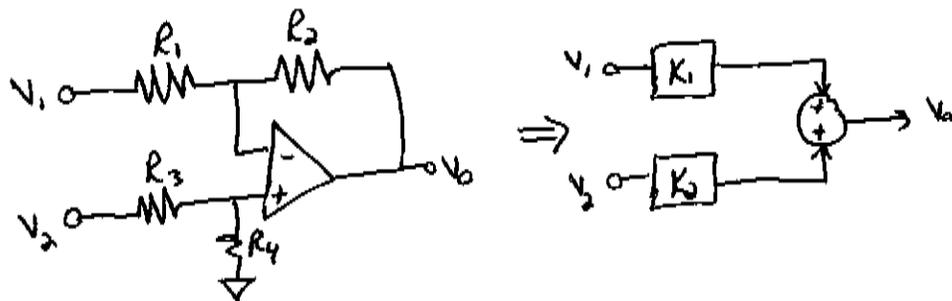


$$K_1 = -\frac{R_2}{R_1}$$


$$K_2 = \left(\frac{R_1+R_2}{R_1}\right) \left(\frac{R_4}{R_3+R_4}\right)$$

Since  $K_2$  doesn't invert input let's put  $V_p$  on this node.

Choose  $|K_1| = |K_2| = 1/6$  for ease

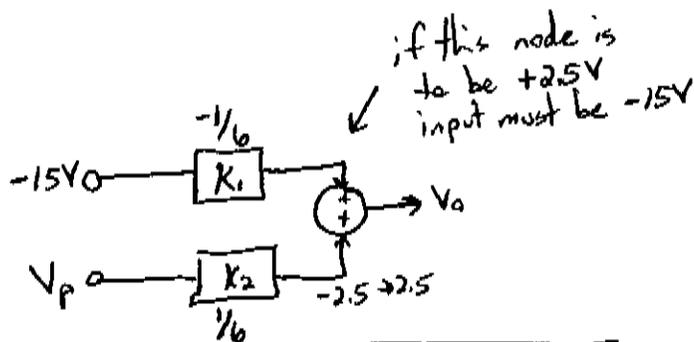
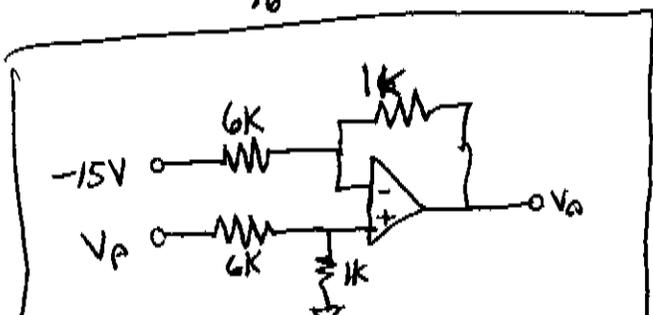
$$\frac{R_2}{R_1} = \frac{1}{6} \quad \frac{R_4}{R_3} = \frac{1}{6}$$



## #2 Temperature Sensor

$$k = 1 \mu\text{A} / \text{K}$$

$$V_{cc} = 10\text{V}$$

$$\frac{dV_o}{dT} = 100 \text{mV} / \text{C}$$

KCL @ x

$$\frac{V_{cc} - 0}{R_1} + \frac{V_b - 0}{R_2} = kT_A$$

$$V_o = R_2 \left[ kT_A - \frac{V_{cc}}{R_1} \right]$$

$$\text{sensitivity} = \frac{dV_o}{dT} = R_2 k = 100 \frac{\text{mV}}{\text{C}}$$

$$R_2 = \frac{100 \text{mV} / \text{K}}{1 \mu\text{A} / \text{K}} = \underline{\underline{100 \text{k}\Omega}}$$

We also want  $V_o$  to be proportional to  $^{\circ}\text{C}$  (not K) so we need to have an offset.


We want  $V_o = 0$  if  $T_A = 273$

$$0 = R_2 k T_A - \frac{R_2}{R_1} V_{cc} = (100 \text{k}) \left( 1 \frac{\mu\text{A}}{\text{K}} \right) (273 \text{K}) - \frac{100 \text{k}}{R_1} (10)$$

$$R_1 = \frac{(100 \text{k})(10)}{(100 \text{k}) \left( 1 \frac{\mu\text{A}}{\text{K}} \right) (273 \text{K})}$$

$$R_1 = 36.6 \text{k}\Omega$$

$$R_2 = 100 \text{k}\Omega$$

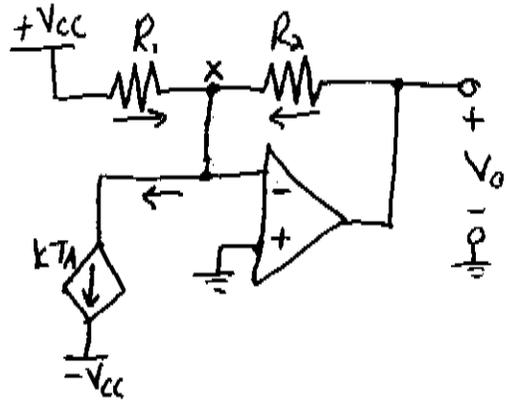

## #3

$$V = 5 \quad t = 5 \text{ms}$$

$$V = 3.5 \quad t = 7 \text{ms}$$

a)

$$\textcircled{1} \quad 5 = V_A e^{-5 \text{ms} / \tau}$$

$$\textcircled{2} \quad 3.5 = V_A e^{-7 \text{ms} / \tau}$$

$$\frac{\textcircled{1}}{\textcircled{2}} = \frac{5}{3.5} = e^{2 \text{ms} / \tau}$$

$$\ln(5/3.5) = \frac{2 \text{ms}}{\tau}$$

$$\tau = \frac{2 \text{ms}}{\ln(5/3.5)}$$

$$\tau = 5.16 \text{ms}$$

Plug into eqn  $\textcircled{1}$  or  $\textcircled{2}$  to

find  $V_A$ .

$$5 = V_A e^{-5 \text{ms} / 5.16 \text{ms}}$$

$$V_A = 12.2 \text{V}$$

← General Exponential Waveform.


Plug values into general eqn. and solve.

$$\text{b) } V = 12.2 e^{-2 \text{ms} / 5.16 \text{ms}}$$

$$V = 8.54 \text{V}$$
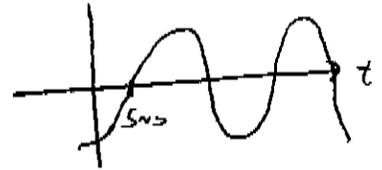
#4

$v(t) = A \cos(2\pi f(t - T_s))$  ← General form of a cosine.



$f = 100\text{kHz}$

$A = 75\text{V}$

$v(t) = 75 \cos(2\pi(100k)(t - T_s))$

$\cos(a \pm b) = \cos a \cos b \mp \sin a \sin b$

$v(t) = 75 [\cos(2\pi 100k t) \cos(2\pi 100k(-T_s)) - \sin(2\pi 100k t) \sin(2\pi 100k(-T_s))]$

$v(t) = a \cos(2\pi f t) + b \sin(2\pi f t)$

Fourier Coefficients


$\begin{cases} a = 75 \cos(2\pi 100k(-T_s)) \\ b = -75 \sin(2\pi 100k(-T_s)) \end{cases}$

What is  $T_s$ ?

$T = \frac{1}{f} = \frac{1}{100k} = 10\mu\text{s}$

$T_s = -2.5\mu\text{s}$

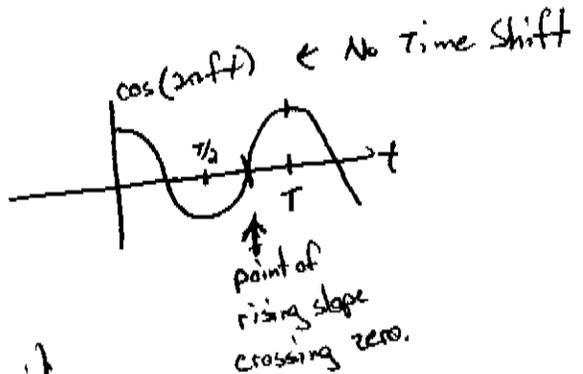if waveform is shifted left by  $2.5\mu\text{s}$  then the zero crossing with positive slope would be at  $5\mu\text{s}$ .



$\begin{cases} a = 75 \cos(\pi/2) = 0 \\ b = -75 (\sin(\pi/2)) = -75 \end{cases}$

What about phase angle?

$v(t) = A \cos(2\pi f t + \phi)$  Another way to write general cosine eqn.

$\phi = -2\pi f T_s = -2\pi(100k)(-2.5\mu\text{s})$

$\phi = \pi/2$

All of the above assumed we were dealing with a cosine wave. Using a sine wave would affect  $T_s$  and  $\phi$  but will not affect the Fourier coefficients.



shift by  $+\frac{\pi}{2}$

For Sin wave

$\begin{cases} \phi = \pi \\ T_s = 5\mu\text{s} \text{ or } -5\mu\text{s} \end{cases}$

#5  
 $V_{cc} = \pm 15V$

$$v(t) = V_0 + 10 \cos(2000\pi t)$$

$$|V_{out}|_{\max} = 15V$$


$$|v(t)| = |V_0| + |10 \cos(2000\pi t)|$$

$$|v(t)| = V_0 + 10$$

$$V_{0_{\max}} = +5 \rightarrow V_{out} = +5$$

$$V_{0_{\min}} = -25 \rightarrow V_{out} = -15$$

$$-5 \leq V_0 \leq +5$$

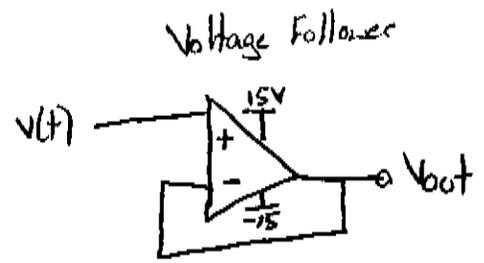

Buffer  $V_{out} = v(t)$