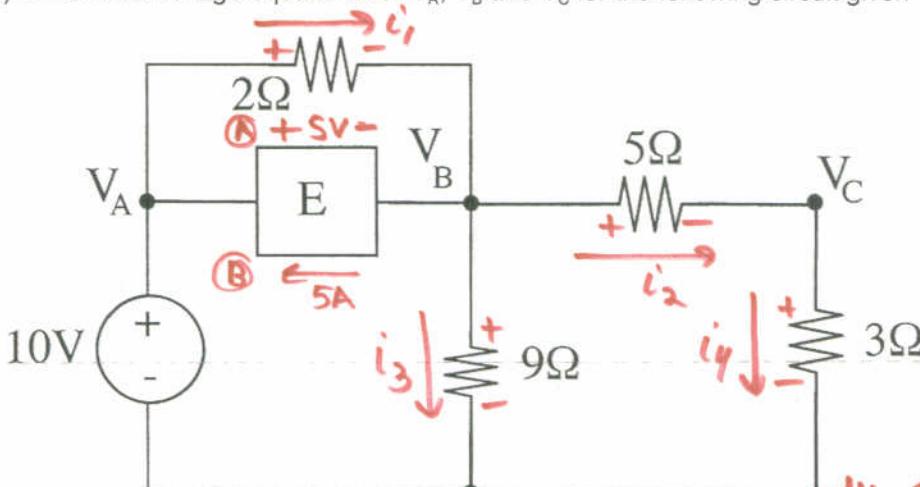


Quiz No. 4

2/11/05

PUT ANSWERS IN THE SPACE PROVIDED AND SHOW YOUR WORK IF APPROPRIATE  
STATE ALL ASSUMPTIONSNODE VOLTAGE ANALYSIS

1. (10 points) Write node voltage equations for
- $V_A$
- ,
- $V_B$
- and
- $V_C$
- for the following circuit given that



- (a) E is a 5 volt voltage source with the plus reference on the left.

NODE	Node Voltage Equations		
A	1	$V_A + 0 V_B + 0 V_C = 10V$	(2) -1 for answer
B	0	$V_A + 1 V_B + 0 V_C = 5V$	(1) -1 for answer
C	0	$V_A + -\frac{1}{5}\Omega V_B + \frac{8}{15}\Omega V_C = 0$	(2) -1 for answer

$\checkmark$   $V_A - V_B = 5V$  also accepted

mode A  $\checkmark$   $V_A - 0 = 10V \quad V_A = 10V$

mode B  $\checkmark$   $V_A - V_B = 5V \rightarrow 10V - V_B = 5V \quad V_B = 5V$

mode C  $\checkmark$   $-i_2 + i_4 = 0 \quad -\frac{V_B - V_C}{5\Omega} + \frac{V_C - 0}{3\Omega} = 0 \quad -\frac{V_B}{5} + \frac{V_C}{5} + \frac{V_C}{3} = 0$

- (b) E is a 5 ampere current source with the reference arrow pointing left.

NODE	Node Voltage Equations		
A	1	$V_A + 0 V_B + 0 V_C = 10V$	(1) -1 for answer
B	$-\frac{1}{2}\Omega$	$V_A + \frac{73}{90}\Omega V_B + -\frac{1}{5}\Omega V_C = -5A$	(2) -1 for answer
C	0	$V_A + -\frac{1}{5}\Omega V_B + \frac{8}{15}\Omega V_C = 0$	(2) -1 for answer


mode A  $\checkmark$   $V_A - 0 = 10V \quad V_A = 10V$

mode B  $\checkmark$   $-i_1 + 5A + i_3 + i_2 = 0 \quad -\frac{V_A - V_B}{2\Omega} + 5A + \frac{V_B - 0}{9\Omega} + \frac{V_B - V_C}{5\Omega} = 0$   
 $-\frac{1}{2}V_A + \frac{73}{90}V_B - \frac{1}{5}V_C = -5A$

mode C  $\checkmark$   $-i_2 + i_4 = 0 \quad -\frac{V_B - V_C}{5\Omega} + \frac{V_C - 0}{3\Omega} = 0 \quad -\frac{1}{5}V_B + \frac{8}{15}V_C = 0$

MESH CURRENT ANALYSIS

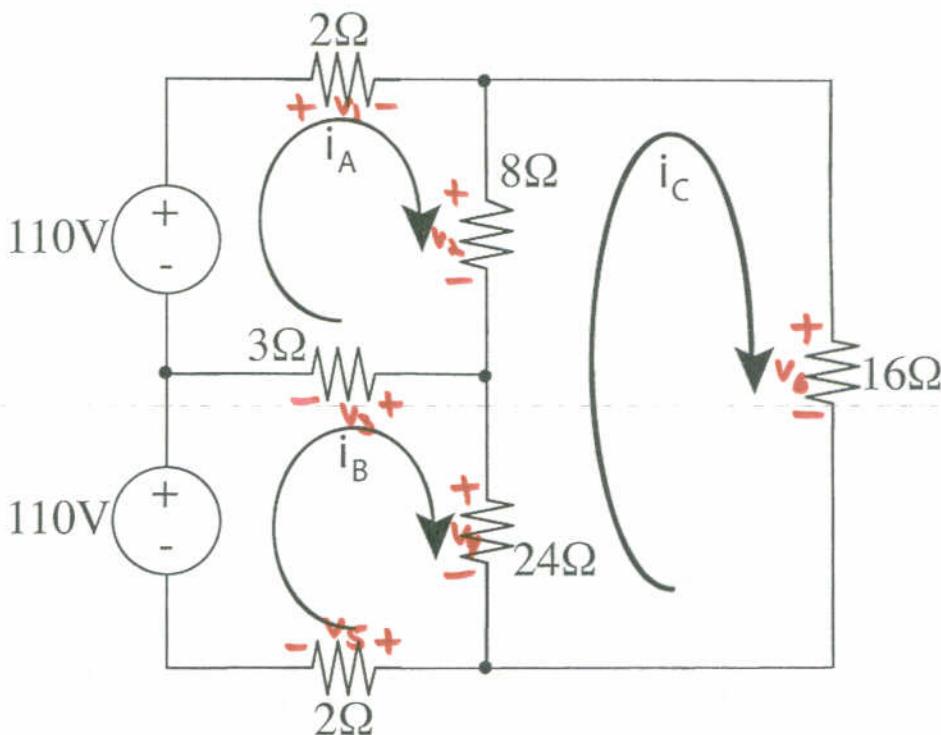2. (10 points) The circuit shown below is a DC model of a residential power distribution circuit. Use the mesh current method to write equations for the indicated currents.



MESH	Mesh Current Equations
A	$13\text{A} - 3\text{B} - 8\text{C} = 110\text{V}$
B	$-3\text{A} + 29\text{B} - 24\text{C} = 110\text{V}$
C	$-8\text{A} - 24\text{B} + 48\text{C} = 0$

- ③ -1 for answer
- ③ -1 for any right zero
- ③ -1 for right equation
- ③ - same as above
- ③ - same as above

$$-110\text{V} + v_1 + v_2 + v_3 = 0$$

$$-110\text{V} - v_3 + v_4 + v_5 = 0$$

$$-v_4 - v_2 + v_6 = 0$$

$$-110\text{V} + 2i_A + 8(i_A - i_C) + 3(i_A - i_B) = 0$$

$$-110\text{V} - 3(i_A - i_B) + 24(i_B - i_C) + 2i_B = 0$$

$$-24(i_B - i_C) - 8(i_A - i_C) + 16i_C = 0$$

$$v_1 = (2\Omega)i_A$$

$$v_2 = (8\Omega)(i_A - i_C)$$

$$v_3 = (3\Omega)(i_A - i_B)$$

$$v_4 = (24\Omega)(i_B - i_C)$$

$$v_5 = (2\Omega)i_B$$

$$v_6 = (16\Omega)i_C$$

① — general  
necessity;  
strategy

$13i_A - 3i_B - 8i_C = 110\text{V}$ $-3i_A + 29i_B - 24i_C = 110\text{V}$ $-8i_A - 24i_B + 48i_C = 0$
---