

FET CHARACTERISTICS, AMPLIFIERS, AND APPLICATIONS

READING ASSIGNMENT: Horowitz, pgs.223-231, 232-234, 240-241.

Abstract:

In this lab you will compare methods for measuring the dc characteristics of an N-channel JFET. The performance of a FET current source will be examined. The common source and common drain amplifiers will be studied.

Part 1 - DC Characterization

In this part, you will use determine your transistor's  $I_{DSS}$  and  $V_P$  by using the curve tracer and by direct measurement. You can use the curve tracer any time during your lab period, so don't waste time standing in line.

- (1) Set the curve tracer to the default drain characteristic settings listed in <sup>Table</sup> Figure 1.

CONTROL	DEFAULT SETTING	DESCRIPTION
13	*	- set so display starts at point labeled 9
12	2 mA	$I_D$ - drain current per vertical cm.
15	2 collector	$V_{DS}$ - drain voltage per horiz. cm.
20	in	gate voltage polarity inverted
17	0.5 V	$V_{GS}$ - gate voltage increment per step
all others	NPN default positions	

<sup>Table</sup> Figure 1 Curve tracer settings for characterizing FETs

- (2) Test the reference transistor to make sure you have the settings right.  
 (3) Display your transistor's drain characteristics and adjust the controls as needed to get a nice display. ACCURATELY record the characteristics in Table 11.1. Pay particular attention to the slopes of the curves in the resistive and saturation regions.  
 (4) Set the curve tracer to the default transfer characteristic settings listed in <sup>Table</sup> Figure 2.

CONTROL	DEFAULT SETTING	DESCRIPTION
13	*	- set so display starts at point labeled 9
12	2 mA	$I_D$ - drain current per vertical cm.
15	steo gen	$V_{DS}$ - drain voltage per horiz. cm.
20	in	gate voltage polarity inverted
17	0.5 V	$V_{GS}$ - gate voltage increment per step
all others	NPN default positions	

<sup>Table</sup> Figure 2 Curve tracer settings for measuring the transfer characteristics of FETs

- (5) Test the reference transistor to make sure you have the settings right.

SAVE A XEROX OF YOUR DATA FOR LAB #12

- (6) Display your transistor's transfer characteristics and adjust the controls as needed to get a nice display. ACCURATELY record the characteristics in Table 11.2. The curve will be a set of points rather than a continuous curve. Pay particular attention to the horizontal ( $V_P$ ) and vertical ( $I_{DSS}$ ) axis intercepts. } do.

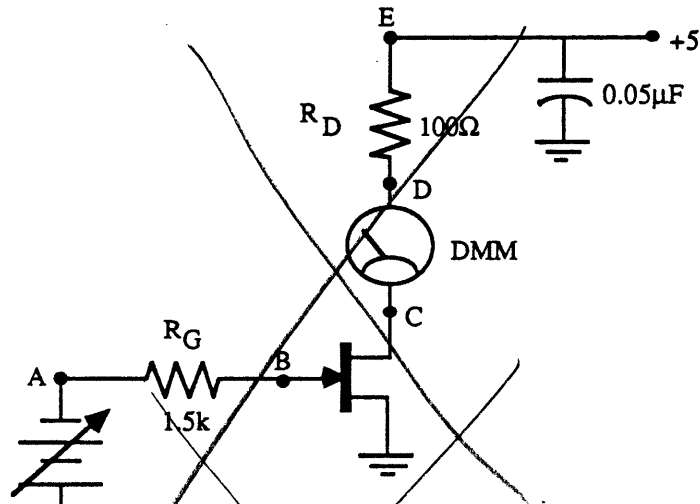


Figure 1 - Circuit for characterizing FETs

- (7) Build the circuit shown in Fig.1.  
 (8) Adjust the variable supply so that the DMM reads approximately  $1\ \mu\text{A}$ .  
 (9) Remove the DMM and use it to measure  $V_{GS}$ , which is very nearly  $V_P$ . Record your results in Table 11.3  
 (10) Put back the ammeter (DMM), remove the variable supply, and ground point A.  
 (11) Record  $I_D$ , which is  $I_{DSS}$ . The current may slowly decrease due to heating of the transistor, so take your reading quickly. Record your results in Table 11.3.

FETs are commonly used as current sources for circuits found on IC's. Consider the FET current source shown in Figure 2.

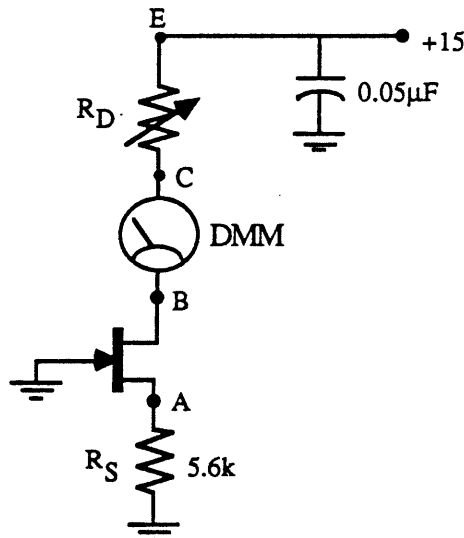


Figure 2A FET current source

- (1) Build the circuit of Figure 2. Use your  $R_S$  for  $R_D$ .
- (2) Measure  $I_D$  for  $R_D$  values of 10k, 20k, 30k, 40k and 50k. Record your measurements in Table 11.4.
- (3) The constant current should break down when  $V_{DS}$  is near  $-V_P$ . Take additional data near this breakdown point. Record your data in Table 11.4.

## Part 2 - AC Characteristics

*Start here*

The value of  $g_m$  for the FET is much more variable than  $\beta_o$  was for the BJT. The gain of an FET amplifier is very dependent on its operating point. Follow these steps to characterize the AC operation of your transistor. You should notice if the CH2 waveform ever becomes distorted.

- (1) Build the circuit shown in Fig. 2. Connect scope CH1 to point A and CH2 to point C. Adjust the generator to produce a 100 mV<sub>p-p</sub> 1 kHz triangle wave at point A.
- (2) Adjust the generator's DC offset so that point A is at approximately +1.0 V DC.
- (3) Use the scope to measure the AC<sub>p-p</sub> voltage at point C. Record your data in Table 11.5.
- (4) Repeat steps 2 and 3 using +0.5 V, 0.0 V, -0.5 V, -1.0 V, -1.5 V, etc. in step 2 until you reach your transistor's  $V_P$ .
- (5) Set the generator's DC offset so that point A is at +1.0 V DC. Use the DMM to measure the DC voltage at point B. Record your result in Table 11.5.

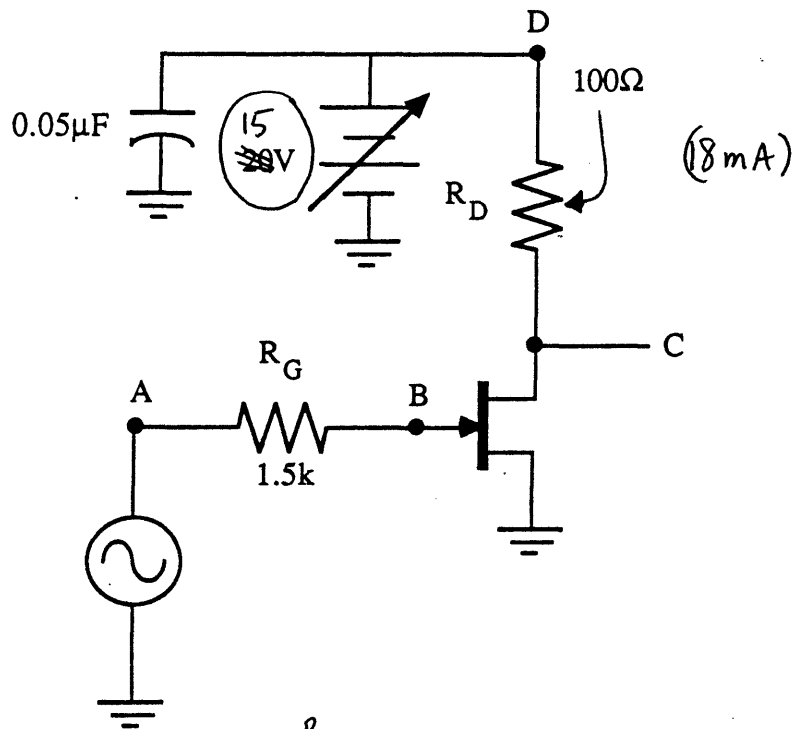


Figure 2<sup>b</sup> FET amplifier

The FET can be used in the common gate, common source mode, or common drain just as a BJT can operate in the common base, common emitter or common collector modes. The common source amplifier configuration of Figure 2 is usually used for voltage amplifiers; however, when impedance matching or high output power is a consideration the source follower (also called the common drain) configuration is usually employed.

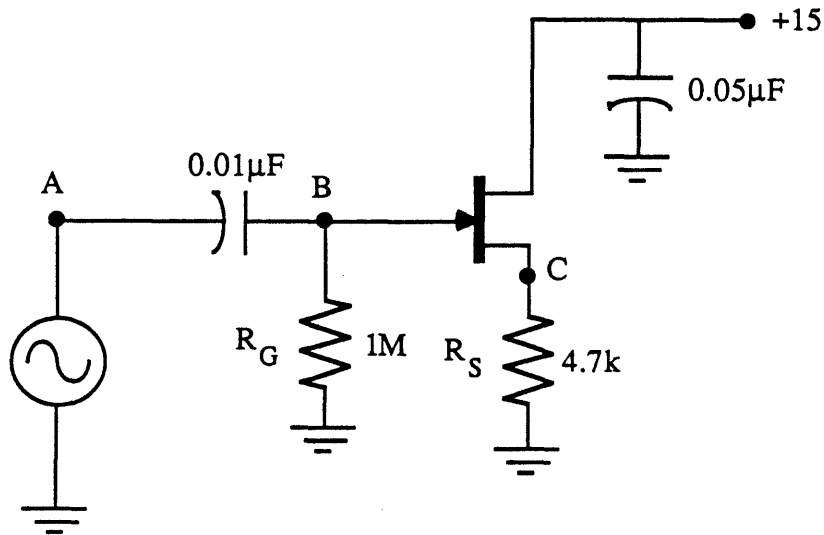


Figure 3 - Source follower

- (1) Build the circuit shown in Fig.3. Connect the scope CH1 input to point A and CH2 input to point C. Use your DMM to measure the DC potentials at points A and C. Record these values in Table 11.6.
- (2) Adjust the generator to produce a 100 mV<sub>p-p</sub> 1 kHz triangle wave at point A.
- (3) Use the scope to measure the AC<sub>p-p</sub> voltage at point C. Record your data in Table 11.6.
- (4) Repeat steps 2 and 3 using 200mV, 400 mV, etc. in step 2 until your signal begins to distort.
- (5) Connect a 1000 ohm resistor between point C and ground. Repeat steps (2) and (3).

The performance of many FET amplifiers can be improved by using current biasing. Modify your circuit to that of Figure 4 which is a source follower with a current source load.

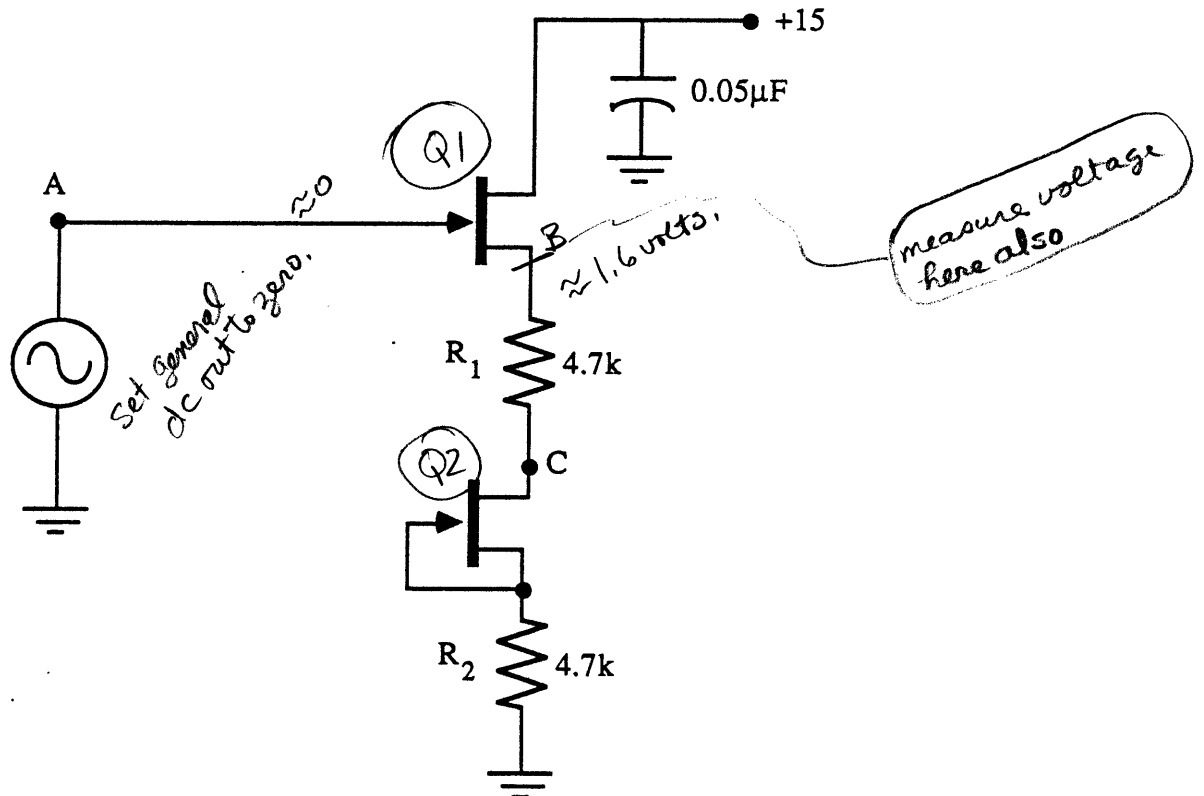


Figure 4 - Source follower with common source load

- (1) Build the circuit shown in Fig.4. Connect the scope CH1 input to point A and CH2 input to point C. Measure the DC voltages at points A and C. Record your measurements in Table 11.7.
- (2) Interchange your FETs. Remeasure the DC voltages at points A and C. Record your results in Table 11.7.
- (3) Adjust the generator to produce a 100 mV<sub>p-p</sub> 1 kHz triangle wave at point A.
- (4) Use the scope to measure the AC<sub>p-p</sub> voltage at point C. Record your data in Table 11.7.
- (5) Repeat steps 3 and 4 using 1V, 1.5V, etc. in step 3 until your signal distorts.
- (6) Connect a 1000 ohm resistor between point C and ground. Repeat steps (3) and (4).

PLEASE CALL A TEACHING ASSISTANT TO CHECK YOUR DATA BEFORE  
CONTINUING.

Questions:


1. (a) What values of  $I_{DSS}$  and  $V_p$  were indicated by the curve tracer?  
~~(b) What values of  $I_{DSS}$  and  $V_p$  were found using the data sheet?~~  
 (c) What are the values for  $I_{DSS}$  and  $V_p$  on the data sheet?  
 (d) What is your most accurate estimate of each parameter? Why?
  
2. You recorded your transistor's drain characteristics using the curve tracer. The slopes of these characteristics in the saturation region are not zero, indicating the presence of an FET parameter called  $g_d$ .  
 (a) Use your knowledge of the BJT model to draw a FET small signal model which includes  $g_d$ . Write an equation for  $g_d$ .  
 (b) Calculate the value of  $g_d$  for each of your curves.  
 (c) Compare  $g_d$  at  $V_{GS} = 0$  to the data sheet value of  $g_{os}$ .
  
3. (a) Use your data of Table 11.5 to make a graph of  $g_m$  vs  $V_{GS}$ .  
 (b) Use your drain characteristics from Part 1 to make a similar graph of  $g_m$  vs  $V_{GS}$ .  
 (c) Compare  $g_m$  at  $V_{GS} = 0$  to the data sheet value of  $g_{fs}$ .  
 (d) What was unusual about the voltage at B when you used +1.0 V? Why?

$$\frac{1}{g_d} = \frac{\Delta I_D}{\Delta V_{GS}}$$

using a linear approximation

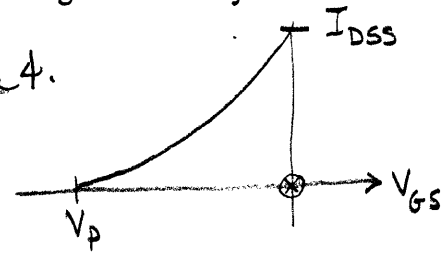4. No question about Figure 4.

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$



$$\approx 125 \mu S$$

$$\approx 8 k \Omega$$


Hint: what was your relationship with  $V_p$ ?

$$g_{fs} \cong \frac{\Delta I_D}{\Delta V_{GS}}$$



small-signal transconductance with common source amp.

$$g_{fs0} = g_{fs} |_{V_{GS}=0}$$

4. Need question about Figure 4.

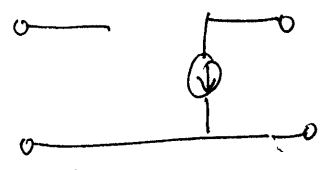

$$\frac{1}{r_d} = \text{slope} = \frac{\Delta I_D}{\Delta V_{DS}}$$

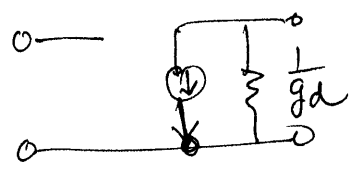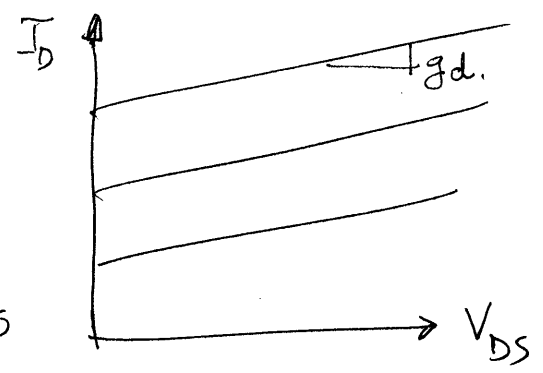

EEAP 243

LAB 11 EVALUATION

NAME (print) \_\_\_\_\_ CHECKPOINT #1 \_\_\_\_ DATE \_\_\_\_\_  
GRADE \_\_\_\_/\_\_\_\_ CHECKPOINT #2 \_\_\_\_ DATE \_\_\_\_\_

With respect to the course material, this lab was: (pick one)  
\_\_\_ highly relevant \_\_\_ relevant \_\_\_ not relevant \_\_\_ completely irrelevant

This lab was: (pick one)  
\_\_\_ too long \_\_\_ long \_\_\_ just right \_\_\_ short \_\_\_ too short

This lab was: (pick one)  
\_\_\_ too hard \_\_\_ hard \_\_\_ just right \_\_\_ easy \_\_\_ too easy

The background material in the lab assignment was: (pick one)  
\_\_\_ too detailed \_\_\_ just right \_\_\_ sufficient \_\_\_ insufficient \_\_\_ totally inadequate

The step by step procedures in the lab assignment were: (pick one)  
\_\_\_ too detailed \_\_\_ just right \_\_\_ sufficient \_\_\_ insufficient \_\_\_ totally inadequate

Describe any mistakes made in the lab assignment.

Describe anything that just didn't work right.

Describe how this lab could be made better.



# QUIZ

NOTE: THE TEACHING ASSISTANT IS TO SELECT BOTH QUESTIONS FROM THE UNDERLINED OPTIONS AT THE SECOND CHECKPOINT

## Question #1

What will be the gain (don't forget the sign) from point A to point B in Fig. 11.2 if we halve/double the resistance of  $R_1/R_2/R_3$  ?

The gain will be \_\_\_\_\_.

## Question #2

What will be the gain (don't forget the sign) from point A to point B in Fig. 11.4 if we halve/double the resistance of  $R_1/R_2/R_3$  ?

The gain will be \_\_\_\_\_.

EEAP 243

NAMES: \_\_\_\_\_

Lab 11 Data

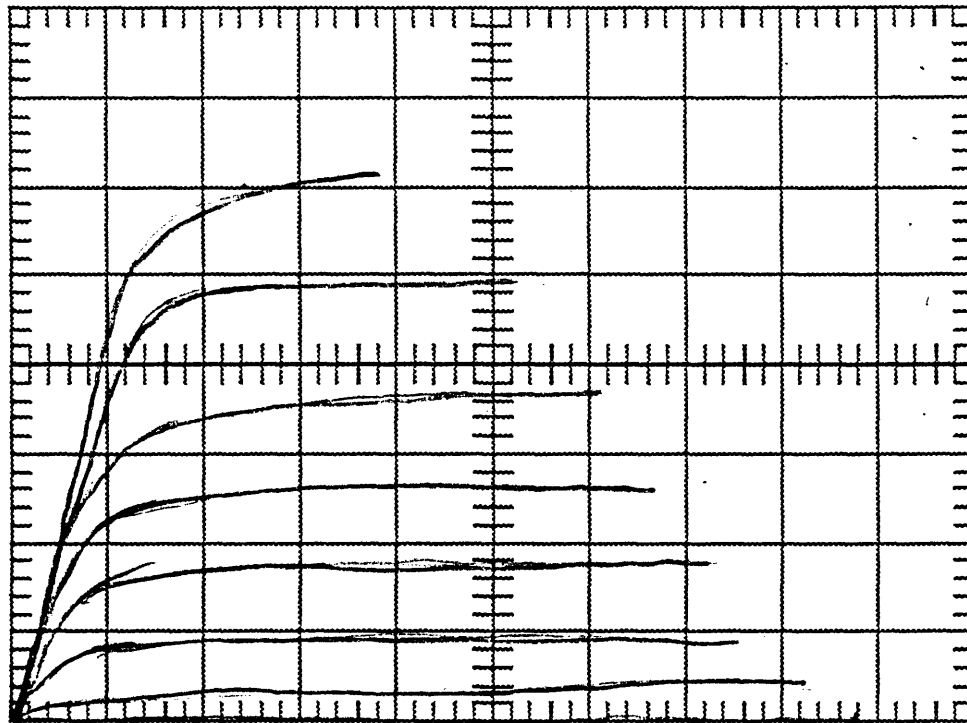


Table 11.1

↑  
go to  
10  
↓

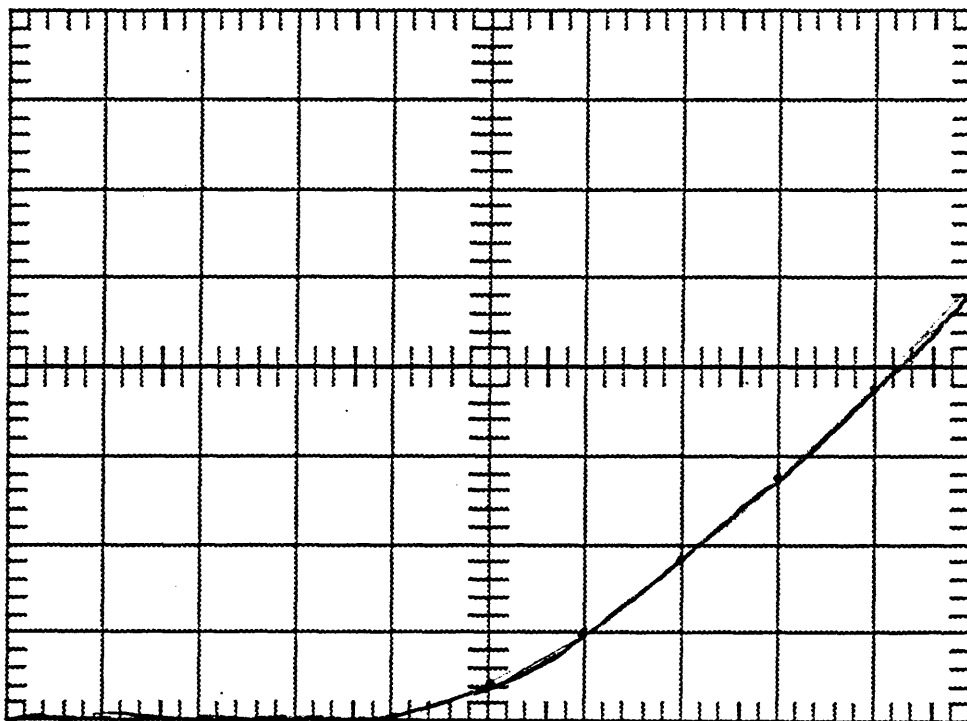


Table 11.2

Difficult to keep at 1mA

V<sub>GS</sub>: -3.55 v      I<sub>D</sub>: -1.02 μA

Table 11.3 DC FET characteristics

I<sub>DSS</sub> = -11.11 mA

R <sub>D</sub>	I <sub>D</sub> mA
10k	<del>0.529</del> 0.529
20k	<del>0.513</del> 0.513
30k	<del>0.415</del> 0.415
40k	<del>0.332</del> 0.332
50k	<del>0.267</del> 0.267
9k	0.530
50k	0.272
70k	0.249

+1.0      1.4 x 50 mV      → V<sub>B</sub> = 0.696 v

Table 11.4 FET current source characteristics

V @ A	Output Voltage (p-p)
+0.5	1.3 x 10 mV
+0.0	1.0 x 50 mV
-0.5	1.0 v 10 mV
-1.0	0.9
-1.5	0.8
-2.0	0.7
-2.5	0.6
-3.0	0.44
-3.5	1.1 x 5 mV
-4.0	<del>_____</del>
-4.5	<del>_____</del>
-5.0	<del>_____</del>
DC V <sub>GS</sub> :	<del>_____</del>

Table 11.5 AC FET characteristics

$V_{GATE}: \underline{0.0V}$   
 $V_{SOURCE}: \underline{2.99V (3.0V)}$

$V_{input,p-p}$	$R_L = \infty$	$R_L = 1k$
	$V_{output,p-p}$	$V_{output,p-p}$
100mV	<u>100 mV</u>	<u>1.45 x 20</u>
200mV	<u>200 mV</u>	<u>1.45 mV</u>
400mV	<u>360</u>	<u>300 mV</u>
800mV	<u>3.8 x 0.2</u>	<u>500 mV</u>
1.2V	<u>2.1 x 0.5</u>	
1.4V	<u>2.35</u>	
1.6V	<u>2.15</u>	
1.8V	<u>1.7</u>	
2.0V	<u>~1.8</u>	

*o/p flatten at bottom after 8V*

*o/p distortion after*  
 $3.6 \times 2 = 7.2V$

Table 11.6 Source Follower characteristics

	Original	Reversed
$V_{GATE}:$	<u>6.9mV</u>	<u>6.9mV</u>
$V_{SOURCE}:$	<u>1.621V</u>	<u>1.523V</u>

$V_{input,p-p}$	$R_L = \infty$	$R_L = 1k$
	$V_{output,p-p}$	$V_{output,p-p}$
100mV	<u>50 mV</u>	<u>0.3 x 50 mV</u>
1.0V	<u>0.5 V</u>	<u>0.3 x 0.5</u>
1.5V	<u>0.75</u>	<u>0.3 x 0.5</u>
2.0V	<u>1.0</u>	<u>0.3 x</u>
2.5V	<u>1.25</u>	<u>0.3 x</u>
3.0V	<u>1.5</u>	<u>0.3 x</u>

*signal distortion after 7.0V*

*o/p distortion after 7.2V*

Table 11.7 Source Follower characteristics

EEAP 243

NAMES: \_\_\_\_\_

Lab 11 Data

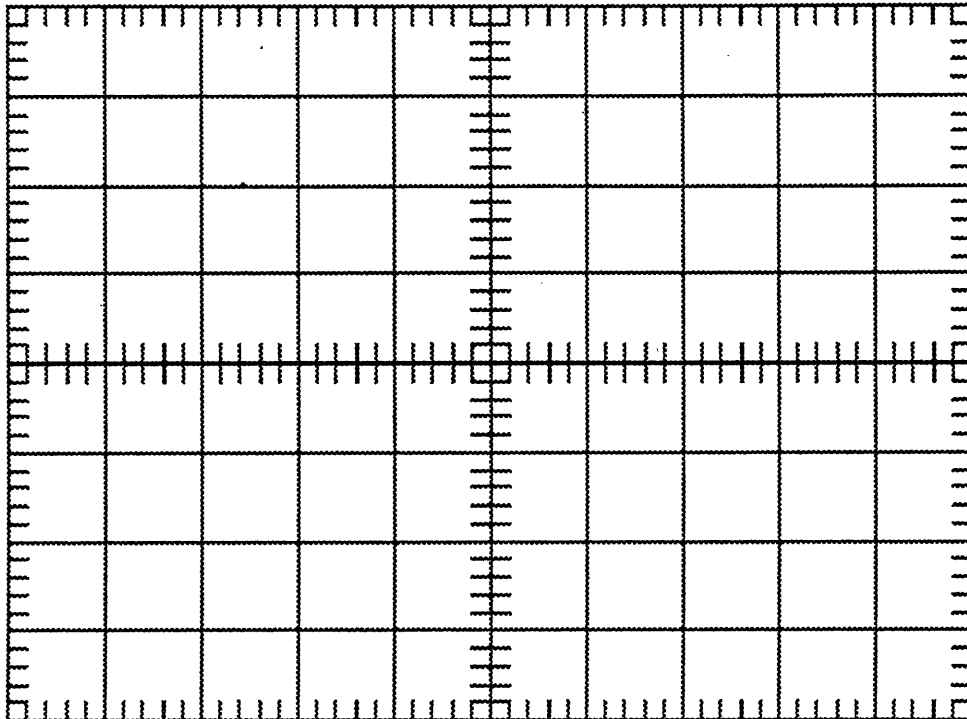


Table 11.1

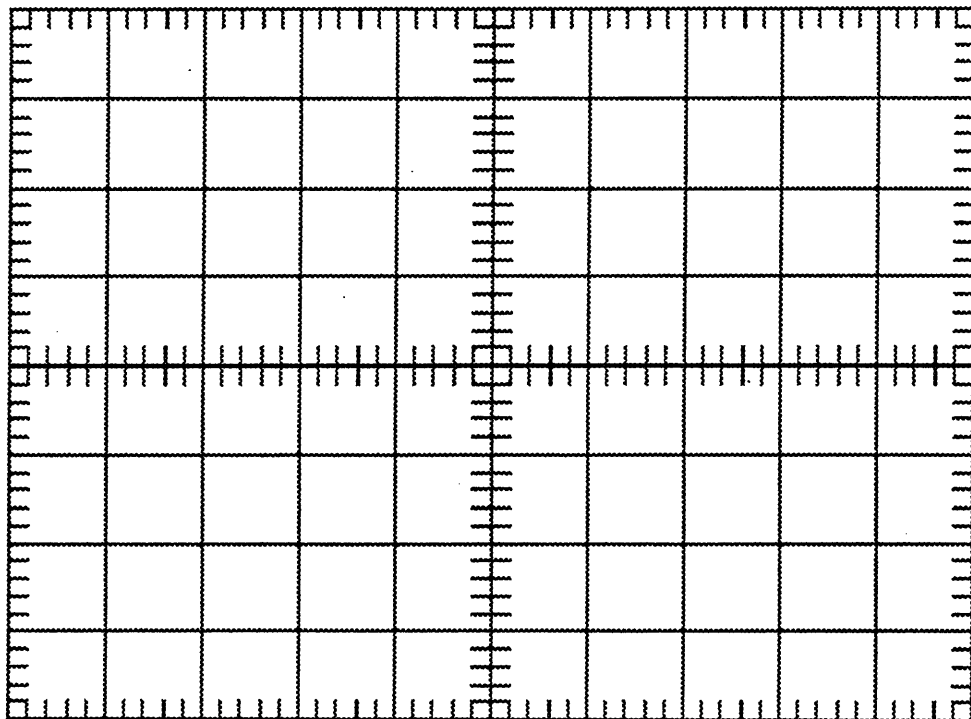


Table 11.2

$V_{GS}$ : \_\_\_\_\_  $I_D$ : \_\_\_\_\_

Table 11.3 DC FET characteristics

$R_D$	$I_D$
10k	_____
20k	_____
30k	_____
40k	_____
50k	_____
_____	_____
_____	_____
_____	_____
_____	_____
_____	_____

Table 11.4 FET current source characteristics

V @ A	Output Voltage (p-p)
+0.5	_____
+0.0	_____
-0.5	_____
-1.0	_____
-1.5	_____
-2.0	_____
-2.5	_____
-3.0	_____
-3.5	_____
-4.0	_____
-4.5	_____
-5.0	_____
DC $V_{GS}$ :	_____

Table 11.5 AC FET characteristics

V<sub>GATE</sub>: \_\_\_\_\_

V<sub>SOURCE</sub>: \_\_\_\_\_

V <sub>input,p-p</sub>	R <sub>L</sub> =∞ V <sub>output,p-p</sub>	R <sub>L</sub> =1k V <sub>output,p-p</sub>
100mV	_____	_____
200mV	_____	_____
400mV	_____	_____
800mV	_____	_____
1.2V	_____	_____
1.4V	_____	_____
1.6V	_____	_____
1.8V	_____	_____
2.0V	_____	_____

Table 11.6 Source Follower characteristics

Original                      Reversed

V<sub>GATE</sub>: \_\_\_\_\_

V<sub>SOURCE</sub>: \_\_\_\_\_

V <sub>input,p-p</sub>	R <sub>L</sub> =∞ V <sub>output,p-p</sub>	R <sub>L</sub> =1k V <sub>output,p-p</sub>
100mV	_____	_____
1.0V	_____	_____
1.5V	_____	_____
2.0V	_____	_____
2.5V	_____	_____
3.0V	_____	_____

Table 11.7 Source Follower characteristics