
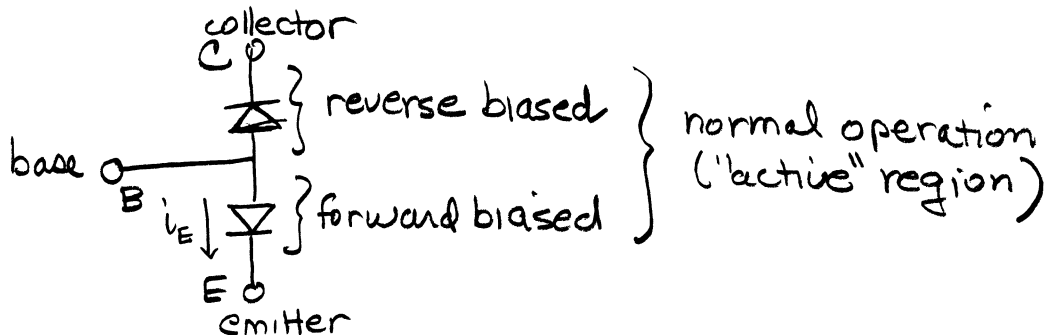
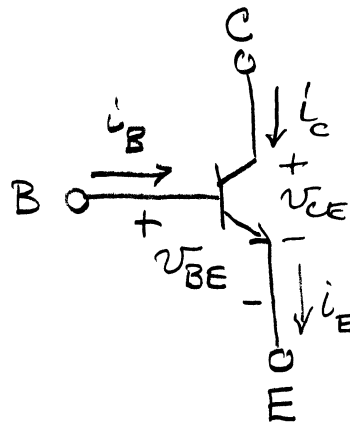


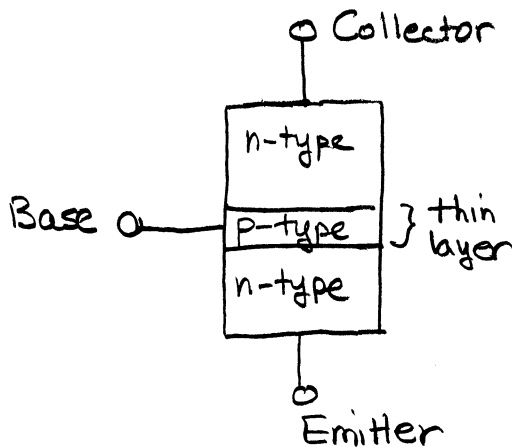4.1 Basic Operation of the npn Bipolar Junction Transistor



How do we bias to make work?

- We need $v_{BE} \approx 0.6$ volts to forward bias bottom diode.
- If $v_{CE} > v_{BE}$ the upper diode is reverse biased.


The operation of the transistor fundamentally depends on the detailed, non-linear operation of the base-emitter junction

Shockley equation:

$$i_E = I_{ES} e^{\left(\frac{v_{BE}}{V_T}\right) - 1}$$

$$V_T \approx 26\text{mV @ room temperature}$$

How does a transistor work physically?

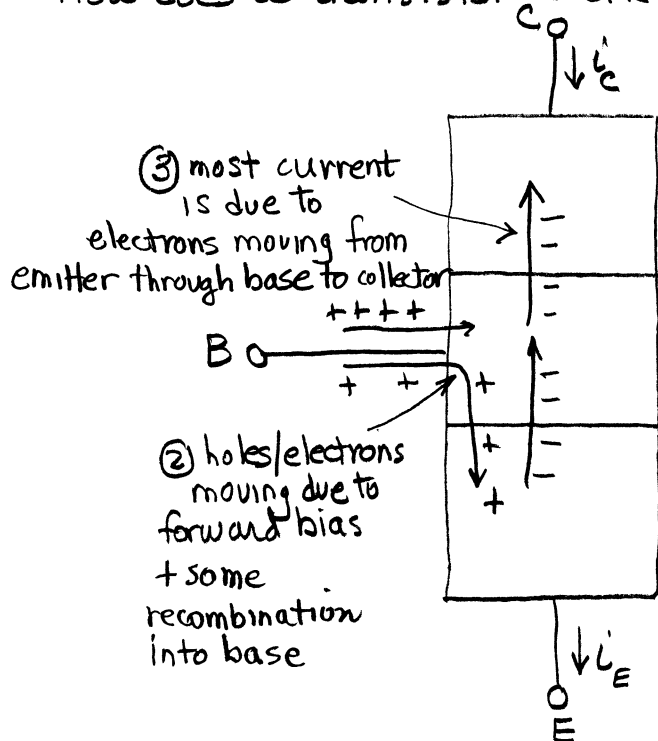


Note: ③ requires a "thin" base


① emitter heavily doped to have lots of free electrons

④ most current across junction supplied by I_C rather than I_B
 $\Rightarrow$ this leads to amplification

Measured characteristics

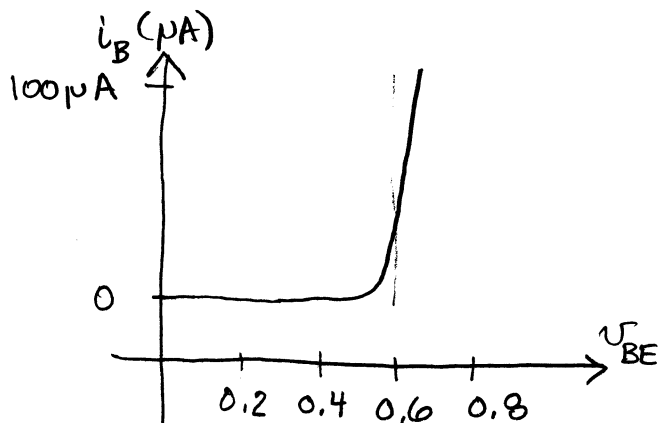

typical base emitter characteristics

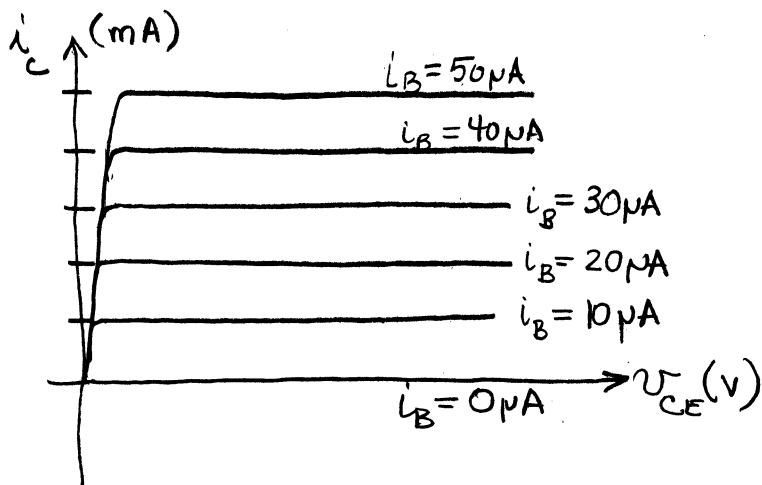


VERY SMALL CHANGE IN I_B
 CAUSES BIG CHANGE IN I_C

AMPLIFICATION

$$\beta \equiv \frac{I_C}{I_B}$$

typically 10-1000

Device equations

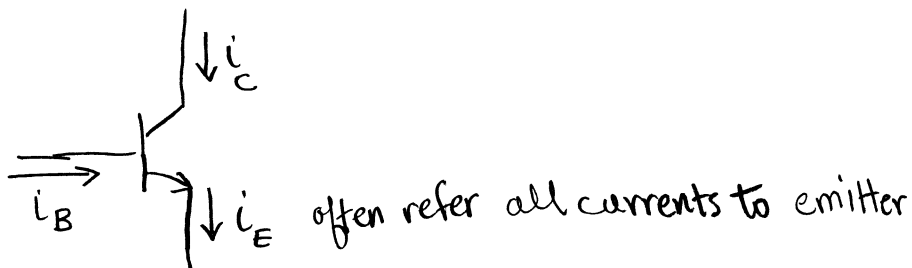

by KCL $i_E = i_C + i_B$

collector current is smaller than emitter current

$$\alpha \equiv \frac{i_C}{i_E} \quad (\text{typically } 0.9 - 0.999)$$


Then $i_B = i_E - i_C = i_E - \alpha i_E = (1 - \alpha) i_E$

where $i_E = I_{ES} \left[e^{\frac{v_{BE}}{V_T}} - 1 \right]$

Recall $\beta = \frac{i_C}{i_B} = \frac{\alpha i_E}{(1 - \alpha) i_E} = \frac{\alpha}{\alpha - 1}$

The equation we always use is $i_C = \beta i_B$ ★

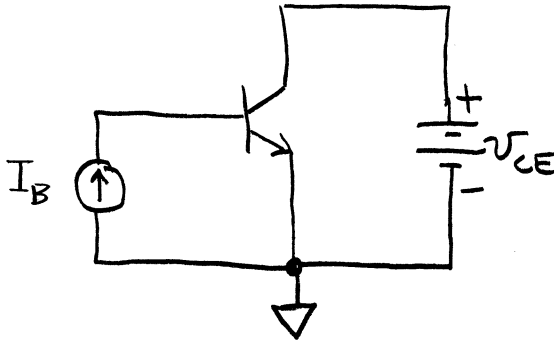Use PSpice to display characteristic curves



Use Qbreak n
click on transistor (turns red)

Under edit menu select

type in $BF=100$

$IS=1E-14$

$VAF=50$

edit model / edit instance model


(FORWARD BETA)

(SCALE CURRENT)


(EARLY VOLTAGE)

LOAD Line analysis

Consider this circuit

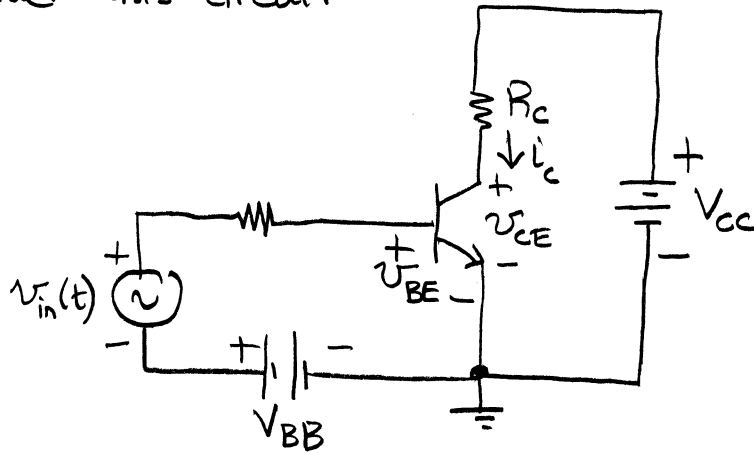


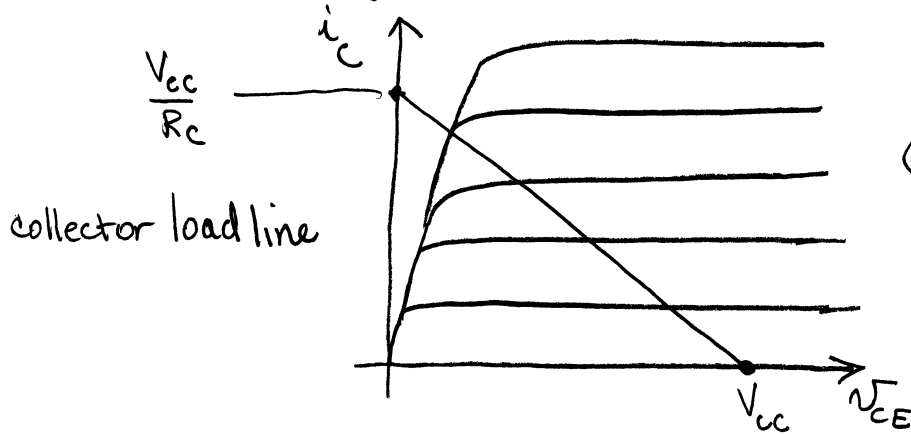This is obviously a non-linear device which we can subject to load line analysis:



② superimpose load line on $i_C - v_{CE}$ characteristics

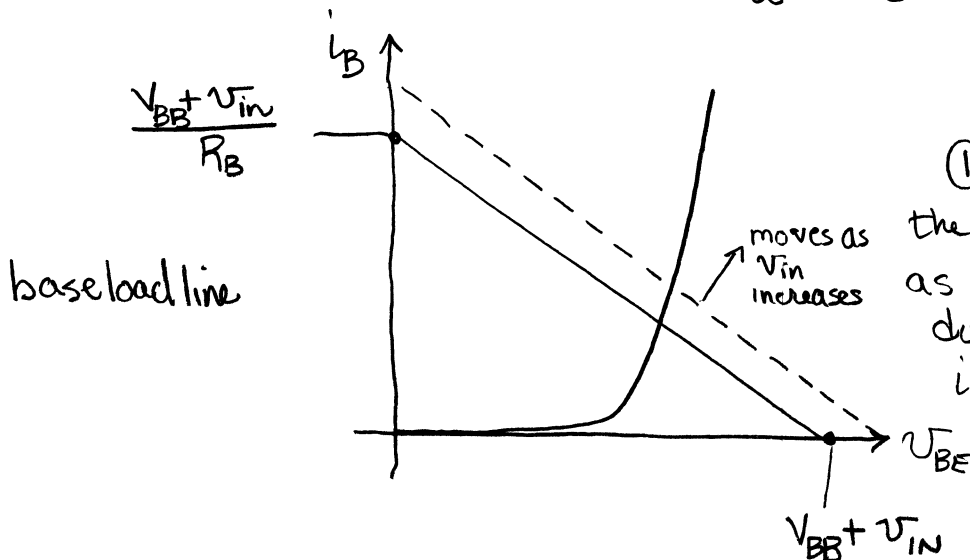
③ As v_{IN} changes, i_B changes and we move to a different operating point.




① As v_{IN} increases the load line moves up, as v_{IN} decreases it goes down. This changes i_B .

Do detailed analysis p. 226.

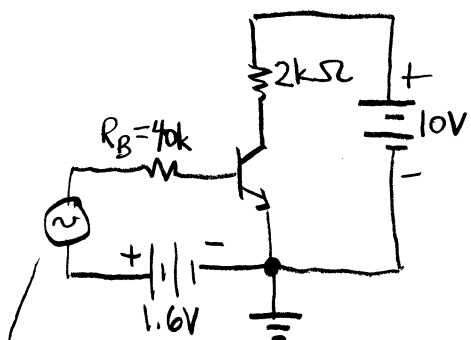What makes the base analysis easier is the vertical diode characteristics



$$0.4\sin(2000\pi t)$$

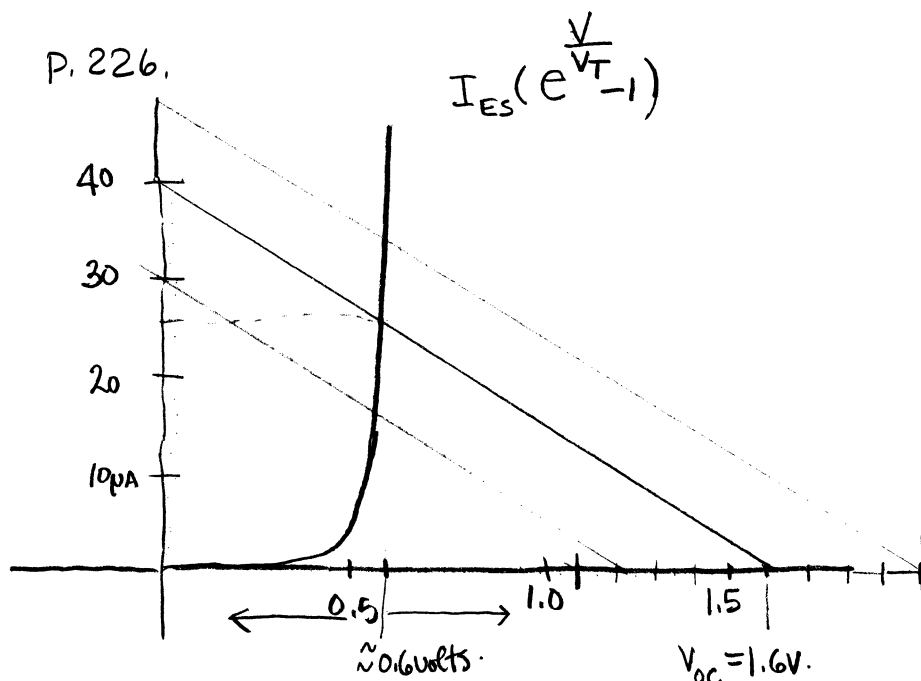

① Draw base load line.

$$V_{oc} = 1.6V.$$

$$I_{sc} = \frac{1.6 \text{ volts}}{40k} = 40\mu A$$

② bias Q-point from intersection

③ Now add in signal voltage to perturb Q-point.
This gives two new load lines.

④ find new Q-points for peaks of signal.

The variation is VERY linear

$$\text{As } V_s \text{ varies from } 1.6 - .4 = 1.2$$


$$1.6 + .4 = 2.0$$

Note V_{BE} almost does NOT change, $\approx$ constant at 0.6volts


$$\text{predict } I_{B1} = \frac{1.6 - 0.6 + .4}{40k} = \frac{1.4}{40k} = 35\mu A$$

$$I_{B2} = \frac{1.6 - 0.6 - 0.4}{40k} = \frac{0.6}{40k} = 15\mu A$$

Now do detailed load circuit analysis

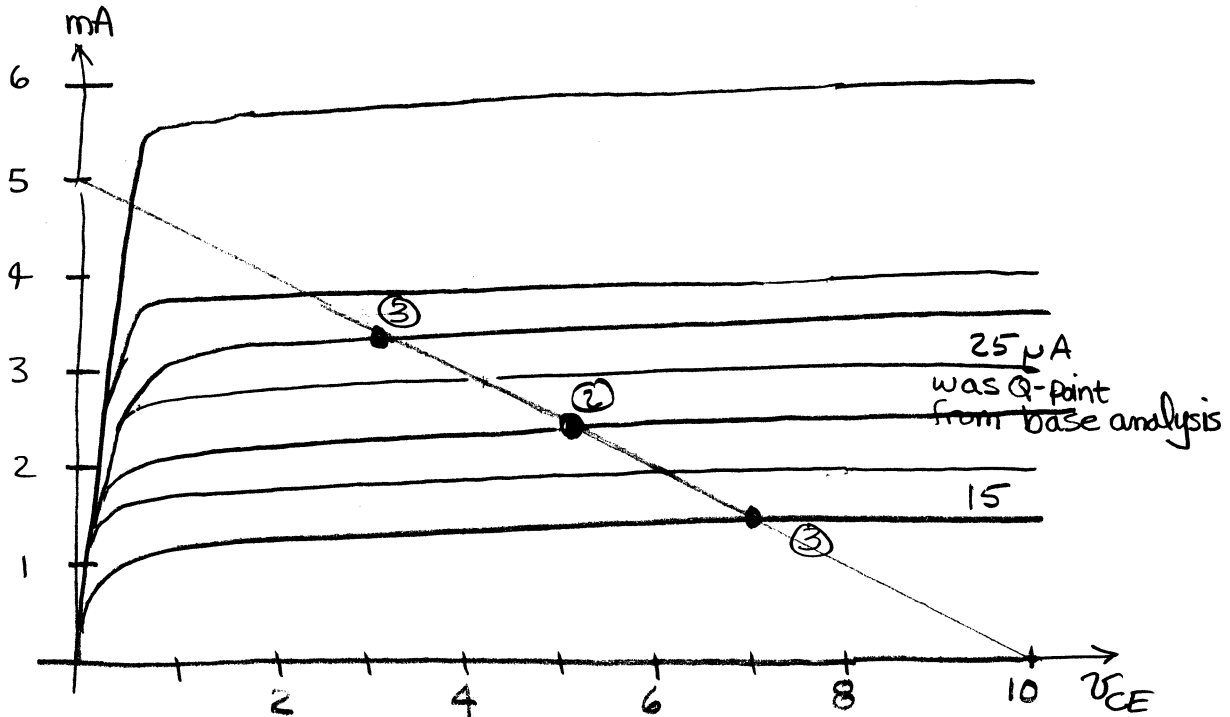

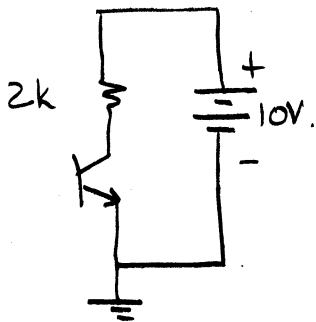- ① draw collector load line on characteristic curves for specific transistor



$$V_{OC} = 10 \text{ volts.}$$

$$I_{sc} = \frac{10V}{2k} = 5mA.$$

- ② identify base curve for DC bias current in this case $I_{BQ} = 25 \mu A$.

This intersection is Q-point for collector circuit.

- ③ Now look at new Q-points corresponding to maximum and minimum of input signal

$$I_{B+peak} = 35 \mu A$$



$$I_{B-peak} = 15 \mu A$$

- ④ V_{CE} varies from 7 volts to 3 volts.



$$A_v = \frac{7-3 \text{ volts}}{+0.4+0.4} = \frac{4}{.8} = 5.$$

Distortion — amplifier is non-linear
due to curvature and nonuniform spacing
of characteristics

exaggerated
example

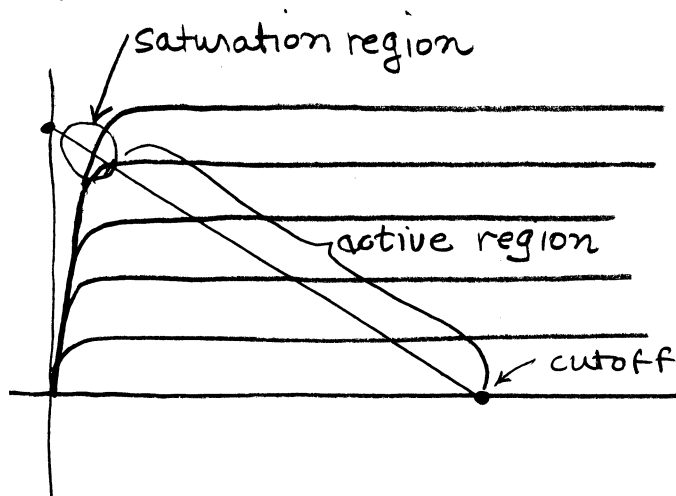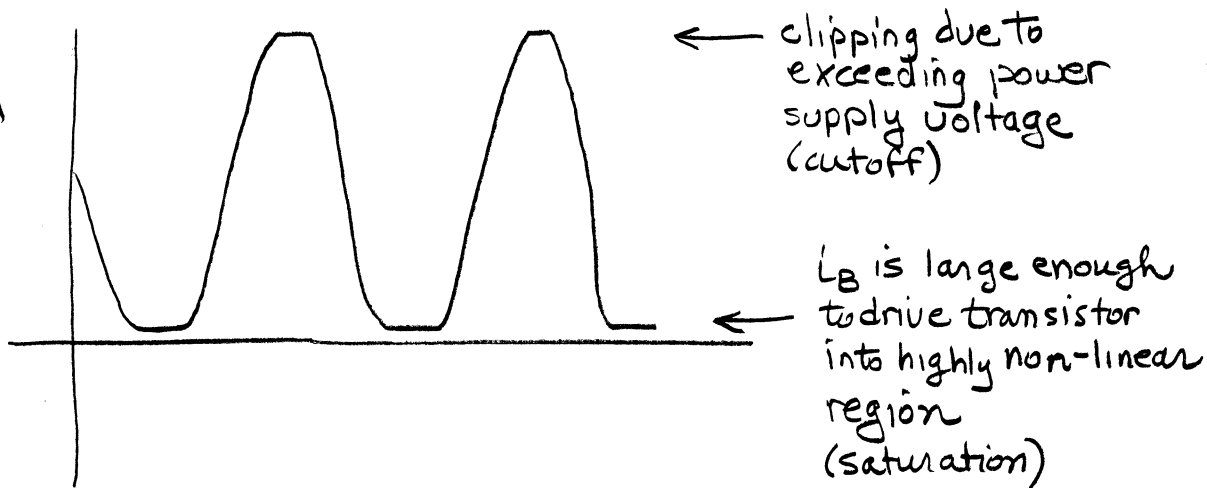

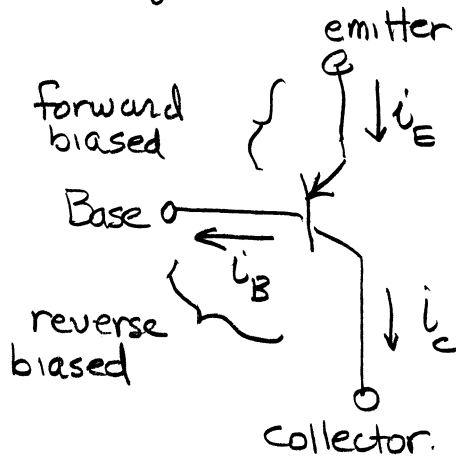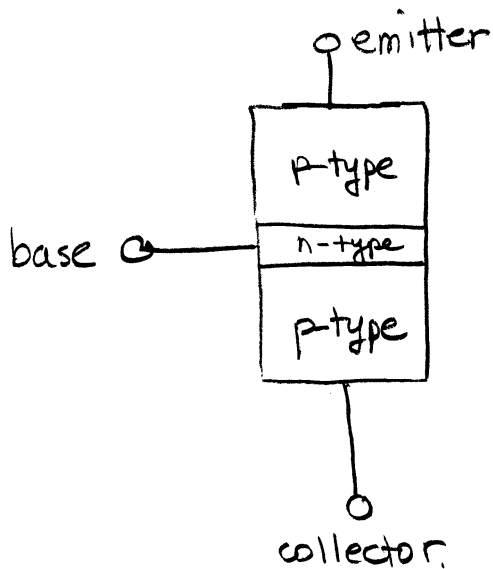18
pnp transistor — the reverse of the npn transistor



note difference
in sign of
collector
current

equations:

$$i_C = \alpha i_E$$

$$i_B = (1 - \alpha) i_E$$

$$i_E = i_C + i_B$$


$$i_C = \beta i_B$$

in active region:

$$i_E = I_{ES} \left[e^{-\frac{V_{BE}}{V_T}} - 1 \right]$$

$$i_B = (1 - \alpha) I_{ES} \left[e^{-\frac{V_{BE}}{V_T}} - 1 \right]$$

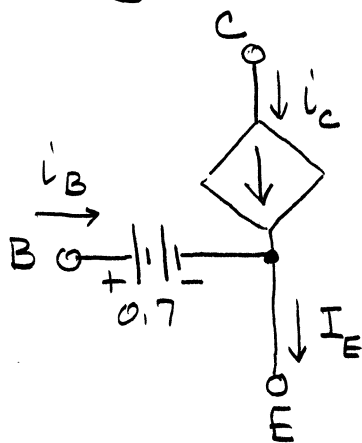
Large signal models
(usually for DC amplifiers)



active region

$$I_B > 0$$


$$V_{CE} > 0.2V$$

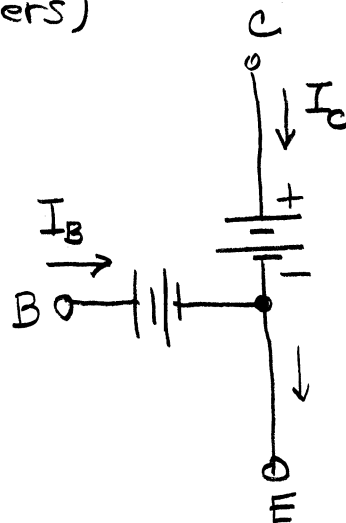

saturation region

$$I_B > 0$$

$$\beta I_B > I_c > 0$$

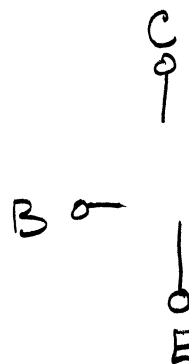


cutoff region

$$V_{BE} < 0.5V$$

$$V_{BC} < 0.5V$$

Three models.

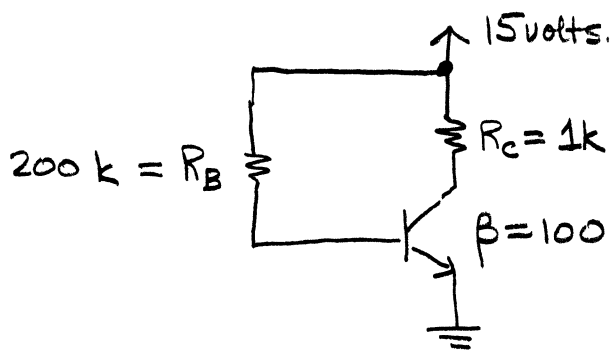

solve for I_c & V_{CE}


This is called a fixed bias point circuit. If β changes the operating point will change.

① Is transistor active, cutoff, or saturated?

assume cutoff then $V_{BE} = 15$ volts and transistor must be ON.

assume saturation

use this model.

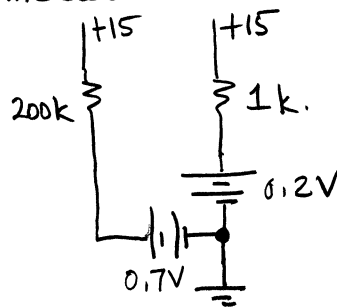

$$I_c = \frac{V_{cc} - 0.2}{1k} = \frac{15 - 0.2}{1k} = 14.8 \text{ mA}$$


$$I_B = \frac{V_{cc} - 0.7}{200k} = 71.5 \text{ } \mu\text{A}$$

$I_B > 0$ so ok

however $\beta I_B = (100)(71.5 \text{ } \mu\text{A}) = 7.15 \text{ mA} < 14.8 \text{ mA}$

$\Rightarrow$ transistor is active

In active region

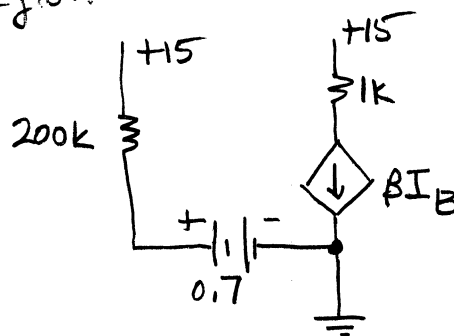

$$I_B = \frac{15 - 0.7}{200k} = 71.5 \text{ } \mu\text{A}$$

$$I_c = \beta I_B = 100(71.5 \text{ } \mu\text{A}) = 7.15 \text{ mA}$$

$$V_{CE} = V_{cc} - I_c R_c = 15 - (7.15 \text{ mA})(1k)$$


$$V_{CE} = 7.85 \text{ volts.}$$

Pspice analysis

gave $I_c = 7.18 \text{ mA}$ and $V_{CE} = 7.82 \text{ volts.}$

Examples:

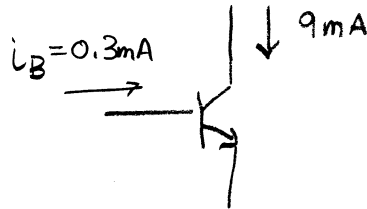4.3 An npn transistor is operating with the base-emitter junction forward biased and the base-collector junction reverse biased. If $i_C = 9\text{mA}$ for $i_B = 0.3\text{mA}$, find i_E , α and β .




$$i_E = i_C + i_B = 9\text{mA} + 0.3\text{mA} = 9.3\text{mA}$$

$$\alpha = \frac{i_C}{i_E} = \frac{9\text{mA}}{9.3\text{mA}} = .9677$$

$$\beta = \frac{i_C}{i_B} = \frac{9\text{mA}}{0.3\text{mA}} = 30.$$

$$\text{As a check } \beta = \frac{\alpha}{1-\alpha} = 30.$$

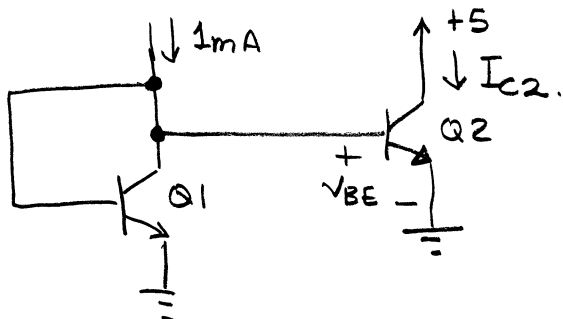4.11 Consider the circuit shown in Figure P4.11. The transistors Q_1 and Q_2 are identical, both having $I_{ES} = 10 \text{ fA} = 10^{-14} \text{ A}$ and $\beta = 100$. Find V_{BE} and I_{C2} . Assume a temperature of 300 K .
Hint: both transistors are operating in the active region.
Because the transistors are identical and have identical values of V_{BE} , their collector currents are equal.



Shockley equation
$$i_E = I_{ES} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$V_T = \frac{kT}{q} \cong 26 \text{ mV} @ 300^\circ \text{K}.$$

The key observation is that since the transistor bases are connected to the same point their V_{BE} 's are identical.

$$i_{B,Q1} + \beta i_{B,Q1} + i_{B,Q2} = 1 \text{ mA}$$

$$i_B + \beta i_B + i_B = 1 \text{ mA}$$

$$102 i_B = 1 \text{ mA}$$

$$i_B = 9.8 \mu\text{A}$$

$$i_{C2} = \beta i_{B,Q2} = (100)(9.8 \mu\text{A}) = 0.98 \text{ mA}$$

$$@ Q1 \quad i_E = I_{ES} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$(\beta + 1) i_B = I_{ES} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$(101) \left(\frac{1 \text{ mA}}{102} \right) = 10^{-14} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$9.9 \times 10^{-4} = 10^{-14} \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$

$$9.9 \times 10^{10} = \left[e^{\frac{V_{BE}}{V_T}} - 1 \right]$$



$$\therefore e^{\frac{V_{BE}}{V_T}} \cong 9.902 \times 10^{10}$$

$$\frac{V_{BE}}{V_T} = 25.318$$

$$V_{BE} \cong 658 \text{ mV}$$

Load line analysis of a common emitter amplifier

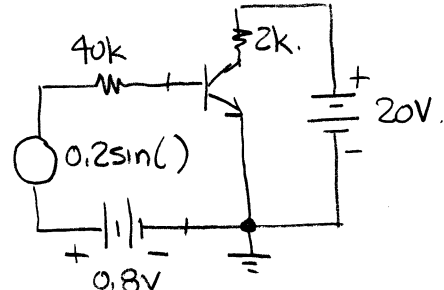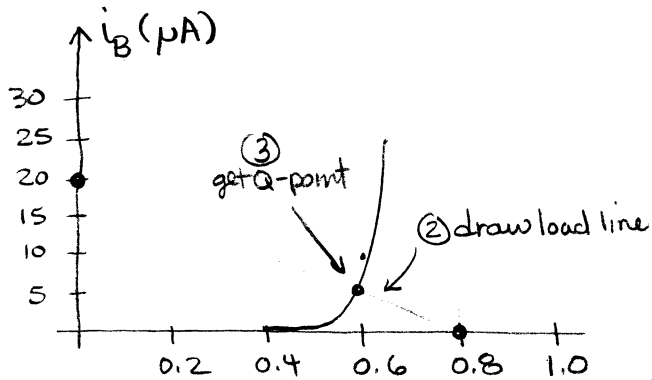4.20. Consider the circuit of Figure 4.10. Assume $V_{CC} = 20V$, $V_{BB} = 0.8V$, $R_B = 40k\Omega$ and $R_C = 2k\Omega$. The input signal is a 0.2 volt peak, 1 kHz sinusoid given by $v_{in}(t) = 0.2 \sin(2000\pi t)$. The common-emitter characteristics for the transistor are shown in Figure P4.20. Find the maximum, minimum, and Q-point values for V_{CE} . What is the approximate voltage gain for this circuit.




① $I_{sc} = \frac{0.8}{40k} = 0.02 \text{ mA}$

④ Alternatively, calculate

$$I_B = \frac{0.8 - 0.6}{40k} = 5 \mu A$$

$$I_{B, \text{max}} = \frac{0.8 - 0.6 + 0.2}{40k} = 10 \mu A$$
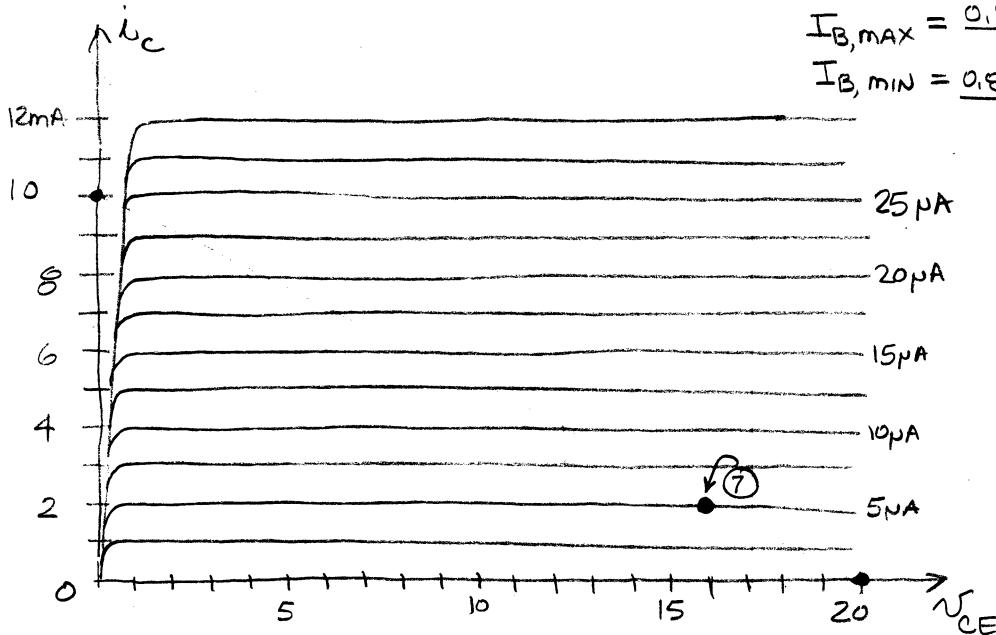
$$I_{B, \text{min}} = \frac{0.8 - 0.6 - 0.2}{40k} = 0 \mu A$$



⑥ determine collector load line

$$I_{sc} = \frac{20V}{2k} = 10 \text{ mA}$$

$$V_{oc} = 20V$$

⑦ Determine Q-point for $I_B = 5 \mu A$.

$$V_{CE, Q} = 16V$$

$$I_{CE, Q} = 2 \text{ mA}$$

⑧ $V_{CE, \text{max}}$ and $V_{CE, \text{min}}$ } Assuming symmetry and no distortion we get $V_{CE, Q} \pm 4V$
or $V_{CE, \text{max}} = 20$

$$V_{CE, \text{min}} = 16 - 4 = 12V$$


What does i_B do. $I_{B, \text{max}} = 10 \mu A$ takes us to about 12V

likewise $I_{B, \text{min}} = 0 \mu A$ takes us to about 20V

⑨ $A_v \approx \frac{8 \text{ volts}}{.4 \text{ volts}} = 20$

Large signal analysis of BJT circuits

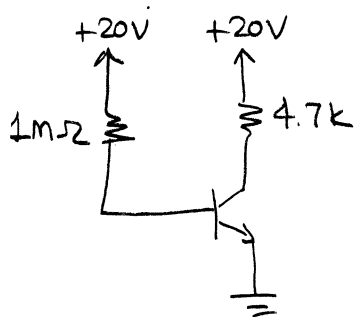
- 4.33 Use the large signal models for the transistor illustrated to find I_C and V_{CE} for the circuits illustrated in Figure P4.33. Assume that $\beta = 100$. Repeat for $\beta = 300$ and compare the results.



Is it cutoff, active, or saturated?

① cutoff has $V_{BE} = 20V$ so NOT this mode $\gg 0.7V$

② active has

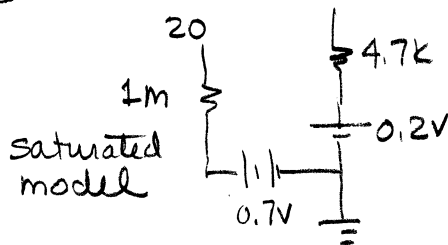

$$i_B = \frac{20 - 0.7}{1M} = 19.3 \mu A$$


$$i_C = \beta i_B = (100)(19.3 \mu A)$$

$$i_C = 1.93 mA$$

$$i_C = \frac{20 - 0.2}{4.7k} = 4.2 mA$$

Since $\beta i_B < i_C$ we are in active region
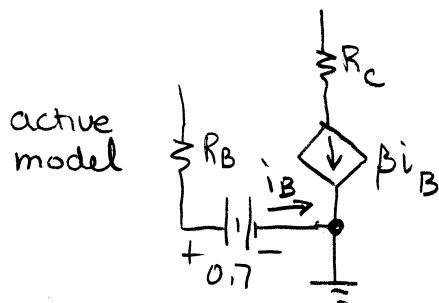
$$i_C = 1.93 mA \text{ so } V_{CE} = 20 - (1.93)(4.7k) = 10.9 \text{ volts.}$$



③ $\beta = 300$ $300 i_B = i_C = 5.79 mA$

$$V_{CE} = 20 - (5.79)(4.7) = -7.2 \text{ volts}$$


$\Rightarrow$ transistor is saturated.

BIAS CIRCUIT DESIGN

fixed-base circuit bias very dependent on β


Consider a bias circuit that provides $I_B = 71.5 \mu A$ to an npn transistor. The β for that transistor varies from 100 to 300.

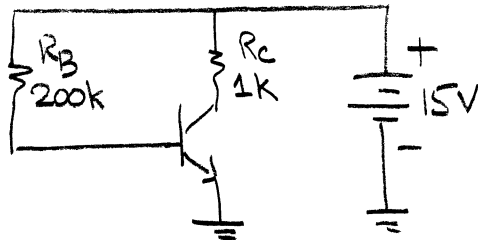The base circuit does NOT change, BUT the load circuit does since the transistor changes.



$$I_B = \frac{V_{CC} - 0.7}{R_B} = \frac{15 - 0.7}{200k} = 71.5 \mu A.$$

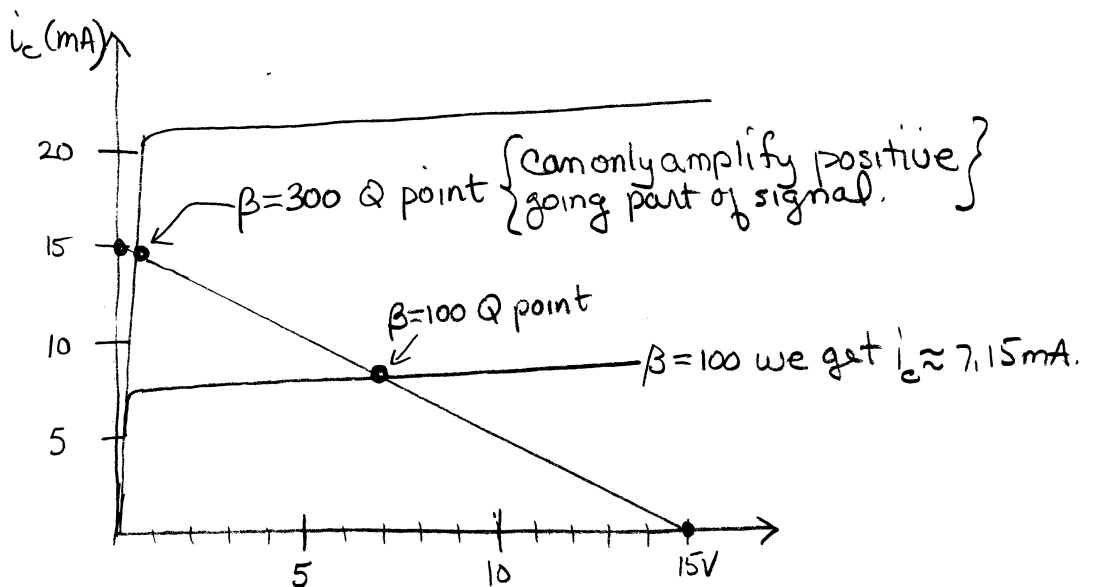
This is independent of β . However, β influences the collector circuit.




$$\begin{aligned} \text{load line } V_{CE} &= 15V \\ I_{CE} &= \frac{15V}{1k} = 15mA. \end{aligned}$$

$$\begin{aligned} \text{for } \beta = 100 \quad i_c &= \beta i_B = 7.15mA \\ \beta = 300 \quad i_c &= \beta i_B = 21.45mA. \end{aligned}$$

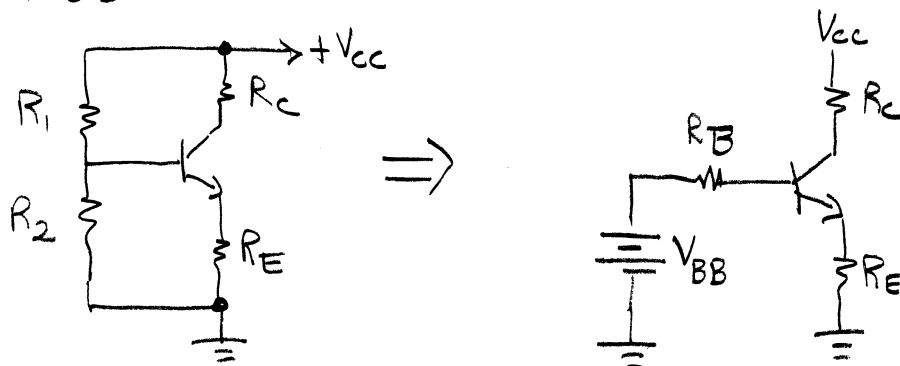If you are designing a discrete BJT bias design you would use a 4-resistor bias circuit.



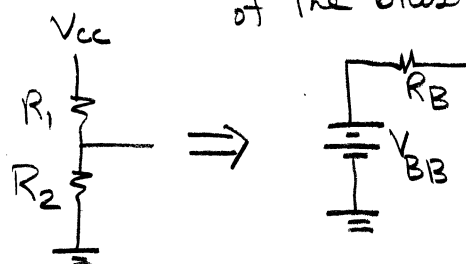where R_B, V_{BB} are the Thevenin equivalent of the bias circuit



$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$V_{BB} = \frac{R_2}{R_1 + R_2} V_{cc}$$

Now do a base circuit analysis for the Thevenized bias circuit.

$$-V_{BB} + I_B R_B + V_{BE} + I_E R_E = 0.$$

Now use $V_{BE} \cong 0.7$ volts.

$$I_E = (\beta + 1) I_B$$

$$\text{Then } I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1) R_E}$$


$$\text{Now consider } I_C = \beta I_B = \frac{\beta (V_{BB} - V_{BE})}{R_B + (\beta + 1) R_E}$$

You can see that if $(\beta + 1) R_E \gg R_B$ Then $I_C \cong \frac{\beta}{\beta + 1} \left(\frac{V_{BB} - V_{BE}}{R_E} \right)$
which is effectively independent of β .

Ways to bias a transistor that are independent of β

1. emitter resistor
 2. 4-resistor bias network
2. current source biasing.

Example 4.6

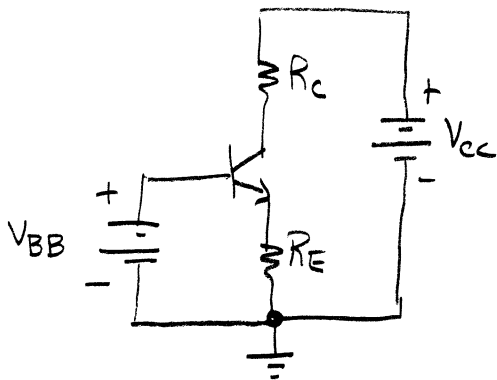

$$\begin{aligned}V_{CC} &= 15 \\V_{BB} &= 5V \\R_C &= 2k\Omega \\R_E &= 2k\Omega \\ \beta &= 100.\end{aligned}$$

We will assume $V_{BE} = 0.7$ volts.

$$\text{For the base } V_{BB} = 0.7 + I_E R_E \text{ or } I_E = \frac{V_{BB} - 0.7}{R_E} = \frac{5 - 0.7}{2k} = 2.15 \text{ mA}$$

Note that I_E independent of β in this equation.

$$\text{since } I_C = \beta I_B \text{ and } I_C + I_B = I_E$$

$$\text{we have } \beta I_B + I_B = (\beta + 1) I_B = I_E$$

$$\therefore I_B = \frac{I_E}{\beta + 1} = \frac{2.15 \text{ mA}}{100 + 1} = 21.3 \mu\text{A}$$

$$I_C = \beta I_B = (100)(21.3 \mu\text{A}) = 2.13 \text{ mA}$$

$$\begin{aligned}V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\&= 15 - (2.13)(2) - (2.15)(2) \\&= 15 - 4.26 - 4.3 = 6.44.\end{aligned}$$


Now, this proves nothing until we compute the same thing for $\beta = 300$. Then

$$I_B = \frac{I_E}{\beta + 1} = \frac{2.15 \text{ mA}}{300 + 1} = 7.14 \mu\text{A}$$

$$I_C = \beta I_B = (300)(7.14 \mu\text{A}) = 2.14 \text{ mA}$$


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 15 - (2.14)(2) - (2.15)(2) = 6.42.$$

Example 4.7

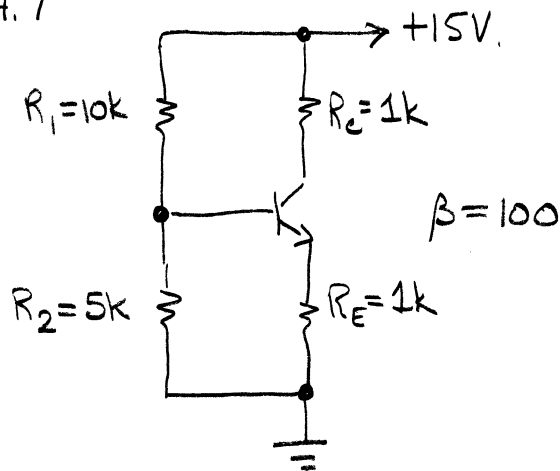

Thevenize the input: $V_{BB} = \frac{5k}{5k+10k} \cdot 15V = \frac{5}{15} \cdot 15 = 5\text{volts.}$
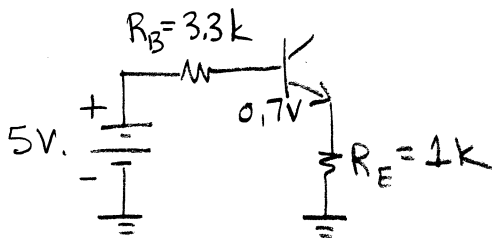
$$R_B = \frac{R_1 R_2}{R_1 + R_2} = \frac{(10)(5)}{10+5} = \frac{50}{15} k = 3.3k$$



$$-5V + I_B(3.3k) + 0.7 + I_E(1k) = 0.$$

$$\text{where } I_E = (\beta + 1)I_B$$

$$+5 - 0.7 = I_B(3.3k) + (\beta + 1)(1k)I_B$$


$$I_B = \frac{5 - 0.7}{3.3k + (101)(1k)} = \frac{4.3}{104.3k}$$

$$I_B = 41.2\mu A$$

$$\text{If } \beta = 300 \quad I'_B = \frac{4.3}{3.3k + (301)(1k)} = \frac{4.3}{304.3k} = 14.1\mu A$$

$$\begin{array}{l} \text{for } \beta = 100 \quad I_C = \beta I_B = (100)(41.2\mu A) = 4.12\text{mA} \\ \beta = 300 \quad I'_C = \beta I'_B = (300)(14.1\mu A) = 4.23\text{mA} \end{array} \left. \vphantom{\begin{array}{l} \text{for } \beta = 100 \\ \beta = 300 \end{array}} \right\} \text{small change!}$$

Current source biasing (used in IC's)

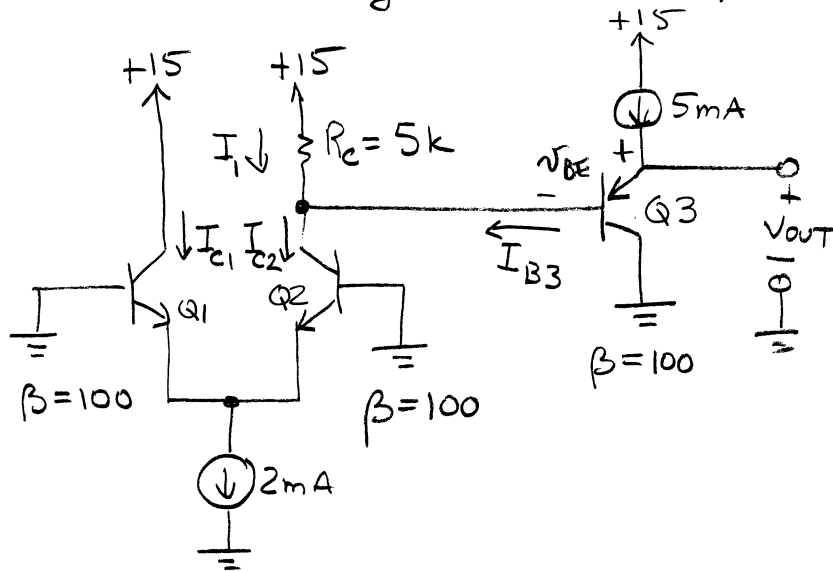

Since Q_1, Q_2 are identical and their V_{BE} 's are identical

$$I_{E1} = I_{E2}$$

From circuit $I_{E1} + I_{E2} = 2\text{mA} \Rightarrow I_{E1} = I_{E2} = 1\text{mA}$.

$$I_{B1} = I_{B2} = \frac{I_{E1}}{\beta + 1} = \frac{1\text{mA}}{100 + 1} = 9.9\mu\text{A}$$

$$I_{C1} = I_{C2} = \beta I_{B1} = (100)(9.9\mu\text{A}) = 0.99\text{mA}$$

Since I_E for $Q_3 = 5\text{mA}$ we have

$$I_{B3} = \frac{I_{E3}}{\beta + 1} = \frac{5\text{mA}}{100 + 1} = 49.5\mu\text{A}$$

$$I_{C3} = \beta I_{B3} = (100)(49.5\mu\text{A}) = 4.95\text{mA}$$

Do KCL at collector of Q_2



$$+ I_1 - I_{C2} + I_{B3} = 0$$

$$\therefore I_1 = I_{C2} - I_{B3} = 0.99\text{mA} - 49.5\mu\text{A} = 0.941\text{mA}$$

$$\text{Compute } V_o = 0.7 - I_1 R_c + 15$$

$$= 0.7 - (0.941)(5) + 15 = 10.3\text{ volts}$$

pnP transistors

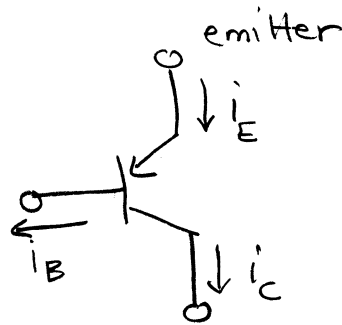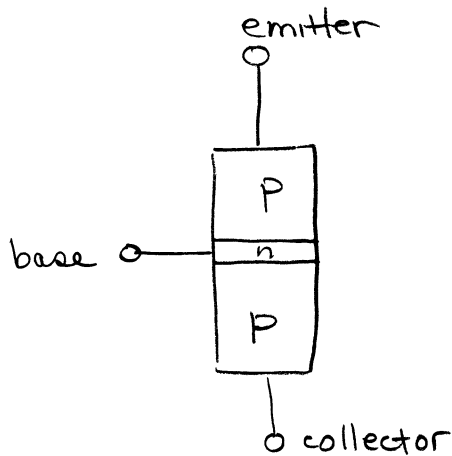


$$i_E = i_C + i_B$$

$$i_C = \beta i_B$$


$$i_E = I_{ES} \left(e^{-\frac{V_{BE}}{V_T}} - 1 \right)$$

the equations for the pnp transistor are exactly the same as for the npn transistor.

Exercise 4.8

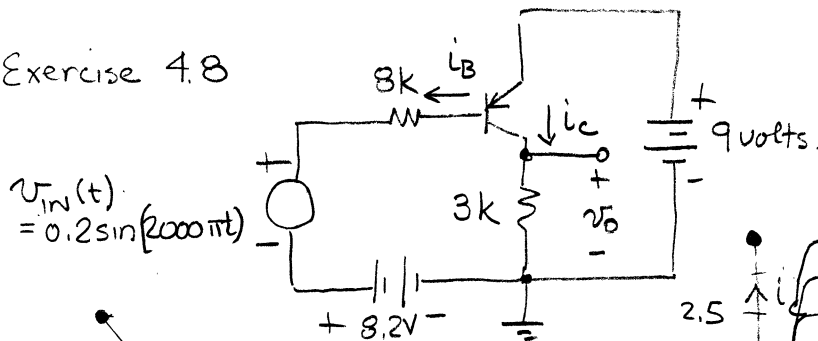

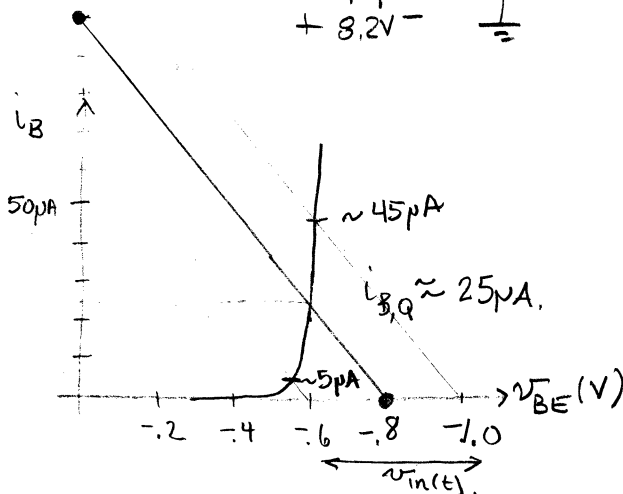
do analysis same as for npn but watch polarities



load line $V_{oc} = -0.8 \text{ volts}$.

$$i_{sc} = \frac{9 \text{ volts}}{8k} = 0.1 \text{ mA} = 100 \text{ pA}$$
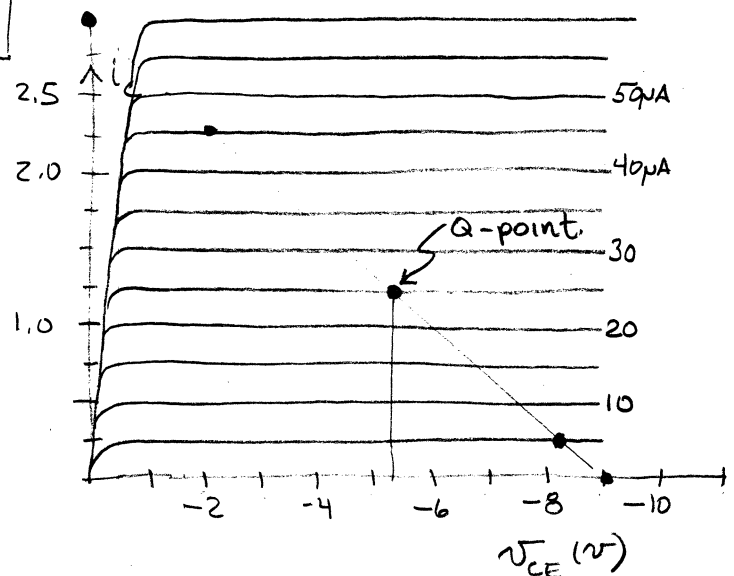
$$\Rightarrow i_{B,Q} \approx 25 \text{ pA}$$



load line: $V_{oc} = -9 \text{ volts}$

$$i_{sc} = \frac{9 \text{ volts}}{3k} = 3 \text{ mA}$$


$$\Rightarrow V_{CE,Q} \approx 5.3 \text{ volts}$$

$$i_{C,Q} \approx 1.25 \text{ mA}$$

$$V_{CE,MAX} \approx -8.2 \text{ V}$$

$$V_{CE,MIN} \approx -2 \text{ volts}$$

Another
pnp example.

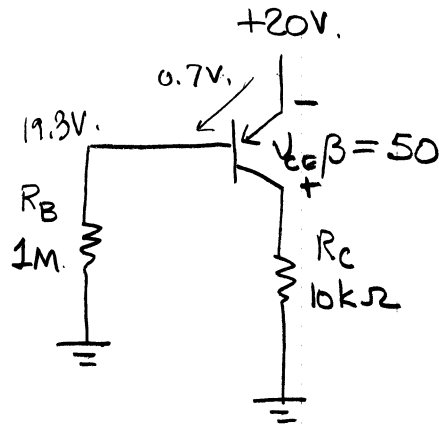

(a) transistor is not cutoff since $V_{BE} > 0.5$ volts.

(b) active analysis:

$$I_B = \frac{20 - 0.7}{1M} = 19.3 \mu A$$

$$I_C = \beta I_B = (50)(19.3 \mu A) = 965 \mu A$$

$$\text{at saturation } I_{C,sat} = \frac{20 - 0.2}{10k} = \frac{19.8}{10} \text{ mA} = 1.98 \text{ mA}$$

$\Rightarrow$ transistor is active and

$$\begin{aligned} V_{CE} &= 20 - I_C R_C = 20 - (0.965 \text{ mA})(10k) \\ &= 20 - 9.65 = 10.35 \text{ volts} \end{aligned}$$

Note polarity actually -10.35 volts.

4.6 Small Signal Equivalent Circuits

Little bit of theory.

$$i_B = (1-\alpha) I_{ES} \left[e^{\frac{v_{BE}}{V_T}} - 1 \right]$$

write in terms of small signal variations about bias point

$$I_{B,Q} + i_b(t) = (1-\alpha) I_{ES} \left[e^{\frac{V_{BE,Q} + v_{be}(t)}{V_T}} - 1 \right]$$

$$I_{B,Q} + i_b(t) \cong \underbrace{(1-\alpha) I_{ES} e^{\frac{V_{BE,Q}}{V_T}}}_{\text{but this is } I_{B,Q}} e^{\frac{v_{be}(t)}{V_T}}$$

$$I_{B,Q} + i_b(t) \cong I_{B,Q} e^{\frac{v_{be}(t)}{V_T}}$$

Now consider small-signals (on the order of millivolts)

$$e^x \cong 1 + x$$

using this approximation

$$I_{B,Q} + i_b(t) \cong I_{B,Q} \left[1 + \frac{v_{be}(t)}{V_T} \right]$$

$$\cancel{I_{B,Q}} + i_b(t) \cong \cancel{I_{B,Q}} + \frac{I_{B,Q}}{V_T} v_{be}(t)$$

$$i_b(t) = \frac{v_{be}(t)}{r_\pi} \quad \text{where } r_\pi \equiv \frac{V_T}{I_{B,Q}}$$


$$\text{or } r_\pi = \frac{\beta V_T}{I_{C,Q}}$$

$$I_{C,Q} + i_c(t) = \beta I_{B,Q} + \beta i_b(t)$$

so the small-signal components are related by

$$i_c(t) = \beta i_b(t).$$

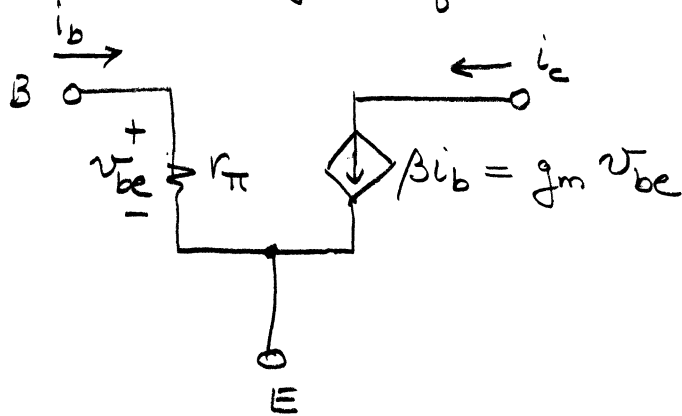This gives the small-signal equivalent circuit



4.42 (partial) An npn silicon transistor at room temperature has $\beta = 100$.

Find the corresponding values of g_m and r_π if $I_{C,Q} = 1\text{mA}$.

Assume that the device is operating in the active region.


$$r_\pi = \frac{\beta V_T}{I_{C,Q}} = \frac{(100)(26\text{mV})}{1\text{mA}} = 2600\Omega.$$

$$\beta = g_m r_\pi$$


$$\text{or } g_m = \frac{\beta}{r_\pi} = \frac{100}{2600}$$

Common-emitter amplifier

4.45

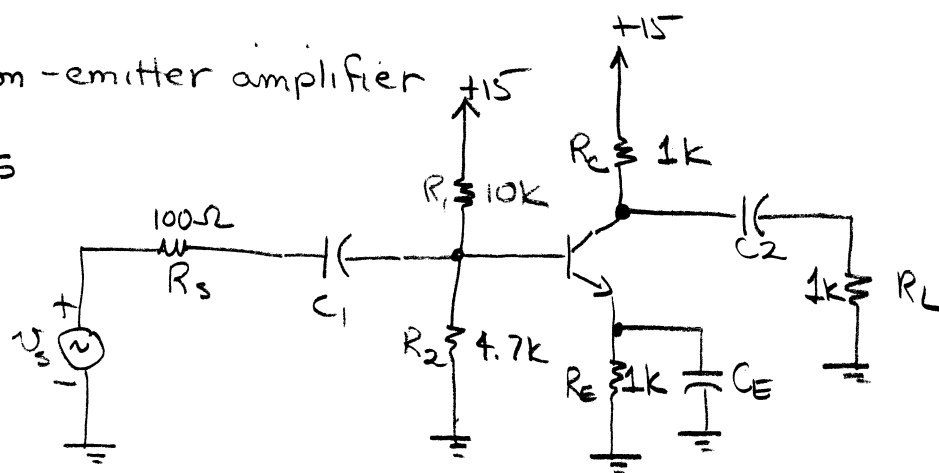


① DC circuit:

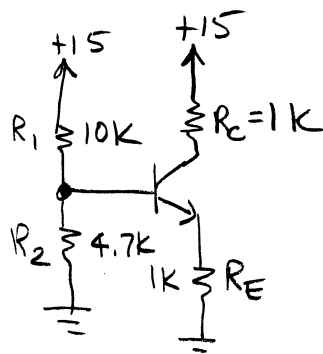

$$\beta = 100$$

$$V_{CE,Q} = 0.7$$


② do Thevenin of the bias circuit

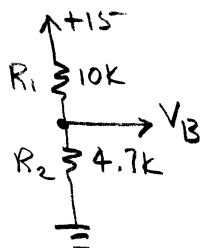

$$V_B = \frac{4.7k}{10k + 4.7k} = 4.796 \text{ Volts}$$

$$R_B = R_1 \parallel R_2 = \frac{(10k)(4.7k)}{10k + 4.7k} = 3.197k$$

③ Determine \$I_B\$

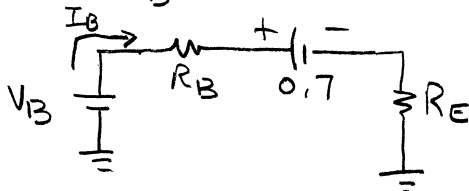

Doing KVL

$$-V_B + I_B R_B + 0.7 + (\beta + 1) I_B R_E$$

$$I_B = \frac{V_B - 0.7}{R_B + (\beta + 1) R_E}$$

$$= \frac{4.796 - 0.7}{3.197k + (100 + 1)(1k)}$$

$$I_B = 39.3 \mu A$$


④ Determine Q-point

$$I_{C,Q} = \beta I_{B,Q} = (100)(39.3 \mu A) = 3.93 \text{ mA}$$

$$V_{CE,Q} = V_{CC} - I_{C,Q} R_c - (\beta + 1) I_{B,Q} R_E$$

$$= 15 - (3.93)(1) - (101)(0.0393)(1) = 7.10 \text{ V}$$

⑤ Now draw small signal circuit

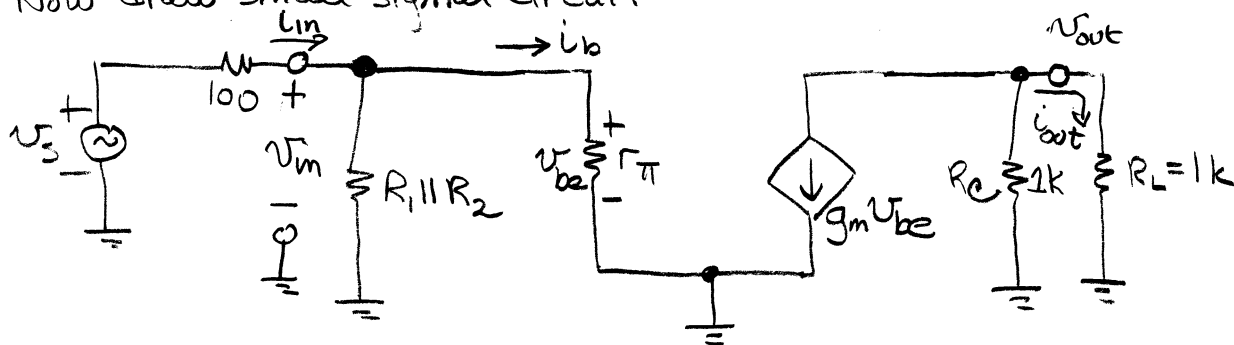

⑥ Compute circuit values

$$R_1 \parallel R_2 = \frac{(10k)(4.7k)}{10k + 4.7k} = 3.198k$$

$$r_{\pi} = \frac{\beta V_T}{I_{C,Q}} = \frac{(100)(26mV)}{3.93mA} = 661.6\Omega$$

$$g_m = \frac{\beta}{r_{\pi}} = \frac{100}{661.6\Omega} = 0.151V$$

⑦ Calculate v_{be}

In this case $v_{be} = v_{in} = \frac{(R_1 \parallel R_2) \parallel r_{\pi}}{(R_1 \parallel R_2) \parallel r_{\pi} + 100} v_s$

$$(R_1 \parallel R_2) \parallel r_{\pi} = \frac{(3198)(661.6)}{3198 + 661.6} = 548.2$$

$$v_{be} = \frac{548.2}{548.2 + 100} v_s = 0.846 v_s$$

⑧ Calculate v_{out}

$$\begin{aligned} v_{out} &= (-g_m v_{be})(R_C \parallel R_L) \\ &= (-0.151)(v_{in})\left(\frac{(1k)(1k)}{1k + 1k}\right) \\ &= -75.5 v_{in} \end{aligned}$$

Note: $v_{be} = v_{in}$

⑨ calculate A_v

$$A_v = \frac{v_{out}}{v_{in}} \approx -75.5$$

Note you could have computed this using βi_b as well ■

⑩ Compute no load gain

$$v_o = -g_m v_{be} R_c = -(0.151)(v_{in})(1000)$$

$$= -151 v_{in}$$

$$A_{v_o} = \frac{v_o}{v_{in}} = -151$$

⑪ Calculate input impedance

$$Z_{in} = \frac{v_{in}}{i_{in}} \leftarrow \text{Note that } v_{in} = 0.846 v_s$$

we know v_{in} and must calculate i_{in} .

$$i_{in} = \frac{v_s}{100 + (R_1 \parallel R_2) \parallel r_{\pi}} = \frac{v_s}{100 + \frac{(3198)(661.6)}{3198 + 661.6}}$$

$$= \frac{v_s}{648.2 \Omega}$$

$$\therefore Z_{in} = \frac{0.846 v_s}{\frac{v_s}{648.2 \Omega}} = (0.846)(648.2)$$

$$= 548.4 \Omega$$

] since all done in terms of v_s this is OK.

⑫ Calculate current gain

$$A_i = \frac{i_{out}}{i_{in}} = \frac{v_{out}/R_L}{v_{in}/Z_{in}} = \frac{v_{out}}{v_{in}} \frac{Z_{in}}{R_L}$$


Note: R_L rather than R_L' because of where we defined the output

$$A_i = A_v \frac{Z_{in}}{R_L} = (-75.5) \frac{548.4 \Omega}{1000 \Omega} = -41.4$$

⑬ Power gain

$$A_p = A_v A_i = (-75.5)(-41.4) = 3126$$

⑭ Output impedance.

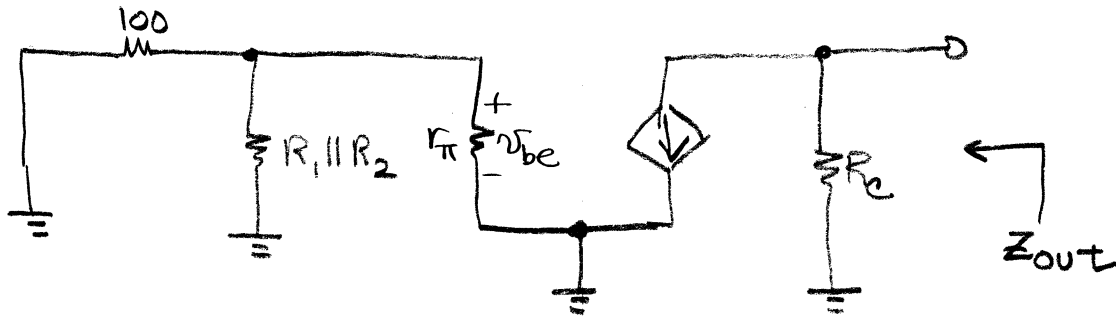


Z_{out} defined to be when $v_s = 0$.


If $v_s = 0$ then $v_{be} = 0$ and $g_m v_{be} = 0$

$$\therefore Z_{out} = R_C = 1k\Omega$$

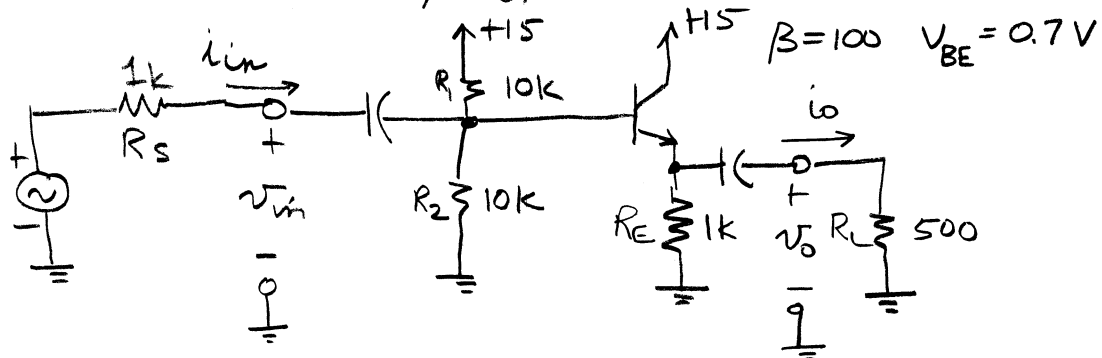
4.51 Consider the emitter follower amplifier. Draw the DC circuit and find $I_{E,Q}$. Find the value of r_{π} . Then calculate midband values for A_v , A_{v_o} , A_i , G and Z_o .



DC circuit

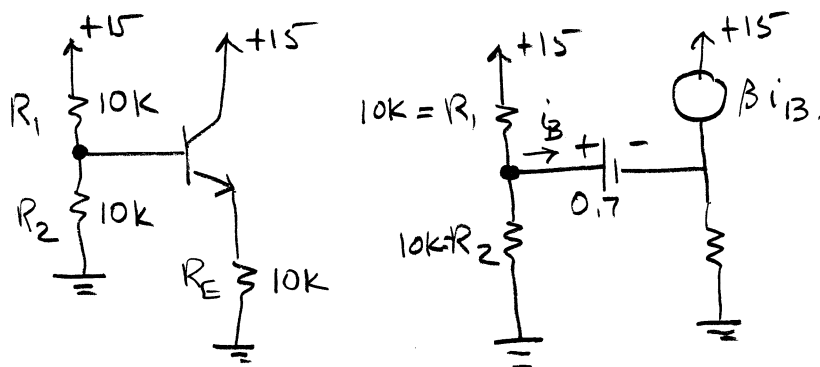

Thevenize input

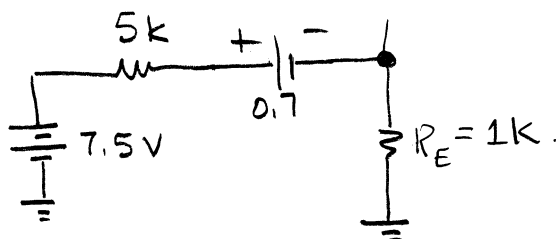

doing KCL $-7.5 + i_B(5k) + 0.7 + (\beta i_B)(1k) = 0$

$$i_B (5k + \beta(1k)) = 7.5 - 0.7$$

$$i_B = \frac{7.5 - 0.7}{5k + 100(1k)} = \frac{6.8}{105k} = 0.065 \text{ mA}$$

$$i_B = 65 \mu\text{A}$$

$$I_{C,Q} = \beta i_B = 6.47 \text{ mA}$$

$$I_{E,Q} = (\beta + 1) i_B = (100 + 1)(65 \mu\text{A}) = 6.54 \text{ mA}$$


$$V_E = i_E R_E = (6.54 \text{ mA})(1k) = 6.54 \text{ V}$$

$$V_{CE,Q} = 15 - 6.54 \text{ V} = 8.45 \text{ V}$$

Now calculate small signal parameters.

$$r_{\pi} = \frac{\beta V_T}{I_{C,Q}} = \frac{(100)(26\text{mV})}{6.476\text{mA}} = 401.5\Omega$$

Now draw small signal circuit

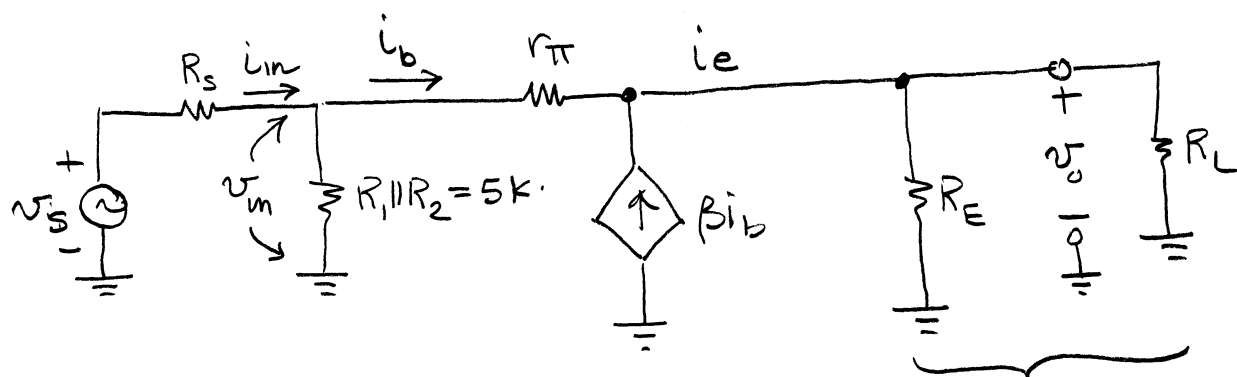

$$R'_L = R_E \parallel R_L = \frac{(1000)(500)}{1000 + 500} = 333\Omega$$

voltage gain:

$$\text{write } v_o = i_e R'_L = (\beta + 1) i_b R'_L$$

then do KVL

$$-v_{in} + i_b r_{\pi} + (1 + \beta) i_b R'_L = 0.$$

eliminate i_b

$$v_{in} = i_b [r_{\pi} + (\beta + 1) R'_L]$$

$$v_o = i_b [(\beta + 1) R'_L].$$

$$\begin{aligned} \therefore A_v &= \frac{v_o}{v_{in}} = \frac{(\beta + 1) R'_L}{r_{\pi} + (\beta + 1) R'_L} = \frac{(101) 333}{401.5 + (101)(333)} \\ &= \frac{33667}{401.5 + 33667} = 0.988 \quad (\text{typical}). \end{aligned}$$

$$A_{v_o} = \frac{v_o}{v_{in}} = \frac{i_b (\beta+1) R_E}{i_b [r_{\pi} + (\beta+1) R_E]}$$

$$A_{v_o} = \frac{(\beta+1) R_L}{r_{\pi} + (\beta+1) R_L} = \frac{(101)(1000)}{401.5 + (101)(1000)} = 0.996$$

define the input impedance of the transistor z_{it}

$$z_{it} = \frac{v_{in}}{i_b} = \frac{i_b [r_{\pi} + (\beta+1) R_L']}{i_b}$$

$$z_{it} = r_{\pi} + (\beta+1) R_L' = 401.5 + (101) 333 = 34034.$$

$$z_i = R_B \parallel z_{it} = (5k) \parallel (34034) = \frac{(5)(34,034)}{5 + 34,034} = 4.36k$$

calculate the current gain


$$A_i = \frac{i_{out}}{i_{in}} = \frac{v_{out}/R_L}{v_{in}/z_i} = \frac{v_{out}}{v_{in}} \cdot \frac{z_i}{R_L} = A_v \frac{z_i}{R_L}$$

$$A_i = (0.988) \frac{4360}{500} = 8.61$$

$$G = A_v A_i = (0.988)(8.61) = 8.51$$

Finally calculate the output impedance
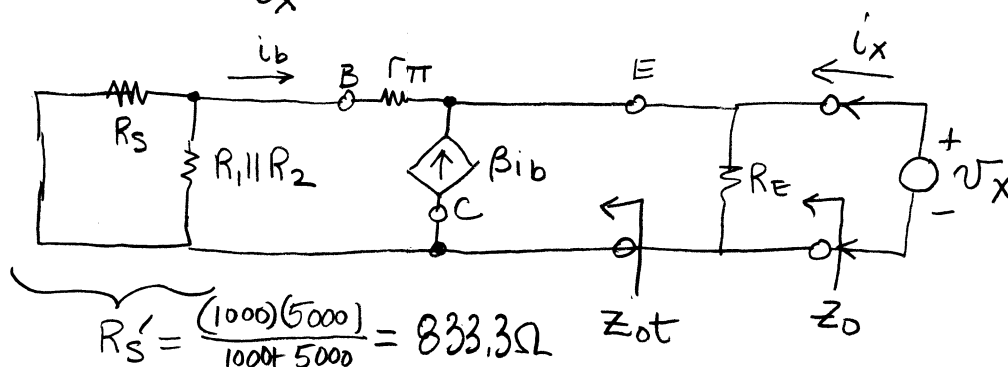
$$z_o \equiv \frac{v_x}{i_x} \text{ where } v_s = 0.$$



/00

Computing the output impedance is pretty complicated.

Write KVL for the outer loop as

$$i_b R_S' + i_b r_{\pi} + v_x = 0 \quad (1)$$

Write KCL for the transistor's emitter

$$i_b + \beta i_b - \frac{v_x}{R_E} + i_x = 0 \quad (2)$$

This gives us two equations which we can use to eliminate i_b

$$\text{From (1)} \quad i_b (R_S' + r_{\pi}) = -v_x \quad \text{or} \quad i_b = \frac{-v_x}{R_S' + r_{\pi}}$$

$$\text{From (2)} \quad i_b + \beta i_b - \frac{v_x}{R_E} + i_x = 0 \quad \text{or} \quad i_b = \frac{v_x}{(\beta+1)R_E} - \frac{i_x}{\beta+1}$$

Equating these results we get

$$\frac{-v_x}{R_S' + r_{\pi}} = \frac{v_x}{(\beta+1)R_E} - \frac{i_x}{\beta+1}$$

$$i_x = \frac{v_x}{R_E} + \frac{v_x}{(R_S' + r_{\pi})/\beta+1} = \left[\frac{1}{R_E} + \frac{1}{\frac{R_S' + r_{\pi}}{\beta+1}} \right] v_x$$

$$\therefore Z_o = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_E} + \frac{1}{\frac{R_S' + r_{\pi}}{\beta+1}}} = R_E \parallel \left(\frac{R_S' + r_{\pi}}{\beta+1} \right)$$

For this amplifier

$$Z_o = R_E \parallel \left(\frac{R_S' + r_{\pi}}{\beta+1} \right) = (1000) \parallel \left(\frac{833.3 + 401.5}{101} \right)$$

$$Z_o = 1000 \parallel 12.22 = \frac{(1000)(12.22)}{1000 + 12.22} = 12.1 \Omega$$