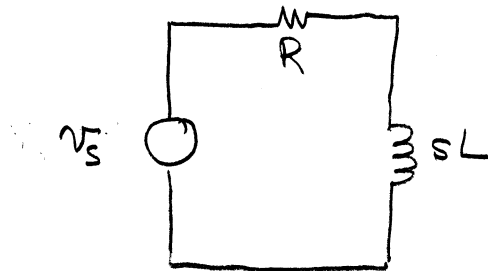


Normally we think of σ as a complex frequency $s = \sigma + j\omega$
 Let's consider responses to exponential functions.




remember $s = \sigma + j\omega$

Consider a source of form $v_s = V_m e^{\sigma t}$

$$\hat{I} = \frac{V_m}{R + \sigma L} = \frac{V_m}{L} \frac{1}{\sigma + \frac{R}{L}}$$

This can be inverse transformed to give $i(t) = \frac{V_m}{L} e^{-\frac{R}{L}t}$


What does $|\hat{I}(s)|$ look like as a function of σ ?

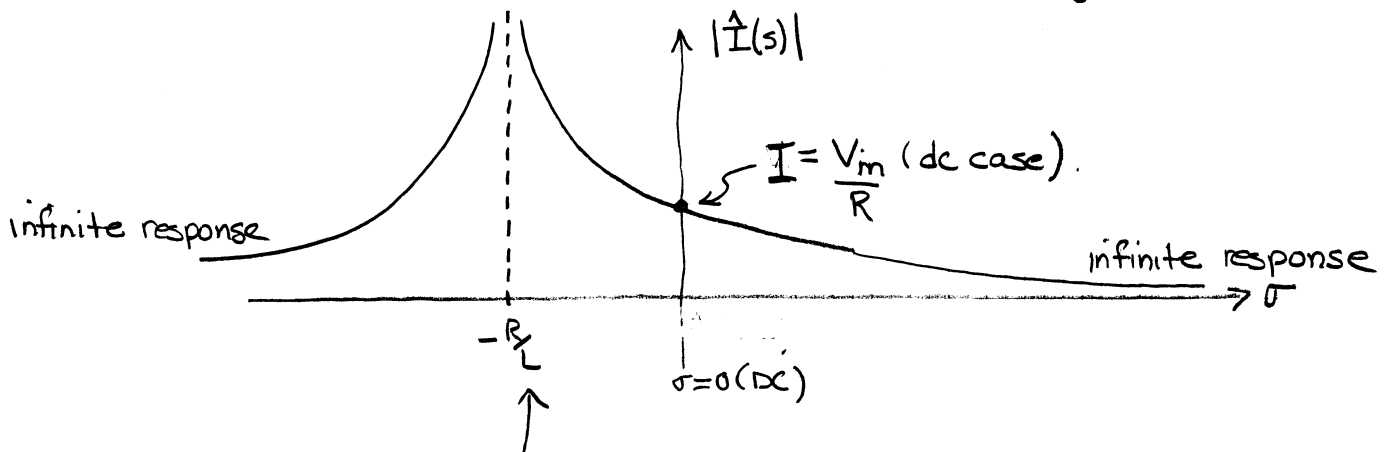

at a pole response $\rightarrow \infty$
 here $|\hat{I}(s)| \rightarrow \infty$ as $s \rightarrow -\frac{R}{L}$

Example

2

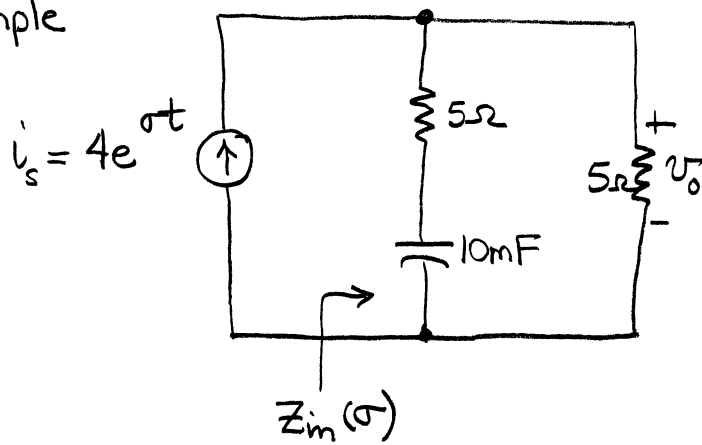

Let's calculate input "impedance" to an exponential.

$$Z_{in}(s) = 5 \parallel \left(5 + \frac{1}{sC}\right) = 5 \parallel \left(5 + \frac{1}{\sigma \cdot 0.01}\right) \quad \text{since } s = \sigma + j\omega$$


$$Z_{in}(\sigma) = \frac{5(5 + 0.01\sigma)}{5 + 5 + 0.01\sigma} = 2.5 \frac{\sigma + 20}{\sigma + 10}$$

What does response look like in σ domain?

$$\hat{v}_o(s) = I_s Z_{in} = (4) \cdot 2.5 \frac{\sigma + 20}{\sigma + 10} = 10 \frac{\sigma + 20}{\sigma + 10}$$


$\uparrow$
 $e^{\sigma t}$ is assumed - just like e^{st}

Now consider this as a function of σ .

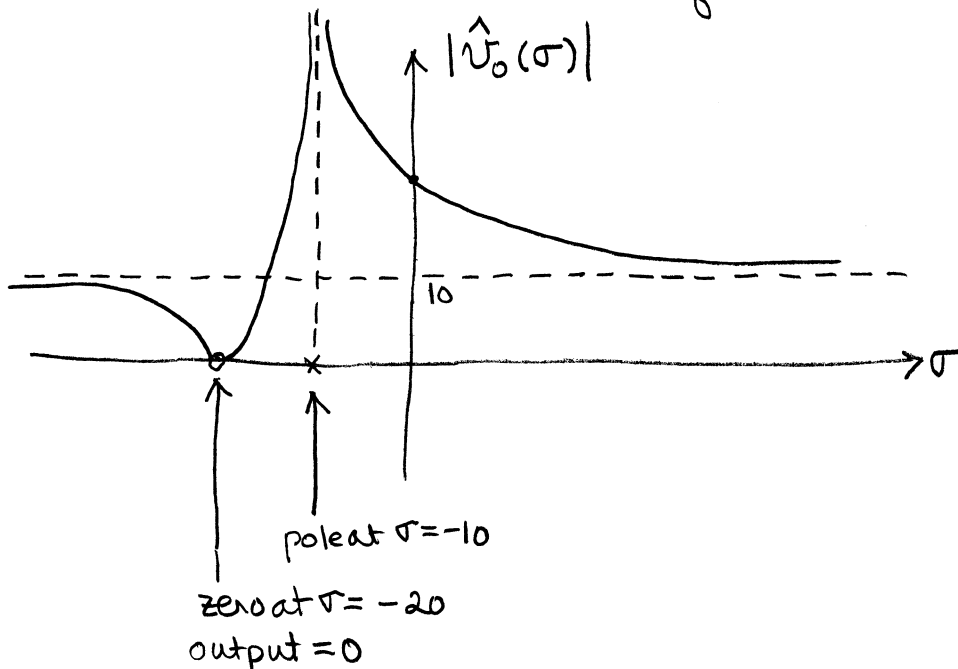

Example

3

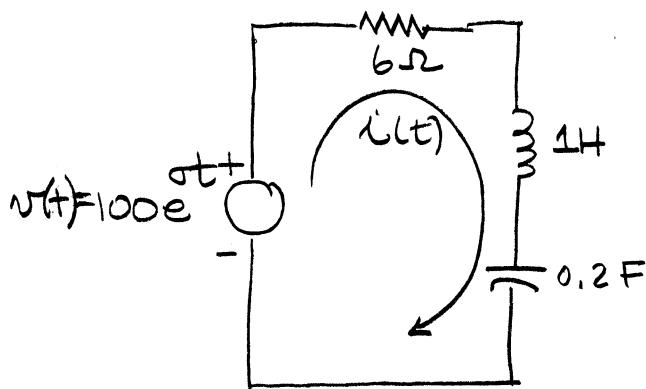


Solving in the s-domain

$$I(s) = \frac{V(s)}{R + sL + \frac{1}{sC}} = \frac{100}{6 + 1 \cdot s + \frac{1}{s(2)}}$$
$$= 100 \frac{1}{6 + s + \frac{5}{s}} = 100 \frac{s}{6s + s^2 + 5}$$

$$I(s) = 100 \frac{s}{(s+1)(s+5)}$$

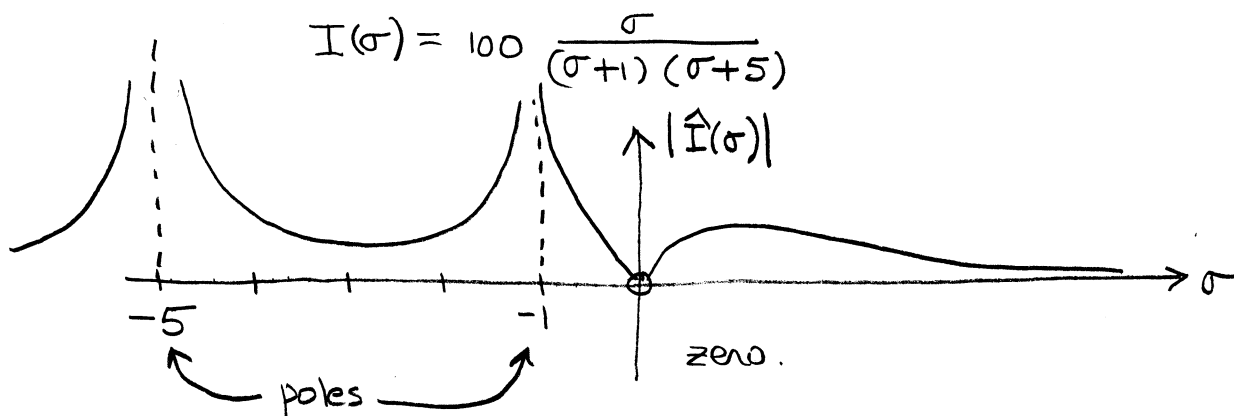Now, since $s = \sigma + j\phi$ in this case




We can calculate forced response for any σ

$$\text{Suppose } \sigma = -3. \text{ Then } \hat{I} = 100 \frac{-3}{(-3+1)(-3+5)} = 100 \frac{-3}{(-2)(2)}$$
$$= +75$$

$$i(t) = 75e^{-3t}$$


Example problem

4

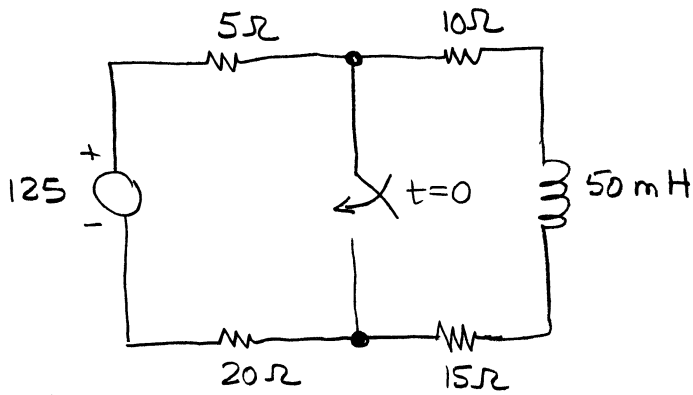

must determine $i_L(0^-)$

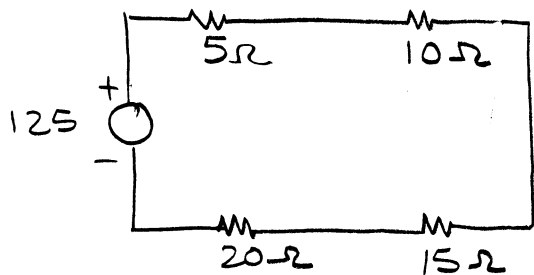
before the switch closes the circuit is this



in dc analysis an inductor becomes a short since $v_L = L \frac{di}{dt} \rightarrow 0$

$$i_L(0^-) = \frac{125V}{5\Omega + 10\Omega + 15\Omega + 20\Omega} = \frac{125}{50} = 2.5A$$

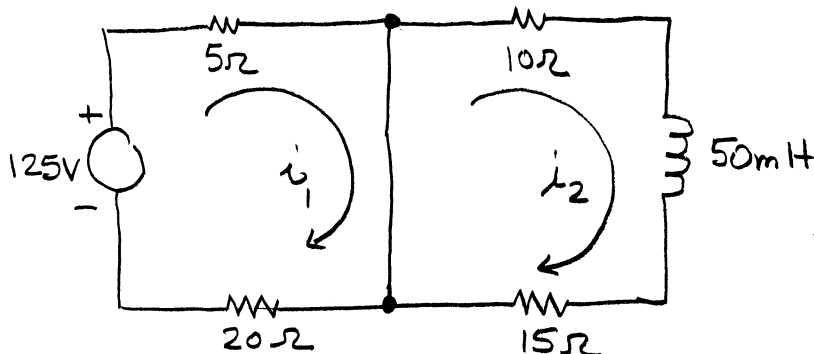Now the switch closes to give this circuit for $t > 0$



doing the left-hand loop

$$-125V + 5i_1 + 20i_1 = 0$$

$$i_1 = 5 \text{ Amps.}$$

There is no voltage contribution thru the short so we see no i_2 .

Now do the second loop. As before there is no voltage contribution from the short.

5

$$+10 i_2 + (50 \times 10^{-3}) \frac{di_2}{dt} + 15 i_2 = 0$$

$$25 i_2 + (50 \times 10^{-3}) \frac{di_2}{dt} = 0$$

Laplace transforming

$$25 I_2(s) + (50 \times 10^{-3}) [s I_2(s) - i_2(0^-)] = 0$$

$$25 I_2(s) + (50 \times 10^{-3}) [s I_2(s) - 2.5] = 0.$$

$$I_2(s) [25 + .05s] - 0.125 = 0$$

$$I_2(s) = \frac{(0.125)}{(.05s + 25)} \frac{20}{20} = \frac{2.5}{s + 500}$$


$$i_2(t) = \mathcal{I}^{-1} \left[\frac{2.5}{s + 500} \right] = 2.5 e^{-500t} u(t).$$

This has the necessary 2.5 Amps at $t=0^+$ and decays to zero as we expect.

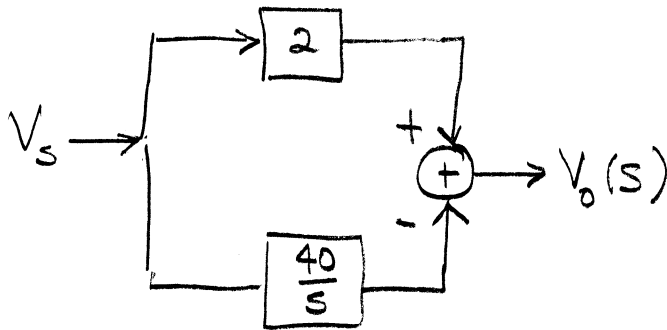9.53 Block diagram of

6

$$(b) \quad V_o(s) = 2V_s(s) - \frac{40}{s} V_s(s)$$



9.50 Use the initial & final value theorems to find the initial and final values of the waveform corresponding to the transforms in 9.26.

9-26 (a) $F(s) = \frac{(s+50)^2}{(s+10)(s+100)}$

! Is not a proper rational function so



cannot compute $f(0) = \lim_{s \rightarrow \infty} s F(s)$

both poles in LHP so we can compute


$$f(\infty) = \lim_{s \rightarrow 0} s F(s)$$

$$= \lim_{s \rightarrow 0} \frac{s(s+50)^2}{(s+10)(s+100)} = 0$$

10-11

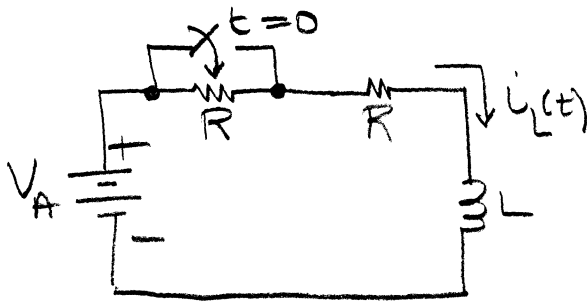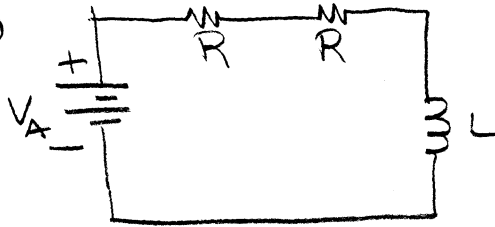 $t < 0$ 

$$i_L(0^-) = \frac{V_A}{2R}$$

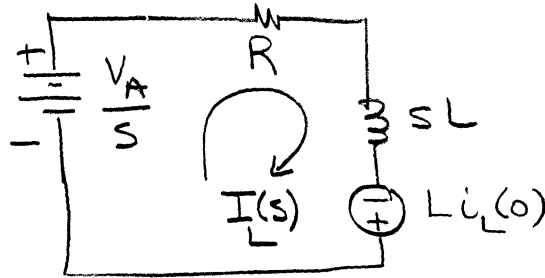 $t > 0$ 


$$-\frac{V_A}{s} + I_L R + sL I_L - L i_L(0) = 0$$

$$I_L = \frac{\frac{V_A}{s} + L i_L(0)}{R + sL} = \frac{\left(\frac{V_A}{s} + L \frac{V_A}{2R}\right) \frac{1}{L}}{(R + sL) \frac{1}{L}}$$


$$I_L = \frac{\frac{1}{s} \left(V_A \frac{1}{L} + \frac{V_A}{2R} s\right)}{\frac{R}{L} + s} = \frac{V_A \left(\frac{1}{L} + \frac{s}{2R}\right)}{s \left(s + \frac{R}{L}\right)}$$

10-15.

8

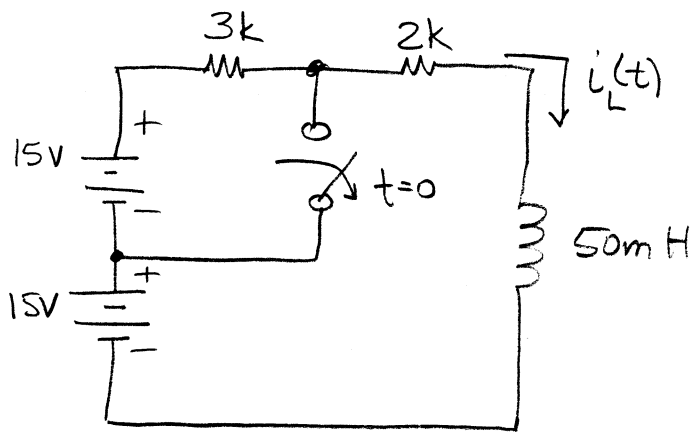


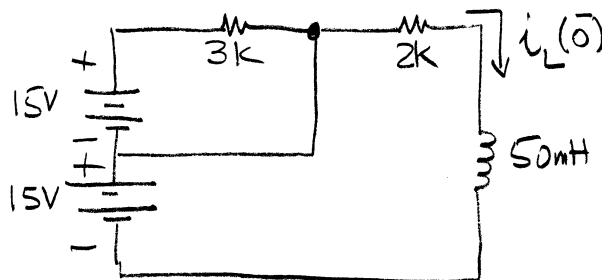for $t < 0$ switch is closed. In this configuration



$$i_L(0^-) = \frac{15V}{2k} = 7.5mA$$

for $t > 0$ the switch is open

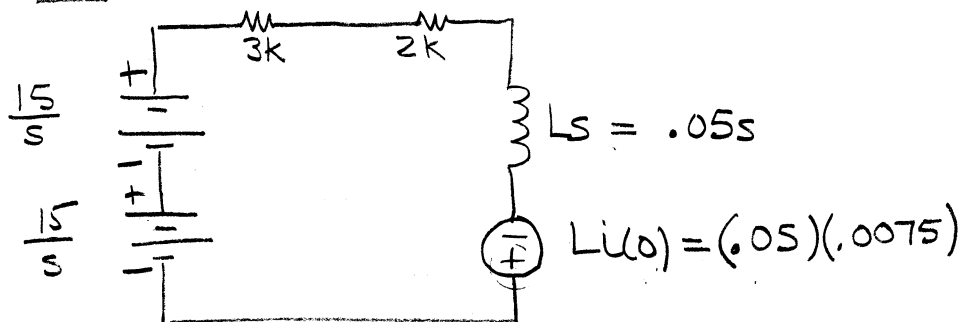

Note: (1) switch explicitly included on voltage sources
(2) initial condition explicitly showed

$$I_L(s) = \frac{\frac{15}{s} + \frac{15}{s} + (.05)(.0075)}{5000 + .05s}$$


$$= \frac{\left(\frac{30}{s} + .000375\right)}{(5000 + .05s)} \cdot \frac{\frac{1}{.05}}{\frac{1}{.05}} = \frac{\frac{600}{s} + .0075}{100000 + s}$$

$$I_L(s) = \frac{600 + .0075s}{s(s + 100000)} = \frac{.006}{s} + \frac{.0015}{s + 100,000} \quad \left[\text{using cover up algorithm} \right]$$

$$i_L(t) = .006 u(t) + .0015 e^{-100,000t} u(t)$$


10-17

9

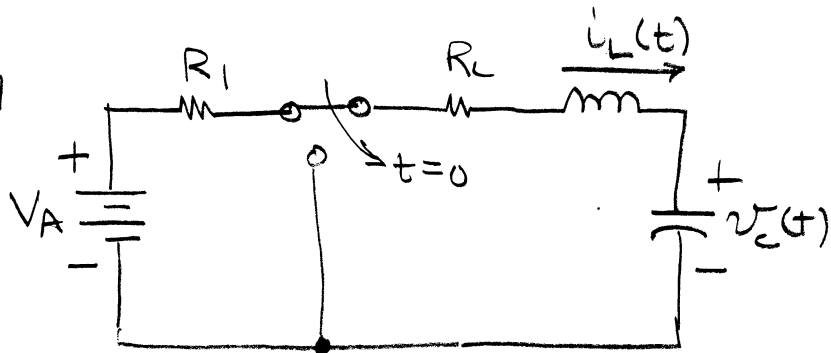

(a) $t < 0$ the initial conditions are $i_L(0^-) = 0$, $v_C(0^-) = V_A$

for $t > 0$ in symbolic form

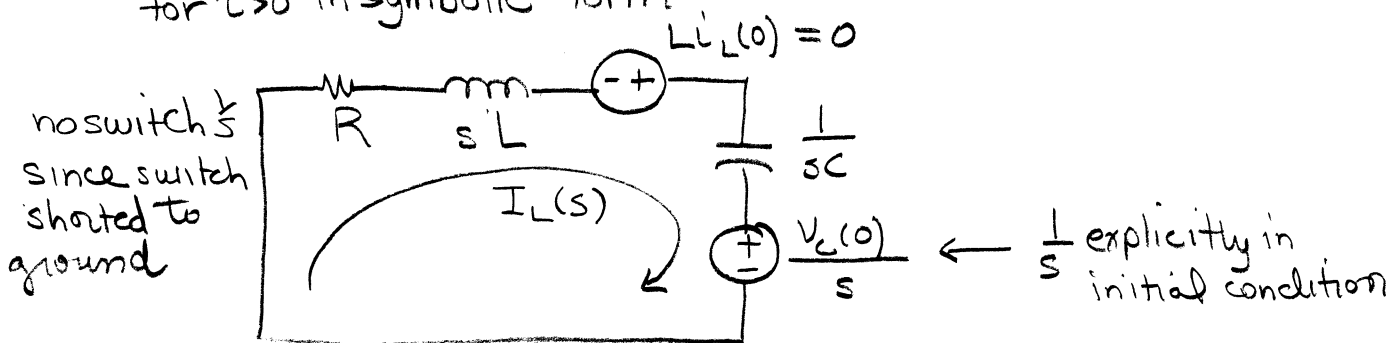


using KVL

$$I = \frac{-\frac{v_C(0)}{s}}{R + sL + \frac{1}{sC}} \quad \text{since other source is zero}$$

$$= \frac{\left(-\frac{V_A}{s}\right) sC}{\left(R + sL + \frac{1}{sC}\right) sC} = \frac{-V_A C}{s^2 LC + sRC + 1}$$

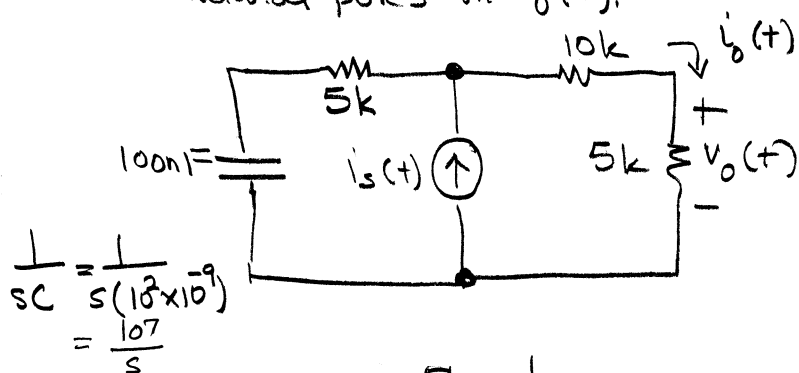10.23 There is no energy stored in the capacitor in Figure 10-23 at $t=0$. Transform the circuit into the s -domain and use current division to find $v_o(t)$ when $i(t) = 0.1 e^{-100t} u(t)$. Identify the forced and natural poles in $v_o(s)$.



$$I_o(s) = \frac{5k + \frac{1}{sC}}{\left(5k + \frac{1}{sC}\right) + (5k)} I_s(s)$$

$$= \left[\frac{5000 + \frac{10^7}{s}}{5000 + \frac{10^7}{s} + 5000} \right] \left[\frac{0.1}{s+100} \right]$$

$$= \frac{5000s + 10000000}{20000s + 10000000} \left(\frac{0.1}{s+100} \right)$$

$$= \frac{5s + 10000}{20s + 10000} \left(\frac{0.1}{s+100} \right) = \frac{s + 2000}{(4s + 2000)(s+100)}$$

$$= \frac{0.25(s+2000)(0.1)}{(s+500)(s+100)} = \frac{0.025(s+2000)}{(s+500)(s+100)}$$

$$V_o(s) = 5000 I_o(s) = \frac{125(s+2000)}{(s+500)(s+100)} = \left[\frac{a}{s+500} + \frac{b}{s+100} \right] 125$$

$$as + 100a + bs + 500b = s + 2000$$

$$a + b = 1$$


$$a + 5b = 20$$

$$-4b = -19$$

$$b = \frac{19}{4} \quad a = 1 - b = 1 - \frac{19}{4} = \frac{4-19}{4} = -\frac{15}{4}$$

$$V_o(s) = \frac{125 \left(-\frac{15}{4} \right)}{s+500} + \frac{125 \left(\frac{19}{4} \right)}{s+100} \quad \text{or} \quad v_o(t) = -468.8e^{-500t} + 593.8e^{-100t}$$

natural.
forced

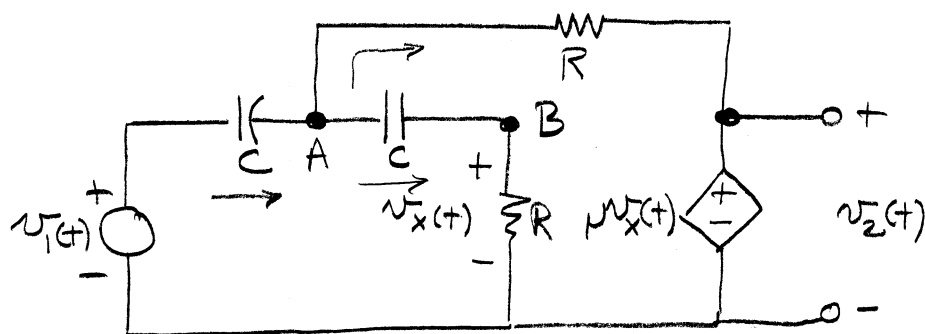

(a) Transform the circuit into the s-domain and find the circuit determinant

Use two nodes A & B.

$$\text{KCL @ A} \quad \sum i = 0 \quad \frac{v_1 - v_A}{\frac{1}{sC}} - \frac{v_A - v_B}{\frac{1}{sC}} - \frac{v_A - \mu v_B}{R} = 0$$

$$\text{KCL @ B} \quad \sum i = 0 \quad + \frac{v_A - v_B}{\frac{1}{sC}} - \frac{v_B - 0}{R} = 0$$

$$\begin{aligned} \left[-sC - sC - \frac{1}{R}\right]v_A + \left[sC + \mu/R\right]v_B + sCv_1 &= 0 \\ + sCv_A + \left[-sC - \frac{1}{R}\right]v_B &= 0 \end{aligned}$$

Rearranging

$$\left[\frac{1}{R} + 2sC\right]v_A - \left[\frac{\mu}{R} + sC\right]v_B = sCv_1$$

$$[sC]v_A + \left[sC + \frac{1}{R}\right]v_B = 0$$

circuit matrix

$$\begin{bmatrix} \frac{1}{R} + 2sC & -(\frac{\mu}{R} + sC) \\ -sC & \frac{1}{R} + sC \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} sCv_1 \\ 0 \end{bmatrix}$$

The determinant is

$$\Delta(s) = \det \begin{bmatrix} \frac{1}{R} + 2sC & -(\frac{\mu}{R} + sC) \\ -sC & \frac{1}{R} + sC \end{bmatrix}$$

$$\Delta(s) = \frac{(RC)^2 s^2 + (3-\mu)RCs + 1}{R^2} \quad v_A \text{ \& } v_B \text{ are of the form } \frac{\Delta}{\Delta(s)}$$

(b) Select R, C \& μ so the circuit has poles at $s = \pm j5000$

The zeros of $\Delta(s)$ are the poles of solutions for v_A and v_B .

For $\Delta(s)$ to be a zero let's require $\mu = 3$


Then $(RC)^2 s^2 + 1 = 0$

$$s^2 = \frac{1}{(RC)^2} \quad \text{or} \quad s = \frac{1}{RC} = 5000$$

$\therefore$ pick $C = 20 \text{ nF}$

$$\text{Then } R = \frac{1}{5000 C} = \frac{1}{(5 \times 10^3)(20 \times 10^{-9})}$$

$$= \frac{1}{10^{-4}} = 10^4$$

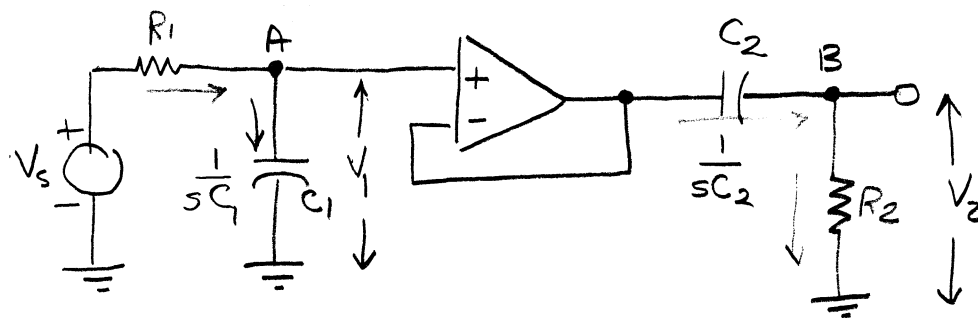

(a) Do KCL @ node A

$$\frac{V_s - V_1}{R_1} - \frac{V_1 - 0}{\frac{1}{sC_1}} = 0 \quad \frac{V_s}{R_1} = \frac{V_1}{R_1} + sC_1 V_1$$

Do KCL @ node B

$$\frac{V_1 - V_2}{\frac{1}{sC_2}} - \frac{V_2 - 0}{R_2} = 0 \quad sC_2 V_1 = sC_2 V_2 + \frac{V_2}{R_2}$$

Solving $V_s = V_1 (1 + R_1 C_1 s) \quad \therefore V_1 = \frac{V_s}{1 + R_1 C_1 s}$

$$sR_2 C_2 V_1 = sR_2 C_2 V_2 + V_2 \quad V_2 = \frac{R_2 C_2 s}{1 + R_2 C_2 s} V_1$$

$$V_2(s) = \frac{R_2 C_2 s}{1 + R_2 C_2 s} \cdot \frac{1}{1 + R_1 C_1 s} V_s$$

poles at $S = -\frac{1}{R_1 C_1} = \frac{-1}{(10^4)(50 \times 10^{-9})} \quad S = -\frac{1}{R_2 C_2} = \frac{-1}{(10^4)(100 \times 10^{-9})}$

$$S = -2000$$

$$S = -1000$$


(b) If $V_s = 10u(t)$

$$V_1(s) = \frac{V_s}{1 + \frac{s}{2000}} = \frac{2000}{s + 2000} \cdot \frac{1}{s}$$

natural pole forced pole

(c) $V_2(s) = \frac{\frac{s}{1000}}{1 + \frac{s}{1000}} \cdot \frac{2000}{s + 2000} \cdot \frac{1}{s} = \frac{\cancel{s}}{s + 1000} \cdot \frac{2000}{s + 2000} \cdot \frac{1}{s}$

two natural poles
forced pole canceled

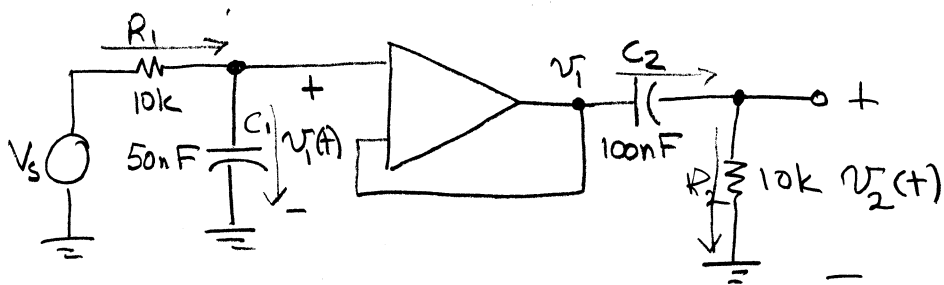

(a) What are the natural poles of this circuit?

At input

$$+\frac{V_s - V_1}{R_1} - \frac{V_1 - 0}{\frac{1}{sC_1}} = 0$$

at output

$$+\frac{V_1 - V_2}{\frac{1}{sC_2}} - \frac{V_2 - 0}{R_2} = 0$$

@ input

$$\frac{V_s}{R_1} = \frac{V_1}{R_1} + sC_1 V_1 = \frac{V_1 (1 + sR_1 C_1)}{R_1}$$

$$\therefore V_1 = \frac{V_s}{1 + sR_1 C_1}$$

@ output

$$sC_2 V_1 - sC_2 V_2 - \frac{V_2}{R_2} = 0$$

$$sR_2 C_2 V_1 - sR_2 C_2 V_2 - V_2 = 0$$

$$sR_2 C_2 V_1 = V_2 (1 + sR_2 C_2)$$

$$V_2 = \frac{R_2 C_2 s}{R_2 C_2 s + 1} V_1$$

$$V_o(s) = \left[\frac{R_2 C_2 s}{R_2 C_2 s + 1} \right] \left[\frac{1}{R_1 C_1 s + 1} \right] V_s$$

poles at $s = -\frac{1}{R_2 C_2} = -\frac{1}{(10^4)(10^2 \times 10^{-9})} = -\frac{1}{10^{-3}} = -1000$

$$s = -\frac{1}{R_1 C_1} = -\frac{1}{(10^4)(5 \times 10 \times 10^{-9})} = -\frac{1}{5} \times 10^4 = -2 \times 10^4 = -20000$$

$$R_1 C_1 = 5 \times 10^{-4}$$

$$R_2 C_2 = 10^{-3}$$