

Chapter 5 Field Effect Transistors (FET)

most common

enhancement mode metal-oxide-semiconductor
(MOSFET)

other types

depletion mode metal-oxide-semiconductor (also MOSFET)

junction field effect transistor (JFET)

MOSFET's


smaller size

fewer processing steps

BJT's

larger currents

Basic structure of a MOSFET

 


L, W define the area of the gate

$0.2 \leq L \leq 10 \mu\text{m}$ $0.5 \leq W \leq 500 \mu\text{m}$



silicon oxide layer $0.05 - 0.1 \mu\text{m}$ thick

IC designer can adjust L, W

Circuit symbol

 

Operation in the cutoff region

 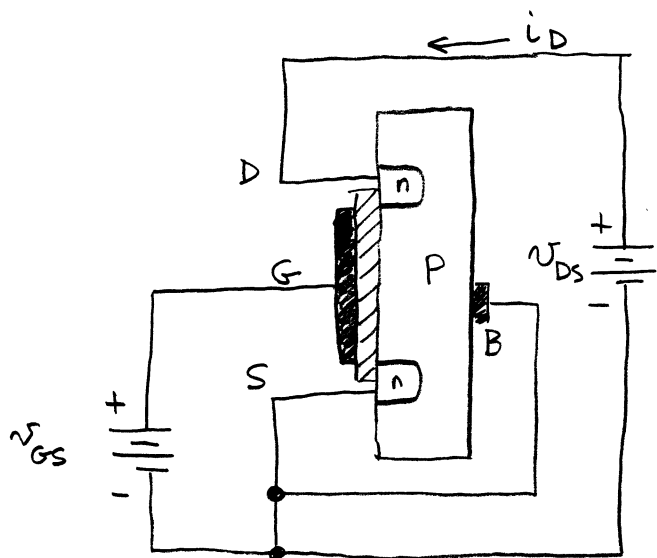



There are p-n junctions at drain-body & source-body
 Drain-source junction is reverse biased so $i_D \approx 0$
 and we say the device is cutoff.

When V_{GS} reaches a threshold voltage V_{to}
 a channel of n-type material is "induced" in the
 region under the gate.

$$i_D = 0 \text{ for } V_{GS} \leq V_{to}$$

Operation in the triode region

10

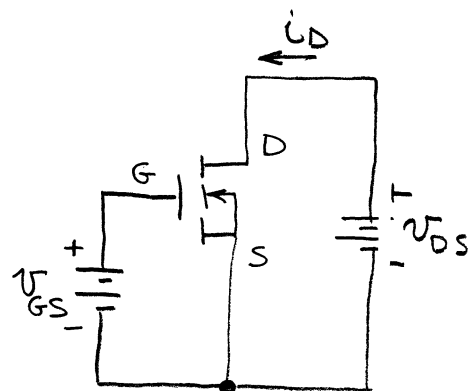 


triode region
 $V_{GS} \geq V_{to}$
 $V_{DS} < V_{GS} - V_{to}$

The electric field from the gate repels holes and attracts electrons (which can flow in the forward direction across :- B) "inducing" a virtual channel under the gate.

For small values of V_{DS} , $i_D \propto V_{DS}$

 It's also proportional to the excess gate voltage $V_{GS} - V_{to}$





In the triode region

$$i_D = K \left[2(V_{GS} - V_{to})V_{DS} - V_{DS}^2 \right]$$
 where $K = \left(\frac{W}{L} \right) \frac{K_P}{2}$ ← process dependent

In this region MOSFETs behave like voltage-controlled resistors.

If V_{DS} increases, the channel "thickness" will vary with position. Because $V_{Gchannel}$ decreases as we get closer to the drain the channel tapers. This leads to saturation.

Operation in the saturation region

  


In the saturation region

$$i_D = k(V_{GS} - V_{to})^2$$

where $V_{GS} \geq V_{to}$

$$V_{DS} \geq V_{GS} - V_{to}$$

MOSFET characteristics

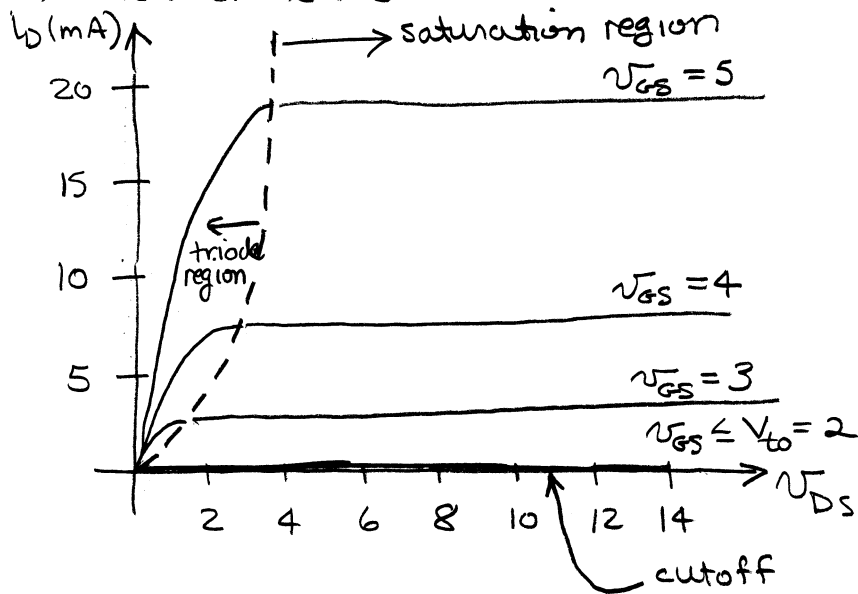

The channel thickness at the drain is zero when $V_{GD} = V_{to}$.

$$V_{GD} = V_{to}$$

$$V_{GS} - V_{DS} = V_{to}$$

$$V_{GS} = V_{to} + V_{DS}$$

But $i_D = K(V_{GS} - V_{to})^2$ in saturation

substituting

$$i_D = K(V_{to} + V_{DS} - V_{to})^2 = K V_{DS}^2$$

which is the equation of the parabola plotted above.

PSpice modeling of MOSFETs

To model MOSFETs we need to add a new parameter ?

For short channels the channel length L can be modified by the depletion region around the drain becoming thicker. This effectively decreases the channel length as v_{DS} increases.

Use breakout part Mbreak N3

Use edit/model/edit instance model

Enter


model MName NMOS

KP = 50 μ


$V_{to} = 2$

LAMBDA = 0.05

Do a DC nested sweep.

 

5.2 Load-line analysis of NMOS amplifier

 


KVL on input loop: $-V_{GG} - v_{in}(t) + v_{GS}(t) = 0$

or $v_{GS}(t) = V_{GG} + v_{in}(t)$

KVL on drain loop: $-v_{DS} - i_D R_D + V_{DD} = 0$

or $V_{DD} = v_{DS}(t) + R_D i_D(t)$

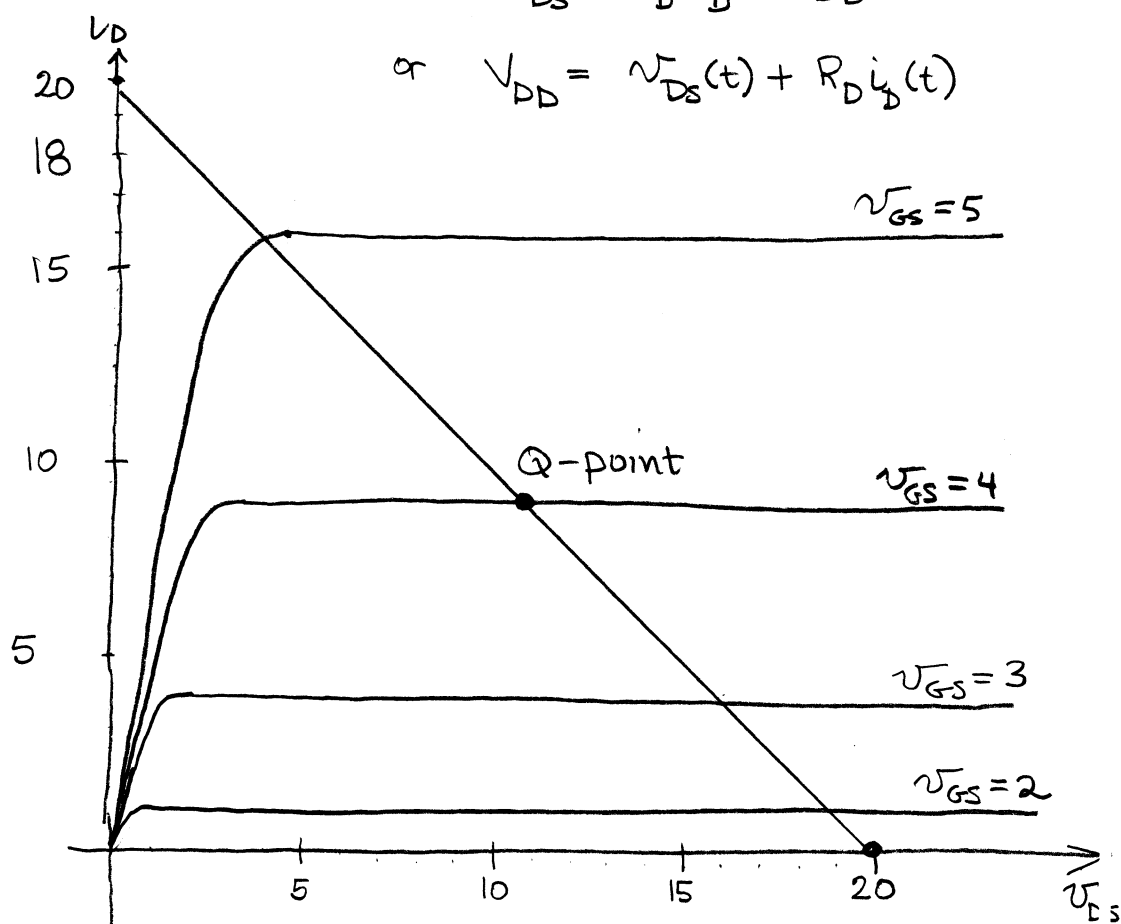

For load line $V_{oc} = 20V$, $I_{sc} = \frac{V_{DD}}{R_D} = \frac{20V}{1k} = 20mA$
 If $v_{in} = 0$ $v_{GS} = V_{GG} = 4V$ establishing Q-point.

Now let v_{in} vary.

For $v_{in} = +1$ volt, we move to $v_{GS} = 1 + 4 = 5$ V.

at $v_{GS} = 5$ on load line

$$v_{DS} = 4 \text{ V}, i_D \sim 15.8 \text{ mA}$$


For $v_{in} = -1$ volt, we move to $v_{GS} = -1 + 4 = 3$ V

at $v_{GS} = 3$ V on load line


$$v_{DS} = 16 \text{ V}, i_D \sim 4 \text{ mA}$$

 5.3 Bias circuits

Because of device to device variation and distortion considerations we use a fixed-plus self bias circuit very similar to that used for BJT amplifiers.



Thevenize gate circuit

 

By inspection

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$


$$R_G = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

For the gate circuit $-V_G + i_G R_G + v_{GS} + i_D R_S = 0$


★ Assuming biased in saturation region $i_D = K(v_{GS} - V_{to})^2$

We can plot this

 load line for gate circuit is called "bias" line



5.22

 

MOSFET has

$$V_{to} = 1V$$

$$\lambda = 0$$

$$K = 0.25 \text{ mA/V}^2$$

Find I_{DQ} , V_{DSQ}

Do KVL of gate circuit

$$+i_G R_G + v_{GS} + i_S R_S - 15 = 0,$$

$$v_{GS} + i_S R_S = 15$$

$$\text{but } i_D = K (v_{GS} - V_{to})^2 \text{ and, since } i_D = i_S$$

$$\text{substituting } \therefore v_{GS} + K (v_{GS} - V_{to})^2 R_S = 15$$

$$v_{GS} + 0.25 \frac{\text{mA}}{\text{V}^2} (v_{GS} - 1)^2 (3\text{k}) = 15$$

$$v_{GS} + \frac{3}{4} (v_{GS} - 1)^2 = 15$$

$$4 v_{GS} + 3 (v_{GS}^2 - 2 v_{GS} + 1) = 60$$

$$3 v_{GS}^2 - 2 v_{GS} - 57 = 0$$

$$v_{GS} = \frac{-(-2) \pm \sqrt{(-2)^2 - 4(3)(-57)}}{2(3)}$$

$$= \frac{2 \pm \sqrt{4 + 684}}{6} = \frac{2 \pm \sqrt{688}}{6}$$


$$v_{GS} = +4.7 \text{ V}, -4.04 \text{ V}$$

$$\text{Must be } v_{GS} = +4.7 \text{ Volts. } \Rightarrow i_D = K (v_{GS} - V_{to})^2 = \frac{1}{4} (4.7 - 1)^2 = 3.43 \text{ mA}$$

$$V_{DQ} = 30 - (3.43)(1) - (3.43)(3) = 16.28 \text{ V}.$$

For the circuit shown below $V_{to} = 2V$, $k = 0.3 \text{ mA/V}^2$.

Determine I_D and V_{DS} .

 

$$i_D = k (V_{GS} - V_{to})^2 \text{ in saturation region (1)}$$

$$V_{GS} = V_G - 0 \text{ since source grounded.}$$

$$V_{GS} = 15 - i_D R_D \text{ since } V_G = V_D$$

$$i_D = \frac{15 - V_{GS}}{R_D}$$

$$\therefore \frac{15 - V_{GS}}{5} = 0.3 (V_{GS} - 2)^2 \text{ by substitution into (1)}$$

$$15 - V_{GS} = 1.5 (V_{GS}^2 - 4V_{GS} + 4)$$

$$15 - V_{GS} = 1.5 V_{GS}^2 - 6V_{GS} + 6$$

$$1.5 V_{GS}^2 - 5V_{GS} - 9 = 0.$$

$$V_{GS} = \frac{-(-5) \pm \sqrt{(-5)^2 - 4(1.5)(-9)}}{2(1.5)} = \frac{5 \pm \sqrt{25 + 54}}{3}$$



$$V_{GS} = +4.63, -1.30$$

Pick $V_{GS} = +4.63$ ($V_{GS} > V_{to}$ in saturation region)

Then $i_D = \frac{15 - (4.63)}{5k} = 2.07 \text{ mA}$

$$V_{DS} = 15 - (2.07)(5k) = 4.63V.$$

3.6.2.

 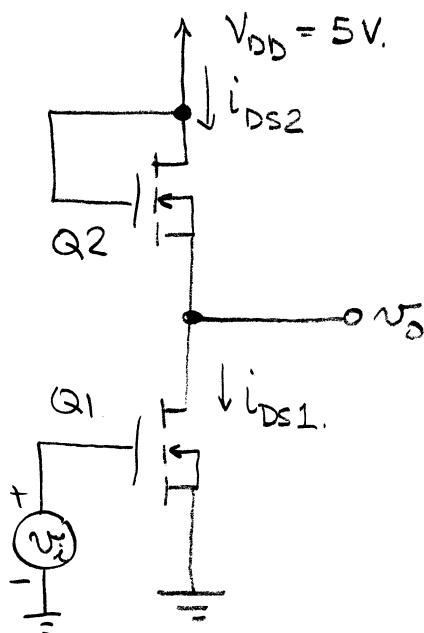

(a) obtain i_{DS1} as a function of v_{DS1}

$$v_{DS2} = V_{DD} - v_{DS1}$$

$$i_{DS2} = K (v_{DS2} - V_{to})^2$$

both transistors
are identical
(Assume saturation)

$$i_{DS2} = K (V_{DD} - v_{DS1} - V_{to})^2$$

(b) The result from (b) represents a non-linear load line for Q1. Plot the load line on the characteristic curve assuming $V_{to} = 1V$ and $K = \frac{3}{16} \times 10^{-3} A/V^2$.

from (a) $i_{DS2} = K(V_{DD} - v_{DS1} - V_{to})^2$

using the problem's values.

$$i_{DS2} = \frac{3}{16} (5 - v_{DS1} - 1)^2 \text{ mA}$$

$$i_{DS2} = \frac{3}{16} (4 - v_{DS1})^2 \text{ mA}$$

Note that $i_{DS2} = i_{DS1}$


$$v_{DS1} = 0 \quad i_{DS2} = \frac{3}{16} (4 - 0)^2 = 3 \text{ mA}$$

$$v_{DS1} = 1 \quad i_{DS2} = \frac{3}{16} (4 - 1)^2 = \frac{27}{16} \text{ mA} = 1.7 \text{ mA}$$


$$v_{DS1} = 2 \quad i_{DS2} = \frac{3}{16} (4 - 2)^2 = \frac{12}{16} \text{ mA} = 0.75 \text{ mA}$$

$$v_{DS1} = 3 \quad i_{DS2} = \frac{3}{16} (4 - 3)^2 = \frac{3}{16} \text{ mA} = 0.1875 \text{ mA}$$

$$v_{DS1} = 4 \quad i_{DS2} = 0$$

 

(c) Plot V_o vs. v_i

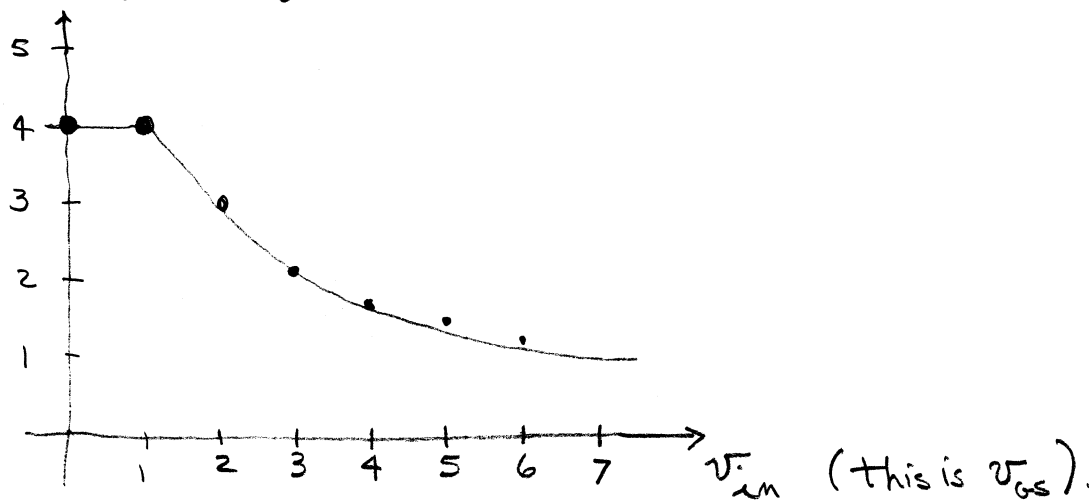

if $v_{in} = 0$ Q_1 is in cutoff since $v_{gs} < v_{to}$
then $V_o = V_{DS1} = 4$ volts.

if $v_{in} = 1$ Q_1 is just turning on, no change
 $V_{DS1} = 4$ volts.

if $v_{in} = 2$ we read off intersection of $v_{gs} = 2$
with non-linear load line.
by inspection $V_{DS1} \cong 3$ V.

if $v_{in} = 3$ $v_{gs} = 3$ and
by inspection $V_{DS1} \cong 2.1$ V.


if $v_{in} = 4$ $v_{gs} = 4$ and by inspection $V_{DS1} \cong 1.75$ V.

if $v_{in} = 5$ $v_{gs} = 5$ and by inspection $V_{DS1} \cong 1.5$ V.


if $v_{in} = 6$ $v_{gs} = 6$ and by inspection $V_{DS1} \cong 1.25$ V.

Technically this could be an NMOS amplifier or inverter

p-channel MOSFETs. (p. 332 of text).

 

 Equations are exactly the same except voltage polarities and current directions are reversed.



5.4 Small-signal equivalent circuits

for small signal analysis let

$$i_D(t) = I_{DQ} + i_d(t) \quad v_{GS}(t) = V_{GSQ} + v_{gs}(t)$$

Assume that the MOSFET is biased in saturation so that

$$i_D = K(V_{GS} - V_{to})^2$$

Substituting the small signal values into this equation gives

$$I_{DQ} + i_d(t) = K[V_{GSQ} + v_{gs}(t) - V_{to}]^2$$

Expanding

$$I_{DQ} + i_d(t) = K[V_{GSQ} - V_{to}]^2 + 2K(V_{GSQ} - V_{to})v_{gs}(t) + K v_{gs}^2(t)$$


$\underbrace{\hspace{10em}}_{\text{DC bias terms cancel}}$

Assume small signal such that $|v_{gs}(t)| \ll |V_{GSQ} - V_{to}|$
 This allows last term to be dropped

$$\therefore i_d(t) = \underbrace{2K(V_{GSQ} - V_{to})}_{\text{define } g_m = 2K(V_{GSQ} - V_{to})} v_{gs}(t)$$

$$\therefore i_d(t) = g_m v_{gs}(t)$$


small-signal equivalent circuit

 

more formally define using Taylor series expansion

$$g_m \equiv \left. \frac{i_d}{v_{gs}} \right|_{v_{ds}=0} = \left. \frac{\partial i_D}{\partial v_{gs}} \right|_{Q\text{-point}}$$

$$\frac{1}{r_d} = \left. \frac{\partial i_D}{\partial v_{ds}} \right|_{Q\text{-point}}$$

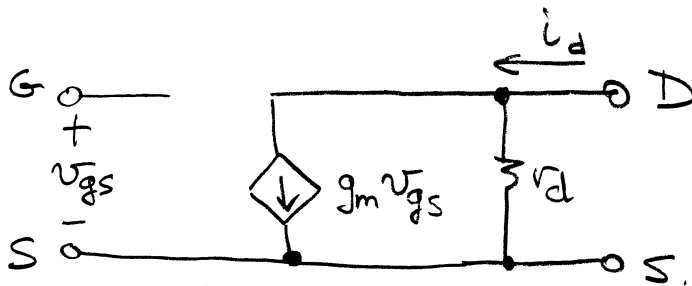


$$i_d(v_{gs}, v_{ds}) = i_d(v_{gsQ}, v_{dsQ}) + \left. \frac{\partial i_d}{\partial v_{gs}} \right|_{Q\text{ point}} \Delta v_{gs} + \left. \frac{\partial i_D}{\partial v_{ds}} \right|_{Q\text{-point}} \Delta v_{ds} + \Delta i_d(v_{gs}, v_{ds})$$

$$\begin{aligned} \therefore \Delta i_d(v_{gs}, v_{ds}) &= \left. \frac{\partial i_D}{\partial v_{gs}} \right| \Delta v_{gs} + \left. \frac{\partial i_D}{\partial v_{ds}} \right| \Delta v_{ds} \\ &= g_m \Delta v_{gs} + \frac{1}{r_d} \Delta v_{ds} \end{aligned}$$

where Δi_D , Δv_{gs} and Δv_{ds} are small signal quantities

5.5 Common Source Amplifier

 

Example 5.28. Analyze in mid-band where
 $v(t) = 100 \sin(2000\pi t)$

Do bias first

Given $K_P = 50 \mu A/V^2$
 $V_{to} = 2V$
 $\lambda = 0$
 $L = 10 \mu m$
 $W = 400 \mu m$


$$K = \left(\frac{W}{L}\right) \frac{K_P}{2} = \left(\frac{400 \mu m}{10 \mu m}\right) \frac{50 \mu A/V^2}{2} = 1 mA/V^2$$

Analyze bias circuit by Thevenize

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = (20V) \frac{1M}{1M + 3M} = 20 \left(\frac{1}{4}\right) = 5V$$

$$R_G = \frac{R_1 R_2}{R_1 + R_2} = \frac{(1M)(3M)}{1M + 3M} = \frac{3}{4} M.$$

bias circuit

 

$$-5V + 750k(I_G) + V_{GS} + I_S R_S = 0$$

$$\therefore V_{GS} + I_{D,Q} R_S = 5$$

$$\text{and } I_{D,Q} = K(V_{GS} - V_{to})^2$$

substituting

$$V_{GS} + K(V_{GS} - V_{to})^2 R_S - 5 = 0.$$

$$V_{GS} + (1 \text{ mA/V}^2)(2.7 \text{ k})(V_{GS} - 2)^2 - 5 = 0$$

$$V_{GS} + 2.7(V_{GS}^2 - 4V_{GS} + 4) - 5 = 0$$

$$2.7V_{GS}^2 - 9.8V_{GS} + 5.8 = 0$$

$$\begin{aligned} V_{GS} &= \frac{-(-9.8) \pm \sqrt{(-9.8)^2 - 4(2.7)(5.8)}}{2(2.7)} \\ &= \frac{9.8 \pm \sqrt{33.4}}{5.4} = \frac{9.8 \pm 5.78}{5.4} \end{aligned}$$

$$V_{GS} = 2.89, 0.79 \text{ V}$$

Choosing $V_{GS,Q} = 2.89$ since $V_{to} = 2 \text{ V}$

$$I_{D,Q} = K(V_{GS} - V_{to})^2 = \frac{1 \text{ mA}}{\text{V}^2} (2.89 - 2)^2 = 0.79 \text{ mA}$$

$$V_{DS,Q} = 20 - (0.79 \text{ mA})(4.7 \text{ k}) - (0.79 \text{ mA})(2.7 \text{ k})$$


$$V_{DS,Q} = 14.15 \text{ Volts}$$

Now do small signal analysis

$$\begin{aligned} g_m &= \sqrt{2KP} \sqrt{\frac{W}{L}} \sqrt{I_{D,Q}} \\ &= \sqrt{2(1.05 \frac{\text{mA}}{\text{V}^2})} \sqrt{\frac{400 \mu\text{m}}{10 \mu\text{m}}} \sqrt{0.79 \text{ mA}} = 1.78 \text{ mS} \end{aligned}$$

$$\text{because } \lambda = 0 \quad r_d = \infty$$

In midband

 

$$R_L' = \frac{(4.7k)(10k)}{4.7k + 10k} = 3197\Omega$$

By inspection

$$v_o = -g_m v_{GS} R_L'$$

$$= -(0.00178) v_{GS} (3197) = -5.69 v_{GS}$$


$$\frac{v_o}{v_{in}} = -\frac{5.69 v_{GS}}{v_{in}} = -5.69 \frac{v_{in}}{v_{in}} = -5.69$$

$$R_{in} = \frac{v_{in}}{i_{in}} = 750k$$

$$R_o = \left. \frac{v_o}{i_o} \right|_{\text{looking into amp.}} = \frac{+g_m v_{GS} R_D}{g_m v_{GS}} = 4.7k$$

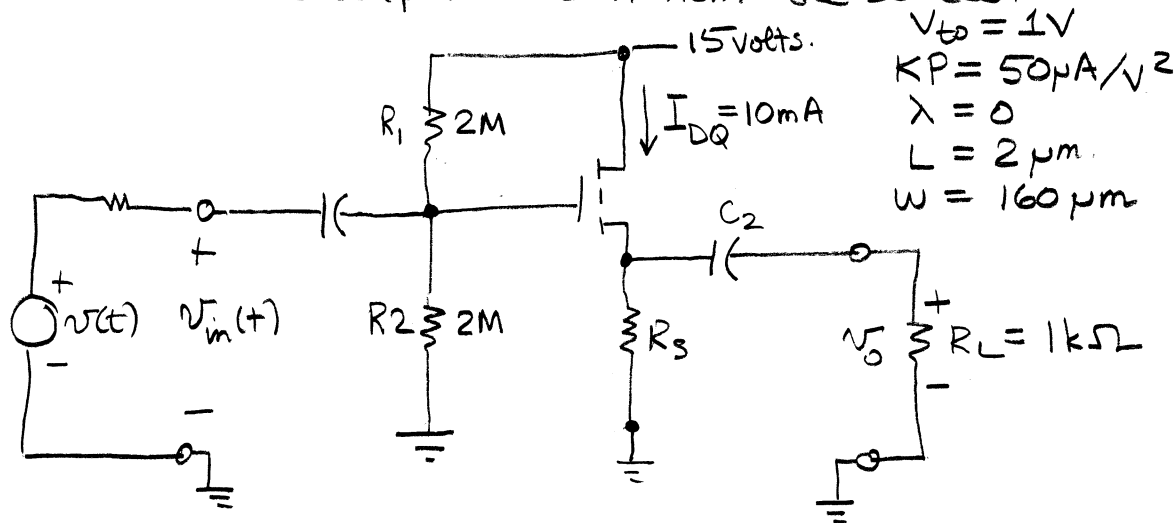5.6 The Source Follower

This is basically identical to the common source analysis EXCEPT the output is taken from the source.



DC Analysis: $K = \left(\frac{W}{L}\right) \frac{K_P}{2} = \left(\frac{160\mu\text{m}}{2\mu\text{m}}\right) \frac{50\mu\text{A}/\text{V}^2}{2} = 2\text{mA}/\text{V}^2$

Now let's calculate the V_{GS} that gives $I_{DQ} = 10\text{mA}$

$$I_D = K (V_{GS} - V_{to})^2$$

$$10\text{mA} = 2\text{mA}/\text{V}^2 (V_{GS} - 1)^2$$

$$5\text{V}^2 = (V_{GS} - 1)^2$$

$$\pm\sqrt{5} = V_{GS} - 1$$

$$V_{GS} = 1 \pm \sqrt{5} = 3.236, -1.236$$

choose this solution since $-1.236 < V_{to}$

Now find the gate voltage by Thevenizing as usual

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{2\text{M}}{2\text{M} + 2\text{M}} (15\text{V}) = 7.5\text{V}$$


This gives us the information to calculate R_S .

$$V_{GS} = V_G - V_S$$


$$\text{or } V_S = V_G - V_{GS} = 7.5\text{V} - 3.236\text{V} = 4.264\text{V}$$

$$R_S = \frac{V_S}{I_D} = \frac{4.264\text{V}}{10\text{mA}} = 426\Omega$$

 Now draw the small signal equivalent circuit



 Note that the drain is grounded through the power supply. We can re-arrange this circuit to more easily see the analysis.



Now calculate the small signal parameters

$$g_m = \sqrt{2kP'} \sqrt{\frac{W}{L}} \sqrt{I_{D,Q}} = \sqrt{2(50 \times 10^{-6})} \sqrt{\frac{160}{2}} \sqrt{10 \times 10^{-3}}$$

$$g_m = 8.944 \times 10^{-3} \text{ S}$$

$\lambda = 0 \Rightarrow$ characteristics are flat in saturation region

$$\text{and } \frac{1}{r_d} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_Q = 0$$

Remaining analysis is straight forward;

$$R_L' = R_S \parallel R_L = 426 \parallel 1000 = 298.7 \Omega$$

$$v_o = (+g_m v_{GS}) (R_L') = (+8.944 \times 10^{-3} v_{GS}) (298.7)$$

$$v_o = +2.672 v_{GS}$$

Now do KVL (recall this is v_{GS})

$$-v_{in} + v_{GS} + v_o = 0 \Rightarrow v_{GS} = v_{in} - v_o$$


$$v_o = +2.672 (v_{in} - v_o) = +2.672 v_{in} - 2.672 v_o$$

$$+3.672 v_o = +2.672 v_{in}$$

$$\frac{v_o}{v_{in}} = \frac{+2.672}{3.672} = +0.72$$

$$R_{in} = R_1 \parallel R_2 = 2m \parallel 2m = 1m$$

 The output impedance is a little harder to calculate.



by definition $R_o = \frac{v_x}{i_x}$

by inspection $V_G = 0, V_S = +v_x$
 $V_{GS} = V_G - V_S = -v_x$

Do KCL at output

$$\sum_{\text{in}} i = 0 \quad +g_m(-v_x) - \frac{v_x}{r_d} - \frac{v_x}{R_S} + i_x = 0$$

$$\left(-g_m - \frac{1}{r_d} - \frac{1}{R_S}\right) v_x = -i_x$$

$$R_o = \frac{v_x}{i_x} = \frac{1}{g_m + \frac{1}{r_d} + \frac{1}{R_S}}$$

For this example:


$$R_o = \frac{1}{.00894 + 0 + \frac{1}{426\Omega}} = 88.6\Omega$$

Calculate current gain


$$A_i = \frac{i_o}{i_{in}} = \frac{v_o/R_L}{v_{in}/R_{in}} = \left(\frac{v_o}{v_{in}}\right) \frac{R_{in}}{R_L} = (0.72) \left(\frac{1m}{1000}\right) = 720$$

$$A_p = A_i A_v = (720)(.72) = 518.4$$


4.56

 

 (a) Draw the small signal circuit in midband.



$$\text{define } R_L' = R_1 || R_2 || R_E || R_L$$

 

$$v_o = i_L' R_L'$$

where

$$i_L' = i_x + (\beta + 1) i_b$$

Since r_{π} & R_b have the same voltage across them:

$$v = i_x R_b = i_b r_{\pi} \quad \text{or} \quad i_x = i_b \frac{r_{\pi}}{R_b}$$

$$\text{Then } v_o = (i_x + i_L') R_L' = \left(i_b \frac{r_{\pi}}{R_b} + (\beta + 1) i_b \right) R_L'$$

$$\text{By inspection } v_{in} = i_b r_{\pi} + v_o$$

$$\therefore A_v = \frac{v_o}{v_{in}} = \frac{i_b \left(\frac{r_{\pi}}{R_b} + (\beta + 1) \right) R_L'}{i_b r_{\pi} + i_b \left(\frac{r_{\pi}}{R_b} + (\beta + 1) \right) R_L'}$$

$$A_v = \frac{(1 + \beta + \frac{r_\pi}{R_b}) R_L'}{r_\pi + R_L' (1 + \beta + \frac{r_\pi}{R_b})}$$


To compute R_{in} we need i_{in}

$$i_{in} = \frac{V_{in} - V_o}{R_b \parallel r_\pi} = \frac{V_{in} - A_v V_{in}}{R_b \parallel r_\pi}$$


$$Z_{in} = \frac{V_{in}}{i_{in}} = \frac{V_{in}}{\frac{V_{in} (1 - A_v)}{R_b \parallel r_\pi}} = \frac{R_b \parallel r_\pi}{1 - A_v}$$

 6.2 Electrical Specifications for Logic Gates.

Transfer Characteristics of Logic Inverters




What inverters actually do at the input.

 


Anything above 2.5V at input is a logic 1.


What devices produce at the output;

 

Types of MOS inverter

 


Resistor pull-up

 

active NMOS pull-up.

NOTE

 
Problem occurs when $v_o = \text{High}$.
 $M1$ $v_{GS} = 0$ and load is OFF.
 Makes circuit susceptible to noise in output.



active NMOS pull-up with separate bias source

Separate V_G can eliminate output noise susceptibility

$$V_{GG} > V_{DD}$$



 


complementary MOS (CMOS)

Most modern logic is this type.


Symmetry between PMOS and NMOS characteristics requires careful selection of $\frac{W}{L}$ ratio.

6.5 Graphical analysis of CMOS inverter

   

- A - $v_i = 0$ PMOS highly ON since $v_{GS} = -5$
NMOS cutoff since $v_{GS} = 0$
- B $v_i > V_{to}$ of the NMOS. but $v_i < \frac{V_{DD}}{2}$
NMOS in saturation region
PMOS in triode region
- C $\rightarrow$ D PMOS load line and NMOS characteristics lie on a line. This is where the circuit switches rapidly from C $\rightarrow$ D.
- E $\frac{V_{DD}}{2} \leq v_i \leq V_{DD} - V_{to}$ PMOS in saturation
NMOS in triode
- F $v_i = V_{DD}$ PMOS cutoff
but NMOS highly ON

propagation delay

 


t_{PHL} - propagation delay $H \rightarrow L$ output transition

t_{PLH} - propagation delay $L \rightarrow H$ output transition

$$t_{PD} = \frac{t_{PHL} + t_{PLH}}{2}$$

can be calculated using the model

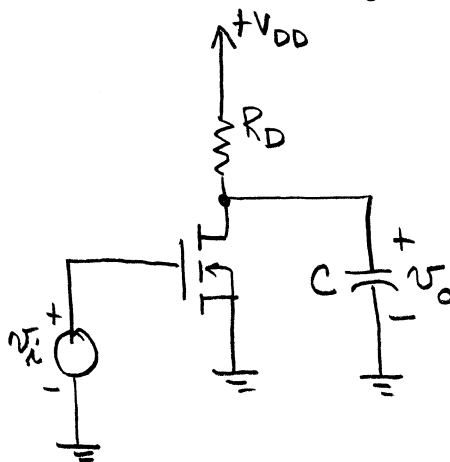

C is the load capacitance
On the order of 1 pf.

This leads into laplace transforms.

CMOS logic gates.

$\text{P-channel ON when } V_G = 0$
 $\text{n-channel ON when } V_G = V_{DD}$

A	B	$A+B$	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

output only high when A and B low so $m1$ & $m2$ are on

$\text{p-channel ON when } V_G = 0$
 $\text{n-channel ON when } V_G = V_{DD}$

A	B	AB	$\overline{AB}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

output high whenever $A \text{ or } B = 0$, but output low ONLY when both A and B are high.